

AMATEUR RADIO 73

First Ham designed IC
Circular Modulation Monitor
Versatile FM Test Set
H Parameters
JFET VFO
1968 Cumulative Index

December 1968

75¢




"HERE'S A REAL WRL SPECIAL—

**—the great GALAXY V Mark 3—
plus two terrific package buys
put together by our Experts!"**



Larry Meyerson
W0W0X

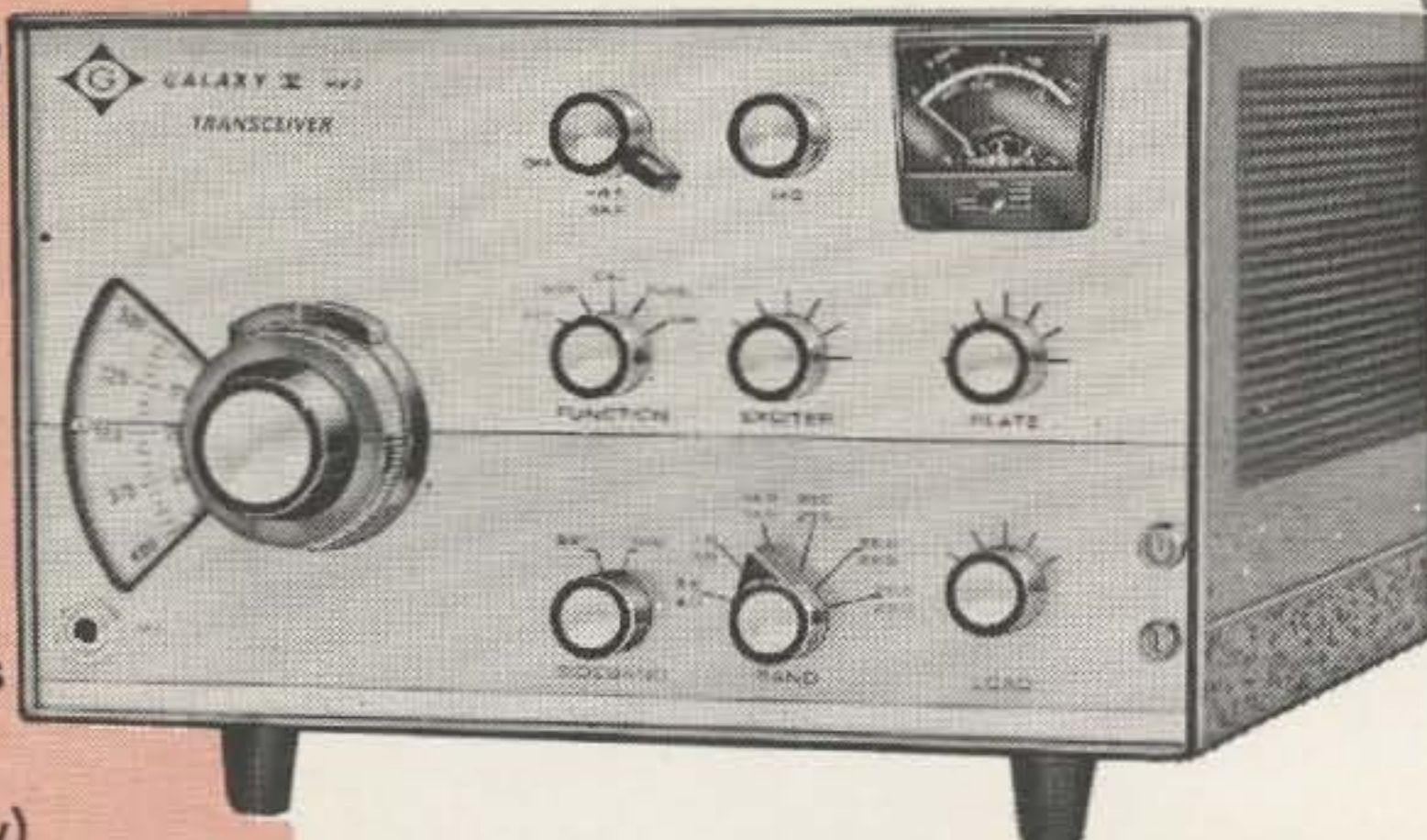**GALAXY V
MARK 3
500 WATT
TRANSCEIVER**
\$420⁰⁰ Less
Accessories




(\$22 Monthly)

- 500 WATTS PEP-SSB
- 475 WATTS CW
- Precision Dial and Vernier Logging Scale
- Solid State VFO
- CW Sidetone
- CW Filter (option)
- CW Break-in (option)

Larry Meyerson of World Radio Laboratories, says —

"Here's a great money-saving deal on one of the finest new transceivers made—or your choice of two great top performance packages put together by WRL's expert staff! You can buy any one of the three, enjoy them NOW and pay for them on World Radio Laboratories easy monthly terms!"

Buy it alone, or —

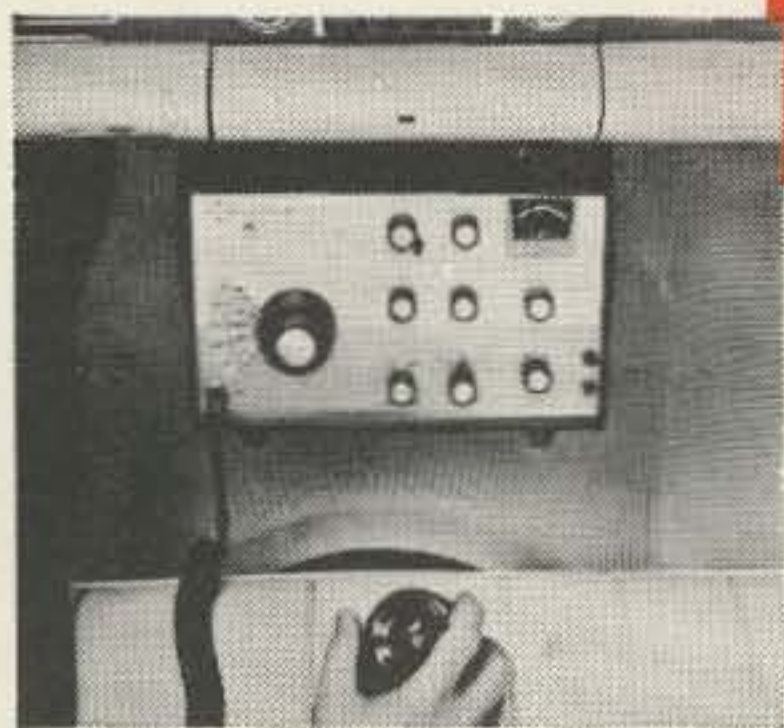

**BUY IT AS A
MOBILE
PACKAGE**


■ A deluxe Mobile Station — includes the new G1000DC mobile supply, New-Tronics "Hustler" antenna system, bumper mount, mini-mobile speaker, all plugs and cables.

\$637⁰⁰

ORDER
ZZMA66

(\$28 monthly without trade)

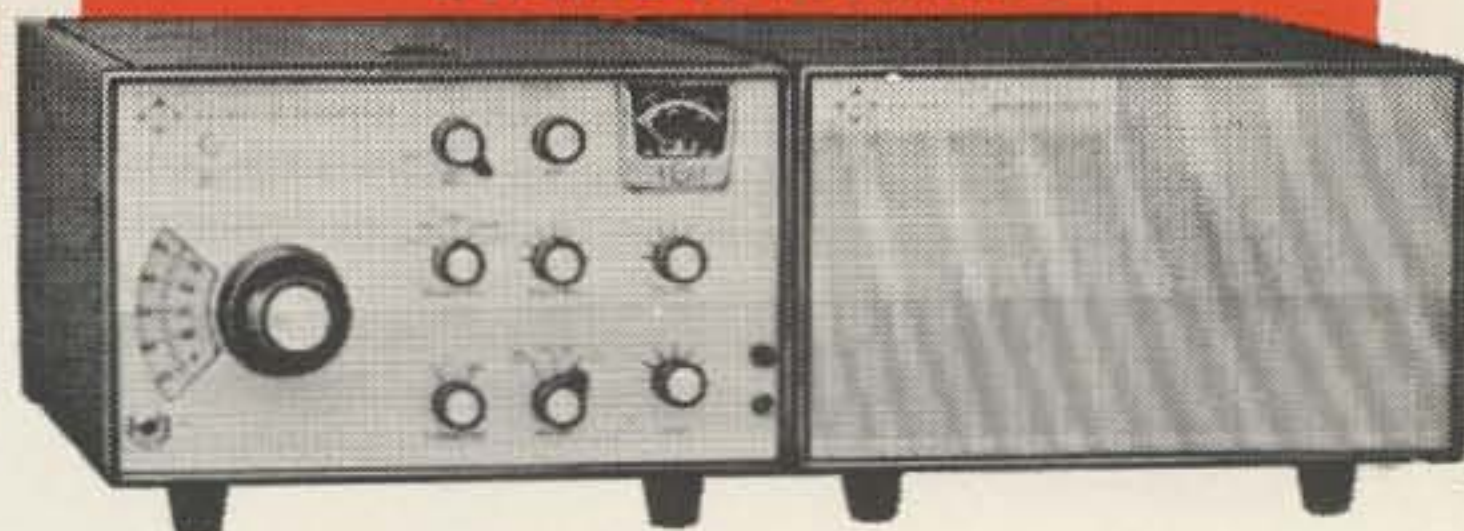**—OR, BUY IT AS A FIXED
STATION PACKAGE**



■ Deluxe Fixed Station package includes Galaxy V Mark 3 Transceiver, 500 watt AC supply, Speaker Console, WRL SB44 dynamic PTT/VOX microphone, Hy-Gain 5BDQ all band doublet antenna, 100 ft. RG8/U coax cable, all cables and plugs.

Order No. ZZMA67

(\$28 monthly without trades)

\$615⁰⁰

plus
\$50⁰⁰ Bonus!

That's right! Take \$50 discount off the two package prices shown — if no trades are involved in your purchase!

Use this Handy
Quick-Mail Coupon
to Order —

WORLD RADIO LABORATORIES

3415 West Broadway 73-P36 • Council Bluffs, Iowa Zip 51501

Please ship the following

- GALAXY V Mark 3 Transceiver
- GALAXY Mobile Package
- GALAXY Fixed Station Package
- Enclosed is my Money Order
- Check
- Charge it
- FREE WRL 1968 Catalog

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

73 MAGAZINE

December 1968
Vol. XLVII No. 12

STAFF

Kayla Bloom W1EMV
Editor

Wayne Green W2NSD/1
Publisher

Jim Ashe W1EZT
Tech. Editor

William Beatty
Advertising Manager

Cover Photo: A collection of current Transceivers you might like to have Santa bring this year.

Editorial Statement: Any errors found in this magazine are put there deliberately. We try to publish something for everyone and some people merely read the magazine to find errors.

Contents

6	Using the First Ham Integrated Circuit Includes several useful circuits	W6DNS
12	Mouse Tunnels Hiding the wiring	K6HKB
14	Circular Modulation Monitor A new Scope	WA9IGU
16	The Mini-Square Square Wave in miniature	WB6BIH
18	Add On FM Test Set Simple to complex in easy stages	K9STH
20	The Elusive H Parameter Not so elusive now.	WB6BIH
24	Zero Temperature Coefficient VFO Sure stability	W6WQC
28	75 Meter DSB Rig A step in the right direction	W3KBM
36	A Novice FET Converter A good building project for the Novice.	K6DBQ
40	Transceiver Review Photos and information about the transceivers now available for Christmas.	Staff
46	30 Watt Transistor Transmitter All Transistorized!	W5PAG
52	Care and Feeding of a Ham Club Part VI Do something interesting	W5NQQ
56	Getting Your Higher Class License Part IX—More on transmitters	Staff
72	Christmas Gifts for Hams Gifts under \$25	Staff
82	Three Black Boxes What constitutes a station	W5EHC
84	Facsimile and the Radio Amateur What is facsimile, and how to do it.	K6GKX
86	Why SSB? Required reading . . . how SSB is different	K3PUR
92	Limitations on Antenna Reciprocity The answer to one way skip?	WA4UZM
98	Index to Articles appearing in 73 in 1968 Cumulative index . . . Where to find it.	Staff

Departments


Editorial Liberties	3	Propagation	106
de W2NSD/1	4	Caveat Emptor	107
Index to Advertisers	112		

73 Magazine is published by 73, Inc., Peterborough, N.H. 03458. Subscription rate: \$12.00 for Three years, \$6.00 for one year. Second Class Postage paid at Peterborough, New Hampshire, and at additional mailing offices. Printed at Pontiac, Illinois, U.S. Entire contents copyright 1968 by 73, Inc. Postmasters, please send form 3579 to 73 Magazine, Peterborough, New Hampshire 03458.

JUST OFF THE PRESS!

NEW 1969

**WRL
Electronics
Equipment
CATALOG**

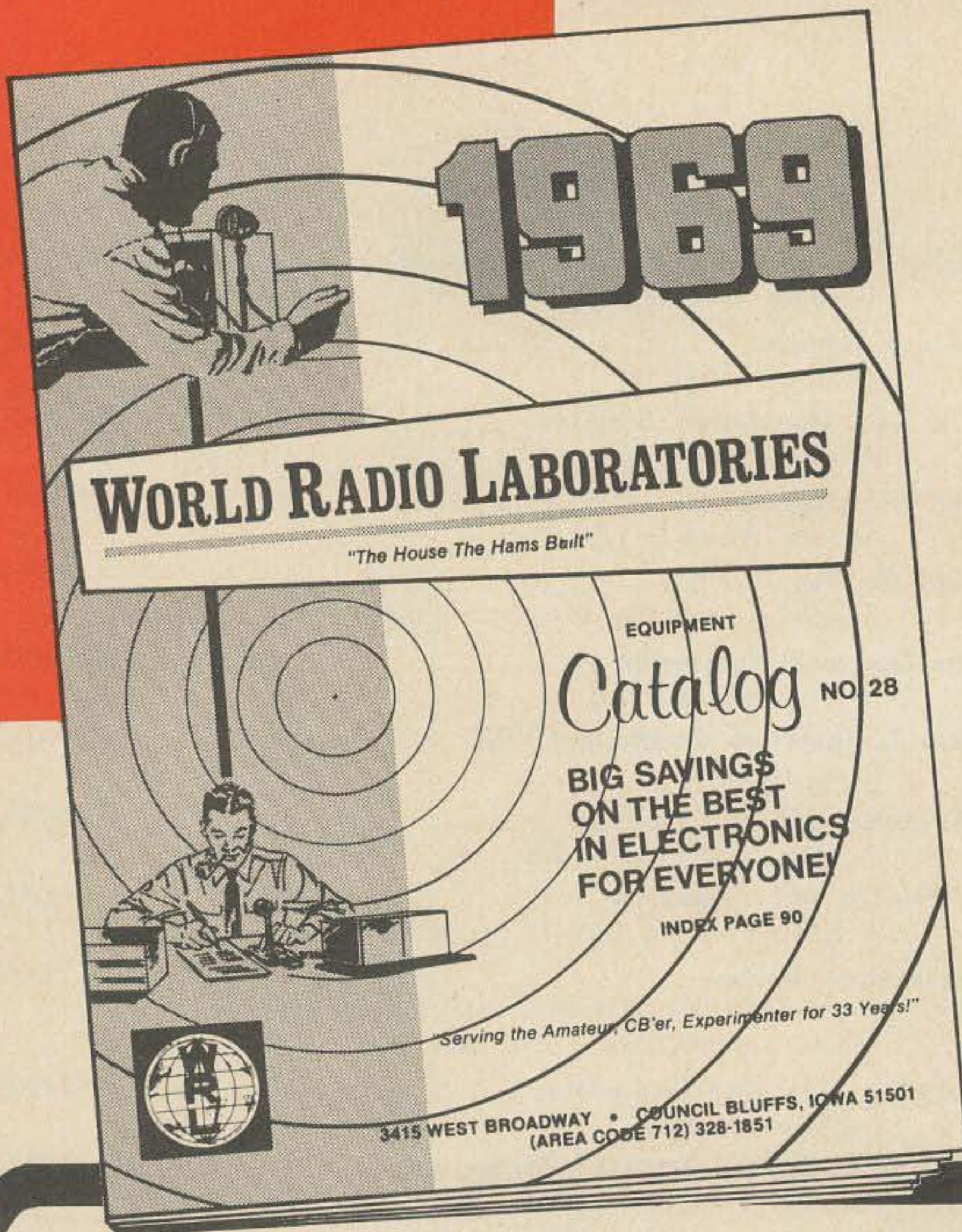

Brand New! World Radio Laboratories' exciting 1969 Catalog. Filled with amazing buys in electronic equipment including dozens of new and exclusive items you can't buy anywhere else!

92 pages — filled with the most complete inventory of Hi-Fi, Radios, Tape Recorders, CB equipment, Ham gear, Electronic equipment, Parts and tools...at real money saving prices.

LATEST...Most Up-to-Date Selection of the Best in Electronics!

- Special Package Buys on name brand Amateur, CB and Hi-Fi equipment — selected by WRL Experts!
- Amateur Gear
- Citizens Band Equipment
- Stereo Hi-Fi
- Electronics & Hobby Kits
- Tape Recorders and Tape
- Walkie-Talkies
- Shortwave Receivers
- Phonographs
- Speakers
- Record Changers
- FM/AM & VHF Radios
- Intercoms
- PA Equipment
- Test Equipment
- Antennas
- Tubes and Transistors
- Automotive Electronics
- Tools & Hardware
- Books
- Headphones
- Microphones
- Wire and Cable
- Parts and Batteries

And, you can buy anything in the Catalog on our easy monthly credit plan!

FREE!

JUST MAIL IN THIS COUPON —

WORLD RADIO LABORATORIES

3415 West Broadway
Council Bluffs, Iowa 51501

73—n36

Gentlemen:

Please send me your Free 1969 Catalog.

Name _____

Address _____

City _____ State _____ Zip _____

Editorial Liberties

With this issue, I complete one year as editor of 73. It has been a very full year for me, and therefore has gone quickly.

Having given some serious thought to amateur radio from what might be considered a commercial view, I am becoming more and more impressed with facts. The 'magic' quality of ham radio simply doesn't exist any longer. Our image has changed, and certainly the role of ham radio has changed in the past years.

We (and I'm speaking of amateurs in general) developed the communications industry. "We" created the firsts in radio technology. Gradually, the ones with foresight began manufacturing radio equipment. They developed a better product than most of us could produce in the dim, dark, dank, dismal, buggy basement to which we were confined by the dictates of our spouses. And . . . we bought their products.

We are often confronted by the term "Appliance Operator," used in a derogatory manner. Do we sneer at the housewife with her push button electric stove, her refrigerator, her modern zig-zag sewing machine. We use these appliances as they were designed to be used. We take advantage of the industry's ability to make a machine which will fill our needs.

Taking a look at other hobby magazines, does a photography magazine tell us how to build a camera? Does the sport car magazine tell us how to build an automobile? Do they tell the flyer how to build an airplane? The answer is, of course, no. They tell us how to *use* the equipment we have bought from a commercially organized company which produces the product we want.

Why is it that amateur radio must take the stand that if you don't build, you aren't really a ham. I firmly believe each ham should understand how his equipment works and be able to do maintenance. But I don't believe many of us could build a modern transceiver which would stack up to any of the commercial equipment available today.

Some hams get their kicks from building. Some read construction articles (even though they don't plan to build) the way others read Playboy. They complain that 73 doesn't have enough construction articles. Believe me, good construction articles are few and

far between. With few exceptions, there isn't much new being built. I suspect, and hope, that ICs are going to spark a whole new era in building, but predictions are dangerous. Where does all this leave four magazines, which are, because of public opinion, devoted to construction? QST has no problem. They are blessed? with a large technical staff who can come up with a construction project. The other three have to fight for the good authors and resort to bribery to try to get their articles. Some you win, some you lose. I will continue to work to get the best people in the field to contribute construction articles as often as possible.

However, the appliance operator should not be looked upon with disdain. Having run the gamut of building and refining until our equipment has reached a point of sophistication which we cannot reproduce in the ham shack, isn't it time we learned to use it to its best advantage. Having built equipment which is designed for communication, shouldn't we learn the art of communicating? Listening to some of the idiotic stuff which goes on, I think we have a long way to go.

If what I hear from members of the industry is true, we may well have to begin building again. Going back to *Callbook* figures, they say we have roughly 290,000 hams in the U.S. By the time we eliminate the duplicates (those holding more than one call, or with expired calls remaining in print) and those who are inactive, we can cut that figure in half. When we eliminate the Novice (don't get mad kids) who doesn't spend much money on gear, we wind up with perhaps 100,000 potential buyers of amateur radio equipment. This is a generous estimate.

The manufacturer of a sophisticated transceiver has an initial investment of perhaps a half million dollars in the design of the equipment before it can actually go into production. The average ham buys a new rig about once in 5 years. So the total market, divided between all the manufacturers, is about 20,000 rigs per year. At an average expenditure of \$1,000 per happy ham, divided between eight major manufacturers, the whole operation borders on charity. You may think, when you spend \$500 on a new piece of equipment, that someone is getting

turn to page 91

de W2NSD/1

This UFO business is beginning to come out in the open a bit more and it is almost respectable to talk about them in many circles. It is interesting that there does not seem to be one single scientist who has carefully investigated the subject without becoming convinced that not only do the UFO's exist, but that they are extraterrestrial. If you have any friends who are still skeptical about UFO's you might suggest that they spend 6¢ and write to their Congressman and ask him to send them a copy of the House of Representatives Symposium on Unidentified Flying Objects, a Hearing before the Committee on Science and Astronautics on July 29, 1968.

The report should leave little room for disbelief in UFOs. Dr. James Harder, Associate Professor at UC Berkeley, says this: "Over the past 20 years a vast amount of evidence has been accumulating that bears on the existence of UFOs. Most of this is little known to the general public or to most scientists. But on the basis of the data and ordinary rules of evidence, as would be applied in the civil or criminal courts, the physical reality of UFOs has been proved beyond a reasonable doubt. With some effort we can accept this on an intellectual level, but find a difficulty in accepting it on an emotional level, in such a way that the facts give a feeling of reality. In this respect we might recall the attitude many of us have toward our own deaths: We accept the facts intellectually, but find it difficult to accept them emotionally." Dr. Harder suggests that the first thing that should be done toward further serious investigations of the UFO's is the establishment of an early-warning network. Since UFOs are frequently seen in the same area on succeeding nights he suggests that research teams set up immediately after a sighting with all of the instruments they can muster. He suggests that the Air Force provide transportation for the teams and their gear.

Dr. Baker of UCLA explained to the Symposium why most tracking radar is adjusted to ignore UFOs and why little is seen of them on our early-warning radars. He suggested changes in the radar systems which

would permit them to sense UFO's and not just throw them out because they don't follow the missile trajectory pattern that the radars are set to watch for. It seems that there are hundreds of uncorrelated targets monthly which are not investigated at all because they are obviously not missiles.


It is interesting that UFOs are seen primarily by people who have not hitherto been believers in UFOs . . . though there is no record of anyone remaining a disbeliever after the experience. Of course only a very small percentage of the people who have seen them actually report their sighting. A recent poll indicates that about 5,000,000 people in the U.S. have seen the UFOs so far, while there have been only about 12,000 filed reports.

Are UFOs spotted on radars? Yes, time after time . . . from land and air radars. Are they ever seen by large groups of people or are they almost always seen by isolated individuals? Frequently by groups and now and then by large groups. Three were seen flying across the airport at Longview, Washington during an Air Show, each from a different direction, about fifteen minutes apart. All three were seen by over 150 gawkers at the show when they were pointed out by the P.A. system announcer. All were seen clearly. Many airline pilots have seen them up fairly close, though few report them any more due to the jibes they get from other pilots and the company.

The hope of the scientists who gathered for the Congressional Symposium was that the "curtain of laughter" could be raised so that serious scientists could study UFOs and observers could more freely report on sightings. They also hope that a world-wide communications network can be established and that automated and instrument teams be set up to provide more information on UFOs.

Stanton Friedman, a physicist with Westinghouse Astronuclear Laboratory takes to task the few remaining critics of UFO reports such as Menzel and Klass saying, "I feel that these gentlemen have made strong attempts to make the data fit their hypotheses rather than trying to do the much

(Turn to page 70)

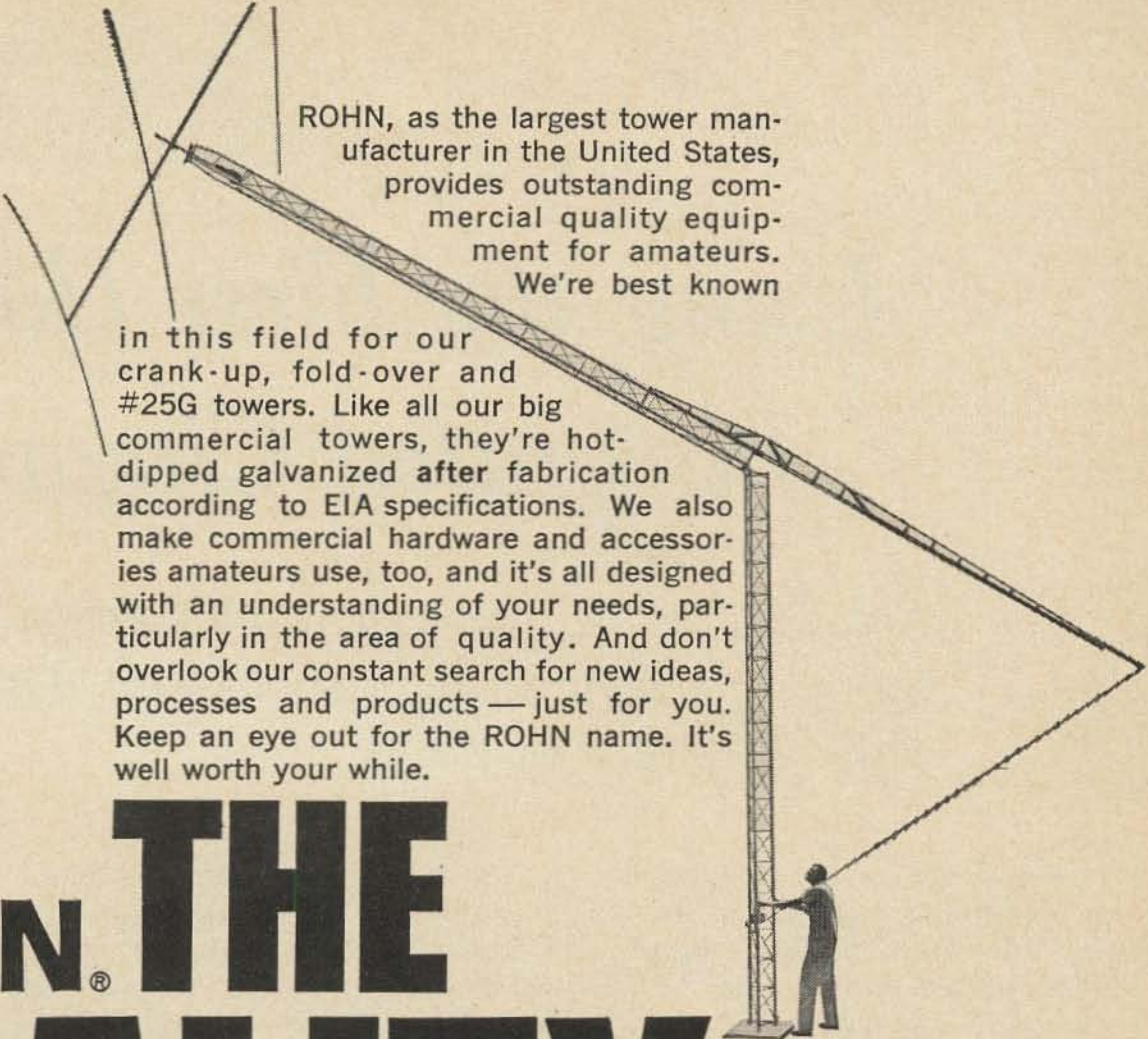

ROHN, as the largest tower manufacturer in the United States, provides outstanding commercial quality equipment for amateurs. We're best known

in this field for our crank-up, fold-over and #25G towers. Like all our big commercial towers, they're hot-dipped galvanized after fabrication according to EIA specifications. We also make commercial hardware and accessories amateurs use, too, and it's all designed with an understanding of your needs, particularly in the area of quality. And don't overlook our constant search for new ideas, processes and products — just for you. Keep an eye out for the ROHN name. It's well worth your while.

ROHN® THE QUALITY PEOPLE

Home Office — Factory
P.O. Box 2000, Peoria, Ill., U.S.A. 61601
Phone 309-637-8416 TWX 309-697-1488


ROHN®

Systems Office —
Box 877, Richardson, Texas 75080
Phone 214-AD1-3481

Western Office
310 Quincy Street, Reno, Nevada 89502
Phone 702-322-9300

Eastern Office
P.O. Box 2101
Hanover, Mass. 02339
Phone 617-826-2511

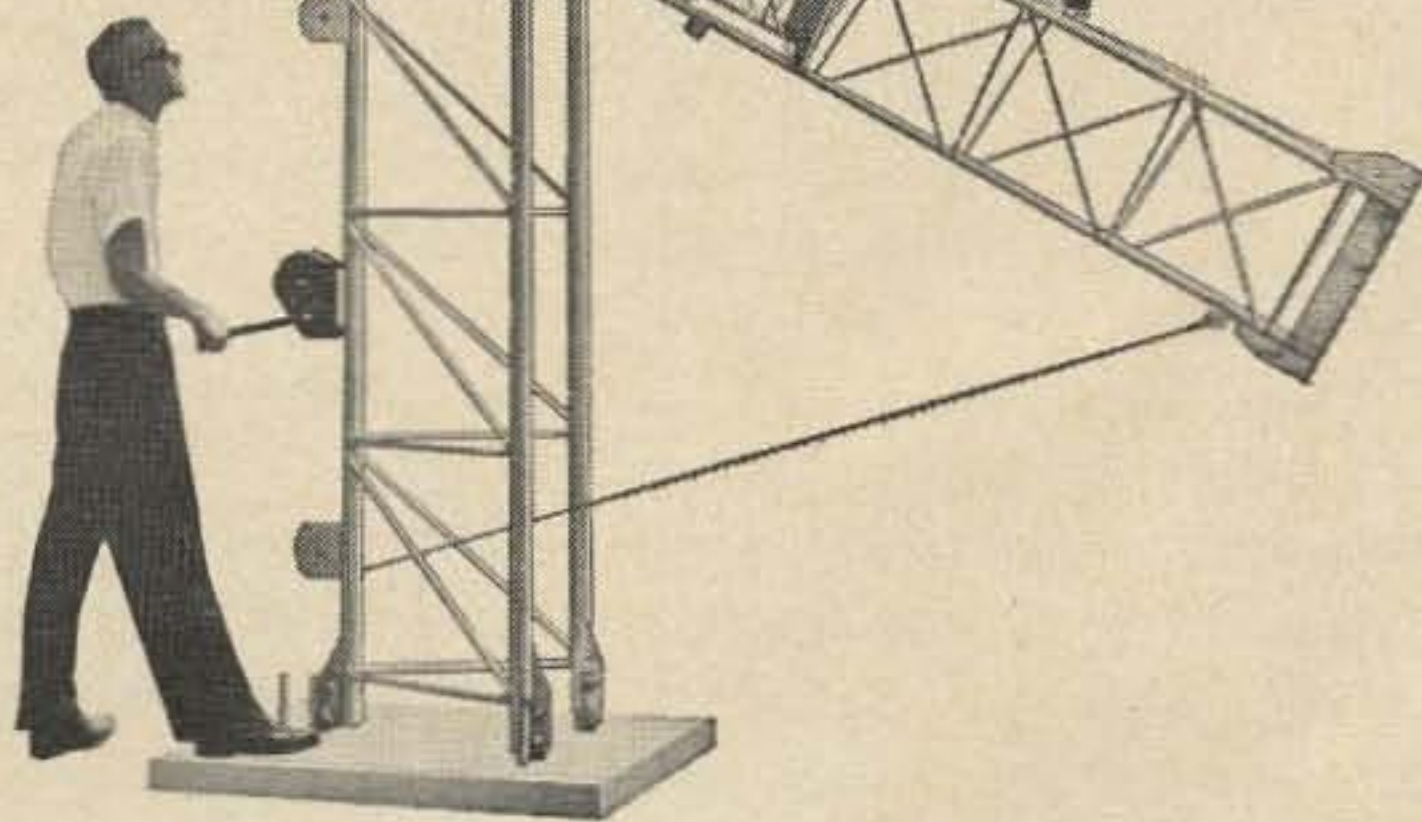Southern Office
P.O. Box 6537, Birmingham, Ala. 35217
Phone 205-841-1789



Robert A. Hirschfeld, W6DNS
Section Head, Communication Microcircuits
National Semiconductor Corporation
2950 San Ysidro Way
Santa Clara, Calif. 95051

Using the First Ham Integrated Circuit

Squelch, VOX, Speech Compression, and more, in a new Integrated Circuit designed with the Ham in mind!

For several years, 73 has been a leader in publishing articles on ham applications for currently available digital and analog IC's. Until now, however, no IC's had been produced specifically for two-way-radio use. At least one IC manufacturer, recognizing the need for such circuits, in the potentially large commercial, military, and amateur market, is now aiming a major development effort toward communication "subsystems on a chip", and it is expected that other manufacturers will follow. Besides the direct benefits of improved performance, decreased size, and lower component costs, which will reach amateur radio through commercially-built rigs, the new specialized chips will enable even the casual homebrew artist to construct sophisticated, complex equipment he might previously have considered beyond his reach.

The first Communication IC now available is the National Semiconductor LM270 Audio AGC/Squelch Amplifier. It is basically an operational amplifier, whose gain is controlled by a dc voltage, plus a built-in sensitive squelch threshold detector. The ten pin circuit replaces entire sections of today's transmitters, receivers, or transceivers, and makes speech compression, VOX, receiver squelch, and other functions practical in even the simplest homebrew rigs. While the chip contains 36 junction devices (transistors and diodes), and 20 resistors, it is size, rather than complexity which de-

termines an IC's cost, so that the LM270, which is about the size of a single medium power transistor, is already cost competitive with the less complex discrete-component circuits it replaces. As volume commercial use of the circuit increases, the circuit is likely to be available at even more attractive prices.

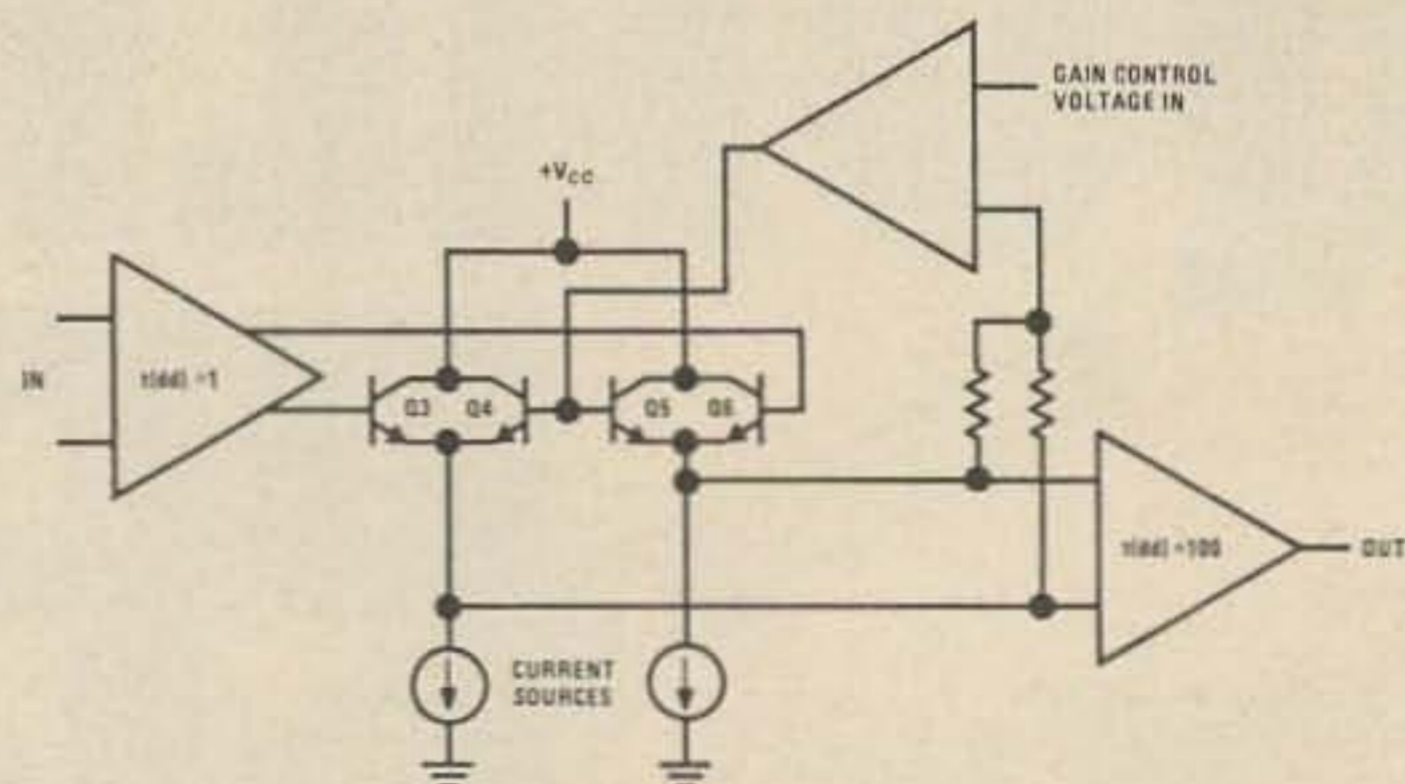


Fig. 1. Block diagram of variable gain amplifier.

Inside the can

The LM270 consists of several separate functions, designed to work together in a self-contained system, to produce control voltages for external use, or to respond to applied control signals. Heart of the circuit is a balanced series-shunt variable attenuator, formed by the four transistors in Fig. 1, which allows a large gain control range, with low distortion (for inputs less than 100 mV p-p), and which can be directly coupled to other parts of the system, eliminating the transformer or capacitor

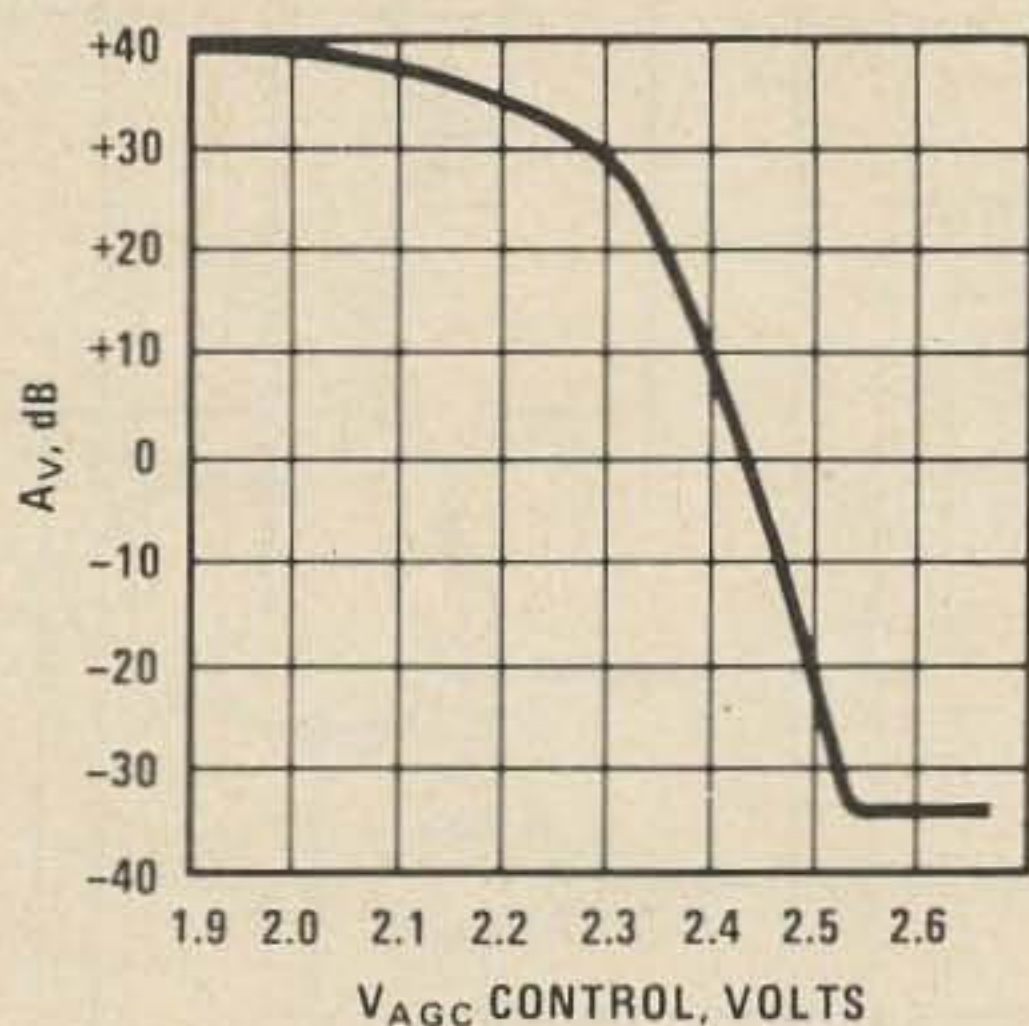


Fig. 2. Typical voltage gain vs. control voltage applied at pin 4.

coupling necessary with all other variable arrangements. From a twelve volt supply, the gain vs. control voltage relationship is a smooth curve, as in Fig. 2, which gives a constant gain of +40 db for control voltages between zero and +2 volts, and is effectively "shut off" above +2.6 volts.

A separate subsystem within the LM270 is the squelch detector, Fig. 3. Using the same input differential amplifier as the variable gain circuit, the high gain peak detector formed by Q20, Q36 and Q21 re-

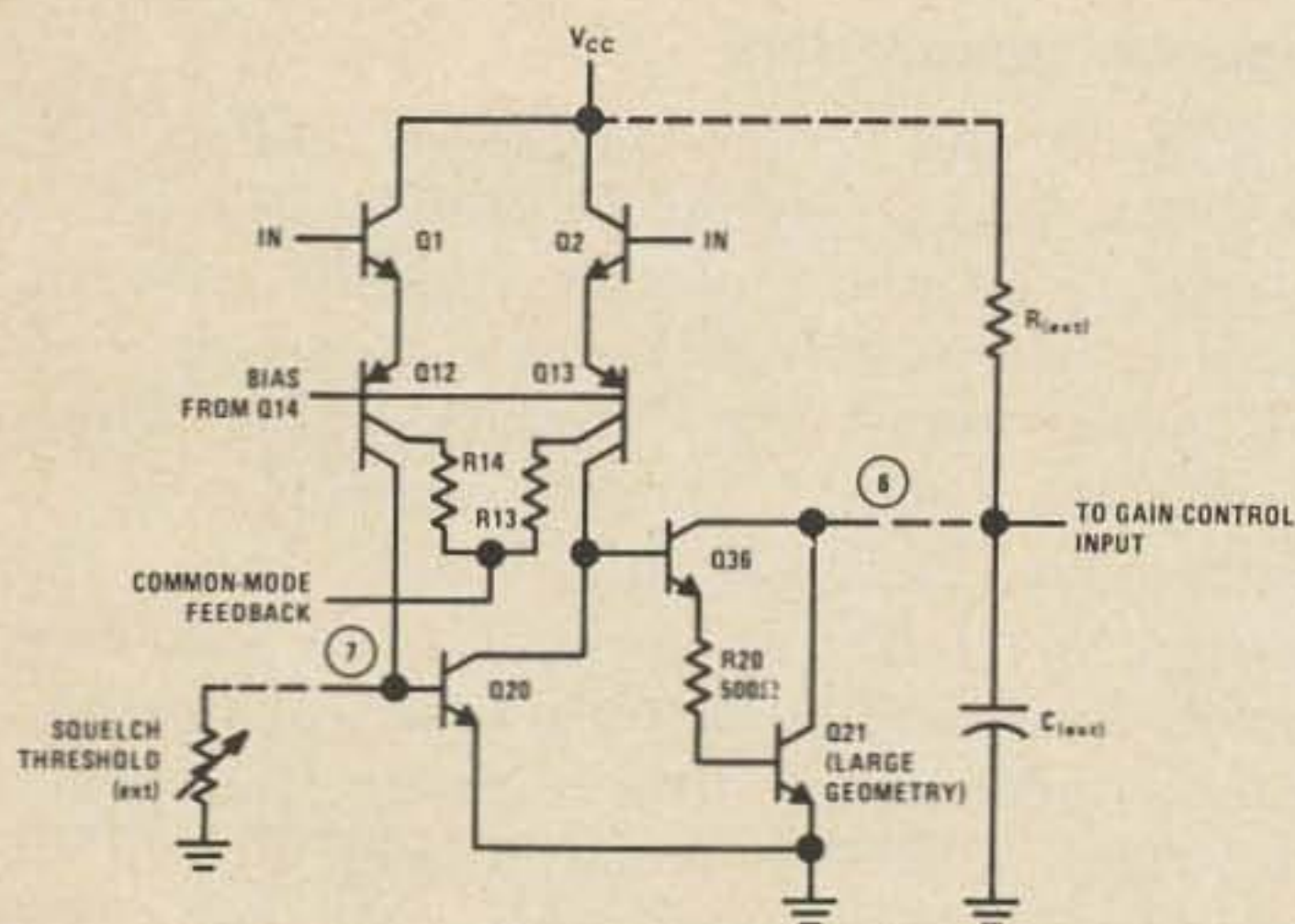


Fig. 3. Differential input circuit and squelch detector.

sponds to very small inputs (as little as a millivolt, depending on setting of the external threshold pot), by rapidly discharging an external capacitor. In the absence of input signal, C(ext) charges above +2.6 V, which, when tied to the gain control input, keeps the output amplifier "off". A momentary input peak above the threshold causes Q21 to rapidly discharge C(ext) below +2 volts, turning the amplifier fully "on". This arrangement gives a fast attack, slow

release squelch, which catches first speech syllables, and waits long enough to avoid "cutting out" between words.

The complete circuit appears in Fig. 4. A detailed explanation of each part, too lengthy for inclusion here, may be found in the references.

Practical ham applications

Before going into specific circuits, a few general remarks are in order. Those familiar with operational amplifiers will easily recognize the LM270 configuration. Differential inputs allow inverting or non-inverting gain, or drive from a "floating" signal source. If single-ended drive is needed, the unused input is simply tied to the same reference voltage as is the actual input. All that is required is that both inputs be at equal dc potential, somewhere between +4.5 volts and the positive supply. Like an "op amp", the LM270's dc output voltage stays at approximately half of the positive supply voltage, for all supplies between +4.5 and +24 volts, so that symmetrical output clipping occurs.

Two identical gain control inputs, pins 3 and 4, are provided, which allows control by two independent sources at the same time, such as simultaneous AGC and squelch. By bypassing pin 2, the gain control inputs become emitter-follower positive peak detectors. The control inputs are protected by 6.5 volt zeners (Q33 and Q34). If the control input is expected to rise above +6.5 volts, a 10K series resistor at that input should be used to prevent excessive dissipation in the zeners.

Remote gain-controlled audio amplifier

A simple application is a preamplifier, Fig. 5, whose gain is manually controlled, noiselessly, by a dc voltage from a remote location, rather than running long, capacitive coax signal lines to and from that location. Pin 4 is bypassed by an external capacitor, to eliminate noise pickup. Since the gain-control curve, Fig. 2, is approximately logarithmic, a linear pot will give a desirable logarithmic audio attenuation characteristic.

For illustration, the second control input is shown connected to an IC logic gate, of the DTL, RTL or TTL varieties now available at low cost. This gate, operating from a five volt supply, can be part of a logic

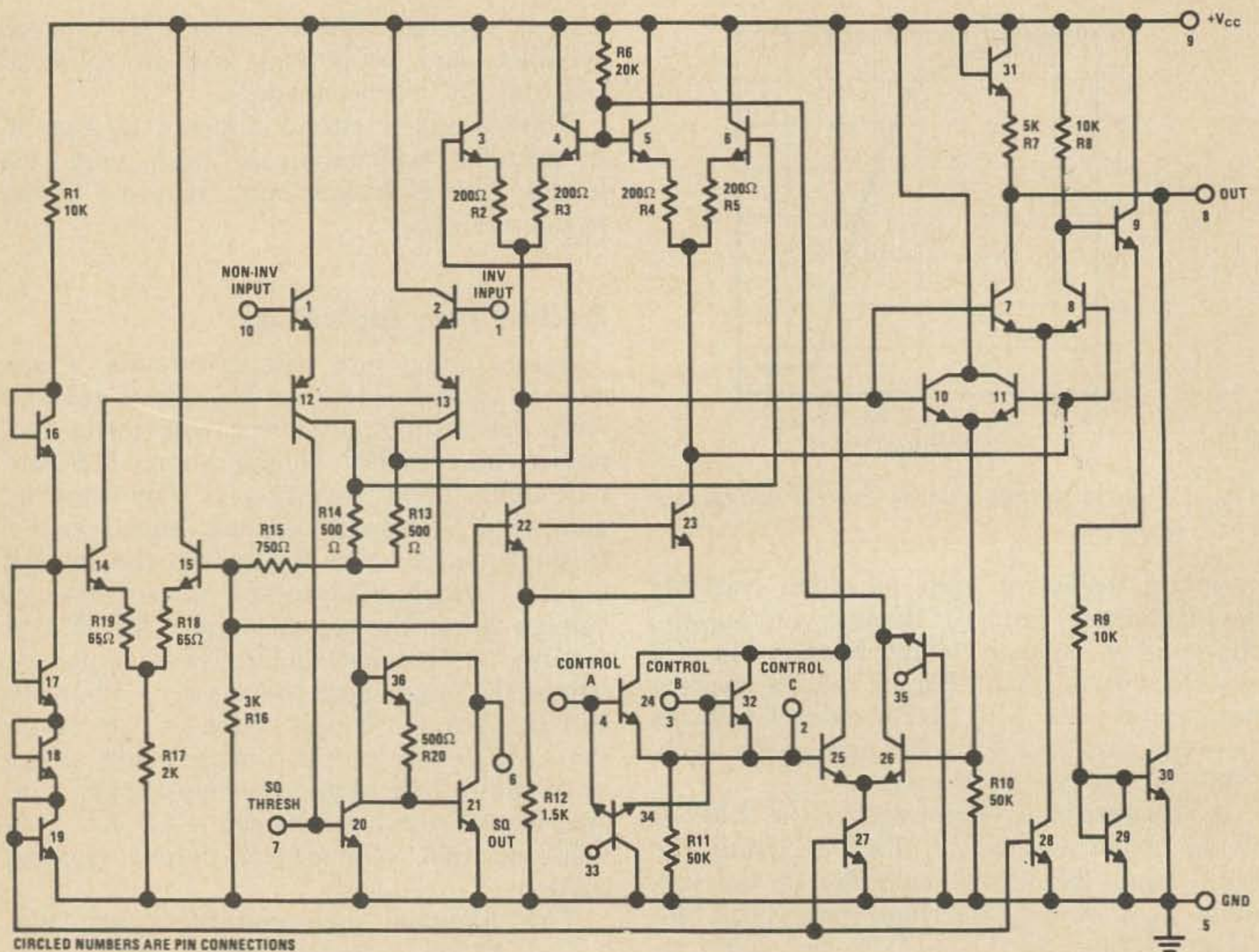


Fig. 4. Complete LM270 Schematic.

arrangement to override the remote control, and shut off the amplifier under present conditions. The resistors and capacitors shown biasing the single-ended input are used to illustrate one way of operating the inputs at a fixed dc voltage; subsequent examples will show simpler schemes.

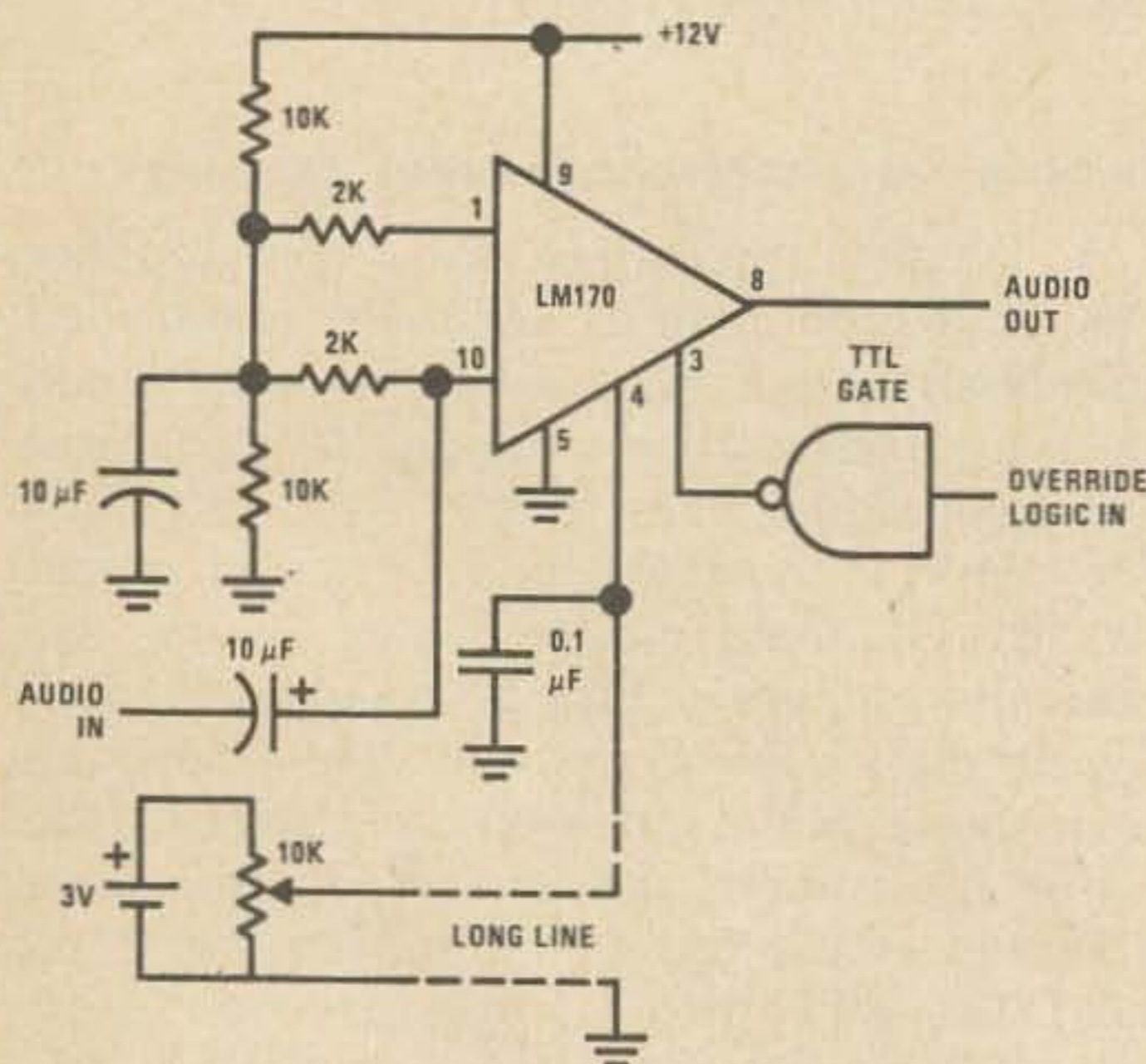


Fig. 5. Remote or digital control amplifier.

Speech compressors

Fig. 6 and 7 are basically audio AGC systems, which respond to peak speech levels above a set threshold by quickly reducing gain to a level which keeps succeeding similar peaks below the threshold. This differs from the usual "speech clipper", as it causes no distortion, but simply keeps the output level at an approximately constant level. In a modulator (any type), such AGC keeps modulation always near, but never in excess of, 100 percent. In Fig. 6, a PNP transistor (almost any type will do) adds enough gain to the control loop to operate over a large range of input levels. In Fig. 7, the additional gain of the receiver or modulator is used for this purpose. Varying load impedances can cause the gain of these stages to vary; taking the control signal from the system's audio output automatically compensates for load variations, in much the same way as an ALC system operates. The scope photo, Fig. 8, shows how the output (vertical axis) remains nearly constant while the input (horizontal axis) varies over a wide range. Note that

both AGC circuits use the internal emitter-follower detectors, and that both inputs are biased from the positive supply through equal resistors, although other biasing works equally well.

Squelch preamplifier with hysteresis

Audio squelch is useful in both receiving and transmitting systems, to cut out background noises. The sensitive circuit of Fig. 9 includes a number of refinements, which make it smooth-acting, and easy on QRM weary ears. The threshold pot at pin 7 can be a front-panel control, to cut in at any desired level. Attack time is on the order of a millisecond for nearly any capacitor value at pin 6, but release time is determined by the external RC time constant. The fixed 100 k resistor may be replaced by a 100 k pot, in series with a 10 k resistor, to give operator-adjusted release time.

Part of the voltage at pin 6 is fed back to the threshold pot; since there is an "on" and an "off" voltage at pin 6, this creates a controlled amount of threshold hysteresis, which greatly enhances the circuit's immunity to rapid fading or erratic speech patterns. A typical threshold control setting

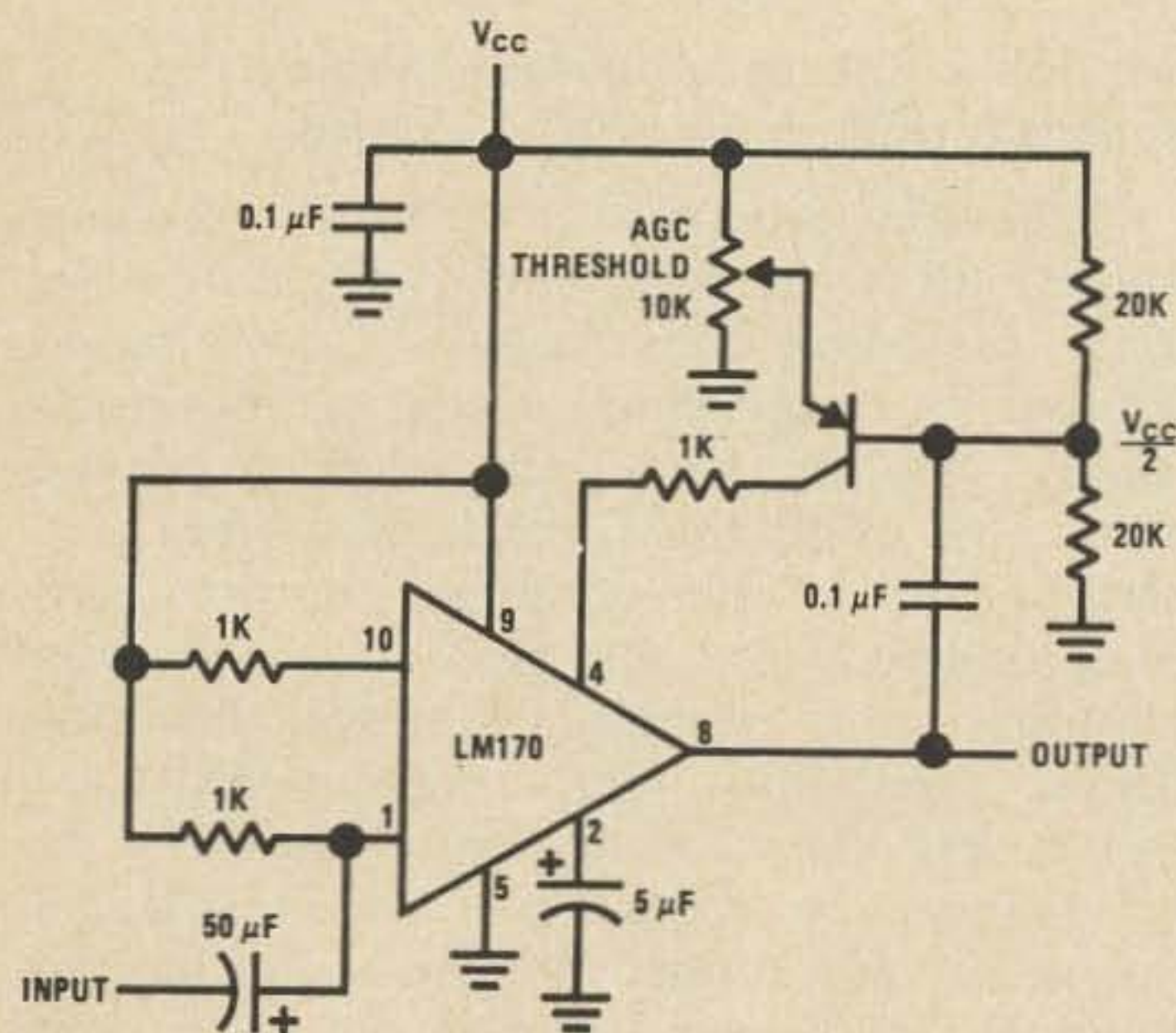


Fig. 6. Speech compressor.

might be one at which amplification cuts in above 20 mV p-p inputs. With the feedback values shown, the input level must drop below 12 mV p-p for a time equal to the RC time constant, before gain is cut off. Shorting across the 200 ohm resistor defeats the hysteresis.

Unlike most squelch systems, which are just switches, the LM270 provides a grad-

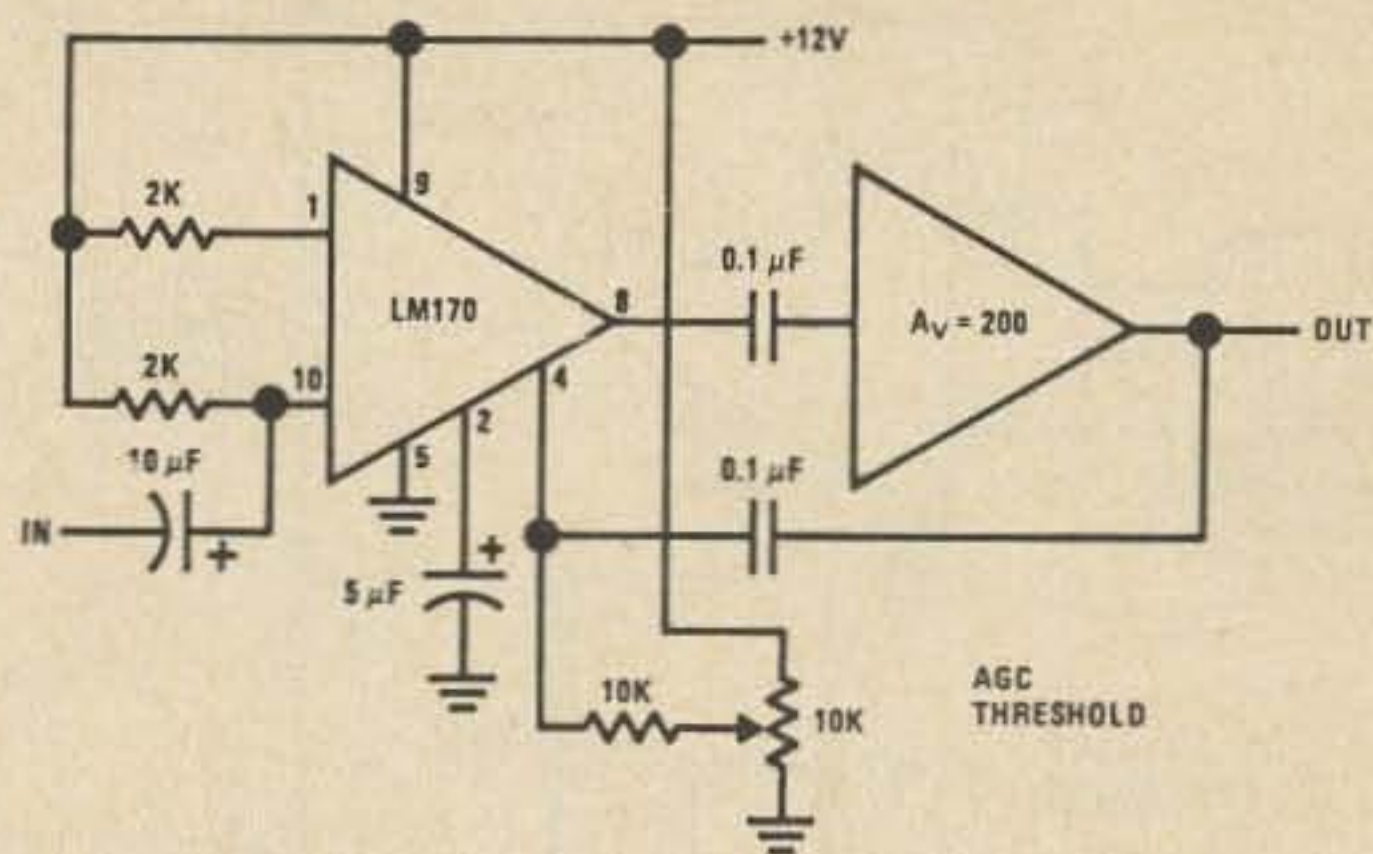


Fig. 7. Speech compressor using subsequent gain for better control.

ual fadeout of background noise, when releasing. This is because the RC combination charges slowly along an exponential curve, and passes through the variable gain region on its way to complete cutoff. Fig. 10 shows the squelch action with a 25 μ F capacitor and 100 k charging resistor. In the upper trace, a constant 1 kHz signal just below the squelch threshold keeps the output, in the lower trace, off. Abruptly increasing the input above the threshold immediately turns the amplifier on. Reducing the input does not turn off the output, but merely reduces it proportionally, during the release period. Finally, after about one second, the output tapers off to zero again.

In this example, another input biasing scheme is illustrated; the LM270 can be driven directly from a high impedance dynamic microphone, such as the Shure 401A, with dc bias for both inputs derived from the positive supply, and no other external components required. In receiver squelch, one of the previously illustrated input arrangements might be used. The high frequency

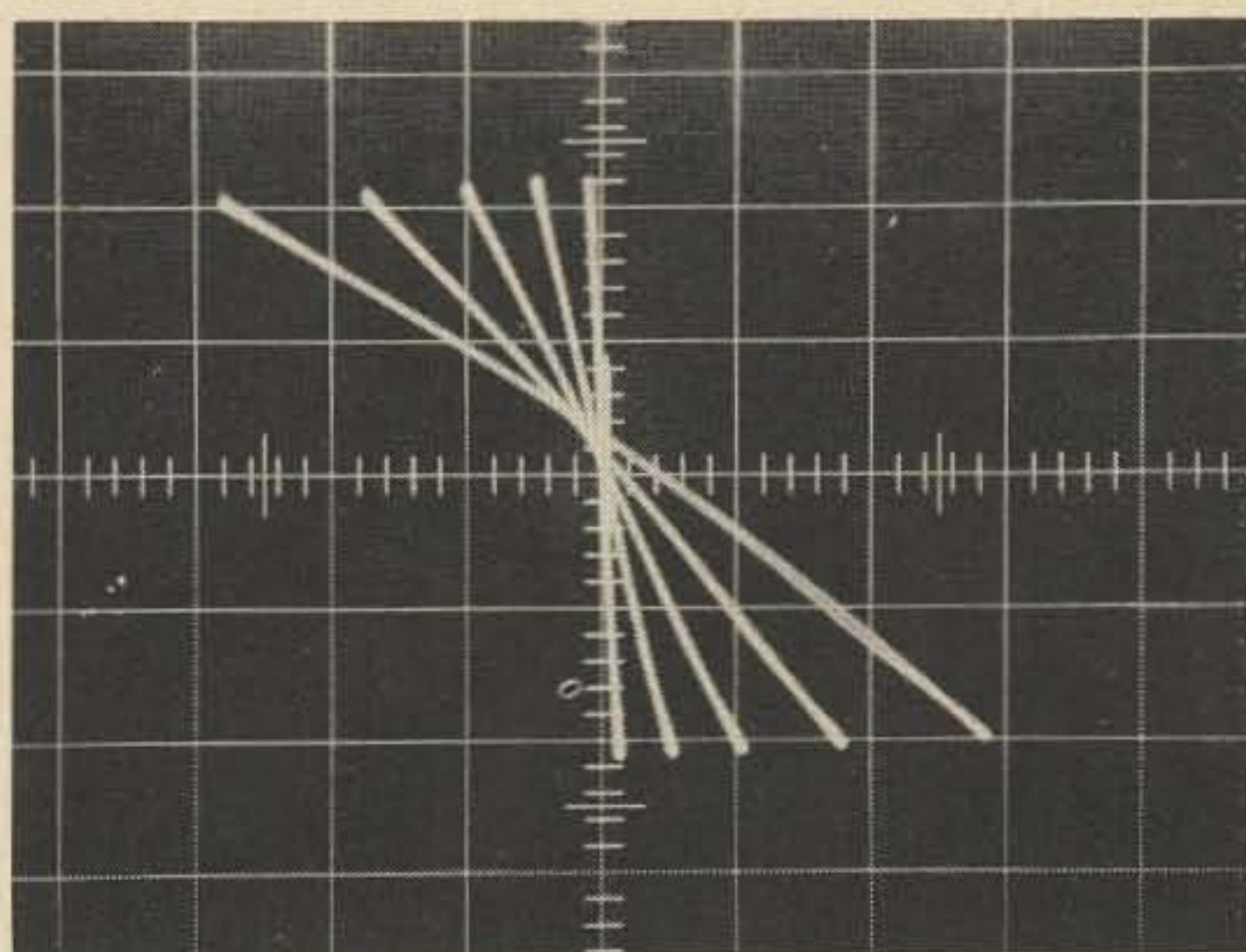


Fig. 8. AGC transfer characteristics, input vs. output, for varying input.

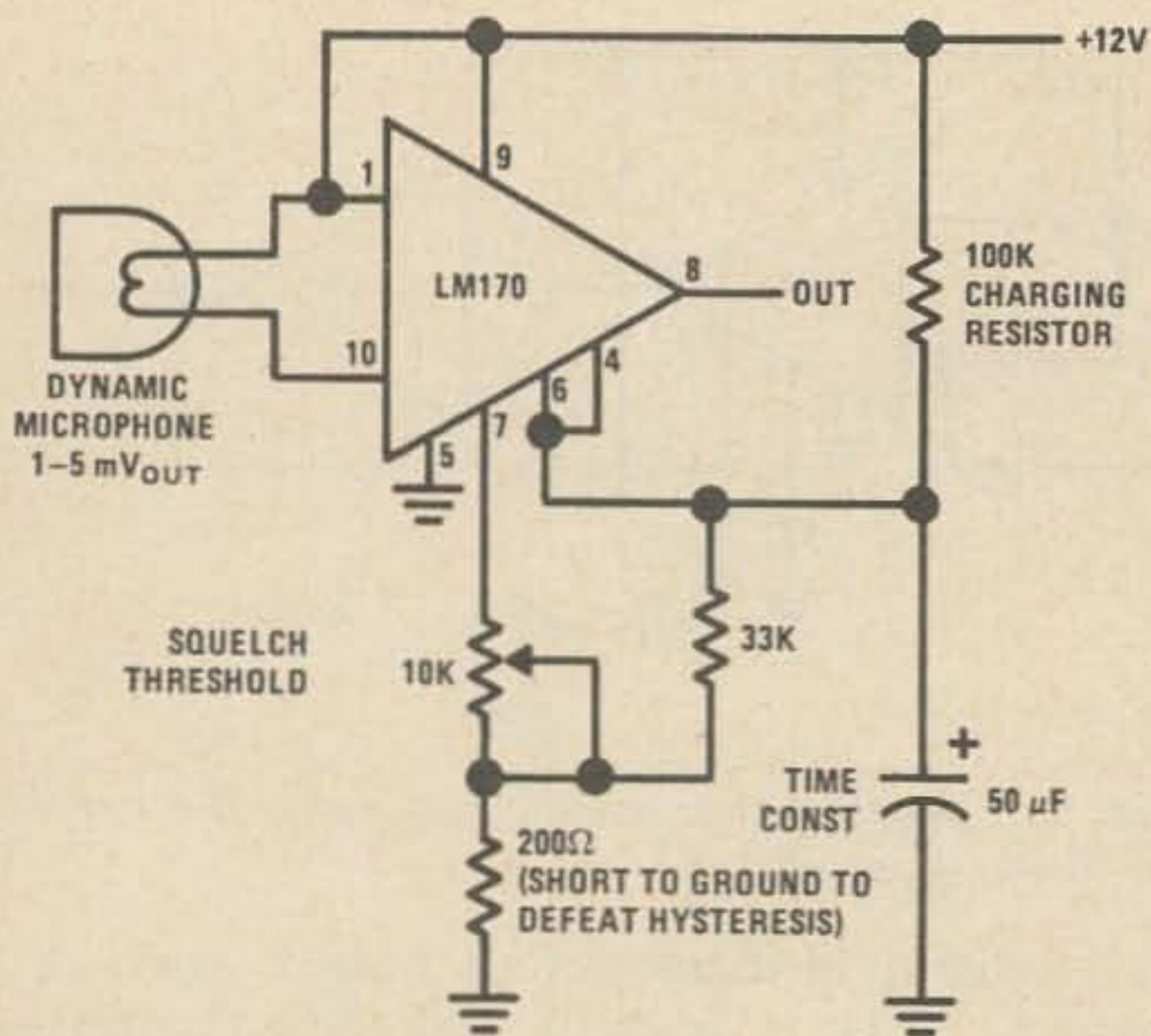


Fig. 9. Squelched preamplifier with hysteresis.

response of the squelch may be rolled off with a $.05\mu\text{F}$ capacitor from pin 7 to ground, to reduce squelch triggering from high frequency noise above the speech spectrum.

A simple VOX mike preamp

Using a small power transistor driving a relay, the LM270 makes a combination VOX and microphone preamp small enough to build into a mobile-type communications mike. With the relay contacts wired across the push-to-talk switch, such a microphone can add VOX to existing transmitters with minimum disturbance of wiring. The basic circuit of Fig. 11 can be improved, as in Fig. 12, by driving one amplifier input from the microphone, and the other from an attenuated part of the receiver's loudspeaker output. (Correct phase must be determined experimentally, by reversing either loudspeaker or microphone leads for best per-

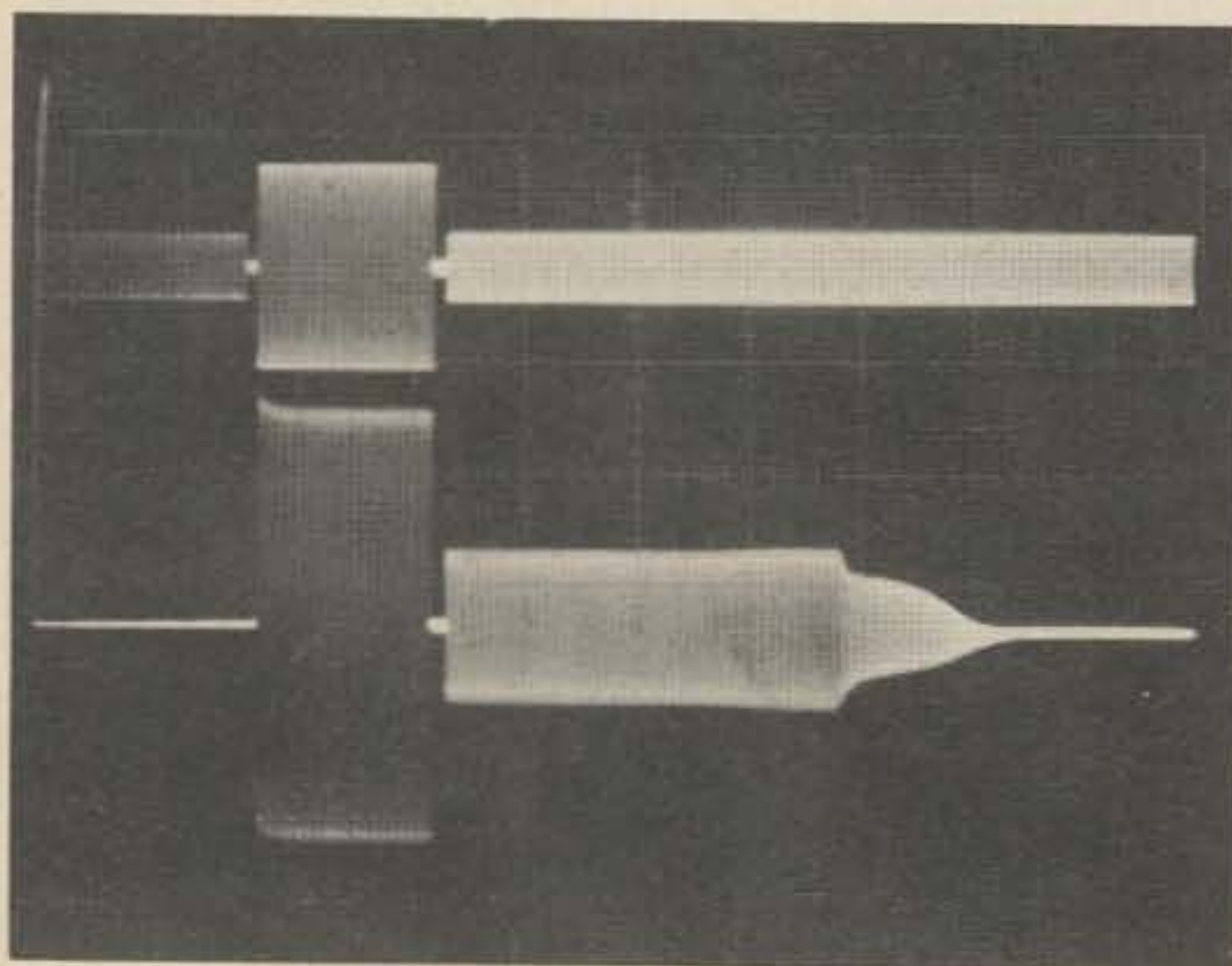


Fig. 10. Fast attack, slow release squelch action.

formance.) This takes advantage of the differential inputs provided on the LM270, to cancel ambient speaker signals reaching the mike (anti-trip VOX). A diode shunts the relay coil to protect the PNP power transistor. Any relay drawing less than 100 mA from a +12 volt supply may be used, small model-airplane types being suited for inclusion inside the mike case. In Figs. 11 and 12, amplifier gain is not cut off by the squelch detector; however, the VOX circuit may combine with any of the preceding applications to give, for example, a preamp containing both VOX and speech compression.

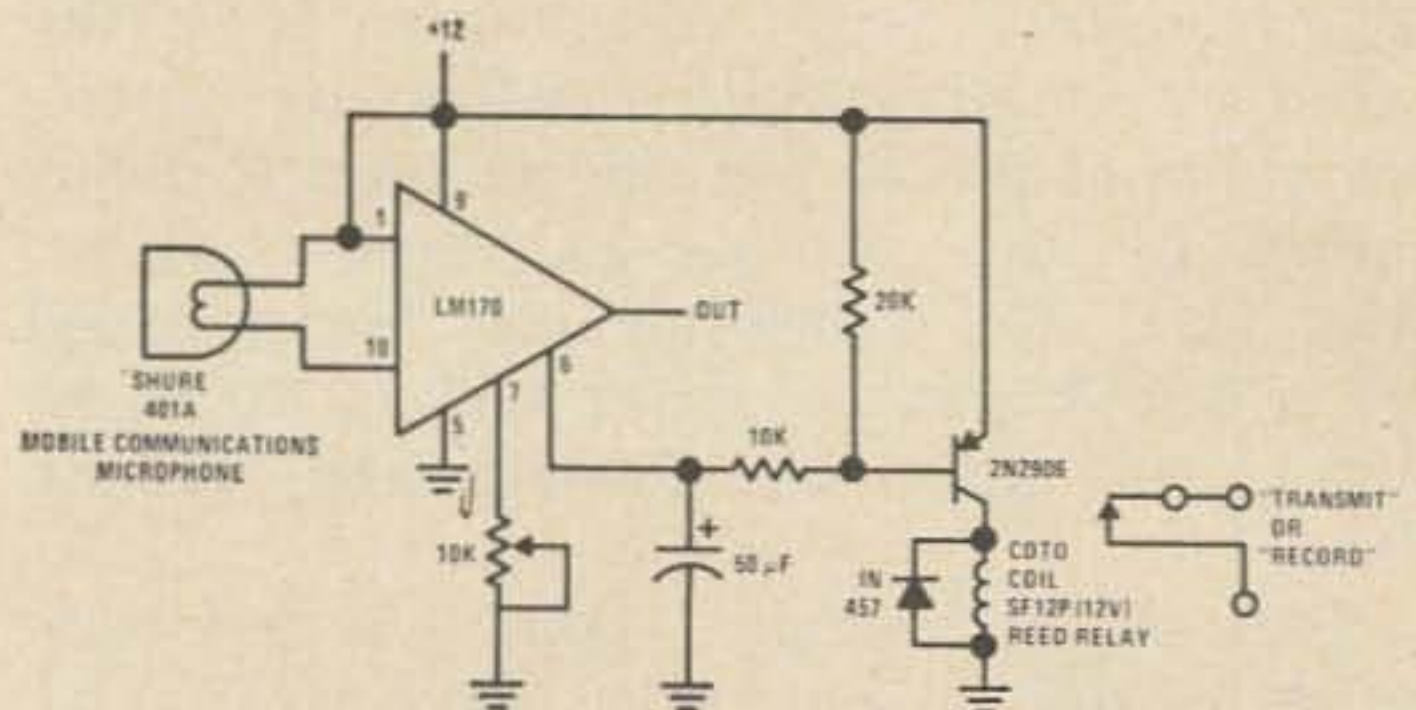


Fig. 11. VOX/mike preamp.

Twin-tee constant amplitude audio oscillator with remote level control

Oscillation occurs in a twin-tee, op-amp type circuit, when total feedback gain equals unity (including filter losses). Conventional methods of regulating oscillator amplitude usually rely on nonlinear loading of the gain stage. With the LM270, however, gain may be set by detecting the output, and using this to force the gain to exactly the minimum value required to sustain low distortion oscillation. The "AGC Oscillator" circuit, Fig. 13, automatically compensates for changes in oscillator load impedance. The exact amplitude at which this action occurs is set by an external pot, and may

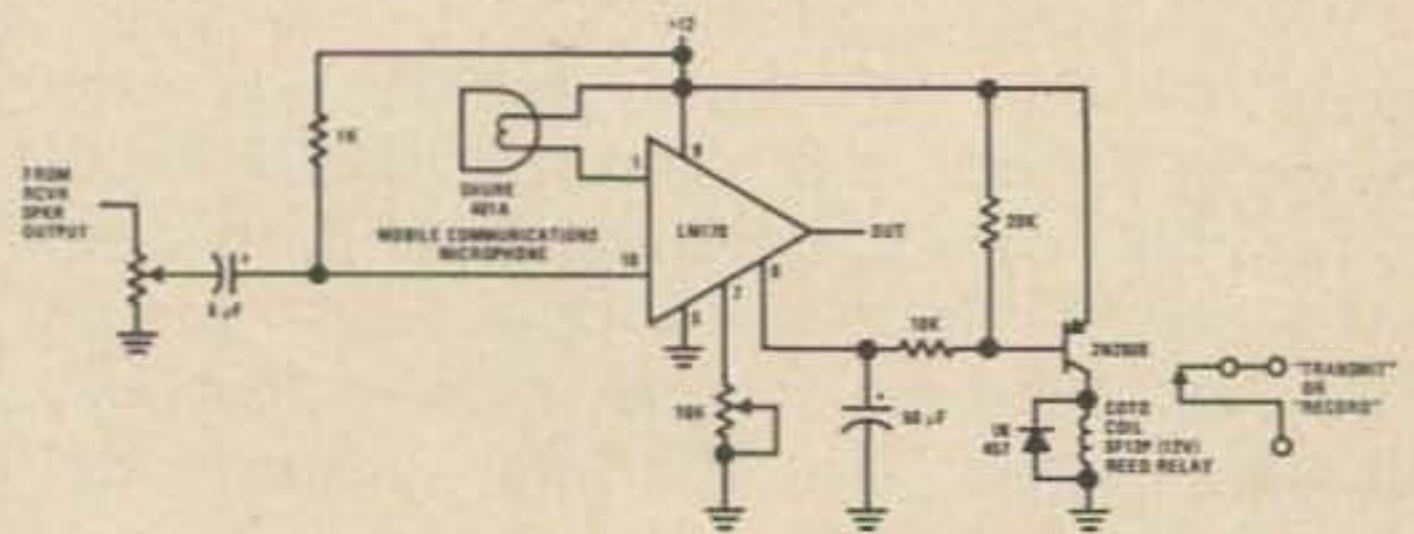


Fig. 12. VOX/mike pre-amp with anti-trip.

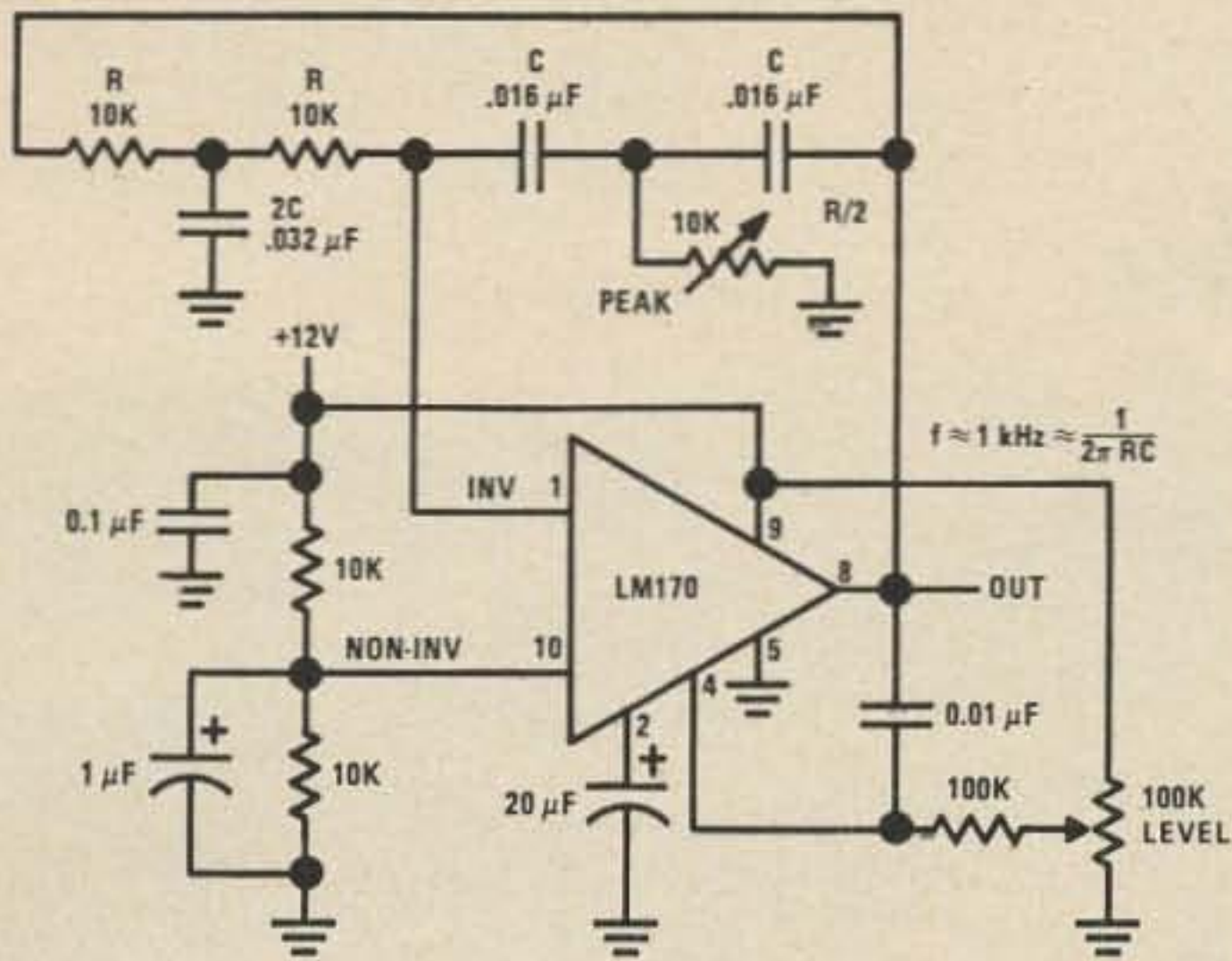


Fig. 13. Twin-Tee constant amplitude audio oscillator.

be set at any value below the maximum undistorted output of the amplifier itself. The "twin-tee" values shown give a 1 kHz output; other frequencies can be calculated from the formula:

$$f = \frac{1}{2\pi RC}$$

A modulated 455 kHz signal generator

An inexpensive, high "Q", 455 kHz ceramic filter can be substituted for the twin-tee feedback network in the preceding example, to make a regulated-output AM *if* alignment generator, Fig. 14. If the AGC threshold voltage, which determines the amplitude of stabilized output, is varied at a slow (audio) rate, the output *rf* amplitude will be forced, by the AGC feedback, to track the audio modulation.

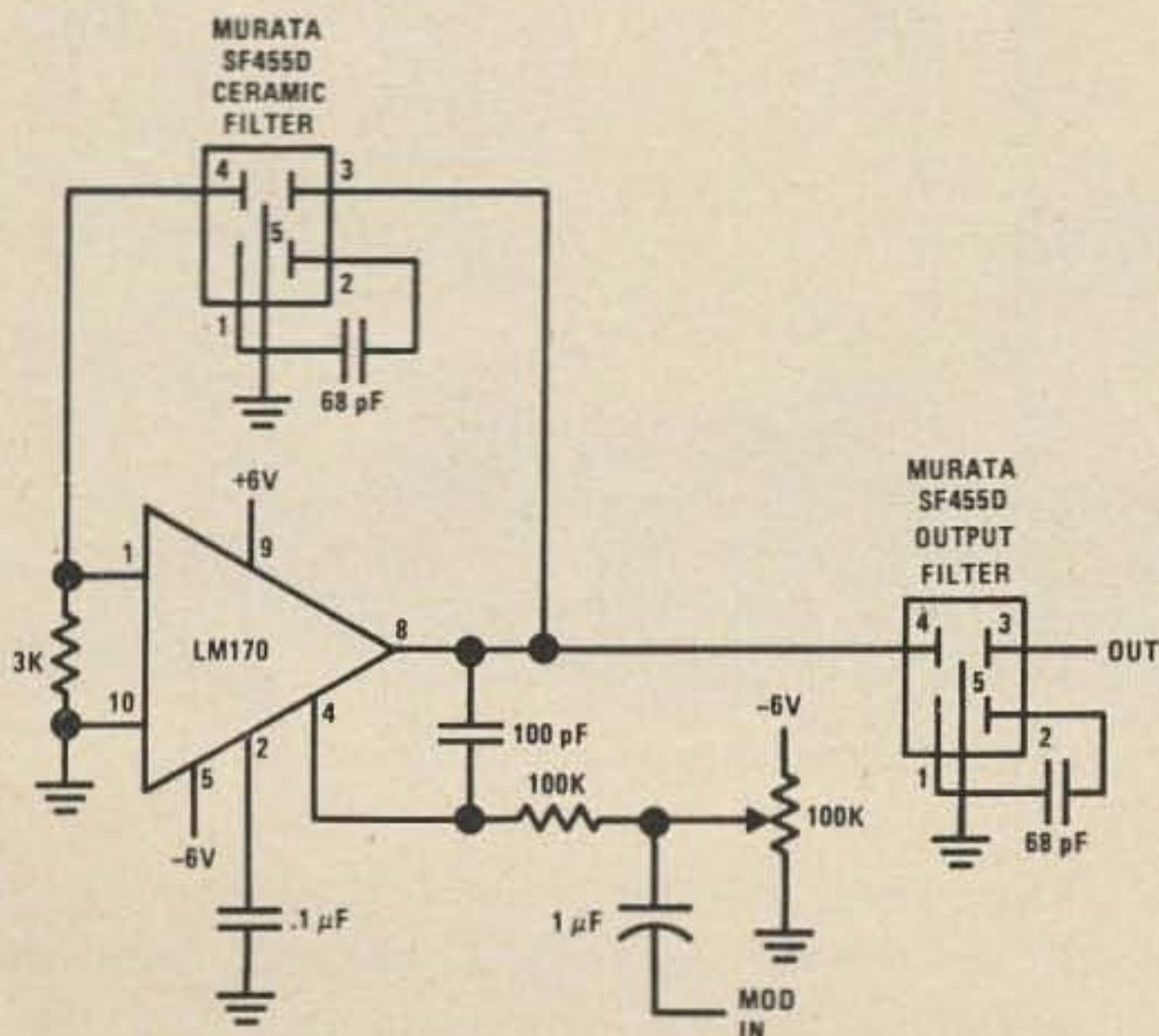


Fig. 14. 455 kHz modulated, regulated output signal generator.


Conclusion

The LM 270 is a very versatile ham IC, which can make your next homebrew rig more advanced than many commercial jobs, with a minimum of the usual headaches. A little thought will reveal many applications, not covered in this article, in speech processing, RTTY, mountaintop repeater control, and others requiring either a variable gain amplifier or a sensitive squelch detector.

Future developments in the communications IC area are going to raise a few more eyebrows; it is expected that nearly all low power level sections of both receivers and transmitters will be built in integrated form in the near future, but these developments must wait for subsequent articles. Meanwhile, whet your appetite with the LM270, the first ham IC. . . . W6DNS

REFERENCES

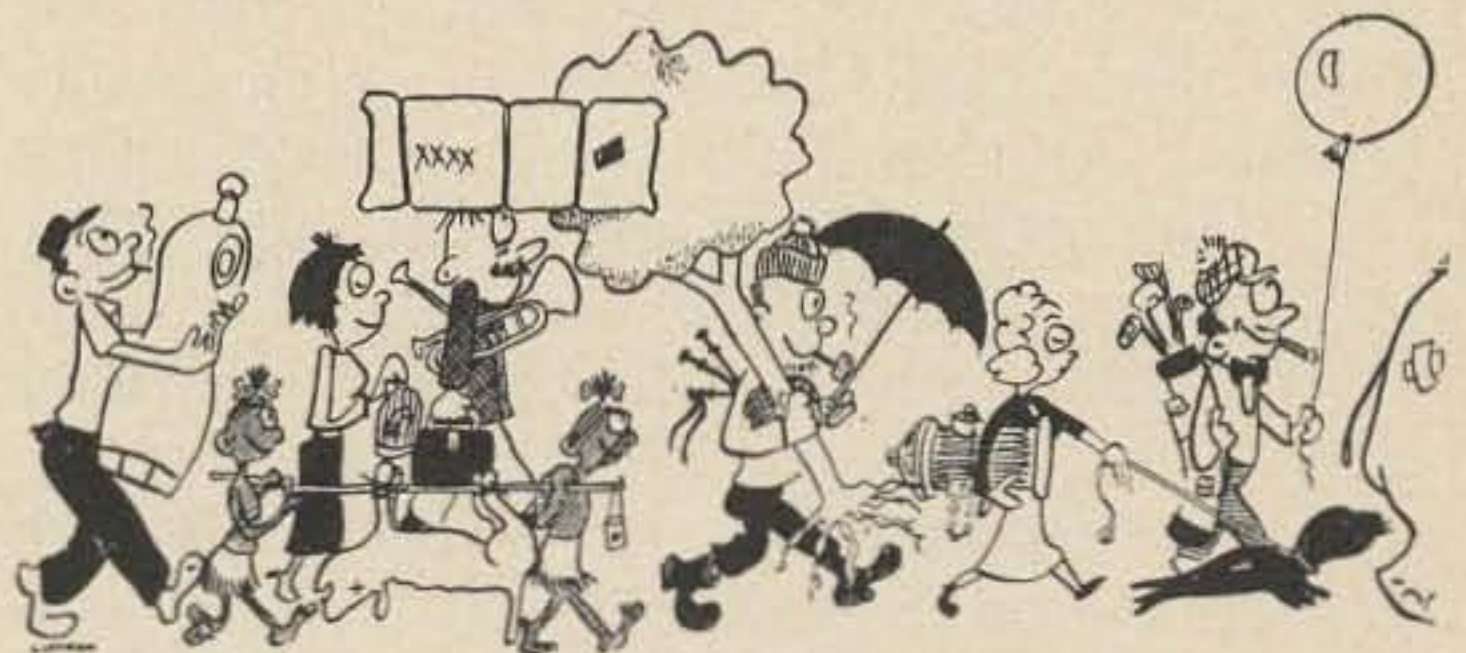1. R. Hirschfeld, "A Unique Monolithic AGC/Squelch Amplifier", Application Note AN-11, National Semiconductor, Santa Clara, Calif. July, 1968
2. R. Hirschfeld, "Linear Integrated Circuits in Communication Systems", WESCON 1968 Proceedings, Session 1, Paper 3
3. "Ceramic Filter Data Sheet", Murata Corp. of America, 160 Broadway, N.Y., N.Y. 10038



**Moving? Please
Let Us Know!**

Compare OUR PRICE, OUR QUALITY
OUR PERFORMANCE

8 OVER 8

Get specifications on other models—harness and accessories.

144 MC . . .	\$36.50
220 MC . . .	\$29.95
432 MC . . .	\$23.95

"J" and "Multifeed"

VHF-UHF BEAMS OF DISTINCTION

- Full band coverage
- No tuning—ever
- Stacked—high gain
- Virtually indestructible
- Exact match insuring low SWR

The Beams Our Customers Recommend To Their Friends
The ultimate in vertically polarized beams, when so oriented—must not in line with elements—the choice of the "FM" boys—everywhere.

GAIN, INC. Dept. 712, Phone (312 568-1973)
27 East 112th Place, Chicago, Ill. 60628

Mouse Tunnels

An Answer to the Rat's Nest


J. A. Carroll K6HKB/1
CMR 1 Box 1438
Westover AFB, Mass. 01022

Most of us get a good-sized collection of cable behind the rig, and sooner or later find reason to cuss the tangle it gets into. About the time my roommate (Fred Wirth, W8DOM) and I couldn't get into certain parts of the room without walking on the wiring, we decided to do something. The objective was to get the wiring out of the way and into a compact form without tying it down permanently and making it hard to rearrange.


Our answer was the "mouse tunnel," a low-cost adaptation of the sheet-metal raceways used in commercial installations. It's a wooden trough with a lid, $2\frac{1}{8}$ " x $3\frac{3}{8}$ " inside, with notches in the front every 6 inches to permit cables to exit where desired.

The photos show most of the construction. After the front board gets its notches, nail a few pieces of scrap wood temporarily to the top edges of the front and back boards to hold them the proper distance apart, so that the joints to the bottom board will hold them that way later on. The two side boards are glued to the bottom, with enough finishing nails to hold them until the glue sets. One every 6 inches is enough. They should be driven below the surface with a nail set, so they won't scratch the floor later.

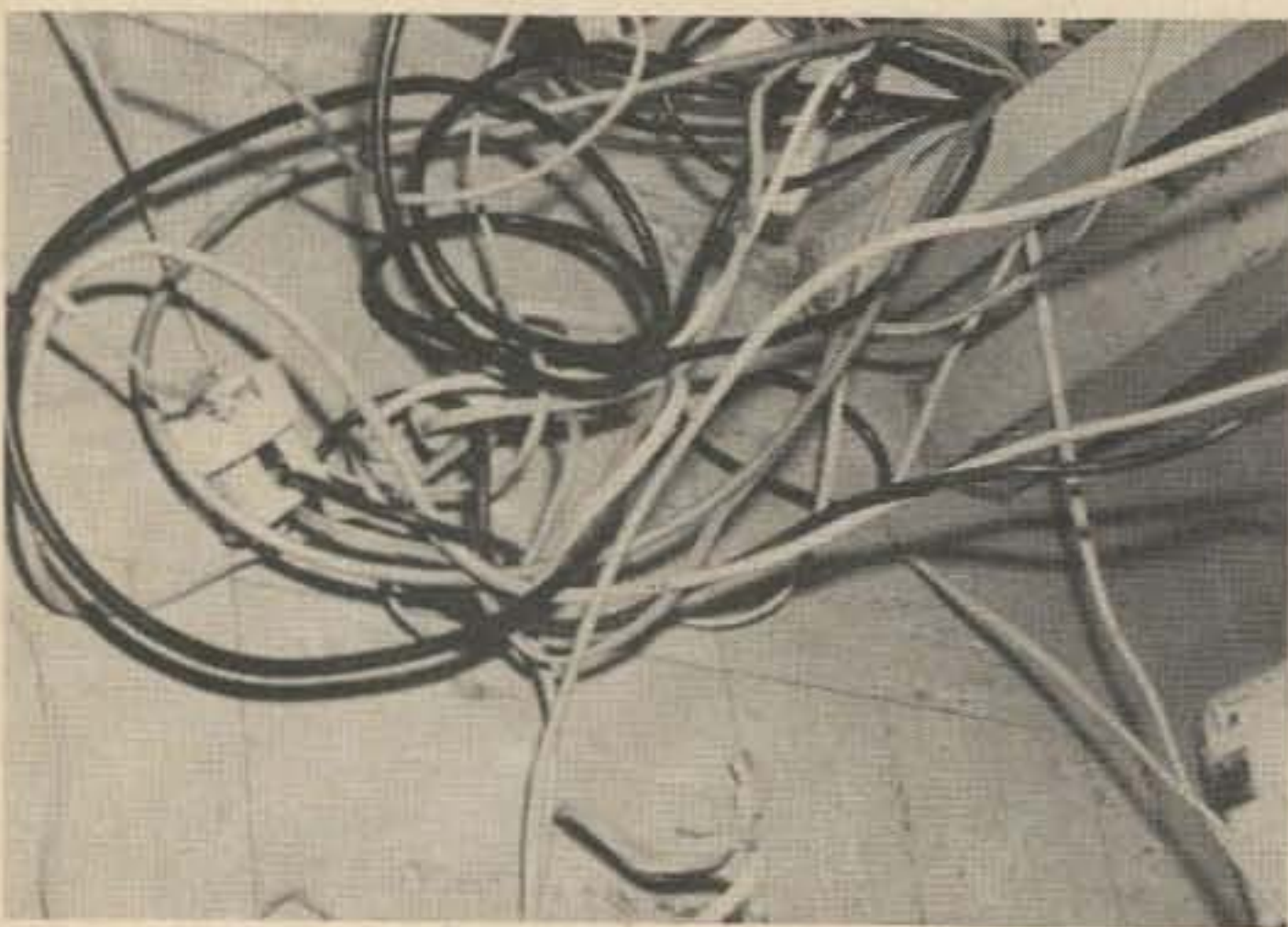One small hinge every 4 feet is enough to keep the lid from sliding off, but a section of any length should have at least two. No other fastenings are needed, because the weight of the lid will hold it closed with



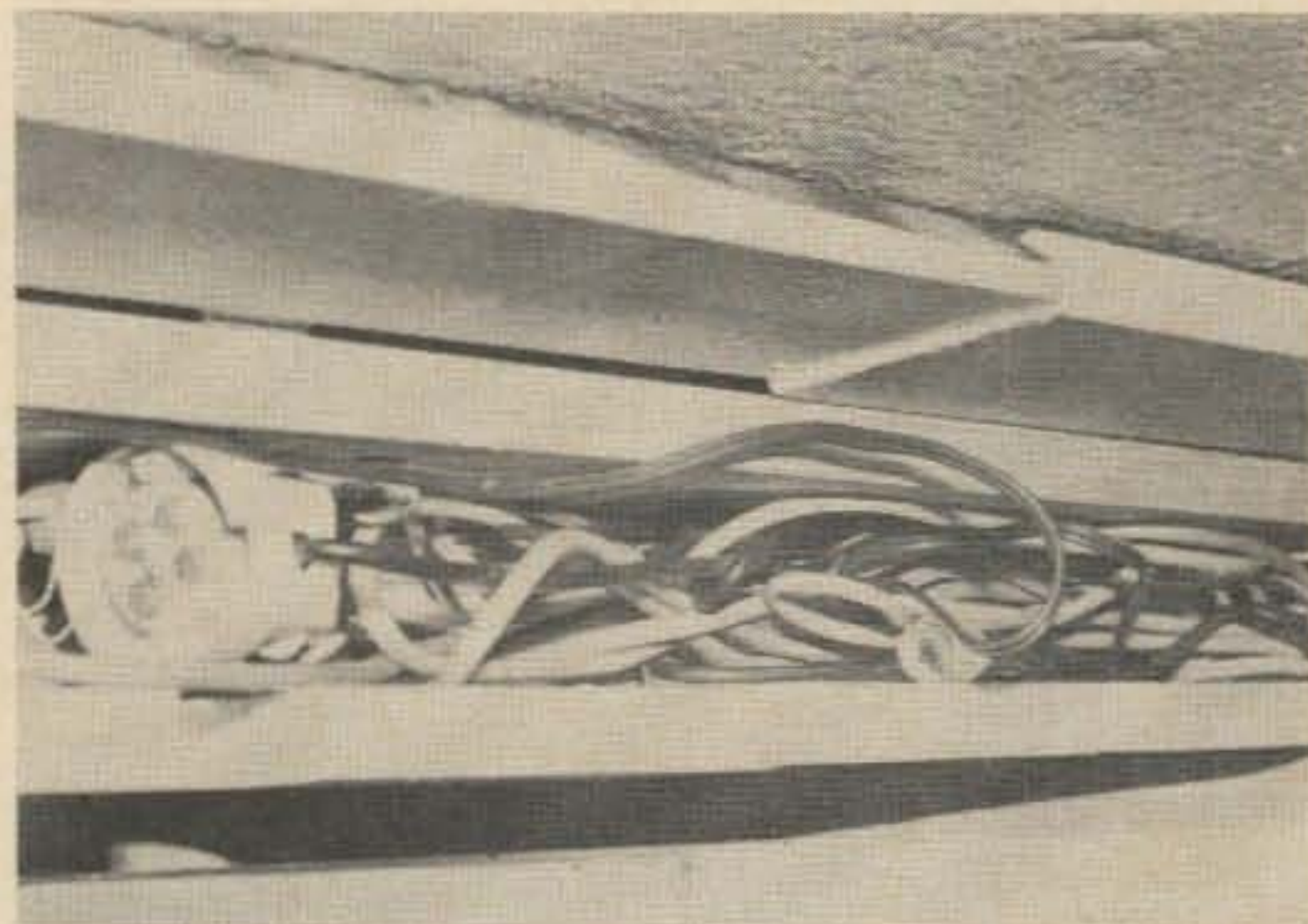Wiring during rearrangement, about the way it looked before installing the raceways




Cables laid in the tunnel

the cables inside.

I built four sections totalling about 20 feet in one evening, and using all new material, spent a little less than \$8.

Installation consisted of laying the tunnels on the floor along two sides of the room, putting the cables inside, and closing the lids. Cables come out the nearest notch to each piece of equipment, and excess is snaked back and forth inside the raceway, so there's no pile left on the floor. Changes in the cable runs are relatively easy, because the cables run parallel, and they don't get tangled because they can't be disturbed.

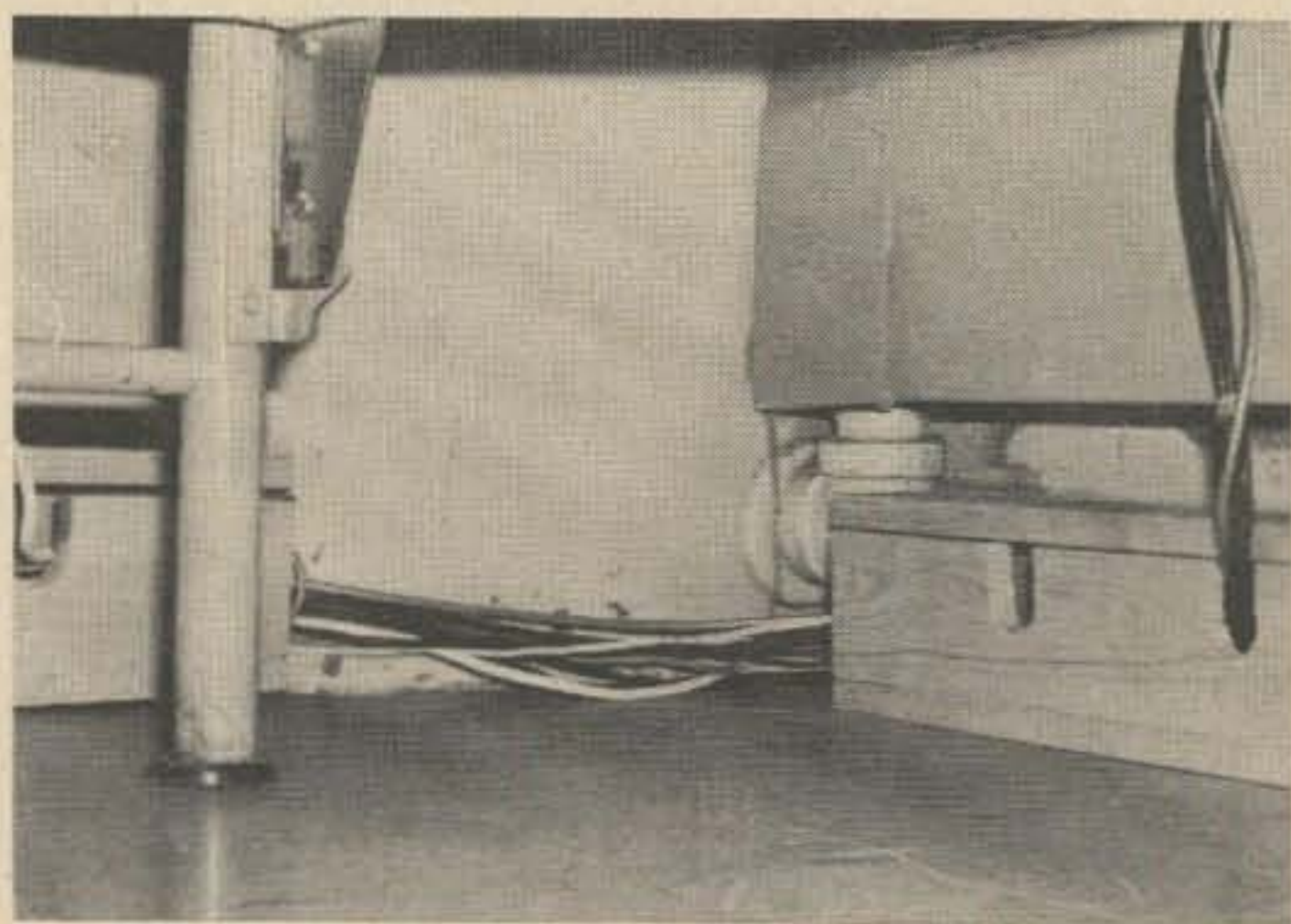

Final appearance—cables in place, lids closed

Wire mesh trough would probably be as good or better, though I haven't tried it. In either case, cost and construction time for a foot-long piece are negligible.

... K6HKB/1

the amateur's most wanted gift



Heathkit® SB-101

\$370

for free catalog write
Heath Company, Dept. 11-12,
Benton Harbor, Michigan 49022

is a plastic wide-mouth bottle cap with the center cut out. It is epoxied in a press-fit hole cut in the front panel. The base of the CRT is supported by the filament transformer. If no socket is available a few pin clips from octal sockets will provide convenient pin connections. Be sure that all 60-cycle and dc voltages are isolated from the chassis. The only chassis grounds, other than in the phase shift circuit, are *rf* bypass capacitors, C7, C8 and C9.

Before *rf* is applied, a single spot will appear on the face of the CRT. This can be centered with R8 and R9 and focused with R4. Its intensity is adjusted with R7. Try one or two turns around L1 for L2, connect the transmitter output to one coax fitting and the antenna or a dummy load to the other. If a diagonal line appears before *rf* is applied, reverse the power line plug. Turn on the transmitter and the CRT pattern will become a circle as C12 and C13 are adjusted to produce the 90° phase shift. This circle should be no more than one-half the diameter of the CRT. If it's too large reduce the turns or the coupling of L2. If too small change L2 to increase power transfer.


Modulate your transmitter and an annulus will result bounded by two circles; one larger and one smaller than the circle produced by the unmodulated carrier. As you talk, this annulus will become thin at low modulation levels and quite thick on modulation

peaks. The percentage of modulation is equal to the difference of the two radii divided by their sum multiplied by 100. At 100% modulation a completely shaded circle will be produced with a dark dot in the center. A bright dot in the center warns of over 100% modulation.

The CRT pattern also tells several other things about your signal. If the shading of the annulus is not uniform when a steady tone is transmitted some distortion is present. If you adjust to a perfect circle using a purely resistive dummy load an antenna with capacitance or inductance will produce an oval. The amount of distortion accurately indicates the extent of maladjustment. Since the size of the unmodulated circle is directly related to the amount of *rf* in your feed-line this monitor can serve as a very sensitive tune-up indicator.

The value given for L1 permits use on the six meter band. By using less inductance you can tune up on two, or move down to the dc bands with more inductance. Increasing L1 to ten turns will permit use on the Citizens' Band. The few CB'ers who still are running five watts will need to increase L2 several turns to pick up enough *rf* for a good pattern. The correct inductance for the frequency of interest can be determined from the charts in the Handbook. Possibly a more scientific approach is by cut and try with a grid dip meter.

...WA9IGU

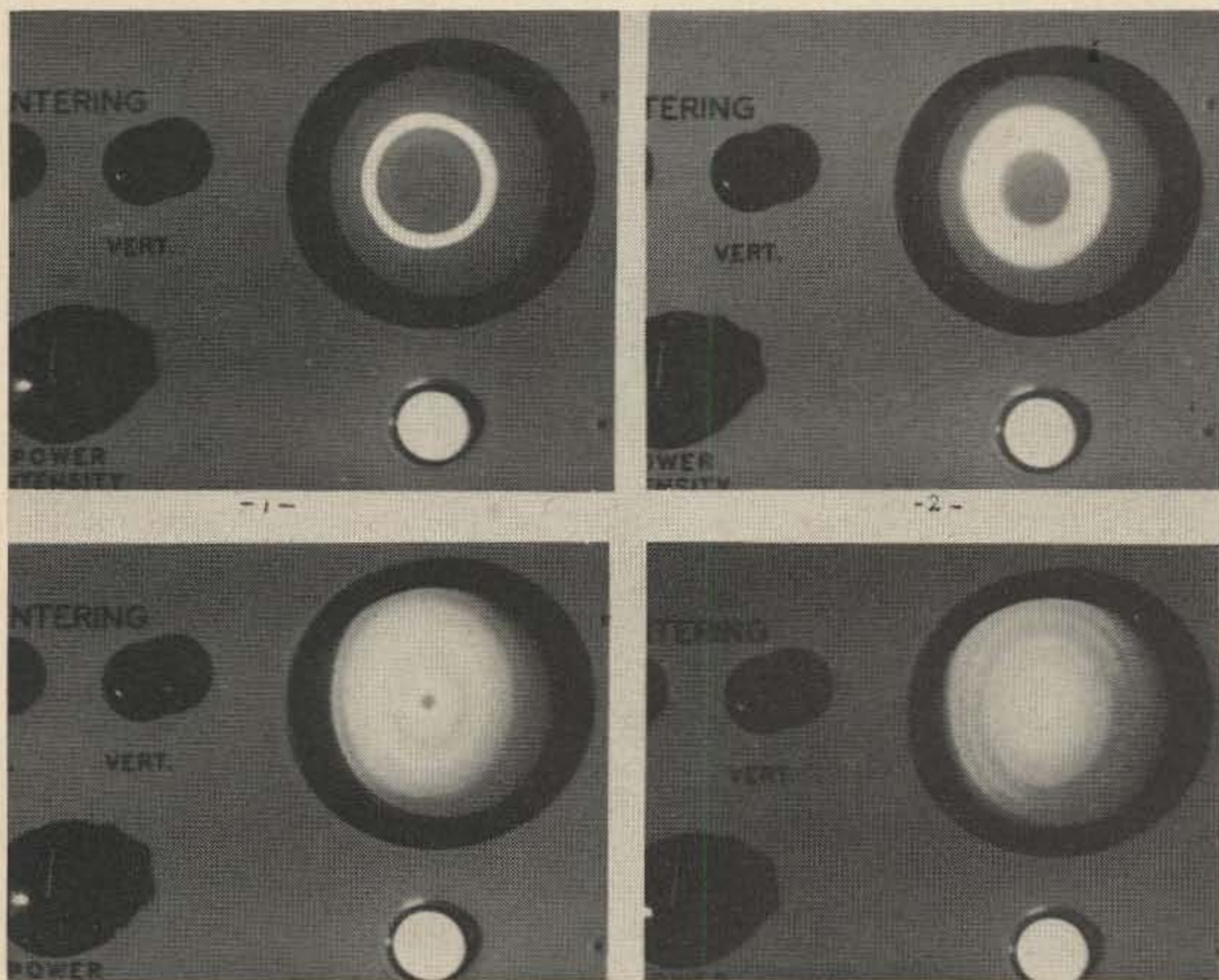


Without a carrier a white spot shows in the center of the CRT. An unmodulated carrier produces a circle.

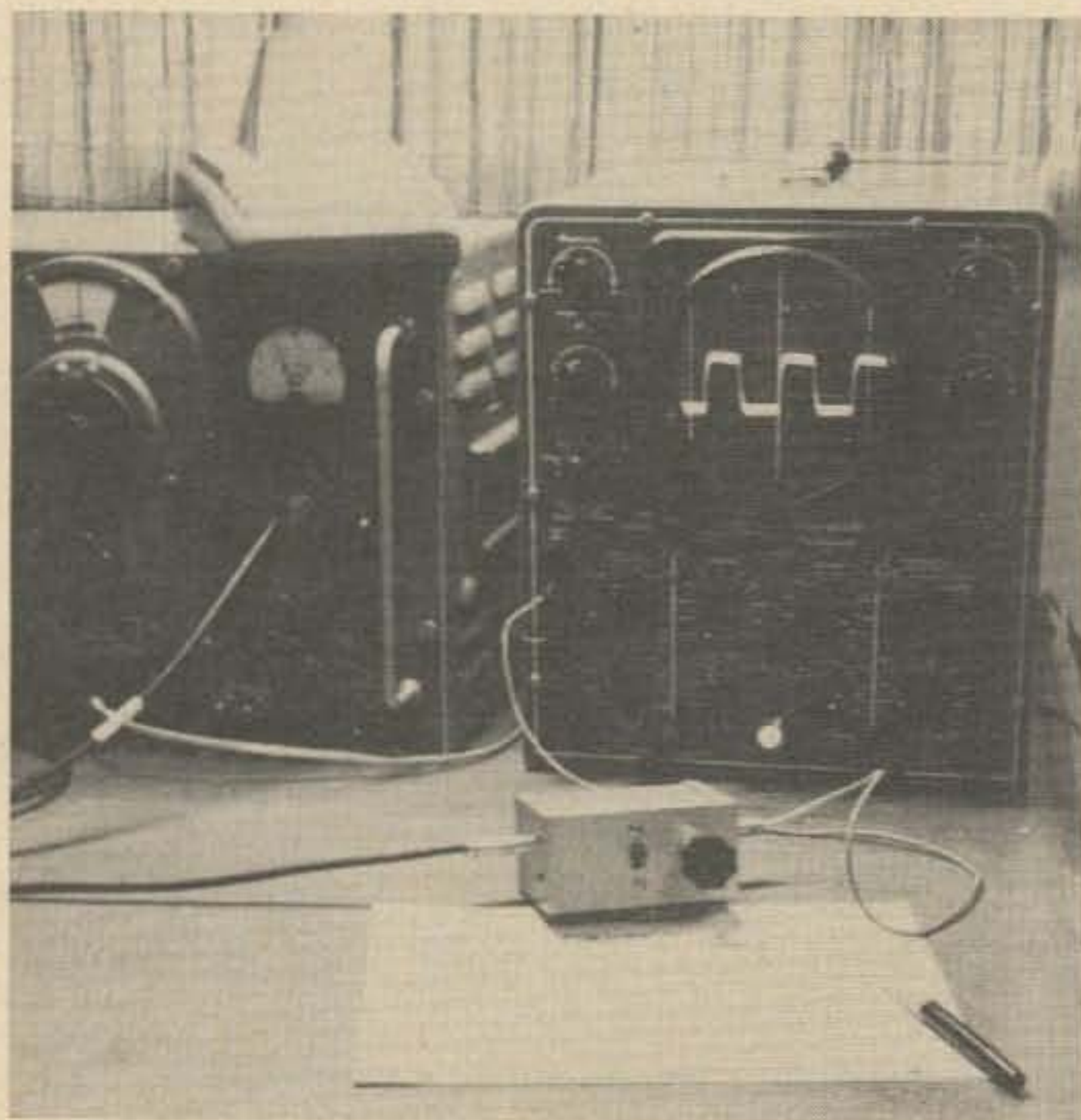1. *Very low modulation.*
2. *Approximately 33% modulation.*
3. *Nearly 100% modulation.*
4. *Bright spot in center warns of over 100%.*

The Mini-Square

Clifford Klinert WB6BIH
520 Division Street
National City, CA 92050




Any technician who has worked with audio equipment knows the value of square waves for checking performance of audio equipment. This article describes a simple and inexpensive integrated circuit amplifier/limiter that can provide a good quality square wave when driven by a sine wave source. The unit should not take more than a weekend to assemble, and will provide the experimenter with an interesting demonstration of the capabilities of this integrated circuit.

The circuit

The CA3011 is a wide band amplifier/limiter that contains ten transistors, seven diodes, and eleven resistors in a TO-5 case. With the connections shown in figure one, taken from RCA, it has a typical voltage gain of 70 db. The input limiting voltage required is about 250 microvolts, but the input voltage for using it as a square wave generator may be as high as several millivolts. It is usable up to 20 MHz, but the gain decreases, and the input voltage required for limiting increases above one MHz. The performance at the lower frequencies may also be reduced. The CA3011 is used typically for FM amplifiers at 10.7 MHz. For information on performance and applications, consult the reference at the end of this article.

Construction

As shown in the photographs, the circuit is assembled on a small piece of perforated board mounted inside a commercially manufactured (LMB) aluminum box. Layout is not at all critical, and almost any method could be used provided that leads are not too long. A small slide switch was used to turn the power off and on from the standard nine volt transistor radio battery. The capacitors can be mylar or ceramic with any voltage rating of ten volts or more. The resistors are half-watt. RCA jacks were used as input and output connectors.

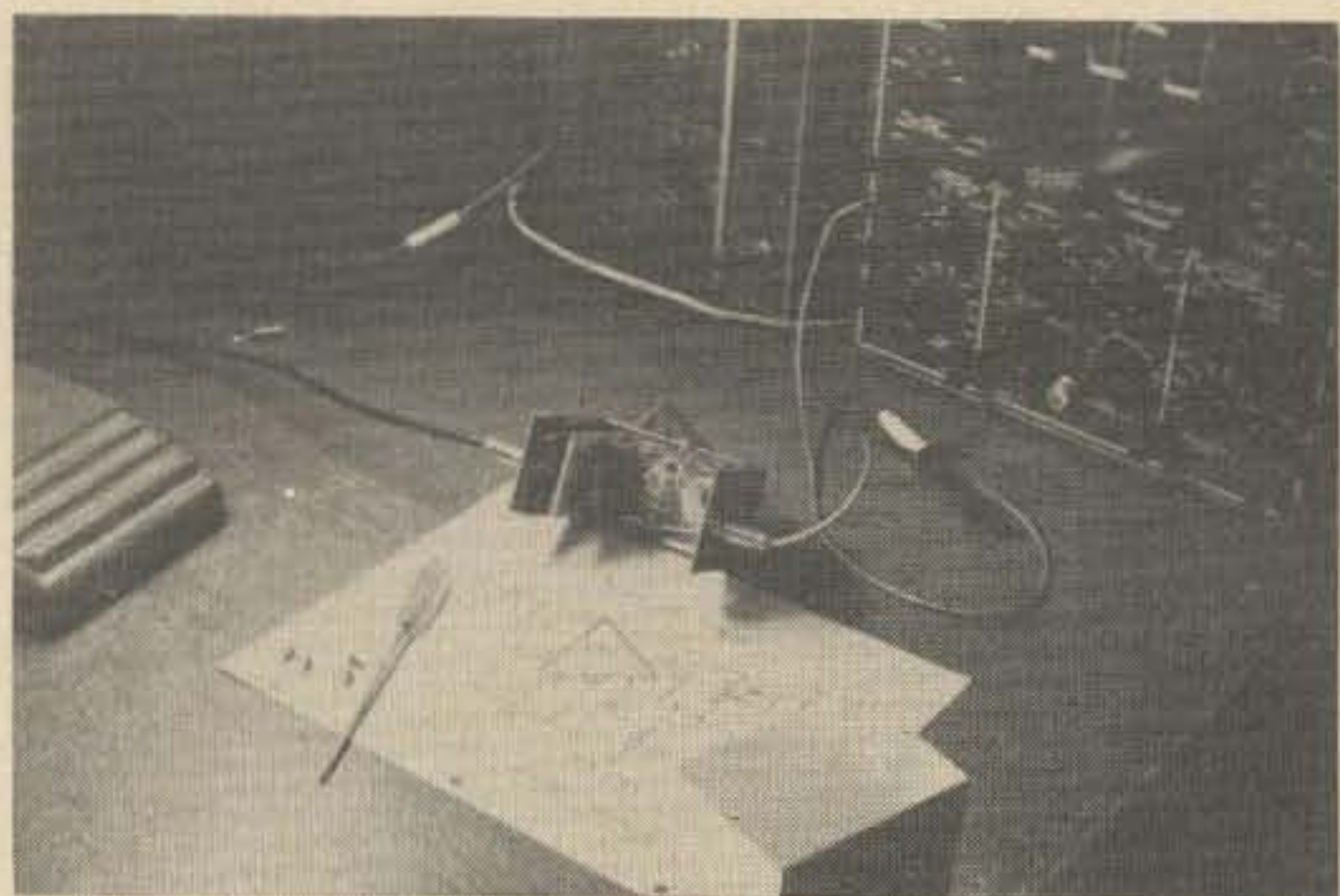

Conclusions


This unit will provide a symmetrical, good quality output wave form, but it must be driven by a good sine wave for best results. Impedance mis-matching can cause distortion in the waveform, and the builder may wish to raise the values of the input and output resistors. For the same reason, varying the output level control may also cause distortion. Increasing the gain control setting on the oscilloscope also affected the shape of the output waveform on the 'scope pattern in the picture.

This has made an interesting project with only a nominal expenditure of time and money, and can introduce the experimenter to other useful and facinating projects in the wonderful world of integrated circuits.

. . . WB6BIH

Reference

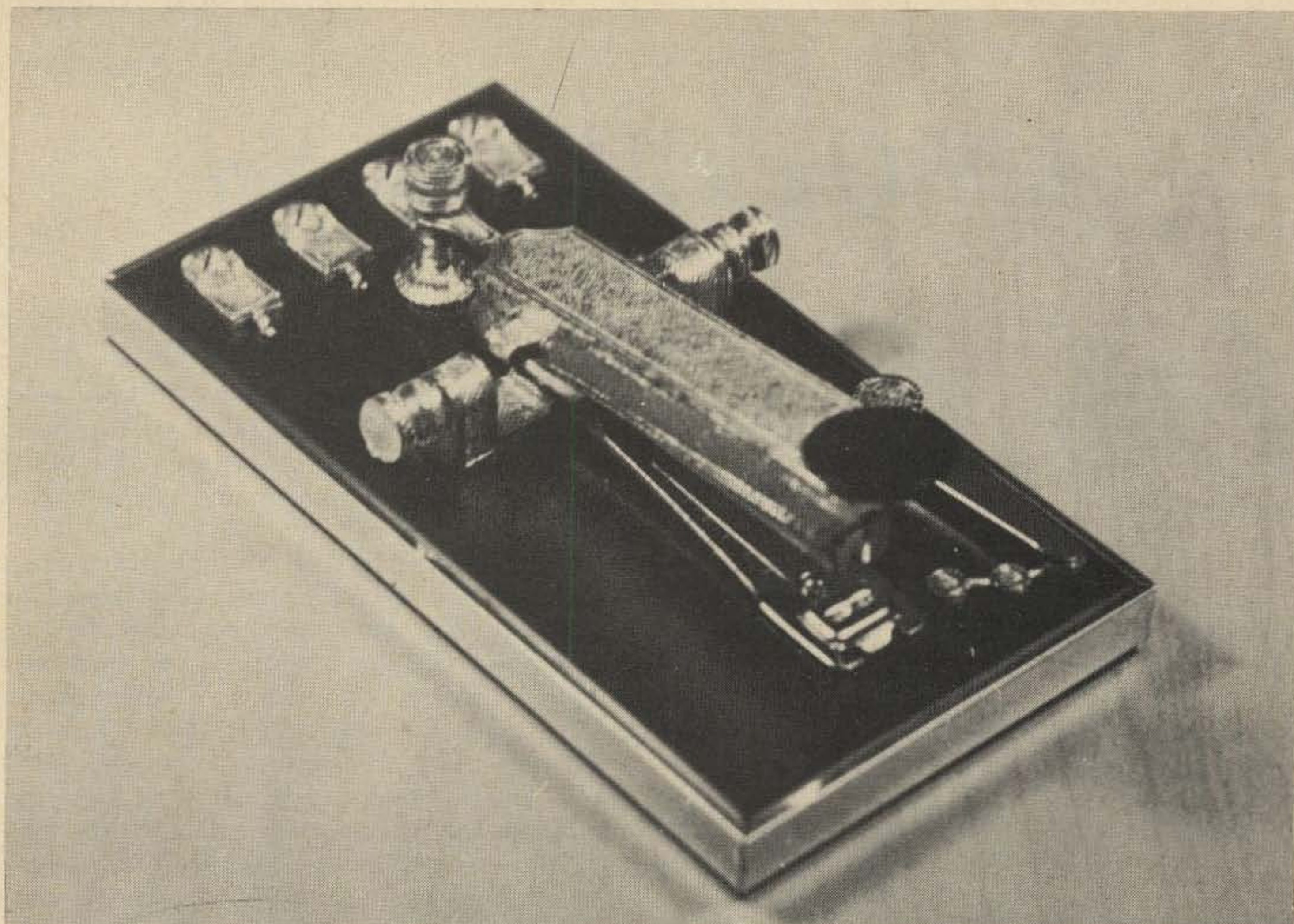Radio Corporation of America, *RCA Linear Integrated Circuits*. Harrison, New Jersey : RCA, 1967.



TELEGRAPH KEY STAPLER

Handsome reproduction of antique telegraph key
This Morse Code Telegraph Key cleverly functions as a stapler. Bostitch stapling mechanism. The rheostat is a staple remover. Antique gold finish on black metal with Chinese-red velvet base. $6\frac{1}{2} \times 3\frac{1}{2}$. Ideal for an original gift for the office or the radio shack.

Built to last

\$10.59 + 80¢ Postage

10 Days money back guarantee

Sorry no C.O.D.

Please send _____ key stapler(s) to

NAME _____

STREET _____

CITY _____ STATE _____ ZIP _____

please print

HUGO H. ROUSSEAU & SONS

210 Post Street • Suite 915

SAN FRANCISCO

CALIF. 94108

Add-On FM Test Set

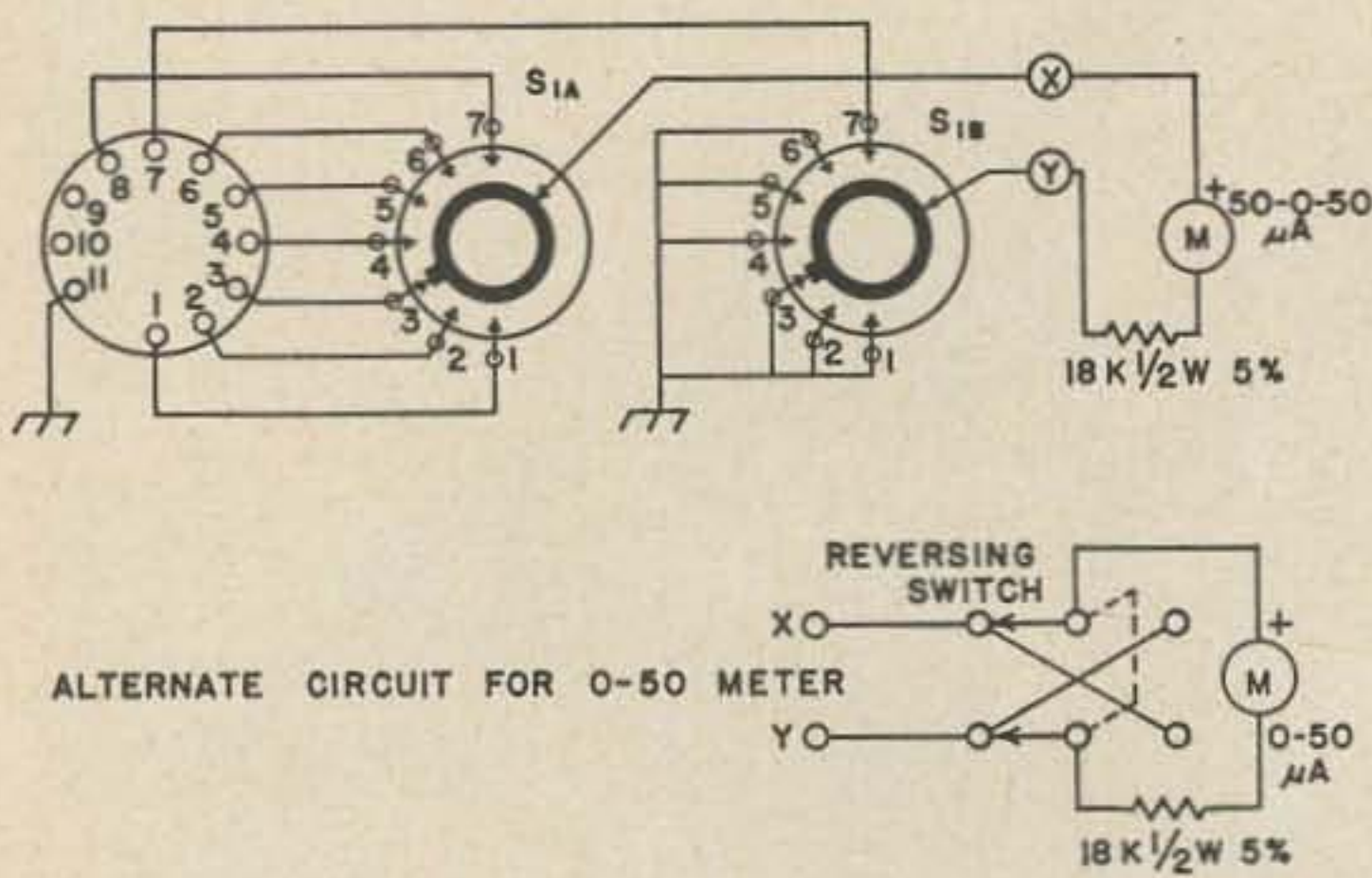


Fig. 1. The basic Schematic for The Casual FM'er.

Most Amateur FM'ers are aware that Motorola base and mobile equipment have central metering jacks for both the transmitter and receiver. These jacks provide a convenient method of measuring each stage during tune-up and alignment procedures. The basic Motorola test set, consisting of the alignment meter, field strength meter, and *if* xtal oscillator, costs approximately \$200. The extra deluxe version with the deviation meter and peaking generator costs almost \$500. Thus, it is easy to see why most amateurs stick to their VOM's when aligning their Motorola equipment.

The purpose of this article is to outline the construction of a suitable test set for Motorola equipment which can be constructed in varying degrees of sophistication. The basic set consists of a 50 μ A meter, and a seven position two pole switch, an 18K 5% 1/2 Watt resistor, and an 11 pin plug to match the metering socket. This basic unit may be plugged into either the transmitter or receiver to meter the various stages. If a 0-50 μ A meter is used a reversing switch will have to be used to allow the discriminator (receiver position 4) to be read in both a positive and negative direction. If a 50-0-50 μ A meter is used (as in the K9STH unit) this switch is not needed.

The basic unit may be constructed on a small chassis or mini-box large enough

to house the meter and switches. The schematic appears as Fig. 1. This unit is quite satisfactory for the casual FM'er who requires limited versatility. In fact, the basic unit is similar to the Motorola P-8449-B metering chassis used in many up-right base stations.

For the more serious FM'er or for clubs which desire a more versatile piece of equipment the basic test set may be expanded in varying degrees. The first expansion consists of adding a microphone and receiver audio output circuits. The microphone circuit allows a conventional Motorola microphone to be used to key and modulate the transmitter without the need for going to the control head. The use of a speaker in the test set will allow incoming signals to be easily heard. The additional circuitry appears as Fig. 2.

The third expansion is the addition of field strength meter facilities. The circuit is quite conventional. A short whip may be used for the input circuit. The additional circuitry appears as Fig. 3.

The fourth expansion makes the meter movement into a 0-15 VDC voltmeter for measuring automobile battery voltages. This is quite useful for many VOM's do not have a 0-15 volt range. Most meters have a 0-10V and 0-50 V range, which do not allow accurate measurement of 12 volt automobile systems. The calibration of the

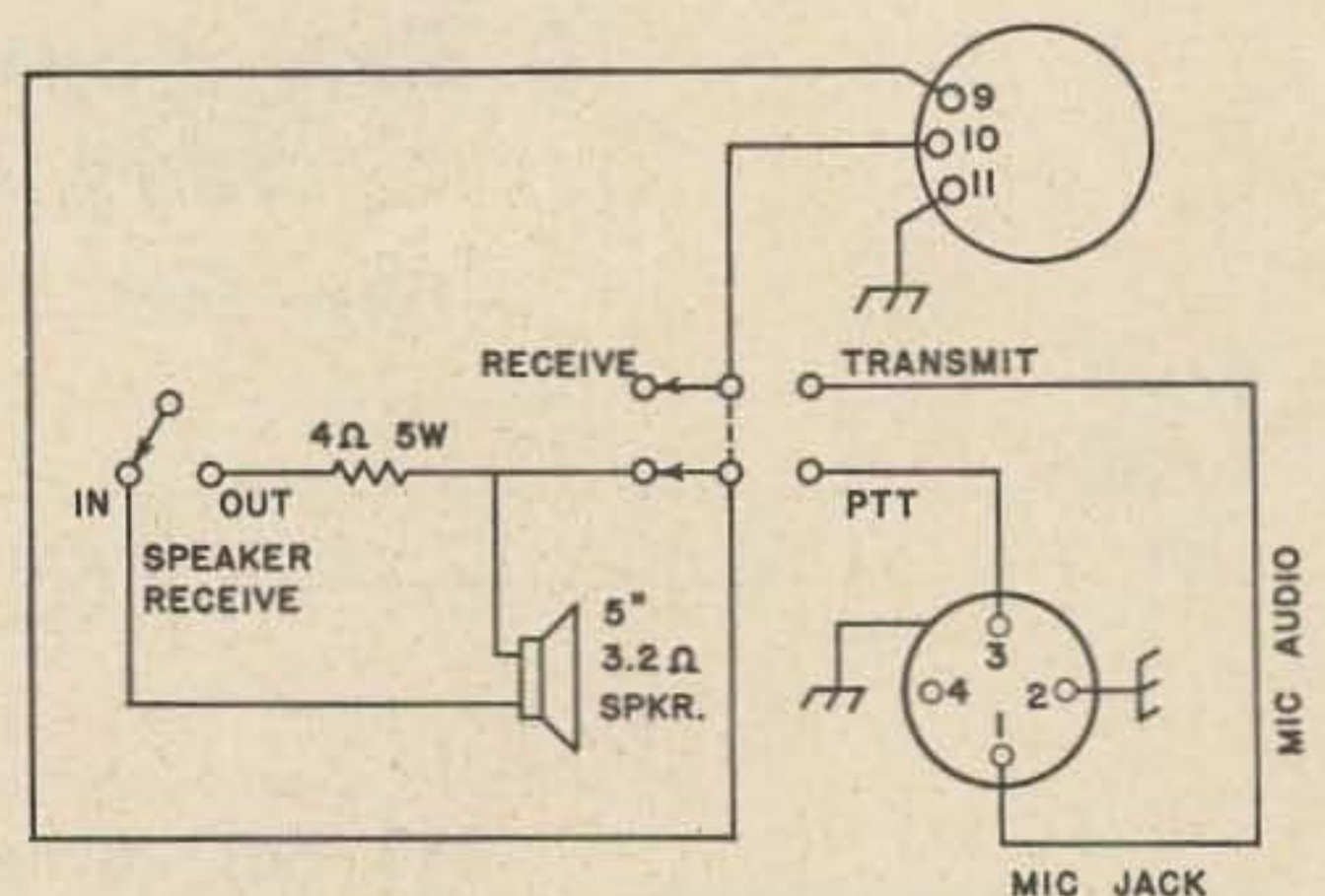


Fig. 2. Addition # 1 Makes Fig. 1 more versatile.

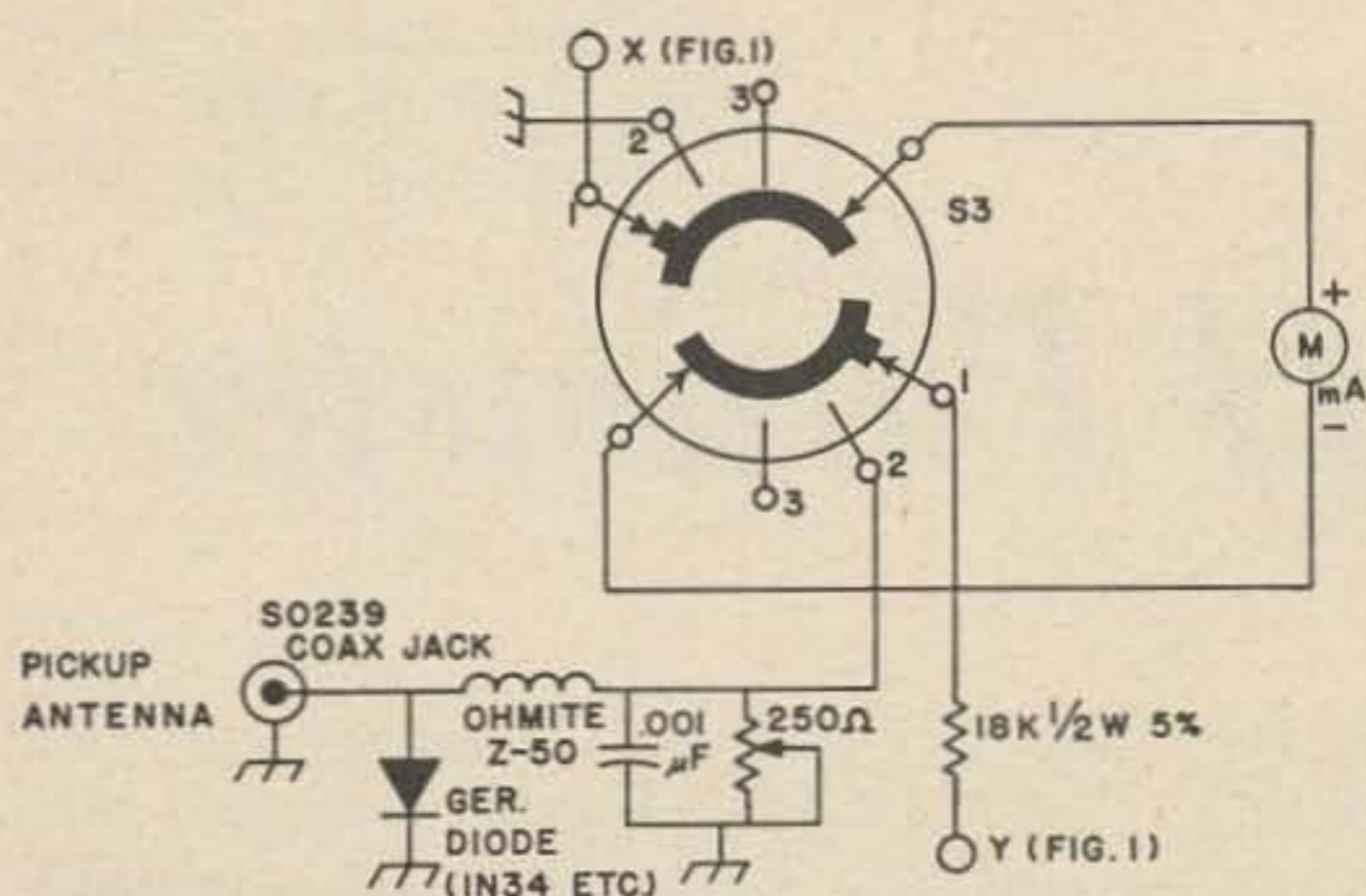


Fig. 3. Adding a Field Strength Meter.

meter can be done either mentally or by the addition of another scale. The easiest method is mental calibration, for each 10 increments on the meter scale represent 3 volts. The additional circuitry appears as Fig. 4.

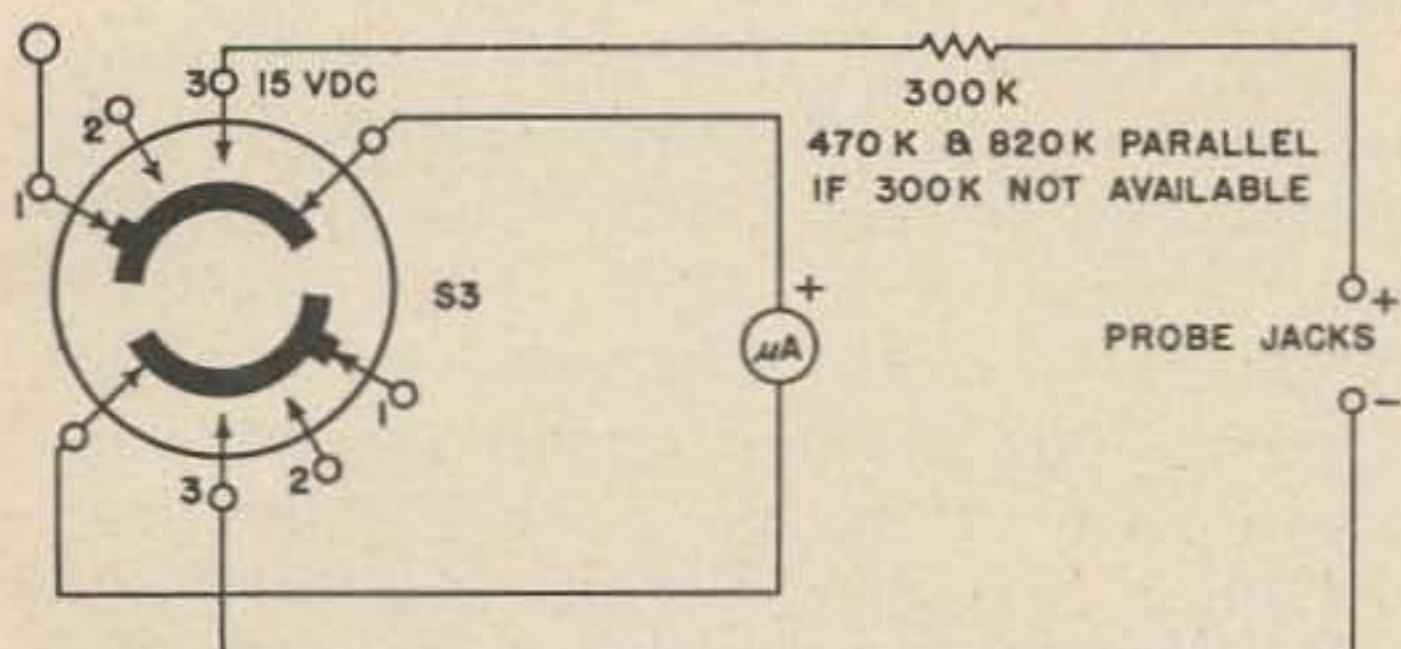


Fig. 4. The Meter becomes a Voltmeter.

The fifth expansion is the addition of a crystal controlled 455 kHz oscillator. This is needed when zeroing the discriminator during receiver alignment procedures. Two other crystal positions may be used for the frequencies of 450 kHz and 460 kHz (for narrow band) or 440 kHz and 470 kHz (for wide band). This allows the low *if* filter to be checked (if the second limiter reading is not almost identical on both crystal positions, the filter is probably defective). Also, the crystal positions may

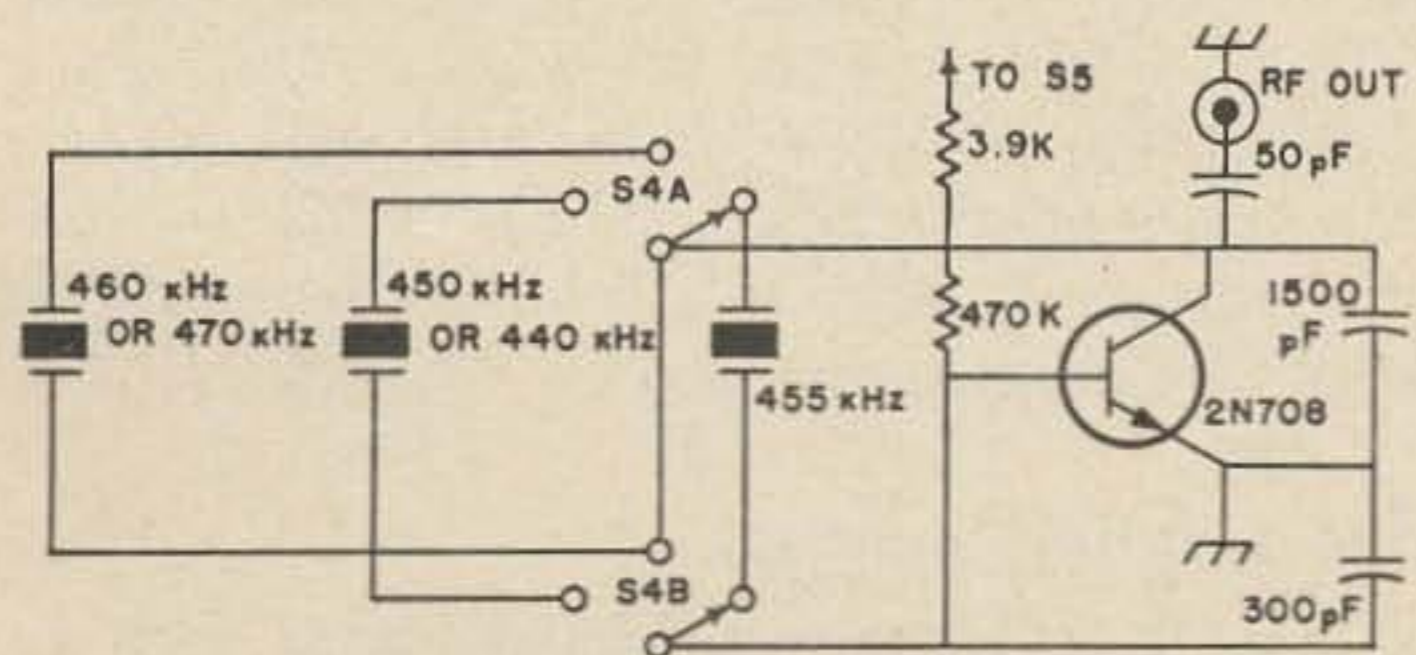


Fig. 5. Adding 455 kHz Oscillator

be used to calibrate an oscilloscope for measuring deviation. Since my semi-conductor supply and knowledge are relatively small, I referred to the March 1967 issue of 73. This is the issue that contains the article entitled "73 Useful Transistor Circuits". The 100 kHz calibrator circuit, figure 62, will oscillate at 455 kHz. The schematic is reproduced as Fig. 5.

The sixth expansion is an audio oscillator. When this oscillator is adjusted for an output of 1 volt RMS the deviation of the transmitter may be easily set. Also, an au-

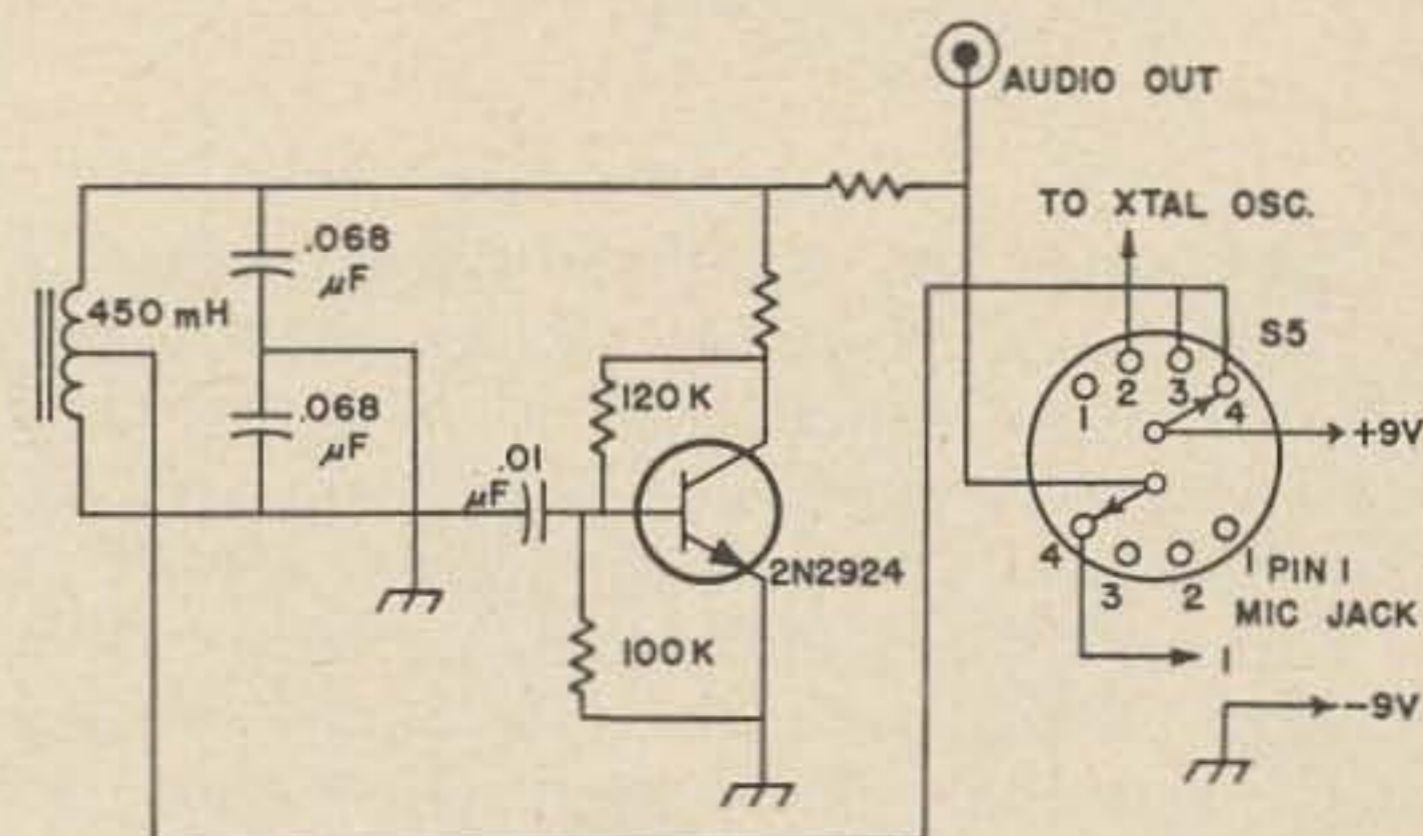


Fig. 6. Audio Oscillator.

dio oscillator is quite useful in trouble shooting both receiver and transmitter circuits. Again reference is made to the article mentioned above. Figure 61, page 26A, is a 1 kHz oscillator. The value of inductor listed may be hard to find, but an audio inter-stage transformer (1:3 ratio) worked in a bread-board circuit when the primary was used for the inductor. The schematic is reproduced as Fig. 6.

The actual constructional details are left to the individual amateur. A medium sized chassis will hold the complete circuit while the smaller versions may be scaled down as needed. The simplest version could be built in a small mini-box with the 50 μA movement of a VOM used as the indicator.

If you are not an active FM'er or have no interest in VHF then this article will have been of no use to you. If you are interested in VHF and/or FM, then I hope that you will find the Add-on Test set a useful addition to your test equipment inventory.

...K9STH

The Elusive H Parameter

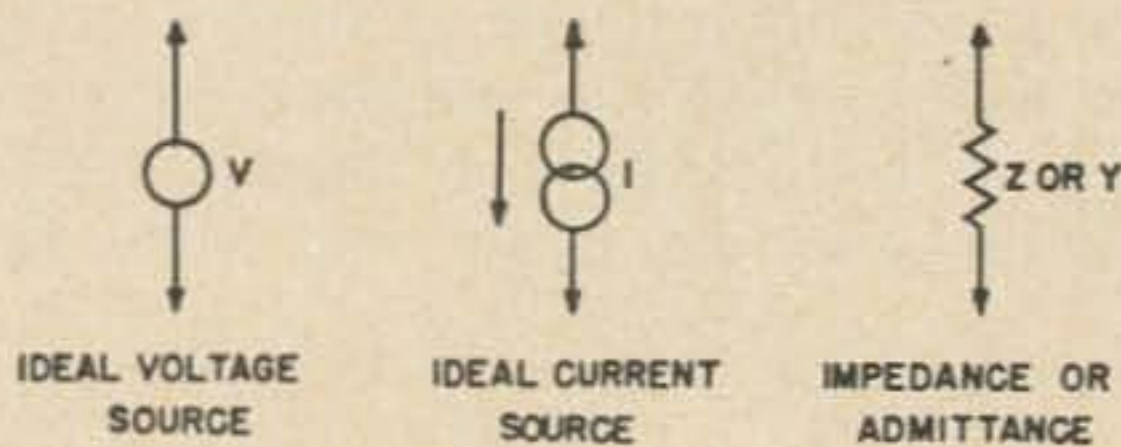


Fig. 1. Basic ideal elements.

Ever since the transistor became readily available at low prices, it has been very popular with experimenters. With a little reading and a good deal of playing around, these people can become quite proficient at this fascinating and relatively inexpensive hobby. Some, however, are quite puzzled at the seemingly nonsensical names given to transistor parameters such as h_{ie} and h_{re} . A description of the origin and development of the h parameters is not a complicated task, and makes a very interesting story. The first step in this investigation will be to consider a few basic concepts in electronics theory that will be used to introduce the h parameter model and explain its elements.

The model concept

The model is a purely theoretical circuit or element that is used to represent or describe a more complex device. The model is made up of "pure" elements that are interpreted as containing only the properties that they describe. For example, the symbol for an inductor would indicate only inductance, while any real coil would also have a finite resistance associated with it.

Three basic elements that will be dealt with in this discussion are indicated in Fig. 1. In part (a), the symbol for a voltage source is shown. The ideal voltage source is assumed to have zero internal resistance so that no matter what is connected in parallel with it, the voltage will always be the same. The magnitude of the voltage is usually given with the symbol, and

is represented by the "V" beside the ideal voltage source. The voltage source also can be a variable source, and the magnitude of the voltage will be given by a mathematical expression, usually the product of two numbers. The ideal current source is shown in part (b) of Fig. 1. This element has an infinite internal resistance, and anything that is connected in series with it will have the same current flow, the magnitude of the source. The magnitude of the current is given by "I", and can also be variable or controlled as with the voltage source.

The reader will probably notice a similarity or contrast between the ideal voltage source and current source. The two are precise opposites, or duals. The concept of duality is a useful tool when an individual gets used to working circuit problems in a certain way. If he does not like the way a circuit is arranged, he can change the circuit to its dual, work the problem, and then get the dual of the answer which will then be the desired result in the original circuit. For example, the dual of voltage is current, the dual of capacitance is inductance, and the dual of series is parallel.

The third basic element that will be needed for this discussion is shown in Fig. 1 part (c). This is the ideal resistance, or its dual the ideal conductance. At this point it will become necessary to make a change in terms. Since the expression "resistance" is valid only for dc, a new term will be needed. The word we are seeking is impedance. Impedance can be used with either dc or ac, and will always mean the voltage in the circuit divided by the current, regardless of whether it is ac or dc. Admittance is the dual of impedance, and will replace the term conductance. The symbol for impedance is Z , and the symbol that will be used for admittance is Y .

The two-port concept

Fig. 2 shows a two port network with an input and output. A signal applied to the

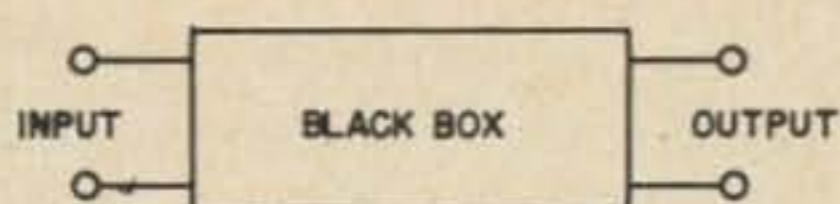


Fig. 2. Two-Port circuit.

left terminals, or port, will appear at the right terminals, modified in some way depending on the contents of the "black box" in the middle. The object in the middle can be any device that is desired, such as an amplifier. It would be handy if we could find a suitable model made up of ideal elements that could be used to represent the behavior of the thing in the black box. One model that could be drawn is shown in Fig. 3. This model can be used to represent a voltage amplifier, and has a characteristically low impedance associated with it. Also, we can take the dual of the circuit as shown in Fig. 4. Note that the dual of a voltage in series with an impedance is a current source in parallel with an admittance. It just so happens that this circuit can represent a current amplifier, and has a characteristically high impedance associated with it.

Now all the building blocks are present to enable us to assemble the final model that will represent a bipolar transistor.

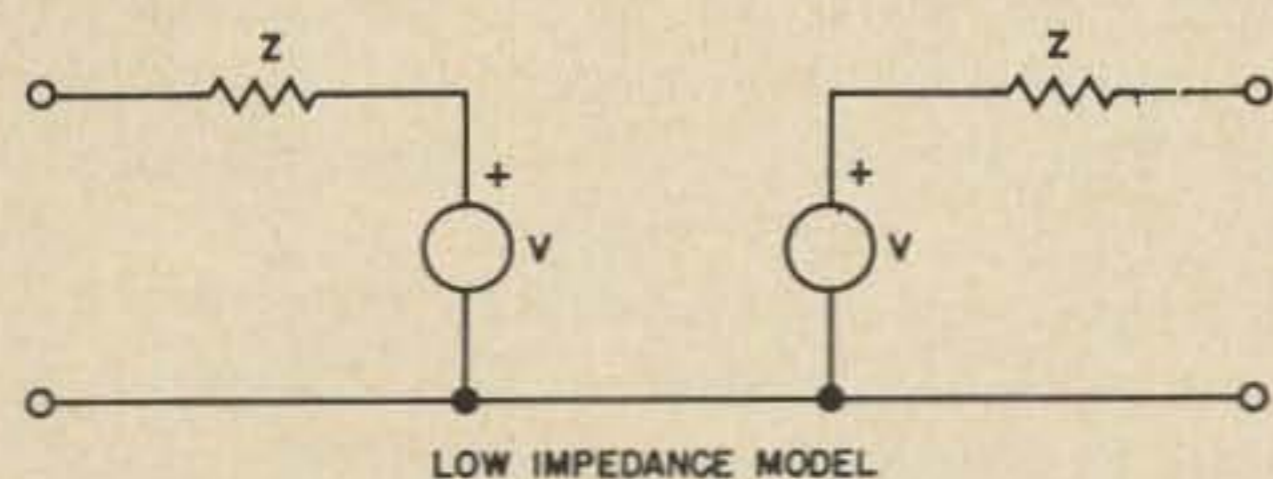


Fig. 3. Low impedance model.

The hybrid model

Since the transistor has a low input and a relatively high output impedance, it is possible to make an appropriate model by combining the models of Figs. 3 and 4 to give the hybrid model of Fig. 5. This model will have a low input impedance and a high output impedance, which is just what we desire. Thus, it is from the word "hybrid" that the h in the h parameters was obtained. The names of the elements in the model represent characteristics of the transistor, and their names were picked completely by convention. The first subscript is used to indicate which particular characteristic in the model is being described, and the second subscript indicates the configuration. The three

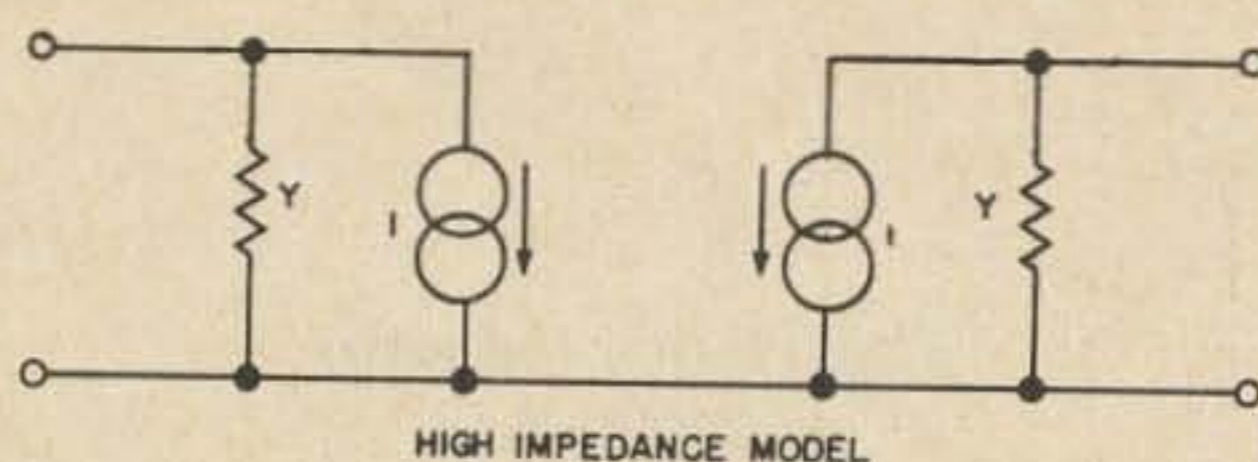


Fig. 4. High impedance model.

Table One
Definition of H Parameters

PARAMETER	COMMON EMITTER	COMMON COLLECTOR	COMMON BASE
<u>INPUT</u> IMPEDANCE	h_{ie}	h_{ic}	h_{ib}
<u>REVERSE</u> VOLTAGE FEEDBACK	h_{re}	h_{rc}	h_{rb}
<u>FORWARD</u> CURRENT GAIN	h_{fe}	h_{fc}	h_{fb}
<u>OUTPUT</u> ADMITTANCE	h_{oe}	h_{oc}	h_{ob}

possible configurations are common base, common emitter, and common collector. These terms are listed in Table 1 with the underlined word in the left column indicating the word from which the symbol was obtained. Most of the terms are self-explanatory, but the term h_{re} is probably unfamiliar. This refers to the effects of base-width modulation at the emitter junction. This is shown as a voltage source in the input, and tends to oppose the input signal. The voltage source is controlled by the collector-emitter voltage, e_{ce} , and the magnitude of the source is h_{re} multiplied by e_{ce} . The term h_{re} is the one that is often ignored because of its very small magnitude, and is usually insignificant for most applications. The forward current amplification factor, h_{fe} , is the most important parameter, and the value of the current source is h_{fe} multiplied by i_b , the base or input current. This discussion has referred to the common emitter configuration because it is the most popular,

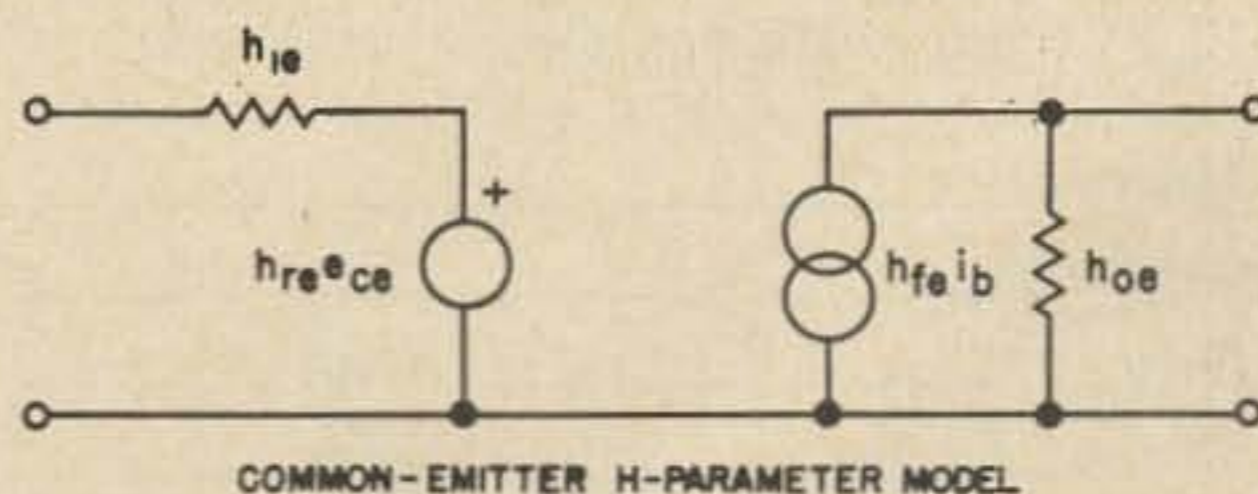


Fig. 5. H parameter model for common emitter.

CRABTREE'S ELECTRONICS

"The Ham's Heaven"
presents



The superb
NEW R-530
by GALAXY

Solid state receiver for the most
exacting performance.
\$695.00

WRITE OR CALL FOR QUOTES
OR TRADE-IN ALLOWANCES

Bob Baker
WA5 BSR/m
Phone 214-748-5361

hy-gain

18HT
HY-TOWER
Multi-band **\$149.50**
vertical antenna

CRABTREE'S ELECTRONICS
2608 Ross Ave., Dallas, Texas 75201

Please ship me the following:

- Galaxy R-530..... \$695.00
- Hy-Tower Model 18HT.... \$149.50

Shipped pre-paid anywhere in "48"

- Check or Money Order attached

Name _____

Address _____

City _____ Call _____

State _____ Zip _____

American Express - BankAmericard - Diners Club

but a similar explanation could be constructed for the two other configurations as indicated in table one. The model discussed is applicable only to ac signals and does not give any information about dc or steady state voltages or currents.

Conclusion



The hybrid model is a very handy tool that was conceived to represent the bipolar transistor and provide a way of naming and describing the characteristics that the designer must know to build any particular piece of electronic hardware where transistors are used. The model is also useful in learning some of the concepts that must be explained in basic transistor theory. Regardless of the way that it may have looked, the h parameters do have a very real meaning, and were not given their names "just for the h of it."

... WB6BIH

HV Choke Protection

A common problem with chokes in high voltage supplies is arcing from the winding to the core. This is due to the full supply voltage appearing between these points. A simple remedy is to move the choke from the positive to the negative power supply lead. This reduces the winding to core potential to a small fraction of its original value and for all practical purposes eliminates choke breakdown. The following half wave example demonstrates the required change. Note that nothing about the current metering, load, or protective circuitry is affected.

William P. Turner, WA0ABI

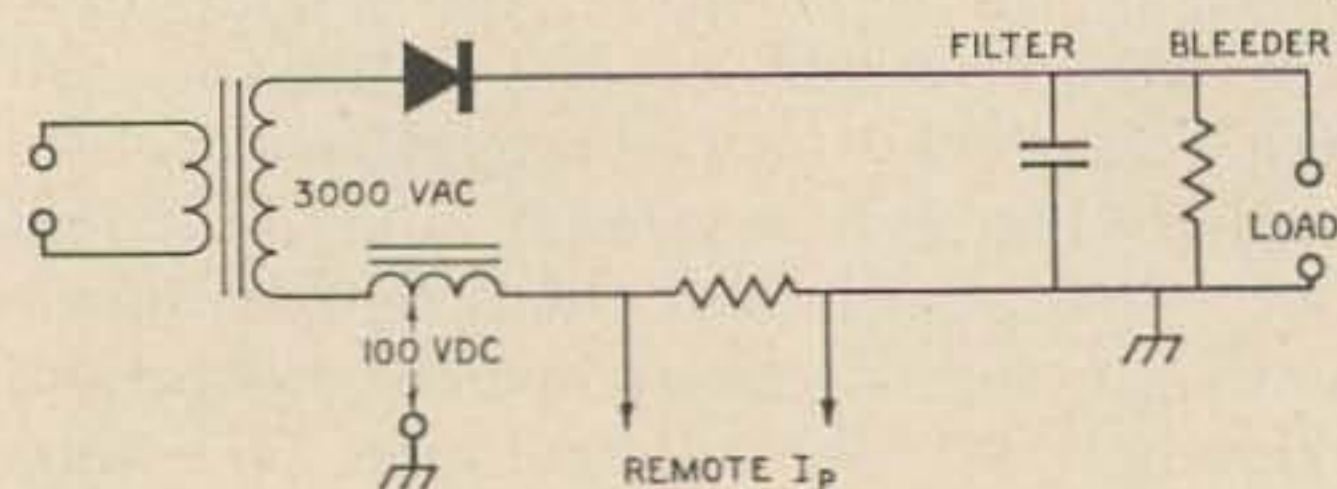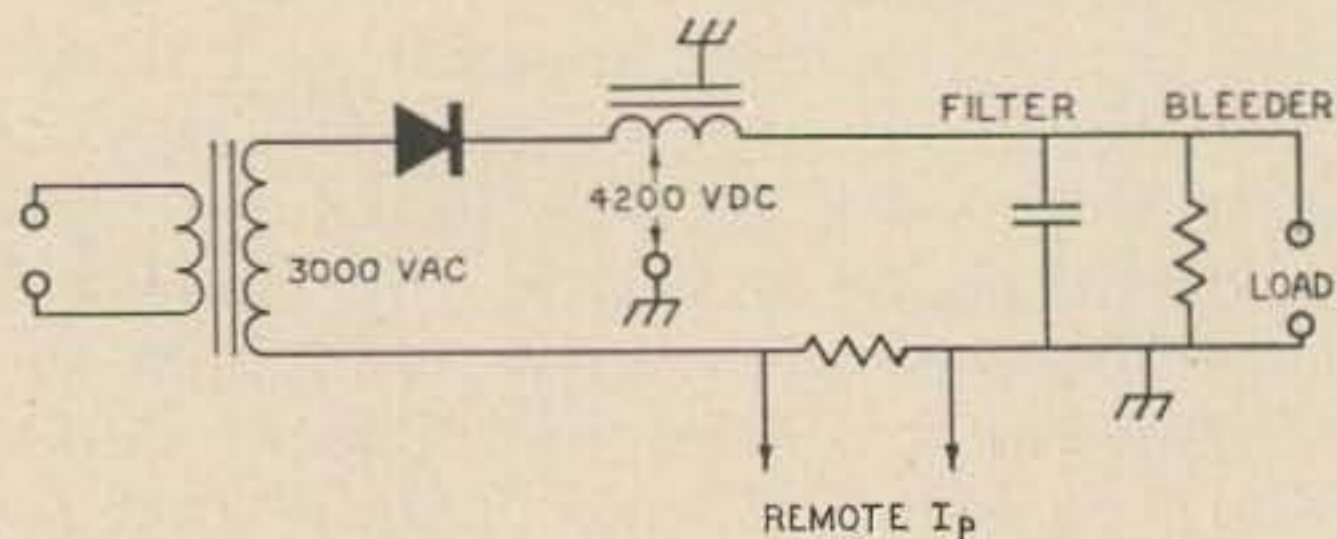

HOLIDAY SALE!

PACKAGE SALE!



SR-400 Cyclone Transceiver



HA-20 VFO

hallicrafters



SR 400 \$799.95

PS 500 AC \$119.95

\$919.90

Write for
SPECIAL PRICE!

hallicrafters

DISCOUNT PRICES. NO ONE ANYWHERE will beat our price! We will **TOP** any advertised or written price from any other dealer. We trade on both new and used equipment and we service what we sell. Instant credit on both new and used equipment. American Express and General Electric revolving charge.

AMATEUR - WHOLESALE ELECTRONICS

A DIVISION OF



International Electronic Systems, Inc.

280 ARAGON AVENUE, CORAL GABLES, FLORIDA 33134

Cable: "INTEL" 305-444-6207 Export orders our specialty

A Zero Temperature Coefficient JFET V.F.O.

The major causes of vfo drift and instability are voltage variations, loading, shock, vibration and temperature. The effects of the first four on oscillator stability can cause chirps, clicks, sudden jumps in frequency and the like. A gradual long or short term oscillator frequency drift on the other hand is primarily a function of temperature.

This article describes a vfo in which the drift due to temperature has been reduced substantially while using inexpensive components and by taking advantage of a peculiar characteristic of the Junction Field Effect Transistor not shared by either tube or transistor: zero dc drift. The FET can be biased to an operating point where its parameters remain constant throughout as large a temperature range as -55°C . to $+150^{\circ}\text{C}$.

The operating point at which the FET exhibits zero parameter change with temperature is called the zero temperature coefficient operating point and is determined by the FET gate to source bias called V_{gs} . It has been experimentally determined that this required bias is from .6 volt to 1 volt less than FET pinch-off voltage.¹ FET pinch-off voltage V_p is a parameter which appears on FET specification sheets. It is defined in two ways. (1) it is that value of gate to source bias voltage which results in drain current cutoff. (2) it is also that value of dc drain voltage corresponding to a point just to the right of the drain voltage/drain current characteristic curve knee. These two voltages are equal in value. An increase of drain voltage above the V_p value results in a very small increase in drain current.

If the attempt is made to use the published value of V_p in order to determine the zero temperature coefficient operating point V_{gs} we immediately run into a two-fold problem. (1) individual FETs, like transistors, may deviate to a large extent from pub-

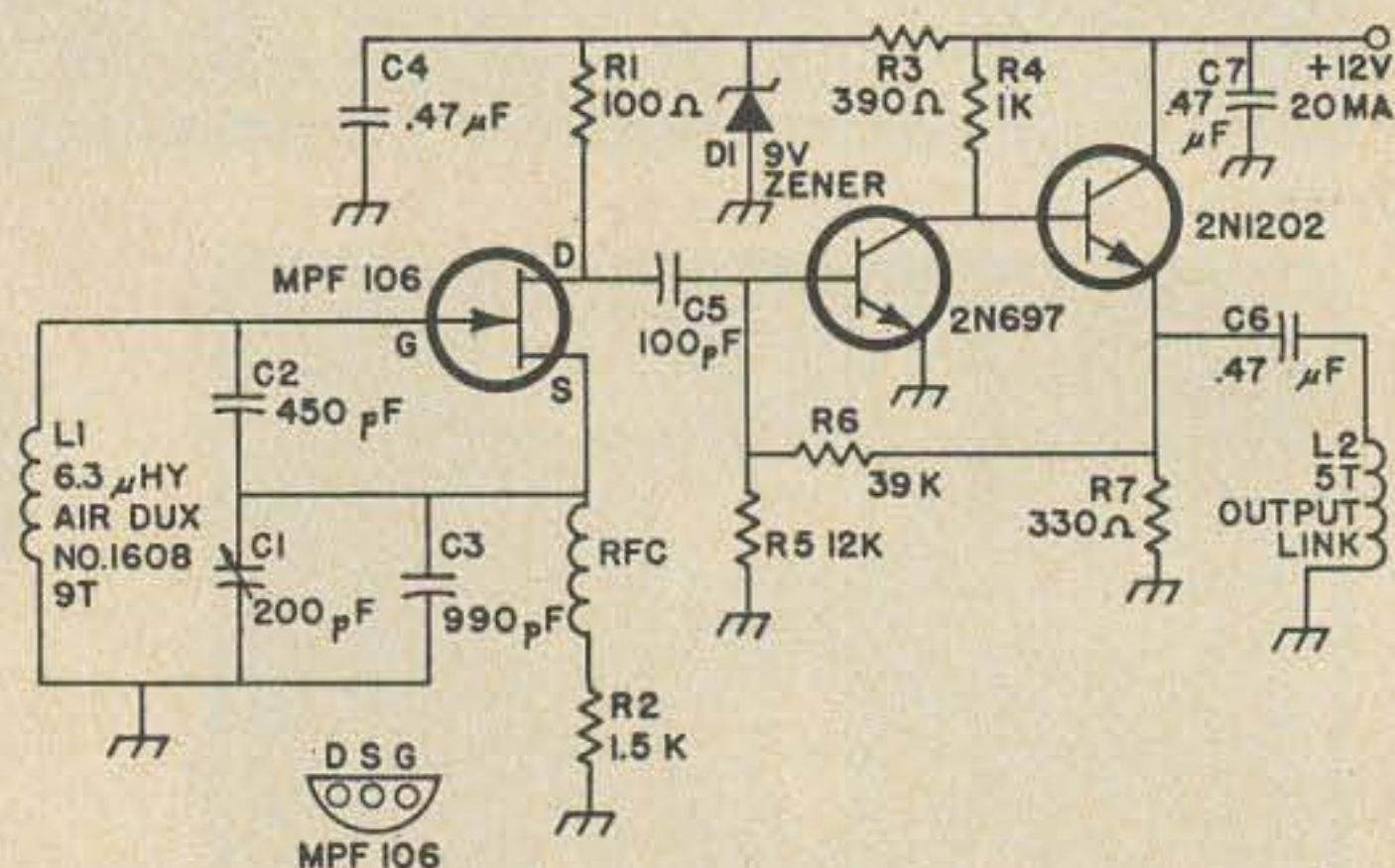


Fig. 1. Schematic diagram.

lished typical specification sheet values. (2) we are faced with the decision to fix a point on a gradually increasing quantity because drain current or gate voltage do not change abruptly in the region of pinch-off. Even manufacturers have difficulty in this regard. A study of several manufacturers specification sheets will reveal drain current cutoff values ranging from 1 milliamperere to 1 microampere.

However all is not lost. It simply becomes necessary to measure FET pinch-off. In order to avoid the second difficulty cited above we shall measure pinch-off indirectly. An expression for V_p is:

$$V_p = \frac{2 I_{dss}}{G_{max}}$$

$$\text{Where } G_{max} = \frac{E_o}{E_{in} R1}$$

I_{dss} is called saturation drain current and is that value of drain current which flows with zero gate to source bias voltage. G_{max} is another FET parameter and is the maximum low frequency FET transconductance. It so happens that this maximum value occurs at zero gate to source bias also. Therefore these two quantities can be measured simultane-

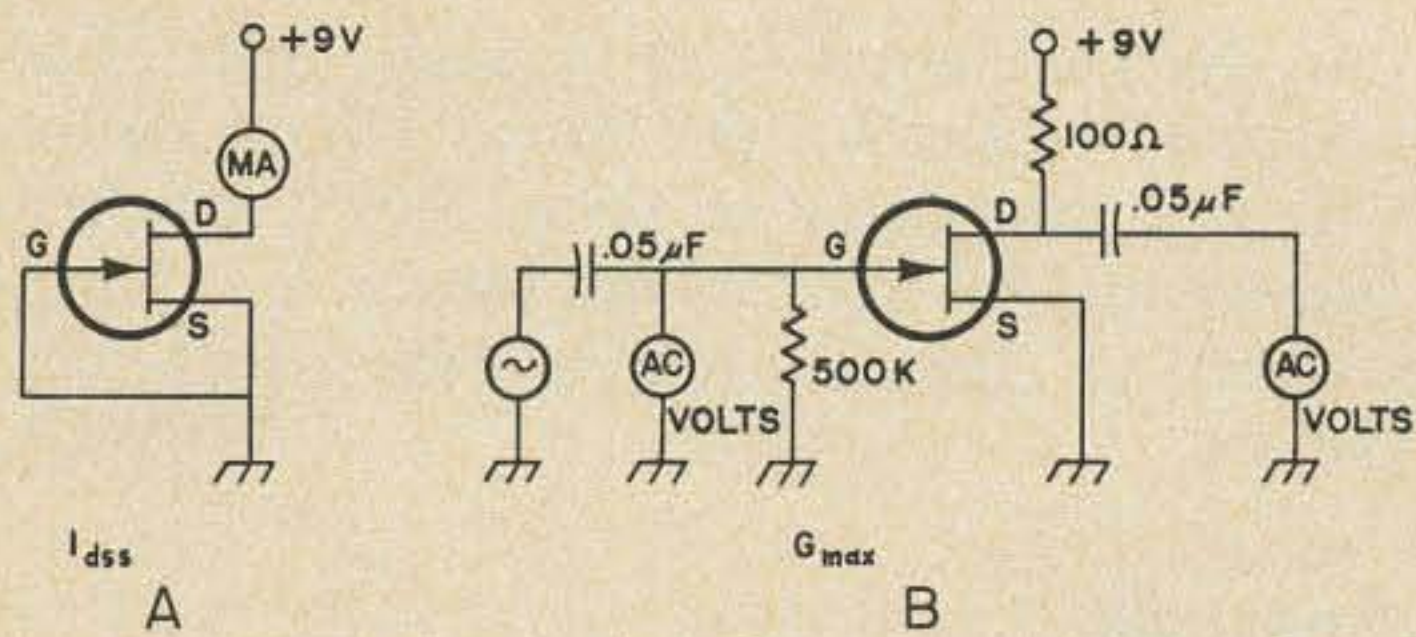


Fig. 2. Simple test set up.

ously. I_{dss} and G_{max} can be measured in the simple test set-up shown in Fig. 2A and 2b. Once I_{dss} and G_{max} have been measured we can calculate V_p by means of the equation for V_p . It then becomes a simple matter to know what the zero temperature coefficient operating point V_{gz} must be. Referring to Fig. 2B, E_o is the ac signal output voltage measured across drain load resistor R_1 by means of an ac voltmeter. E_{in} is the ac signal voltage input to the FET as measured by the ac voltmeter. E_{in} should be kept in the range of tenths of a volt in order to avoid overdriving the test FET into saturation or cutoff. The signal input voltage should be just sufficient to yield usable readings on the ac voltmeter.

In order to reduce further calculations the graph of Fig. 3 has been prepared. From this graph the value of drain current can be determined as a percentage of I_{dss} saturation current plotted against pinch-off voltage V_p .²

FETs are inherently high impedance devices. In the usual class C oscillator operation the input gate to source junction becomes forward biased during part of the input voltage cycle. The FET input impedance then drops to a very low value and results in heavy damping of the tuned circuit. The presence of the gate leak resistor imposes additional loading of the tuned circuit. In some oscillator designs this has reached a surprisingly low value. The net result is a lowering of tuned circuit Q which in a vfo must be maintained as high as possible. To circumvent this undesirable situation the FET oscillator will be operated class A.

Fig. 1 shows the schematic of a JFET class A oscillator operating at the zero temperature coefficient point in the 3.5 mHz band. The immediate distinguishing features of the oscillator are the absence of the familiar gate resistor/capacitor combination and the presence of the source bias resistor.



DECEMBER CLEARANCE RECONDITIONED HAM GEAR RECEIVERS

CLEGG	
Zeus 2-6 M 185 watts XMTR	\$319.00
COLLINS	
75A4 (early Model) RCVR	\$349.00
75S-1 RCVR	295.00
DRAKE	
2B Φ Multiplier	\$ 29.00
Drake 2B RCVR	179.00
Drake 2-C RCVR	195.00
GALAXY	
Galaxy III	\$229.00
Galaxy V	319.00
GONSET	
Gonset Comm. II 2M XCVR	\$119.00
Comm. III 6M XCVR	99.00
GSB 100 XMTR	179.00
HALLICRAFTERS	
SX99 RCVR	\$ 79.00
SX96 RCVR	129.00
SX110 RCVR	99.00
SI20 RCVR	49.00
SX108 RCVR	129.00
SX115 RCVR	369.00
HT 37 XMTR	229.00
HAMMARLUND	
HQ140X RCVR	\$129.00
HQ 110C RCVR	129.00
HQ145X RCVR	179.00
HQ170C RCVR	189.00
SP600 RCVR	199.00
HEATH	
HR-20 RCVR	\$ 69.00
MR-1 w/p.s.	29.00
HW12 80 meter XCVR	89.00
JOHNSON	
Valiant XMTR	\$159.00
Thunderbolt 80-10M Linear	260.00
Ranger II XMTR	149.00
NATIONAL	
NC173 RCVR	\$ 79.00
NC183D RCVR	129.00
NCX-5 XCVR	385.00
NCL-2000 Linear	385.00
SWAN	
SW175 XCVR 75 meters	\$129.00
Swan 240 (75-40-20) XCVR with TCU VFO	269.00
Swan 420 VFO	79.00
400 XCVR	339.00

ALL CASH ORDERS SHIPPED FREE IN THE 48 STATES

MISSION HAM ELECTRONICS

3316 Main Street, Riverside 3, California 92501
Phone 683-0523 (area code 714)

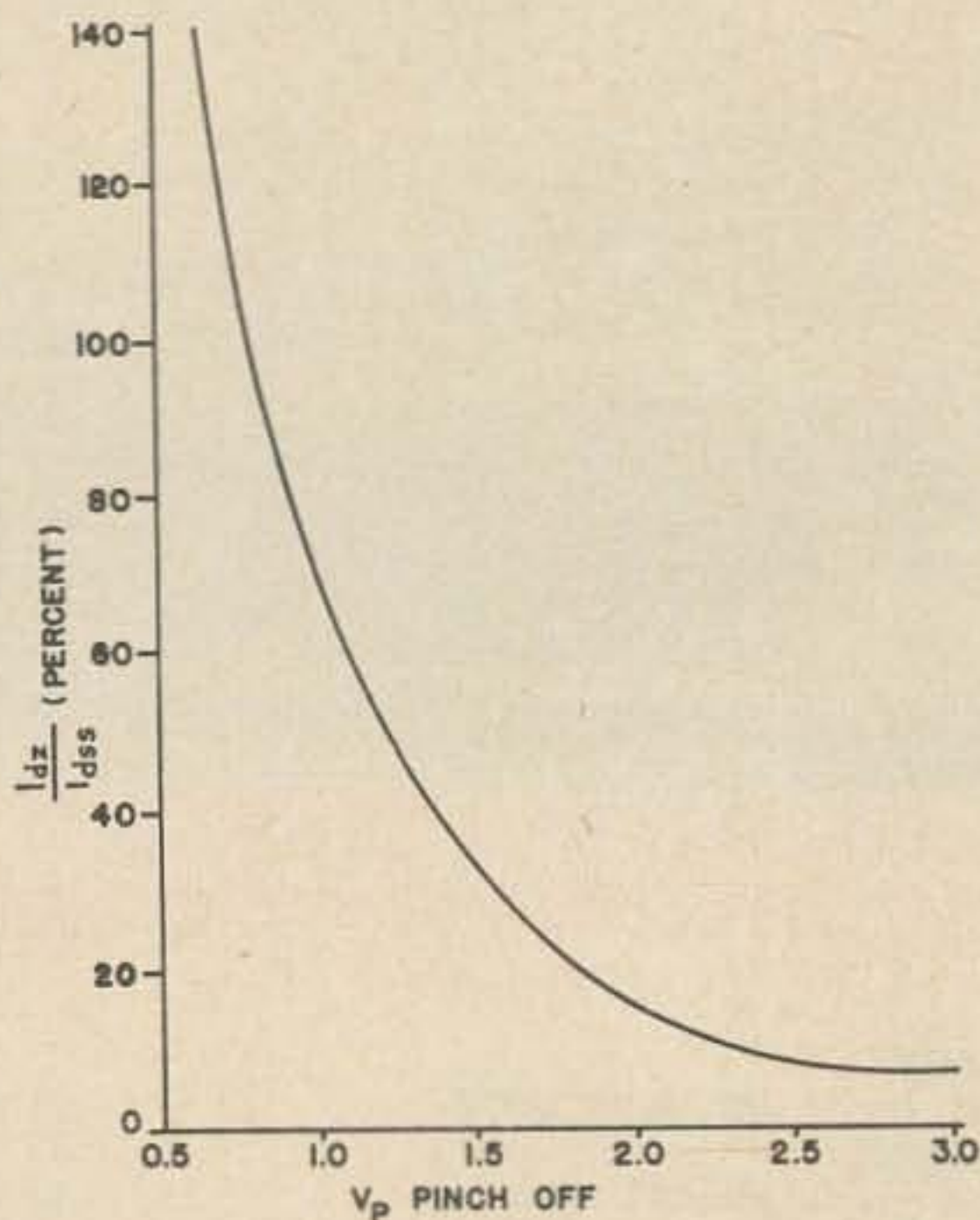


Fig. 3. See Text.

In class A operation the gate-source junction must not be driven into forward bias. Since the gate bias has been fixed due to the considerations described above the only remaining variable is gate signal voltage. Gate signal voltage is determined by the ratio of C2 and C3. The source tapping point is a compromise between sufficient voltage feedback to insure oscillation and a value of voltage which will not overdrive the gate. While the FET is oscillating momentarily ground the gate lead; drain current must not change by more than a barely perceptible amount. As a practical matter, there is nothing particularly critical about the source tapping point and the values of C2 and C3 shown on the schematic are correct for several FET samples.

In this circuit, in which particular attention has been given to achieving maximum drift stability do not expect appreciable power output from the FET. FET power output is in the region of microwatts. A two-transistor buffer amplifier is used following the FET to provide load isolation and yield a usable power output.

No degree of drift stability in the FET can ever compensate for the thermal drift characteristics of the tuned circuit coil/capacitor combination. In ordinary operation a FET is a negative temperature coefficient device. At a gate voltage or bias beyond V_{gs} the FET exhibits positive temperature coefficient characteristics. The intriguing possibility immediately suggests itself that the operating bias can be trimmed to purposely

introduce an equal and opposite drift characteristic to that of the tuned circuit. Alternately a thermistor or temperature sensitive resistor can be used in the source lead to introduce a precise temperature drift correction. . . . W6WQC

Appendix

In the vfo constructed by the author a Motorola MPF 106 FET was used. The test results from Fig. 2A yielded an I_{dss} of 7 milliamperes. The test result for G_{max} using Fig. 2B with .5 vac input yielded .32 vac out across the 100 ohm drain load resistor. G_{max} was therefore 6400 micromhos.

$$G_{max} = \frac{E_o}{E_{in} R_1} = \frac{.32}{.5 (100)} = 6400 \text{ micromhos.}$$

V_p was then 2.2 volts.

$$V_p = \frac{2 I_{dss}}{G_{max}} = \frac{2 (.007)}{.0064} = 2.2 \text{ v.}$$


From the graph of Fig. 3 $\frac{I_{dq}}{I_{dss}} = 15\%$ therefore $I_{dq} = .15 (I_{dss})$

$$I_{dq} = .15 (.007) = 1.05 \text{ milliamperes.}$$


The value of the FET source resistor was chosen to result in a drain current of 1 milliampere. The resistor value was 1.5 k.

References

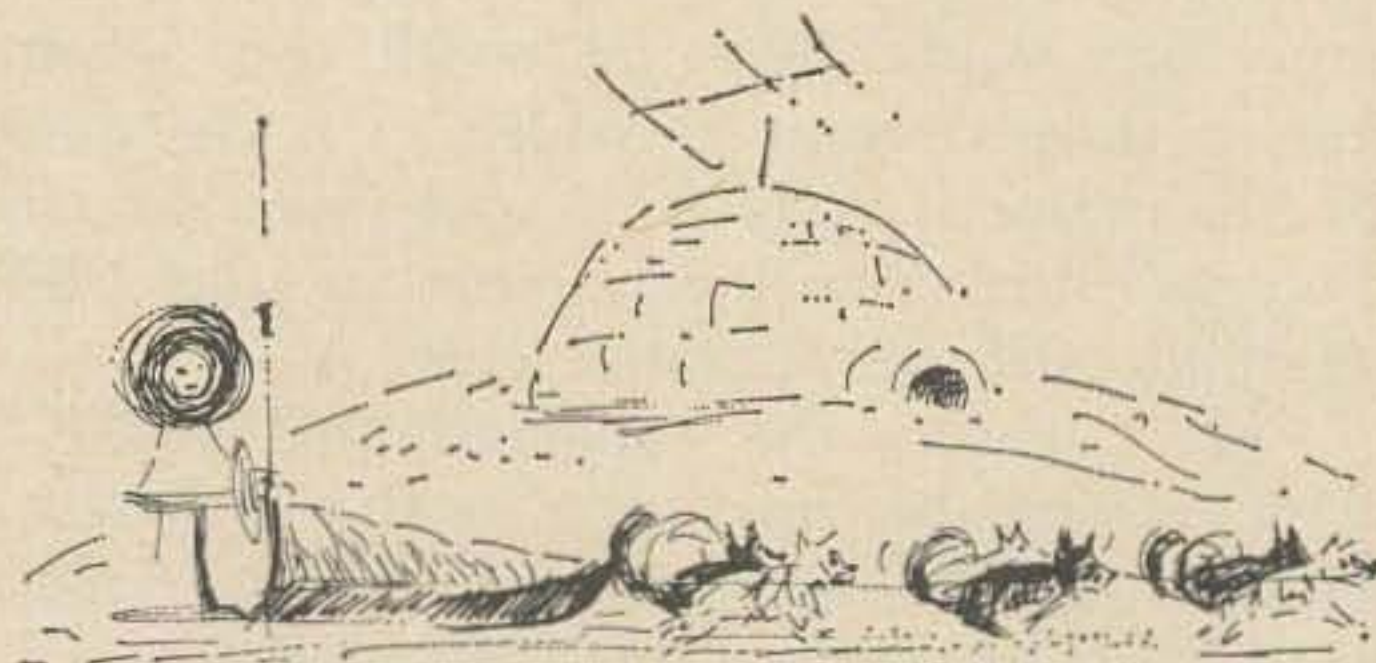- References
- (1) *Specifying FET's*—J. S. Sherwin, Electronics Products, August 1966.
 - (2) *Behavior of Field-Effect Transistor Characteristics With Temperature*—L. J. Sevin, Texas Instruments Application Note, July 1, 1963.



VALUE ENGINEERED

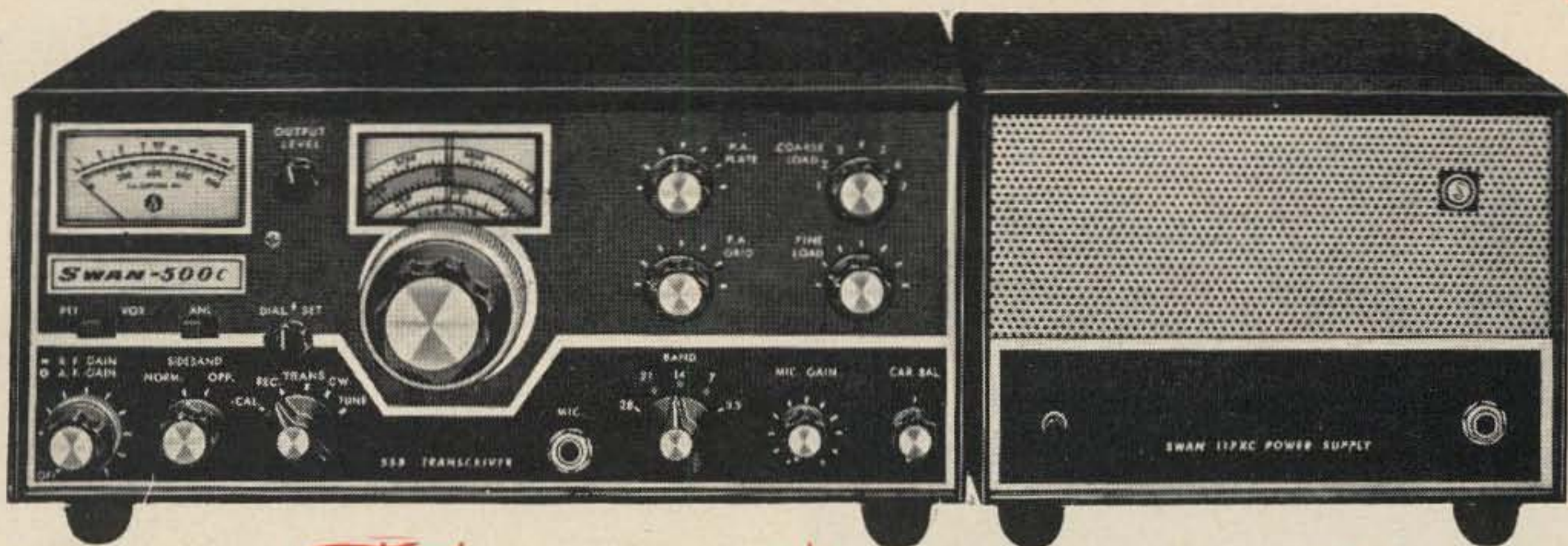

SWAN 500-C

WRITE FOR
SPECIAL HOLIDAY
PACKAGE PRICE!

LIKE NEW TRADE-IN
EQUIPMENT

Ameco	
TX-62	\$79.00
B&W	
5190 & 51SB	\$105.00
Central Electronics	
100V	\$225.00
200V	\$375.00
600L	\$149.00
Model "B"	\$35.00

Clegg	
22'er	\$149.00
Thor 6 with AC/mod.	\$125.00
Collins	
T5A-1 and HC-10	\$115.00
T5A-4 (early)	\$335.00
T5A-4 (late)	\$345.00
T5B-1	\$295.00
T5B-2B	\$425.00
KWM-2 with PM-2	\$795.00

T5B-1 (early)	\$265.00
T5B-2	\$375.00
516P-2	\$115.00
R. L. Drake	
1-A	\$119.00
2-A	\$129.00
2-B	\$159.00
2-BQ	\$29.00
B-4A-Extra	\$295.00
TR-3	\$300.00
AC-3	\$59.00
DC-3	\$79.00
B-4A	\$255.00
Galaxy	
Galaxy 5 Mk II	\$265.00
AC supply	\$59.00
DAC-25 console	\$76.00
Gonset	
G-76, AC, DC	\$99.00
Hallcrafters	
8X-99	\$79.00
8X-100	\$99.00
8X-101 Mk III-A	\$99.00
HT-37	\$175.00
HT-32B	\$245.00
Hammarlund	
HQ-110	\$99.00
HQ-110AC	\$175.00
HQ-180AC	\$249.00
HQ-170	\$139.00
Heathkit	
DX-40	\$29.00
DX-60	\$55.00
HA-10 Linear	\$99.00

HP-23	\$24.00
HR-10	\$45.00
HW-12A	\$79.00
HW-22A	\$79.00
HW-22A	\$79.00
HW-20	\$135.00
VF-1	\$9.50
Johnson	
Viking II	\$59.00
122 VFO	\$9.00
Ranger 1	\$89.00
Vikant 1	\$119.00
Knight	
T-60	\$34.00
B-100A	\$49.00
Thunderbolt 500	\$195.00
National	
NC-155	\$69.00
NC-270	\$89.00
NC-363	\$189.00
NCX-2	\$150.00
NCX-A	\$59.00
Polytronics	
PC-6	\$125.00
Swan	
210	\$149.00
250 (early)	\$235.00
250 (later)	\$275.00
117XC	\$55.00
200	\$345.00
200C & AC	\$495.00
Utica	
850 arrv/VFO	\$89.00
TMC GPR-50 & GSB-1	\$375.50
Thorn KE-50 w/AC, S meter	\$69.00

HIGHEST TRADES! NO ONE ANYWHERE will beat our price! We will **TOP** any advertised or written price from any other dealer. We trade on both new and used equipment and we service what we sell. Instant credit on both new and used equipment. General Electric revolving charge.

AMATEUR - WHOLESALE ELECTRONICS

A DIVISION OF



International Electronic Systems, Inc.

280 ARAGON AVENUE, CORAL GABLES, FLORIDA 33134

305-444-6207 Cable: "INTEL" Export orders our specialty

75 Meter DSB Rig

Allan S. Joffe W3KBM
531 E. Durham Street
Phila., Penna. 19119



After some ten years of absence from the low frequency ham bands in deference to the sun spot cycle and the lack of space for an antenna for other than six and two meters I heard rumors that ten meters was once more opening up. In a fit of wild spending I purchased a Lafayette HA-350 and started listening in on the low bands. Everybody seemed to be running gallons, half gallons and some poor slob's were only using quarter gallons. To me this was very surprising and just a bit painful to contemplate, as in the old days 100 watts was a thing to reckon with. Everybody seemed to be SSB and anyone who was running an "old fashioned" AM rig always seemed to be somewhat apologetic about his behaviour. To be very honest I don't know a thing about the highly refined theory of how the modern SSB rigs work so I promptly subscribed to "73 Magazine" to get a good ham periodical coming once more into the shack. I cracked the *Radio Handbook* and started to read the ads for commercial rigs. The price structure of an outfit I would like to own caused me to review the finances and after rejecting a new mortgage on the family shack I felt that there had to be a home brew means of getting back on the low ham bands without having the SSB boys become unhappy with "another old fashioned ham" on the band.

The answer I turned to was DSB. Sure I would radiate two sidebands, but that tell-

ing tale carrier would be so weak that I would maintain my respectability.

A search of the junk box turned up a couple of 6146 tubes from my old modulator and a husky power transformer from an old TV set. With an assortment of old chassis at my disposal I started to work. The original design called for crystal control but when I went to my friendly ham store and asked for 80 meter phone crystals he looked at me like I was from Mars. He patiently explained that he hadn't had a call for 80 meter phone crystals in seven years. Back to the drawing board. I had heard about the Clapp circuit and all its variations but the good old High C circuit with a 6AG7 was as up to date as I was prepared to be. The VFO was built in a separate 3 by 4 by 5 inch box with heavy components rigidly braced. The main fault of the old High C circuit seemed to be capacitor heating due to the somewhat high circulating tank current. I attempted to avoid this by using four good quality mica's in series parallel in the feedback divider of the oscillator. This plus the lack of heat due to the VFO being in its own box away from all tube heat turned out a VFO that just sits where you set it from a cold start. With a stable VFO under my belt I next turned to an isolating stage between the VFO and the high level balanced modulator. This used another 6AG7 with an untuned or aperiodic grid circuit and a tuned plate circuit. This tuned circuit is a center tapped coil wound on a five inch piece of old broom handle. The coil is shunted by two 220 pF silver micas in series. The variable element is a split stator capacitor (donated by a fellow ham) of 100 pF in each section. The tuning range covers the entire 80 meter band with 10 kHz to spare on each end so there is no chance of accidentally doubling in this stage.

The balanced modulator which feeds the antenna was next. Since the 6146 grids are being fed in push pull the plates have to be tied together to get the carrier eliminated.



tion. The modulator I used was a junk box three watt amplifier with a 6V6 in the output and an output impedance of 8 ohms. After much trial and error I found that feeding the 8 ohm output of this audio amplifier into the six volt winding of a small power transformer whose secondary was 250-0-250 was just the thing to do. Under modulating conditions the amplifier and the transformers are running pretty much unloaded and this can lead to transient difficulties on peaks which earned me a few reports of lousy audio before I found out how to solve the problem. One side of the 8 ohm primary was grounded and about six dB of feedback was introduced into the modulator from the hot side. This feedback from an essentially unloaded winding acts like a peak limiter, in effect up to a point the quality improves with increased output. With this modification to the modulator the "poor audio" reports vanished. A feedback loop within the amplifier did not do the job, it was only when the output transformer was included in the loop that the problem vanished.

Power supplies

The VFO and the buffer are fed from their own 300 volt supply. The particular transformer used measured 300-0-300 and is a conventional full wave condenser input supply using 800 V PIV rectifiers of the bargain type. Notice that the filament winding on this transformer is used only to light a pilot lamp and to operate K-1.

The High Voltage supply for the 6146 high level balanced modulator consists of an old TV transformer which gives 800 volts across the secondary. This feeds a full wave semiconductor bridge and is filtered by three 80 mfd 450 volt electrolytics in series. Each

diode in the bridge is paralleled with a 470 k 1 watt resistor and a 0.01 disc ceramic for voltage division and spike protection. The entire bridge assembly is mounted on a 4 by 4 by ¼ inch plexiglas sheet. Each electrolytic is paralleled with two 47 K 1 watt resistors in series for voltage division and bleeding purposes. This supply delivers about 1100 volts unloaded and about 1000 volts full load. Respect its ability to put you out of this world if you get careless. Notice that the filament winding of this transformer does nothing but light a pilot lamp indicating that the transformer is hot.


As a tribute to modern technology, the low voltage supply boasts a VR-150 to supply regulated voltage to the VFO screen.

All filaments are lit from a separate six volt six amp filament transformer, which same also sports a pilot light showing that the filaments have been energized.

Relay operation

K-1 performs two functions. The first is to cut off screen voltage to the VFO in the receive mode. If this were not done the VFO would continue to operate until the low voltage supply filters had drained down below about 15 volts. The second function is to throw a shunt across the receiver antenna so that on either the "spot" function mode or transmit the receiver is not overpowered with rf. This Relay is a small DPDT 6 volt ac unit.

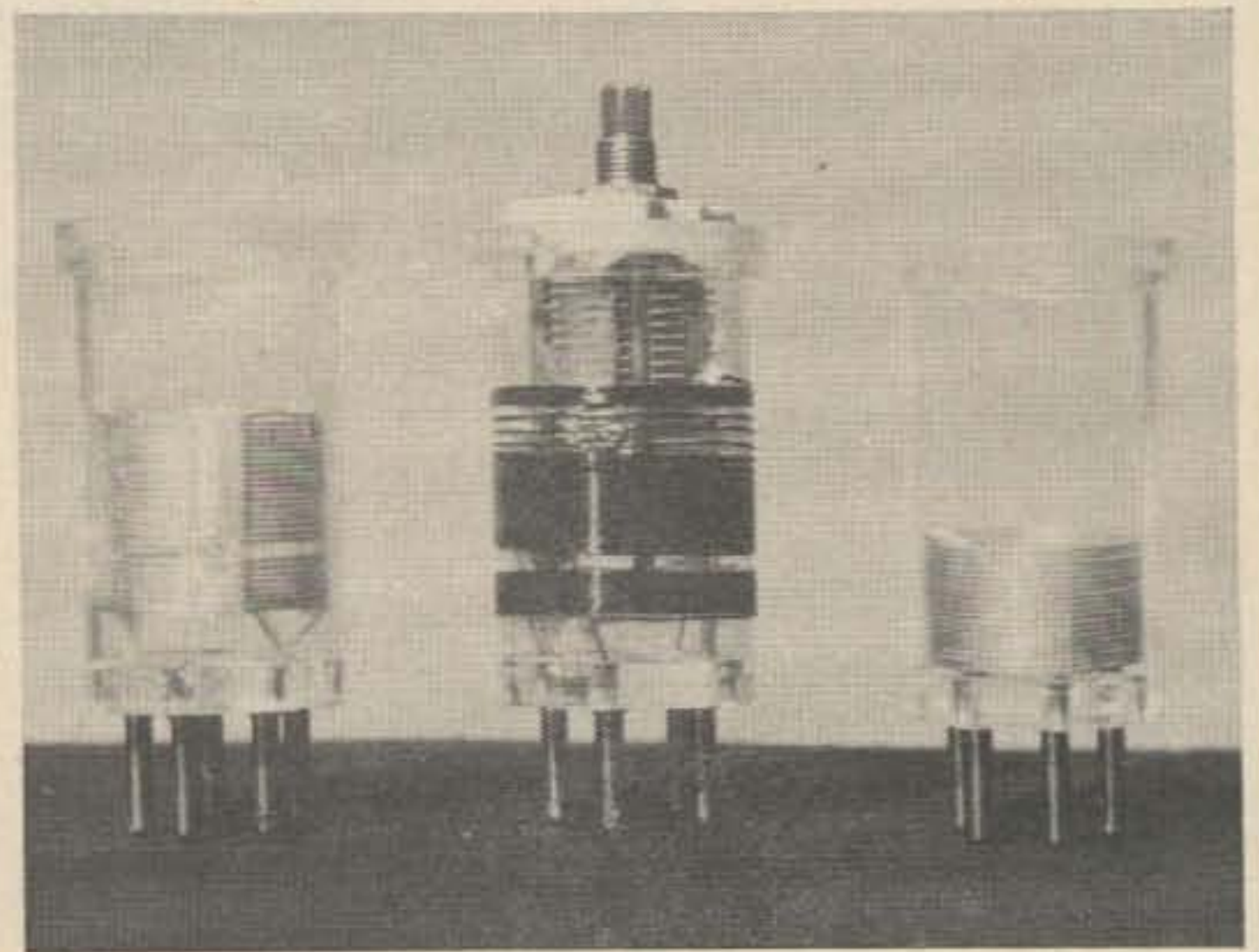K-2 Performs three functions. First, one pair of contacts shunts the send/receive switch of the receiver. Secondly, it transfers the antenna from the transmitter to the receiver. The third function is to complete the ac circuit to the high voltage supply primary, and the low voltage supply primary. The switch that operates this relay is the one designated as transmit/receive. (SW-3).



"It Speaks for Itself..."



BACK IN SEPTEMBER as the deadline approached, we scrapped the copy that had been prepared for this month and instead—because of all the curiosity aroused by our first announcement—we offer you a preview . . .

IT SPEAKS FOR ITSELF!

(Please don't call it a transceiver . . . but that's another subject . . .)

 **signal/one**
A Division of Electronic Communications, Inc.

2200 Anvil Street N. • St. Petersburg, Florida 33710

Spot function

In the spot position of Sw-2 K-2 is bypassed and the low voltage primary is energized. K-1 closes, turning on the VFO and shunting the receiver antenna input. When spotting has been accomplished Sw-2 is returned to the normal position and the low voltage supply is once more under control of the K-2 contacts.

Metering

The final stage is the only stage metered. A nine position two pole rotary switch is used with every other position being blank. This is to get enough physical separation between positions for easy marking of the functions. Each grid current and each cathode current is metered for the final tubes accounting for the first four positions of the switch. The fifth position is used to measure total plate and cathode currents along with the small current through the light bleeder on the HV supply.

Electrically the meter is a 0-1 mil movement with enough series resistance to make it a two volt meter full scale.

The grid currents are read across 200 ohm resistors making the meter approximately 0-10 mA. Each cathode current is read across a 20 ohm resistor making the scale approximately 0-100 mA and the total current is read across a 10 ohm resistor connected between the negative terminal of the bridge and ground. This scale is roughly 0-200 mA. Normal grid current is between three and four mA, normal cathode currents is 12-15 mA with no modulation. Total plate current on voice peaks will hit 60-80 mA on the meter. With steady sine wave input the meter will hit 90-100 plate mils. With this much input the transmitter will fully light a 75 watt lamp used as a dummy load. Actually it's a pretty bright 75 watts but this is subjective and not very scientific so use your imagination.

The only mildly critical thing about the metering set-up is to try to get the two grid current metering resistors as close as possible in value. This will help in balancing the modulator as we shall see later on.

Tune Up from a cold cold start

Plug in the ac cord, cross your fingers and turn on the filament switch (Sw-1) Throw Sw-2 to spot which will turn on both the


VFO and the buffer. Tune in the VFO signal on the receiver and set the slug in the coil so that the upper and lower limits of frequency are those that you desire. The prototype hit the upper band limit with the slug almost all the way out of the coil. The phone band covered 80 divisions of the 100 division dial.

Turn the meter to check for final grid current. If you are unusually lucky the currents will be equal but the odds are quite against it. The small 3-20 pF trimmer across the grid tank should be adjusted to make the grid currents equal. Depending on your own physical layout as it affects the capacity balance of the grid tank you have to experiment with which side of the coil the trimmer has to go to be most effective. You only have two choices so it's no big deal to get the right position. Once you have the grid currents balanced the cathode currents may be checked for curiosity but their balance is generally more indicative of the shape the tubes are in than anything else and the readings are not critical as long as they are within 10-20% of each other. Restore Sw-2 to its "normal" position which is opposite to the "spot" position. Connect a 75 watt lamp as a dummy load and plug the modulator into the rig.

Throw Sw-3 to Xmit and recheck the grid current. Using the grid tuning as an excitation control set the grid currents for about 4 mA.

Put some sort of a sine wave signal into the modulator (steal some filament ac thru a resistor if you don't possess an audio generator) and crank up the gain a bit. Put the meter on the plate current position and goose up the audio until it shows about 30 mA. Tune the Pi input condenser for plate dip and the output condenser for maximum output as shown by the bulb load. Then crank up the modulator until the plate current rises to about 80-100 mils. Retune the final tank condensers and if all is well your 75 watt bulb should be glowing with a nearly blinding iridescence. Disconnect the rig and install the mike into the modulator. Talk into the mike and observe the action of the plate meter. A full whistle will make the meter and the bulb agree that power is being produced. It will also show you that only a professional liar could look at the plate meter under modulation and guess what the input power is. On a rough basis the peak plate current is about 60% over what the meter

Patience.

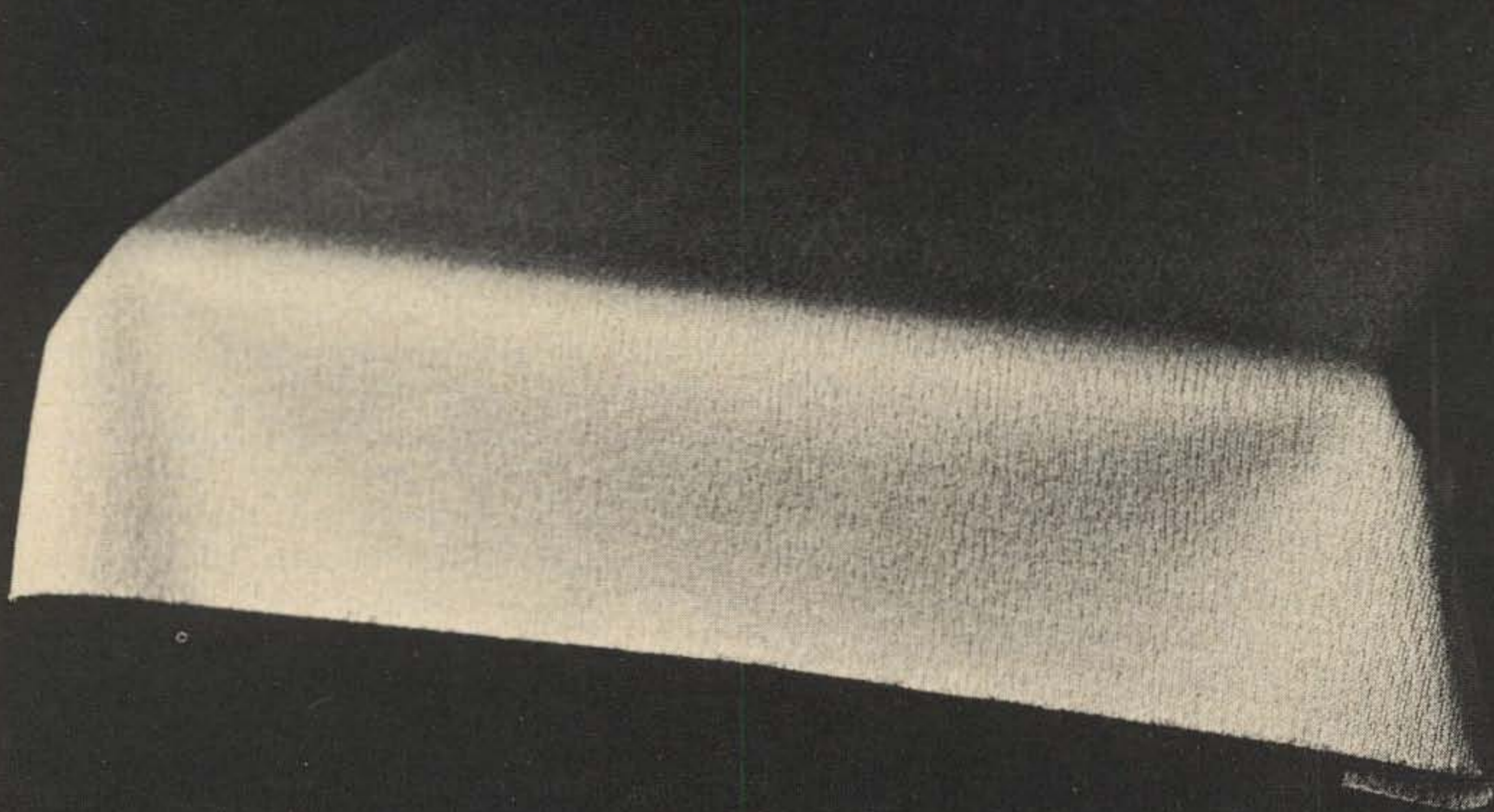

Just because it's Christmas, don't make a hasty move. Like spending \$650 on a receiver that will be obsolete in January.

And the receiver you buy today will be obsolete in thirty days. Because that's when Davco Electronics will again revolutionize the amateur radio industry with the unveiling of the DR-50 solid state receiver.

The DR-50 has an integrated circuit IF strip which includes two mechanical filters. It features a built-in AC or DC power supply, a built-in speaker, a linear slide rule dial, a positive acting noise blanker, and weighs in at only nine pounds.

Have patience. It could be your best Christmas ever.

DAVCO

ELECTRONICS, INC.

P.O. Box 2677

Tallahassee, Florida 32304

sluggishly shows. With a convenient 1000 volts on the plate which makes each input mil an input watt (isn't that convenient) you can questimate to your hearts content what your power input is. What really counts is the other guys receiver combined with your consumate operating skill to make a successful contact.

Making a bulb light up is one thing but getting the soup into the antenna is something else. My own personal antenna for 80 meters is 180 feet of wire that goes from the cellar back to the garage, over the garage roof and back to the old apple tree. Since the Pi net won't match the wild blue yonder impedances of this lash-up (apple trees have very high impedance when used as antenna terminations) I feed the Pi output into an L section, which consists of about thirty turns of #18 wire close wound on a scott towel core followed by a shunt variable of about 200 pF. This lets me feed my long wire in good style. A true space age rf tuning and modulated rf output indicator consists of an NE-2 with a 47 K series resistor shunted across the L section condenser to ground. This little blinking light never fails to impress visitors to the shack much more than the miracle of ham radio communication, the unanimous never varying comment being "ooooh look, that little light blinks when you talk.

Most articles end just about here because the writer has just torn up the tenth rewrite and snarled at his wife and kids for some peace and quiet. The end result is that some things meant for inclusion never get included much to the discomforture of the innocent reader who promptly damns the publisher. Take heart and read on.

Little things that count

If the plate meter is watched carefully as you switch from receive to transmit you will see it bounce to full scale before it settles down to normal readings. This is normal as it is the result of filter charging current.

If you hear a sort of gargling sound in your receiver as you switch from transmit to receive your own particular VR tube may be at odds with the world. Don't throw it out. Just ground the unused contact on K-1 that is on the B plus switching side. This will cure the problem. Personally I like the sound so I took the ground off after I learned it would cure the trouble.

During the spot function you may notice some modulation on your signal if someone happens to talk in the shack and the mike gain is up. This is normal. The rf to the grids of the final is being modulated by the audio getting to the screens.

Also regarding the spot function. You may find that having the oscillator and the buffer on during "spot" is just too much rf floating around for your particular receiver. Notice that Sw-2 calls for a DPDT switch but the schematic shows only one set of contacts being used, namely those associated with the low voltage xfmr primary. If you are troubled by excess spot rf simply wire the unused contacts of this switch so that the buffer plate and screen gets no B plus in the spot function mode. If you wire the rig in this manner don't forget to short out the switch connections during the initial first tune up or you will not be able to check the grid drive and set the grid balance as described earlier. After this balance is set remove the shunt from the switch and you are in business.

Make sure that the modulator you use will give a good three watts of clean audio measured into a resistive load. If you do this and troubles arise you can be sure that it is not "Modulator power." It helps greatly to tailor the audio response of the modulator. Ideally it should be well down by 250 cycles and roll off pretty well by 4500-5000 cycles. If somebody says you sound mushy it means you forgot something. What you forgot is that the screen bypasses in the final are across the high impedance winding of the modulator secondary. Do your high frequency roll off correcting with these shunt condensers in mind and you won't get a "mushy" report.

The VFO inductor utilized a national XR-50 slug tuned coil form wound full of #20 plastic insulated hook up wire. This may cause some consternation from the purist to use such wire for a VFO inductor, all I can say is it works just fine.

The Final tank inductor is in reality a part from an ARC-5. It is a winding as described, wound on a beautiful ribbed ceramic form. It cost all of forty cents at Fertik Electronics, 9th & Tioga streets here in Philadelphia.


The three pole double throw 115 volt ac relay came from the same place with a \$1.50 price tag. Naturally you can substitute other coil voltages depending on your junk box.

The virtue of the control set-up as described is that there is but one switch to throw in going from transmit to receive.

This little rig puts out a clean DSB signal. It has given no TVI trouble although I do make it through the little 5 tube acdc cracker box in the kitchen, a la donald duck. The low frequency bands have changed greatly in the last ten years but some things never change. If you have some guy running a gallon on your frequency, you lose. However, intelligent listening, picking your spot, plus a good receiver and a fair amount of good old fashioned ham courtesy will let you make many enjoyable contacts with this rig. Happy DSB.

... W3KBM

Controlling the Linear Changeover Relay

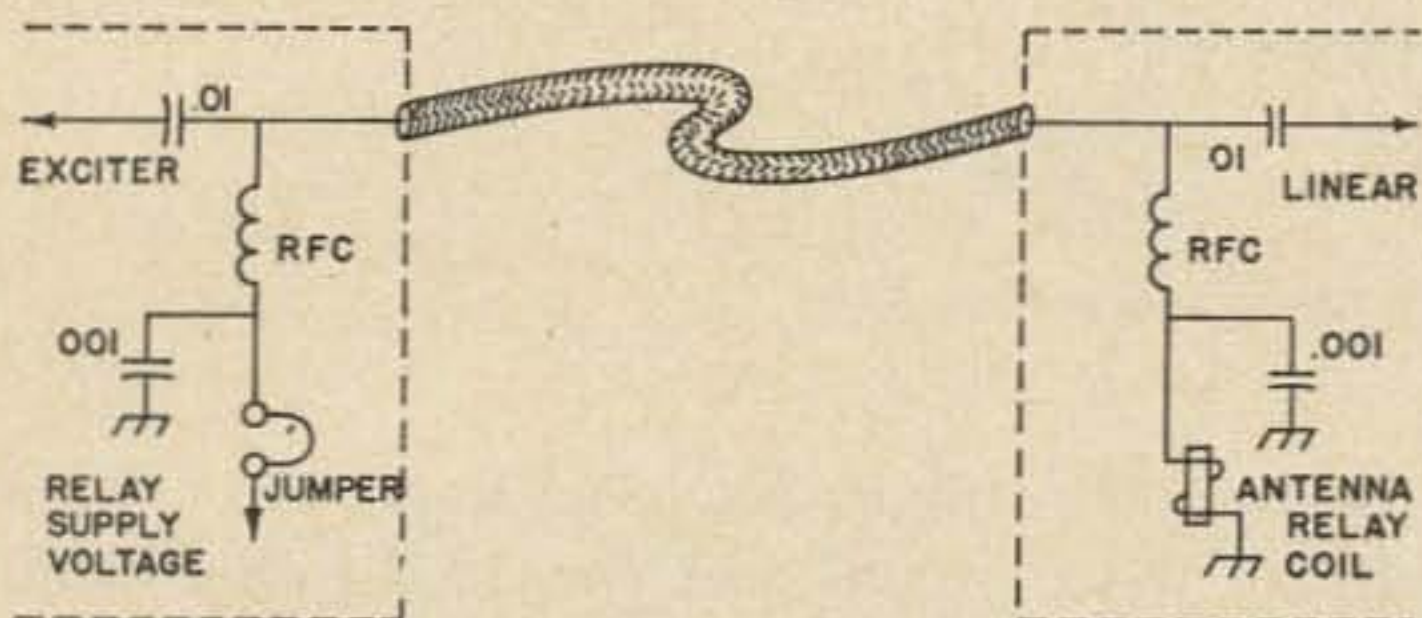

One of the design considerations faced by the builder of a linear amplifier is how to activate the antenna changeover relay within the linear.

It can be done directly with a switch or in a more elaborate manner with an *rf*-biased tube with a control relay in the plate circuit.

The system shown here, particularly useful in connection with a mobile truck-mounted linear amplifier, impresses the relay control current onto the coax link between the exciter and the final right along with the *rf*.

.01 dc isolating capacitors must be used at either end of the line as shown, if not already present. The *rf* chokes can be almost any variety that will safely handle the relay current, since the *rf* voltage is low on a low impedance line and hence not very demanding on the characteristics of the chokes used.

A removable jumper or a switch must be used at the exciter end to disconnect the relay supply voltage when the exciter is used to drive an antenna directly.

R. B. Kuehn WØHKF

SPECIAL TV CAMERA PARTS KIT

ONLY

\$99.95

including vidicon and lens!

To meet the many requests for a low-priced solid state TV camera kit, we have made available from our factory stock the following parts which you can assemble at very little additional expense into a superb TV camera. Included in the kit are the following:

1) **Completely assembled and tested video amplifier plug-in circuit board with a 10-transistor 6 MHz bandwidth amplifier and keyed clamp with adjustable pedestal and sync mixer.**

2) **Completely assembled plug-in sweep circuit board with 8 transistor and 5 diode horizontal and vertical sweep generators and amplifiers featuring excellent linearity and more than enough drive for 1" vidicons.**

3) **Excellent quality deflection yoke and focus coil with beam alignment magnets and raster positioning adjustment. Also included is the vidicon tube clamp and target connector.**

4) **Camera tested vidicon excellent for amateur use and matched to the deflection assembly above.**

5) **Good quality F1.9 or better achromatic lens with matching lens mount.**

Note: All items are brand new except vidicons which we guarantee will work with the parts kit supplied when assembled according to the schematic and adjusted according to normal procedure. Since step-by-step instructions are not available, we recommend this kit only to those who can follow a schematic.

Due to the low price and limited quantity, we cannot sell the above components separately.

When our present stock is exhausted, it will cost at least \$160.00 to repeat this offer. Order now to avoid disappointment.

VANGUARD LABS

Dept. H

196-23 Jamaica Ave., Hollis, NY 11423

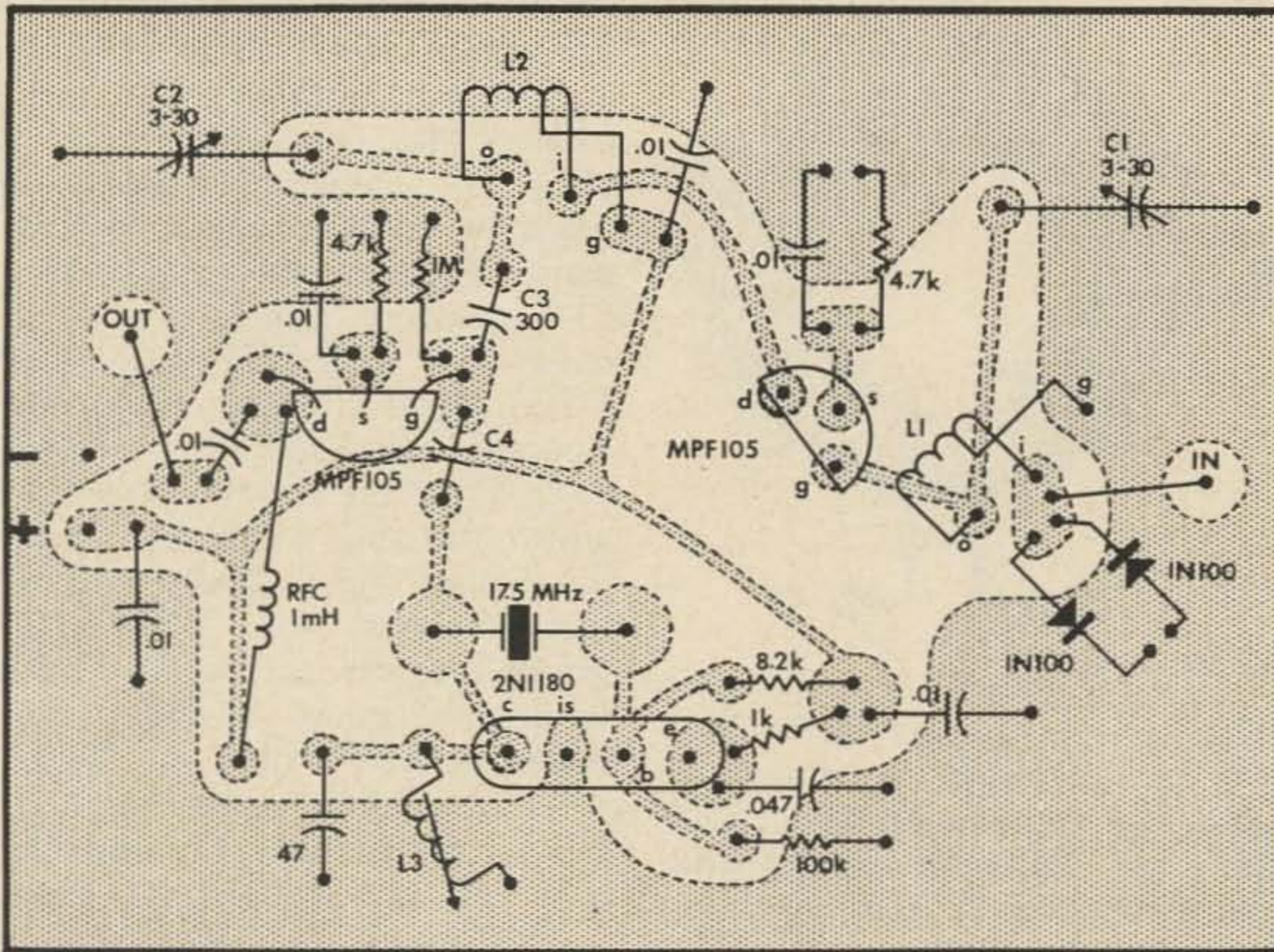


Fig. 2. Component side of the printed circuit board for the Novice converter.

Three models of the converter were made using conventional air-core coils and all were unstable to a degree, even with shielding.

A pair of 1N100 diodes is connected across the converter input to prevent excessive voltages from being applied to the first FET when the station transmitter is on the air.³ A socket is provided for this FET to facilitate replacement, if necessary.

Coil data

- C₄—two 2-inch lengths of insulated hookup wire twisted together.
- L₁—23 turns no. 24 enamel wire, tapped at 4 turns, on 1/2-inch O.D., 5/16-inch I.D., 3/16-inch long powdered-iron toroid core. (Ami-Tron Associates T-50-2 Red).
- L₂—21 turns no. 24 enamel wire, tapped at 4 turns, on same type form as L₁
- L₃—25 turns no. 30 enamel wire, close-wound on 1/4-inch diam. iron slug tuned form (Miller 20A000RBI usable).

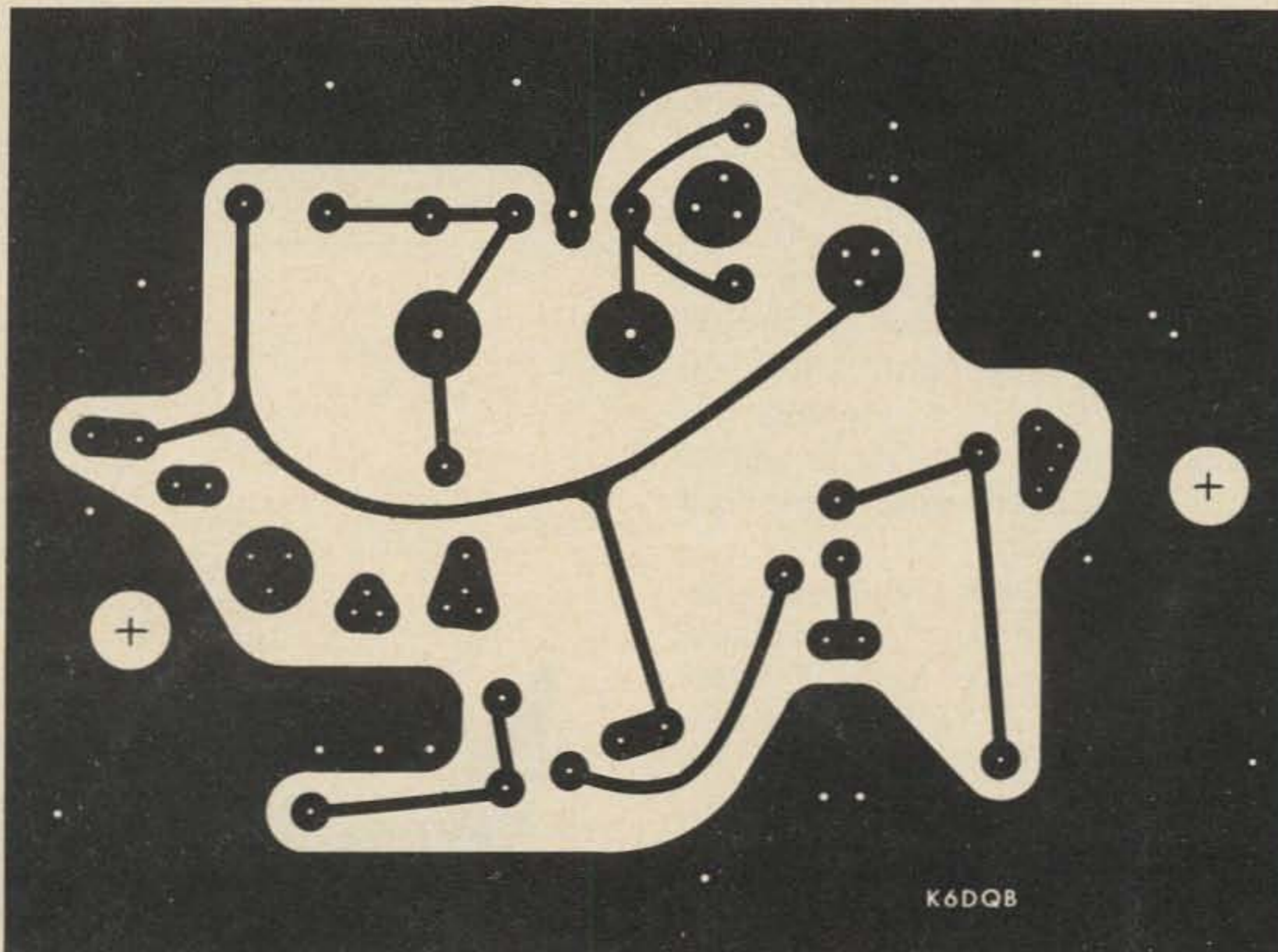


Fig. 3. Copper foil side of the printed circuit board for the Novice converter.

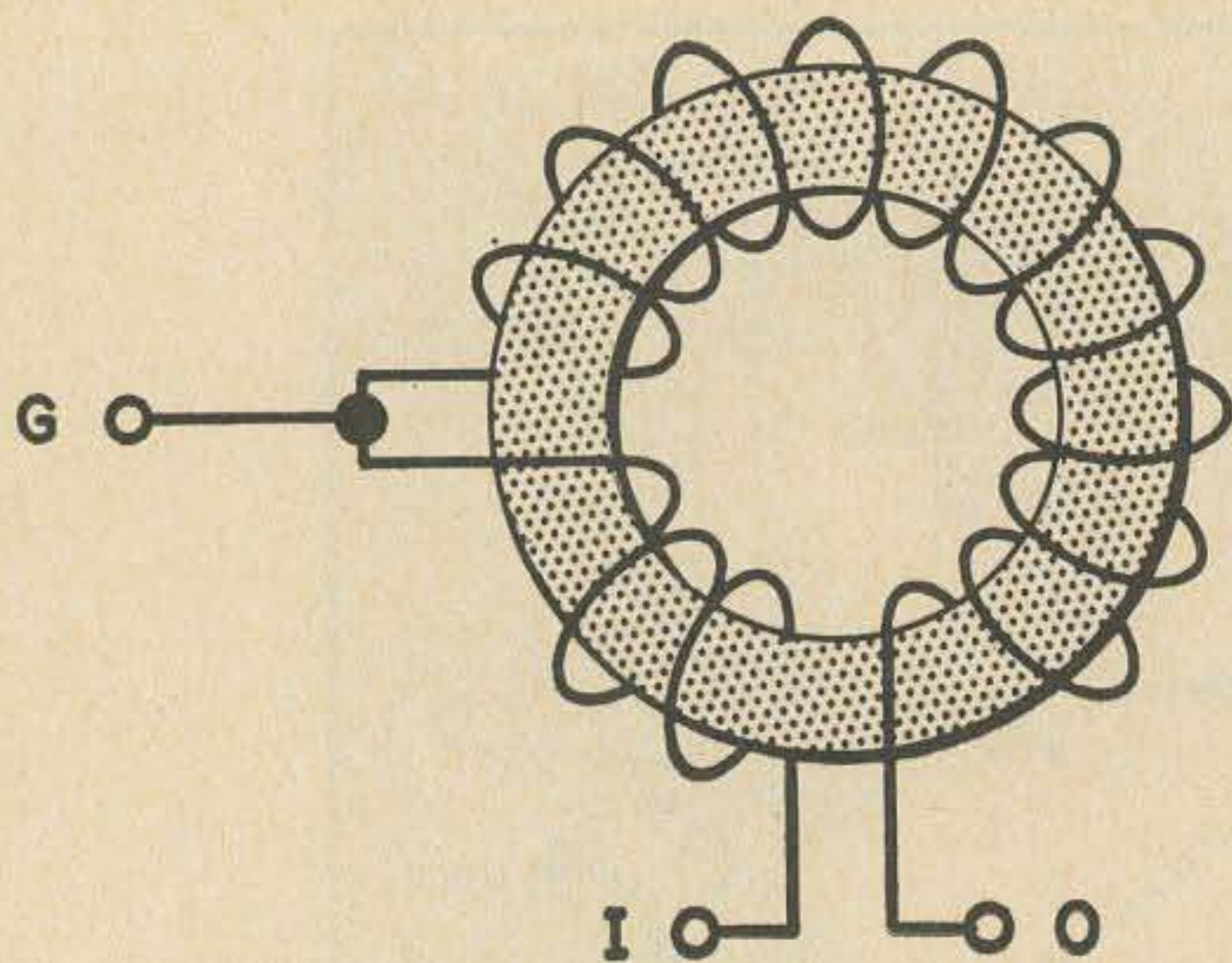


Fig. 4. Detail of the toroid.

The converter is constructed on a 3 x 4 inch printed circuit board as shown in the photograph. The component layout and masking pattern are shown in Figs. 2 and 3. The author used an E-Z Etch kit from Ami-Tron Associates⁴ which contained a 4 x 6 inch board, etchant powder, and masking material. The board was cut in half and etched with half the etchant supplied. Although the kit provides ample masking material for making narrow lines and small circles, there is no provision for masking the large solid areas at the edges of the board. A heavy coat of fingernail polish makes an acceptable mask for this purpose and can be removed with polish remover or steel wool after etching is complete.

The tuned circuit inductors are wound on toroid cores which were also obtained from Ami-Tron. A convenient method for tapping the coils is shown in Fig. 4. Starting with the input (I) lead, add turns until the tapped turn is reached. Form the wire into a U on the outside of the toroid and twist the sides of the U together. Scrape away the enamel at the bottom of the U (but do not break the wire) and solder on the ground (G) lead. Continue winding until the required number of turns is in place. The turns should be spaced around the full circumference of the toroid.

The transistors and diodes should be the last components to be soldered to the board as they are quite susceptible to heat damage. As a transistor or diode lead is soldered to the board, it should be held firmly by a pair of long nose pliers on the component side of the board. The pliers will act as a heat sink and protect the device.

After the converter is completed, check the foil side of the board for accidental shorts,


poor connections, and the like. When all is in order, insert the 17.5 MHz crystal and the *rf* amplifier FET in their sockets, connect the converter to an antenna and 80 Meter receiver, and apply power. *Never insert or remove transistors with power applied.* Tighten the screws in C_1 and C_2 . If no Novice signals are heard when the receiver is tuned between 3.60 and 3.75 MHz, adjust the slug in L_3 until they are. Tune in a weak 15 Meter Novice signal near 3.65 MHz on the 80 Meter receiver and adjust the slug in L_3 and the screw in C_1 for loudest signal. Then tune in a 15 Meter Novice signal near 3.70 MHz on the 80 Meter receiver and adjust the screw in C_2 for loudest signal. If either signal is loudest when the screw of C_1 or C_2 is fully clockwise (maximum capacity), add a turn or two to the output (O) end of the appropriate coil and readjust the capacitor.

The author has no means by which to quantitatively evaluate cross-modulation susceptibility, but the converter seems to perform well in that respect. Its sensitivity is about the same as that of the 'authors' 10-20 Meter FET converter of similar design. For a \$15 investment (if all parts are purchased new), it gives a good account of itself.

... K6DQB


Bibliography

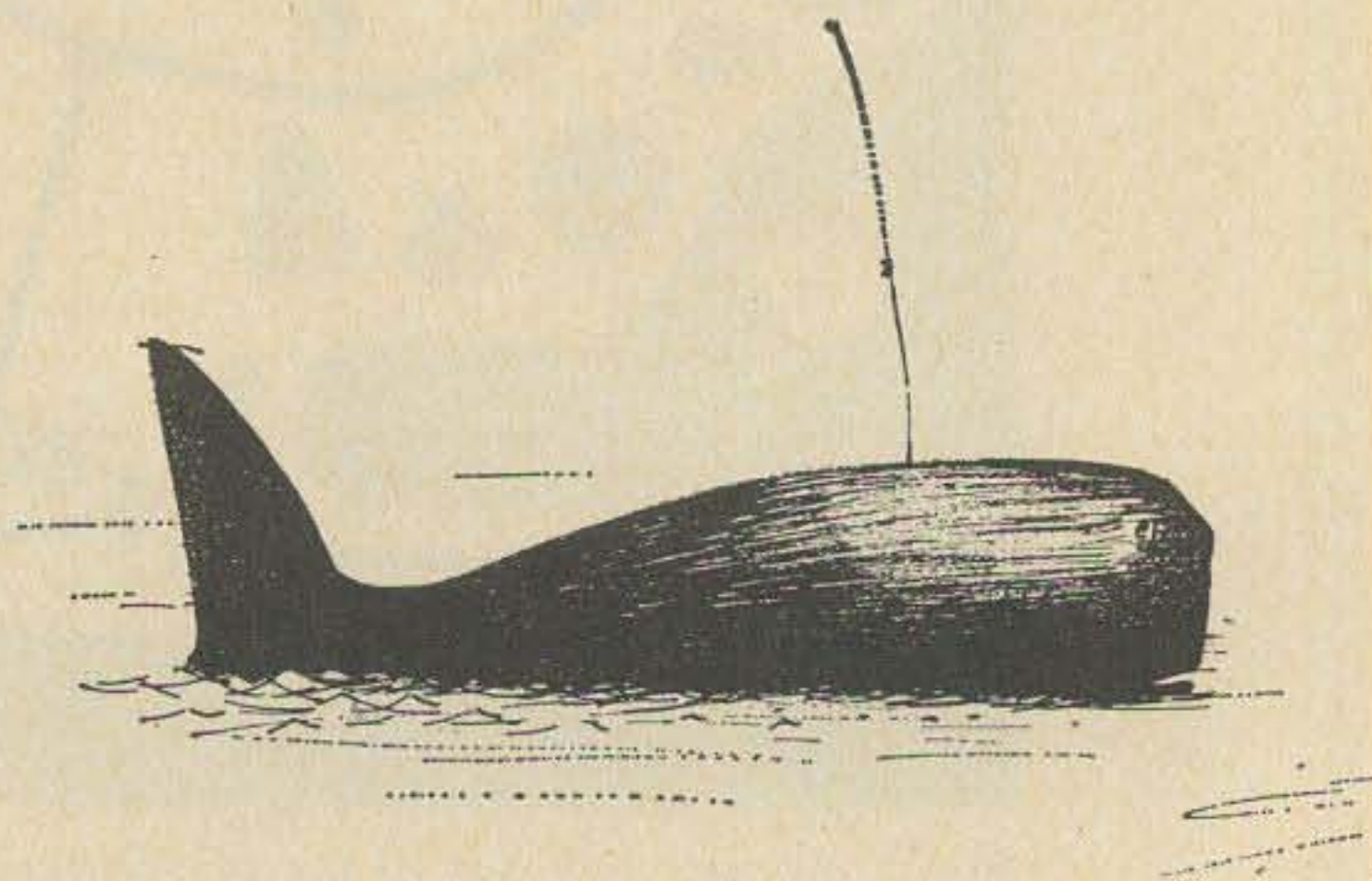1. Creason, *A Field Effect Transistor Converter For 10, 15 and 20 Meters*, 73, May, 1967.
2. Creason, *A Field Effect Transistor Converter For 40 and 160 Meters*, 73.
3. Jones, *Using Low Cost FET's on Six*, 73, February, 1967.
4. Ami-Tron Associates, 12033 Otsego St., North Hollywood, Calif., 91607. The 1-board E-Z Etch kit sells for \$3.49, the T-50-2 Red toroid core for \$0.45.






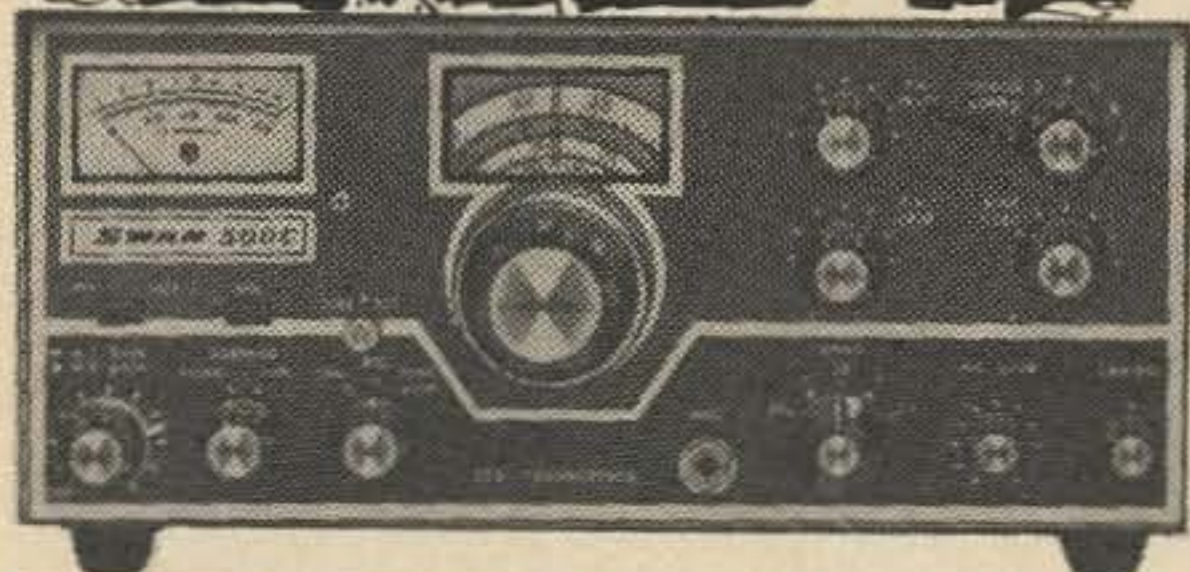Open the best on Christmas Day (or any other day)... a Swan transceiver from Henry Radio



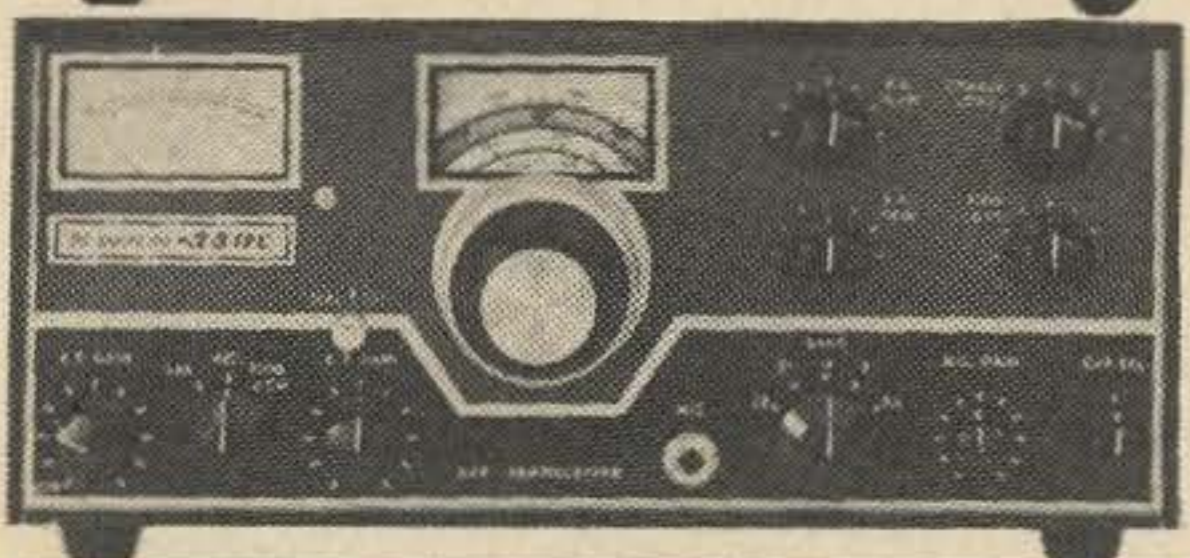MODEL 500C A complete SSB-AM-CW transceiver. Five bands, 520 watts . . . for home station, mobile and portable operation. Voice quality, performance and reliability are in the Swan tradition of being second to none. **\$520.00**



MODEL 350C An improved version of the classic Model 350. An SSB-CW-AM transceiver, featuring 5 bands, 520 watts SSB P.E.P. input. Ideal for home station, mobile or portable operation. Dependable and loaded with worthwhile features. **\$420.00**



MODEL 250C The newest member of the Swan family. A full 6 meter SSB-AM-CW transceiver. 240 watts P.E.P. input, selectable sideband, built-in 250 kc calibrator . . . plus many more worth-while features. **\$420.00**



MODEL TV-2 2 meter single sideband, 144-148 mc 240 watts P.E.P. input. The new Swan TV-2 transverter is a superb receiving and transmitting converter for the 2 meter band, designed to operate with most Swan transceivers. **\$295.00**

Henry Radio and Swan, long a great team and old time friends of Hams the world over, presents a choice of transceivers to fill the heart of any amateur with joy. There is no better time to buy than now and, of course, the very best place to shop is Henry Radio. At Henry Radio you can compare makes and models from exceptionally large stocks. You can trade in your old equipment and take advantage of our generous terms.

Exports! Of course, Henry Radio makes it simple for amateurs around the world to own the finest American radio equipment. Write for details.



CALL DIRECT . . . USE AREA CODE

Butler, Missouri, 64730	816 679-3127
11240 W. Olympic, Los Angeles, Calif., 90064	213 477-6701
931 N. Euclid, Anaheim, Calif., 92801	714 772-9200

"World's Largest Distributor of Amateur Radio Equipment"

Transceiver Review



Heathkit SB-101

Heath is producing a sizable line of transceivers, and at the top of the pile we find their SB-101 transceiver tuning all ham bands over 80 thru 10 meters. It goes in a case 14 $\frac{7}{8}$ " x 6 $\frac{5}{8}$ " by 13 $\frac{3}{8}$ " deep, and weighs 17 $\frac{1}{2}$ pounds. The kit comes for \$340, or you can purchase it assembled for \$540. An external power supply is required priced at \$64.95 for the mobile 12-volt supply or \$49.95 for the ac supply.

Tuning ranges and stability are guaranteed by Heath's preassembled Linear Master Oscillator. Receiver sensitivity is better than 0.5 microvolt for 10 db. signal-plus-noise to noise ratio in sideband operation. Sideband selectivity is 2.1 kHz at minus 6 db., 5 kHz at minus 60 db. for a 2:1 shape factor. An optional filter is available for CW work offering 400 Hz bandwidth at minus 6 db. and 2.0 KHz at minus 60 db. When this filter is installed a choice of filters is available from the front panel.

Transmitter final power input is 180 watts PEP continuous voice, or 170 watts CW at a 50% duty cycle. RF power output is 100 watts to a 50 ohm nonreactive load on 80 thru 15 meters, down to 80 watts on 10 meters.

Transmit-receive control is PTT or VOX on sideband, keyed-tone VOX on CW. A CW sidetone is available to speaker or phones when operating CW.

Heathkit HW-100

Heath's Single-Banders have been extremely popular and several conversion articles have appeared describing modifications for greater utility. Seeing the writing on the

wall, Heath has recently introduced a 5-band version of their Monobanders, with a few trimmings thrown in from their more expensive SB-101A rig. The economical design methods and use of already-available engineering components have held the price down to \$240 for a really versatile piece of gear.

The HW-100 weighs under 18 pounds, uses a Monobander power supply to run 180 watts PEP sideband or 170 watts CW. Operating range is 80 thru 10 meters in five bands, and frequency stability is less than 100 Hz per drift after warmup or for plus/minus 10% line voltage drift. Sensitivity is better than 0.5 microvolts for 10 db signal




to noise ratio, and filter bandwidth is 2.1 kHz at minus 6 db, 7 kHz at minus 60 db.

Heathkit HW-12A, HW-22A, HW-32A.

Shown above is Heath's HW-12A, one of three 200 watt PEP single-band transceivers that have been very popular over several years. All are designed to use the same stable low-frequency VFO, tuning from 1.5 to 1.8 MHz, and in their latest form all offer a choice of upper or lower sideband. Size is 6 $\frac{1}{4}$ " x 12 $\frac{1}{4}$ " by 10" deep, weight 15 pounds for all models.

Separate power supplies are required, and these are available for ac operation, or for dc mobile application.

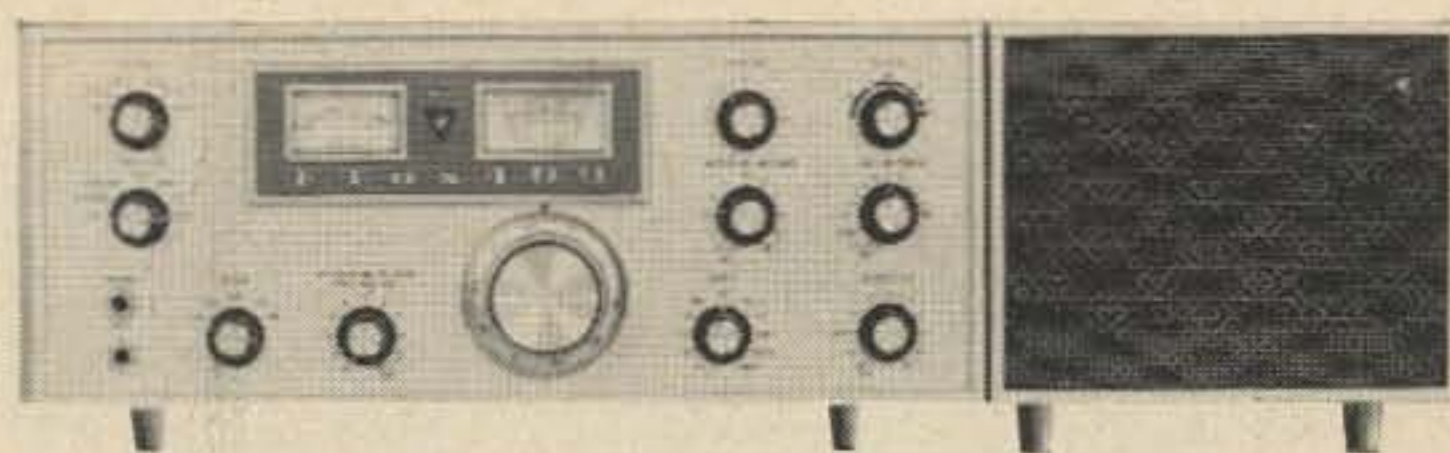Receiver sensitivity is 1 microvolt for 15 db signal to noise ratio, audio output 1 watt into 8 ohms. Drift is 200 Hz per hour after warmup, selectivity fixed by a crystal lattice bandpass filter. Carrier and unwanted sideband suppression is 45 db. HW-12A, \$99.95; HW-22A, \$104.95; HW-32A, \$104.95.



YAESU FTdx 400

A recent arrival from Japan, the FTdx 400 transceiver was planned and designed for the American amateur utilizing standard locally-available parts. It covers the bands 80 thru 10 meters, with provision for three additional 500 KHz receiver bands. Frequency stability is better than 100 Hz drift per 30 minutes after warmup.

The transmitter is rated at 500 watts PEP sideband, 440 watts CW or 125 watts AM. This transceiver has a built-in power supply, which must be a pretty good one because although the transceiver is not notably larger than others it is considerably heavier: it weighs 50 pounds. Its cabinet size is 15 $\frac{1}{4}$ " x 6 $\frac{1}{4}$ " by 13 $\frac{3}{4}$ " deep.

Receiver sensitivity is 0.5 microvolt for 20 db. signal to noise ratio on 14 MHz sideband. Bandwidth is 2.3 KHz at minus 6 db. and 3.7 KHz at minus 55 db. with IF and RF images better than 50 db. down. Audio output is 1 watt at 5% distortion, and frequency stability is less than 100 Hz drift per 30 minutes after warmup.

Active elements are present in unusual profusion. The Yaesu transceiver uses 18 tubes, which is about average, but it also has 42 additional semiconductors in a hybrid circuit, designed to make the most effective use of both tubes and semiconductors. One unusual feature is calibration points at 25 KHz intervals as well as 100 KHz points, with vernier dial accuracy specified as better than 500 Hz when calibrated at the nearest 25 KHz point.

Any units not shown in this review are not due to lack of editorial interest, but because the manufacturer did not send us information.




SB-34

The SB-34 is unlike most transceivers in having a built-in power supply. And the supply is a universal type, which will operate from either a 12 volt battery or from 117 VAC. The only revision required is a change of leads. And for mobile operation the SB-34 has a low-drain standby setting which turns off the transmitter tube filaments and some other circuitry to reduce car battery drain to $\frac{1}{2}$ ampere.

Frequency coverage is 3.775 to 4.025, 7.050 to 7.300, 14.100 to 14.350 and 21.200 to 21.450 kHz, with 1 KHz divisions on all bands. Selectable upper or lower sidebands, three IF's with a collins Mechanical Filter on 455KHz.

Case size is 5" x 11 $\frac{1}{4}$ " by 10" deep, weight 19 pounds. The transmitter PEP input is 135 watts to two 6GB5's, and drift is under 100 Hz per 30 minutes under normal ambient conditions.

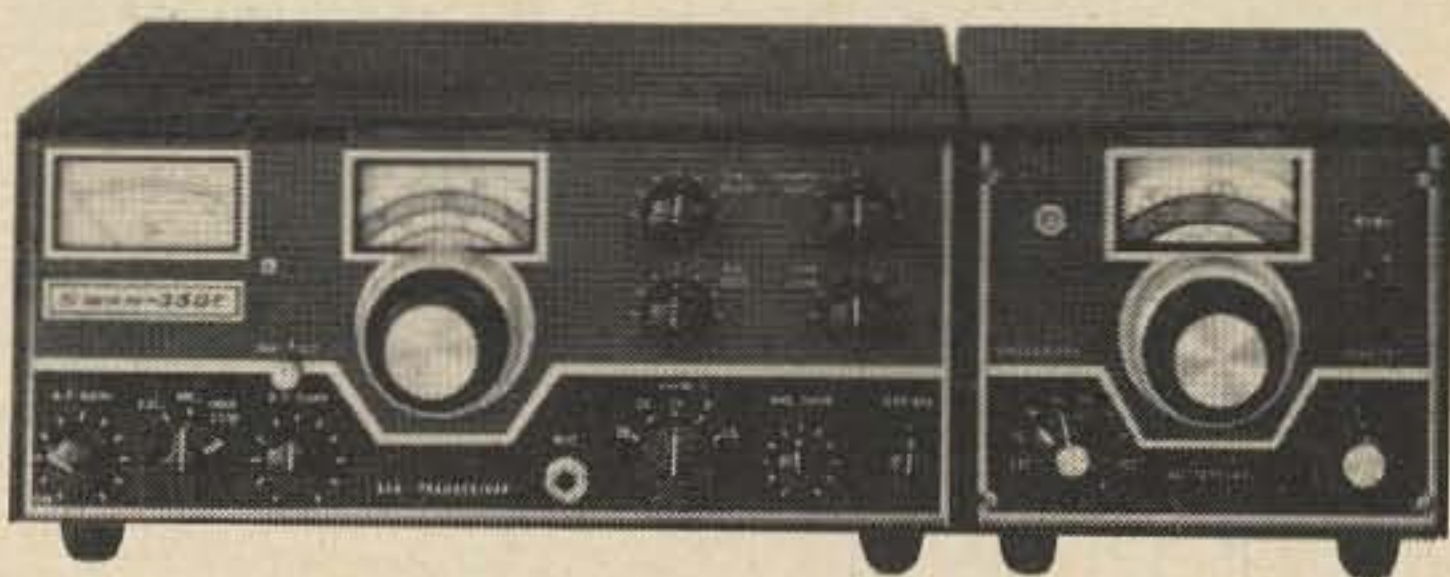

SWAN 350C


Looking at the model designation you might believe the Swan 350C is rated at 350 watts somehow. Actual ratings are 520 watts PEP sideband input on all bands, 360 watts CW and 125 Watts AM SSB plus carrier.)

Receiver sensitivity is better than 0.5 microvolt for 10 db signal-plus-noise to noise, with audio output rated at up to 4 watts into a 3.2 ohm load. Filter specs are 2.7 kHz at minus 6 db, 4.6 kHz at minus 60 db, and ultimate rejection better than 100 db.

The tuning range is 80 thru 10 meters in five bands. Metering checks PA cathode current to 800 mA on transmit, with the same meter indicating up to 70 db over S9 on receive.

Swan's Operation & Maintenance manual contains some very nice material about sideband theory and operation, and includes some useful information. For instance, if a sideband signal is transreceived at 20 db over S9 and the unwanted sideband is suppressed 50 db (Swan's spec for their 350C) the unwanted sideband will be audible at about S5. The manual is a strong sales point for the transceiver. Price: \$420.00.

A power supply with speaker is available for 117 vac operation, at \$105, or for 230 volt operation at \$115. Another supply without speaker is available for \$65. For dc mobile operation an ac supply can be used with Swan's Converter Module, at \$65, or the ac supply can be left in the house and the Swan operated from a complete 12 vdc supply costing \$130. The new 500-C Swan described below uses the same power supplies as the 350C.

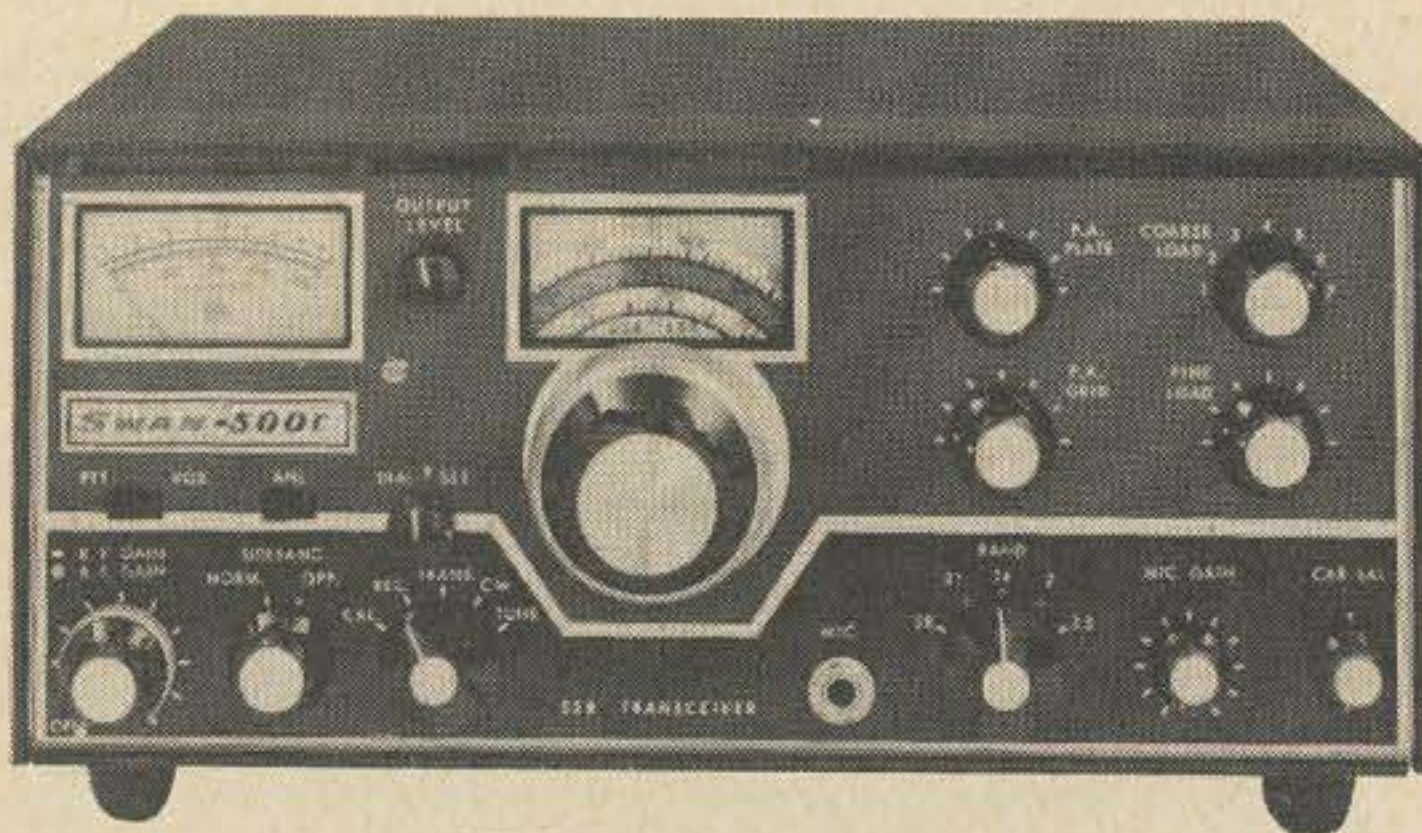

SWAN 500C

The new Swan 500C is similar to the 350C, but has been refined by the introduction of a pair of RCA's 6LQ6's, development of the drive mechanism, a new *if* frequency of 5.5 MHz, and an increased number of tuned circuits in the receiver. All this has upped the price from the 350C's \$420 (the 350C is still in production) to \$520 for the improved model.

General technical specifications remain about the same, but Swan mentions the new 6LQ6 final can usually get up to 570 watts before flat-topping. Also, the new Swan has acquired a number of additional diodes and two new tubes. One of these is a 100 kHz crystal calibrator, optional in the 350C. The new panel suggests other changes not mentioned in the manufacturer's literature.



Hallicrafters SR-400

Hallicrafters' SR-400 contains some interesting ideas in transceiver design. For instance, it has a noise blanker circuit that turns off the receiver *if* when noise pulses exceed a given level. This prevents overloading and blocking, allowing the *if* to return to operational condition in far less time than would be required for an overloaded circuit to recover.

The SR-400 comes in a 16½" x 7¼" x 15" deep case. Power supply is external, and may be Hallicrafters' PS-500 supply containing a loudspeaker, or a dc supply operating off 11 to 16 volts for mobile operation.

Transmitter linear power input is 400 watts PEP on sideband, or 360 watts maximum for CW. Distortion products are down 30 db minimum, carrier and spurious emissions 50 db below rated PEP output. An 800 Hz sidetone oscillator is provided for CW monitoring.

Tuning ranges cover 80 thru 10 meters in eight 500 kHz bands, with the variable-tuning portion of the circuitry always operating in the range of 6.0 to 6.5 MHz. The six-pole crystal lattice filter is 2.1 kHz wide at minus 6 db, and 4.2 kHz wide at minus 50 db. Frequency stability is better than 250 Hz drift in the first hour and under 100 Hz drift per hour after warmup.

Receiver sensitivity is better than 0.3 microvolts for 10 db signal to noise ratio. Audio output is one watt maximum, and the AVC control is at least 60 db input change for 10 db change of output level. Price: \$799.95 less Power Supply.

Hallicrafters SR-2000

Squeezed into a cabinet the same size as Hallicrafters' SR-400 we find a complete kilowatt-type transceiver. It tunes all the amateur bands, and runs up to 2000 watts PEP sideband or 900 watts CW.

Shown next to the transceiver is the special power supply required. This supply is probably about 50 pounds weight, and contains metering as well as a loudspeaker for the transceiver. The metering is designed for safety.

Tuning ranges and general performance are very similar to the SR-400, evidently the SR-2000's junior brother. Cost is higher, though, at \$1095 for the transceiver power supply.



Drake TR-4B

Trying to get a TR-4B photo we wound up with a TR-4 instead. However, the B version is not very different. Fitted into a case 10 $\frac{3}{4}$ " x 5 $\frac{1}{2}$ " x 14 $\frac{3}{8}$ " deep, this transceiver uses 20 tubes, two transistors and eight diodes. Weight is 16 pounds, external power supply required.

Transmitting specs are 300 watts PEP input to the PA in sideband operation, 260 watts CW. This transceiver can run AM, using screen modulation, with 260 watts PEP input. VOX and PTT functions are provided, and a transmitter alc circuit prevents driving the output stage into non-linearity. For CW, there is a sidetone oscillator.

The filter shape factor is extremely good. Minus 6 db bandwidth is 2.1 kHz, and at minus 60 db the bandwidth is broadened out (if you can call it that) to 3.6 kHz, for a shape factor of 1.7:1.

Receiver sensitivity is less than 0.5 microvolt for 10 db signal to noise, and audio output is 2 watts maximum. An rf gain control also adjusts the effectiveness of the agc system, which at maximum setting can maintain the output within 3 db for a 60 db change in input signal. That is, if the input

increases from 1 microvolt to one millivolt, you will just about hear the difference.

Tuning ranges cover the amateur bands 80 thru 10 meters in seven 600 kHz ranges. The solid state VFO is a linear permeability tuning design, fixed at a coverage of 4.9 to 5.5 MHz for all input frequency ranges.

An ac power supply is available at \$99.95, or a 12-volt dc supply for \$125. A new 24-volt dc supply has just been introduced at \$210, and this one carries a 110 VAC outlet for operating accessory gear. A remote VFO and additional accessories for mobile operation are also available. Price: \$599.95.



Galaxy V

That frequency scale way off to the left side of the panel looks as though it is about ready to jump off. But by all reports the users like it, and it seems to be a good arrangement for mobile work.

The Galaxy transceiver is rated at 300 watts PEP sideband or 300 watts CW. Upper or lower sideband outputs are available, with VOX operation with an accessory unit. Sideband suppression is better than 55 db, with the carrier 45 db down. Overall audio response in transmitting is down 6 db at 300 and 2400 Hz.

Receiver sensitivity is better than 0.5 microvolt for 10 db signal to noise ratio. The agc system will maintain the audio output within 6 db for a 60 db change in signal strength. Over a 40 db range, the output is essentially free from pops and pumping, and these nuisances can be avoided over any range with the help of the rf gain control.

The receiver audio output is 3 watts at low distortion into a speaker impedance of 4 to 8 ohms nominal impedance. Price is \$420.00.



NCX-500

National's new NCX-500 is a surprisingly light (15 lb.) transceiver, rated at 500 watts PEP sideband, 360 watts CW or 125 watts AM. An external power supply provides for fixed or mobile operation.

Carrier suppression in the transmitter is minus 50 db, and the unwanted sideband is at least 40 db down. The transmitter is designed to work into an impedance of 40 to 60 ohms. An ALC system prevents flat-topping from noises or too-loud speech. Sideband output is Lower on 80 and 40, Upper on 20, 15 and 10 meters.

Receiver sensitivity is nominally 0.5 microvolts for a 10 db signal/noise ratio. Full AGC on receive, and audio output is 2 watts into 3.2 ohms. 5 kHz dial calibration is the same on all bands. The crystal lattice filter operates at 5.202 MHz with a 2.8 kHz bandwidth at minus 6 db, and a 2.2:1 shape factor.

The transceiver is 6 $\frac{3}{16}$ " high, 13 $\frac{3}{8}$ " wide and 11" deep. Its front panel is $\frac{1}{8}$ " extruded aluminum. The AC-500 power supply is the only one listed in National's literature but since the rig comes with a mobile mounting bracket a dc supply should be along very shortly. An accessory 100 kHz crystal calibrator is available.

Priced at \$399.95, the NCX-500 is available from National Radio Co., 37 Washington St., Melrose, Mass. 02176. The AC-500 power supply, which operates from ac only, is priced at \$95.00.



Collins KWM-2


The KWM-2 comes in a 14 $\frac{3}{4}$ " wide, 7 $\frac{1}{4}$ " high, 14" deep case, light gray with a simulated leather front panel. Weight is 18 pounds three ounces. External power supply is required.

Frequency coverage is in 200 KHz wide tuning ranges fixed by a set of 14 crystals. As provided, the KWM-2 covers the amateur bands from 80 thru 10 meters. For commercial or MARS operations the KWM-2A carries an extra crystal board for an additional 14 ranges. Except for this modification the KWM-2A is the same as the KWM-2.

Power input to the final is 175 watts PEP sideband, 160 watts CW. There is no AM capability. Carrier and unwanted sideband are minus 50 db. Other engineering specs are equally impressive, with the help of special negative feedback design of the final amplifier.

The receiver sensitivity is 0.5 microvolt for 10 db signal to noise. Selectivity is 2.1 kHz at 6 db, 4.2 kHz at 60 db down. Image rejection is better than 50 db, receiver output 1 watt max. AGC holds audio within 20 db for a 100 db input signal change from 10 microvolts to 1 volt.

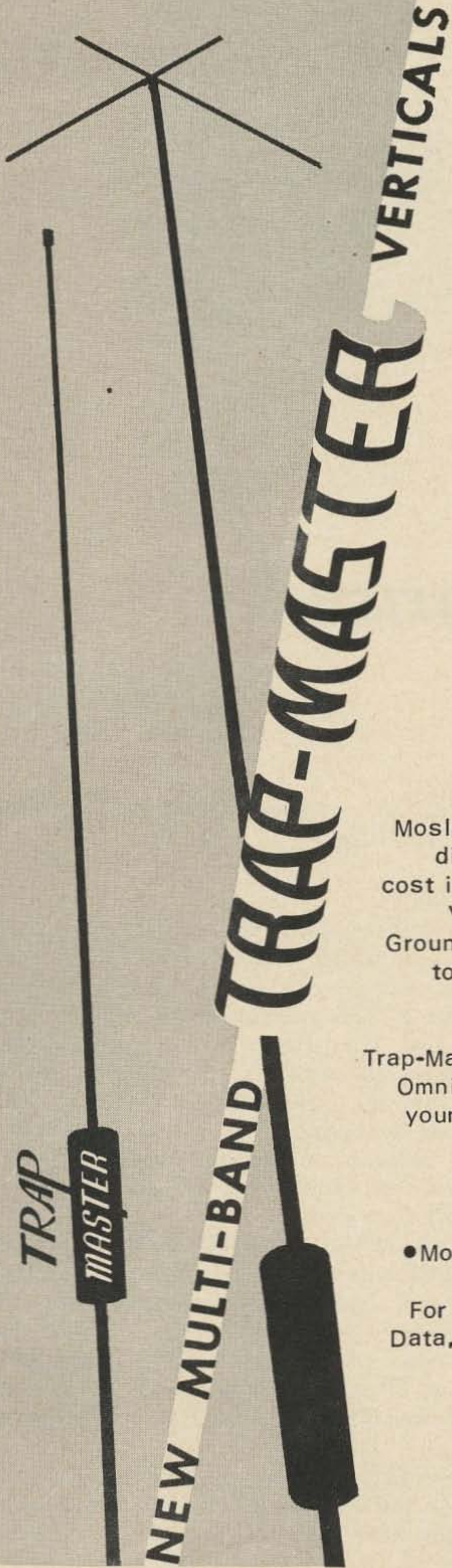Related gear is ac external power supply, \$168; dc external power supply, \$235; 30L-1 linear power amplifier for 1000W PEP, \$520. Price: \$1150.



Great Things are Happening with Verticals

**at
Mosley**

- All New 3 and 5 Band Operation
- Improved 4-Band Performance
- New Simplified Ground Mount
- Versatile Ground or Roof-Top Installation


Mosley's World-Renowned TRAP-MASTER traps offer a new dimension in Vertical Performance . . . plus easy, low cost installation. Three New RV-Series Verticals with the Versatility of Six! New design — from the Simplified Ground Mount (no longer is a concrete footing necessary) to the addition of a 'Top Hat' where it counts most for a low, low angle of roof-top radiation.

Trap-Master Verticals will take you places . . . Outstanding Omni-Directional Radiation — Top DX-Ability. Whatever your needs, Mosley has a New RV-Vertical designed and engineered to give you a real 5-9 signal.

- Model RV-3C for 10, 15, and 20 Meter Bands
- Model RV-4C for 10, 15, 20, and 40 Meter Bands
- Model RV-5C for 10, 15, 20, 40, and 75/80 Meter Bands

For detailed Brochure on Specifications and Performance Data, see your nearest authorized Mosley dealer, or write factory direct: Dept. 170

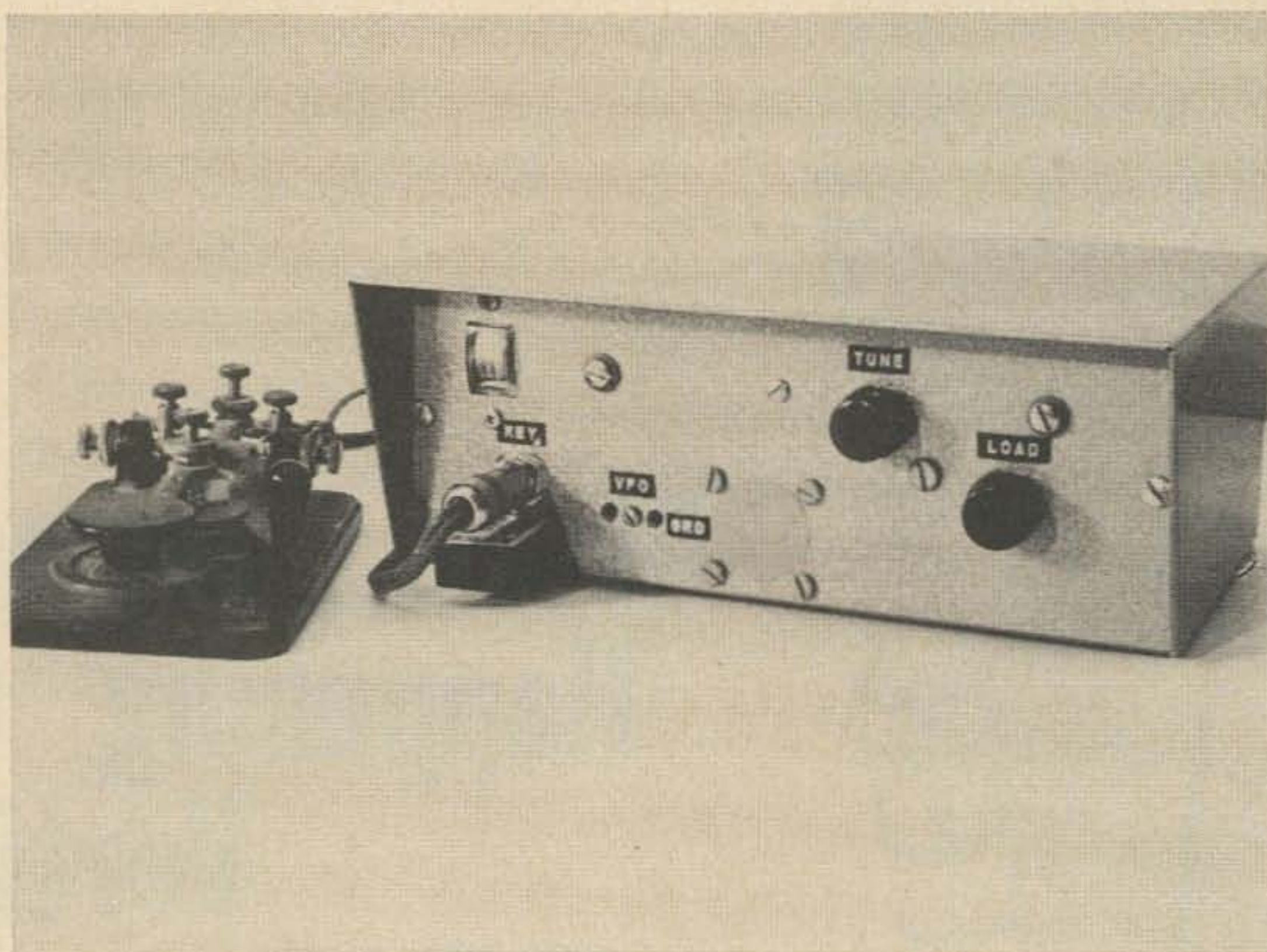Mosley Electronics, Inc. 4610 N. Lindbergh Blvd.,
Bridgeton, Mo. 63042



30 Watt Transistorized Transmitter

Roy E. Gould W5PAG
4748 DeBeers Drive
El Paso, Texas 79924

For several years I have been interested in transistorized transmitters and have read all the magazine articles I could find on the subject with interest. The first transmitters I read about were very low power, but the power has slowly been rising. The biggest problem in building a transmitter that puts out very much power has been in locating a suitable transistor for the final.

I have been disappointed until recently in finding an inexpensive transistor that can handle much power at amateur frequencies. Several months ago I learned about the Texas Instruments TIP 14, which has a 10 watt power rating and sufficient frequency response to be a good 80 meter amplifier. It doesn't cost a fortune, only \$1.50. After learning of the existence of this transistor, I couldn't resist building a transmitter with a pair of them in the final.

This article describes that transmitter, a 30 watt, 80 meter CW rig. While 30 watts is not high power it is sufficient to do a good job when conditions are favorable and is relative high power for amateur band transistorized rigs. The final uses a form of π -net


coupling, an unusual circuit in amateur transistorized rigs.

The circuitry

The oscillator is crystal controlled and is otherwise untuned. The circuit is simple and a major component in the circuit is the transformer. This transformer is wound on a toroid core. The primary is connected to the collector of the oscillator transistor. A feedback winding excites the crystal and the remaining secondary drives the next stage. The 47 ohm emitter resistor raises the input impedance of the stage to a level the crystal can work into easily.

The use of the toroid allows the building of a small circuit, makes tuning the stage unnecessary, and greatly reduces feedback from the final tank coil. These are important considerations when building the transmitter into a small cabinet. The cost of the toroid core is about the same as that of a tuning capacitor.

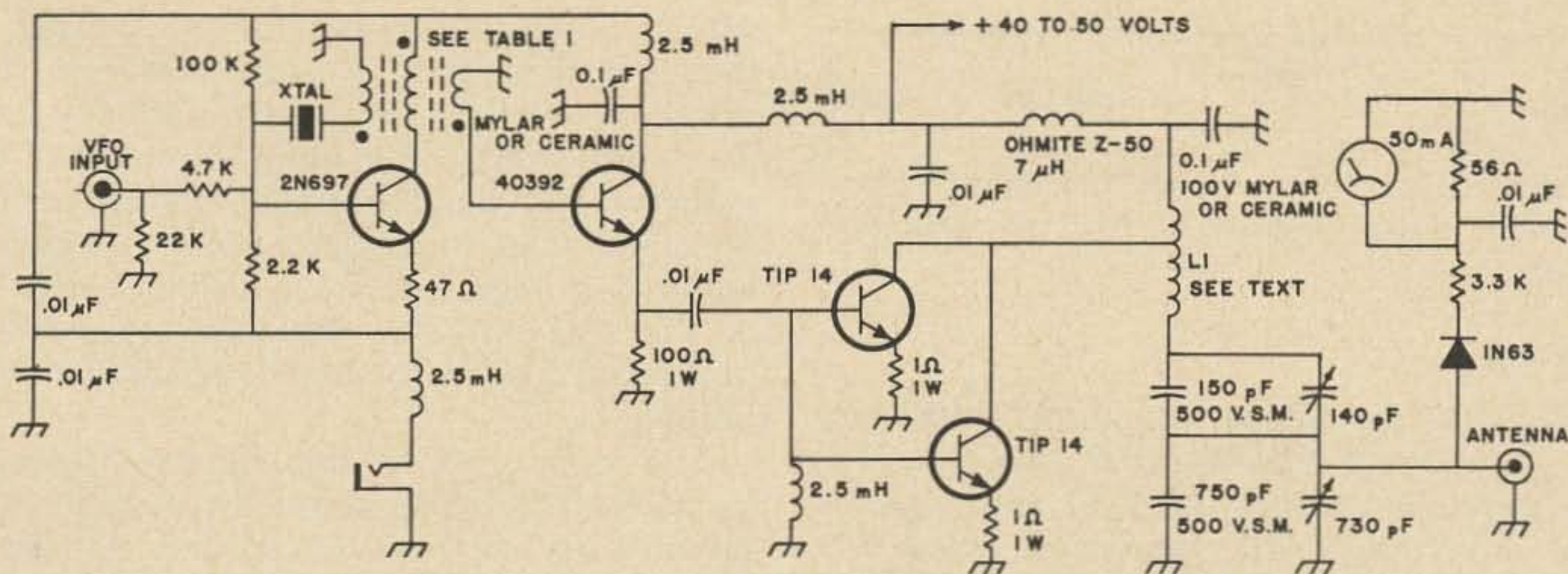The oscillator stage can also be used as an amplifier and can be driven by a vfo. I used a Knight tube type vfo that has a no-load



ALL CAPACITORS ARE DISC CERAMIC, 1000 WVDC EXCEPT AS NOTED
ALL RESISTORS ARE 1/2 WATT EXCEPT AS NOTED

Fig. 4. Circuit diagram of the transistorized transmitter.

output voltage of 110 volts rms. The vfo voltage is fed to the base of the oscillator transistor through an attenuator network to obtain a drive voltage the stage can safely work with. The circuit works well and greatly increases the flexibility of the transmitter.

The driver stage is basically an emitter follower and isolates the oscillator from the final and drives the final from a low impedance source. The driver transistor is operated with no bias and amplifies only the positive portion of the input voltage. When there is no drive, the transistor draws no current. The stage provides no voltage gain, but does give current gain.

The final amplifier is a parallel class-C amplifier. The collectors and bases of the two TIP 14's are connected together but the emitters go to ground through 1 ohm resistors. The main purpose of these resistors is to divide the collector currents evenly between the two transistors. This helps to minimize the effect of using two transistors whose gains are far from equal.

The rfc provides a dc connection to ground for the base circuit of the final transistors, placing a small reverse bias on the final transistors. Since transistors don't conduct unless base current flows, no collector current will flow unless drive is applied.

Proper tuning is indicated by an rf voltmeter. The rf voltage is rectified and the pulsating dc is applied to the tuning meter through a resistive voltage divider. Proper tuning is indicated by maximum indication on the meter.

The Texas Instruments TIP 14 transistor

is ideal for use in an 80 meter power amplifier because it has a minimum f_t of 40 MHz and has a power rating of 10 watts up to a temperature of 75°C. It is further attractive because it costs only \$1.50.

Since the TIP 14 is rated at 10 watts up to a temperature of 75°C, it can handle more power than most transistors with a 10 watt rating. This is because most transistors are rated at their maximum power level at 25°C (room temperature). Above this temperature, the power rating of the transistor decreases. Because the transistor ordinarily has to be above room temperature to get rid of the power it is dissipating, its power rating is reduced. The TIP 14 need not suffer any decrease in power rating because with a good heat sink, its temperature can be kept below 75°C.

The combined power dissipation rating of the two TIP 14's used in the final is 20 watts, and if the efficiency of the final were 50 percent, the power input to the final could be 40 watts without exceeding the power rating of the transistors. In a breadboard circuit, the power output from the final was measured to be slightly over 19 watts and the power input was nearly 40 watts. The transmitter described in this article cannot deliver that much power because there is not enough drive for the final. The breadboarded driver circuit would not work in the small cabinet used because the transmitter oscillated severely in the close quarters. A different driver circuit was devised and it cannot drive the final to full output.


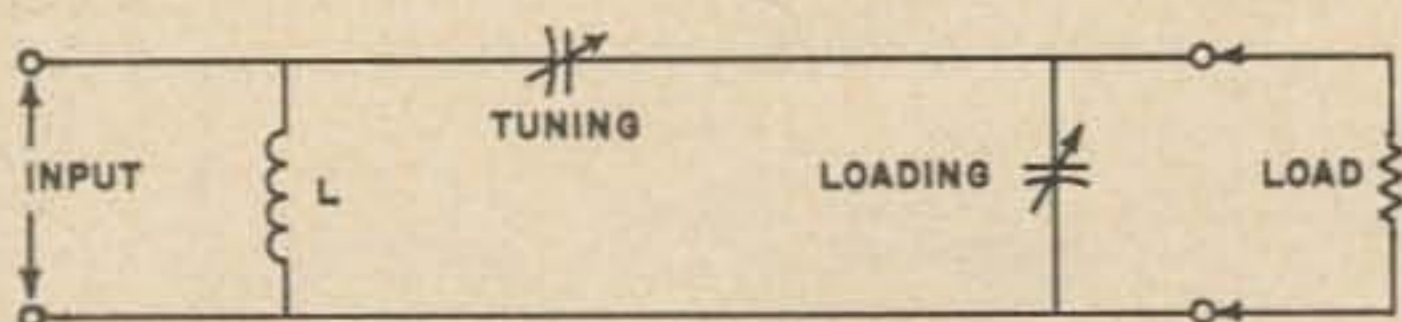


Figure 2. Basic π -network used as the final tank circuit.

The tank

Perhaps the largest stumbling block for the designer of transistorized transmitters is the requirement that the final must operate into a relatively low impedance load if a very large amount of power is to be obtained. Tank circuits conventionally used in tube circuits are not practical because very large values of capacitance and low values of inductance are required if a tank with a low input impedance is to be obtained. The often used π -net in its common form could provide the required impedance transformation but is not very practical because very large tuning capacitors in the $0.01 \mu\text{F}$ range are required. Two π -nets could be used back to back but this is not very handy because three controls would be required. The usual tank used by amateurs is a simple L-C circuit with two taps on the coil; one for the final and one for the antenna. This works but has the disadvantage of requiring an antenna tuner or of finding the proper tap points by trial and error for the antenna to provide a proper load.

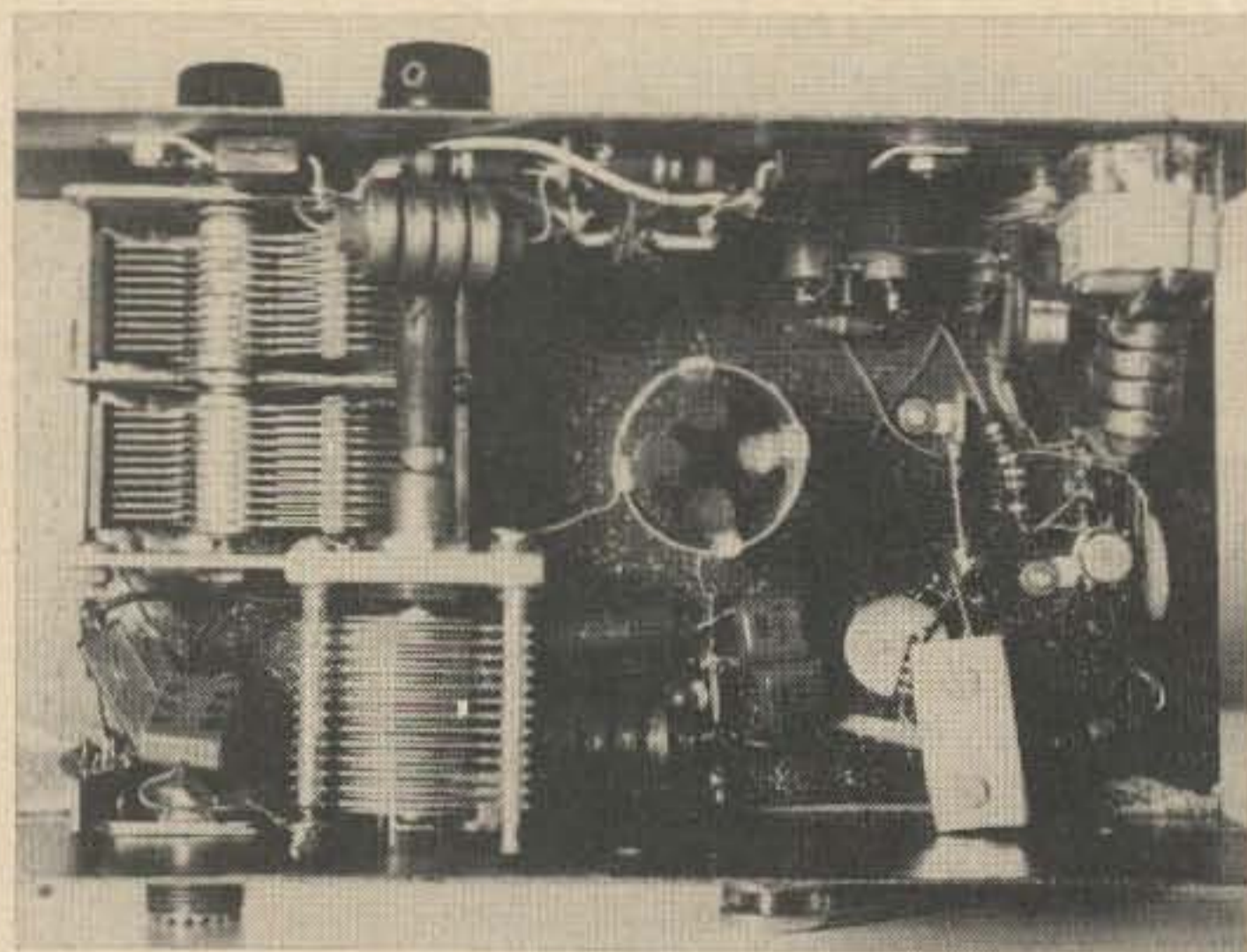I have always liked the π -net as the tank and coupling circuit for final amplifiers because of its flexibility and ability to adjust to changing loads. Therefore, I tried to design a π -network that would work with tran-



Top view of the inside of the transmitter. The tuning capacitor is mounted on the top and back of the loading capacitor and the tank coil is glued to four plastic mounting rods.

sistors. The basic π -net circuit I used is shown in Fig. 2. The basic difference between this circuit and the one normally used for tubes is that the input element is the inductor and the horizontal element is the capacitor. The input impedance across the inductor is high but a tap near the bottom of the coil provides the impedance transformation needed to match the load to the transistor.

The π -net used in this rig was designed to match 5000 ohms across the inductor to a resistive load of between 25 and 100 ohms. The coil is tapped near the bottom of the coil at a point which presents a load of 30 to 40 ohms to the final transistors. The tank is designed to have a Q of 15.

A tank using the same circuit could be used with tubes but ordinarily wouldn't be because there is no advantage over the conventional circuit, and the tuning capacitor has to be isolated from ground. Isolating the tuning capacitor from ground is not really a serious disadvantage however, and creates a problem mainly in mounting the capacitor.

Construction

Good high frequency construction techniques should be used. The oscillator circuitry should be separated from the final tank coil as far as possible to avoid unwanted oscillations. A wire connection should be used between ground points rather than relying upon the chassis connection. All bypass capacitors are disc ceramics except the $0.1 \mu\text{F}$ capacitors which are made with Mylar.

The tuning capacitor must be electrically insulated from ground. The section of this capacitor that is connected to the shaft should be connected to the high side of the loading capacitor because the voltage at this point is not high. Preferably, the shaft should be insulated from the knob.

The oscillator transistor does not require a heat sink, but the driver and final transistors do. The driver transistor is easy to heat sink because its case has a mounting flange. I bolted a piece of aluminum to the top of this transistor using silicone grease to increase heat transfer. The TIP 14 transistors are easy to mount with one screw. They are encased in plastic and are mounted with a mounting tab which also provides the connection to the heat sink. This tab is in electrical contact with the collector and must

be insulated from the cabinet on which it is mounted. I mounted the two final transistors on the inside of the front panel using mica and silicon grease. One reason I mounted them on the front panel was to make it easy to test their temperature with a finger. With the low voltages used there is no shock hazard, but slight rf burns can occur. (Don't touch the mounting screws when the key is down.

The transformer used in the oscillator is wound on $\frac{3}{8}$ inch diameter toroid core. Winding data for this transformer is given in Table 1. The transformer must be connected with the polarity indicated in Fig. 1 if the oscillator is to operate properly.

The final tank coil, L_1 , was made from a one inch diameter Miniductor with 16 turns per inch. The coil has 29 turns and the final transistors connect to a tap $3\frac{1}{2}$ turns from the bottom of the coil.

Table 1
Toroid Transformer Data

Winding	No. of Turn	Wire Size
Primary	16	26
Output	9	32
Feedback	14	32

Most of the parts used should be easy to obtain, however, the RCA 40392 transistor, the toroid core and the TIP 14 transistors may be difficult to obtain locally. All are listed in the *Newark Electronics Corporation Catalog No. 68*. The 40392 costs 91 cents, the TIP 14 costs \$1.50 and the toroid core costs \$1.20. The $\frac{3}{8}$ inch diameter toroid core is manufactured by the Indiana General Corporation and is made of Q-1 material.

I built the transmitter except for the power supply in a 3 x 4 x 8 inch Bud Mini-Cowl cabinet. There is plenty of room in this

SIGNAL TRACER

Here is an exceptional value. This solid state signal tracer will make servicing of your receiver, AM/FM and TV very easy. Comes complete with shielded prod and clip cord. Self-powered. Six transistors, four diodes and one thermistor. Built in speaker and 200 uA meter. Attenuator 20-40-60 dB. Gain over 70 dB. Outputs for 8 and 600 ohms. You can track down the trouble in a receiver in minutes with this little unit.



ONLY \$22.50

TRANSISTOR DC SUPPLY

This power supply will operate transistor radios and other devices under repair or where batteries are a drag to replace. Voltage range: 0-20 vdc continuously variable. Meter ranges: 0-20 vdc, 0-20 mA, 0-200 mA. Maximum current capacity: 150 mA/20 v or 200 mA/10 v. Pilot lamp. AC ripple: less than .25 mv rms. Fused. Has built in power transformer and 30 watt power transistor. Built for continuous duty.



ONLY \$16.95




MINI-LAB

Here is a complete test laboratory all in one package! A modern miracle of electronics. This one unit contains an AC-DC Voltmeter: 50, 150, 500 volts; 0-500 mA; 10K, 100K, 1M ohms; resistance and capacitance substitution; 9 vdc battery supply; RF Signal generator 455 kHz (and up to 700 kHz); plus an audio generator at 400 Hz. You can service just about anything with this lab. You can signal trace and align receivers and trace audio systems, speech equipment, hi-fi and tape recorders. This is probably the single most useful piece of test equipment ever to come along.

SPECIAL \$24.95

Distributors and Reps Wanted!

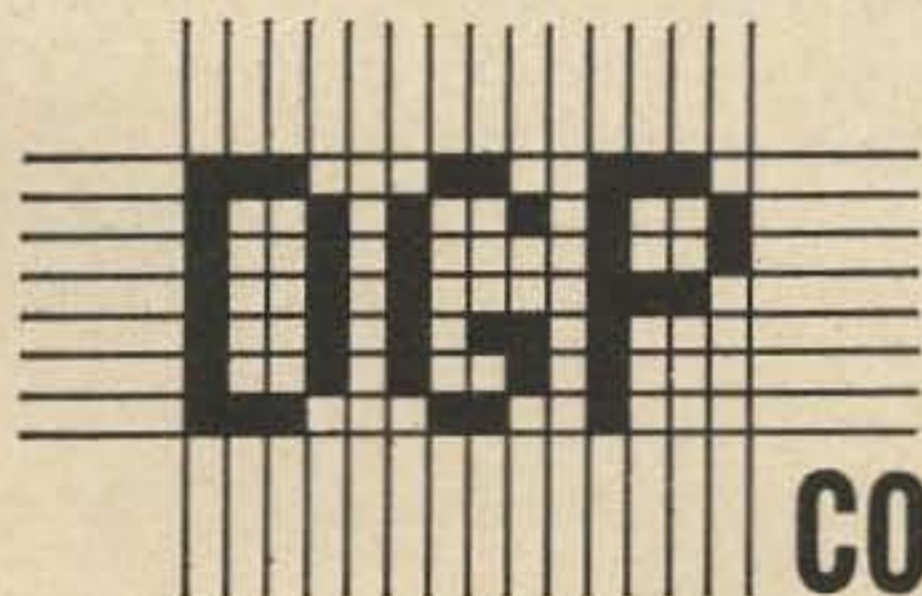Please write to John Kneeland, Sales Manager about handling this fine line of imported test equipment.



CO. P.O. box 231 JAFFREY, N. H. 03452

If your local distributor does not handle the DGP line you may order direct from Redline, Jaffrey, N.H. 03452. Please include a little extra for postage charges.

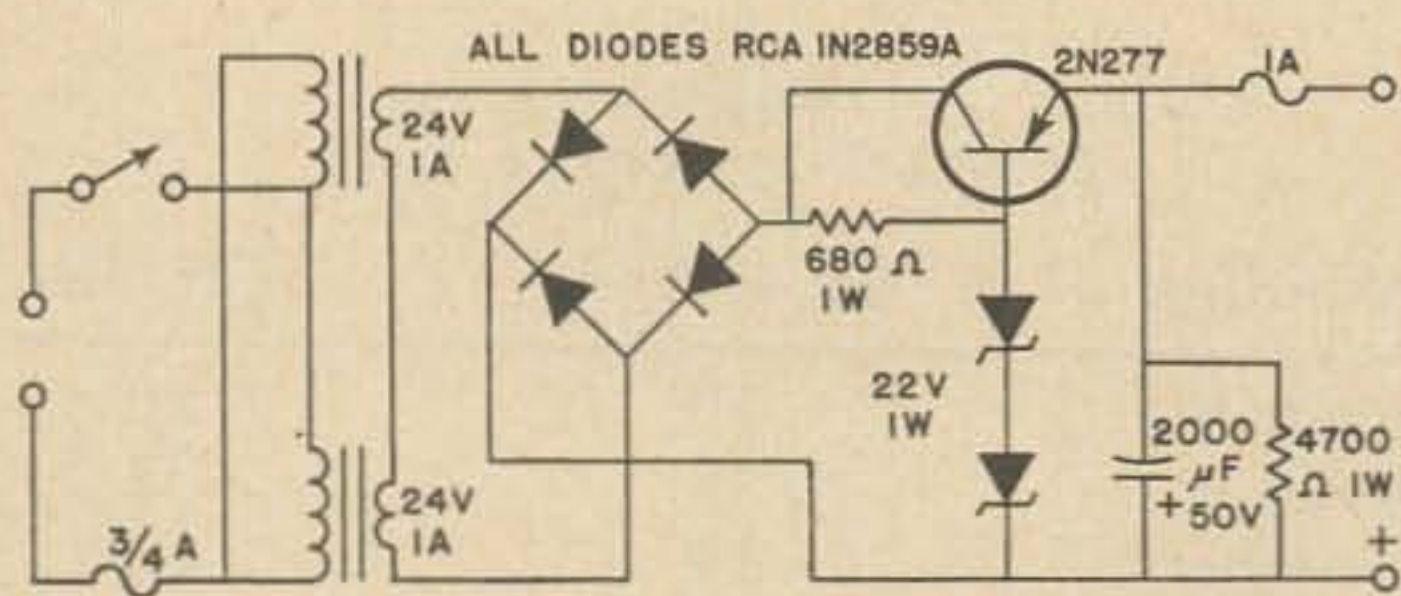


Figure 3. Schematic diagram of the power supply.

cabinet although the construction is fairly compact. The final tuning capacitor is mounted on the back of the loading capacitor. Since a shaft extension was needed, I used a piece of polystyrene rod for the extension, which insulated the knob from the rf.

The oscillator and driver stage could be built on a printed circuit board or on a vector board, but I used two, five terminal strips to build these sections. There are not many connections and this is an easy way to build the circuits. Most of the components in the final are mounted to the cabinet and a two terminal strip was required to wire this section.

The power supply

The power supply uses two 24 volt filament transformers with the secondaries connected in series. The secondary voltage is rectified by four diodes in a bridge. The voltage is then regulated by the transistor, whose reference voltage is fixed by the Zener diodes. The voltage is then filtered by the 2000 μ F capacitor.

The power supply works well and the regulation is good. The Zener diodes I used are actually a little higher in breakdown voltage than their rating indicate, and the no-load output voltage is 47 volts. The output voltage with a 1 ampere load current is 43.5 volts and the percent ripple at this current is 1.4 percent.

The construction of the power supply is not critical. The main problem is getting the secondaries in series so that their voltages add. If the voltage from the two secondaries in series is nearly zero, reverse the connection to one winding.

Operation

The transmitter should be connected to a fairly well regulated power supply capable of delivering 40 to 50 volts at 1 ampere. The transistors have 60 volt ratings so don't

apply over 60 volts under any circumstances. The dc from the power supply should be fused with a 1 ampere fast blow fuse to protect the final.

A ground and a good antenna, preferably a half-wave dipole, should be connected to the transmitter. Even though the final uses π -net coupling, it cannot match badly mismatched loads. If a badly mismatched load is to be matched, an external antenna tuner can be used or the tap on the final tank coil could be changed.

An active 80 meter crystal should be plugged into the crystal socket or a vfo into the vfo socket. Most crystals should operate satisfactorily in the circuit. If a vfo is to be used, its no-load output voltage should be near 110 volts rms. If it is much different than 110 volts, the value of the series resistor in the attenuator network (4.7 K Ω on the circuit diagram) may need to be changed. If there is too much drive, increase its value; if there is not enough, decrease it.

The only controls on the transmitter are the final tuning control and the loading control. The final should be loaded by first completely closing the loading capacitor. Then tap the key and turn the tuning knob until maximum voltage is indicated on the tuning meter. Then turn the loading control until maximum voltage is indicated, followed by again peaking the voltage with the tuning control. After the maximum voltage indication has been obtained by alternately adjusting the tuning and loading knobs, the rig should be ready to operate.

The power input to the final can be determined by measuring the input power to the entire transmitter and subtracting 4 watts, the approximate amount of power consumed by the oscillator and the driver. The efficiency of the final is about 50 percent, so the output is about one-half the input power.

Final comments

This is not a high powered rig, but it has been a good performer for me. I used it with a quarter-wave antenna about 20 feet high. My best DX was with a station in Washington state, an airline distance of about 1500 miles. It should do as well for you.

. . . W5PAG

Acknowledgement

The author is indebted to Mr. Brice for taking the photographs.

When Hallicrafters says
"dual receive" we mean
SIMULTANEOUSLY!
SIMULTANEOUSLY!



That's right—*simultaneous dual receive!* Unlike any other transceiver/VFO combination, the SR-400 Cyclone and HA-20 VFO lets you "Double-Team" the competition in any DX contest. You can "Band-Scan" for a second contact while you are working another. You can set VFO's on two separate DX stations, receive both simultaneously, and be instantly ready to "Tail-End" on either station. And of course, Hallicrafters' winning performance features don't stop here. Get in front of this rig and you'll know. Hallicrafters has built another "great one" in the fine tradition of the HT-32 and HT-37.



PS: Want simultaneous dual receive with 2 KW on SSB? Put an SR-2000 in your shack.

the hallicrafters CO.

A Subsidiary of Northrop Corporation

600 Hicks Road, Rolling Meadows, Illinois 60008



The Care and Feeding of a Ham Club—VI

*Carole Allen W5NQQ
308 Karen Drive
Lafayette, La. 70501*

Do Something Different!

Variety is the spice of radio club life, and some of the country's most active groups credit their successes to their special projects. The Stuyvesant High School Radio Club, for instance, distributes "The Groundwave," a publication acquainting over 1000 area residents with accomplishments in the electronics field.

The RAMS of California decided to equip its members with as many hand-held transceiver type emergency units as possible. They also assisted an invalid boy in getting his novice license and setting up a station. Since there are countless hams around the country who cannot see or move about to erect antennas, construct equipment, or maintain it, one of the most worth-while projects a club can choose is to aid a handicapped ham in keeping his station in running order.

Volumes could and should be written about groups such as the San Gabriel Valley California club who developed a satellite tracking receiver in 1957 which was nationally recognized. The receiver design incorporated a principle which was soon being used by U.S. tracking stations.

Along this same line, club participation in satellite tracking and high frequency communication offers the ultimate in electronic adventure. Information on transmitters, receivers, antennas, frequencies, and all the necessary scoop is available from the American Radio Relay League, Newington, Connecticut. Project Oscar (Orbiting Satellite Carrying Amateur Radio) launched December 12, 1961, was a grand chance for a club to listen with collective ears for the fading HI it sent on its orbits.

Back to earth, there are smaller projects to be undertaken that are just as rewarding. Club stations can be constructed, permanent antenna installations completed, emergency power plants set up, trouble-shooting gear bought, and other jobs that are too big for one but just perfect for many.

And as a strictly-for-fun project, the Possum-Trotters, a club with headquarters at Paris, Illinois, bought matching hamfest shirts in bright yellow for every ham and family member from baby to grandpa. Every summer, they pack picnics and "caravan" together to hamfests.

Whether it's big or small, pick a project and see the club light up!

Double "Trouble"

If your club has a high percentage of "live wires" and an extra portion of pep, why not sponsor a hamfest or a convention some time? Sure, either one takes a lot of work, but it can also be fun. And just in case you're thinking you need a hundred members to try something big, take a look at the Starved Rock Radio Club of Ottawa, Illinois. Here in the Midwest scarcely more than a dozen hams put on a hamfest every June for over 5000 persons. Admittedly, the more workers the easier the job, but the point is that a tiny club can sponsor either a hamfest or a convention if they put their minds and shoulders to it.

A convention can be called more of a white shirt and tie affair while a hamfest is a shirt sleeve gathering with families and picnic baskets in the great out-of-doors. Weather, of course, is a very vital factor at a hamfest while a convention is usually held in a hotel and lasts two or three days requiring an hour by hour schedule of forums, lectures, exhibits, luncheons, banquets, and speakers.

Aside from these basic differences, much of the same planning goes into both events. For instance, most of the committee chairmen, listed below, would also be needed to promote a hamfest:

General Chairman
 Vice-Chairman
 Publicity
 AREC and RACES
 ARRL Booth
 Exhibit Manager
 Finance
 Ladies Program
 Awards Booth
 Registrations
 Mobile Judging
 Hidden Transmitter Hunt
 Hospitality
 Programming
 Parking

If you and your club are "newcomers" in the sponsoring "game," it's good to take a look at other clubs. Hit the road for every hamfest and convention you can find. Take a notebook along and jot down ideas you like and those you don't. Whoever said to profit by other's mistakes must have planned a hamfest.

The Dayton Hamvention and many other large gatherings are held year after year resulting in committees of cool-headed veterans who can meet any emergency. But, for the most part, conventions are sponsored once-in-a-blue-moon by a group or council of clubs. Enlisting the help of ten or twenty clubs and coordinating all the volunteers is a challenge; in fact, the General Chairman has to be a "miracle worker" to organize all the groups and come up with cooperation.

A small club actually has the advantage here because all the members know each other. Around a metropolitan area, there are so many hams that few are well-acquainted, and the General Chairman has to introduce his helpers right off the bat.

The first big machine to roll is pushed by the publicity people since hams have to know before they go. Individual mailings may be expensive but they're vital in order to get dates and rates around. Notices in magazines and signs erected at events earlier in the year are effective with last minute mailings to jog an absent minded ham's mind.

George Griffis, K7EIS, was Promotion Chairman of the ARRL's 25th Annual Convention September 1, 2, and 3, 1962 at Portland, Oregon. Knee-deep in planning, he reports that a skeleton group of eight men

"Your Friendly Supplier"

FROM STOCK!

OFFERS

CHRISTMAS GIFT SUGGESTIONS

A COMPLETE "LINE-UP" OF ACCESSORIES FOR THE HAM-SHACK

EICO

Vibroplex

ASTATIC

AMECO

MASTERCRAFTERS & PENNWOOD 24 HR CLOCKS

WELLER

TRIMM

TURNER

COMDEL

E. F. JOHNSON

JONES MICRO-MATCH

W2AU BALUNS

B.W.

ElectroVoice

XCELITE

DOW-KEY

... plus many more nationally advertised standard brands.

We maintain the largest stock of used equipment in the Northeast — Engineering Department — Time Payment Plan available.

WRITE FOR LATEST COMPLETE LIST

Evans RADIO

BOX 893

CONCORD NH 03301

FONE 603-225-3358

CAN I GET A PRIZE WITH MY RENEWAL?


Yes . . . if you bring a friend.

Your renewal (or extension of subscription) plus a new subscription for a friend is the key to the prices given below. USA or APO only. And please send us the address from your wrapper. All items are postpaid unless marked FOB.

	your cost
1. Digital clock with date (\$50)	\$38.00
2. Caslon Digital desk clock (\$25)	15.00
3. Rotating three tier parts bin (\$5)	free
4. K&E Slide Rule (\$5)	free
5. Inside-outside thermometer (\$5)	1.00
6. Rand-McNally Imperial Atlas (\$13)	4.00
7. Rand-McNally Magellan Globe (\$14)	6.00
8. Car blanket with case (\$12)	free
9. 15 Transistor AM/FM bat.-ac (\$35)	18.00
10. AM/FM-Clock (\$65)	30.50
11. Lamp-clock-radio (\$35)	18.50
12. 13" Hammond world globe (\$13)	5.00
13. 13" Hammond lighted globe (\$17)	8.00
14. 18" Hammond world globe (\$17)	10.00
15. 18" Hammond lighted globe (\$25)	12.00
16. Polaroid Big Swinger camera (\$25)	17.90
17. Polaroid 215 camera (\$56)	43.00
18. 4-drawer desk (\$45) (FOB)	24.00
19. Encyclopedia (\$160) (FOB)	52.00
20. Cassette tap recorder (\$45)	30.00

Send us your address from your wrapper, the name, call and address of your friend on a 3 x 5 card who gets the new one year subscription together with \$6 for your one year renewal, \$6 for your friend and the amount for one of the above "gifts". USA-APO only. Offer expires December 31, 1968.

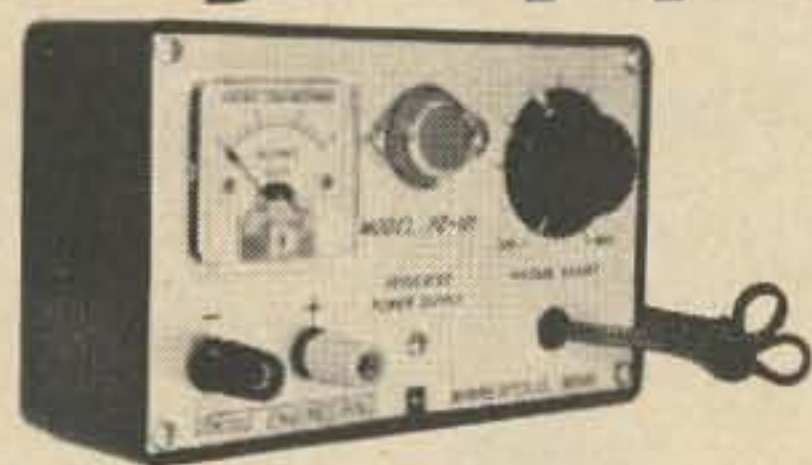A regulated DC supply for any application...or budget



Model PZ-121
.5-15V @ 100ma

- Input: 110-125v 60 cy
 - Regulation: \pm .2v
 - Ripple: 5mv
 - Size: 6¼ x 3¾ x 2
 - Weight: 2 lbs. (shipping)
 - Protected against short duration short circuits
- FACTORY ASSEMBLED \$19.95
 KIT \$15.95



Model PZ-131C
.5-15V @ 350ma

- Input: 110-125v 60 cy
 - Line Regulation: \pm 10mv
 - Load Regulation: 50mv
 - Ripple: 1mv
 - Impedance: .25 ohm
 - Size 4½ x 2½ x 4
 - Weight: 3 lbs. (shipping)
 - Electronic current limiting
- \$39.95**



Model PZ-241A
.5-25V @ 1 amp

- Input: 110-125/220-250v 50-60cy
 - Line Regulation: \pm 10mv
 - Load Regulation: 50mv
 - Ripple 1mv
 - Impedance: .1 ohm
 - Size: 5½ x 3 x 7
 - Weight: 6 lbs. (shipping)
 - Adjustable electronic current limiting
 - Remote sensing
- \$69.95**

SAME DAY SHIPMENT ON MOST ORDERS.

Terms: Cash. Rated firms, institutions—net 30 days. COD orders require minimum \$5.00 deposit. Prices F.O.B. St. Paul (include postage)
COMPLETE LINE OF LOW COST POWER SUPPLIES. WRITE FOR OUR CATALOG.

Viking Engineering of Minn. / 915A So. McKnight Road
 St. Paul, Minn. 55119 / (612) 735-4278

were carrying the ball there. Starting at the top is an Executive Chairman, then the Council Chairman of radio clubs in the Portland area, with Chairmen of Registration, Promotion, Program, Finance, and Entertainment and a Convention Manager, too. Behind the scenes are dozens of assistants and just as many patient XYL' who spent many a lonesome evening and probably wound up at the registration desk or working on the women's program.

Decisions by the hundreds face the folks who organize hamfests and conventions, and since at least 75 per cent of them involve money, the first thing to do is get financial feet on the floor. Ideally, the committee should strive to keep prices as low as possible—not only for registrants but for manufacturers who sign up for booths and exhibits. Money doesn't grow on anybody's tree not even the fellow who represents the hottest selling rig in the country. Sure, manufacturers make hay among crowds of prospective check-writers, but let's face it, they have a load of expenses for transportation, meals, tips, rooms, and you-name-it. Since no big affair is complete without exhibits of new and surplus equipment, it seems only

fair that factory reps and their budgets should be handled with kid gloves.

Along this same dollar-sign line is the price of registration. "The lower the better," most hams agree, but obviously a convention held at a hotel where minimum payments must be made, come rain or shine, will cost more than a hamfest held in an open pasture. Those who like conventions and can attend them regularly expect to pay, but if entrance fees can be kept down, a greater number of hams will probably flock in to enjoy the exhibits and forums. The treasurer may get nervous about the lower charges, but not when he finds himself opening the cash drawer twice as often to take in registrations.

Prizes, of course, are a "must" and two important points to ponder are (1) how to get 'em and (2) how to get rid of 'em. Practically every manufacturer or businessman in the electronics game is prepared to donate a raft of prizes every year or offer some kind of "mark-down" on new equipment. It's up to the committee to decide whether to put all the eggs in one basket and give a complete station as first prize or to buy lots of small prizes to accompany the

donations. Unless you have personally waltzed out of a convention or hamfest with a \$1000 prize, you'll probably agree that the more prizes awarded, the happier the hams involved.

It's going to take time to award a lot of loot, and many prize chairmen advocate hourly drawings to get rid of small prizes, saving the big stuff until last. This eliminates a three hour drawing of log books, single tubes, and screw drivers while an antsy audience boils in the sunshine or fidgets about getting the suitcases out of the hotel room before check-out time.

Anyone who's been through the mill will tell you that it would take at least ten volumes to describe every phase of planning for a hamfest or convention. And, beside that, the best way to learn is to get into the swim of things. In short, if you and your club aren't afraid of hard work, late hours, and last minute jitters followed by feelings of real accomplishment and wonderful memories, take some advice from our astronauts, and GO! . . . W5NQQ

TRADE EVEN

NEW BOXED SWAN 500C WITH 117XC POWER SUPPLY FOR ANY OF THE FOLLOWING SURPLUS IN GOOD CONDITION.

TEST EQUIPMENT: SG-1A/ARN WITH PP-348, SG-2/GRM-4, SG-13/ARN, UPM-98, UPM-99, ARM-22, ARM-25, ARM-47, HLI-103A, ARC H-14A, MD-83A/ARN, HEWLETT-PACKARD 606A, 608D, 612A, 618A, 620A, COLLINS 479S-3, 479T-2, 477U-2, 678Y-3, TEKTRONIX 535A, ETC.

AIRBORNE EQUIPMENT: ARC-51, ARC-54, ARC-94, ARC-102, ARC-134, RT-220C/ARN-21, 618T, 618S, ARN-83.

RECEIVERS: R-390A/URR WITH DUST COVERS.

Write, wire, phone (813) 722-1843, Bill Slep, W4FHY, if you have any of the above and we will trade even!

SLEP ELECTRONICS COMPANY

2412 HIGHWAY 301 N.
ELLENTON, FLORIDA 33532

MERRY CHRISTMAS! ALREADY?

Yes.

YOU SEND A CHRISTMAS GIFT SUBSCRIPTION TO 73 AND WE WILL REWARD YOU WITH AN ABSOLUTELY FREE COPY OF OUR GIANT DX HANDBOOK WITH WALL MAP OF THE WORLD!

Name Call

Address

City State Zip

New sub Renewal (Please send address from wrapper if possible).

GIFT SUBSCRIPTION PLUS DX HANDBOOK TO YOU . . . TOTAL \$6.00!

Your name Call

Address

City State Zip

While you are at it enter a new ____ or renewal ____ sub for me for \$5 per year. (Please enclose label from wrapper on renewals)

Gift subscriptions will start with the January issue. Gift note will be sent too if desired.

73 MAGAZINE PETERBOROUGH NEW HAMPSHIRE 03458

Getting Your Higher Class License

Part IX—More on Transmitters

Much of the technical content of all our license exams deals with the proper adjustment and operation of transmitters. This month, we'll wrap up the last of three installments covering the Advanced Class transmitter-oriented questions.

The specific questions we're covering this time are as follows (numbers, as always, are those from the FCC study list):

28. How does a full-wave bridge rectifier operate? What is the schematic diagram of this rectifier circuit?

43. Define frequency deviation in FM transmission.

49. How should a linear amplifier be adjusted for linear operation?

50. How is the power output of a 100-percent modulated AM signal related to the carrier power?

51. Why does a type 6146 tube have three prongs connected to the cathode?

As you can see, this is somewhat of a Mulligan stew of subject matter; the power-supply question could just as easily have been discussed under the heading of "receivers" and the remaining ones include design, adjustment, and operating techniques. However, we'll try to follow our usual practice and rephrase the questions into broader ones covering not only the specific details asked in the study list but as many related points as possible.

In order to define "frequency deviation" a knowledge of all the special terms used to describe FM is necessary. Our first question thus becomes "What Terms Are Used To Describe FM and What Do They Mean?"

Adjustment of linear amplifiers is included in the answer if we ask "How Are RF Amplifiers Adjusted For Proper Operation?", so that becomes question number two for us.

The full-wave bridge is only one of the popular power-supply circuits. Question num-

ber three therefore is "What Are The Popular Power Supply Circuits and How Do They Work?"

Multiple cathode conversions on the 6146, again, are only one example of some of the practical problems of tube design. All can be answered if we find out "Why Are Tube Pins Connected As They Are?"

And finally, power output of an AM signal when modulated is just one of the factors involved in determining the power output of any rig. "What Is Output Power, Anyway?" wraps them all up.

Ready for our modified question list? Let's go!

What terms are used to describe FM? What do they mean? While the theoreticians insist that only two kinds of modulation are possible—amplitude and angle—those of us who must deal with the real (that is, non-mathematical) world have quite a few more kinds to keep in mind. To name only those more commonly used in hamdom, there are CW, AM, SSB, DSB, and FM.

Each of these has its own particular set of words to describe the essential characteristics of the modulation; in CW keying may be "hard" or "soft", AM may overmodulate, either type of sideband may generate "buckshot"—and FM may do almost anything.

Most of us have already learned the essential words to talk about AM, CW, and sideband just in the course of everyday operation. Unless you're an FM buff, though, the chances are good that you aren't as familiar with the FM jargon—and that's what this question is all about.

While it doesn't *really* work like this, most of us find it easiest to think about FM by visualizing a carrier of steady power being moved about in frequency by the

audio which is modulating it. The *rate* at which the carrier frequency swings is determined by the *frequency* of the audio, and the *distance* from the center frequency that it swings is determined by the *loudness*.

In this oversimplified picture, a low-frequency signal and a high-frequency signal (both audio, that is) will swing away from center equally if both are equally loud. The bass tone, though, will swing more slowly than the treble.

While an AM signal can overmodulate and cause objectionable splattering across the bands, an FM signal cannot be overmodulated at the transmitter. "Overmodulation" in FM is determined at the receiver; any time the signal swings across a wider range than the receiver can handle, it is overmodulated. For legal purposes, the equivalent of AM's overmodulation is "excessive frequency deviation"—or too wide a swing. In the bands below 52.5 MHz, maximum swing permitted is 3 kHz.

Now about those words. We've been using some of them so far. "Frequency swing" is the number of Hertz, kilohertz, or megahertz that the signal moves from one side to another. The bandwidth occupied by the signal is equal to two times its maximum frequency swing. "Frequency deviation" is the same as "frequency swing".

"Modulation index" is another term employed frequently in FM. The modulation index of an FM signal is equal to the frequency deviation divided by the modulating frequency. That is, if your audio is a 3-kHz tone and your deviation is also 3 kHz, the modulation index is 1.0. With the same deviation but a modulating frequency of 300 Hz, the modulation index is 3000/300 or 10.0.

"Modulation index" also applies to AM but is determined differently there—"modulation percentage" is simply 100 times the "modulation index" in an AM transmitter, so that the maximum modulation index permissible in AM is 1.0 and the average is more like 0.3 to 0.5. The higher modulation index attainable in FM is one of the advantages of this type of modulation.

FM is frequently divided into two classes for discussion—"wide band" and "narrow band". "Narrow band" always has a smaller modulation index (less frequency swing) than does "wide band", but beyond that

the terms "wide" and "narrow" are strictly relative.

For instance, when hams talk of narrow-band FM (NBFM) they mean FM with less than 3 kHz frequency deviation or swing, as prescribed by FCC rules for operation below 52.5 MHz. In this kind of conversation, "wide band" means anything with wider deviation than 3 kHz.

But in the two-way communications industry, "wide band" means anything greater than 15 kHz or so swing, and "narrow band" is anything less. Thus a signal with 5 kHz swing would be "wide band" to a ham and yet "narrow band" to a two-way man.

It gets worse. FM broadcasting has a maximum frequency deviation of 75 kHz while TV's deviation (on the FM audio part of the TV signal) is 25 kHz. The TV audio signal is sometimes called narrow-band since it is not as wide as FM broadcast. So it all depends to whom you're talking.

We've used another FM term, "center frequency", quite a bit already without defining it. That's the frequency of the carrier when no modulation is present. It gets its name because it's at the "center" of the channel. Frequency deviation is to both sides of the center frequency. If your center frequency is 50.055 MHz, for instance, and you are using 3 kHz deviation, your signal may swing from a low of 50.052 to a high of 50.058 MHz as it is modulated.

The final important term in FM is "threshold"; FM signals have a special characteristic not found with any other type of modulation. When they're strong enough, they actually take over and suppress background noise. They even suppress any interfering signals on the same channel. Up until the FM signal is strong enough to exercise this "capture effect", though, you can't even find it.

The signal strength at which the signal is "strong enough" is known as the "threshold" of the signal. It is determined almost exclusively by the modulation index of the signal. The greater the modulation index, the greater the signal you must have to reach the threshold—but the greater will be the noise suppression, once the threshold is reached.

For illustration, if an FM signal has a

modulation index of 1 (such as a ham NBFM signal), the signal must be about 3 db above the background noise for the threshold to be reached. By the time the signal is 4 db above noise, capture effect has cut in and the noise is reduced another 4 db. This gives an 8 db signal-to-noise ratio, twice as good as that provided by the signal alone.

If, however, that same signal had been a ham WBFM signal with modulation index of 4, it would have had to be at least 10 db above the noise level to reach the threshold. The improvement, however, would have been almost 15 db instead of just 4—so that the received signal would be 25 db above received noise instead of merely 10 db. The total signal-noise ratio, in this case, is 3 times better than that for the NBFM signal.

How are rf amplifiers adjusted for proper operation? Like any other amplifier, an rf amplifier consists of three major portions—the input circuit, the amplifier itself, and the output circuit. To operate properly, all three of these portions must be functioning as the designer intended.

The adjustments available to us as operators, though, normally affect only two of the three portions. The amplifier itself usually has no adjustments which we can readily reach (although in some cases, bias on the amplifier tube is adjustable). Operating adjustments—for any rf amplifier, linear or not—are usually limited to those for drive, tuning, and loading. The drive adjustment is a part of the input circuit, while tuning and loading are in the output circuit.

All rf amplifiers must be properly tuned in order to operate. This is accomplished, as you probably are aware, by applying a steady input signal and tuning for a pronounced “dip” in final plate current. The only critical point here is to be certain that the amplifier is tuned to the desired frequency rather than to some unwanted harmonic of the input signal—and that’s a relatively easy check to make.

The differences in adjustments for the different kinds of amplifiers (CW, modulated AM, linear AM, or sideband linear) show up most prominently in the drive and loading controls, although loading and tuning adjustment do interact with each other. Before we look at the details of these ad-

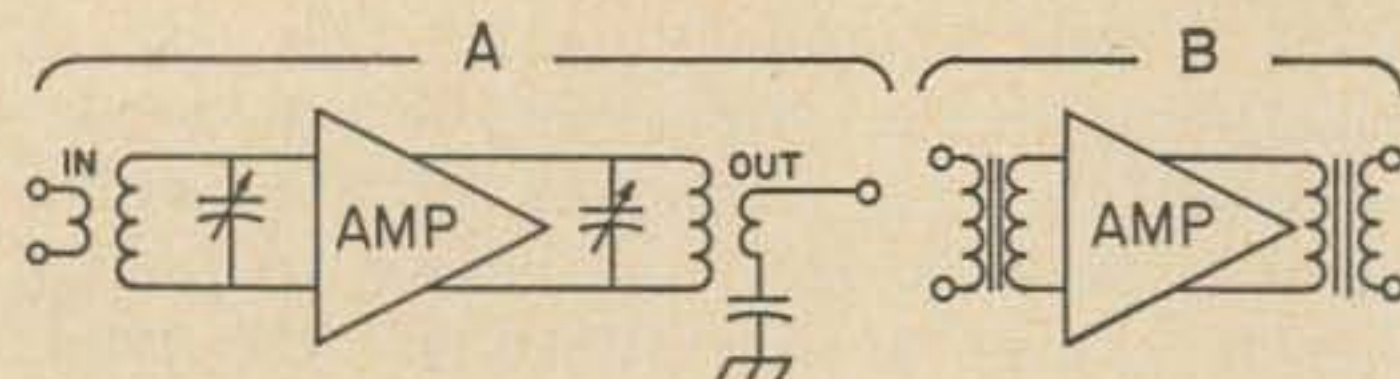


Fig. 1. A typical rf amplifier circuit is shown at left; Audio equivalent at right. Adjustments are drive (input circuit), tuning (output circuit), and loading (indicated).

justments, let’s examine again how any such amplifier works.

Fig 1 shows a block diagram of a typical rf amplifier. This may be a linear, a CW final, or a high-level modulated unit; it makes no difference. In fact, you could even replace the input and output tank circuits with transformers as shown in Fig. 1B and it would be a good audio amplifier (if the tube voltages were properly chosen).

The tube amplifies the signal, by using the grid *voltage* to control plate *current*. The particular class of amplification (A, B, or C) and a major portion of the amplifier’s linearity as well will be determined by the voltages applied to the tube.

The input circuit’s main job is to provide the desired amount of voltage swing to the grid of the tube. Depending upon the amplifier design, this circuit may have to transform “power” input into voltage for the grid, or it may merely have to transform the voltage to a higher or a lower level than that swing provided by the preceding stage.

The output circuit has many jobs, but we’ll concentrate on only one: it provides the “transformer” action necessary to convert the plate current swing into rf power at the right impedance level to feed our antenna line. This normally involves an impedance step-down, just as an audio amplifier ends up at a transformer which steps the output tube’s impedance down to match a speaker’s voice coil.

When this step-down is correct, the output circuit provides a “load” for the tube—and the choice of voltages for the tube depends in part upon the load seen by the tube. Thus all three major parts of this circuit interact with each other, and no one can operate properly unless both the others are also in the right ball park at least.

An audio amplifier is a broad-band device; the average stereo console amplifier handles a frequency range from below 50

Hz up to at least 15 kHz, which is a 300-to-1 ratio. *rf* power amplifiers, on the other hand, are all relatively narrow-band. Even a "broad-band" final which would cover 80 through 10 meters without retuning would be covering only a 10-to-1 frequency ratio. And the average final tuned to, say, 3900 kHz is covering only about a 3 kHz bandwidth, for a 1-in-1300 ratio of bandwidth to frequency.

The broad-banded audio amplifier requires a specially designed transformer to provide its output circuit. Handling *rf* as we do, we get out more easily. A simple tuned circuit, if properly adjusted, does the impedance transformation for us. One of the "proper" adjustments, though, is the tuning. The other one is the "loading" adjustment, which actually adjusts the coupling between the amplifier and the antenna. The effect is to change the transformation ratio of the output circuit.

The tube's load, provided by the output circuit, is electrically the same as a large resistor. Adjustment of the "loading" controls varies the effective resistance. The lighter the loading, the higher the effective resistance. With higher resistance, less plate current flows and the "dip" when tuning is extremely deep.

The higher resistance also, though, means less power can be transferred through the circuit—or even produced by the tube in the first place. With light loading, the tube is virtually loafing along and little power is delivered to the antenna. This is bad for any *rf* amplifier because all that *potential* power's energy is still wandering around the rig in the form of excessively high voltage swings, and sparks may be expected at the very least.

As loading is made heavier by increasing the adjustment of the loading control, the effective resistance of the output circuit goes down. As the resistance drops, more plate current flows. The additional plate current is able to produce more power by using that high-voltage energy, and the increased coupling which increased the loading in the first place permits more of that extra power to flow out to the antenna.

With a normal class C amplifier (non-linear), standard practice is to crank up grid drive until rated grid current flows, tune the final for the dip which indicates that it is tuned to proper frequency, and increase

loading until the desired amount of plate current is indicated on the meter (taking care that the tuning remains correct, since a change of loading will affect the tuning adjustment also).

If you're going all out for maximum power, you may keep on cranking up the loading until the "dip" is virtually undetectable in the belief that this is producing maximum output.

Unfortunately, when you get the effective resistance of the output circuit down to a much lower value than the designer intended in the first place, the amplifier actually puts out *less* power—although it continues to draw more and more current, as you would expect with less resistance. This too is a condition to avoid; the extra current isn't going to the antenna, but is merely trying to melt out your rig!

If maximum power output is your goal, you must have some type of relative power indicator to tell how much is actually getting out. This can be anything from a SWR bridge in the feedline to a field-strength meter—or even a pilot bulb coupled to the feedline, not to the final tank where it won't tell you nearly as much. Then increase loading so long as the power output keeps climbing—and stop!

Drive, the third adjustment, is relatively uncritical in a class C rig. The only requirement is that there be enough of it. Good operating practice indicates that there should *not* be an excess of drive, which will increase the chances of harmonic problems. The grid-current ratings, though, are not Gospels. Once the rig is tuned and loaded properly, drive can be reduced until a reduction in power output is just detectable, and then increased about 20% above this point. For CW use, no increase is necessary. If the rig is modulated, though, additional drive is advisable in order to have a reserve on hand for peaks of modulation.

So far we've looked at the three adjustments for non-linear amplifiers. What happens to them if we are trying to be linear instead?

Tuning remains pretty much the same, if we keep in mind that the permissible operating range of the tube is much more critical for linear than for non-linear use. If the amplifier is properly designed, though, this factor will already be taken care of.

Loading is much more critical. Either under-loading or over-loading in the output

circuit of a linear leads directly to distortion.

Drive adjustment also is much more critical. Under-drive is no problem, but excessive drive will lead directly to severe distortion and splattering. Let's look at these two adjustments more closely.

When a linear amplifier is not loaded heavily enough, the effective resistance of the output circuit is too high. At very low levels of input signal this has no harmful effect—but as the input signal increases during transmission of even a single syllable of speech, the too-high resistance sets a limit beyond which output signal cannot climb.

The result is peak clipping, which generates splatter all over the bands and can even put the suppressed sideband back on to the signal.

As the load increases, by adjusting for tighter coupling to the antenna, the effective resistance of the output circuit decreases. When it gets to the point at which the amplifier circuit was designed to operate as a linear, the maximum output power is developed and distortion is minimum.

Increasing loading still more reduces output but does not add significant distortion until the over-loading is severe. Usually the tube is damaged by excessive power dissipation by the time this point is reached.

Distortion is still present in an amplifier which is too heavily loaded, although it is not so severe as in one which is under-loaded. The distortion created by too-heavy loading is more usually in the form of intermodulation or "third-order" distortion, which is not so obvious when listening to the desired output signal but which does put back in parts of the sideband you went to such trouble to get rid of in the first place.

While the loading of a non-linear amplifier can be checked quite easily by means of an output-power indicator, that of a linear amplifier virtually requires oscilloscope measurements of the signal. We'll go into this a little later, since most improper operation of linears is due to maladjustment of the drive rather than of loading.

The drive adjustments are probably the most critical ones in adjustment of a linear amplifier. Excessive drive in a linear is a sure way to generate a lousy and illegal signal.

The idea, in adjusting drive to a linear,

is to provide *enough* drive for the amplifier to operate properly yet not provide *too much*. Since a linear's input signal may be anything from no signal at all up to the maximum permitted by the drive adjustments, the condition of "too little" drive simply cannot exist. All the adjustments have to do with setting an upper limit beyond which drive cannot go.

In the initial adjustment of a linear rig, each stage from the exciter on out to the final must be adjusted individually. Only after the lowest-power stage in the rig is operating properly can you move on to the next stage toward the antenna. Of course, if you're adjusting a factory designed and built unit, most of this will have already been done for you.

In each stage, the drive must be adjusted so that enough is available to drive that stage to the full rated undistorted output, without driving it over the limit into distortion. Once distortion is put into the signal, at any stage, getting it back out is like trying to remove one piece of solder from the middle of a molten blob on the bench!

In many rigs, the output circuit for one stage is a part of the input circuit of the next. In these cases, the loading control for the first stage is the drive control for the second, and so forth.

With such rigs, the "drive" control employed for final operator adjustment is usually the audio gain control on the exciter. To tune such a unit up—and the same practice can be employed for any linear amplifier—first apply an audio signal a little stronger than your mike can ever develop to the mike jack and ascertain that the audio amplifiers in the exciter can handle this signal without distortion.

When the exciter is adjusted to produce undistorted output from such an input signal, connect the exciter to the linear amplifier and adjust the linear one stage at a time until each, in turn, is producing its rated output—still without distortion.

Should any stage prove incapable of producing its expected output, check that stage carefully. Try adjusting the loading for that stage, as well as rechecking all previous stages.

When the entire amplifier is tuned up in this manner, it will be able to handle any signal delivered by the mike in a linear fash-

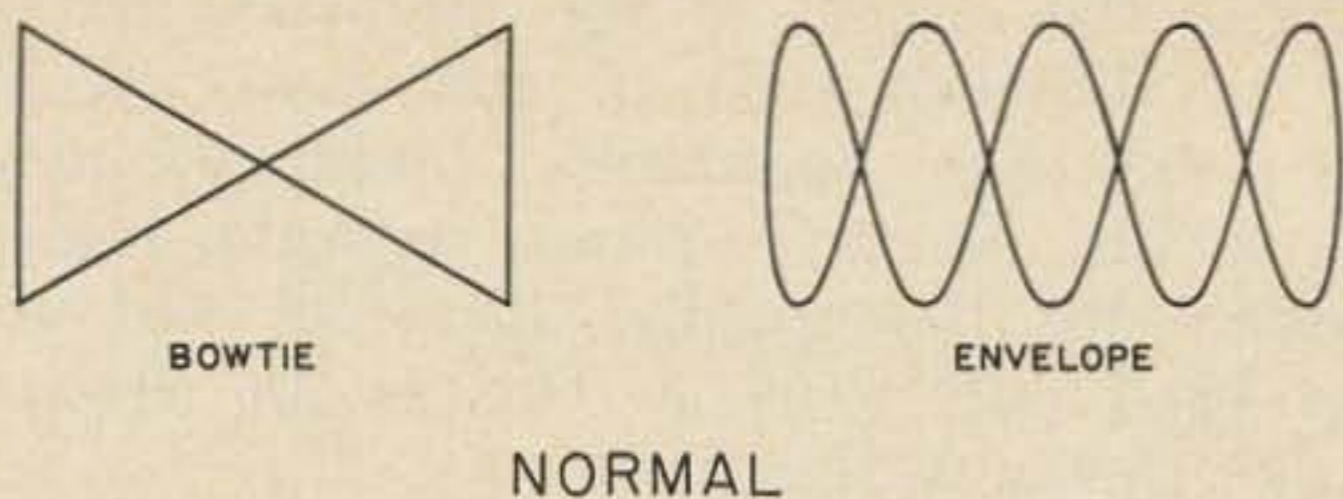


Fig. 2. Oscilloscope displays above are normal indications of linear-amplifier operating properly.

ion. Lock all the adjustments except final tuning and drive.

It should go without saying all these adjustments should be made using a dummy load, rather than with the rig actually on the air. If a legal-limit amplifier is being tuned in this fashion, it will be operating at several times the legal limit during the final stages of adjustment.

All that is now necessary to complete adjustment on the air is to retune the final and readjust final loading after connecting the antenna, to the same operating conditions. This is easiest to do if, after the initial tune-up, you reduce the audio gain until the rig is operating at about half its rated power. Note the audio gain setting and final plate current. With steady-tone audio, plate current will also be steady.

Then after connecting the antenna just apply the same input signal with the same audio gain setting, and load for the same value of plate current. The same loading conditions will automatically be established.

From this point on, the only operating adjustment is the audio gain control—which determines the drive applied to the entire rig.

To determine the proper settings, though, requires (as we mentioned earlier) a scope hooked up to view the output signal. Either an "envelope display" or "bow-tie" pattern can be used. Fig. 2 shows the output patterns to expect from either when everything

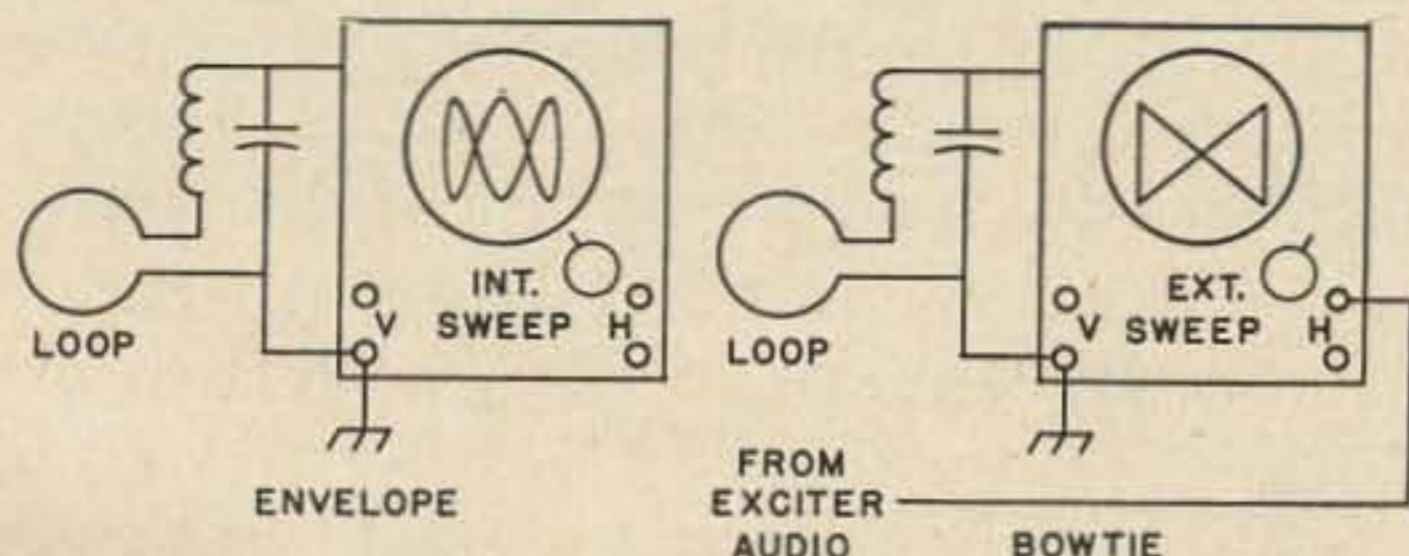


Fig. 3. Test set-ups for both types of displays. In either case, tank circuit is tuned to operating frequency and connected through a capacitor directly to vertical deflection plate of CRT.

is correct. Fig. 3 shows the hookups for generating both types of displays. Fig. 4 shows some of the abnormal patterns you may get with excessive drive, under-loading, or over-loading.

What are the popular power supply circuits and how do they work? Power supplies show up in many places. In this question, we aren't even considering the transistorized power supplies used for mobile work, either. But receivers, transmitters, and test equipment alike share the requirement for dc to operate—and the wall plugs provide us with ac. The power supply does the job

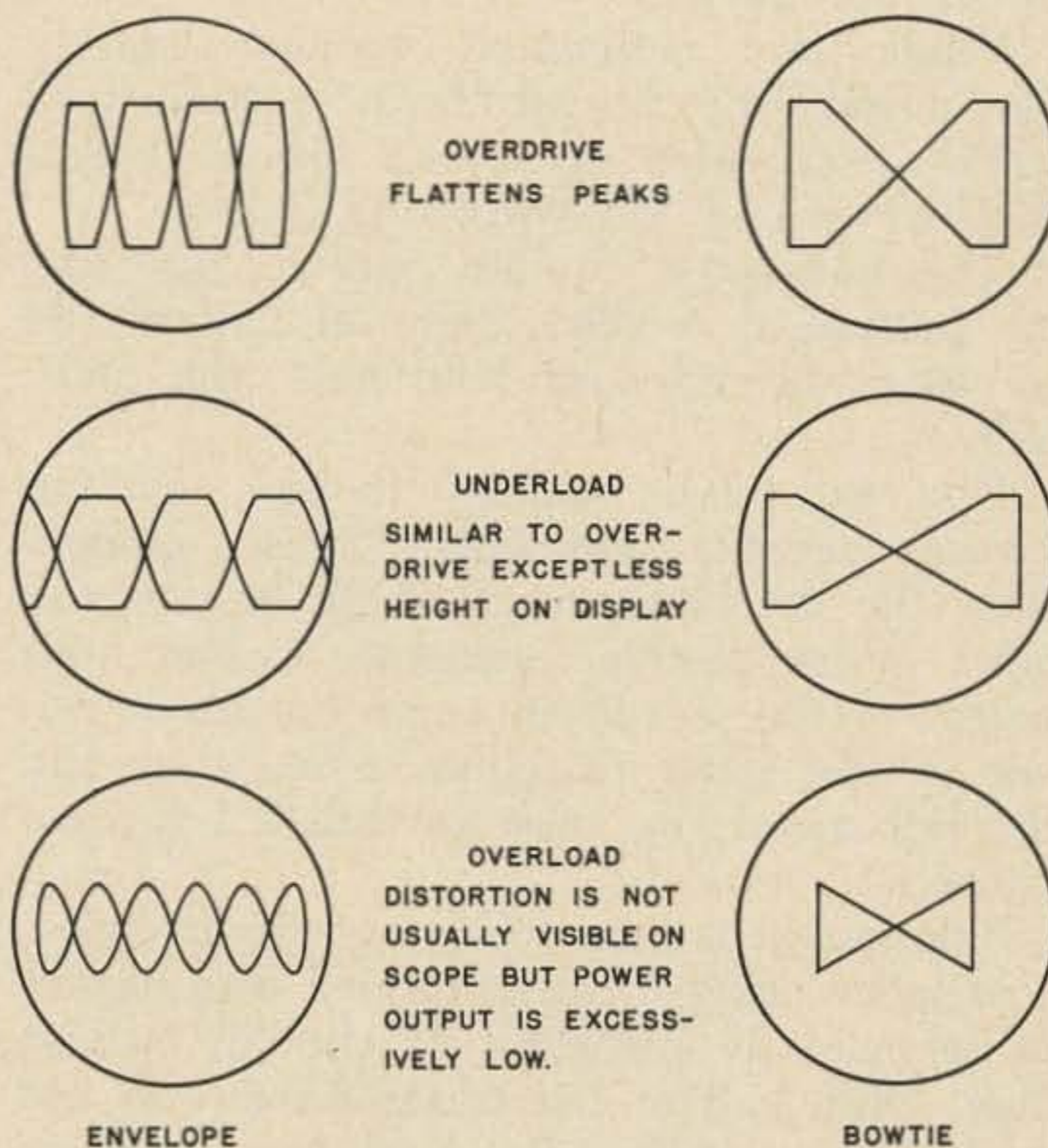


Fig. 4. Typical patterns exhibited by linear amplifier with operation not normal. Refer to SSB handbooks for more detailed views; these are to illustrate the theory involved rather than to provide an operating guide.

of changing the 115-volt 60-Hz ac from the wall plug into dc of the proper voltage and current characteristics to power our equipment.

All power supplies for this purpose employ rectifiers, either solid state (silicon diodes or selenium stacks) or tube type (vacuum tubes or mercury-vapor tubes). Most also employ transformers to adjust the voltage level although some operate directly from the power lines.

The job of the rectifier is to change ac into dc. Any individual rectifier element operates by simply blocking half of the ac waveform so that what gets through is all

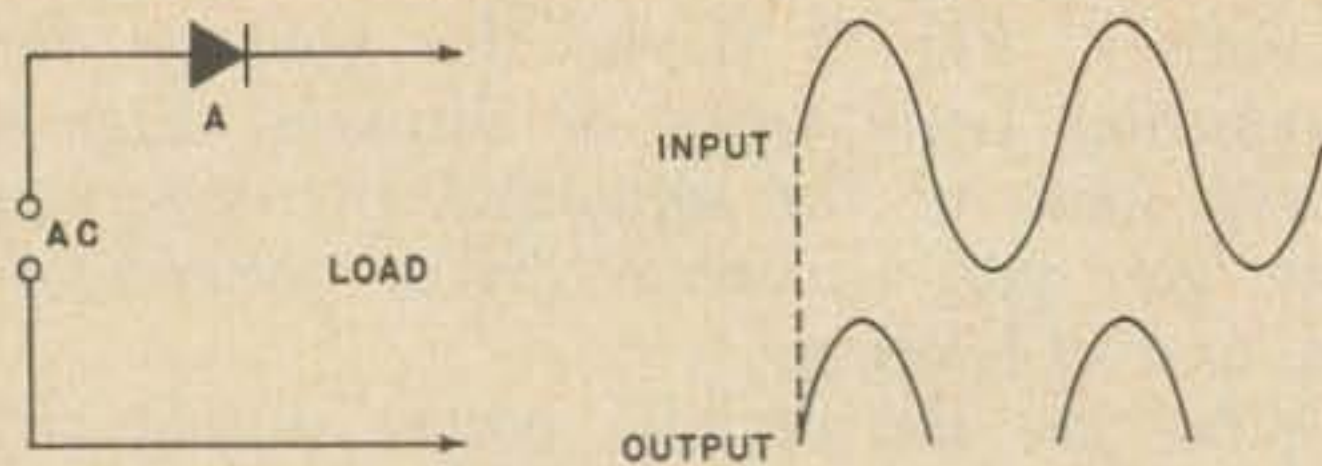


Fig. 5. Half-wave rectifier circuit and waveforms.

going the same direction—and this accomplishes the change. The resulting dc, although still pulsating at a rate related to the frequency of the original ac, is all going the same way. The filter circuit then smooths out the pulsations to provide “pure” dc for our devices.

While any individual rectifier merely blocks half the ac waveform, rectifier circuits are divided into two classes called “half-wave” and “full-wave” respectively.

The half-wave circuits operate just like the individual rectifier; they let half of the ac wave through and hold back the other half.

The full-wave circuits, though, contain several rectifier elements. These circuits *steer* the ac waveform through one or the other of the rectifier elements, so that both halves of the waveform come out as dc going in the same direction. Since they use the full waveform, they are called full-wave circuits.

The most common full-wave circuit cheats a little by using a center-tapped transformer to reverse the direction of the ac current flow. Only half of the transformer is in use during any half-cycle, and the rectifiers determine which half this is.

Fig. 5 shows the operation of this circuit, in comparison to the half-wave circuit in Fig. 6. You can see that the circuits are most similar. In both, rectifier A begins to conduct at the point marked “1” in the waveforms and conducts until the point marked “2”. When time “2” is reached, rectifier A begins blocking current flow. In the half-wave circuit, no current flows again until time “3”. In the full-wave circuit, rectifier B begins to conduct at time “2” and conducts until time “3”. However, rectifier B is connected to the other side of the transformer center-tap, and the circuit’s electrical return path is through the center tap. Thus the transformer is effectively turned end-for-end at time 2, and back to its original position at time 3. Both halves of the input ac are used—but only half the transformer is in use at any given instant.

With the advent of the solid-state rectifier, a different type of full-wave circuit has come into popularity. (With vacuum tubes, the circuit requires separate transformers for the rectifier filaments and so was used only rarely.) This is the bridge circuit shown in Fig. 7.

The major advantage of the bridge circuit as compared to the older full-wave circuit of Fig. 5 is that the full, transformer secondary is used at all times. It also permits full-wave rectification without requiring a transformer. The bridge circuit operates entirely by “steering” current flow.

For instance, at the point marked “1” in the waveforms both rectifiers A and C can conduct while rectifiers B and D are blocked. This condition continues until time “2”, and so current flows out of the bridge as indicated by the arrow.

At time 2, the polarity of the ac input reverses. This blocks rectifiers A and C, but permits rectifiers B and D to conduct. Current out of the bridge still flows in the same direction.

At time 3, the ac polarity reverses again and returns to the same condition that existed at time 1. You can see that the full ac cycle is steered through to the load, but is always flowing in the same direction when it reaches the load circuit. For half a cycle it flows through rectifiers A and C, and for the other half through rectifiers B and D.

Most tube-type receivers use either the full-wave circuit of Fig. 5 or the half-wave circuit of Fig. 6 (if they are inexpensive receivers without a power transformer). Solid-state equipment, on the other hand, employs the bridge almost exclusively. Transmitter power supplies almost invariably use full-wave rectification because it is more efficient and is also easier to filter into “pure” dc required by law. The choice between bridge and center-tap circuits is about even, though, with medium-power rigs more likely to use the bridge and high-power equipment usually using center-tap circuits together with mercury-vapor rectifier tubes.

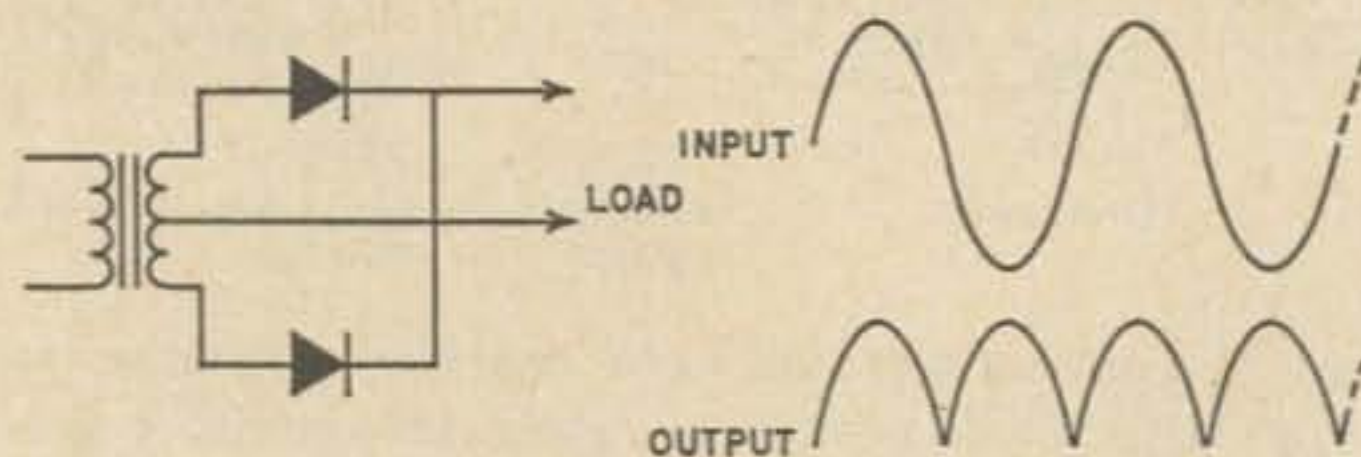


Fig. 6. Full-wave circuit and waveforms.

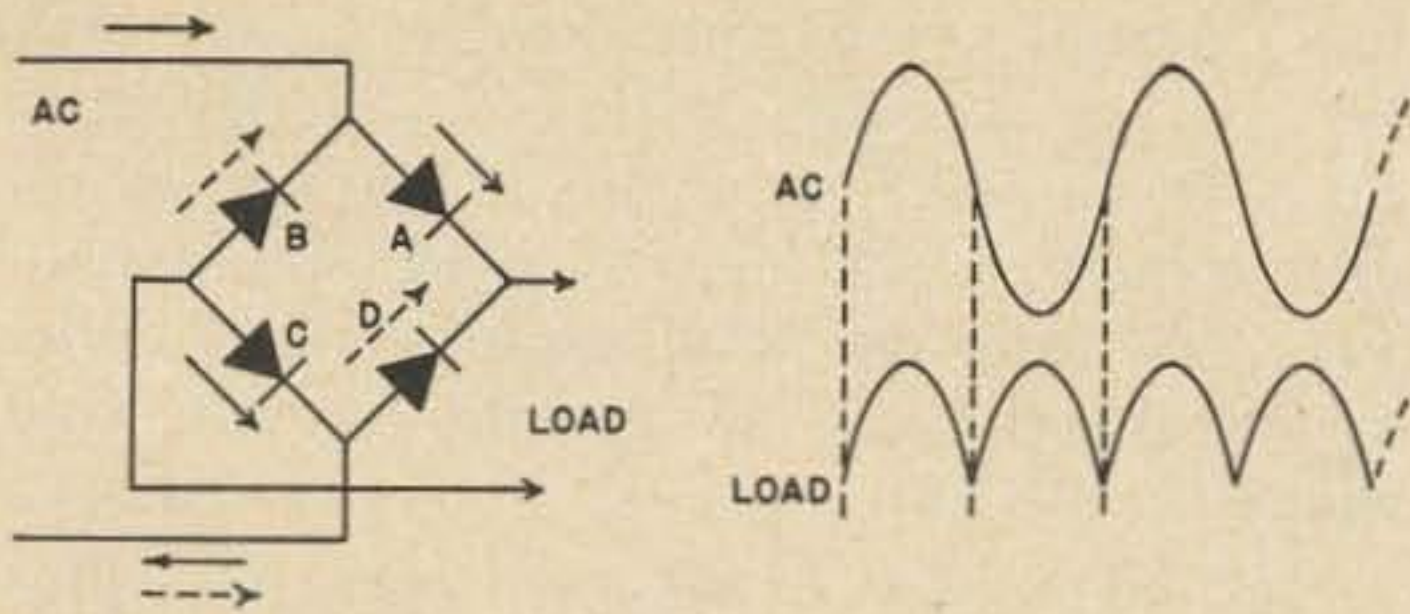


Fig. 7. Full-wave bridge circuit and waveforms.

Why are tube pins connected as they are? The earliest vacuum tubes had only four pins—two for the filament, and one each for the grid and the plate. Many modern tubes have many more pins, but no more elements—and yet every pin is connected to an element. A 9-pin miniature receiving triode for VHF amplifier use, for instance, may have two of its nine pins connected to the filament, one to the plate, three to the grid, and the remaining three to the cathode.

A single wire suffices to make electrical contact between two points. Why, then are tubes built with two, three, or even four pins connected to the same internal elements?

Manufacturers design tubes this way for two major reasons. Both reasons have to do with high-frequency performance.

Multiple grid pins are most frequently found in tubes intended to be used as grounded-grid amplifiers at VHF. In such an application, it's important that the grid actually be at ground for the *rf* as well as for dc. In fact, there's really no need for a dc ground so long as the grid is completely grounded for the *rf*—and some circuits are so designed.

And while a single wire suffices to make electrical contact between two points so far as dc is concerned, it may *not* do so for *rf*.

Any wire has a certain amount of inductance, even if it's not bent into a coil. To high-frequency *rf*, this inductance acts about the same way a resistor does to dc. A single wire, if it has great enough inductance, *doesn't* make proper electrical contact.

The inductance can be reduced by shortening the wire's length, or by using larger wire. In a tube, though, both the length of the wire and its maximum diameter are fixed by mechanical considerations. A limit

is soon reached, for any particular tube design, beyond which the inductance of each lead cannot be reduced.

Three resistors connected in parallel will have only one-third the resistance of each one individually (if all are of the same value). Similarly, three separate leads connected in parallel will have one-third the effective inductance of one.

Thus by using more than one lead, with a separate pin for each, the tube designer can reduce the inductance between the actual tube element and the point outside the tube to which it is connected.

That's one of the reasons. Associated with this reason is a sub-reason: In any circuit using a vacuum tube, the reference "ground" point for the circuit's current flow is *not* the equipment chassis. Instead, it is the tube's cathode. All plate and/or grid current must flow through the cathode surface.

Since the cathode must be in vacuum inside the tube, though, you can't get to it directly to make any connections. All your connections have to be made to the tube's pins.

The inductance of the leads from the pin to the cathode itself, as we said, acts about like a resistor. When current flows through a resistor, it produces a voltage across that resistor. Similarly, when *rf* flows through an inductor it produces a voltage across that inductor—even if the inductor is a length of wire inside the tube.

Modern amplifier tubes have extremely high gain. A very small signal in the grid circuit is amplified into a rather large signal in the plate circuit.

The cathode's surface is in both the grid and the plate circuits. This cannot be avoided. If both the grid and the plate external circuits return to the cathode by way of the same tube pin, then the inductance of the lead from cathode surface to pin is also in both the grid and the plate circuits.

And when the amplified signal in the plate circuit flows through this inductance, the resulting voltage is automatically in the grid circuit as well. The result—feedback and possible oscillation (see Part III of this series for more on this).

By using two or more separate pins, each with its own leads, from the cathode to the rest of the circuit, the lead inductance can be kept effectively out of the picture. With the grid circuit returning to one pin

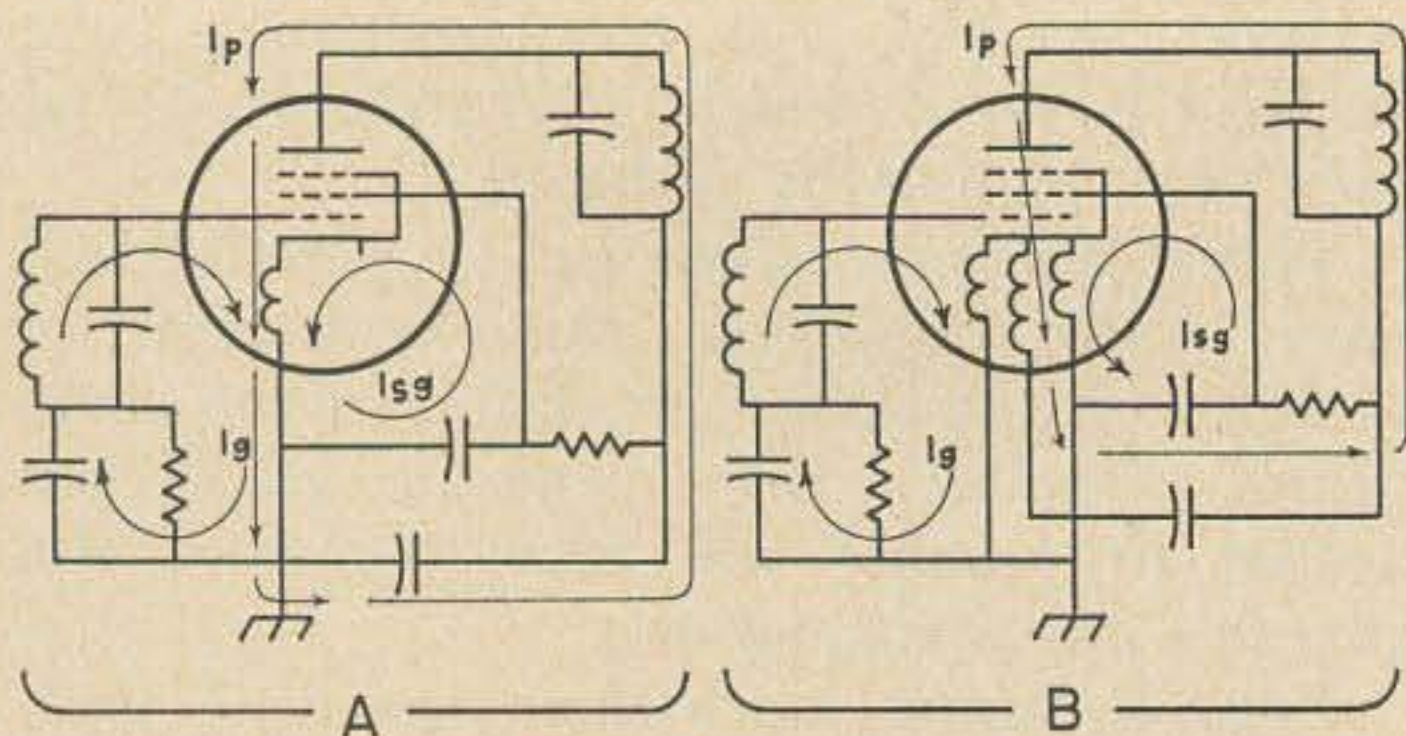


Fig. 8. Multiple pins are used in modern tubes to provide separate paths for input and output circuits involving same element. A shows only one cathode pin is available, so grid, plate, and screen current all circulate through inductance of single cathode lead and may interact. Three separate pins in B permit the three circuits to be kept completely separate. Effect is of importance only at high frequencies.

and the plate circuit to the other, any voltage developed across the plate circuit's lead inductance cannot get into the grid region—and one built-in source of feedback is eliminated. This is the reason that most modern high-gain transmitting tubes provide multiple cathode connections, as in the 6146.

Fig. 8 shows this effect pictorially. The lead inductance is shown as an *rf* choke—because, as the frequency gets high enough, that's how it acts. And we learned back in Part III of the series that feedback can be effective at *any* frequency, not just at the frequency you're tuned to. The type of feedback the multiple pins are intended to eliminate is one of the primary causes of parasitic oscillation.

The other major reason for use of multiple pins also has to do with feedback, but does not involve lead inductance at all and is usually applicable to VHF receiving tubes *not* intended for grounded-grid amplifiers.

Many of these tubes have multiple cathode pins, all of which are intended to be strapped directly to ground. These pins are located on the base in positions which separate the grid, plate, and other-active-element pins. When all these pins are grounded, they form effective shields to reduce feedback between input and output circuits of the tube.

The pin arrangement on multi-section-receiving tubes is also chosen with a sharp eye toward the intended uses of the tube. Pins are usually located in such a manner

that external connections can be made with the shortest possible wires. This is the reason why several types of tubes are available having identical electrical characteristics, but different pin arrangements—some are arranged for one specific circuit, and others for others.

Not all tubes, of course, even use pins for the external connections. The popular 4x150/4CX250 series of power tubes, for instance, has no plate pin; the outer shell of the tube is the plate and any connection is made directly to it. The older "lighthouse" tubes featured similar construction, as does the 416B UHF tube. Planar tubes carry this idea into today's designs. Again, elimination of lead inductance and shielding between input and output circuits are the primary reasons for such arrangements.

What is output power, anyway? One of the least understood quantities we'll ever deal with in radio is that known as "transmitter output power".

For instance, most of us are aware that the maximum legal *input* power to a transmitter, as indicated on the meters, is 1000 watts. It's also no secret that most transmitters are at best no more than 75% efficient at turning this input power into output power, so it would be logical to expect that the maximum legal output power would be somewhere fairly close to 750 watts.

However, it's possible to run a rig *legally* on the HF bands with as much as 4000 watts input power and corresponding 3000 watts output power with one type of modulation while another type of modulation is restricted to only 1000 watts in and 750 watts out. When you get into the VHF and UHF regions where pulse modulation is permissible, input powers on the order of 100,000 watts can be had legally. At these frequencies efficiency drops so your output probably won't exceed 50 kilowatts or so—but still!

The trick in all this lies in that innocent phrase "as indicated on the meters". Even when running 100-kw peak input during pulse modulation, the meters must not exceed a 1-kw input reading. Since meters are relatively slow to react—a dc meter cannot, for instance, react rapidly enough to indicate 60-cycle ac—the meter cannot tell whether you are applying 100 kilowatts for 10 microseconds and then no power at

all for the next 990 microseconds, or are putting in a steady 1000 watts all the time.

This is not the magic trick it might appear to be; the receiver at the other end of the line is hard-pressed to tell the difference either. A 100-kw pulse signal which is present only 1 percent of the time is no more effective than a 1-kw steady signal which is always there. The advantages, if any, of pulse modulation do not lie in the field of getting extra power for nothing.

The 4-kw figure mentioned for HF bands is more of a play on words. Power, either input or output, comes in several different flavors. There is "peak" power—which may mean any of three distinctly different conditions—, "average" power, and "RMS" power.

To get an idea of the different possible meanings of the term "peak power", let's look at an ordinary 60-watt light bulb operating from normal 117-volt ac wall power.

During each cycle of the ac power, the voltage on the line rises from some negative value through zero to a positive peak, then falls back smoothly through zero to a negative peak which is a mirror image of the positive peak, and returns to its original value.

This complete cycle is repeated 60 times every second. And while we call this power "117-volt" or maybe "110 volts", its voltage is actually always changing. It is exactly 117 at only four instants during each cycle—once on the way up between zero and positive peak, once again on the way down, a third time between zero and negative peak, and the final time as it climbs from the negative peak toward zero.

The reason we call it "117-volt" power is that it will produce the same amount of heat in a resistor as would 117 volts of dc applied to the same resistor. This is the "RMS" value, and is a convenient label.

But the peak voltage of this 117-volt power line is actually about 165 volts; it reaches this voltage only twice during each cycle, and doesn't stay there any appreciable length of time either time.

Our light bulb is a resistor. The more voltage we apply to it, the more current will flow. The RMS current in a 60-watt 117-volt bulb would be $60/117$ amp, or about 0.513 amps. The resistance, by Ohm's law, equals the voltage divided by the current or $117/0.513$, which comes out to be about 230 ohms.

Now when we apply that "peak" voltage of 165 volts to the 230-ohm resistor which is our light bulb, we will get a "peak" current of about 1.38 amps—and when we multiply voltage by current to find out the "peak" power we discover that our "60-watt" bulb uses a peak power of 230 watts!

This is an impressive figure, sure. But the bulb doesn't give us a bit more light at peak power of 230 watts than it does at "60" watts. This is *one* meaning of "peak power", and you can see that it's not very meaningful. By this viewpoint, *any* full gallon is running 4000 watts peak input power.

This kind of peak power is sometimes called "instantaneous peak power", because it is present only for an instant at the peak of each cycle of the ac.

A more meaningful way of talking about "peak" power is to discuss "peak envelope power". This refers to the RMS power (or dc power, if input power is under discussion) present when the *audio* modulating signal is at its peak. Most sideband rigs are rated on PEP power.

This kind of peak power is what actually gets the signal through. The figures are much less than those for the same transmitter for "instantaneous peak power", but are higher than for "meter peak power" which we'll discuss next, or "average power". In sideband operation, PEP power is the power you get when the rig is adjusted for maximum linear output as discussed earlier in this installment.

In a FM rig, the output power does not change appreciably with modulation. In a CW rig, the power is either there or it is not. PEP power of a CW rig is the same as the key-down power; the term is almost meaningless for FM.

An AM transmitter, with carrier, is much like an FM or a key-down CW rig when nobody is talking. The carrier is still present. When you modulate, however, the audio power from the modulator is either added to, or subtracted from, the carrier power. The result is that peak envelope power is greater than the average carrier level.

Virtually all of the theory about AM modulation and its effects on power assumes modulation with a steady audio tone rather than voice, because the steady tone is a known signal and voices differ in their characteristics.

With a steady tone, and modulating the carrier to the 100-percent level, the resulting modulated signal's power will drop exactly to zero at the negative peak of the tone's cycle. In order for this to happen, the modulator's average power must be exactly half that of the carrier. On the positive peak of the tone's cycle, then, the envelope will have all the power of the carrier *plus* all the power from the modulator, and so will be half again greater than that of the carrier alone.

The peak envelope power of a 100-percent modulated AM signal—when the modulation is a steady tone—is always half again greater than the PEP of the same carrier unmodulated.

When voice is applied rather than the steady tone, the picture changes. Voices are not symmetrical; their positive peaks may be higher than their negative peaks or vice versa. The "100-percent" modulation point is defined as that amount of modulation which permits carrier power to be reduced to zero at any point in the modulating cycle. If the voice's highest peak comes out as a negative peak from the modulator, this will cause 100-percent modulation to occur with less voice loudness than if it comes out positive. In any case, the average level of the voice is far lower than those peaks—and so the 50-percent increase of power with modulation never occurs.

Now let's look at the "meter peak" power. This is simply the *highest* power indicated by the rig's meters while you're talking. Its chief importance is that *it* is the power which is regulated by the FCC, and must never exceed 1000 watts.

A properly operating AM rig will show no fluctuation at all in the meters when audio is applied, unless it's using "controlled carrier" modulation. Any flickering indicates improper modulation. The theoretical 50-percent increase in PEP is never visible on the meters, because the meters indicate only dc and the power from the modulator is ac in the audio range.

A sideband rig, on the other hand, will flicker widely with speech. So will a CW rig being keyed, or an AM rig using controlled carrier. Regulations specify that power of a CW rig be measured with key down; for the others, the requirement is simply that the meters never indicate power above the legal limit.

Next Month. We've come all this way and managed to bypass those little problems which require arithmetic, such as the calculation of series impedances or determinations of transformer turns ratios. Next month we'll explore those. Don't let the prospect scare you—nothing more complex than arithmetic is involved. Until then, happy hunting. ■

Give "him" or "her"
THE ALL-SEASON

Gift

GREATEST VALUES EVER OFFERED

INCOMPARABLE

telrex
BEAMS



Also: Rotator-Selsyn-Indicator Systems, Inverted-V-Kits, "Baluns," Towers, "Bertha" Masts, 12-Conductor Control Cable and Co-ax. Send for PL68.

The design, craftsmanship and technical excellence of Telrex —

"Beamed-Power"

"Balanced-Pattern" Rotaries

have made them the standard of comparison throughout the world! Every Telrex antenna model is engineered, precision machined, tuned and matched, then calibrated for easy and correct assembly at your site for repetition of our specifications without 'cut and try' and endless experimentation.

COMMUNICATION
SYSTEMS
SINCE 1921

Communication

Engineering

telrex Laboratories

ASBURY PARK, NEW JERSEY 07712, U.S.A.

We say:

the

2K3

is the best \$1000 linear amplifier ever made for the amateur service

(and we sell it for only \$745)

Other manufacturers look at the 2K-3 and shake their heads in disbelief. They say it can't be sold for \$745. But we do it! We do it by working a little harder, by being a little more efficient and by selling DIRECT from factory to user.

Compare the quality of the components used in the 2K-3 and its true value becomes more apparent.

1. Look at the superb 20 mfd 5000 volt test oil filter condenser...exceptional dynamic voltage regulation.
2. Heft the heavy duty, high efficiency transformer...38 pounds of brute power with exceptional voltage regulation and peak current capability.
3. Observe the rugged, high-cost, double section bandswitch.
4. Note the commercial duty 25 ampere mercury power relay.
5. Experience the reliability of special design solid state bridge rectification.
6. Relax with a host of other conservatively rated deluxe components no other competitive amplifier can equal...high efficiency, silver-plated tank coil, silver-plated L-section coil, unique toroid type filament choke, resonant input filter choke, high reliability bronze gear drive assembly, modern design illuminated push-button start-stop switch, all DC relay systems. And there is more, but let us send you a descriptive brochure on the 2K-3. Let us help you own this outstanding linear amplifier.

The 2K-3, Floor Console or Desk Model \$745.00

ATTENTION! Military, commercial, industrial and scientific users... please write for information on our custom line of high power communication linear amplifiers and RF power generators.

EASY FINANCING • 10% DOWN OR TRADE-IN DOWN • NO FINANCE CHARGE IF PAID IN 90 DAYS • GOOD RECONDITIONED APPARATUS • Nearly all makes & models.



1.



2.



3.



4.



5.

Henry Radio Stores

CALL DIRECT . . . USE AREA CODE

Butler, Missouri, 64730

816 679-3127

11240 W. Olympic, Los Angeles, Calif., 90064

213 477-6701

931 N. Euclid, Anaheim, Calif., 92801

714 772-9200

East Coast Rep.: John W. Richardt, Route 46,
Pinebrook, N.J. 07058, (201) 228-0600

"World's Largest Distributor of Amateur Radio Equipment"

MERRY CHRISTMAS

You can do good and do well at the same time. Do good by selling or giving gift subscriptions to 73 to friends. Do well by getting rather nice premiums for your effort or thoughtfulness. Some amateurs are working their way right through our whole list. All subs, other than one for yourself, must be new and will start with the November issue. You can renew yours if you send your address label from the wrapper and it will count towards the prizes. To make some of the bigger items easier to get you have a choice of substituting cash for some subscriptions.



\$5 THREE SHELF ROTATING PARTS BIN

Free with 2 subs or \$3 with 1 sub. Great around the shack or workshop. 11 compartments in each shelf.

\$13 RAND-MCNALLY IMPERIAL WORLD ATLAS

Free with 3 subs or \$6 with 1 sub. 300 pages of maps and info. Fine for DXing, school, arguments.



20,000 O/V V-O-M, 5000 VDC

Free with 3 subs or \$7 with 1 sub. Keep one in the car, one in the workshop and one in the shack. Plus maybe a loaner?

HAMMOND WORLD GLOBE 18" DIAMETER

Costs \$17. Free with 5 subs or \$12 with 1 sub. Wonderful globe for DXing as long as you don't use any pins.



\$25 MINI-TEST LAB

Free with 7 subs or \$15 with 2 subs. VOM, rf-af generators r & c substitution, etc. Incredibly handy.



\$12 WARM CAR BLANKET

Free with 2 subs or \$4 with 1 sub. Handy around house, football, etc. Comes with zipper case & handle.

K & E SLIDE RULE

Free with 2 subs or \$2 with 1 sub. You need a good slide rule every now and then.



Polaroid Big Swinger

Free with 10 subs or \$20 with 2 subs. Uses regular pack Polaroid film, gives big size pictures. Foolproof?


AM-FM 15 TRANSISTOR RADIO

Free with 8 subs or \$18 with 2 subs. This radio sells for \$30 normally. AC or battery.



24 HOUR DIGITAL DESK CLOCK

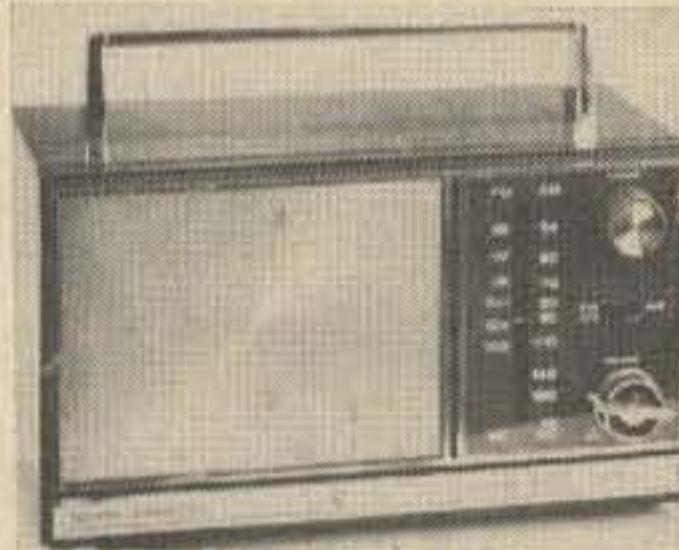Free with 7 subs or \$15 with 2 subs. Large numbers, prize-winning design. Makes ham shack look like \$million. Sells for \$25.



\$35 HI-INTENSITY LAMP-RADIO AND CLOCK!

Free with 8 subs or \$18 with 2 subs. Clock operates radio, etc. Fine for desk.

AM-FM 10 TRANSISTOR AC-BATTERY RADIO

Free with 8 subs or \$18 with 2 subs. Works like crazy. Fabulous gift too. Be loved.




HAMMOND 18" LIGHTED \$25 WORLD GLOBE

Free with 6 subs or \$12 with 2 subs. Get two, one for jr op. No pins.

NAME & CALL PLATE

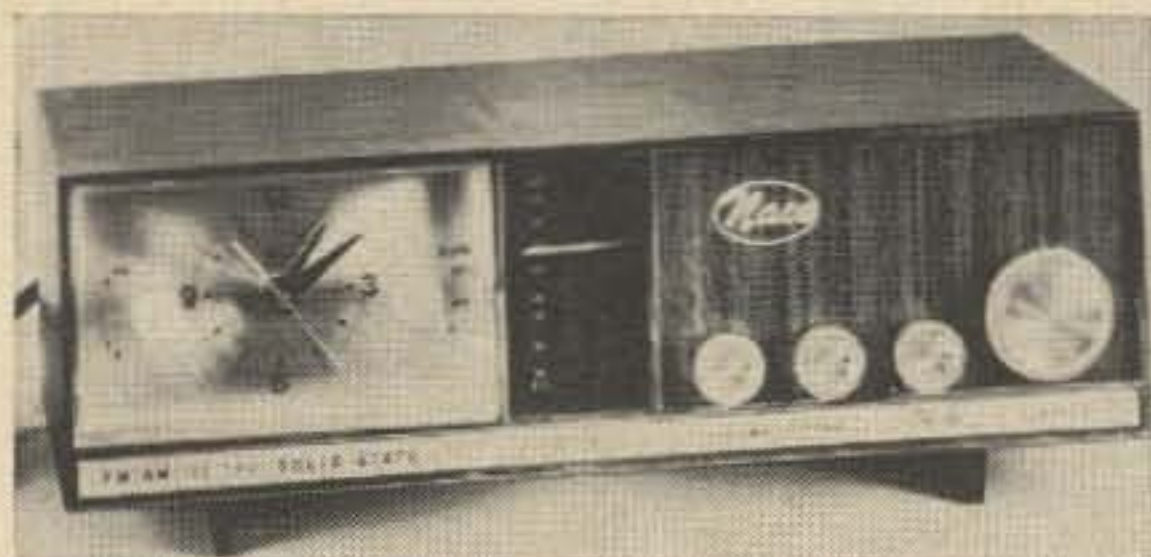Free with 1 sub. Up to 20 letters and spaces on 10" desk plate. Walnut with white letters.







AM-FM TELECHROME CLOCK RADIO

Free with 12 subs or \$30 with 2 subs. This really beautiful clock-radio usually sells for \$65. Has buzzer, radio alarm, slumber button, and delayed snooze turn off. Give yourself one . . . or the XYL.

\$50 CASSETTE TAPE RECORDER

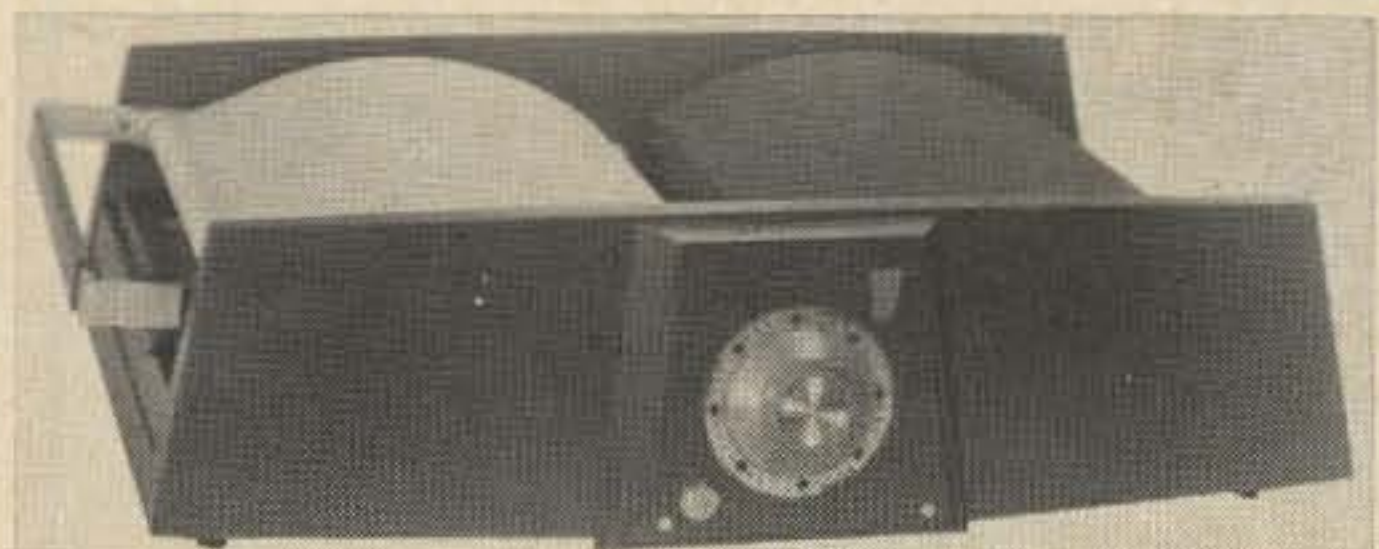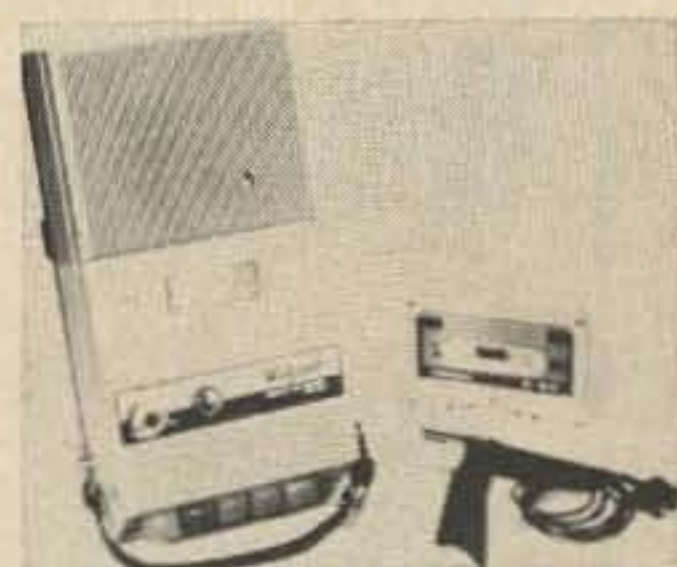Free with 12 subs or \$30 with 2 subs. We tested a dozen recorders before we found this darby. Really works. Record birds, rare DX, family squabbles, jokes, singing. Sneakily small.




COPYMATE PHOTO COPIER MACHINE

Free with 10 subs or \$24 with 2 subs. This does every bit as good a copy job as a well known \$400 copier and uses same inexpensive paper. Comes with paper all set to go.

DIGITAL CLOCK AM-FM RADIO

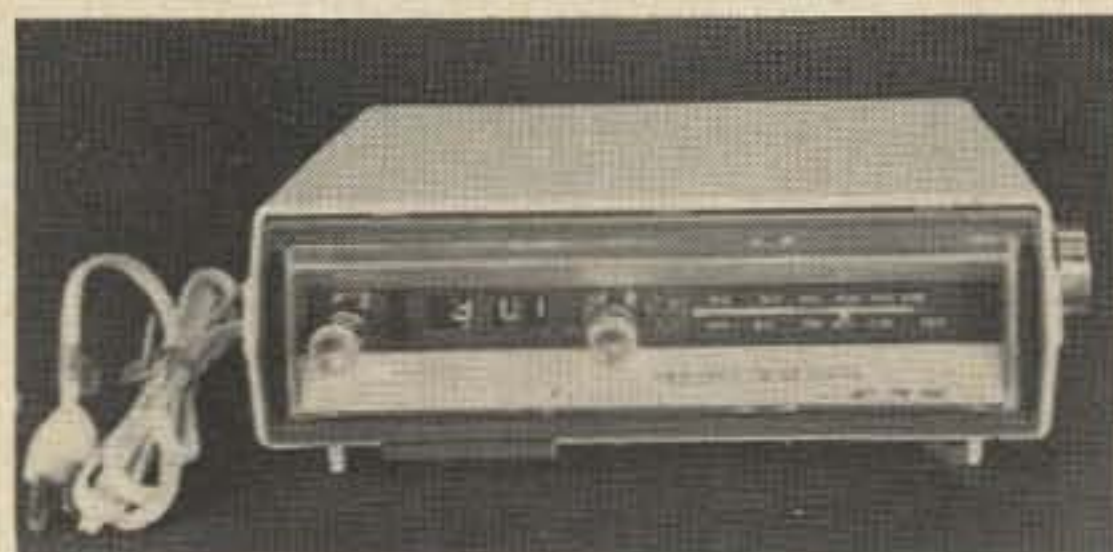Free with 9 subs or \$20 with 2 subs. This is the only digital clock radio we've ever seen. Fine FM radio built in with sleep alarm, buzzer, whole schmear. Like the unusual and new?



OPERATING DESK

Free with 9 subs or \$23 with 2 subs. \$35 desk just right size for modern transceiver ham station. Shipped FOB factory in Michigan.





RAND-MCNALLY MAGELLAN WORLD GLOBE

\$15 globe free with 3 subs or \$8 with 1 sub. You can't beat a deal like that.

CASLON 601 DIGITAL DATE-DAY CLOCK

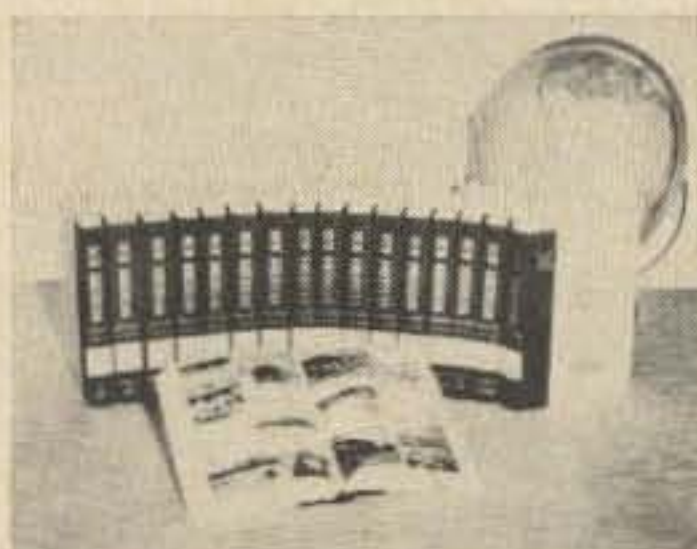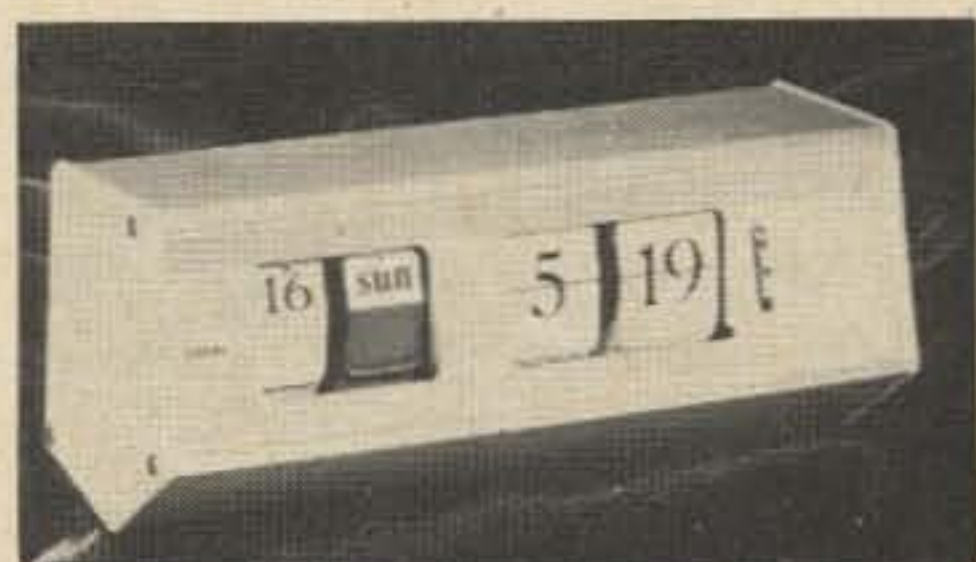This \$50 Ferrari of desk clocks is free with 12 subs or \$32 with 3 subs. Brushed aluminum. The last word in operating aids. 24 hour clock, naturally. Those who can't tell time should specify the 12 hour model.



\$160 ENCYCLOPEDIA SET

Free with only 20 subs or \$45 with 8 subs. This is a first rate encyclopedia. This one is FOB the publisher. Tap your fellow club members for 73 subs and win this mass of books.

Send each gift subscription on a separate 3 x 5 card with name, call, address and zip. All must be new one year \$6 subscriptions to start with the December issue. You want to renew your own subscription? OK, if you include the label from your wrapper. On another card write your name and address and indicate which prize you wish. Allow up to eight weeks for delivery in case we are back ordered from the factory. Prizes will be sent postpaid unless otherwise stated. This offer is good for the USA and APO only and expires shortly.

73 MAGAZINE, PETERBOROUGH NH 03458

Unique opportunity to own one of the world's finest all-band receivers. 500 kc to 32 mc!



R-390A/URR
Radio Receiver

Limited quantity of famous R-390A/URR radio receivers . . . brand new. Original manufacture, 1968 production . . . fully tested to meet U.S. Government specifications. Range 500 kc to 32 mc, 30 1-mc bands, digital readouts. Original pack, includes two instruction books, complete set running spares. New low price \$1,700* . . . fully guaranteed.

*A few new, but shelf-worn, units available at lower prices.

WRITE OR CALL FOR DETAILS

EAG Industries, Inc., 20 Bridge Avenue, Red Bank, N.J./201/747-5100, Ext. 51.

W2NSD/1 from pg 4

more difficult job of creating hypotheses which fit the data." He goes on further to say, "I have concluded that the earth is being visited by intelligently controlled vehicles whose origin is extraterrestrial."

Dr. McDonald of the University of Arizona has been studying UFO reports on an intensive basis for over two years and has interviewed several hundred witnesses. He has reluctantly come to the conclusion "that the UFOs are entirely real and we do not know what they are, because we have laughed them out of court. The possibility that these are extraterrestrial devices, that we are dealing with surveillance from some advanced technology, is a possibility I take very seriously." Dr. McDonald goes on further to say, "For the record, I should have to state that my interviewing results dispose me toward acceptance of the existence of humanoid occupants in some UFO's. I would not argue with those who say this might be the single most important element of the entire UFO puzzle."

Friends, something very definitely is up here and it looks as if a large responsibility for the expansion of investigation of the

UFOs rests on the shoulders of amateur radio. With only a small amount of organizing we can be set up to provide nationwide alerting when UFOs are spotted.

Send for the free 250 page book on the Congressional Symposium and read about hundreds of virtually unarguable sighting cases . . . cases that have been exhaustively investigated. Read about hundreds of pictures and films that have been taken. See 63 UFO photographs assembled on one page.

Next comes the need for your own personal decision that you are going to try to help those interested in doing something to bring this problem out into the open. Your interest and a little time are needed to get the amateur radio UFO network built up into a 24-hour a day alerting amateur net. Amateurs who have substantial signals and will be available on the same evening week after week for about an hour of net operation should drop a card to Jim Sipprell K2HYQ, the overall net coordinator, at Box 209, Kenmore, New York. The frequency is 14.3 and the time is 0200 GMT, which is 9 PM EST.

By next spring I hope we will be ready to get everyone interested in the net set up

with an alerting system. I believe that we will use a 60-cycle calling arrangement. This will be easy to standardize. Graybar has some 60-cycle tuned relays available inexpensively which can be hooked up to the receiver and left tuned to the Net channel. They are sensitive to within a half cycle so other frequencies won't bother them. When any station comes on the net channel and sends a tone which is modulated with a 60-cycle note the relay will pick up and let you know. This means that both AM and SSB stations can work together in the net.

If you feel that you are ready to become involved in something really important then join the UFO net merely by checking in on any Wednesday night. In your own area you should contact your newspaper, radio and television stations, and police and let them know that you are a member of a national communications effort towards investigating UFO's. Ask that any reports be given immediately to you and offer to let them know, if they are interested, if something should appear to be headed your way from some other area.

... Wayne

radio amateur callbook



GET YOUR NEW ISSUE NOW!

Over 283,000 QTHs
in the U.S. edition
\$6.95

Over 135,000 QTHs
in the DX edition
\$4.95

See your favorite dealer or order direct (add 25¢ for mailing in U.S., Possessions & Canada. Elsewhere add 50¢).

These valuable EXTRA features included in both editions!

- QSL Managers Around the World!
- Census of Radio Amateurs throughout the world!
- Radio Amateurs' License Class!
- World Prefix Map!
- International Radio Amateur Prefixes
- Radio Amateurs' Prefixes by Countries!
- A.R.R.L. Phonetic Alphabet!
- Where To Buy!
- Great Circle Bearings!
- International Postal Information!
- Plus much more!

**WRITE FOR
FREE
BROCHURE!**

RADIO AMATEUR
callbook INC.
Dept. B, 4844 W. Fullerton Ave.
Chicago, Ill. 60639



GSB 201 MK III

10-80 METER LINEAR AMPLIFIER

...THE WORK HORSE



Exceptionally compact—only 8½" high, 12⅝" wide and 17" deep—the GSB 201 lends itself readily to table top mounting.

- Four (not two) type 572B tubes for a full 2000 watt P.E.P. SSB input.
- Full wave solid state power supply.
- Universal rear of cabinet circuitry may be connected for transceiver or receiver-transmitter use without internal modification.
- Plus many, many more features.

AMATEUR NET\$375.00

Also available: GSB 201 MK II — employs four type 811A economical triodes for 1500 watt P.E.P. input.

AMATEUR NET\$325.00

See your favorite distributor
— Write for brochure

GONSET® ANOTHER DIVISION OF AEROTRON, INCORPORATED
P. O. Box 6527 / Raleigh, North Carolina 27608

Christmas Gift Ideas


Are you trying to choose a gift for somebody with technical or amateur radio interests? That can be a very hard problem, if you do not understand what it is all about. Where can you turn for advice?

After reading through this list maybe you will feel a little more confident, and would like to try a catalog. Why not try our advertisers first? If you have a rather general kind of idea coming up maybe it's right in here on another page. Still another good approach is to talk with somebody having interests similar to the set you're trying to match. Finally, it helps to do some outside reading. Maybe you'll catch the bug and become a radio amateur too!

The items listed here are not specialized. Test instruments are good reliable gifts, since some overlapping of their functions is good practice and the fellow with an expensive piece of gear usually likes to have a simpler, cheaper one. And since the fellow who is just starting generally wants the less expensive variety, too, a purchase in this department is almost sure-fire. Some caution, and good advice in choosing your purchase is indicated, though.

73 Magazine

At a risk of sounding slightly prejudiced we have to admit *73 Magazine* is an excellent publication for anybody seriously interested in modern ham radio and technology. This year's issues have carried a wide variety of material ranging from simple construction articles to news about recent events in technology, from using old transistor radios to the latest on those remarkable radio signals from space. No other ham magazine offers this wide range of material, interesting to the career oriented man as well as to the hobbyist. A subscription will set you back \$6.00 per year or \$12.00 per three years, and might be supplemented with a book or two from 73 Press. Try our "73 Useful Transistor Circuits" or "Diode Circuits Handbook," two of the best idea books on the market and available at a dollar each.

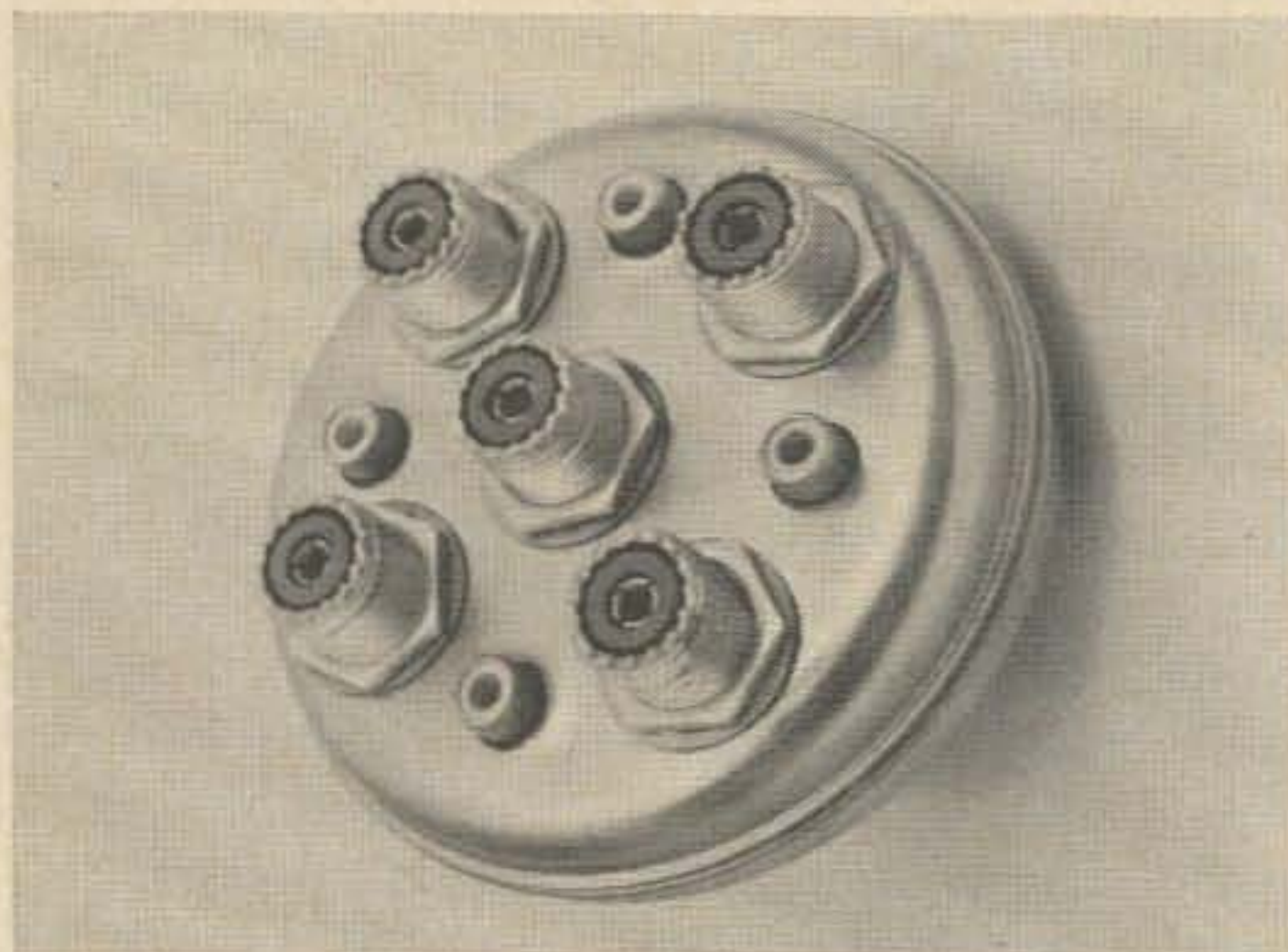

New Coax Switch

You can disconnect your antenna and still use it, with this new 4-position tapped coaxial switch. In addition to the usual UHF fittings it has four RCA jacks permanently connected to the output lines. Circuits or antennas may be monitored even when they are not connected into the operating system.


Some suggested applications are the connection of a general coverage of WWV receiver to the antenna system, installation of measuring devices or fix-tuned monitor receivers, or operation of a low-power rig through one of the disconnected antennas while the high-power rig is feeding another antenna.

Priced at about \$12. For further information contact John W. Richardt, Jr., Electronic Applications Co., Route 46, Pine Brook, N.J. 07058.

James Research Presents

Permafex Key — \$19.95
Oscillator/Monitor — \$14.95

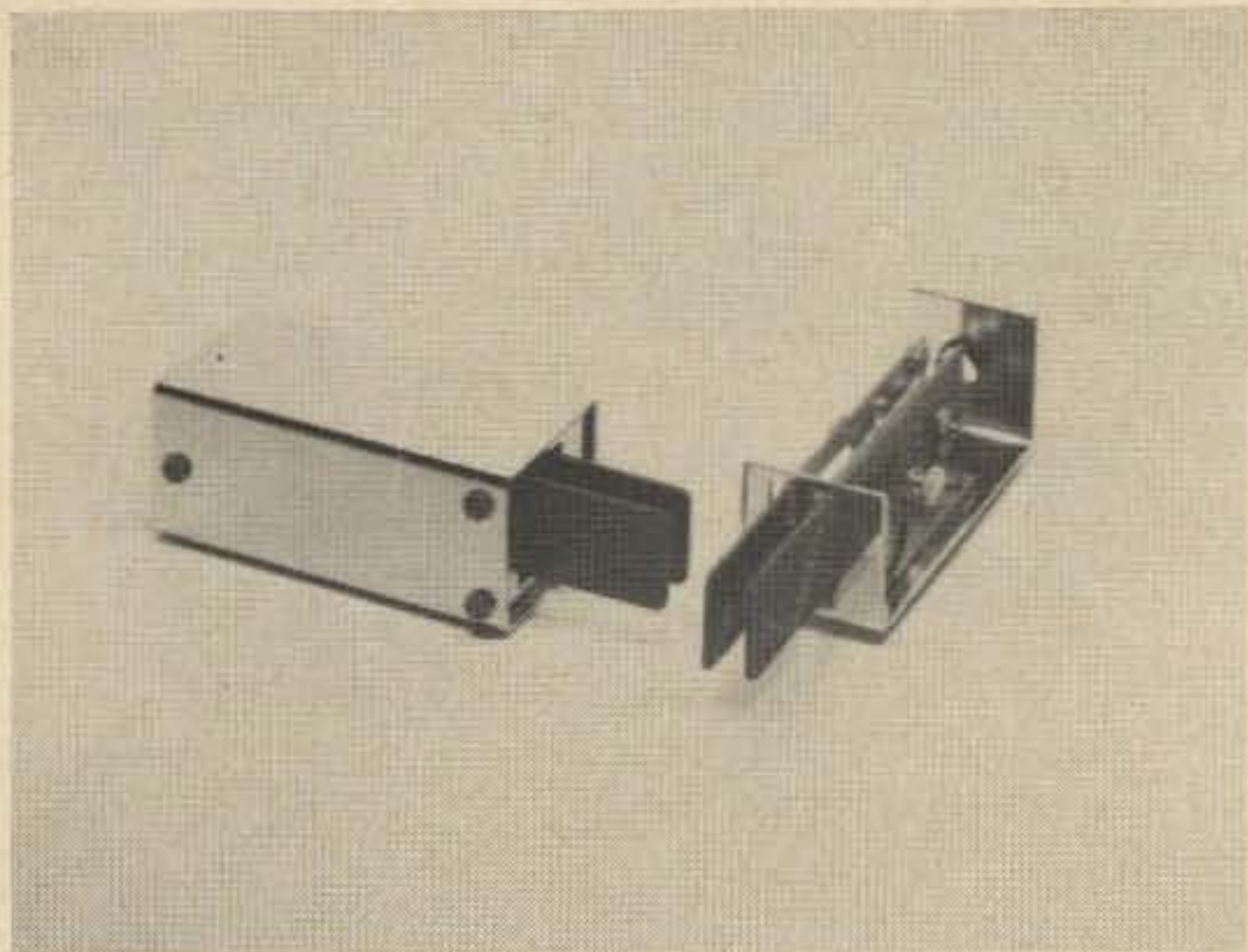Many of the items offered in the Christmas Present line tend to be quite gadgety. Here are a couple of items that could be confused with members of this class, if you have to go by eye alone, but which really belong in the active & useful category. Both appear simple, yet both are unusual in some way, and will do effective jobs around the ham shack.



First, there is the Permaflex Key. It looks simple, and it is, in a way which hides the ingenuity and careful thinking that has gone into making this a really versatile and reliable key. We can expect imitations to appear in a few months; get the original.



The other item is a simple monitoring device, offering remarkable sensitivity. It serves to tell the operator when his CW transmitter is radiating *rf*, rather than when the transmitter is expected to be working. There is a large difference, sometimes. It requires no connection to the transmitter, a point with appreciable safety factor. It can also be used for workbench applications in new gear construction, and finally it will serve as a code practice oscillator.

The Mark 2 Oscillator/monitor incorporates all of the features of the original unit which has gained acceptance by amateurs as a sensitive *rf* type of CW monitor and a code practice oscillator.

Extended amateur as well as professional use of the unit as a Test Instrument has prompted improvement in its performance and utility.

The Mark 2 features:

Increased *rf* sensitivity by the use of cryogenic production control techniques. The Mark 2 will trigger on less than 10 Milliwatts without direct connection.

Greater audio volume and wider tone control range through the use of improved components.

Improved reliability by the use of stainless steel battery contacts which are impervious to corrosion.

A more rugged finish by the use of hard anodic coating on the aluminum cabinet.

Improved ease of use by supplying test leads, tip jacks, battery, and convenience magnetic base with each unit.

Longer assurance of trouble-free performance as backed up by our extended guarantee of 1 full year.

Price \$14.95.

Address all correspondence to: THE JAMES RESEARCH COMPANY, DEPT AR-M 11 Schermehorn Street, Brooklyn, New York 11201.




Printed Circuit Kit


Injectorall Electronics Corp. has just released a much-needed printed circuit circuit kit. It contains etchant, resist ink, resist solvent, and other material required

to make up two small printed circuit boards. And then the pen and ink will do for very many additional boards, using surplus or other available board materials. Retail at \$5.95, from local distributors. For further information write to Injectorall Electronics Corp., Great Neck, N.Y. 11024.

New Mosley Antennas

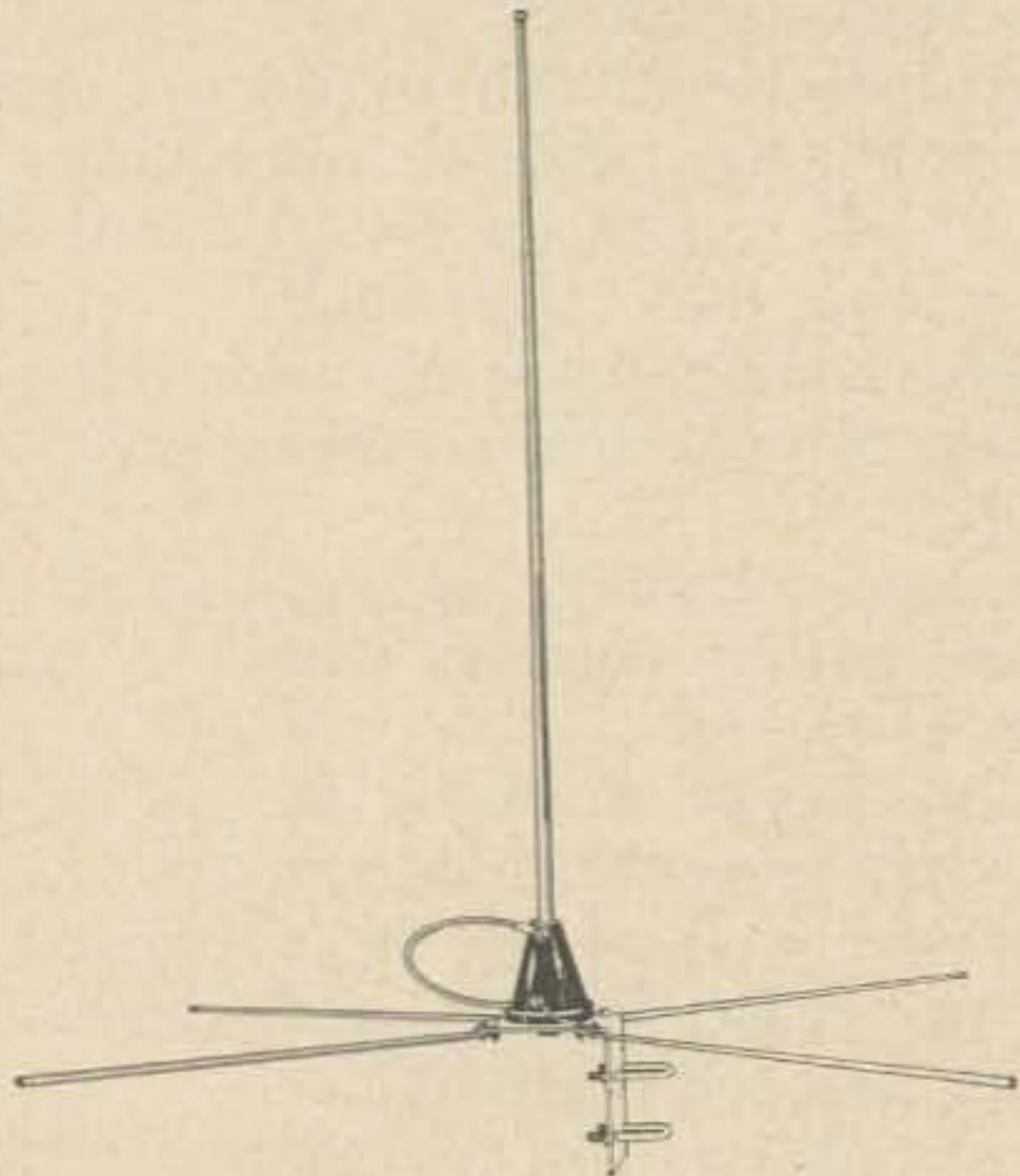

Here is a simple 2-meter antenna, engineering and construction all done, which comes at a very competitive price. The price is even competitive with building your own, if you consider the time that takes and the cost of materials. VSWR better than 1.5:1 over the range of 144 to 148 MHz. \$10.58, ask for the Model D1-2 manufactured by Mosley Electronics, Inc., 4610 N. Lindberg Blvd., Bridgeton, Missouri.

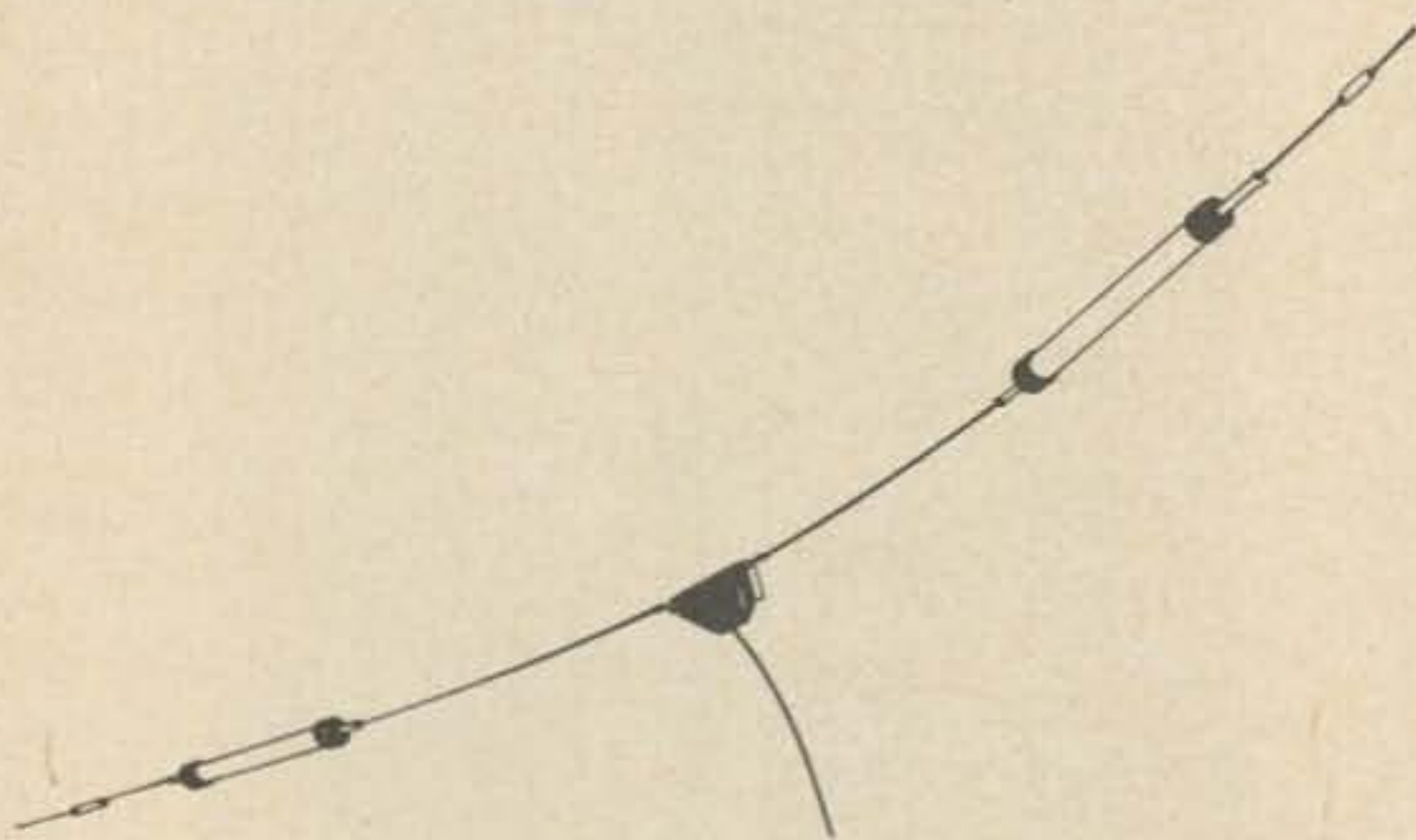


Which are the three best ham bands? If you'd like to try for 10, 15 and 20 meters, or for 10, 15 and 40 meters, here is a trap antenna that will operate as a half-wave on three bands without any switching operations. A strain-relief connector takes 52 or 72 ohm coax cable, and end insu-

lators are provided with the antenna. Rated at 1000 watts PEP for sideband communications. Priced at \$17.59 from Mosley Electronics, Inc., 4610 N. Lindbergh Blvd., Bridgeton, Mo. 63042.

MOSLEY DIPLOMAT 6

ANTENNA MODEL DI-6

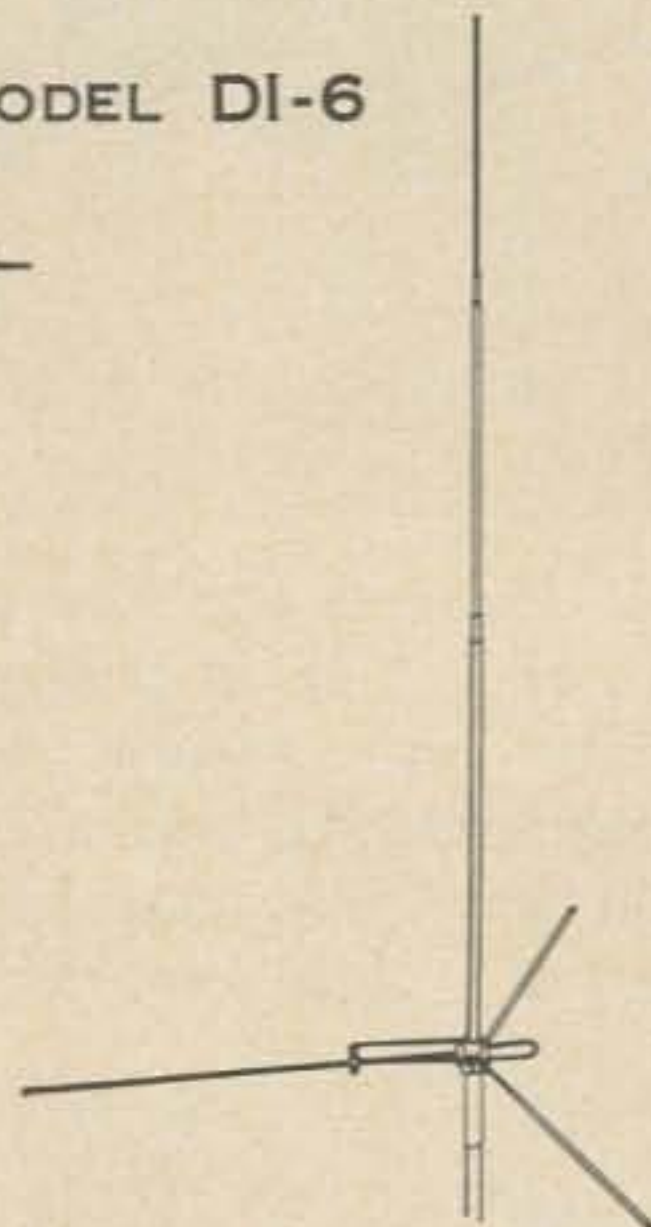

Rated at 2000 watts PEP or 1000 watts CW, the Mosley DI-6 six-meter antenna offers an omnidirectional pattern for general communications use. It is vertically polarized. A special adjustable coupling arrangement provides for optimizing operation at either end of the six-meter band, and swaged aluminum rods serve to reduce wind loading and metal fatigue. The antenna mounts on 1" to 1 1/4" pipe. Priced at \$19.76. Write to Mosley Electronics, Inc., 4610 N. Lindbergh Blvd., Bridgeton, Mo., or ask your local ham or electronics dealer.

Here is a complete dipole antenna system priced well under our rather stretchy \$25 limit. A dipole antenna is about the simplest kind of antenna that is really effective without getting into special circuits. Very appropriate for the young short-wave listener, the antenna can also be used for transmitting up to maximum legal power on all amateur bands through 10 meters.

The set comes with detailed assembly instructions for installing the antenna as a horizontal dipole or inverted V configuration. A center connector provides for connection to a coax cable, and end insulators are included. The DIV-80 kit is available from Mosley Electronics, Inc., 4610 N. Lindbergh Blvd., Bridgeton, Mo. 63042. Shipping weight 3 pounds, and it is indeed under \$25—it's priced at \$7.42. A Best Buy.


SURPRISE THE OM WITH A NEW GALAXY FOR XMAS!

GALAXY V MARK 3 500 WATT TRANSCEIVER

- 500 WATTS PEP-SSB
- 475 WATTS CW
- Precision Dial and Vernier Logging Scale
- Solid State VFO
- CW Sidetone
- CW Filter (option)
- CW Break-in (option)
- AC Power \$79.95 extra

\$420⁰⁰

Less
Accessories

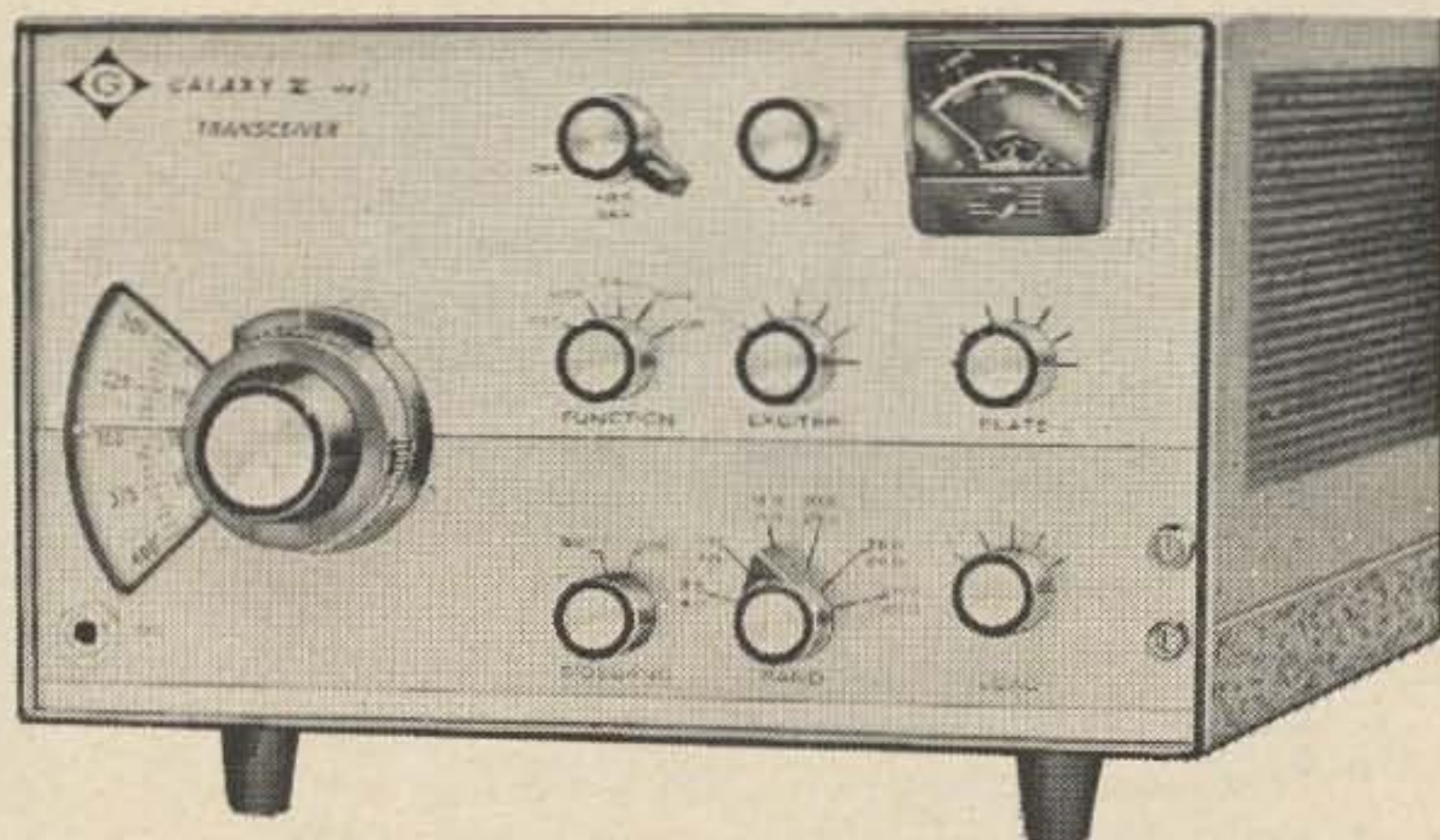

(Ready for immediate delivery)

The superb, new

GALAXY R-530 \$695.00

Phase-locked
Frequency
Synthesizer
for Maximum
Stability!



(All items in stock)

TRADE IN THAT OLD EQUIPMENT ON A NEW GALAXY!

LOOK AT THESE CHRISTMAS SPECIALS!

Barker & Williamson	
5100	\$ 89.00
Central Electronics	
10B	69.00
BC-458A	49.00
20-A	99.00
600L	199.00
Collins	
75S-1	295.00
KWS-1	\$500.00
MP-1	119.00
516E-1	69.00
351D-1	65.00
75A-3	295.00
32-51	650.00
AC	150.00
3253	649.00
KWM-2 #16011	\$795.00
75A2 w/filter	169.00
75S3	\$395.00
32S3	\$650.00
312B4	\$145.00
Clegg/Squires & Sanders	
Thor 6	175.00
AC Supply	75.00
Drake	
2-BQ	29.00
2A	159.00
2AQ	29.00
Eico	
753 NEW F/W	199.00
753	99.00
751	49.00
720	49.00
Eldico	
TR-1TV	150.00
VFO-2	15.00

Elmac	
AF-67	45.00
PMR-7	45.00
A54-H	34.00
PMR-8	95.00
AF-68	85.00
AF-68A	95.00
Globe/Galaxy/WRL	
500B	\$195.00
DSB-160 kit, new..	59.00
DSB-100	49.00
300	199.00
PSA300	75.00
Gonset	
G-63	119.00
Hall crafters	
S-38E	34.95
SX-101A	199.00
SR-2000	\$795.00
AC	325.00
SR-46	149.00
P-150-12	75.00
P-26	49.00
HT-37	225.00
SX-99	75.00
S-108	99.00
S-85	69.00
SX-71	99.00
SX-62	149.00
SX-111	139.00
SR400-PS500	\$750.00
AC2000	\$325.00
Hcath	
HA-14/HP-14	169.00
HA-20	75.00
QF-1	5.00
VF-1	17.00

HW-12	\$89.00
HW-32	\$89.00
AC pwr	\$39.00
HD-11	10.00
HG-10	29.00
VHF-1	149.00
DX-100	\$39.50
Sixer	39.00
HP-20	29.00
DX-40	49.00
HX-30	175.00
GR-54	79.95
SB-300	249.00
SB-400	295.00
SR-40	49.00
SR-400 (like new)..	675.00
HAMMARLUND	
HQ-110C	100.00
HQ-100C	110.00
HX-50	225.00
HQ-170	169.00
E. F. Johnson	
Ranger 11	179.00
Viking mobile kit ..	50.00
Courier Amplifier ..	139.00
Adventurer	35.00
Challenger	59.00
Audio Amplifier ..	75.00
Valiant I	150.00
Viking II	75.00
Viking I	54.95
Valiant	159.00
122 VFO	17.00
6N2 VFO	29.00
Thunderbolt	325.00
Pacemaker	149.00
Knight	
R-55	39.00

R-100	59.50
T-60	35.00
Lafayette	
HA-90	29.00
HE-30	39.00
HE-45B	75.00
HE-50/3-10M	69.00
Mosley	
CM-1	95.00
National "Special"	
NCL-2000 NEW ..	495.00
NC-46	45.00
HRO-60 w/coils ..	225.00
NC-100A	50.00
NCX-A	95.00
VX-501	149.00
NC-109	79.00
NC-155	99.00
HRO-500 NEW ..	1675.00
NCX 3	219.00
Polytronics	
PC-62B	199.00
PC 6	175.00
RME	
VHF-602	189.00
4300	89.00
Swan Electronics	
SW-120	125.00
SW-240	199.00
SW-117AC	85.00
TCU	65.00
S. B. E. SB33	199.00
Miscellaneous items:	
500 watt phone & CW xmtr. 6' rack & cabinet	\$299.00
Assorted power supply	10.00

**MORE WATTS
PER DOLLAR
AT FRECKS!**

FRECK RADIO & SUPPLY CO., INC.

38 Biltmore Avenue • Ashville, N.C. 28801
T. T. Freck W4WL 704-254-9551 Doug Jones WB4IHO

SPACE AGE KEYS

Only
\$67.50



- Planar epitaxial integrated circuits for reliability. No tubes—No separate transistors.
- Precision feather-touch key built-in.
- Fully digital—Dot-dash ratio always perfect.
- No polarity problems—Floating contacts switch 1-amp.
- Rugged solid construction—will not walk.
- Send QSL or postcard for free brochure.

PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CAL. 92026

USED MODEL 501 TV CAMERAS



\$160.00 FOB Hollis

Each month we have a limited number of used TV cameras which we make available to hams at greatly reduced prices. These cameras were rented out for temporary surveillance jobs on construction sites, county fairs, conventions, etc. All have been checked out and are guaranteed for 90 days. Complete with vidicon and lens.

**Used Model 501 sale priced
\$160.00 FOB Hollis**

Don't delay. Only a few used cameras are available each month. For specifications send for our illustrated catalog.

VANGUARD LABS

Dept. H, 196-23 Jamaica Ave., Hollis, N.Y. 11423



Antenna Switch

Not all ham radio work goes on indoors, as you probably know already. Maybe there are several outside antennas, fed by one transmission line (which may be a powerful economy arrangement) or perhaps there are adjustments that must be made at the base or the center of the antenna. The least expensive approach involves many trips out to the antenna, or up the mast, but here is a remote-control switch arrangement that may do the same job. It will work with balanced or unbalanced lines (and that's all there are!) for switching or tuning applications. Ask for their Tenna Switch from the Cubex Co., PO Box 732, Altadena, Calif. 91001, at \$17.95 postpaid. Also available from some dealers.

IC Projects Handbook

If you'd like to pick up two or three IC's and try getting your feet wet in the field, a copy of Brown & Kneitel's book may be just the thing for you. There isn't much chance of going in over your head, and some of the projects are unbelievably simple. To an eye accustomed to the complex schematics of discrete-components circuits IC circuits just don't look real. Yet the trend in electronics is to these tiny functional packages, and they do deserve a lot of attention. With this handy collection, you can get in some good bench work without spending days catching up on the literature.

The fifty circuits include power supplies (which I'd have placed to the front of the

book), a variety of preamps, amplifiers to 50 watts, three code keyers, some signal boosters and other circuits. There are several lab circuits, and I specially noticed a TV color-bar generator that is about as complex as a basic AM receiver—because it uses IC's.

I thought the book seemed a little odd, without any schematics of the circuits inside the IC's. But then I came to page 127 and found Brown provided a complete set of IC schematics in a separate section. Sometimes these are needed to answer hard questions about circuit behavior. It would have been nicer if parts values could have been included since manufacturers do supply this information. And a couple pages of acknowledgements and a bibliography of other places to look for more details would have been nice, too.

This looks like a nice book to have around, if you're interested in modern electronics. *Electronic Hobbyist's IC Project Handbook* TAB book # 464 by Bob Brown and Tom Kneitel \$6.95 hardbound, \$3.95 Paperback



Second Op.

Recently revised and brought up to date, the *Second Op* operating aid quickly provides DX data on stations all over the world. Which zone is he in? Which continent? Country? How about postage, IRC data, QSL bureaus? It is all there and the complete collection, ready to use, sets you back a buck and a half postpaid. Current fifth edition, from Publications in Electronics, Inc., 610 Tower Bldg., 216 West Washington Ave., South Bend, Indiana 46601.

STATEMENT OF OWNERSHIP, MANAGEMENT AND CIRCULATION (Act of October 3, 1962; Section 4307, Title 49, United States Code)		Publisher: File two copies of this form with your postmaster. Postmaster: Complete verification on page 2	Form Approved Budget Bureau No. 44-8027
1. DATE OF FILING October 18, 1968	2. TITLE OF PUBLICATION 73 Magazine		
3. FREQUENCY OF ISSUE Monthly			
4. LOCATION OF KNOWN OFFICE OF PUBLICATION (Street, city, county, state, ZIP code)	Peterborough NH 03458		
5. LOCATION OF THE HEADQUARTERS OR GENERAL BUSINESS OFFICES OF THE PUBLISHERS (Not printers)	Peterborough NH 03458		
6. NAMES AND ADDRESSES OF PUBLISHER, EDITOR, AND MANAGING EDITOR			
PUBLISHER (Name and address): Wayne Green Peterborough NH 03458			
EDITOR (Name and address): Kayla Bloom Dublin NH			
MANAGING EDITOR (Name and address):			
7. OWNER (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 percent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual must be given.)			
NAME		ADDRESS	
73 Inc.		Peterborough NH 03458	
Stockholder: Wayne Green		Peterborough NH 03458	
8. KNOWN BONDHOLDERS, MORTGAGEES, AND OTHER SECURITY HOLDERS OWNING OR HOLDING 1 PERCENT OR MORE OF TOTAL AMOUNT OF BONDS, MORTGAGES OR OTHER SECURITIES (If there are none, so state)			
NAME		ADDRESS	
9. FOR COMPLETION BY NONPROFIT ORGANIZATIONS AUTHORIZED TO MAIL AT SPECIAL RATES (Section 132.122, Postal Manual) (Check one) The purpose, function, and nonprofit status of this organization and the exempt status for Federal income tax purposes: <input type="checkbox"/> Have not changed during preceding 12 months <input type="checkbox"/> Have changed during preceding 12 months (If changed, publisher must submit explanation of change with this statement.)			
10. EXTENT AND NATURE OF CIRCULATION		AVERAGE NO. COPIES EACH ISSUE DURING PRECEDING 12 MONTHS	ACTUAL NUMBER OF COPIES OF SINGLE ISSUE PUBLISHED NEAREST TO FILING DATE
A. TOTAL NO. COPIES PRINTED (Net Press Run)		60,275	65,189
B. PAID CIRCULATION C. SALES THROUGH DEALERS AND CARRIERS, STREET VENDORS AND COUNTER SALES			
D. MAIL SUBSCRIPTIONS		59,650	64,591
E. TOTAL PAID CIRCULATION		59,650	64,591
F. FREE DISTRIBUTION (including samples) BY MAIL, CARRIER OR OTHER MEANS		135	120
G. TOTAL DISTRIBUTION (Sum of E and F)		59,785	64,711
H. OFFICE USE, LEFT-OVER, UNACCOUNTED, SPOILED AFTER PRINTING		560	478
I. TOTAL (Sum of G and H) - should equal net press run shown in A.		60,275	65,189
I certify that the statements made by me above are correct and complete. <i>(Signature of editor, publisher, business manager, or owner)</i> <i>Wayne Green</i>			

radio amateur callbook



GET YOUR NEW ISSUE NOW!
Over 283,000 QTHs in the U.S. edition **\$6.95**
Over 135,000 QTHs in the DX edition **\$4.95**

These valuable EXTRA features included in both editions!

- QSL Managers Around the World!
- Census of Radio Amateurs throughout the world!
- Radio Amateurs' License Class!
- World Prefix Map!
- International Radio Amateur Prefixes
- Radio Amateurs' Prefixes by Countries!
- A.R.R.L. Phonetic Alphabet!
- Where To Buy!
- Great Circle Bearings!
- International Postal Information!
- Plus much more!

WRITE FOR FREE BROCHURE! RADIO AMATEUR **callbook** INC.
Dept. B, 4844 W. Fullerton Ave.
Chicago, Ill. 60639



RCA Hobby Circuits Manual

This new 224 page manual contains detailed instructions on the construction of 35 practical solid-state circuits for use in the home, automobile, photo lab, and ham shack. It also contains easy to read sections on the theory and practical application of solid-state devices, including ICs and MOS FETs. It should be a useful and interesting book to anyone interested in the dynamic field of semiconductor circuits.

The dip-wave meter being examined by Jack Sterner W2GQK is only one of a dozen solid state circuits of interest to the amateur, covered in the Solid State Hobby Circuits Manual (HM-90) which is available from RCA for \$1.75. Additional information is available from your RCA Distributor or from Commercial Engineering, RCA/Electronic Components, Harrison, N.J. 07029.




Radio Shack

A very important part of learning electronics is the discovery of the basic relation between real physical circuits and the schematic diagrams that represent the circuits to the engineer and the designer. This

relation is clearest to the beginner who uses it most, and Radio Shack's 10-8 in-one Electronic Project Kit is a good beginner oriented instruction device.

Without soldering or exposure to high voltages, the beginner can quickly wire up several assorted, quite different circuits. They can be torn down and reassembled again, in the manner of a Tinkertoy set. Are those still on the market? If you're old enough to be raising a family you may remember those. Well, this is a sort of an electronic Tinkertoy set, and has excellent educational and practical value.

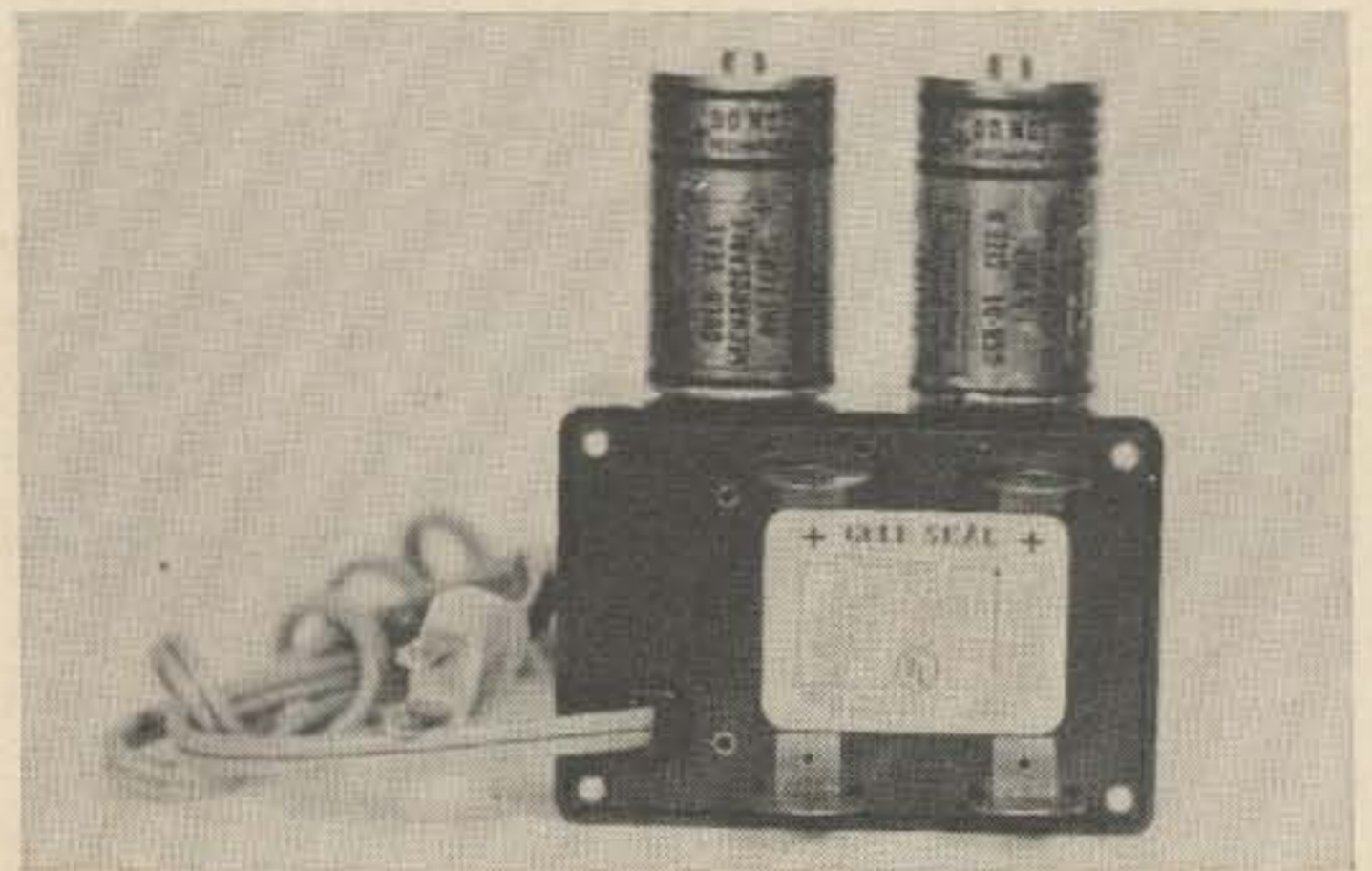Ask for Radio Shack's #28-202 Electronic Project Kit, at \$7.95.



Battery Recharger

If you have an application that uses lots of batteries, why not think about a rechargeable cell installation? For instance, Gold Seal Battery Co. announces one of their new low cost rechargeable cells will replace a series of 100-zinc-carbon cells, at a cost of \$1.10. The rechargeable cells are sealed. A charger drawing 3.3 watts is also available, with a capacity of one or two cells for recharging.

Rechargeable batteries are available from stock at \$.10 per D cell, and the Model 201 charger is priced at \$4.75. Mail orders add 50¢ please, or you can try a local dealer. From Gold Seal Battery Co., 7350 Reseda Boulevard, PO Box 927, Reseda, Calif. 91335.

From Spark To Space

The story of ham radio in Canada is presented in a very interesting and readable booklet put out by the Saskatoon Amateur Radio Club. I very much enjoyed reading it. The editors (I think it was written by a group) used a historical approach, covering their subject from the beginning right

NOT FOR THE NOVICE



THE FT DX 400 "FULL HOUSE"

Conservatively rated at 500 watts PEP on all bands 80 through 10 the FT dx 400 combines high power with the hottest receiving section of any transceiver available today. In a few short months the Yaesu FT dx 400 has become the pace setter in the amateur field.


FEATURES: Built-in power supply • Built-in VOX • Built-in dual calibrators (25 and 100 KHz) • Built-in Clarifier (off-set tuning) • All crystals furnished 80 through the complete 10 meter band • Provision for 4 crystal-controlled channels within the amateur bands • Provision for 3 additional receive bands • Break-in, CW with sidetone • Automatic dual acting noise limited • and a sharp 2.3 KHz Crystal lattice filter with an optimum SSB shape factor of 1.66 to 1.

Design features include double conversion system for both transmit and receive functions resulting in, drift free operation, high sensitivity and image rejection • Switch selected metering • The FT dx 400 utilizes 18 tubes and 42 silicon semi-conductors in


hybrid circuits designed to optimize the natural advantages of both tubes and transistors • Planetary gear tuning dial cover 500 KHz in 1 KHz increments • Glass-epoxy circuit boards • Final amplifier uses the popular 6KD6 tubes.

This imported desk top transceiver is beautifully styled with non-specular chrome front panel, back lighted dials, and heavy steel cabinet finished in functional blue-gray. The low cost, matching SP-400 Speaker is all that is needed to complete that professional station look.

SPECIFICATIONS: Maximum input: 500 W PEP SSB, 440 W CW, 125 W AM. **Sensitivity:** 0.5 uv, S/N 20 db. **Selectivity:** 2.3 KHz (6 db down), 3.7 KHz (55 db down). **Carrier suppression:** more than 40 db down. **Sideband suppression:** more than 50 db down at 1 KHz. **Frequency range:** 3.5 to 4, 7 to 7.5, 14 to 14.5, 21 to 21.5, 28 to 30 (megahertz). **Frequency stability:** Less than 100 Hz drift in any 30 minute period after warm up.

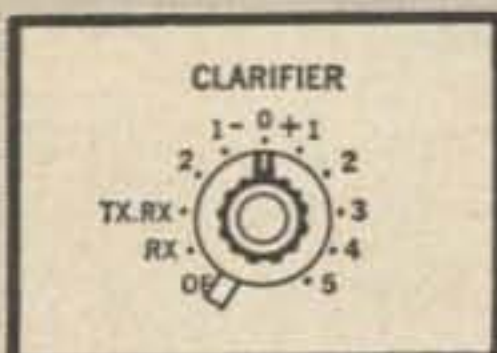


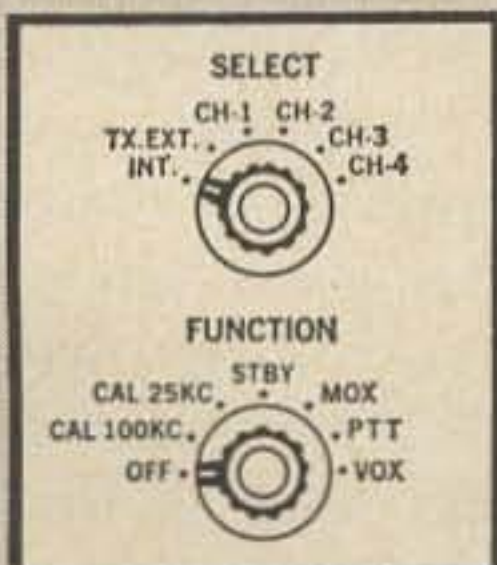CLARIFIER CONTROL — Does the work of an external VFO — allows operator to vary receive frequency 10KHz from transmit frequency, or may be used as an extra VFO combining transmit and receive functions.



SELECT CONTROL — Offers option of internal or outboard VFO and crystal positions for convenient preset channel operation.

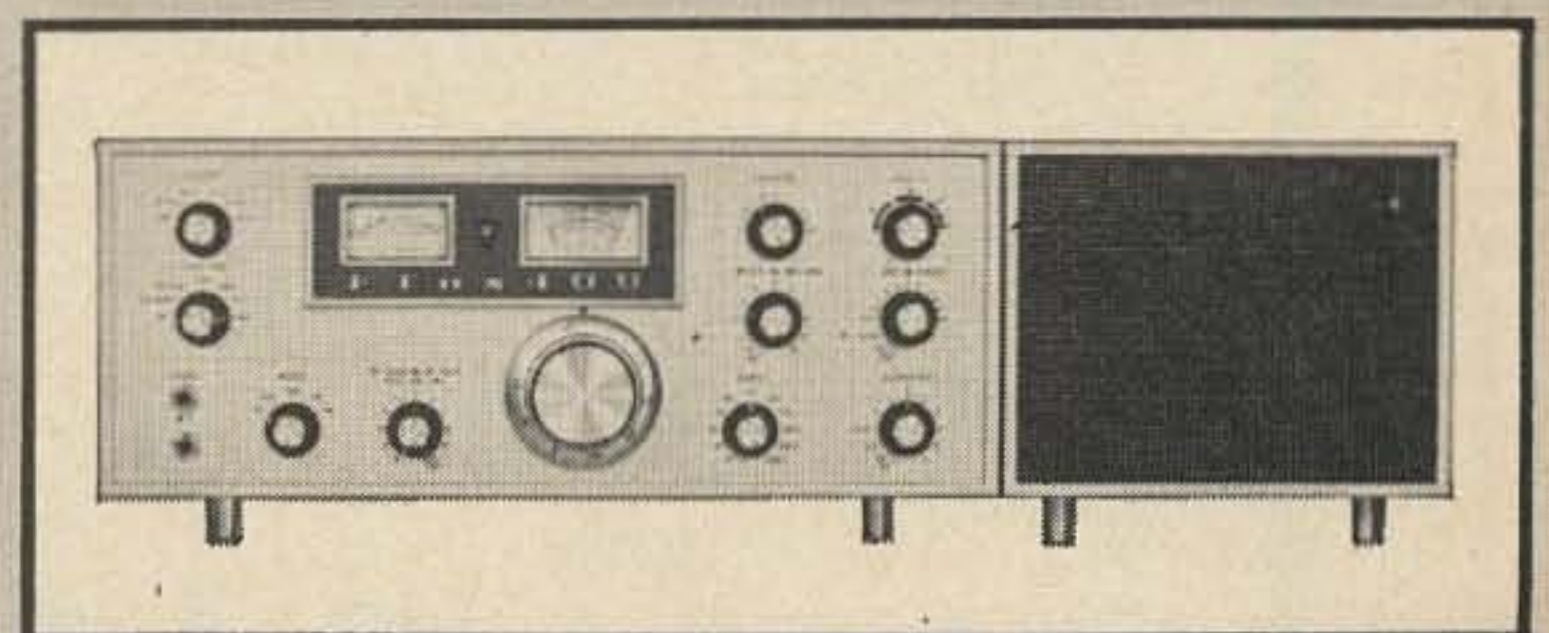FUNCTION CONTROL — Selects crystal calibration marker frequency and desired transmit mode of operation.



FT DX 400 \$599.95 — SP-400 \$14.95



SPECTRONICS BOX 356, LOS ALAMITOS, CALIFORNIA 90720

— PROFESSIONAL EQUIPMENT FOR THE AMATEUR —

SAROC

Sahara Amateur
Radio Operators Convention

FOURTH NATIONAL FUN CONVENTION

hosted by Southern Nevada ARC, Inc.
in HOTEL SAHARA'S new
SPACE CONVENTION CENTER
LAS VEGAS, NEVADA

JAN. 8, 9, 10, 11, 12, 1969



EXCITING ENTERTAINMENT...

Buddy Hackett and Dean Jones in
Hotel Sahara's Congo Room

LUXURIOUS ACCOMMODATIONS...

1,000 beautiful rooms. Special "SAROC"
ROOM RATE OF ONLY \$10 plus room tax per
night, Single or Double occupancy

"SAROC" CONVENTION SPECIAL EVENTS...

- Ladies Program in Don the Beachcomber
- Golf and Bridge Tournaments
- Breakfasts and Luncheons
- Ham Radio Awards
- Three evening Cocktail Parties hosted
by HALLICRAFTERS ... SWAN ... GALAXY

ADVANCE REGISTRATION \$12

per person accepted until Jan. 1, 1969;
regular registration at the door

INCLUDED IN REGISTRATION...

- Special "SAROC" room rate
- Buddy Hackett and Dean Jones, late show
and drinks
- Admittance to Exhibit Area, Technical Seminars,
Cocktail Parties
- Sunday Safari Hunt Breakfast 10 am to 2 pm

Ray E. Meyers, W6MLZ, Master of Ceremonies
Edward Perkins, W7PRM, Club President
L. M. Norman, W7PBV, "SAROC" Chairman

Send separate checks now for registration and
accommodations to "SAROC"

HOTEL


SAHARA!

LAS VEGAS, NEVADA 89109

up to some space communications work hams are doing now. I especially liked the many excellent photos of old radio gear and workers, and on page 87 I noticed the Lakeshore Darts, Draughts, Chowder and Marching Society.

Seems some Canadian hams had a problem of commuting to Montreal to make regular meetings. After discussions on 75 Meters they tried a meeting at a local tavern. About 50 hams attended the meeting and shortly decided on a highly informal approach. Wonderful idea, isn't it? Somehow they ended up with a club title that is often abbreviated to "The Darts & Draughts Club."

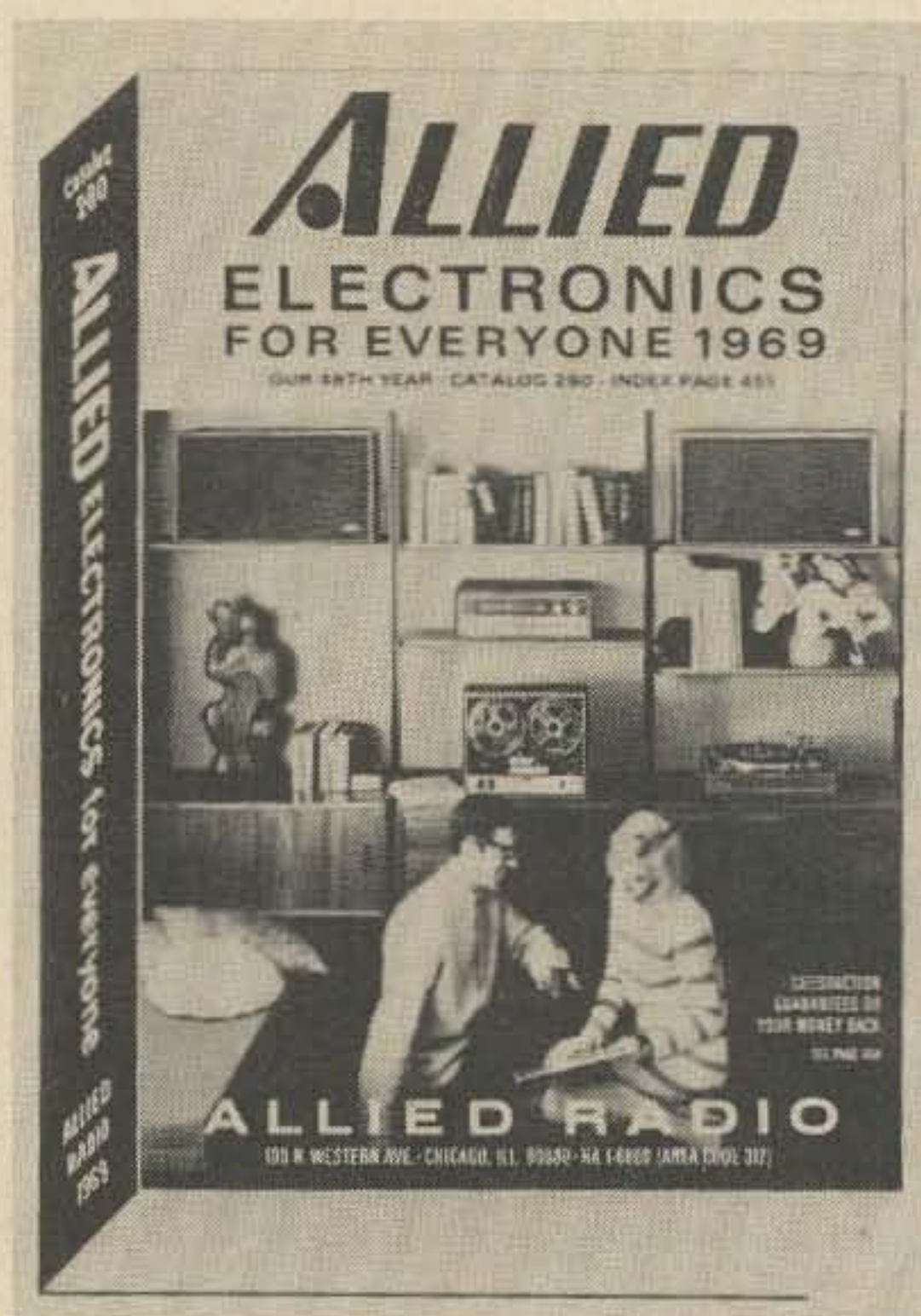Its thoroughgoing historical approach recommends this book. Grade: A.
\$2.50 from P. O. Box 751, Saskatoon, Sask., Canada



Allied Radio

If you are interested in some good basic hardware and utility test gear, try Allied. Incidentally, they sell some very expensive and good materials, too.

Allied's KG-646 VOM kit #22C3907 goes for \$11.95 (one pound), is a general-purpose basic meter, very appropriate for many bench testing applications. It is good around a car, too. A more elaborate instrument, well worth the higher price, is Allied's KG-620 VTVM kit. 22C 3911 W The VTVM does the same job as the KG-646 multimeter but uses a vacuum tube to improve its sensitivity. It can be used for applications

where the less sensitive multimeter will not work, and there are typically so many of these that a technical worker will purchase the VTVM first.

Two other items from Allied's large catalog deserve special attention. One is their top-quality Ersin solder, available in 1 pound rolls at \$3.40 (1¼ lb. shipping wt.) Order #26C1733. This is very good stuff and a pound will last for some time. And the other suggestion is several Vlchek plastic parts boxes, #26C2094 at \$1.95. (1 lb. shipping wt. each). These are the best product available for dealing with the parts situation.

Remember to ask for their catalog #280, too. All from Allied Radio, 100 N. Western Ave., Chicago, Ill. 60680.

Lafayette Radio Co.

Maybe this is a bit out of the ham radio field, or maybe not. A really good loud-speaker can do wonders for a radio receiver, since incoming signals are distorted less during their transition from electrical to sound waves. Lafayette has been selling their SK-58A speakers for several years, and these remain popular because they offer a lot for the price. Try their number 99H0014W 12" hi-fi speaker (11 pounds) at \$24.95.

Or if you want to achieve the same effect on a smaller scale you could try a pair of Lafayette's F-767 hi-fi stereo headphones. Consumer Reports gave these an excellent rating a few years back and they have been selling like mad ever since. Two significant advantages are, they will do a fine job on a couple of milliwatts of power, and they are not audible all over the house. Tone quality is excellent. Lafayette #99H0035, (2½ pounds) a Best Buy at \$11.88.

ARRL Books

The ARRL sells a large variety of simplified technical literature. Some people think this material does not reflect the progress of modern communications and electronics, but there is a gradual year-to-year improvement. And the publications are found everywhere.

At \$3.00, the Radio Amateur's Handbook is one of the most generally used construction and shop practices handbooks available, and you can probably find it locally at a radio store. Try your library if you want to see a copy, and almost anybody who is an amateur operator will have one.


Ver-r-r-y Inter-r-r-esting Bar-gains!!!

Send for our ver-r-r-y inter-r-r-esting 68 page catalog !!! 23c (Free with an order !!!)

P.P. = POSTAGE PAID

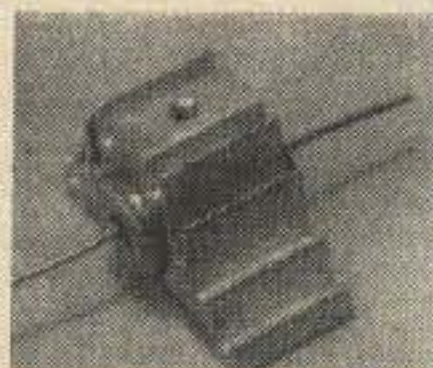D. C. to 400 CYCLE POWER SUPPLY KIT

This is an indispensable item if you want to run Gov't Surplus aircraft or missile electronics. It will convert 12VDC or 6VDC to 110 volts, 400 cycle 35 watts. The kit includes a high quality potted transformer, transistors, resistors, diodes and instructions. No hardware or cabinet is provided. The output waveform is square, rather than sinusoidal, but our experience has been that this will not make any difference since military equip. is insensitive to waveform distortion. Wt. 3 lb, 400 Hz P.S.\$3.50



SILICON RECTIFIER AND HEAT SINK ASSEMBLY — 4 for \$2.50

This is by far the best rectifier deal we have ever offered. Four heat sinks each containing two Motorola or Delco I N 3661 25 ampere 200 PIV rectifiers. These are not factory rejects but unused termination material. With the four assemblies containing eight (8) diodes you can make either one 50 ampere bridge, two 25 AMP bridges, or four 25 AMP full wave center tapped rectifiers. Comp. w/instr. 4SRHS\$2.50 P.P.

DIGITAL VOLTMETER KIT \$19.50

Would you believe a Digital Voltmeter for \$50.00? Would you believe \$25.00 or \$19.50.

We supply a large 6 Digital Numeral Precision Counter, a 1N 429 Precision Reference Zener Diode, a 10 turn 0.25% Linearity, Potentiometer, A.D.C. Motor, and a precision gear train with mounting, for \$19.50. You must beg, buy, borrow or steal a \$10.00 operational amplifier (Analog Devices, Nexus or equal) & you're ready to roll. Schematic, instructions included. List price of components we supply is over \$175.00.

DIGITAL VOLTMETER KIT\$19.50 P.P.

B & F ENTERPRISES

P.O. BOX 44, HATHORNE, MASS. 01937

TWO WAY RADIO CALIBRATION

We can repair, align and calibrate:

- Gertsch FM7 and FM9
- General Radio 1606A
- General Radio 916AL
- General Radio 1601A
- Empire Devices equipment
- RF Voltmeters
- RF Ammeters
- Stoddard Field Intensity meters
- Narrow band
- High band — low band FM

We do authorized warantee repairs for:

Julie Research Laboratories, Datapulse, Micro-Power, Power/Mate, National Radio, Data Technology Corp. (digital voltmeters), Singer Metrics.

LEGER LABORATORIES

Groton Street, East Pepperell, Mass. 01437
Phone: 617-433-2721

To get here from Harvard take 495 north to 119 and then 111 into Pepperell. From Concord NH take the Everett Turnpike to route 3 to 111 to Pepperell. Come see our new building. Come buy a beam or a tower . . . or get just about anything fixed.

Three Black Boxes

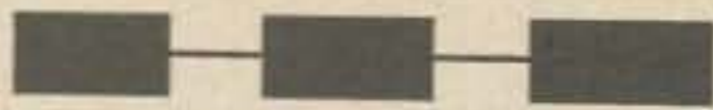


Fig. 1. Three black boxes which make up a station.

The basic concept of a radio transmitting station often gets overlooked in concern with details. It is good to back off and take a look at just what makes up a radio transmitting station. With this thoroughly understood, we can make a more fruitful approach to the design and application of those components that make up a station.

If we erase the black and look into the left-most box, we could see any one of an almost infinite variety of radio-frequency generators plus its primary power supply. Stripped down to basic symbolic representation, it looks like what's shown in Fig. 2. This is true regardless of whether the transmitter uses vacuum tubes, transistors, *rf* alternator, or any other simple or exotic device for generating *rf* energy. It's also true whether the device is for radiotelegraphy or for radiotelephony; whether it is amplitude modulated, frequency modulated, pulse modulated, or any other variant you can dream up.

For the next step, let's skip the middle box and consider the right-hand one. It denotes the radiating device, normally an antenna. An antenna, like a generator, can have an infinite variety of forms: Capacitor, loop, ferrite, magnetic, electrostatic, vertical polarization, horizontal polarization, active, passive, frequency-discriminating, broad-band, etc., etc.

To this, add another infinite series of possible feed systems and you'll see why it's wise to show just a black box! Regardless of its physical nature or its electrical configuration, the antenna (and its feedline, if one's involved) has but one function: To couple the *rf* power output of the

transmitter to the 377-ohm intrinsic impedance of space in such a manner as to obtain the required radiation pattern (directional, non-directional, vertically-polarized, etc.) At the space-antenna interface, the impedance is 377 ohms. What that impedance is at the spot where the antenna-feeder system inter-connects with the middle black box is a matter that varies greatly, both in the magnitude of impedance and in the nature of impedance (resistive, capacitive plus resistive, inductive plus resistive). This is why the middle box is so important to the functioning of the total radio transmitting station.

Two basic functions are performed by the middle black box. One is frequency discrimination (or selection). The other is impedance matching. Very few generators of radio-frequency alternating current produce pure sinusoidal waveforms. Almost always there is an appreciable harmonic content which must be rejected. In certain types of transmitters, there are undesired by-products of frequency conversions that must not be allowed to radiate. Therefore the middle box has a "tuning" function.

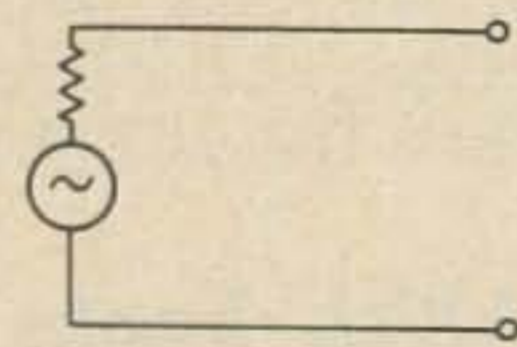


Fig. 2. Basic symbolic representation of any *rf* generator.

The second function, impedance matching, is more complex. Because of this complexity, it is more difficult to achieve during design and construction. By the same token, it's less well understood. Too many publications gloss over the subject with a few time-worn platitudes that serve only to entrench misunderstanding. The discussions you hear over the air and at amateur radio gatherings reveal the lack of understanding. Yet the basic subject, like most

basic subjects, is quite simple and should not be difficult to understand thoroughly. This, of course, holds true only if you don't confuse the situation by making it unnecessarily complex.

Go back to Fig. 2 and take another look at it. You'll see a generator with its internal resistance. To take maximum power out of this generator, you need to have a load equal to that internal resistance. (Sometimes, for reasons we'll not treat here, we want to mismatch the load. This will decrease the transfer of power but may achieve another, and desired, purpose.) Note that I wrote "resistance", not "impedance". In almost all instances, we'll need a pure resistance to load the generator. Supplying this pure resistance, in the desired magnitude, is the second job we ask the middle black box to do.

You'll recall that the right-hand black box, the antenna plus its feed system, had a very wide range of possible impedances. The middle black box must process these impedances and convert them to a stipulated value of pure resistance. Note that I used the plural form, not singular. Very seldom will this impedance remain constant in an amateur radio station, with its ability to cover many frequencies within a band and many bands within the Amateur Service allocations.

Let's say we have a transmitter with a vacuum tube requiring a load (resistive of 4000 ohms. Also, that we have a doublet antenna center-fed with 52-ohm coaxial cable. There is a small probability that at one frequency (hopefully within an amateur band) this will present an impedance of $52 + j\emptyset$ to the middle black box. Transforming this to $4000 + j\emptyset$ with a pi-network presents no real problem to either a designer or a constructor. Even

$25 + j\emptyset$ or $100 + j\emptyset$ can be copied readily. These idyllic situations seldom are found in amateur radio stations other than those using rhombic, disc-cone, or log-periodic antennas! So let's go back to that doublet. As soon as you depart from the one frequency where you found the "ideal" impedance, you'll notice $j\emptyset$ vanishing. In its place will be a finite value of either plus or minus j (depending upon the direction of frequency departure) which will increase in magnitude quite rapidly as you swing away from the "ideal" frequency. These values of reactance ("j") are not so simply dealt with by the usual pi-network. They can be coped with, within reason, but to do so requires the design (and construction) of a very flexible impedance-matching circuit. If the middle black box is to perform its full function, this flexibility must be present. Because this device helps to achieve an impedance match, it should be thought of as an integral part of the middle black box.

So you see, a radio transmitting station may be shown as three black boxes. One holds the generator, one holds the impedance-matching portion, one holds the radiating section. One generates the rf power, one matches the generator to the radiator, one matches the radiator to space. Quite simple!

... W5EHC

DIODE CIRCUITS HANDBOOK


An invaluable reference book. Covers rectifiers, meter circuits, mixers, detectors, modulators, products, FM detectors, noise limiters, squelch, AGC, BFO/Q-multiplier, xstr protection, AFC, Varicap tuning, audio clippers, FM modulator, balanced mods, Varactor multipliers, field-strength meters, wavemeters, RF probes, dummy loads, SWR bridge, tachometer, noise generator, square-wave gen, zeners, control circuits, voltage control, etc. 111 different circuits.



An absolute steal at \$1.
73 MAGAZINE
Peterborough, N.H. 03458

HUNTER

LINEAR AMPLIFIER by Hunter

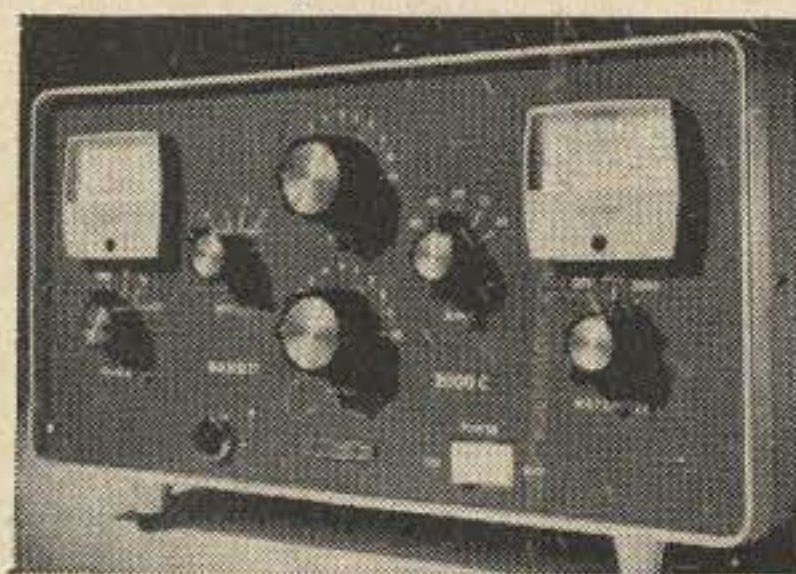

BANDIT 2000C

- 2000 watts PEP ●
- Five bands ●
- Kit form ●

Write for details

HUNTER SALES INC.

Box 1128A University Station
Des Moines, Iowa 50311

Ralph Steinberg K6GKX,
110 Argonne Ave.
Long Beach, Calif. 90803

Facsimile and the Radio Amateur

It's fun and exciting to experiment with facsimile. This mode of communication is gradually becoming as popular as slow-scan television and teletype. There are many potentials for which facsimile can be used in amateur radio. Before we discuss these potentials there are some facts and experiences your author had with facsimile which may be interesting.

From April to the middle of September, Project Facsimile Antarctic logged more than 300 hours transmitting pictures to KC4USV at McMurdo Station. Although the distance was 8000 miles from the transmitting station to the receiving station, eight-five percent of the pictures received were of good quality and contrast on their initial transmissions. The small percentage which were of poor or fair quality were retransmitted and received in normal quality. Successful transmissions were made with signal reports of S3 although for the majority, reports were S7 to S9. Some evenings only one picture got through to McMurdo Station before the band "folded", while on other evenings as many as two to ten pictures were transmitted with very good copy. Very little interference was noticed during the six months period of facsimile operations and this may have been due to the selection of frequencies (14.100 to 14.200 MHz) authorized by the Federal Communications Commission. The biggest problem of the facsimile operations were the magnetic storms in the Antarctic which delayed transmitting schedules from one day to a week at a time.

For those not acquainted with facsimile equipment or the operations, this introduction may be of interest and possibly the beginning of another mode of communications for experimentation.



Facsimile Photo of Miss California as received at McMurdo.

Introduction

Facsimile transmission consists of sending pictures or other printed material by radio or land line. It makes use of the process known as scanning. The scanning like the human eye follows each horizontal line from left to right and returns to a starting point at the left hand side of the page or picture and repeats the process many times to reach the bottom. This produces a permanent copy of any material whether type, script, photographs or schematics. Facsimile equipment as used today requires a slow speed (usually 60 rpm for amateur radio) which produces a copy of the record in a matter of minutes.

In the transmitting of facsimile a picture is scanned about 100 lines per inch. As the light beam passes over each portion of the picture it is reflected into a photoelectric cell and the variation in the intensity of the reflected light, due to the character of the picture, creates voltage variations in the output circuit of the photo-cell. These variations make up the picture signal and are a source of modulation for the radio frequency carrier of a transmitter. At the receiving station, the signal is demodulated and the voltage variations created at the transmitter are used to operate a recorder.

The potentials of facsimile communications in amateur radio are unlimited. It needs only imagination to find ways to use facsimile for many purposes. Some common applications in amateur radio are sending and receiving pictures, schematics, bulletins or QSL cards plus anything that calls for a permanent record. There are radio amateurs who have facsimile equipment and use it for copying weather maps from Canada and the satellites high above the earth. In tornado and hurricane areas, these weather maps would help the NCS of the warning networks. The NCS with facsimile equipment would have advanced information on the weather and a permanent record of the weather map.

Equipment

The equipment used by Project Facsimile Antarctic during the facsimile operations to the Antarctic was the TXC-1B Times Corporation Transceiver, MD 168 Modulator, RD 92A/UX Receiving Recorder and CV 1066A Receiving Converter. This was all compatible with the facsimile equipment at McMurdo Station in the Antarctic. Although the TXC-1B Transceiver can be used for transmitting and receiving, the RD 92A/UX was used as a monitor for all transmissions and occasionally for receiving.

The TXC-1B Transceiver is an electro-mechanical-optical facsimile set of the revolving drum type for the transmission and receiving of pictures, printed matter, maps or sketches. Received copy is recorded on chemically treated paper. The equipment will transmit or receive a page of copy 12 x 18 inches in 20 minutes. The MD 168 Modulator is used to convert amplitude modulated facsimile signals from the TXC-1B Transceiver to audio frequency shift facsimile signals of 1500 to 2300 cycles. The input signal to the modulator has a frequency of 1800 cycles and an amplitude that varies with the light and the dark parts of the picture being scanned at the facsimile transmitter. The output signal from the modulator is an audio signal with 1500 cycles the maximum signal input and 2300 cycles the minimum signal input to the modulator from the facsimile transmitter. As the audio frequency-shift signal from the modulator is of constant amplitude the transmitted radio frequency from the radio transmitter is modulated at a constant percentage of modulation and is known as subcarrier - frequency modulation.

To receive the audio frequency-shifted signal, the RD 92A/UX Recorder was connected with a CV 1066A/UX Converter. This converted the audio frequency-shifted signal output of the radio receiver into an amplitude modulated signal suitable for the facsimile recorder.

Although Times Corporation Facsimile equipment was used for the operations of Project Facsimile Antarctic, there are other manufacturers of this equipment such as J. P. Seeburg Corp. who build their machines for Western Union Telegraph Company and the Alden Electronic & Impulse Recording Equipment Company for the U.S. Weather Bureau Stations. Both companies have adjustable speeds on their recorders and can be made compatible between receiving and transmitting stations.

Radio amateurs interested in experimenting with facsimile equipment can secure it through the MARS program, when available. Recently Western Union Telegraph Company donated some of their older model "Interfax" equipment to the radio amateurs in some of the larger cities. If you live in or near one of the larger cities of the United States, contact the technical service manager of the telegraph company. Mention you are a radio amateur and that you wish to experiment with facsimile and would appreciate one of their discontinued models of facsimile equipment, *interfax*. You might be lucky. On the Alden Facsimile equipment, this company sells their discontinued models and inquiries should be addressed to their main office in Westboro, Mass.

Facsimile operations at present are assigned to the frequencies from 50 MHz to 40,000 MHz, however special permission must be authorized by the Federal Communications Commission to use it on the low bands. With slow-scan television just recently becoming legal on the low bands, it is hoped that facsimile operations will also be legally allowed on these bands.

There was lots of work attached to Project Facsimile Antarctic, but Earl, WA6URW, Ellis, WB6EGH and I enjoyed every minute of it. Try experimenting with facsimile and you will feel the same way. . . . K6GKK

*Tell Our Advertisers
You Saw It in 73*

Why SSB?

F. Dale Williams, K3PUR
HRB-Singer, Inc.
State College, Pa. 16801

Required Reading for the Die-Hard AM Operator

Would you believe that, in this electronic age, there are still amateur radio stations without the capability of SSB operation? If you find this fact plausible, it should not be difficult to convince you that there are also many hams who don't really know what single sideband is all about (and some of these hams are operating SSB exclusively). We are all familiar with the clichés of the SSB versus AM controversy: "Twice the output of AM with the same power"; "I would need a special receiver"; "I don't want anything to do with that quack sounding stuff"; "It only uses half the spectrum space of AM". But how many of us have actually taken the time and trouble to do a little reading to see just what the advantages are to utilizing single sideband as a mode of transmission, and what we must obtain in the way of basic equipment, or put out in cash, to either change to or add SSB to the present station?

Fig. 1 is provided as an overall comparison of AM, double sideband, and single sideband in easy-to-read table format with the hope that it will create enough interest among the non-believers to convince them to read the article. The gain figures are computed with a reference of 1 and are given only as average power values which do not show actual gain advantage. If you have already designed and constructed a single sideband transmitter, this article probably won't tell you anything new. If you have just added a product detector to that old station receiver to make it easier to receive SSB signals, but haven't gotten around to obtaining a transmitter, this article should convince you to take the final step. In the event any of the die-hard AM operators have been stimulated to read this far, be advised that this article is mainly meant for you. Even if you don't believe everything you read it might give you some extra ammunition for your altercations with the "Quack-

ers". In the following paragraphs I have tried to state the differences (not necessary advantages) between AM and SSB in easy to understand terms and give examples which should emphasize the points in various ways. Although double sideband is not a common mode of transmission for hams, its characteristics are included for comparison purposes.

Power

Unfortunately, the most important consideration of the present-day ham appears to be the amount of power the transmitter can provide. With a well matched antenna system we expect all the power in the transmitter final to be transferred to the antenna and into the ether. This case naturally considers the transmission line to be lossless and the antenna to be a perfect radiator. This generalized impression is misleading. First, considering AM transmitters, we must remember that the power is usually given by the manufacturer as so many watts input. This value is dc watts input to the final and, since we cannot expect the final tube to be much over 75% efficient, the unmodulated output will be much less than the rated input. When the transmitter is modulated 100% with a pure sine wave the dc power is varied at the frequency of the sine wave and increased 50% in amplitude. That sounds fine, you say, because allowing for some peak power loss we still have as much average output when modulating with voice as the stated dc power input. However, the power leaving the final of the AM transmitter, and thus that power being sent along the airwaves toward that rare DX station, is not all contributing to the best possible reception on the other end. The transmitter had a carrier frequency which was modulated in order to transmit some intelligence, in this case your voice. Therefore, a band of frequencies

1000 W Av. Output Eff. = 100%	Carrier	Power Distribution USB	LSB	System Gain	Power Gain	Spectrum Space	S/N Advan.
AM	666.6 W	166.7 W	166.7 W	25 db	22 db	6 kHz	None
DSB	Insig.	500 W	500 W	27 db	27 db	6 kHz	None
SSB	Insig.	1000 W in either sideband		30 db	30 db	3 kHz	None

Fig. 1. Overall comparison of the three modes.

determined by your voice and the circuit elements of the modulator was mixed with the carrier frequency, producing the carrier, upper sideband, and lower sideband, both of which contain the same information. However, as you remember, we said above that the power could be increased a maximum of 50% by 100% modulation. This increase in power is equally divided between the two sidebands while the major part of the transmitted power is taken by the carrier. Since the carrier contains no intelligence, and only one sideband is necessary at the receiving site for demodulation, our effective power is only one sixth of that being transmitted. In other words, the transmitted AM signal has two thirds of its power in the carrier and only one third in the sidebands.

If we were to suppress the carrier and feed only the two sidebands to the final stage all power would be transmitted in the sidebands, thus doubling our effective power.

Progressing further along this line of thought, if we suppress the carrier and feed the final stage with only one sideband, it should be possible to use the available power to transmit the single sideband, thus utilizing all the power for the transmission of intelligence. This is indeed the case and we have again doubled our effective power.

Example 1: For a transmitter rated at 5KW output and modulated 100%, the power will be divided:

	LSB	Carrier	USB
AM	833.3W	3333.2W	833.3W
DSB	2.5 KW	Insig.	2.5 KW
SSB	5 KW in either sideband		

Example 2: Looking at it another way, the AM transmitter in the above example must have a total output of 30KW to equal the power of the 5 KW SSB transmitter. Therefore, the system gain of the SSB transmitter is six times that of the AM transmitter and the gain in db is:

$$10 \log 6 = 7.78 \text{ db}$$

The above examples were made on the basis of equal signal-to-noise ratios at the receiver, which as explained later is valid,

and no limitation to the peak power of the AM final amplifier. However, since the amateur service is allowed to feed the final transmitter stage with only 1000 W, this value obviously becomes the limiting factor.

In an AM transmission the peak amplitude (at maximum voltage swing) for a 100% modulated wave is twice the amplitude of the carrier wave alone. Therefore, the peak power of the modulated wave is four times the normal carrier power. This is caused by the doubling of the plate voltage of the amplifier at the peaks of the modulating wave. When the voltage (E) is doubled, the power will increase four times according to the formula:

$$P = \frac{E^2}{R}$$

Where P = Power out
E = B+ Voltage
R = B+ Resistor

In other words, the power in a 100% modulated wave is 50% greater than the carrier wave alone. Then, if we have a 1 KW carrier signal and a 100% modulated feeding the final stage, our modulated output would be 1.5 KW, disregarding tube efficiency. The peak power output would be four times the normal carrier power or 4 KW.

Example 3: Using the limiting factor of 1000 W unmodulated input to the final we can see that only 500 W can be provided for both sidebands or 250 W in each. This means the AM system can provide an average power (both sidebands) of 500 W to 1000 W for the SSB system, or a 2:1 advantage for the SSB system.

Example 4: Utilizing peak power as a reference, the AM system must peak at 4 KW to equal the SSB peak power of 1 KW. However, the AM system can produce only 500 W in both sidebands while the SSB system can put the whole gallon in one sideband. This ratio of 4 KW:0.5 KW or 8:1 gives the SSB system a signal power advantage of:

$$10 \log 8 = 9 \text{ db}$$

This is just about the difference between a dipole and a junior sized 3 element beam!

Spectrum Requirements

A well designed communications system is not intended to efficiently transmit high fidelity music. If we desired to transmit such material with a frequency range of 20 Hz to 20 kHz using normal amplitude modulation, 40 kHz of spectrum space would be necessary. Some time ago telephone company engineers found that satisfactory voice communications could be transmitted using only the 300 Hz to 3 kHz portion of the audio range. Therefore, audio amplifiers, modulators, and filters are designed to pass only this range of frequencies. Although seemingly narrow when compared to the high fidelity limits, this band of audio frequencies provides intelligible communications. If you have ever noticed the problem of tuning in a YL operator on SSB, you will realize that the higher range of voice frequencies appears to make the bandwidth narrower than it really is.

Example 5: Utilizing only these audio frequencies, the normal AM transmitter will produce sidebands a minimum of 3 kHz above and below the carrier frequency, thus using a total spectrum space of 6 kHz.

Example 6: A single sideband transmitter using the same audio frequencies will produce only one sideband either 3 kHz above or below the carrier frequency, depending on which sideband is being transmitted. As shown, a single sideband transmitter requires only one half the spectrum space necessary for AM transmission.

In addition to the above saving in spectrum space, there is another benefit of SSB which is often forgotten. By greatly suppressing the carrier, we have removed a major source of interference from the bands. When two AM stations are utilizing frequencies less than 6 kHz from each other, interference is caused by heterodyning of the carriers. Two SSB stations, both operating on the same sideband, can easily transmit within 3 kHz of each other without causing interference. It is also possible to operate SSB at even narrower intervals due to the missing carrier, the only interference being in the form of "monkey chatter" caused by the audio of the nearby station.

Example 7: Considering the above facts, a 96 kHz portion of the frequency spectrum could be effectively utilized by 16


AM stations or 32 SSB stations. Intelligible communications could also be obtained if an additional 16 SSB stations were evenly spaced among the already present 32. This would give every one of the 48 SSB channels a bandwidth of 2 kHz. Thus an average ratio number of possible transmitters per mode to required spectrum space would show a 48:16 or 3:1 advantage for the SSB mode.

Noise and Propagation

In examples 1 and 2, we noted that the calculations were made on the basis of equal signal-to-noise ratios in the receiver for both AM and SSB signals. The AM receiver detector usually has a 6 kHz bandwidth signal to work with so that both sidebands are demodulated producing equal audio outputs. The SSB system has only one sideband to be demodulated, thus produces only one detector output at one half the amplitude of the AM radio.

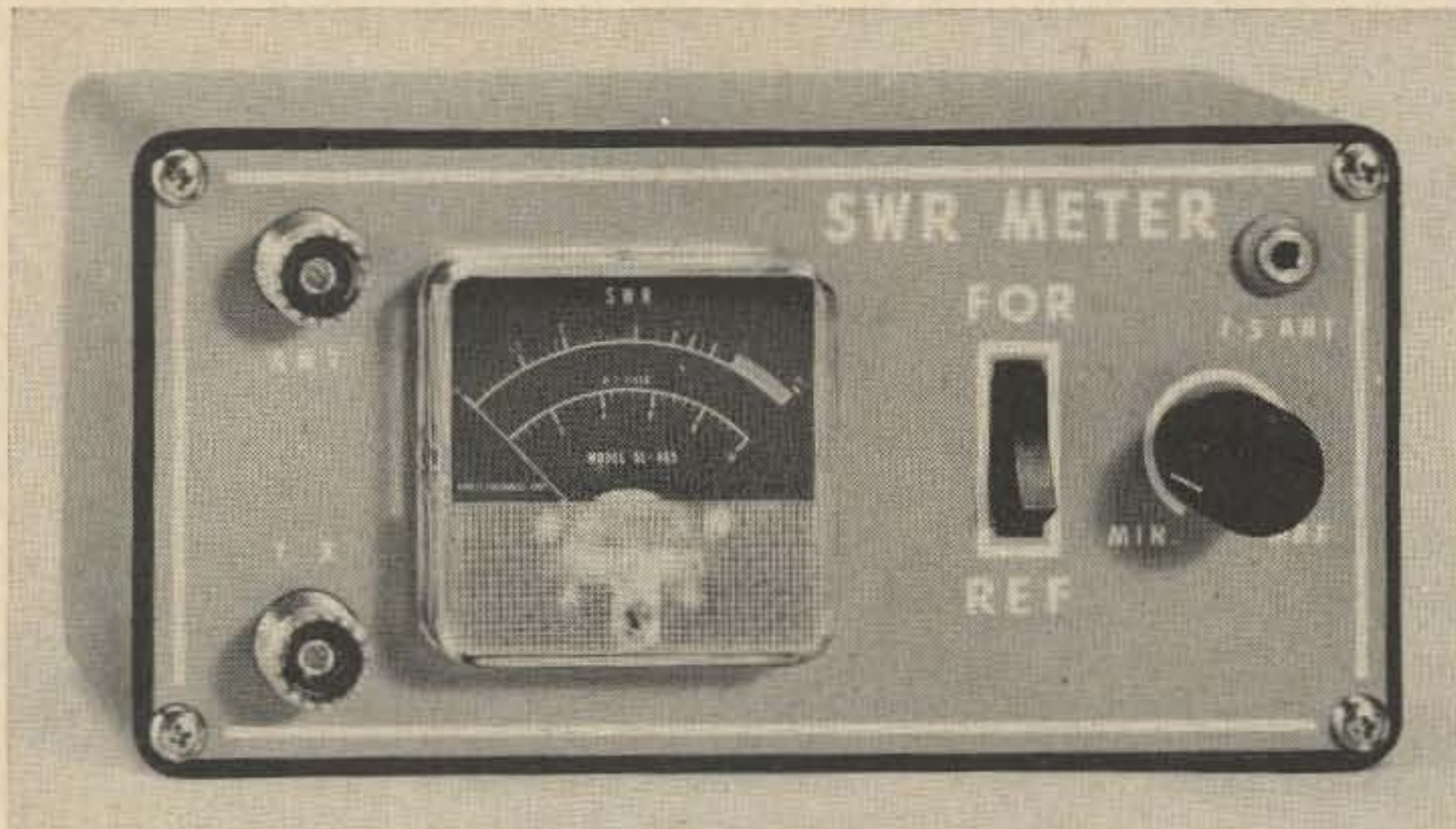Example 8: Although the AM receiver detector produces twice as much audio from an AM signal, the noise on both AM sidebands is twice that on the one SSB sideband, thus there is no signal-to-noise advantage for either system.

At first glance it would appear that we should see some improvement in AM long distance communication over SSB, as far as the signal-to-noise ratio is concerned, due to the wider bandwidth. The Hartley-Shannon law tells us that the total information in a signal is directly proportional to the bandwidth, time taken to send the information, and the signal-to-noise ratio. Therefore, a certain amount of noise interference on a long transmission path can be overcome by increasing the bandwidth of the signal. However, although the AM sidebands cooperate to raise the power output in an AM system, they tend to work against each other over the long distance path when fading occurs. This is due to the fact that the sidebands in an AM system are being "transmitted" by the carrier. When the carrier is received by two different ionospheric signal paths, the different lengths of the paths cause the received signals to be out of phase with each other. The amount of phase difference is dependent on the signal paths and can be 180°, in which case complete cancellation occurs. Any phase difference of the carrier other than 180° will cause some de-



52 Ohm 1 KW SWR Meter

- Simple
- Inexpensive
- Effective

\$14.95

SEE YOUR LOCAL DISTRIBUTOR

(Distributors and Reps please write as several areas are still open for distributing these fine products)

MAIL ORDER SALES


Include \$1 for packing and mailing and send to **REDLINE** Company, **JAFFREY, NEW HAMPSHIRE, 03452**. Money back guarantee on all DGP equipment!



RF Field Strength Meter 1-400 MHz

Comes with 5-section antenna and earphone for modulation checking. Invaluable for tuning any transmitter. Magnetic base for mobile use.

only
\$8.95

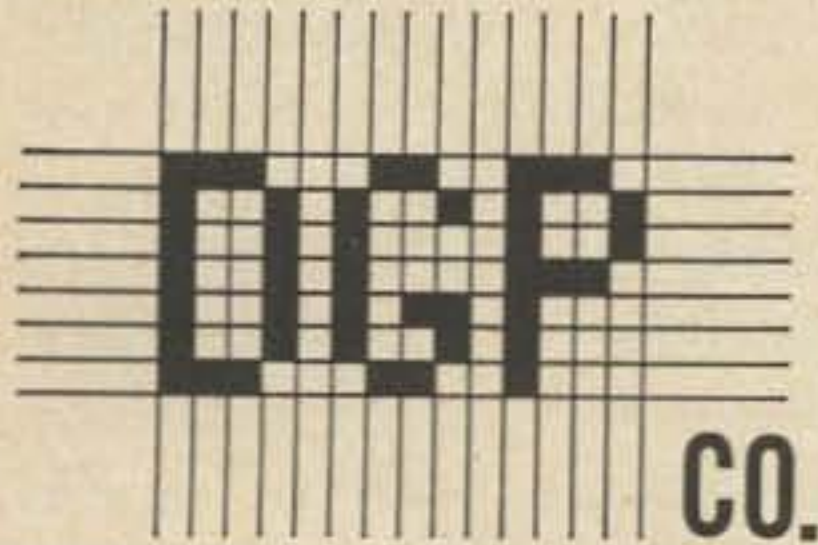

**BOX 231
JAFFREY
N.H.
03452**

CLUB SECRETARIES NOTE!

Your club can round up some extra funds by imploring, cajoling, convincing, or forcing your members to subscribe to 73 Magazine. Never mind the cries of anguish, just remember that you are doing what is best for them . . . and the club.

Subscriptions to 73 are \$6 per year regularly. The special club rate is exactly the same . . . \$6. The only difference is that the club treasury holds on to 25% of the loot and sends the rest to 73. Send us \$4.50 for each one year subscription, in groups of at least five subs. Just think, if your club has 10,000 members you can quickly make \$15,000 for the club on this deal.

Send the subscriptions to us on 3 x 5 cards, giving the name, address, call, city, state, and zip code of each subscriber. If the subscription is a renewal please include the address label from a recent 73 wrapper. Indicate all renewal subscriptions so we won't just start a second subscription. We have been known to do that.

Send to: CLUB FINAGLE, 73 MAGAZINE, PETERBOROUGH, NH 03458

gree of fading but, more important, it will cause the sidebands to interfere with each other producing distorted audio. Such fading can be avoided by diversity reception (two receivers and two separate antennas) or refined receiver design with special phasing circuitry.


Example 9: Since the transmitted SSB signal contains no carrier, selective fading is not a problem and, under the same conditions, a 12 to 16 db improvement over AM can be realized.

It is possible to use the scatter phenomenon for medium distance (1000-2000 miles) communications. This effect is more prevalent on the high bands and is utilized by the military and government for reliable "back-up" systems. The transmission path is scattered and therefore is dependent on transmitter power rather than propagation conditions.

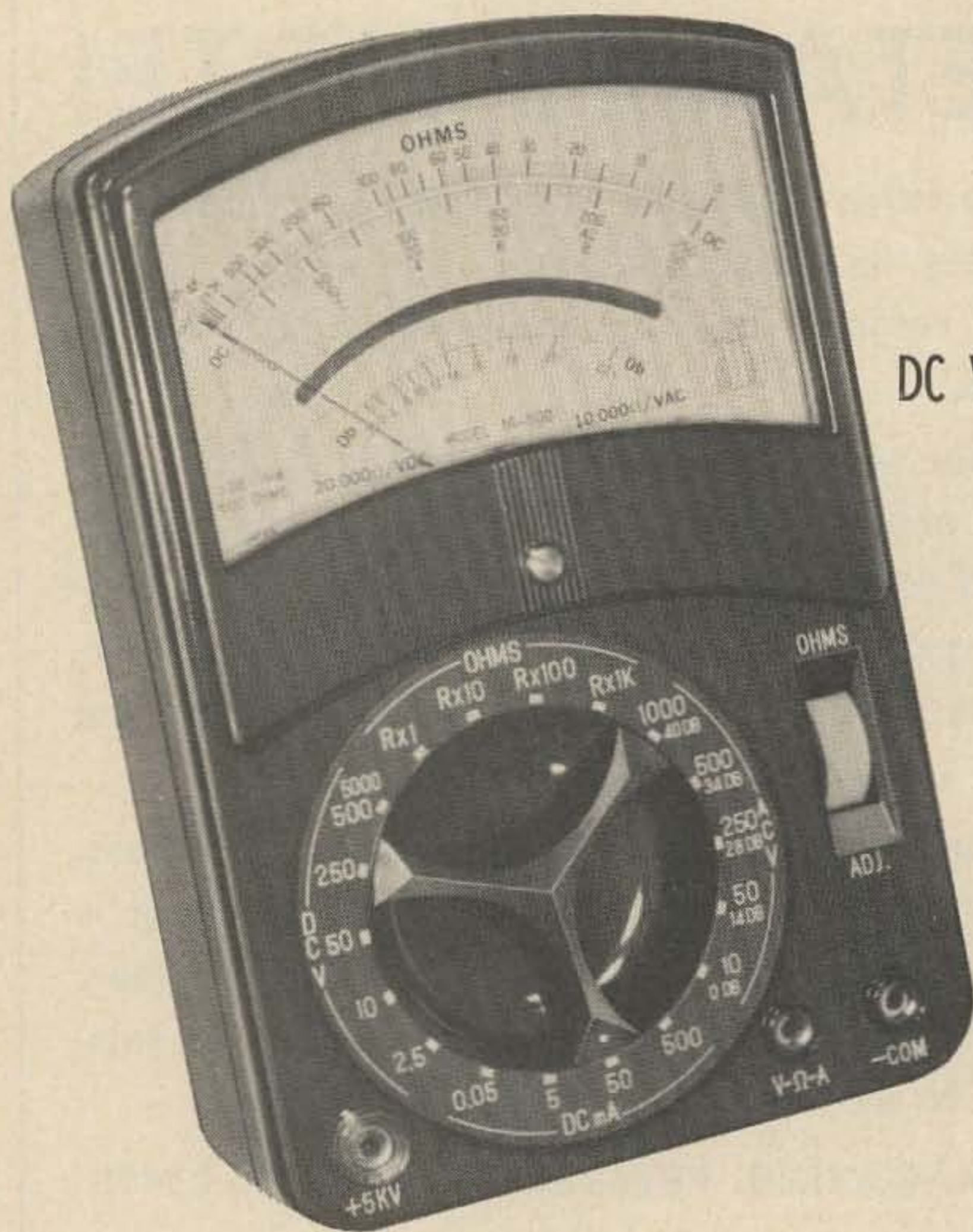Example 10: Since communications using the scatter phenomenon is dependent on transmitter power and more power is available in the SSB system as compared to an AM system, it is possible to make contacts with SSB when the bands are "dead" for AM.

Reception

Because an AM signal is transmitted with a carrier it is a simple matter for the operator to find the signal and for the receiver detector to demodulate it producing an audio output. However, in SSB, where no significant carrier is transmitted, there will be no indication at the receiver of any signal being transmitted except when the operator at the other end speaks into the mike. Without a carrier to beat with the receiver heterodyning oscillators the AM detector has no reference and produces only unintelligible distortion. In order to receive SSB the carrier must be reinserted at the receiver. The point of insertion may be almost anywhere before the detector but must be the frequency of the transmitted signal. The best way to convert an AM receiver for SSB reception is to add a product detector. Since this article is not meant to get into the necessary circuitry for single sideband, suffice it to say that the product detector is essentially a mixer/demodulator which is fed with the incoming SSB signal at the *if* frequency. Because there is only one sideband, the driving oscillator output must be quite a bit higher than the signal amplitude to provide a useful audio



OUTSTANDING HAM V-O-M

20,000 Ohms per volt dc
5,000 volt dc range!

DC Volts: 2.5, 10, 50, 250, 500, 5000.

Ohms: 12K, 120K, 1.2M, 12M

DC MA: .05, 5, 50, 500.

AC Volts: 10, 50, 250, 500.

DB: 0, 14, 28, 34, 40.

PRICE ONLY **\$9.95**

plus 90c postage and shipping
no taxes anywhere

REDLINE Co.
JAFFREY, N.H. 03452

output. The biggest problem in this system, which may be considered a disadvantage by homebreeders, is the necessary stability required for the BFO, or oscillator feeding the product detector.

Example 11: If the reinserted oscillator frequency is different from the transmitter suppressed carrier frequency, the output from the synchronous detector (product detector) will show an equal difference in the audio from the original modulating frequency. The injection oscillator frequency may differ from the carrier frequency by ± 20 Hz without affecting intelligibility. However, frequency deviations greater than 50 Hz will produce only distortion from the product detector.

Reception of SSB on a receiver with a bfo is possible by setting the bfo at the center of its range and adjusting the *rf* gain control for best reception. Since only one sideband is being received, the audio gain will have to be increased. Although changing the *rf* gain will affect the S meter reading, such adjustment is necessary so that the bfo signal amplitude will be as high as possible above the signal level.

Transmission and Basic Costs

There are a number of companies which manufacture SSB adapters which can be used with most AM transmitters. The best route to go, however, is to purchase a new transmitter or transceiver. If you are still using an old AM/CW rig remember the trade-in value is getting lower every day. The cost of a 500 W (1000 WPEP) single sideband transmitter, which can be used on AM and CW by inserting the carrier, is no more expensive than an AM rig of the same power. Although the transmitter front end components, such as filters, audio networks, and

WIEMV continued from pg. 3

rich. Don't you believe it. Ham radio is merely a sideline with most of our manufacturers, or they couldn't afford to stay in business. The best you can say is that they get a tax break on their *losses* from ham radio. Just hope they stay with it, or you may have to drag out the soldering iron and go back to the easy building of AM equipment.

... Kayla WIEMV

balanced modulators are more expensive to design, there is a savings in the final amplifier where dissipation ratings can be lower than those required for AM. If you don't want to lay out any more cash than necessary (who does?) you can use the old transmitter and receiver as trade-ins on a new transceiver.

Example 12:

	<i>Old</i>
Surplus SP-600	\$300
65 W Ranger II	\$150
	<hr/>
Trade-In Value	\$450
	 <i>New</i>
400 WPEP Swan 350	\$525
w/Power Supply	
Trade-In	\$450
	<hr/>
Cash Outlay	\$ 75

If you have a linear amplifier, it can be used on SSB as well as AM. If you have been using a Class B amplifier for AM, there are plenty of articles in the "Radio Amateur's Handbook" and past issues of "QST" and "73" which provide information on construction of a linear and which could be used to modify the Class B amplifier to Class AB.

Now that you have read about the differences and possible advantages of SSB, how about dropping a line to one of the equipment dealers advertising in "73" and asking for a trade in quote on your old rig toward a more efficient SSB system. They will even pay the shipping costs!

... K3PUR

References:

- Stoner, "New Sideband Handbook"
- Capitol Radio Engineering Institute, "Communications Engineering Technology"
- ARRL, "The Radio Amateur's Handbook"
- Goodman, "What is Single Sideband Telephony?", QST, January 1948
- Norgaard, "What About Single Sideband?", QST, May 1948

MOVING?

Every day we get a handful of wrappers back from the post office with either a change of address on them or a note that the subscriber has moved and left no address. The magazines are thrown out and just the wrapper returned. Please don't expect us to send you another copy if you forget to let us know about your new address. And remember that in this day of the extra rapid computer it takes six weeks to make an address change instead of the few days it used to when we worked slowly and by hand.

Limitations on Antenna Reciprocity

W. B. Cameron WA4UZM
324 South Riverhills Drive
Temple Terrace, Florida 33617

This is an attempt to answer the question "How come?" in the February, 1968 issue of 73. Most amateurs are acquainted with the theory (variously called the Rayleigh-Helmholtz theory or the Carson theory of reciprocity) that a good transmitting antenna is reciprocally a good receiving antenna. This works well enough for us to tune an antenna in the one mode with reasonable confidence that it will then perform adequately in the other. However, as with most scientific theories, there are a number of underlying assumptions about other conditions being limited, uniform, and unvarying, and if one or more of these assumptions is not met, performance will be different from what is theoretically predicted. As anyone who has studied antennas carefully will attest, the complications in this field are indeed wonderful, but let us briefly examine a few which are quite likely to affect the amateur's attempt to estimate antenna performance.

In the first place, arguing that an antenna will perform reciprocally in the receiving and transmitting modes assumes that the medium in which wave propagation takes place is homogeneous. This is pretty nearly true for antennas which are mounted high above the earth and operating at line of sight distances with their major axes properly oriented, such as with VHF antennas situated on high towers operating over flat terrain. This assumption is almost never met on the lower bands or under skip conditions. Most amateurs are acquainted with what is called "one-way skip". Conditions can exist whereby the medium in which the wave is propagated is much more favorable for transmission from point A to point B than it is from point B to point A. One of the situations in which this is most readily apparent is on the VHF bands when there is a discontinuity in the temperature of the air masses overhead, producing what is frequently called tropospheric bending. The

lens or prism effect in the air masses does not always work precisely the same going both ways. However, the lens is merely a crude analogy when applied to a discontinuity of the air, as is the analogy of a mirror to describe the higher ionized strata which turn a radio wave back toward earth.

Another complication of reflected propagation is that radio waves which go into the ionosphere may become turned around or twisted before being sent back. The result is that a wave which is vertically polarized upon leaving the transmitter may return to some far distant receiving station in a horizontally polarized condition. This means, of course, that an antenna which favors horizontal polarization usually works much better in receiving such a DX signal, although it may not make much difference in transmitting. This may be one of the reasons why people complain about the ineffectiveness of vertical antennas for receiving, although they consistently perform well for low-angle radiation in transmitting. It is not merely that the antenna may not work exactly the same both ways, but the same antenna used for receiving may not face the same conditions that it itself produces in transmitting.

On 144 MHz in the early 1950's, some of us in Cincinnati established to our own satisfaction that, for receiving, capture area was almost as important as gain itself. One of my friends found that transmitting with a large collinear ("bedspring") instead of a Yagi did not produce an appreciably greater signal in the other man's receiver but its use would greatly enhance the signal received at his own end. The explanation seems to lie in the greater capture area of the large "flat" antenna compared to the small "pointed" one. Unfortunately, to simulate this on low frequencies would require an installation comparable to some of the big transmitting antennas at the Voice

of America, consequently few hams ever get a chance to investigate the effect of capture area on the low frequency bands.

Related to this problem of capture area is what we might term the angle of acceptance of an antenna. This becomes a factor in multiple element arrays which are not flat with respect to the incoming wave front, whether of the Yagi or Quad or other type. We said that the reciprocity theory could be expected to work only if the antennas were properly oriented. Very few amateurs, even on the VHF or UHF bands, have facilities for controlling the orientation of the antenna except in rotating it horizontally (northeast, southwest, etc.) We know that the signal is not coming in parallel to the earth, but we usually do not do anything about it. Now if we were able to tilt the antenna boom and also rotate the boom axially we could begin to adjust the antenna to the proper attitude with respect to the wave fronts coming in. Some very surprising things would result if we could do so, and anyone who has tried it will bear this out.

I suspect that it is this factor of vertical orientation which may go far to explain the question asked by W4YM, with reference to comparing his two-element and four-element Quads. Much of the signal coming into either antenna is not coming straight on into the cone which we imagine in front of the leading element. Much of the signal is coming in from various angles above this.

Now if the vertical pattern of the antenna were smooth and regular, the angle at which the signal came into it would of course affect the "S" meter reading to some extent, but would not be very critical. Certainly it should not be any more critical than the horizontal angle, which is what we usually consider in the case of a beam. However, the fact is that on many antennas the vertical pattern exhibits several lobes and partial nulls. These are not planned and they are not particularly useful, and for the most part they are completely ignored. However, if the antenna happens to have a null in the forward direction at say, thirty degrees from the vertical, then with signals coming in at this angle, rotating the antenna horizontally will have very slight or erratic effects as compared to the antenna's performance on low-angle DX signals. Anyone who has played around with rotary beams during times of extreme short

DUAL GATE MOSFET PRE-AMPS



to 175 MHz. **\$19.95** ppd.
to 300 MHz. **\$23.95** ppd.
to 400 MHz. **\$27.95** ppd.
to 450 MHz. **\$31.95** ppd.

- Available from 5 MHz. to 450 MHz. Bandwidth is approximately 3% of frequency.
- Voltage gain 30 to 40 DB depending on frequency.
- Two **Dual Gate** MOSFET amplifier stages with each having a tuned input and tuned output. Each Dual Gate MOSFET is actually an integrated cascode circuit thus giving you 2 cascode circuits equivalent to 4 triodes.
- Exceptionally low noise (2.5 DB at 175MHz.), greatly reduced cross modulation and 10 times the dynamic range (signal handling capability) of the best bi-polar transistors. Also superior to preamps using junction FETs and Single Gate MOSFETs.
- Internal connections for high impedance AGC or manual gain control if needed.
- Type BNC input and output receptacles for minimum loss at UHF. Standard impedance is 50-75 ohms.
- Carefully tuned at our laboratory with sweep generator and oscilloscope for the best bandpass characteristic.
- Full wave UHF diodes protect input transistor.
- Operates on 6 to 16 volts DC, 5 to 15 Ma.

VANGUARD LABS

Dept. H

196-23 Jamaica Ave., Hollis, NY 11423

*Please use your Zip
Code When Writing 73*

CLEVELAND OHIO

TT63A Repeater	NEW	34.95
255A Polar Relay	NEW	2.95
ID91B/ARN6 Radio Compass	Used Good	4.95
Model 19, like new		145.00
Duodial Turns Counting 0-40-1/4" Shft.		1.25
1M-123/PD Radiation Detector		10.95
Sound Powered Telephones, new case		10.95
AA 210 Monitor Scope 2" PT of URA/8....		7.50

DIXONS

586 E. 140-AT-FREEWAY
216-421-2230

**"THE COMPLETE HAM STORE"
WHERE YOUR DOLLAR BUYS THE MOST**

All leading lines of amateur gear:
We give best trade-in allowance
for your gear on new equipment:
Call us for the best deal:

**WE PAY CASH FOR HAM & CB RADIOS
CALL OR WRITE**

BOB'S AMATEUR ELECTRONICS
927 N.W. 1st. St., OKLA. CITY, OKLA. 73106
Phone 405-CE-5-6387

SURPLUS ELECTRONICS

ARC-3 TRANSMITTER 100-156 MCEX \$24.95
SK-980 PHANTOM ANTENNANEW \$ 6.50
GO-9 TRANSMITTER 300 KC-18MCNEW \$75.00
GP-7 TRANSMITTER 800 KC-9 MCNEW \$37.95
BC-604 FM TRANSMITTER 20-27 MCEX \$ 7.50
BC-924 FM TRANSMITTER 27-38 MCEX \$12.95
BN IFF SET 150-180 MC 110VAC 60CYNEW \$59.95
BC-456 ARC-5 MODULATORNEW \$ 3.75
WESTINGHOUSE 6 IN. DC AMP METERS, LEE SHUNT
A1 100-0-100 AMP
A2 150-0-150 AMP
A3 200-0-200 AMPNEW \$ 8.50
T-26 CARBON MICROPHONENEW \$ 1.30
MP-22 ANTENNA BASENEW \$ 2.75
ARB CONTROL BOXNEW \$ 1.25
BC-450 CONTROL BOXNEW \$ 2.39
T-28/APT-1 RADAR TRANSMITTER
90-200 MCNEW \$19.95
RT-45/ARQ-1 TRANSCEIVER-JAMMER
14-50 MCNEW \$34.95
BC-617 FM RECEIVER 30-50 MCEX \$24.95
BC-1158 AM TRANSMITTER 50-90 MCEX \$29.95
TS-11 HANDSET WITH PL-106NEW \$ 4.50
BC-605 INTERPHONE AMPLIFIER 12VDC ..NEW \$ 5.95
MARK II HAND GENERATOR, OUTPUT
162 VDC, 3.1 VDC\$ 5.95
T-61/AXT-2 TELEVISION TRANSMITTER ..NEW \$42.95
PRICES: FOB INDIANA, PA. NO C.O.D. ORDERS
MIN. ORDER \$5.00 NOT INCLUDING POSTAGE.

PENNSYLVANIA ELECTRONICS
P.O. BOX 127
INDIANA, PENNSYLVANIA 15701

DXERS and DXERS-TO-BE

Want to keep up to the minute of what's happening DXwise? Subscribe to Gus Browning W4BPD's new weekly DXERS MAGAZINE. 24 pages of DX events, coming up DXpeditions, QSL info, pix, etc. Rates, US surface \$11.00. US air mail \$12.90, West Indies \$18.50, S. America and Europe \$23.00, rest of world \$30.00.

New rates due to postal increase

The DXERS MAGAZINE

c/o W4 BPD

Route 1, Box 161-A,
Cordova, S.C., U.S.A. 29039

**HEY, THERE!!!! YOU WITH ALL THAT
ELECTRONIC GEAR IN YOUR SHACK!**

Don't clutter up your home with all that stuff! Better to clutter up our warehouse — and get paid in the bargain! Don't waste time asking us for prices. **Tell us exactly what you want** for your Gen Radio, H-P, Tektronix, ARC. GRC, TED, PRC, VRC, ARN, URR, APN and other military/commercial gear.

COLUMBIA ELECTRONICS, Dept. 7

4365 W. Pico Blvd. Los Angeles, Calif. 90019
Phone: (212) 938-3731 Cable: COLECTRON

skip can verify these facts and can probably appreciate this explanation. This does not in any way mean that under conditions of high-angle radiation and reception a beam antenna is worthless, but it does mean that we just can't point the receiving antenna at the transmitting station in *one axis alone* and expect optimum results.

By the way, one of the major advantages I see in the Quad over the Yagi is that it compresses the signal vertically as well as horizontally and for a given horizontal angle of radiation or acceptance compresses more energy, and with a smooth pattern, since it is compressing at about the same angle vertically. With many Yagis things are very much different. Some Yagis which show a fine smooth pattern horizontally have a miserable and erratic pattern vertically. The easiest way to test this is to build small tabletop antennas, using as a signal source something like an *rf* interferometer. You can learn a great many instructive things about antenna patterns in this way without a great deal of expense. A satisfactory setup is a pingpong table sitting in your carport or out in the backyard, assuming that the antenna half-wave is only about four or five inches. A severe limitation on this method, however, is that it is exceedingly difficult to learn anything about antenna feed line impedences on these small antennas. As with all other branches of antenna experimenting, you give up something for everything you get.

Further complications in trying to compare a given antenna for transmission and reception lie in matching the feed line to the load. We all know that, in transmitting, antennas should be matched, to reduce the SWR. Moreover, we have reasonably good methods of measuring this in most modern amateur shacks. Note that I only say reasonably good, because our methods are far from any laboratory standard, but they are about as close as any practical need requires. However, I have never been in a ham shack which could do an equally good job of determining the match to the receiver. If the line is behaving differently in the receiving mode from its performance in transmission, we should not expect closely reciprocal results.

When it comes to signal level measurement, most amateurs are unable to compare from one station to another with even a usable degree of accuracy. About all an

"S" meter is good for is a tuning indicator and a take-off point for limited conversation with the man at the other end. I have tried calibrating "S" meters carefully on some of the receivers that I have built, but in recent years have given up and left the things off the receiver entirely. It was simply too much trouble to try to get a scale honest and linear across a usable range and when I did, an accurate report merely insulted the guy at the other end, who had been used to inflated reports from other people using some of the commercial receivers. Let me just state briefly and succinctly that any definitive work testing the reciprocity of a receiving-transmitting antenna would require signal measurement capabilities which were both appropriate and comparable at both ends of the circuit. This is almost never approximated. The best I could ever do was to calibrate my own receiver accurately for one band, using as a reference a transmitter across town where we had a pretty good measurement of the input power, and then testing the antennas we wished to compare between these same two stations, holding other variables constant. This, bear in mind, was for one path only. I could not say anything definitive about these same antennas operating across the reverse path.

Even working between stations in close proximity you may have to select sites carefully to get a clear path. Reflections from objects near the earth do some mighty funny things to a signal and severely distort the "free space" antenna patterns. Reflections from objects far from the earth can also do funny things. I'm told that signals coming back from the moon have a reverse spin, which means that the best antenna for transmitting is precisely the opposite in this aspect from the best one for receiving. The well known spiral ray used on VHF bands attempts to accommodate waves which may be arriving horizontally, or vertically, or somewhat in between. However, it does not take into account the variability in the direction of spin. Even imagining an antenna patterned after the spiral ray but equipped with enough rotation to adjust the elements for spin, and the tilt, axial rotation, and azimuthal rotation of the boom makes one shudder. By this time, we would have so many control wires going up to the antenna that the signal would have a hard time deciding what was the feedline.

Reflectometer SWR Bridge w/Meter, 30-1000mc. ...EX 8.50
 TD123/GKA4 Demultiplexer w/132 tubes, boxed...NEW 27.50
 TS717A/APG26 Test Set for APG26, complete ...NEW 65.00
 BC733F 108-110mc Converts to Satellite Recvr. ...EX 8.75
 Weston Motor Model 843, Type 5, 500-0-500 ua ...EX 4.75
 R26/ARC5 3-6mc Receiver w/Tubes & Dynamotor...EX 9.75
 T20/ARC5 4-5.3mc used 5.00—T21/ARC5 5-7mc ...EX 6.00
 T465/ALT7 200W Xmitter 168-352mc w/2 6161's ...EX 19.50
 T465 Schematic pp. 1.00....Complete Manual pp. 6.50
 TCS12 Xmitter/Recvr Control Box with Speaker ...EX 6.75
 Jones No. 574.23 Micromatch Double Coupler ...EX 12.50
 C18 A.R.C Type 12 Equipment Control BoxNEW 1.50
 C1457 Control Box for R550/ARR40 ReceiverLN 1.75
 C760B/A Control Box for ARN14B&C ReceiversLN 2.75
 C45 Control Box for ARC1, 4 & 12 Equipment ...EX 1.35
 6161 Tube w/Connectors, 100 Watts to 1200mc.EX 6.75
 R101A/ARN6 100-1750kc Receiver. Four Bands ...EX 27.50
 ID91B/ARN6 4" Navigators Bearing Indicator ...EX 7.50
 AS313B/ARN6 Station Seeking Loop, 100-1750kc. ...EX 6.25
 ID169C/APN12 3JP1 CRT Scope. Coax Switch ...NEW 14.50
 PP336 Main Power Supply for APR9 Receiver ...EX 16.50
 PP337/APR9 Klystron Supply for TN130, TN131 ...EX 10.50
 ID226 Panoramic Indicator for APR9 Receiver ...EX 14.50
 Scope Xformer 1950@3ma 5 Fil Windings 60cy ...NEW 4.75
 SA325/U Coaxial Swith SP4T 28VDC MotorEX 6.50
 Adaptor Cable PL259 to BNC Panel SocketLN 3/1.75
 Fiberglass Insulating Rod ¼" Dia by 7½" Long ...EX 5/1.00
 OHMITE Z-50 Radio Frequency ChokeEX 6/1.00
 Rt. Angle Drive w/Gears, Universal, ¼" Shafts...EX 2/2.50
 Feed-thru Capacitors 15 on Panel....Three Panels .../1.00
 BNC (UG290/U Coaxial Panel SocketsEX 8/1.00
 Coax 6" long w/BNC (UG260A/U) Plug each end EX 5/1.00
 Coax 8" w/1 BNC Plug & 1 BNC Panel Socket ..EX 4/1.00
 Schematics: R45/ARR7, R105/ARR15, R316/ARR26, R5/
 ARN7, R101A/ARN6, RT58/ARC12, ID226/APR9 pp Ea. \$1

E. C. HAYDEN Box 294, Bay Saint Louis,
 Mississippi 39520.
 Prices: FOB Bay Saint Louis. Terms: Net, Cash.

**Wouldn't Your
 Ad
 look good Here?**

the permaflex key

- both a twin lever & straight hand key in a pivotless 2 paddle design.
- gives instant choice of automatic semi-automatic & straight hand keying.
- use directly with any transmitter or through an electronic keyer.
- 8 amp. gold diffused silver contacts adjust from 0-.060" & 5-50 grams.
- distinctive blue paddles are of rugged G-10 fiberglass epoxy.
- cabinet is 16 gauge polished chrome steel: 1.95" sq. x 3.75", paddles extend 1.25", weight app. 1 pound.
- silicone rubber feet for stability.
- 100% US made & guaranteed for 1 yr.



1995 complete,
 ppd usa & can.
 send a check or m.o.
 sold by mail only

James Research company, dep't: AR-K
 11 schermerhorn st., brooklyn n.y. 11201

In short, reciprocity theory is a great thing if you respect it for what it is. It does not readily permit an amateur to compare two different kinds of antennas with respect to different modes of use without controlling any of the other variables, which include all of the ones we have listed and a few more. In the words of one of my engineer friends, "What you have here is a complex system, and complex systems are always worse than simple systems, and simple systems are bad enough!"

...WA4UZM



CASSETTE TAPE RECORDER


After testing a dozen different makes of cassette tape recorders we found that the Valiant was by far the easiest to use. The fidelity is good and the push button system outstanding. Has battery level meter, recording level meter, jack for feeding hi-fi or tv, operates from switch on mike. Great for recording DX contacts, friends, at the movies, parties, unusual accents and things like that. Once you try it you will be using it like a camera. Check this price anywhere, it is a lulu!

SPECIAL, ONLY \$33.00 pp

24 HOUR CALENDAR CLOCK

This clock reads out the day, date and time in large, easy to read numbers. None of that little tiny number business for your shack. Set this up on GMT and never make a mistake again on logging time and date. 8"x3 1/2"x3 1/2", brushed aluminum case. Synchronous self-starting movement, 110 v 60 cycles. Make your operating desk look outstanding with this new type of clock.


SPECIAL \$49.50 pp

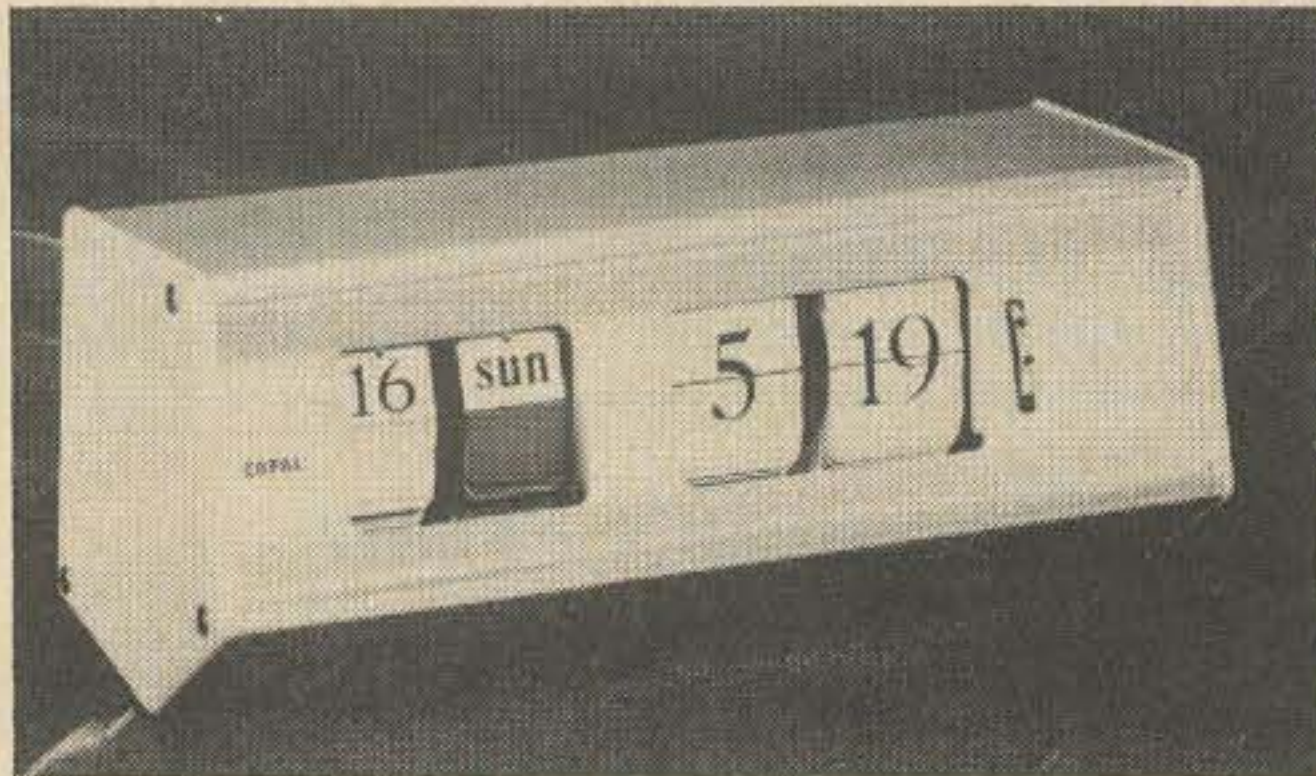

TRAVEL-CLOCK RADIO

Eight transistor clock radio, complete with clock, radio alarm, and slumber setting! Weighs less than 1 1/2 pounds. Great gift for a traveling friend or relative. Or yourself. Earphone for private listening, if you like. Batteries included.

SPECIAL ONLY \$24.00 pp

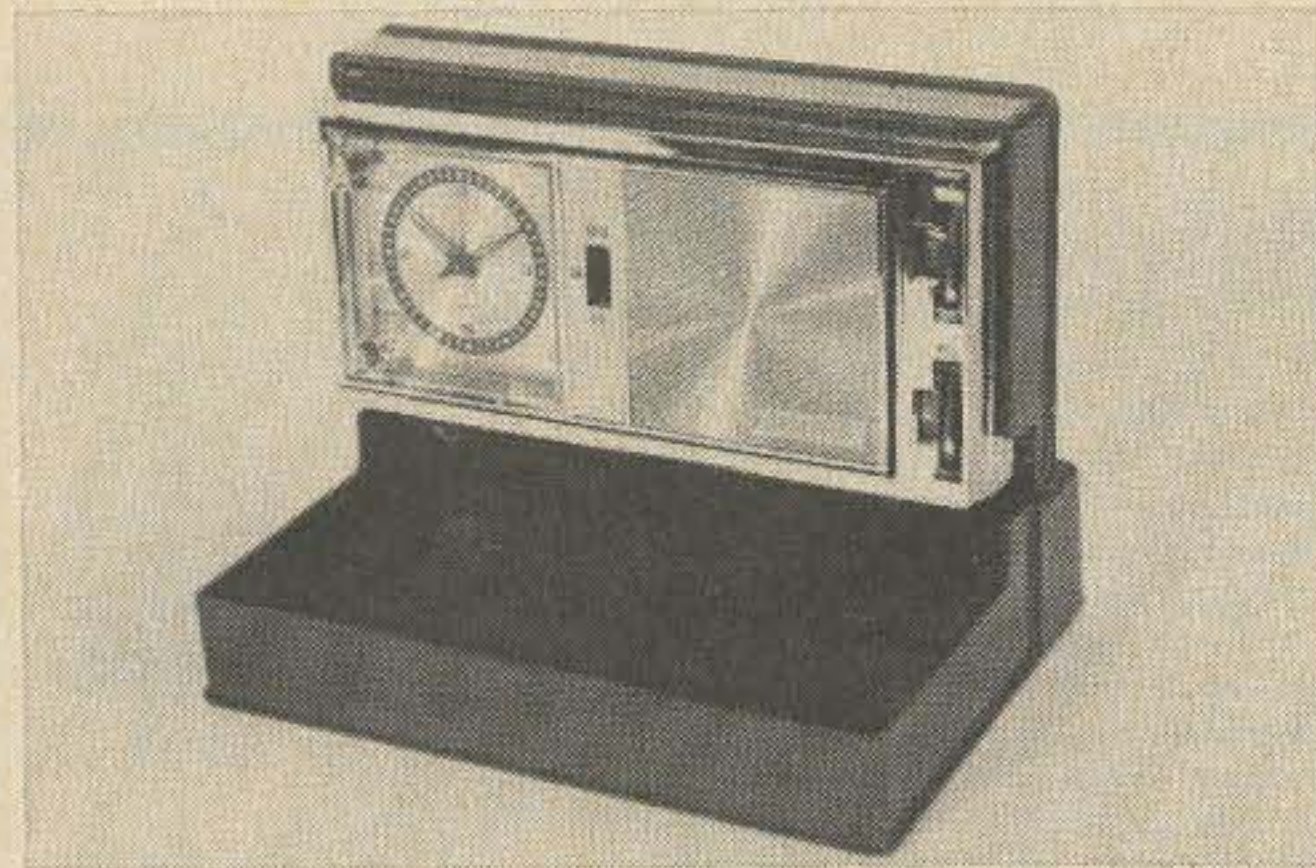

AM-FM DIGITAL CLOCK RADIO

Here is something entirely new in clock radios - a digital clock plus a very sensitive AM-FM with AFC radio. This is the first digital clock radio ever imported into the U.S. The radio is all solid state, of course. This makes a wonderful radio for the bedroom. Price clock AM-FM radios, even in the bargain fliers, and notice the amazing low price for this one.

SPECIAL ONLY \$38.00 pp

DESK NAME PLATE

Your name and call on a beautiful desk plate might normally cost you around \$10. These plates are walnut grained and are available with up to 20 letters and spaces. You can have your full name or your first name and call. Immediate delivery on all orders. 10" long by about 1" high. Identify your station with one of these plates.

SPECIAL \$2 pp



REDLINE, Jaffrey, N.H. 03452

Please send postpaid the following;
check enclosed.


- | | |
|---|-------------------------------------|
| <input type="checkbox"/> tape recorder | <input type="checkbox"/> desk clock |
| <input type="checkbox"/> travel clock radio | <input type="checkbox"/> name plate |
| <input type="checkbox"/> clock am/fm | |

Name & call

Address

City & State Zip

FOLLOW ME TO FOR YOUR

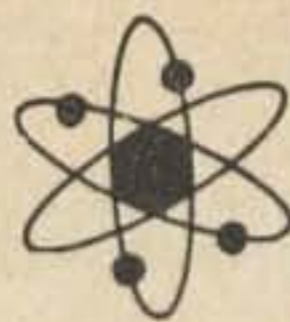

stellar industries
DIV. OF STELLAR I, Inc.
SALES AND SERVICE

AEROTRON
AMECO
ANTENNA SPECIALISTS
COLLINS
CORNELL DUBILIER
CUSH CRAFT
R. L. DRAKE
DOW KEY
EDITORS & ENGINEERS LTD.
EICO
ELECTRO-VOICE
ESSCO
E-Z WAY
GALAXY

GONSET
HALLETT
HALLICRAFTERS
HAMMARLUND
HY-GAIN
ICE
E. F. JOHNSON
LINEAR SYSTEMS
MARS (PAUSAN)
McINTOSH
MOSLEY
MOTOROLA
NATIONAL
NEWTRONICS

OMEGA-T
RSGB
RADIO AMATEUR CALLBOOK
REGENCY
RUSSELL INDUSTRIES
SBE — WEBSTER
SHURE
SWAN
TELEX
TURNER
UNADILLA
VIBROPLEX
WATERS
WILCOX
NEEDS

GLEN FADDEN, W2CXX/2

10 GRAHAM ROAD WEST • ITHACA, N. Y. 14850 • TELEPHONE AREA CODE 607 273-9333


HOURS: 9:00 A.M. to 5:30 P.M. Monday through Friday 9:00 A.M. to 5:00 P.M. Saturday



"I wouldn't mind so much—but she got custody of our color TV and my short wave rig."

M. W. TOWNSEND

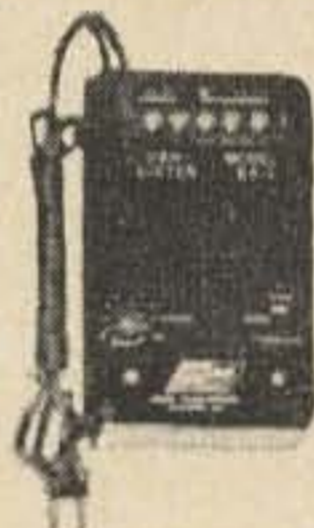HAVE YOU A PERFECT FIST? M&M'S NEW ELECTRONIC KEYS CAN PERFECTIFY YOUR CW TO 40 WPM!



- Trouble free solid state circuitry.
- Every letter perfect: self completing dah's and dits, 3/1 perfect ratio.
- AC powered: no batteries to die.
- Isolated relay output works with any rig.
- Built in monitor.
- Works with your present key or bug.

M&M Electronics Dah-Ditter model EK-1 only \$34.95 postpaid in USA and possessions

Send your order direct to:

M & M ELECTRONICS Keyer Dept.
6835 Sunnybrook, N.E., Atlanta, Georgia 30328

oscillator/monitor^{mark 2}

- makes an audible tone to monitor the RF of any CW transmitter from 10Mw to 1 Kw & 100Kc to 1000Mc, using only an 8" pickup antenna.
- can be self-triggered for code practice or the testing of solid state components and circuits.
- aids in tuning up & testing RF oscillator and power circuits.
- 4 transistor, 2 diode circuit, speaker, tone adjust, AA pencil, test leads, 8" ant., & magnetic base.
- cabinet is 16 gauge black & clear anodised aluminum, 3.4 x 2.3 x 1.2" US made & guaranteed for 1 year.



14.95 complete, ppd usa & can. send a check or m.o. sold by mail only

James Research company, dep't: AR-M
11 schermerhorn st., brooklyn n.y. 11201

Index To Articles

Appearing in 73 Magazine in 1968

Antennas and Transmission Lines

General

2 Elements Spaced a Quarter-Wavelength Schultz, W2EEY	Jan. p. 22
How Come? Van Slyck, W4YM	Feb. p. 14
Waterproof Connections, Townsend, K9BXG	Feb. p. 89
Witching for Better Grounds Davey, W7CJB	Mar. p. 46
Getting the Most Out of Link Coupling, Thoma, K1GBF	Mar. p. 62
Checking Your VSWR Indicator, Drumeller, W5EHC	Apr. p. 22
Do It With a Wire, Stortz, K3QKO	May p. 14
A Durable New Gamma-Match, Attaway, K4IIF & Frederick, K4ELB	May p. 16
How To Hang a Dipole, Ashe, W2DXH	May p. 18
Computer Design of Beam Antennas, Cameron, WA4WWM	May p. 34
Triangular Loop Beam 7 thru 28 MHz, Watson, W6DL	May p. 50
Detriments Can Be Beneficial, Roberts, W9HOV	May p. 79
The 321—A New Quad Design, Johnson, WA1BUN	May p. 99
Getting Your Higher Class License Part 4—Antennas, Transmission Lines and SWR, Staff/73	
The Collinear Resurrected, Babcock, WA1DVB	Aug. p. 28
Using Thin-Wire Antennas, Schultz, W2EEY/2	Nov. p. 42
Limitations on Antenna Reciprocity Cameron, WA4UZM	Dec. p. 92

hf (to 30 MHz)

Wideband Baluns the Easy Way Cooper, K4ZZV	Jan. p. 24
The Ferris Wheel Antenna for 160- and 80-meters (correction Apr. p. 26) Spillane, W7UGV	Feb. p. 20
160 Meter Flat Top Herr, W3WPV	Mar. p. 30
More on More Contacts from Within Curtis, K3RXX	Mar. p. 54
Converting the TA-33 Jr. to Full- Power 15 Meter Beam, Attaway, K4IIF	Mar. p. 78
Practical Miniature Antennas For 80 Through 10 Meters, Gilmer, W8VVT	May p. 6
The Diamond Array, Gardner, W6LNN	May p. 10
How to Hang a Dipole, Ashe, W2DXH	May p. 18
Matching Stubs, Evans, WA5STM	May p. 24
A Ten Meter Folded Dipole Antenna Marriner, W6BLZ	May p. 30
The Duo Vee Beam Antenna Spiess, K1UFQ	May p. 32
A Primer of Basic Antenna Theory Nelson, K6ZGQ/5	May p. 40
Triangular Loop Beam 7 thru 28 MHz Watson, W6DL	May p. 50
3 on 20 for 15, Rock, WA4YVQ/4	Aug. p. 24
Mini Boom Quad, Jordan, VE6FS	Aug. p. 26
The Collinear Resurrected Babcock, WA1DVB	Aug. p. 28
Trapping Strong Signals, Conklin, K6KA	Aug. p. 68
The Hustler 4-BTV Fixed Station Trap Vertical Antenna, Lovelock, W6AJZ	Aug. p. 70

vhf (30 to 300 MHz)

The Two-Meter Groundplane as a Gain Antenna, Sessions, K6MVH	Jan. p. 18
A Simple and Inexpensive Cavity for Six Meters, Marquardt, K9SOA	Jan. p. 76
Why Not? Lingenbrink, W6HGX	May p. 11
The Plan Ahead Antenna Mollentine, WAØKKG	Aug. p. 69
Going VHF—In the Mobile Brown, W9HDF	Sept. p. 6
Starting Off on VHF, Irace, WA1GEG	Sept. p. 32
The VK3ATN Moonbounce Rhombic Green, W2NSD/1	Sept. p. 44
Building a Two Meter Ground Plane Klinert, WB6BIH	Oct. p. 91
Practical 6 Meter Ground Plane Construction, Brown, W8JZI	Oct. p. 102

uhf (300 MHz up)

1296 Megacycles—1968, Ashby, K2TKN	Sept. p. 42
------------------------------------	-------------

Towers

A Solid Dead-Man, Woolner, WA1ABP	Apr. p. 30
Let's Build a Tower, Cousins, VE1TG	July p. 6
Why Not a Tilting Tower? Watson, W6DL	July p. 12
A 40 Foot Non-Conductive Sky-Hook Peterson, K7VBJ	July p. 16
The Beam Pole, Hirt, W7GBJ	July p. 24
Tilt That Tower, Bryan, W2AJW	July p. 28
The New Tower, Smith, WA2GXT	July p. 37
Wind Loading on Towers, Eldridge, VE7BS	Nov. p. 117

Clubs, Amateur Radio

A Word To Radio Clubs Green, W2NSD/1	Feb. p. 32
How is your Club Paper? Good or Bad? Steinberg, K6GKX	Feb. p. 38
How to Publicize Your Club Sheldon, K4HKD	Feb. p. 54
The Care and Feeding of a Ham Club Allen, W5NQQ	
Part 1	July p. 54
Part 2	Aug. p. 50
Part 3	Sept. p. 86
Part 4	Oct. p. 98
Part 5	Nov. p. 118
Part 6	Dec. p. 52

Corrections

The Ferris Wheel Antenna (Feb. p. 20), Spillane, W7UGV	Apr. p. 26
Mighty Four on Six (Nov. 67 p. 24), Davisson, K9VXL	June p. 39
Narrow Band Frequency Modulation (Mar. 68 p. 6), Berhley, WB2CPG	June p. 47

Commercial Equipment

Reviews

- The Amphenol Millivolt Commander
Bloom, W1EMV June p. 56
- Reviewing the Heath HW-16 CW
Transceiver, Curtis, K3RXX June p. 76
- An Evaluation of the Heathkit IM-17
Solid State Voltmeter
Pfeister, W2TQK Aug. p. 34
- The Hustler 4-BTV Fixed Station Trap
Vertical Antenna, Lovelock, W6AJZ Aug. p. 70
- A Review of the Heathkit SB-110A
Lewis, Matthew Sept. p. 60
- Hallicrafters SR-400, Green, W2NSD/1 Oct. p. 48

Modifications

- Transceiving With an Outboard Receiver
Lehrbaum, WA2APT Mar. p. 62
- Full Breakin for the Galaxy III or V
Bierbaum, W0JHD May p. 80
- Modifying the Clegg 99'er
Porcaro, WB2JOS June p. 12
- Low-Cost Conversion of Surplus
Oscilloscopes, Brown, W8JZI June p. 22
- Crystalize that FM Rig
Zook, K9STH/5 June p. 24
- Restoring Old Equipment
Schleicher, W9NLT June p. 32
- SB-33 Note, Agrelius, K9SHA June p. 39
- New Life for an Old Work-Horse
Zook, K9STH/5 June p. 40
- ALC for the C E 100V and 200V
Sieg, K1AQI June p. 66
- Eliminating Chirp in the DX-60A
Fetner, WB4EFA July p. 59
- Split Frequency with the S-Line
Milius, W4NJF Aug. p. 45
- Make Your Swan 250 6-Meter Transceiver
Even Better, Mohr, K8ZHZ Aug. p. 77
- De-Humming the Swan, Conklin, K6KA Aug. p. 85
- Communicator Reborn
Lingenbrink, W6HCX Sept. p. 14
- More on Receiver Blocking
Conklin, K6KA Oct. p. 72
- Improving Frequency Stability in
Older Receivers, Wilson, W6NIF Oct. p. 94

Conversions

- The ARC-5 Transmitter Receiver
Klinert, WB6BIH June p. 10
- Use of the Wilcox F3 as a WWV Receiver
Olson, W6GXN June p. 28
- Modification of the TRA-19 Amplifier Cavity
to 432 MHz, Crowell, K6RIL June p. 44
- A Poor Man's Mil Spec
Pafenberg, W4WKM June p. 58
- Putting The RF-209/PRC on Two Meter FM
Owings, K0AHD June p. 96
- Converting the ARC-1 Guard Channel
for Two Meters, Davey, W7CJB June p. 100
- Save That Cordless! Smith, W3GKP Oct. p. 88
- Double Conversion of the BC-348-M,
George, VU2TV Nov. p. 54

Construction Techniques

- Preventive Maintenance
Brogdon, K3KMO Apr. p. 70
- Crystal Etching Tips, Stinnette, W4AYV Apr. p. 76
- Restoring Old Equipment
Schleicher, W9NLT June p. 32

- Labels for Homebrew Gear
Grimes, W4LLR June p. 48
- Soldering is Easy, Stankiewicz, WB2ZNC June p. 75
- A Plague in Your Panel, Green, W3RZD June p. 108
- More On Crystal Etching, Kyle, K6GRP July p. 50
- Photographic Printed Circuit Process
Connors, W6AYZ Aug. p. 14

Counters

- Counter Connections, Smith, W3GKP June p. 50
- Additional Notes on the IC Electronic
Counter, Jones, W1PLJ June p. 74
- Integrated Circuit Frequency Counter,
Votipka, WB6IBS Nov. p. 20

CW and Keying

- An Integrated Circuit Electronic Keyer
Jones, W1PLJ Feb. p. 6
- Tips for the CW Contester and DX'er
Nose, KH6IJ Feb. p. 50
- The Polar Key, Oliver, K4YWS Apr. p. 20
- The Dollar Fifty-Super Nifty
Joffe, W3KBM June p. 30

DX

- Gus: Part 31, Browning, W4BPD Jan. p. 114
- How to Plan Your Own DXpedition
Persons, W4PJJ Feb. p. 34
- How to Get Better Returns from Your QSL
Persons, W4PJJ Feb. p. 48
- The QSL Manager, Milius, W4NJF Mar. p. 26
- Recovering "Lost" QSLS,
Etheredge, K6UMV Apr. p. 58
- The Anatomy of a Pile Up
Wagner, G3BID July p. 74

Fiction and Humor

- A Grey Beard Writes, Hellman, K2TAJ Feb. p. 62
- The Ham, Day, Nina Mar. p. 50
- S-9-Manship, Wren, W6DFT Mar. p. 56
- A Ham's Shack Is His Castle
Semorile, W6LNG Mar. p. 64
- The Scientific Method
Foster, Herbert Mar. p. 82
- The YF Fights Back, Sessions, WA6SPT Apr. p. 48
- And They Called "Mother Shipton" Crazy
Spencer, K4FQU Apr. p. 56
- Take Uncle Alf's Advice and You Will
Do All Right, Wilson, W6NIF Apr. p. 86
- Dilemma In Surplus, Cole, James June p. 78
- Ipecac Work on Lids, Manning, K1SYD Nov. p. 102

FM

- Narrow Band Frequency Modulation
(Correction June p. 47)
Berhley, WB2CPG Mar. p. 6
- FM'ing A VFO, Schliesser, WA6UFW Oct. p. 110

Hints and Kinks

Getting the Most out of Small Modulation Transformers, Byrne, G3KPO	Jan. p. 101
Cheap & Rugged Portable Speaker Enclosure Sheldon, K4HKD	Feb. p. 88
Waterproof Connections Townsend, K9BXG	Feb. p. 89
A Sturdy Boom Clamp, White, W6BKX	Mar. p. 34
The Crystal Shopping List Cameron, WA4UZM	Mar. p. 44
Detriments Can Be Beneficial Roberts, W9HOV	May p. 79
Transformer Tricks, Grimes, W4LLR	June p. 6
Banana Plugs Fit Into Coax Jack Hausman, VE3BUE	June p. 31
Stop Those Slipping Knobs Hausman, VE3BUE	June p. 42
Salvage Those Old Transistor Radios and Recorders, Eslick, KØVQY	June p. 46
Amateur Applications For Inexpensive Tape Recorders, Schultz, W2EEY	June p. 70
Coiled Cords Untangle Test Leads Hausman, VE3BUE	June p. 98
250 Sockets, Jack, WA3AQS	June p. 99
Non Slip Key Base, Hausman, VE3BUE	June p. 103
High Voltage Battery, Hausman, VE3BUE	June p. 109
Burn Prevention, Hausman, VE3BUE	July p. 21
Panel Gap Filler, Ives,	July p. 33
A Confined Space Nut Starter Hausman, VE3BUE	July p. 59
Ventilation by Elevation Hausman, VE3BUE	Aug. p. 27
Trapping Strong Signals, Conklin, K6KA	Aug. p. 68
Increasing Pilot Lamp Life Urke, WB6ZOA	Aug. p. 84
Surplus 220 Volt AC Circuit Hartstein, WB6NWW	Aug. p. 87
Build Yourself a Relegator, Kyle, K6GRP	Oct. p. 75
Test Aid for Motorola FM Transmitters Romelfanger, K6PKQ	Oct. p. 79
VOM Sensitizer, Firestone, WN6ZRB	Oct. p. 96
Darn-Handy VHF Monitor Campbell, W4KAE	Oct. p. 104
A Real "Big Switch," Turner, WAØABI	Nov. p. 19
Organizing a Resistor Collection, Turner, WAØABI	Nov. p. 64
Cheap rf Weatherstrip, Turner, WAØABI	Nov. p. 75
Cord Untangler, Turner, WAØABI	Nov. p. 85
The Solder Saver, Klinert, WB6BIH	Nov. p. 116
Mouse Tunnels, Carroll, K6HKB	Dec. p. 12

Instruction, general

Sideband Filters, Silverman, WB2GYS	Jan. p. 14
Diode Circuits Handbook Franson, WA1CCH	Jan. p. 1A
Novice Data, Welsh, W6DDB	Jan. p. 90
An Amateur Tries IC's McCullagh, VE3DAN	Feb. p. 16
Electronic Temperature Measurement McCarthy, K6EAW	Feb. p. 70
DB—A Curious Animal, Roberts, W9HOV	Mar. p. 17
Receiver Front End Protection Jones, W6AJF	Mar. p. 20
Getting the Most out of Link Coupling, Thoma, K1GBF	Mar. p. 52
VHF Operation by Remote Control Sessions, K6MVH	Apr. p. 32
A Career in Electronic Engineering Kelly, W6JTT	Apr. p. 50
You Can Pass The Extra, McKee, K6YA	Apr. p. 73
Some Audio Thoughts, Joffe, W3KBM	July p. 40
db, Bach, WB2PAP	July p. 42
How To Pass Your Extra by Learning Klinert, WB6BIH	Aug. p. 74
Transit Time—So? MacArthur, K9UYA	Aug. p. 80
So You Think You're on Frequency Sessions, K6MVH	Sept. p. 27
Parallel-T Network Design, Kyle, Jim	Sept. p. 30

Learning the Radio Code if You're Over 30, Ashe, W1EZT	Sept. p. 34
TABLES OF ELECTRONIC SYMBOLS FOR 73 CONTRIBUTORS	Sept. p. 94
Transistor Regenerative Detector Ashe, W1EZT	Oct. p. 76
"Q", "Q", Who Got "Q", Votipka, WM6IBS	Oct. p. 82
Harness Your Wiring, McGee Jr., K5LLI	Nov. p. 66

Instruction, Special

Getting Your Higher Class License, Staff/73	
Part 1. Radio Wave Propagation	Mar. p. 92
Part 2. Sideband	May p. 82
Part 3. Oscillation, Feedback, Harmonics	June p. 80
Part 4. Antennas, Transmission lines, and SWR	July p. 76
Part 5. Receivers	Aug. p. 54
Part 6. Transmitters	Sept. p. 74
Part 7. Measurements	Oct. p. 58
Part 8. Transistors	Nov. p. 92
Part 9	Dec. p. 56
Copper Wire, Ashe, W1EZT	Nov. p. 70

Lab and Workshop Notes

The Nurture and Care of a Junk Box Fleming, WØHMK	Feb. p. 30
Solder, Ashe, W2DXH	June p. 60
Appliance Operators—Please Turn Page Lansing, WA4WAI	Sept. p. 59
The Ham Workshop, Hayward, WØPEM	Oct. p. 38
"CV" Transformers for Ham Applications, Collyer, WA9CQN	Nov. p. 28

Miscellaneous

Tuning in on Bonadio's Satellites Bonadia, W2WLR	Jan. p. 10
Fire in the Hamshack—Are You Ready? K4SEL/DL5AF	Jan. p. 34
A Homebrew Operating Desk Michaels, WB2WYO	Jan. p. 74
1968 YL/OM Contest, WØHJL	Jan. p. 82
Hydonics or Radio? Eldridge, VE7BS	Feb. p. 66
Go Ahead! Run Away To Sea Treftz, K4UDP	Mar. p. 32
The Little Gem Fuse Tester Baird, W7CSD	Apr. p. 15
An Invisible Antenna, Bloom, W1EMV	Apr. p. 42
Using Your Electromagnetic Wave Padgett, WA5HPV	Apr. p. 44
What is YOUR "Amateur Q?" Fincutter, K3STU	Apr. p. 52
ASSB, Mei, K6ICU	Apr. p. 64
Amateur Radio and Public Service Flinn, W2CFP	May 1968 p. 74
Microfilm Your Magazine, Allen, WA4HRX	May p. 76
Electricity Abroad, Marovich, Scott	July p. 27
How To Write for Service Information Fried, K2PTS	July p. 52
Why Not a Photographic QSL? Green, W3RZD	July p. 60
QSL Display—The Easy Way Hausman, VE3BUE	Aug. p. 48
Binding 73, Kirk, W6DEG	Aug. p. 49
A Two Dollar Phone Patch Writer, W6TRU	Aug. p. 64
A Military Career for the Ham Martin, G5ACY	Aug. p. 76
I Rode with the (excuse the expression) CB's, Sheldon, K4HKD	Aug. p. 78
Who Says You Can't Take It With You? Hannigan, WB6AGM	Nov. p. 76
Are You Really Ready for the Next Emergency? Baldwin, WØDDW	Nov. p. 88
Happiness is Being a Novice, Colker, WN3INL	Nov. p. 125
Using the First Ham Integrated Circuits, Hirschfeld, W6DNS	Dec. p. 6

SUPER SALE! HAMS, SCHOOLS, INDUSTRY! ONCE IN A LIFE TIME PRICES!

Order NOW from this ad. Wholesale prices.

VHF RECVR, Collins or Wilcox, 118-136 mHz, AM, 110 vac, makes first class net or monitor recvr, ex-FAA, was \$125.....\$60.
DIGITAL COUNTER, 4 row, good condition\$90.
SIGNAL GEN., Phillips PHP22, German copy of GR equipment, 10 KHz-50MHz \$50.
RECVR, RDE, fixed frequency, ac\$20.
DUAL TAPE RECORDER, 4 channel, remote control, with floor rack, excellent for station logging or background music, was \$495\$240.
NEW, SONEY TAPE DECK, stereo, was \$45\$25.
TRANSCEIVER, Lear LVTR-36, 118-136 mHz, 42 crystals, 12 volts, AM, 2E26 final, was \$99\$50.
SIGNAL GEN., 8-330 mHz, modulation, 115 v., General Radio type 804-C or Federal, was \$124\$85.
FREQ. METER, 100-500 mHz, .001% accuracy, excellent performer, excellent condition, heterodyne operation, 25 tubes plus crystal and original calibration book, 115/230 volts, civilian type LA-6 or military FR-6, was \$495\$350.
FREQ. METER, 10-100 mHz, similar to above instrument, rack mount, 115/230 volts with original calibration book and schematic, best quality made, was \$495\$250.
PULSE GENERATOR, Measurements Corp type 79A, required for all digital circuit work, 115 vac, was \$88\$49.
RECVR, ARR-15, 1.5-18.5 mHz, designed by Collins, frequencies to 1 kHz, converted, was \$65\$40.
FIELD STRENGTH RECVR, 15-150 mHz, ac or dc operation, high quality unit for FM or TV use, Measurements type 59, was \$299\$180.
TRANSCEIVER, APN-1, 420-260 mHz, dopplar radar, renew, was \$9\$3.50
TUNER, 300-1000 mHz, TN-18/APR-4, was \$39\$18.
RECVR, ham band only, 160-10 meters, RME 4350, was \$99\$70.
SCOPE, Dumont 340, dc to 3 msec. rise time, was \$84\$55.
MEMO SCOPE, Hughes type 104, with WB/4 plug-in preamplifier, high quality scope, workable, good condition except scope tube, was \$325\$150.
SPECTRUM ANALYZER, TS-148/UP, 8.4-9.97 GHz, compact, good shop instrument, good condition, was \$99\$45.
HUNTER 330S, light operated device, commercial quality, for counters, door alarms, or station antenna lights, was \$10\$5.
VERY LOW FREQUENCY RECVR, audio distortion analyzer, covers 30-16,000 Hz, may be shifted some to receive low freq. stations, General Radio type 736A, was \$269.....\$99., or HP type 300A, was \$175\$68.

VTVM Multimeter, Hewlett-Packard type 410A, 1-300 vac, 6 ranges, 1-1000 vdc, 7 ranges, 0.2 ohms to 500 meg, 7 ranges, read to 700 mHz, still an industry standard instrument, requires ac probe tip, was \$89\$45.
SIGNAL GEN., HP 608B, 10-410 mHz, calibrated output in db, internal modulation, may be pulsed, 115-230 volts, industry standard, was \$449\$300.
FREQ. METER, GR 720A, 100-3,000 mHz, heterodyne type, accuracy 0.1%, portable, good condition, was \$75\$65.
SIGNAL GEN., sweeper, X band, made by Kay, has freq. meter, attenuation, other controls, 110 vac, was \$59\$45.
SURVIVAL TRANSCEIVER, 121.5 & 243 mHz, waterproof, hand-held, VHF-UHF transmitter-recvr, RT159B/URC-4, was \$49\$20.
TRANSPONDER, radar, X band, RT-93A/APN-11, picture on p. 766 vol 7 MIT Rad. Lab gook. was \$25\$10.
TRANSMITTER AND POWER SUPPLY, 2-18 mHz, good condition, ART-13 (AM-CW), calibration book, commercial 115 volt power supply, was \$95\$50.
TRANSCEIVER, FM, Motorola FHTRU-1DL Handie-talkies, plug-in modules, can be modified and repaired, now on business band, working condition, schematic, was \$50\$20.
TRANSCEIVER, LF recvr, VHF transmitter, Bendix PATR-10A, 12 volts power, was \$25\$10.
THEODOLITE, Perkin-Elmer, azimuth alignment, electro type, topped by K&E transit, in original steel, shock mounted shipping case, good condition, 200 lbs., was \$495\$150.
RADAR CONSOLE, FAA type FA-52108, 22 inch PPI display, vertical roll around cabinet, requires only video and sync, inputs plus antenna position data, all standard, with very complete manual, truck only, was \$299\$75.
DUMMY LOAD, high quality, oil filled with sample diode, Bird type 81, 51 ohms, 50 watts, was \$24 SOLD OUT
GEIGER COUNTER, continuous duty monitor, Baird-Atomic model 410, was \$98\$30.
DIGITAL PRINTER, Colored TV Inc. type 103 A, desk sized, was \$45\$25.
FREQUENCY METER, 500-1000 mHz, built-in meter, made in England, excellent condition\$25.
ATTENUATOR, UHF type, 1-10 db\$7.
DECIMAL COUNTER UNIT, Model 705A, Berkeley, counts pulses to 10, has neon lighted numerals, zero to nine\$12.75
TELETYPE, Model 26, (\$10. crating chg.), was \$99\$75.
PLUG IN 250 CPS FILTER, 455 kc., Electronics Inc., EIC-7, complete unit, good \$3.50

This is the same equipment we have been selling regularly but due to a redirection of company policy, we are closing out many surplus items. Sorry but at these low prices our usual guarantee does not apply. Actual equipment photos available at 50 cents each. Sale ends Feb. 28, 1969.

THE R & C WILSON COMPANY

Box 393, Littleton, Colorado 80120 Phone: 303-798-2629

Radio _____ Confirming
 our QSO _____ 19__ at _____ T
 on _____ mhz. Ur am cw ssb rty
 RST _____ Watts _____ Ant. _____
 Xmtr. _____ Rcvr. _____
 Rmrx: PSE QSL TNX 73

NOW ANY PICTURE POST CARD
 IS A QSL CARD. ONLY \$2.00

K8SRA

UR CALL STAMP ONLY \$1.00
 3 LINE QTH STAMP \$3.00
 ALL 3 STAMPS ONLY \$5.50pp
 (Ohio Res. please add 4% tax)

John D. Kirke Co.
 17711 Lakewood Hts. Blvd.
 Cleveland, Ohio 44107

AMATEURS-C-B-COMMERCIAL USERS
 Indicates maximum dc current your
 transceiver/transmitter draws on peaks.
 Safeguard your equipment. Indicates
 quickly and easily faulty equipment.

MODEL 763
 READS BY INDUCTION \$5.25 PPD.

Hoyt BURTON-ROGERS Company
 44 Carleton Street, Cambridge, Mass. 02142

SPACE PROBLEMS SOLVED WITH
JOYSTICK
 VARIABLE FREQUENCY ANTENNA SYSTEMS
 With ATU's for 10-160 Meters Under \$50

SHORTWAVE GUIDE
 414 Newcastle Rd. Syracuse, NY 13219

FREE Catalog
 OF THE WORLD'S FINEST
 ELECTRONIC GOV'T
 SURPLUS BARGAINS

Now **BIGGER**
 And **BETTER**
 Than Ever!

MAIL COUPON NOW

NAME: _____
 ADDRESS: _____
 CITY: _____ STATE: _____ ZIP: _____

FAIR RADIO SALES
 Dept. 73 • Box 1105 • LIMA, OHIO 45802

Mobile Operation

The XYL Pleaser Mobile Mount
 Sheldon, K4HKD Feb. p. 85
 Installing a Transceiver in a Hired
 Car, Wagner, G3BID Apr. p. 66
 A Unique Transistorized Inverter
 Belcher, WA4JVE Aug. p. 12
 Going VHF—In the Mobile
 Brown, W9HDF Sept. p. 6
 VHF rf Noise Suppression
 Glazier, K6ZJV Oct. p. 44

News, amateur radio

Hamming—The Navy Way
 Steinberg, K6GKX Jan. p. 26
 Operations Deep Freeze—1957-1967
 Steinberg, K6GKX Mar. p. 38
 Are Phone Patches Legal?
 Sessions, K6MVH May p. 72
 Ships of Mercy, Steinberg, K6GKX June p. 68
 VHF Awards, Hall, K4LLF Sept. p. 43
 K2US: 1968 Ham Radio Expo
 Synder, WB2DLW/K3AFW Sept. p. 48

Power Supplies

A Regulated DC Voltage Divider
 Lamprecht, W5NPD Mar. p. 24
 Versatile Variable Power Supply
 Couch, W6SLP June p. 18
 A Transformerless Tranceiver Power
 Supply, Bell, W5NGX June p. 62
 A Unique Transistorized Inverter
 Belcher, WA4JVE Aug. p. 12

Propagation, Radio Wave

Line of Sight, Roberts, W9HOV Feb. p. 85
 Getting Your Higher Class License
 Part 1—Radio Wave Propagation
 Staff/73 Mar. p. 92
 Going VHF—In the Mobile
 Brown, W9HDF Sept. p. 6
 Starting Off on VHF, Irace, WA1GEK Sept. p. 32

Receivers and Converters

General

Receiver Front End Protection
 Jones, W6AJF Mar. p. 20
 ITV Got You Down? Cook, WA7CSK Apr. p. 46
 Use of Q-Multiplier to Increase
 Intelligibility of Received Voice
 Signals, Ives Apr. p. 74
 Basic High Frequency Receiving
 Converter, Cameron, W., WA4UZM Aug. p. 22
 Getting Your Higher Class License
 Part 5—Receivers Staff/73 Aug. p. 54
 A Collection of Thoughts on Receiver
 Design, Klinert, W6BIH Oct. p. 6
 The MO Receiver, Cleland, K5WYG Oct. p. 20
 A High Performance Receiver for
 Two Meters, Lawshe, W2HUX Oct. p. 30
 Neutralization! McCarthy, K6EAW Oct. p. 56
 Transistor Regenerative Detector
 Ashe, W1EZF Oct. p. 76
 Improving Frequency Stability in
 Older Receivers, Wilson, WGN1F Oct. p. 94
 Simplified Decibel Leveling
 Chapin, W2DUD Oct. p. 106
 FET Preamplifiers, Schultz, W2EEY/1 Oct. p. 112
 Crystal Filters, Clepper, W3RET Nov. p. 12
 A Novice FET Converter, K6DBQ Dec. p. 36

Low Frequency

Modifying The BC-1206, Olson, W6GXN June p. 14

HF

- High Quality Hybrid Receiver
Cousins, VE1TG Feb. p. 42
- Transceiving With an Outboard
Receiver, Lehrbaum, WA2APT Mar. p. 62
- The ARC-5 Transmitter Receiver
Klinert, WB6BIH June p. 10
- Use of the Wilcox F3 as a WWV
Receiver, Olson, W6GXN Mar. p. 62
- New Life for an Old Work-Horse
Zook, K9STH/5 June p. 40
- High Quality Hybrid—Postscripts
Goldstein, VE3GFN Aug. p. 72
- 3-Tube Superhet Short-Wave Receiver
Speer, W6ELJ Oct. p. 14
- The MO Receiver, Cleland, K5WYG Oct. p. 20

VHF

- Crystallize that FM Rig
Zook, K9STH/5 June p. 24
- Putting the RF-209/PRC on Two
Meter FM, Owings, KØAHD June p. 96
- Converting the ARC-1 Guard Channel for
Two Meters, Davey, W7CJB June p. 100
- Basic High Frequency Receiving
Converter, Cameron, WA4UZM Aug. p. 22
- Quick Converters, Schleicher, W9NLT Sept. p. 20
- Starting Off on VHF, Irace, WA1GEK Sept. p. 32
- Six Meter Transceiver, Bryan, W2AJW Sept. p. 62
- A High Performance Receiver for
Two Meters, Lawshe, W2HUX Oct. p. 30
- A Low-Noise FET Converter for
50 MHz, Morrison, WB6YVT Oct. p. 52

UHF

- 432 MHz Amplifiers, Jones, W6AJF Sept. p. 16
- 1296 Megacycles—1968, Ashby, K2TKN Sept. p. 42

RTTY

- RTTY in Holland and Belgium
The Selcal Jan. p. 64
- Malloch, WA8PCK & Lamb, K8ERV May p. 58
- Hybrid RTTY TU, Sherill, K6JFP June p. 104
- Rejuvenating Old RTTY Ribbons
Wright, W5AQN Sept. p. 67
- Using a SCR in a Teletype Series Wound
Motor, Suding, W8NSO Nov. p. 82


Semiconductors

- Diode Circuits Handbook
Franson, WA1CCH Jan. p. 1A
- IC Square-Wave Generator
Jimenez, WA4ZQO Jan. p. 6
- An Integrated Circuit Electronic
Counter, Jones, W1PLJ Feb. p. 6
- An Amateur Tries IC's
McCullagh, VE3DAN Feb. p. 16
- An Integrated-Circuit Audio Oscillator
and Amplifier, Estep, W7AKS July p. 34
- Transistor Regenerative Detector
Ashe, W1EZT Oct. p. 76
- FM'ing a VFO, Schliesser, WA6UFW Oct. p. 110
- FET Preamplifiers, Schultz, W2EEY/1 Oct. p. 112
- Troubleshooting Solid State Circuitry,
Jones, K3PBY Nov. p. 16
- The Thermistor, Klinert, WB6BIH Nov. p. 78
- The New Hi Voltage Transistors,
Nickel, K3VKC Nov. p. 84

Space Communications

- Project MOONRAY, NASTAR Apr. p. 60
- The VK3ATN Moonbounce Rhombic
Green, W2NSD/1 Sept. p. 44
- A Space Communications Odyssey,
Berman, K6BW Nov. p. 32
- Surprise in the Skies, Ashe, W1EZT Nov. p. 36

THE BEST 2 METER CONVERTER

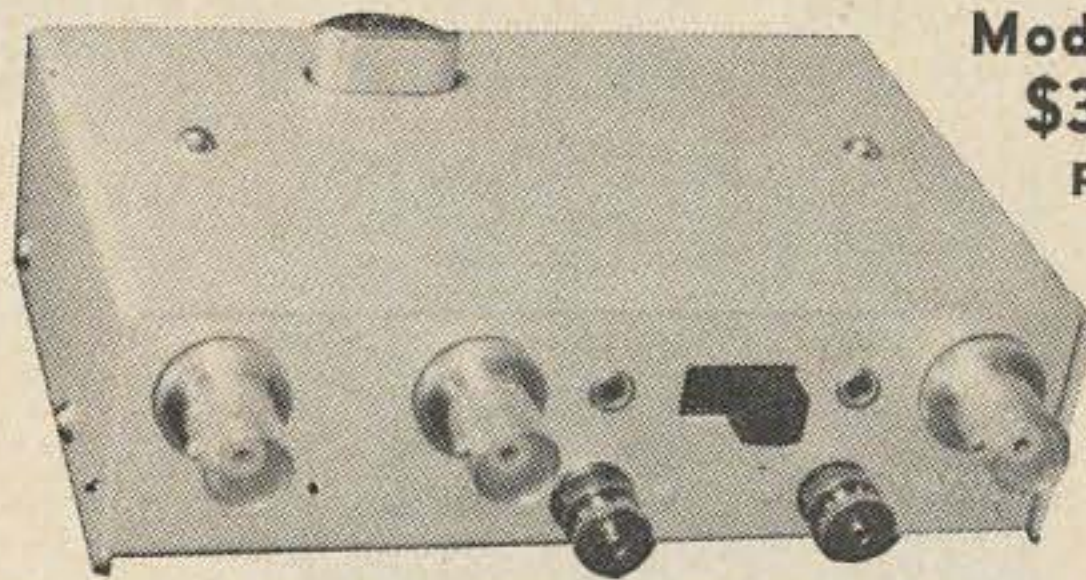

Model 407
\$34.95
ppd.

144-146 MHz in. 28-30 MHz out
or 146-148 MHz with a second crystal

A full description of this fantastic converter would fill this page, but you can take our word for it (or those of hundreds of satisfied users) that it's the best. The reason is simple—we use three RCA dual gate MOSFETs, one bipolar, and 3 diodes in the best circuit ever. Still not convinced? Then send for our free catalog and get the full description, plus photos and even the schematic.

Can't wait? Then send us a postal money order for \$34.95 and we'll rush the 407 out to you. NOTE: The Model 407 is also available in any frequency combination up to 450 MHz (some at higher prices) as listed in our catalog. New York City and State residents add local sales tax.

VANGUARD LABS

Dept. H, 196-23 Jamaica Ave., Hollis, N.Y. 11423



Gateway


Tower Co.

7530 BIG BEND
ST. LOUIS, MO. 63119
(314) 644-1500

ALUMINUM TOWERS

Send postcard for Literature

LEARN RADIO CODE

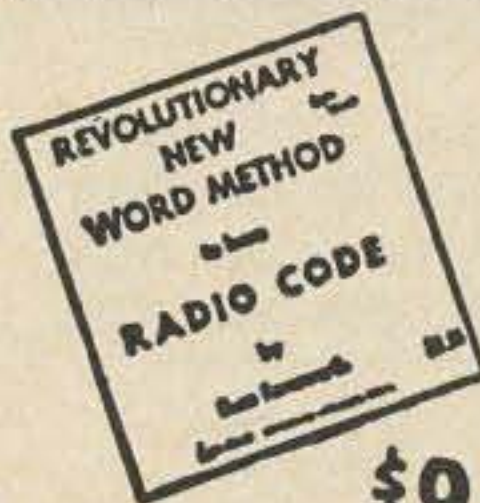

\$9.95

Album contains three 12" LP's 2½ hr. Instruction

THE EASY WAY!

- No Books To Read
- No Visual Gimmicks To Distract You
- Just Listen And Learn

Based on modern psychological techniques—This course will take you beyond 13 w.p.m. in LESS THAN HALF THE TIME!

Also available on magnetic tape. See your dealer now!

EPSILON RECORDS


206 East Front Street, Florence, Colorado

JOHN MESHNA JR.

19 ALLERTON ST. LYNN, MASS. 01904

COMPUTER GRADE CAPS

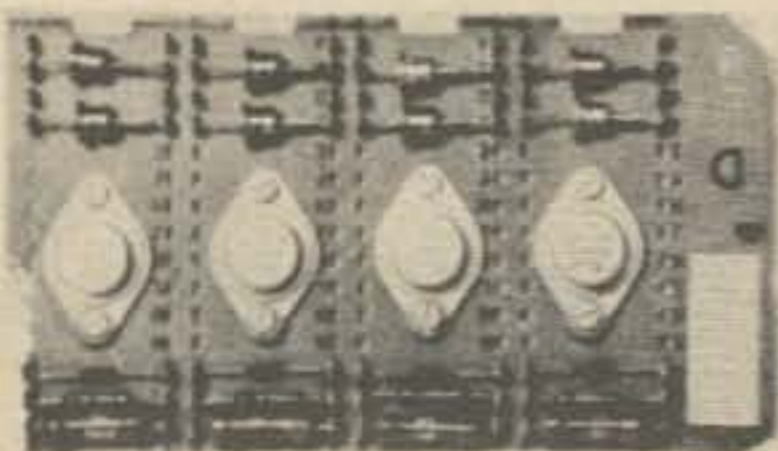4,000 mfd at 50 volt ...\$1.00 ea., 12 for \$10.00
6,500 mfd at 18 volt ...\$1.00 ea., 12 for \$10.00




60 WATT TRANSISTORS 80 VOLTS

From computer assemblies, board with 4 each power transistors 2N1137B, 60 watt, 80 volt PNP power \$1.25 per board



SUPER VALUE \$2.50

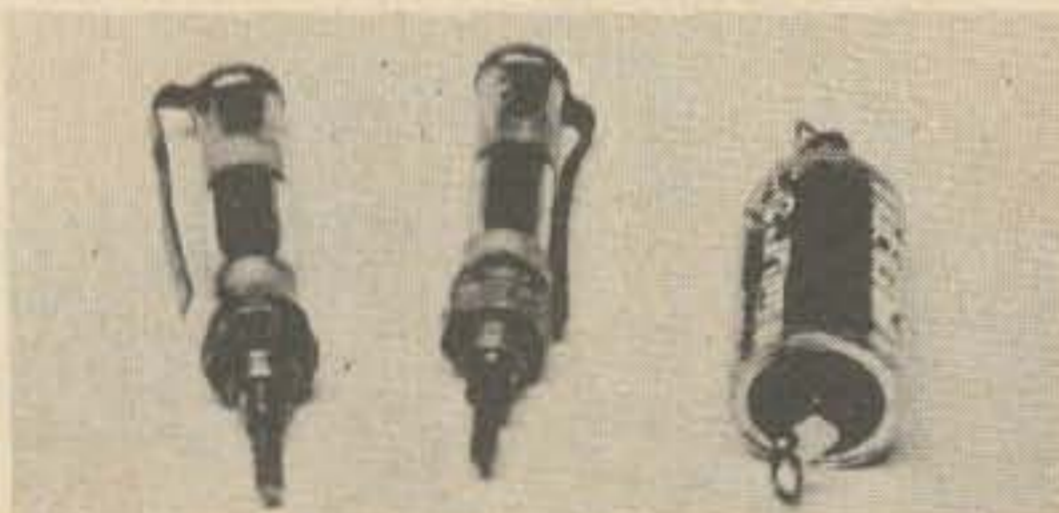Computer boards with 8 each 2N1137B power transistors and mounting hardware, also include on the board, 4 each 10 volt zeners, 4 silicon diodes 1 amp 800 volt PIV, computer grade cap 2000 mfd 65 volt Bourns trimpots, precision resistors, etc. Complete assembly like new Ship wgt. 3 lb. \$2.50



RF FILTER

From HAWK MISSILE termination contract. Good for 5 amps, 600 volt, 10 cycles to 500 mc, insertion loss 60 DB-plus, low pass pi-network type, excellent as feed-thru filter in converters, transmitters. Hermetically sealed inside are 2 toroidal chokes and 4 low induct. caps. #41102 \$1.00 each, 6 for \$5.00

PISTON CAPS

Corning glass, direct traverse type, min. Q at max. C—500 at 50MC. 500 volt breakdown. Capacitance range 1-8 uufd. Brand new military surplus 3 for \$1.00 or \$3.00 per doz.

10 amp TRIACS

SALE	PRV	100	200	300	400
	Sale	1.40	1.75	2.25	2.60

VARACTOR SIMILAR TO MA4060A

Good for 40 watts at 432 MC, ea. tested in circuit, w/diagram for 432 MC tripler. \$5.00 ea.

Station Setup and Control

- The RF Patch, Kelly, W6JTT Mar. p. 58
Methods of Transceiver CW Switching
Schultz, W1DCG Apr. p. 16
VHF Operation by Remote Control
Sessions, K6MVH Apr. p. 32
RF Controlled Switch, Jack, WA3AQS June p. 61
Three Black Boxes, Drumeller, W5EHC Dec. p. 82

TV, Slow Scan and Facsimile

- The Vidicon Minicamera, Gibson, W8TYY Apr. p. 6
Video Mixing Amplifiers, Walker, W8VCO, Apr. p. 24
APS-12 ATV Transmitter, O'Hara, W6ORG June p. 16
Project Facsimile Antarctic
Steinberg, K6GKX Oct. p. 28
Project Facsimile Antarctic . . . Part II,
Steinberg, K6GKX Nov. p. 86
Facsimile for the Radio Amateur,
Steinberg, K6GKX Dec. p. 84

Test Equipment

- IC Square-Wave Generator
Jimenez, WA4ZQO Jan. p. 6
Voltage-Doubler RF Probe
Marriner, W6BLZ Jan. p. 16
100 KHz Thin-Line Pulse Generator
Ashe, W2DXH Feb. p. 24
The Quartenna, Krause, WA6OBH Feb. p. 64
Tunnel Dipper on 160, Pleasant, W5MPX/5 Mar. p. 87
Low-Cost Conversion of Surplus
Oscilloscopes, Brown, W8JZI June p. 22
An Integrated-Circuit Audio Oscillator
and Amplifier, Estep, W7AKS July p. 34
"Q", "Q", Who Got "Q", Votipka, WB6IBS Oct. p. 82
The Gentrac, Lovelock, W6AJZ Nov. p. 58
Circular Modulation Monitor,
Winklepleck, WA9IGU Dec. p. 14
The Mini-Square, Klinert, WB6BIH Dec. p. 16
Add On FM Test Set, Zook, K9STH Dec. p. 18
The Elusive H Parameter,
Klinert, WB6BIH Dec. p. 20

Transmitters

General

- Line Noise in the Heath Monitor
Scope, Kashubosky, K8RAY Feb. p. 57
Transmitter Keying—with Transistors
Gabrielson, W6HEK Mar. p. 14
Tube Abuse in SSB Gear,
Hayward, W0PEM Mar. p. 61
Using 400 Hz Transformers
Littrell, W4VBH June p. 106
Built-in Microphone Preamplifier
Clipper, Schultz, W2EEY/1 Aug. p. 32
Getting Your Higher Class License,
Pt. 6—Transmitters, Staff/73 Sept. p. 74
New Life for an Old Circuit
Thorpe, Darrell Oct. p. 40
Neutralization! McCarthy, K6EAW Oct. p. 56
Computer Card Transmitter,
Allen, K1EUI Nov. p. 6
7 MHz Transistor Transmitter,
Krutz, WA6JND Nov. p. 50

HF

- The Wolverine, Marriner, W6BLZ Jan. p. 66
Mini-Mitter: The Ultimate in
Miniatures! Pyle, W7OE Mar. p. 18
SB-33 Note, Agrelus, K6SHA June p. 39
A Terminated Grid Linear Amplifier
Hartley, W1DIS Aug. p. 6
A Simple Method of DSB Conversion
McGee, K5LLI Aug. p. 18
A 4E27 Grounded Grid Linear RF
Amplifier, Krawetz, WA6WUI Aug. p. 42
Zero Temperature Coefficient VFO,
Lorona, W6WQC Dec. p. 24
75 Meter DSB Rig, Joffe, W3KBM Dec. p. 28
30 Watt Transistor Transmitter,
Gould, W5PAG Dec. p. 46

VHF

- RF Insertion Amplifier for 2 Meters
Hoisington, K1CLL Jan. p. 20
- Modifying The Clegg 99'er
Porcaro, WB2JOS June p. 12
- Starting Off on VHF, Trace, WA1GEK Sept. p. 32
- 6 Meter Exciter, Robbins, W1KNI Sept. p. 52
- Two Sidebands From The Tower
Campbell, W4KAE Sept. p. 70
- Six Meter Transceiver, Bryan, W2AJW Sept. p. 62
- New Life for an Old Circuit
Thorpe, Darrell Oct. p. 40


UHF

- APS-13 ATV Transmitter, O'Hara W6ORG June p. 16
- Modification of the TRA-19 Amplifier Cavity
to 432 MHz, Crowell, K6RIL June p. 44
- 1296 Megacycles—1968, Ashby, K2TKN Sept. p. 42

Writing

- Hamwriting, Sessions, K6MVH Aug. p. 36
- TABLE OF ELECTRONIC SYMBOLS
FOR 73 CONTRIBUTORS Sept. p. 94

LESS THAN \$2.00 PER STAGE

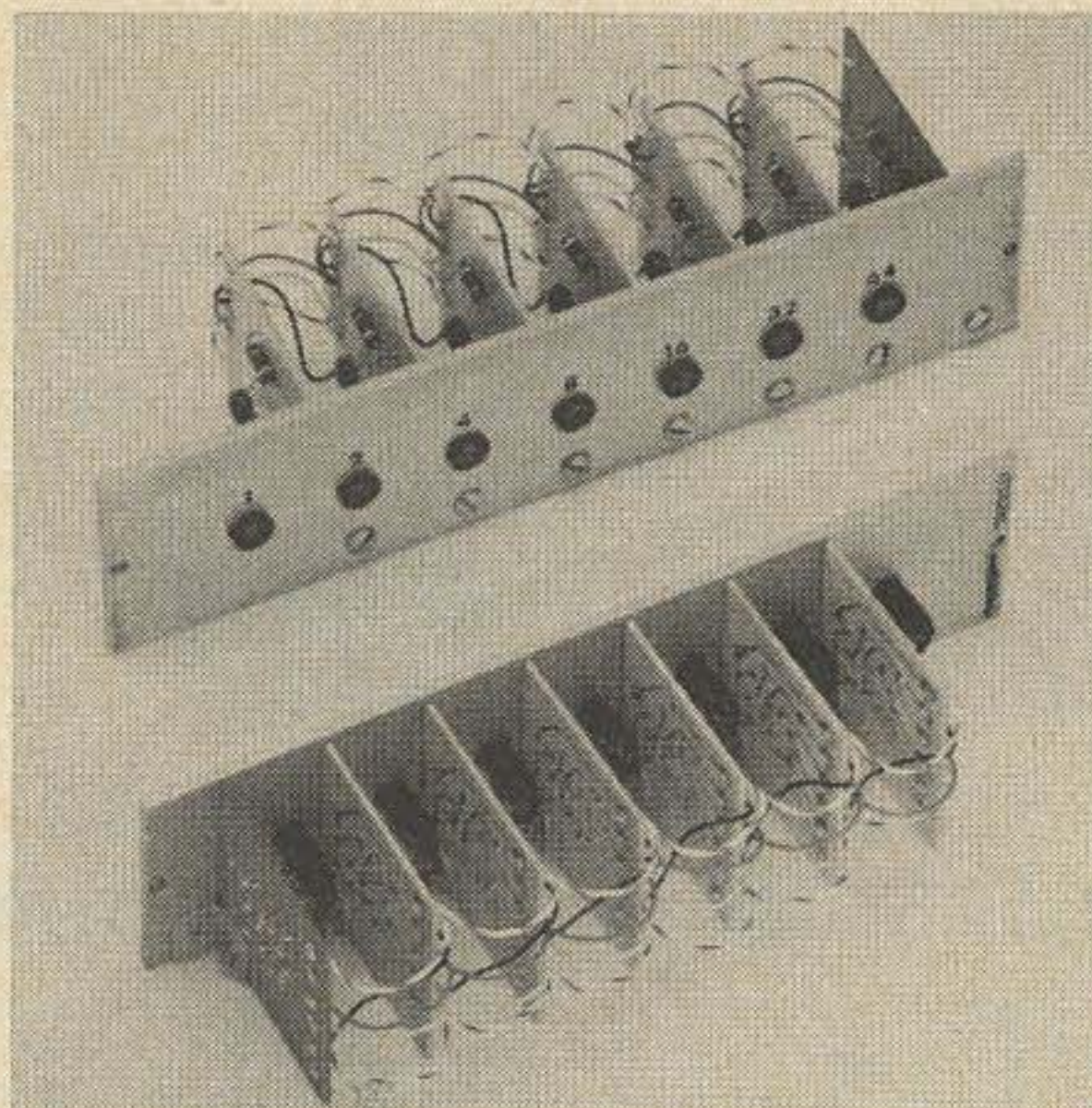

Low Cost Integrated Circuit Counter

Has many uses such as frequency counter, electronic stop watch, frequency meter, event counter, etc. This unit is a binary counter, the first light reads -1- each lite (stage) you add doubles the count.

Example:

No. of stages	Lite no.	Count
1	1	1
2	2	3
3	4	7
5	16	31
10	512	1023
15	16,384	32,767

No limit to the stages you can add. The total count is twice the value of the highest numbered light minus -1-. Each kit contains one complete stage with instructions for assembly in minutes.

Diagrams for power supplies included. Printed circuit board measures 2" square*

Kit for stages

\$2.49 ea.2 to 9 — \$2.29 ea.10 or more \$1.99 ea.
mechanical trigger or Schmit (electrical) trigger.
Photo shows sample mounting of 7 stages.
Additional information upon request.

COPPER P.C. BOARDS

2 x 2	10¢ ea	12/\$ 1.00
3 x 6	25¢ ea	10/\$ 2.25
4 x 6	35¢ ea	10/\$ 3.25
12 x 12	\$1.95 ea	10/\$17.00

FERRIC CHLORIDE etching solution 75¢ Pt.

NEW STRAIGHT FROM FACTORY

Fairchild I.C.'S

- UL914 with 30 Projects Diagrams \$1.00 ea. 10/\$7.95
- UL923 J.K. Flip Flop with spec sheet \$1.75 ea. 10/\$14.95

CRYSTAL OSCILLATOR KITS

using I. C. UL 914 Stable, harmonic-rich output osc. range 100 KC to 10 MC - Kit includes Fairchild I.C. UL 914, crystal sockets, resistors, capacitor, & PRINTED CIRCUIT BOARD, with instructions for assembly
\$2.00 per Kit.



Visit our 2nd Store
247 So. Meridian, Indianapolis, Ind.



R & R ELECTRONICS
1953 S. YELLOWSPRINGS ST.
SPRINGFIELD, OHIO
DEPT. 7F

\$2.00 minimum order FOB Springfield, Ohio. COD order 25% deposit. Please add sufficient postage, we refund all unused amount. Ohio customers add 4% sales tax.

radio amateur
callbook

Radio Amateur Emblems engraved with your call letters.



Charm

- Gold
- Rhodium

call letters
\$5.00 Ea.



Tie Bar

- Gold
- Rhodium

call letters
\$5.00 Ea.



All illustrations are actual size.

Lapel Pin

- Gold
- Rhodium

call letters
\$5.00 Ea.

Two or more emblems at the same time \$4.00 each. Illinois residents add 5% tax.

Amt. enclosed \$ _____


Name _____

Address _____

City & State _____ Zip _____

Rush Order To: RADIO AMATEUR CALLBOOK, Inc.
4844 Fullerton Ave., Chicago, Illinois 60639

THE BEST 6 METER CONVERTER

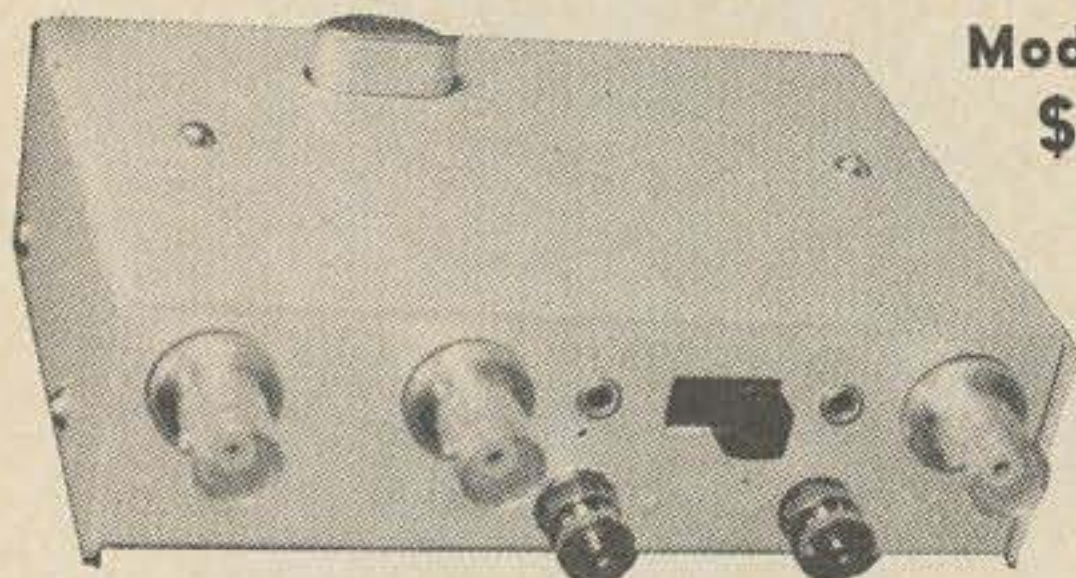

Model 407
\$34.95
ppd.

**50-52 MHz in. 28-30 MHz out
or 52-54 MHz with a second crystal**

A full description of this fantastic converter would fill this page, but you can take our word for it (or those of hundreds of satisfied users) that it's the best. The reason is simple—we use three RCA dual gate MOSFETs, one bipolar, and 3 diodes in the best circuit ever. Still not convinced? Then send for our free catalog and get the full description, plus photos and even the schematic.

Can't wait? Then send us a postal money order for \$34.95 and we'll rush the 407 out to you. NOTE: The Model 407 is also available in any frequency combination up to 450 MHz (some at higher prices) as listed in our catalog. New York City and State residents add local sales tax.

VANGUARD LABS

Dept. H, 196-23 Jamaica Ave., Hollis, N.Y. 11423

CUSTOM TRANSFORMER DESIGN & MANUFACTURE

Write today for a free quotation on any transformer, choke, or saturable reactor. Each unit will be designed and manufactured to your exact specifications. Standard E-I and tape wound "C" cores are available. Quantities from single units to production runs may be accommodated.

PETER W. DAHL CO.
5325 Annette Ave., El Paso, Texas 79924
Tele: 915-751-4856

CONVENTION 69 ARRL NATIONAL

Des Moines, Iowa
June 20, 21, 22
P.O. Box 1051, 50311

ARNOLD'S ENGRAVING Personalized

ELECTRIC
**ON-THE-AIR
SIGN**
WITH CALL



Works on
110 VAC
\$12.95



Metaltext Lapel Bar - \$1.50 Metaltext Tie Clip - \$2.25

ARNOLD'S ENGRAVING

2041 Linden St.

Ridgewood, N.Y. 11227

Propagation Chart

December 1968

ISSUED SEPT. 1

J. H. Nelson

EASTERN UNITED STATES TO:

	GMT: 00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	14	7	7	7	7	7	7	14	21	21A	21
ARGENTINA	14	14	14	7	7	7A	14A	21A	28	28	28	21
AUSTRALIA	21	14	7B	7B	7	7	7B	14B	14	14A	21A	21A
CANAL ZONE	21	14	7	7	7	7	14A	21A	28	28	28	28
ENGLAND	7	7	7	7	7	7A	14A	21A	28	21	14	7
HAWAII	21	14	7	7	7	7	7	7B	14A	28	28	28
INDIA	7	7	7B	7B	7B	7B	14	21	14	7B	7	7
JAPAN	14	14	7B	7B	7	7	7	7	7B	7B	7B	14A
MEXICO	14	14	7	7	7	7	14	21A	28	28	21A	21A
PHILIPPINES	14	14	7B	7B	7B	7B	7B	14B	14	14	7B	14
PUERTO RICO	14	7	7	7	7	7	14	21A	21A	21	21	21
SOUTH AFRICA	14	7	7	7	7B	14	21A	28	28	28	21A	21
U. S. S. R.	7	7	7	7	7	7B	14	21A	21	14	7B	7
WEST COAST	21	14	7A	7	7	7	7	14	21A	28	28	28

CENTRAL UNITED STATES TO:

ALASKA	21	14	7	7	7	7	7	7	14	21	21A	21A
ARGENTINA	21	14	14	7	7	7	14	21A	28	28	28	21
AUSTRALIA	28	21	14	7B	7	7	7	14B	14	14A	21A	21A
CANAL ZONE	21	14	14	7	7	7	14	21A	28	28	28	28
ENGLAND	7	7	7	7	7	7	14	21	21A	21	14	7B
HAWAII	28	21	14	7	7	7	7	7	14	21A	28	28
INDIA	7A	7A	7B	7B	7B	7B	7B	14	14B	7B	7B	7
JAPAN	21	14	7B	7B	7	7	7	7	7	7B	14	21
MEXICO	14	14	7	7	7	7	7	14	21A	21A	21	21
PHILIPPINES	21A	14	7B	7B	7B	7B	7	7	14	14	7B	14A
PUERTO RICO	21	14	7	7	7	7	14	21A	28	28	28	21A
SOUTH AFRICA	14	14	7	7B	7B	7B	14	21A	28	28	21A	21
U. S. S. R.	7	7	7	7	7	7	7B	14	14	14	7B	7B

WESTERN UNITED STATES TO:

ALASKA	21	14	7	7	7	7	7	3A	14	21	21	21A
ARGENTINA	21	14	14	7	7	7	7B	14A	21A	28	28	21
AUSTRALIA	28	28	21	14	14	7	7	7	14	14A	21	21
CANAL ZONE	21	14	14	7	7	7	7	14A	21A	28	28	28
ENGLAND	7B	7	7	7	7	7B	7B	7B	14A	21	14	7B
HAWAII	28	28	21	14	14	7	7	7	14	21A	28	28
INDIA	14	14A	7B	7B	7B	7B	7B	7	14B	7B	7B	7B
JAPAN	28	21A	14	7B	7	7	7	7	7	7B	14	21A
MEXICO	21A	14	7	7	7	7	7	14	21A	28	28	28
PHILIPPINES	21A	21A	14	7B	7B	7	7	7	14	14	7B	14A
PUERTO RICO	21A	14	7	7	7	7	7	14A	21A	28	28	28
SOUTH AFRICA	21B	14	7	7B	7B	7B	7B	14	21A	28	21A	21
U. S. S. R.	7B	7	7	7	7	7B	7B	7B	14	14B	7B	7B
EAST COAST	21	14	7A	7	7	7	7	14	21A	28	28	28

A - Next higher frequency may be useful this period

B - Difficult circuit this period

Good: 1-5, 11-14, 16-21, 23, 24, 26-29, 31

Fair: 6, 8-10, 15, 25, 30

Poor: 7, 22

Caveat Emptor?

- ★ Price—\$2 per 25 words for non-commercial ads; \$10 per 25 words for business ventures. No display ads or agency discount. Include your check with order.
- ★ Deadline for ads is the 1st of the month two months prior to publication. For example: January 1st is the deadline for the March issue which will be mailed on the 10th of February.
- ★ Type copy. Phrase and punctuate exactly as you wish it to appear. No all-capital ads.
- ★ We will be the judge of suitability of ads. Our responsibility for errors extends only to printing a correct ad in a later issue.
- ★ For \$1 extra we can maintain a reply box for you.
- ★ We cannot check into each advertiser, so Caveat Emptor . . .

TELETYPE MOD. 14 reperforator with automatic tape take up rewriter new, unused, \$69.95 . . . 4-400's \$14.95 . . . transformers: Plate 5KV-1.6ADC \$59.95 . . . Modulator 811A's \$35 . . . Filament 12.6DCT-10A \$4.95. Ideal for transistor supply, battery charger . . . catalog 10¢. Fertik's, 5249A "D", Phila., Pa. 19120.

RF MULTIMETER measures ten millivolts to three volts rms and VSWR down to 1.05:1 as high as 2GHz. RADEVCO, Box 8450, Baltimore, Maryland, 21234.

VIBROPLEX or semiautomatic key wanted. Write Box 691, Savannah, Georgia, 31402.

MERRY XMAS AND HAPPY NEW YEAR from WØCVU. See you at Des Moines, Iowa. June 20-22, ARRL 1969 National Convention.

CHRISTIAN HAM FELLOWSHIP being organized for Christian fellowship and gospel tract work among licensed amateurs. Christian Ham Callbook for \$1 donation. For details write Christian Ham Fellowship, 5857 Lakeshore Dr., Holland, Mich. 49423.

WANTED: GONSET #3269, 100KC calibrator, or circuit diagram, used in G-76. Swap: Ranger II and 6 Meter SSB gear for G-76 or Gonset 2 meter gear. J. Gysan, 53 Lothrop St., Beverly, Mass. 01915.

ON AIR NOW: Apache, SB10 SSB, SWR, All Heath, all in like-new condition. \$159.50 FOB. Newton, Mass. K1ZYG.

WANTED: McElroy XTR-442-C automatic tape keyer and tape perforator. John R. Hinegardner WØBFB, Mitchelville, Iowa. 50169. Phone 515-967-2898.

AMATEUR and CLOSED-CIRCUIT TV Technical Literature, Plans, Kits

5 TUBE VIDICON TV CAMERA CONSTRUCTION MANUAL-16 page booklet gives complete details for building, testing and operating your own "live" TV camera. Simplest tube type TV camera circuit known! Designed to use maximum number of readily-available components normally found in amateur junk boxes. ONLY \$3.00**

TRANSISTOR VIDICON TV CAMERA CONSTRUCTION MANUAL-31 page manual gives step-by-step instructions for building a high quality fully transistorized camera. Thousands of hours of lab and field testing have gone into this circuit thus making it the perfect choice for the serious constructor. Order stock #XT-VCM Only \$5.00**

TELEVERTER FLYING SPOT SCANNER TV CAMERA CONSTRUCTION MANUAL. This 22 page step-by-step manual contains complete details for building an unusual flying spot scanner type camera suitable for televising 35mm slides. The unit is very easy and economical to build since it makes use of a standard TV set to provide the scanning circuitry. ABSOLUTELY NO WIRING MODIFICATIONS are required on the TV set. Requires only 4 tubes plus photomultiplier. Order Stock #TV-1 \$2.50

MONOSCOPE CAMERA CONSTRUCTION PLANS-Ideal camera for testing and servicing work where a "standard" fixed video signal is required. No lens system, external lighting or test charts are required since the pattern is built inside of the tube. Straightforward 4 tube plus monoscope circuitry. Order Stock #LPS-1 Only 50¢

ONE WATT 432 Mhz TRANSMITTER-MODULATOR PLANS-Complete details for building a simple 5 tube ham TV transmitting station. Stock #LPS-2 Only 50¢

432 Mhz TV CONVERTER PLANS-uses 6CW4 RF amp, 6AF4A osc and 6BQ7A i.f. amp. No difficult plumbing required. Easy to tune up. Order Stock #LPS-5 Only 50¢

420-450 Mhz TV ANTENNA CONSTRUCTION PLANS-12 ele. Yagi. #LPS-3 25¢

CAMERA DEFLECTION COILS-Technical data sheet explaining phasing and testing of vidicon and image orthicon yokes. Ideal for do-it-yourself yoke builders. Prevent costly damage to camera tubes by using these simple techniques. #LPS-6 25¢

NEGATIVE-POSITIVE VIDEO INVERTER CONSTRUCTION PLANS-Complete details for building an adaptor that can be inserted between the output of any video TV camera and the video monitor to reverse the polarity of the video signal but not the sync-blanking pulses. Perfect for observing negatives, etc. Stock #LPS-8 \$1.00

BASIC LENS THEORY FOR APPLIED TV-A short course in basic lens theory designed to assist the user in the selection and operation of lenses for TV cameras. Especially valuable to those designing their camera from available parts. LPS-4 50¢

GLOSSARY OF APPLIED TV TERMS-120 different TV terms defined. Very valuable for those just getting started in the Applied TV field. Stock #LPS-7 Only 50¢

SET OF TEST PATTERNS-6 individually printed patterns. Stock #TCS-6 \$2.25

STATION I.D. ILLUSTRATIONS-Set of 12. High contrast line drawings. #IDS-12 \$3.50


WARNING: THESE PREMISES ARE PROTECTED BY CLOSED-CIRCUIT TV-8½" x 11" warning signs. Large black letters on colored card stock. Stock #SS-1 3 for \$1.00

**Full price of these manuals refundable with later kit purchase.


WRITE for your FREE catalog fully describing our line of TV camera kits and parts.

13th & Broadway North, **ATV RESEARCH** Dakota City, Nebr. 68731

VIBROPLEX

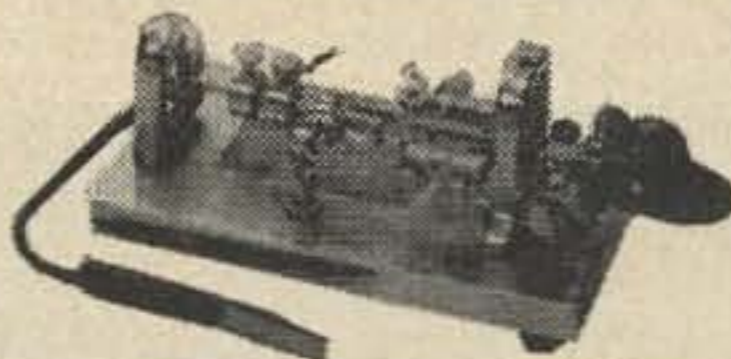

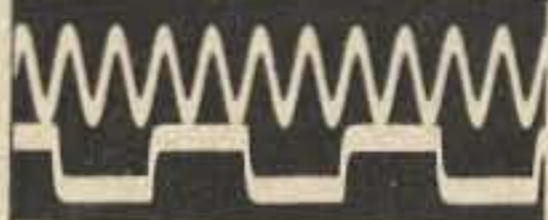ENJOY EASY, RESTFUL KEYING
\$21.95 to \$43.95
THE VIBROPLEX CO., INC.
833 Broadway,
N. Y. 3, N. Y.



25KC MARKS!

Locate New Sub-Bands

Accurately! Four wires connect IC-3 Divider to your 100KC calibrator to give 25KC marks. Circuit board 1¼" x 1½". Specify supply voltage — 3-300, 10 ma. (Lowest is best.) Send for IC-3, \$5.95, + 30¢ postage.

PAXITRONIX INC. BOX 1038 (B) Boulder, Colo. 80302

CRYSTALS—low frequency types available at \$2.50 each postpaid USA in hermetically sealed HC6 or HC13 metal holders with 2½ inch wire leads. Frequency in KC: 2.000, 4.0457, 6.4000, 16.000, 32.000, 75.000, 96.000, 100.000, 128.000, 218.000. Form page brochure available for stamp. **QUAKER ELECTRONICS, HUNLOCK CREEK, PA. 18621**

WE PAY CASH FOR TUBES

Lewispaull Electronics, Inc.
303 West Crescent Avenue
Allandale, New Jersey 07401

**LARGEST SELECTION in United States
AT LOWEST PRICES—48 hr. delivery**

**JAN
CRYSTALS**

Thousands of frequencies in stock. Types include HC6/U, HC18/U, FT-241, FT-243, FT-171, etc. SEND 10¢ for catalog with oscillator circuits. Refunded on first order. 2400B Crystal Dr., Ft. Myers, Fla. 33901

ELDICO SSB Adapter SBA-1 with book, converts any receiver with 455 kc IF to SSB; select either upper or lower side band: in neat cabinet **\$127.50**

Silie. Rect. 8000 PIV 400 ma. Pair \$5.30
R-23/ARC-5 Command revr 190-550 kc. Shpg. wt. 9# .. 14.95
A.R.C. 12 #22 Command revr 540-1600 kc. 9# 17.95
LM-14 freq. meter, .01% 125 kc-20 mc. 15# 57.50
TS-323/UR freq. meter 20-480 mc. .001% 169.50
TS-175 Freq. Meter. 85-1000 Mc. .04% \$125.00
CLOSING OUT Radio Receivers 38-4000 mc at **CRAZY LOW PRICES!** Ask for APR-4Y/CV-253 sheet.

R-392; Compact version of R-390. Tubes work on 24v 3A. Same digit tuning. W/pwr sply & book 525.00

WANTED: GOOD LAB TEST EQUIPT & MIL COMMUNIC.
WE PROBABLY HAVE THE BEST INVENTORY OF GOOD LAB TEST EQUIPMENT IN THE COUNTRY. BUT PLEASE DO NOT ASK FOR CATALOG! ASK FOR SPECIFIC ITEMS OR KINDS OF ITEMS YOU NEED! WE ALSO BUY! WHAT DO YOU HAVE?

R. E. GOODHEART CO. INC.

Box 1220-GC, Beverly Hills, Calif. 90213
Phones: Area 213, office 272-5707, messages 275-5342

BUSINESS OPPORTUNITY

Young man wanted to learn management of surplus electronics firm in New York-New Jersey area. Small investment or none. Participate in profits and ownership. Equipment and know-how supplied, all that is needed is a good ham background and an earnest desire to learn and work. Call 201-824-1244.

MOTOROLA FM EQUIPMENT SCHEMATIC DIGEST

91 pages (11 1/2" x 17") of schematics, crystal information, alignment instructions, service hints and specialized information. \$3.95 post paid.

TWO-WAY RADIO ENGINEERS, INC.

1100 Tremont Street
Boston, Massachusetts 02120

NCX-200, USED ONLY FIELD DAY, \$300, in original box. Will include heavy home built supply free. FOB. WAØNDV, 611 No. Hartup, McPherson, Kansas 67460.

CRYSTALS—Low frequency types. Available at \$2.50 each postpaid USA in hermetically sealed HC-6 or HC-13 metal holders with 2-2 1/2" wire leads. Frequency in kilocycles. 2.000 4.0457 6.400 16.000 32.000 75.000 96.000 100.000 128.000 183.000 218.000. 4-page brochure available for stamp. Quaker Electronics, Hunlock Creek, Pa. 18621.

DISCOUNT PRICES. All equipment listed is new, factory sealed cartons, full manufacturers warranty. Our policy: new equipment at low prices. Swan SW-500C \$468, SW-350C \$378, Swan 14-117 AC-DC P/S \$115, Hygain TH6DXX (Reg. \$159) \$135, TH3MK3 (Reg. \$125) \$112, CDR Ham-M rotator with indicator \$99.95, Tri-ex W-51 self supporting crank up tower (Reg. \$362) \$299.95 pre-paid, Mosley TA-36 (Reg. \$153) \$137, TA-33 (Reg. \$121) \$109, Hammarlund HQ-180A (Reg. \$480) \$432. Many factories prohibit discount advertising; write or call for discount price catalog on brands not listed in this ad. Time payments available. Bryan Edwards Electronics, 1314-19th St., Lubbock, Texas. 806-762-8759.

WANTED: Magazines, VHRer & ATV. K6KTP, Berry St., Lemon Grove, Calif. 92045.

HQ100 WITH SPEAKER and xtal BFO very good at \$110; DX40 oldie but goodie at \$40; Knight V44 \$15. N. Dowling, 733 Mohawk, Lynchburg, Va. 24502.

HQ-140X, VALIANT I, B&W51SB. Good condition. With manuals. \$235.00. Shipping collect. John Rains, 3200 Long Blvd., Nashville, Tenn 37203.

WANTED: Must have manual and/or instruction book for Heathkit DK-40 XMTR, will pay cost. Philip Napora, 474 Tonawanda St., Buffalo, N.Y. 14207.

NEGATIVES MADE for use with photoresist P.C. boards. As described in Aug. 73. 4x5 in. \$2.00. D. Goodman, Bx 94, Catheys Valley, Calif. 95306.

FOR SALE: Motorola FMTR 80D, 52.525 Mc with AC supply, accessories, no speaker. \$95. FOB. C. G. Reinsel W3WUA. Box 25, Bigler, Pa. 16825.

COMMUNICATIONS TECHNICIAN position desired, 16 years experience, first class phone and advanced class amateur. Family, willing to relocate. Write for resume. 73. Box 1168, Peterborough, N.H. 03458.

SELLING MY old radio books, magazines, catalogs, and parts. Send stamped, addressed envelop for price list. W6CID, Elmer A. Piercy, Box 666, Victorville, Calif. 92392.

SWAN 250 6 METER Transceiver with power supply, \$250. Vanguard TV camera, \$175. Lafayette HA-6, \$65. P. Franson WA7KRE, 7312 E. Oak St., Scottsdale, Arizona 85257. 602-947-6052.

NEEDED: Electronic maintenance and operation men for color TV station control room work. First class ticket required. Salary range, depending on experience, \$600-\$700 a month. Call collect 313-239-6611 or write Chief Engineer, WJRT-TV, Flint, Mich. 48503.

AMATEUR RADIO CERTIFICATE: Display impressive 8 1/2" x 11" personally endorsed certificate in your shack. Send \$1.00 to Amateur Radio Certificate, Box 244, Miami (Kendall Br.) Fla. 33156.

WRL'S USED GEAR has trial—terms—guarantee!
 900A Sidewinder—\$219.95; Galaxy 5—\$289.95;
 Galaxy 300—\$159.95; HW22—\$89.95; HT40—\$49.95;
 HX500—\$289.95; 51J3—\$449.00; 75A1—\$169.95; NC155
 —\$119.95; NC190—\$139.95; SB300—\$249.95; RME6900
 —\$149.95; and hundreds more. Free Blue-Book list.
 Write WRL, Box 919, Council Bluffs, Iowa 51501.

DRAKE 2-A FOR SALE, \$100. Want SK-506 chimney and APX-6 in any condition. LA35G1W4, K. Midtseter, 1490 NW 58 Terrace, Ft. Lauderdale, Fla. 33313.

FOR SALE: Yaesu FTDX 400—\$325. Heath HR 20—\$70. SB 175—\$50. With all manuals. WB4APZ, 1900 8th Ave., Immokalee, Fla. 33934. (813-OL7-3288).

NATIONAL 200, AC-200. Absolutely mint condition. In original cartons. \$320 or best offer. Terry Taylor, 1459 Jaywood, Creve Coeur, Mo. 63141.

SALE: Comdel Speech Processor (CSP-11) excellent condition, \$75 PPD. WB6YVW, 1755 N. Wilcox, Hollywood, Ca. 90028.

THE WHEATON COMMUNITY RADIO AMATEURS (WCRA) will hold the 7th annual Mid-Winter Swap and Shop Sunday, February 16, 1969 at the DuPage Count Fair Grounds, Wheaton, Ill. Hours—9:00 a.m. to 5:00 p.m. \$1.00 donation at the door. Refreshments and unlimited parking. Free coffee and doughnuts 9:00-10:00 a.m. Hams, CBers, electronic hobbyists, friends and commercial exhibitors are cordially invited. Contact Bill Lester, WA9FGP, Box 1, Lombard, Ill. 60148 for information.

WANTED: Teletype equipment & parts. Also R-390A, U-R, R-220, etc. Cash or trade for new amateur equipment. All-tronics-Howard Co., Box 19, Boston, Mass. 02101. (Tel. 617-742-0048).

MICRO-MICRO-TO-KEYER: Perfect code from one cubic inch, microcircuit digital electronic keyer module designed for mounting inside any transmitter. Speed range 4-40 WPM. Grid block keying only allows price of \$19.95. Includes mounting hardware. Unconditionally guaranteed. Micro-Tech Labs. PO Box 884 (I.A.B.), Miami, Fla. 33148.

ESTATE LIQUIDATION: Telrex combination beams 10M-518 over 15M-525 over 20M-505. Self supporting tower 50 ft. and H.D. rotator cost over \$1000. Asking price \$200 and you take down. Mint condition. Arthur W. Lee, Rt. #1, Box 23A, North Monmouth, Maine 04265; Tel. 207-933-2869.

ESTATE LIQUIDATION: Collins 75A4 receiver serial 3316 and matching speaker two filters F455-J-08 and F445-J-31; Collins KWS-1 SSB-AM transmitter serial 953. New final tubes, mint condition. \$650 for both. Arthur W. Lee, Rt. #1, Box 23A, North Monmouth, Maine 04265; Tel. 207-933-2869.

SELL: COLLINS KWS1-1721 \$795, 75A4-4325 \$450, both \$1150, prefer local sale, like new, ship cod original packing. Barnett, 1310 Navajo, Florissant, Mo. 63033.

"NORTHERN CALIFORNIA HAMS." Best deals—new and reconditioned equipment. Write, call or stop for free estimate. The Wireless Shop, 1305 Tennessee, Vallejo, Calif. 707-643-2797.

WANTED: Back issues of 73 Magazine, November 1960 through March 1961. C. W. Janes K2KS, 2 Windsor Gate, Upper Saddle River, N.J.

GATEWAY ELECTRONICS

6150 Delmar Blvd., St. Louis, Mo. 63112

Facsimile Machine—complete with simple instructions for auto-start and auto-phase. Can be operated back to back or via radio. Machines in excellent condition and in working order when removed from service. 115 Volt AC 60 cycle. Shipping wt. 25 lbs.\$ 19.50

Automatic Ice Maker—for refrigerator—new with instructions and water valve ..\$ 14.95

Sealed Mercury Wetted Polar Relay (direct replacement for model 255) No adjustments required\$ 4.95

40-0-40 uA Weston Meter\$ 2.95


7200 VCT@1A Transformer 110/220 volt primary 60 cycle. Shipping wt. 110 lbs. \$ 25.00

Jennings Vacuum Variable (UCS-300) with motor drive 10-300pf new\$ 35.00

X-Y Plotter — Pace Electronic Associates Inc. Variplotter\$395.00

Minimum order \$5.00. Sorry, no catalog at this time. Write for specific items. Watch for our future ads in 73. Stop in and see us when you're in St. Louis.

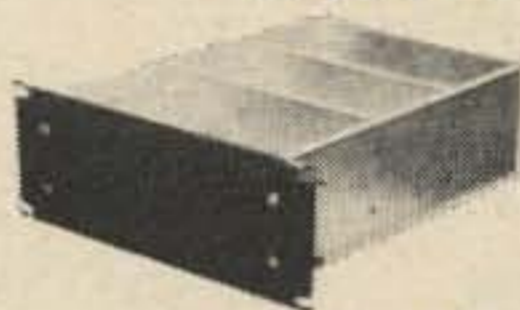**EASY CONSTRUCTION
MEANS
UNIT CHASSIS
WRITE
DEVICES**



BOX 136, BRONX, N.Y. 10463

CQ de W2KUU

All tubes bought • Electronic items wanted
Topping all offers

TED DAMES CO.

308 Hickory St., Arlington, N.J. 07032

ARC-1 Transceiver 100-156 Mc, 25 Watts AM, with tubes, schematic, conversion info for 2-meters. Used, good. 50 lbs. \$20.00

ARC-1 only, less tubes, \$12.00

BC-221-AK with AC Power, Calib. Book & Xtal. \$95.00

TS-174, 20-250 Mc. Freq. Meter, on rack panel with AC Power, Calib. Book & Xtal. \$95.00.

Brush BL-202 2-channel oscillograph, Used, Exc. \$90.00

Sorensen 3000S AC Line Voltage Regulator, 3000 V.A. Used, Exc. \$125.00

Non-Linear-Systems 451 Digital Voltmeter. P.U.R. Send 10c for flyer listing surplus equipment, test equipment, new and used ham gear.

JEFF-TRONICS

4252 Pearl Rd. Cleveland, Ohio 44109

NOW TUNAVERTER[®] X
WITH NEW ELECTRONIC SQUELCH ACCESSORY FOR NOISE FREE MONITORING OF . . .
POLICE - FIRE - G. DEFENSE AIRCRAFT - AMATEUR CALLS, ON YOUR BROADCAST RADIO!



Tunable plus Crystal controlled (selectable with switch) solid state converters to change your auto and home radios into excellent, sensitive, selective, calibrated VHF receivers!

CRYSTAL & TUNABLE. = VERSATILITY!
CHANGABLE CRYSTALS = USABILITY!"
AND NEW ADJ. SQUELCH

- 9 volt battery powered
- Includes coax, mount
- New FET transistor osci.
- 1 year guarantee
- Size—2 1/2" x 3 1/2" x 4 1/4"
- 100% American Made

Models for AM & FM Tunable & Crystal!				
BAND	MODEL	COVERS	OUTPUT	PRICE EACH
CB & 10 M	273 X	26.9-30 mc	1500 kc	
6 meters	504 X	50-54 mc	1500 kc	
Pol. ce, fire, } Weather, etc. }	1450 X	144-150 mc	1500 kc	\$32.95 ppd.
	348 X	33-48 mc	1500 kc	Less Crystal
2 meters	1564 X	150-164 mc	1500 kc	
Aircraft	1828 X	118-128 mc	1500 kc	

Models for AM & FM Tunable only				
Model	Band	Covers	Output	Price
Marine	Marine	2.0-2.85 mc	550 kc	\$19.95 ppd.
SW & WWV	SWL	9.5-16 mc	1500 kc	\$19.95 ppd.

SQUELCH FOR YOUR TUNAVERTER!!
 Noise free monitoring with adj. electronics squelch! No wires to Radio or Converter! Just plug in coax! For all 1500 kc outputs, 9 or 12 V. 1 x 4 x 2 inches.
 Model ST mounts on bottom of Tunaverter\$17.50 ppd.
 Model SU has individual swinging mount\$18.50 ppd.
 Coupling Loop & Ext. Antennas for use with home and Transistor Radios\$3.95 ppd.
 Mobile Battery Eliminator, 12V to 9V\$4.95 ppd.
 Crystals—State Exact listening Freq.\$5.10 ppd.
 Order from: **AIR MAIL add \$.85 ea.**

HERBERT SALCH & CO. Marketing Division of
 Woodsboro 79, Texas Thompsonkins Radio Products

YOUR SURPLUS WANTED BY THE FASTEST GUN IN THE EAST



No horsing around, we pay fast . . . in 24 hours . . . and we pay more. We'll swap or trade new equipment too . . . We quote fast too. We also pay for shipping, insurance, etc. You call fast, now, collect, for fast quote.

SPACE ELECTRONICS
 div. of MILITARY ELECTRONICS CORP.
 11 Summit Ave., East Paterson, N.J. 07407, (201) 791-5050



U. S. CRYSTALS
 Surplus Crystals — Amateur
 FT243, DC34, CRIA/AR, FT241, HC6/U and other misc. crystals
 Write for Free Catalog
U. S. CRYSTALS
 Los Angeles, Calif.
 P.O. Box 78397

GO VHF

Go VHF the easy VHF Associates way. Send for descriptive Technical Bulletins describing our complete line of TRAN-SISTOR RECEIVING CONVERTERS and VARACTOR FREQUENCY MULTIPLIERS for 50, 144, 220, 432 and 1296 MHz.

VHF ASSOCIATES, INC.
 P.O. Box 22135, DENVER, COLORADO 80222

ESTATE SALE: 110 ft. Telrex Big Bertha tower with three stacked 6 element beams on 20, two 5 element beams on 15, two 4 element beams on 10, one 3 element beam on 40, Spiral on 6, 20 elements on 2 meters. All Telrex. Must be removed from present location. Original cost \$12,000. Make offer. 73 Magazine, Box 69, Peterborough, N.H. 03458.

DAYTON HAMVENTION April 26, 1969: Sponsored by Dayton Amateur Radio Association for the 18th year. Technical sessions, exhibits and hidden transmitter hunt. An interesting ladies' program for XYL. For information watch ads or write Dayton Hamvention, Dept. S, Box 44, Dayton, Ohio 45401.

RTTY GEAR FOR SALE. List issued monthly, 88 or 44 MHy torroids 5 for \$1.50 postpaid. Elliott Buchanan & Associates, Inc., 1067 Mandana Blvd., Oakland, California 94610.

WANTED: Military, commercial, surplus Airborne, ground, transmitters, receiver, testsets accessories. Especially Collins. We pay freight and cash. Rico Electronics, Box 156, Annandale, Va. Phone 703-560-5480 collect.

3000 V @ 3μF brand new GE Pyronal oil capacitors \$3 each. Can mail, 3-lbs each shipping wt., FOB. P. Wandelt, RD #1, Unadilla, New York 13849.

DANGER

73 Transistor Circuits has driven hundreds of amateurs right out of their minds with joy. Do not send \$1 for this dangerous book. Do not send it to: 73 Magazine, Peterborough NH 03458.

Your ad in this space will reach 65,000 paid readers (an honest Figure!). Plus all their friends who are too chintzy to buy their own copy.

Call or Write for Ad rates today
73 Magazine,
Peterborough, N.H.
03444
Phone 603-924-3873



"FLAT PAK" INTEGRATED CIRCUITS!!

BRAND NEW!
\$1.49
DUAL 914*

★ First time anywhere two identical IC's in one, package.

We include
 30 Basic IC Projects
RADIO-ELECTRONICS
 January & JULY 68



RTL Logic

-55° C to +125° C
 Electronics World:

EPOXY SILICON TRANSISTORS

- 3-FK-4046, 1W, 0.5A, npn, 250MC \$1.00
- 3-2N3568, 350MW, 200MC, 200BVC, NPN \$1.00
- 4-2N3563, NPN, 600MC, 200MW \$1.00
- 3-2N3683, NPN, 1000MC, 5MA, 200MW .. \$1.00
- 3-14 WATT, B-5000, npn, 3A \$1.00
- 4-2N4313, PNP, 600MC, 200MW \$1.00
- 4-2N3565, 500HFE, npn, 200MC \$1.00

FAIRCHILD INTEGRATED

IN-LINE CIRCUITS



Tested, with data sheets

- 930 DUAL 4 INPUT GATE & EXPANDER \$1.00
- 933 DUAL INPUT EXPANDER \$1.00
- 944 DUAL POWER GATE \$1.00
- 946 QUAD 2 INPUT NAND/NOR GATE \$1.00
- 952 DUAL 2 INPUT INVERTER GATE \$1.00
- 953 2-2-3 INPUT AND GATE \$1.00
- 954 DUAL 4 INPUT AND GATE \$1.00
- 955 8 INPUT AND GATE W/2 INPUTS \$1.00
- 956 DUAL INPUT BUFFER \$1.00

100's of other IC's including: Flip-Flops, Registers, Adders, etc. Write for listing.

FAIRCHILD ** BRAND NEW! "FLAT PAK" RTL INTEGRATED CIRCUITS Sale

- 900 Buffer \$1.49
- 903-903* 3 Input Gate \$1.69
- 904-904* Half Adder \$1.69
- 914-914* Dual 2 Input Gate \$1.49
- 923 JK Flip Flop \$1.69
- 923-923* JK Flip Flop \$1.98
- 927 Quad Inverter \$1.69

*First time anywhere two identical IC's in one package, example 923-923 contains two separate JK flip-flops in one package. 914's and 923. We include 50 uses. ** Licensed. 1/4" x 1/4"

LINEAR AMPLIFIERS with circuits & data

- 702C WIDE BAND DC \$3.98
- 703H RF-IF-FM \$1.49
- 709C HI-GAIN OPERATIONAL \$3.98
- 710C HI-SPEED DIFF. COMP. \$3.98
- 711C DUAL COMPARATOR \$4.98

400 mc
5 for \$1 NPN
2N706
 Watts | V_{cb} | H_{fe} | ma
 .5 | 30 | TO-300 | 150
 SILICON

\$10 ORDERS
 CHOOSE
 ANY
\$1 ITEM **Free**

100 MICROAMP PANEL METER



SILICON POWER STUD RECTIFIERS

PIV	3A	6A	12A	55A
50	<input type="checkbox"/> .06	<input type="checkbox"/> .16	<input type="checkbox"/> .20	<input type="checkbox"/> .50
100	<input type="checkbox"/> .07	<input type="checkbox"/> .22	<input type="checkbox"/> .25	<input type="checkbox"/> .75
200	<input type="checkbox"/> .09	<input type="checkbox"/> .30	<input type="checkbox"/> .39	<input type="checkbox"/> 1.25
400	<input type="checkbox"/> .16	<input type="checkbox"/> .40	<input type="checkbox"/> .50	<input type="checkbox"/> 1.50
600	<input type="checkbox"/> .20	<input type="checkbox"/> .55	<input type="checkbox"/> .75	<input type="checkbox"/> 1.80
800	<input type="checkbox"/> .30	<input type="checkbox"/> .75	<input type="checkbox"/> .90	<input type="checkbox"/> 2.30
1000	<input type="checkbox"/> .40	<input type="checkbox"/> .90	<input type="checkbox"/> 1.15	<input type="checkbox"/> 2.70

1 AMP TOP HAT AND EPOXIES

PIV	SALE	PIV	SALE	PIV	SALE
50	<input type="checkbox"/> .05	800	<input type="checkbox"/> .19	1800	<input type="checkbox"/> .87
100	<input type="checkbox"/> .07	1000	<input type="checkbox"/> .31	2000	<input type="checkbox"/> 1.05
200	<input type="checkbox"/> .08	1200	<input type="checkbox"/> .44	3000	<input type="checkbox"/> 1.60
400	<input type="checkbox"/> .11	1400	<input type="checkbox"/> .62	4000	<input type="checkbox"/> 1.90
600	<input type="checkbox"/> .16	1600	<input type="checkbox"/> .72	10000	<input type="checkbox"/> 4.80

★ Handles 2 Amps
2 AMP
800 PIV for
TOP HAT
RECTIFIERS **\$1**

6
TUNNEL DIODE
 1N3716/TD3
 Actual Size
 Used in many oscillator and amplifier circuits **\$1**



1. AMP

MICROMINIATURE SILICON RECTIFIERS

Actual Size

PIV	SALE	PIV	SALE
50	<input type="checkbox"/> 5¢	600	<input type="checkbox"/> 20¢
100	<input type="checkbox"/> 7¢	800	<input type="checkbox"/> 25¢
200	<input type="checkbox"/> 9¢	1000	<input type="checkbox"/> 31¢
400	<input type="checkbox"/> 12¢		

10¢ for bargain catalog on 100's of \$1 Poly Pak assortments, transistors, rectifiers, zeners, ICs, Triacs, SCRs, etc., parts & equipment. "It's the hottest bargain parts catalog in the industry."

Terms: add postage. Rated: net 30, cod's 25%
 Phone Orders: Wakefield, Mass. (617) 245-3829
 Retail: 211 Albion, St., Wakefield, Mass.

POLY PAKS

P.O. BOX 942 A
 Lynnfield, Mass. 01940

LIBERTY
PAYS

MORE!

WILL BUY FOR CASH ALL TYPES

- ELECTRON TUBES
- SEMICONDUCTORS
- Military Electronic Equipment
- Test Equipment

WIRE, WRITE, PHONE COLLECT! WE PAY FREIGHT ON ALL PURCHASES

Liberty Electronics, Inc.

548 Broadway, New York, New York 10012, Phone 212-925-6000

"ARCTURUS" SALE

- Tube cartons 6AU6 etc. size, \$2.15 per 100. 6SN7 etc. size, \$2.55 per 100. 5U4GB size, \$2.95 per 100. 5U4G size, .03c each.
- 7" 90° TV bench test picture tube with adapter. No ion trap needed. Cat. #7BP7, \$7.99.
- Silicon rectifier, octal-based replacement for 5U4, 5Y3, 5AS4, 5AW4, 5T4, 5V4, 5Z4. With diagram. Cat. # Rect 1, 99c each.
- 5 transistor circuit boards containing up to 6 transistors, plus diodes, resistors, capacitors, etc. Cat. # TB10, 99c.
- Kit of 30 tested germanium diodes. Cat. #100, 99c.
- RCA-110° flyback transformer, latest type, includes schematic diagram, applicable to any TV. Cat. # BR-1, \$2.99.
- Color yokes. 70° for all round color CRT's. Cat. # XRC70, \$12.95. 90° for all rectangular 19 to 25" color CRT's. Cat. # XRC90, \$12.95.
- Transistorized U.H.F. tuners used in 1965 to 1967 TV sets made by Admiral, RCA, Motorola, etc. Removable gearing may vary from one make to another. Need only 12 volts d.c. to function. No filament voltage needed. Easy replacement units. Cat. # U.H.F.567, \$4.95.
- U.H.F. Tuner—original units as used in TV sets such as RCA, Admiral, etc. covering channels 14 through 82, as part of #94D173-2. Complete with tube. Drive gearing is removable. Can be used in most sets. Cat. # U.H.F. 3, \$4.95.
- F.M. tuner—Hi-Fi amplifier tuning unit. Tunes from 88 to 108 mc. Contains two 10.7 Mc. I.F. transformers, one 10.7 sound discriminator, R.F. oscillator and mixer stages and 12DT8 tube. I.F.'s are standard "K" type. Circuit diagram for building F.M. radio included. Also plan for building F.M. tuner. Sam's photofact #620 shows 2 applications, 1 for radio, 1 for Hi-Fidelity tuner and amplifier. Cat. #FM-20, \$4.95. Send for our free catalog listing thousands of similar best buys in tubes, parts, kits, transistors, rectifiers, etc. Orders under \$5.00, add \$1.00 handling charge. Include 4% of dollar value of order for postage. Canadian postage \$1.00 extra.

ARCTURUS ELECTRONICS CORP.
502-22nd St., Union City, N.J. 07087 Dept. 73
Phone: 201-UN 4-5568

LIBERTY
OFFERS

MORE!

PRESTEL FIELD STRENGTH..METER

(Model 6T4G)



Frequency Range: 40 to 230 and 470 to 860 Megahertz. Calibrated outward from 10 to 50,000 Microvolts. Nothing makes it easier to properly and speedily find the correct place to install TV, FM and Communication Antennas. You can measure and hear the signals

with this 4½ volt battery economically powered unit. There is nothing else like it!


Only \$120.00

INDEX TO ADVERTISERS

- | | |
|-----------------------------------|-------------------------------------|
| Aerotron (Ameco), 71 | Leger Labs, 81 |
| Amateur Wholesale Elect., 27, 67 | Lewispaull, 108 |
| Arcturus, 96 | Liberty, 112 |
| Arnolds Engraving, 106 | M&M Electronics, 97 |
| ARRL, 106 | Meshna, 104 |
| ATV Research, 107 | Mission, 25 |
| B&F, 81 | Mosley, 45 |
| Bob's Am. El., 94 | Newtronics, Cover IV |
| Burton-Rogers, 102 | Palomar, 76 |
| Columbia Electronics, 94 | Paxitronix, 107 |
| Crabtree's Electronics, 22 | Pennsylvania El., 94 |
| Dahl, 106 | PolyPaks, 111 |
| Dames, 109 | Quaker, 107 |
| Daveo, 33 | Radio Amateur Callbook, 71, 77, 105 |
| Devices, 109 | R&R Electronics, 105 |
| DGP, 49, 89 | Redline, 90, 96 |
| Dixons, 93 | Rohn, 5 |
| DXer Magazine, 94 | Rousseau, 17 |
| Electronics Asst., 70 | Saleh, 110 |
| Epsilon Records, 103 | SAROC, 80 |
| Estes, 00 | Shortwave Guide, 102 |
| Evans, 53 | Signal One, 31 |
| Fair Radio, 102 | Slep, 55 |
| Freek, 75 | Space/Military, 110 |
| Gain, Inc., 11 | Spectronics, 79 |
| Gateway Elect., 109 | Stellar, 97 |
| Gateway Tower, 103 | Telrex, 66 |
| Goodheart, 108 | Two-Way Radio, 108 |
| Hallierafters, 51 | U.S. Crystal, 110 |
| Hayden, 95 | Vanguard, 35, 76, 93, 103, 106 |
| Heath, 13 | VHF Associates, 110 |
| Henry Radio, 39, 67 | Vibroplex, 107 |
| Hunter, 83 | Viking Eng. of Minn., 54 |
| International Crystals, Cover III | Wilson, R&C., 101 |
| Int. Electronics Systems, 23, 27 | World Radio Labs, 2, Cover II |
| Jan., 108 | |
| James Research, 95, 97 | |
| Jeffronics, 109 | |
| Kirke, 102 | 73 Magazine, 53, 55, 68, 69, 89 |



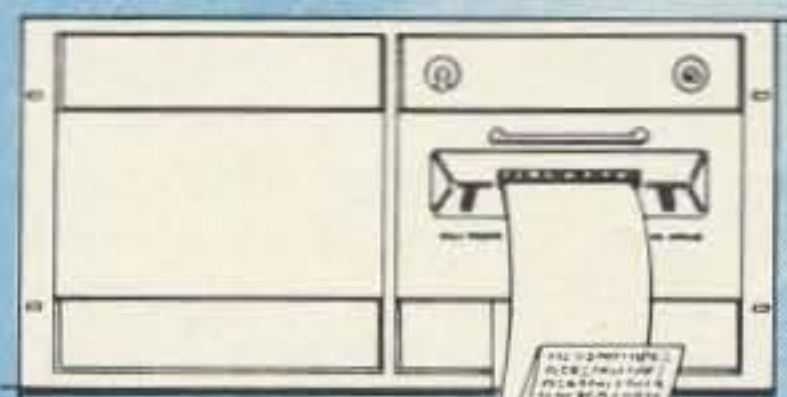NOW . . . AUTOMATIC
TEMPERATURE CERTIFICATION
 FOR INTERNATIONAL
HIGH ACCURACY CRYSTALS



International High Accuracy Crystals (HA-1 type) receive a five-point temperature check at 60°C, 25°C, 0°C, -10°C and -30°C. The temperature vs frequency test, recorded automatically from an electronic readout printer, is supplied with each individual crystal. This special service (at no extra cost) is your assurance of crystal perfor-

01520061952
03520081582
01520010903
01304904403
03520032031
01520025102
03104251142
05520028202
05520012282
02520010002
01304915710

mance at tested temperatures. We will furnish additional temperature readings (on request) for a nominal charge. *Note: Our calibration service is available to customers desiring temperature run on other crystal types and oscillators.*



CRYSTAL MFG. CO., INC.
 10 NO. LEE • OKLA. CITY, OKLA. 73102

*if you don't own a **HUSTLER** antenna...you obviously never heard one*

HUSTLER base station antennas look special . . . and are. Each is precision engineered by the undisputed specialists of the communications industry. Hustler works better—lasts longer—installs easier.

TRAP VERTICAL

One tuning adjustment to cover both phone and CW! Individually and precisely, optimum tuned traps, lowest SWR at resonance. Broadest bandwidth with SWR 1.6:1 at band edges 40 thru 10 meters. Can be top loaded for 75 meters.

Model 4-BTV User Net—\$35.95

CLIFF-DWELLER

Remotely tuned dipole for 40, 75 and 10 meters in limited antenna space. The one and only of its kind with three motors to remotely tune and band-switch. No traps or baluns—no special matching requirements. Strong, heavy duty iridited aluminum die cast housings, heat treated aluminum and chrome plated brass tubing.

Model CD-40-75. User Net—\$159.95

COVEYA-6

The famous Hustler 6 meter antenna with cardioid pattern. The ideal beam for round table QSO's. 10 db. gain over 1/2 wave dipole —25 db front to back ratio —SWR at resonance, 1.1:1—band width, 1000 kc with SWR under 2:1. Compact design, light weight—8 1/2 pounds.

Model COV-6 User Net—\$35.95

Investigate Hustler...you'll never buy anything else!

**NEW-TRONICS CORP. / 3455 Vega Avenue
Cleveland, Ohio 44113**