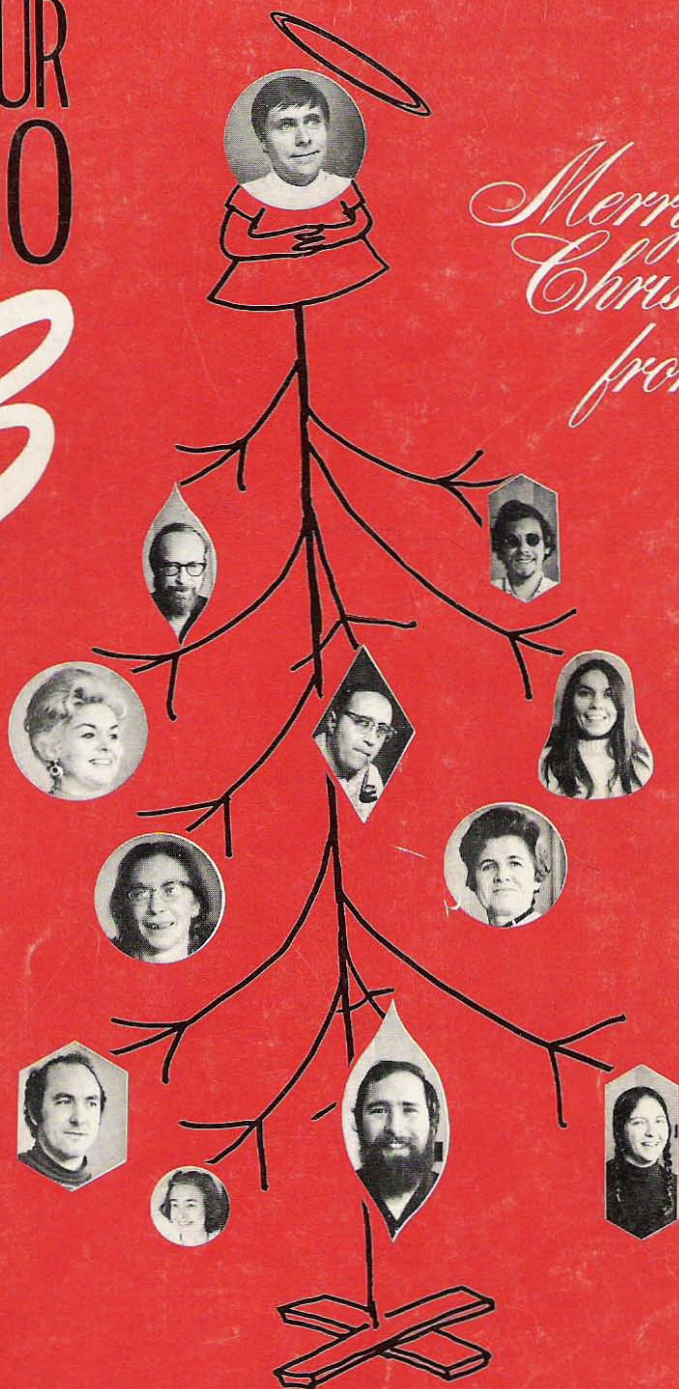


AMATEUR RADIO 73

\$1.00
(one dollarett)

*Merry
Christmas
from 73*



30 Letter Code Memory
You Can Build
Code Shorthand
Indoor Quad

ALL BAND your 40m quad
73 Tests the:
Curtis Identifier
Gam Gain Vertical

Gladding 25
TPD Car Alarm
2 Meter DSB transmitter
Mobile Theft Alarm

CONTENTS

FEATURES

- 2 Radio Amateur News Page
- 3 Hot Gear
- 4 DX Footnotes
- 4 Repeater Update
- 6 New Products
- 8 Never Say Die W2NSD/1
- 10 Letters
- 12 Caveat Emptor
- 12 Novice
- 94 Simple Squelch
- 96 Propagation
- 96 Advertiser Index

STAFF

Editor-Publisher

Wayne Green W2NSD/1

Associate Editor

Jim Kyle K5JKX

Assistant Publisher

Phil Price

Assistant Editor

Eric Falkof K1NUN

WTW Editor

Dave Mann K2AGZ

Advertising Manager

Aline Coutu

Art Director

Roger Block

Advertising Layout

Nancy Estle

Composition

Ruthmary Davis

Subscriptions

Dorothy Gibson

Circulation

Barbara Block

Comptroller

Georgianna Sage

Publications

Biff Mahoney

Traffic

Taylor Sage

Propagation

John Nelson

Drafting

R.K. Wildman W6MOG

- 13 Convert Your 7 MHz Cubical Quad to All Bands K6DDO
Everybody's doing it.
- 17 The Indoor Quad K9RJO
How to cram a quad into an apartment.
- 19 Getting to Know Tee Squared EII. Thorpe
This is a very logical article.
- 27 More Power From 6146's W2YW
Getting more power without disaster.
- 29 Radio Direction/Range Finder K6BIJ
Think Piece.
- 31 Curtis CW Identifier K6MVH
For repeaters and remote base stations.
- 37 Morse Memory WA6ATT
30 letter memory for ident, contests, etc.
- 49 73 Tests the GLADDING 25 FM Transceiver Staff
25 watt \$250 FM transceiver.
- 77 73 Tests the GAM TG-5-S Gain Vertical Staff
Why we use it for our repeater.
- 80 SCR Mobile Theft Alarm W1BHD
Burglars please do not read this article.
- 81 DX QSO's or Contacts G3BID
The human side of DXing.
- 83 Code Shorthand K2EE
Toward speedier copying.
- 85 VHF Double Sideband W4KAE
Sideband? On two meters?
- 92 73 Tests the 270 Automatic Alarm W2NSD/1
And likes it . . . and likes it!

73 Magazine is published monthly by 73 Inc., Peterborough, New Hampshire 03458. Subscription rates are \$6 for one year in North America and U.S. Zip Code areas overseas. \$7 per year elsewhere. Two years \$11 in U.S. and \$12 overseas. Three years \$15, and \$16 overseas. Second class postage paid at Peterborough, N.H. and at additional mailing offices. Printed at Menasha, Wisconsin 54952 U.S.A. Entire contents copyright 1971 by 73 Inc., Peterborough NH 03458. Phone: 603-924-3873.

COVER: A fairly merry Christmas from the dedicated little group that brings you 73 each month. Reading down, left to right, we have controversial Wayne Green, editor, resident gourmet cook and bon vivant. Phil Price is next, our architect of the newspages, solver of circulation miseries and about 50 other jobs. Eric Falkof K1NUN, the new assistant editor, will be the scapegoat for all of Wayne's blunders. Aline Coutu, one of the reasons 73 is doing so well with advertising, is a church organist as well as advertising manager at 73. Roger Block, art director, designs covers like this one, draws hilarious cartoons, and smokes a stink-pot pipe. Nancy Estle, our artist, puts together most of the pages of 73 as well as a lot of the ads. Isn't she a doll? Ruthmary Davis fights the vagaries of the IBM composer to set the type for 73 and our growing line of books. Dotty Gibson handles the subscriptions and tries her best to deal with the seemingly insane computer which tries to screw up our mailing list every month. Biff Mahoney tends the cantankerous presses in the 73 printing department. He has developed an impressive vocabulary of blue words which seem to help keep things running. Barbara Block keeps your information requests flowing smoothly (please send in one to her today with a little note of thanks and let her know that she is not forgotten), a chore which helps Aline keep the advertisers happy and, in turn, 73 in business. Taylor Sage does almost everything else. . . like keeping everything running despite the best efforts of our machines to self-destruct, getting the mail, putting on a new roof, binding books and magazines, and etc. Gigi Sage, Taylor's wife, bookkeeps, making herself known primarily to delinquent advertisers. Taylor and Gigi live in a nice little place they call Motley Gardens out in the woods at the end of a long driveway. If you find yourself in New Hampshire please stop in and say hello to all of us!

Amateur Radio

DECEMBER MCMLXXI

Monthly Ham

21 CB'ERS INDICTED

Reprinted from *The Cedar Rapids Gazette*: October 9, 1971.

DES MOINES (UPI) — A federal grand jury has returned 121 indictments against 21 Polk County residents on 14 different violations of the Federal Communications Commission regulations.

U.S. Attorney Allen Donielson said it was the first time a grand jury anywhere in the nation had indicted citizen band radio operators for alleged violations of the FCC rules.

The 21 persons indicted, all members of a citizen band radio operator club called "Apollo," were accused of making it impossible for legitimate users of citizen band radios to transmit messages in the Des Moines area.

Donielson said the indictments climaxed a nearly eight month investi-

gation by the FCC, the grand jury and his office. He said some of those named in the warrants were licensed citizens band operators and some were not, and all the alleged violators were "using the citizens band like a ham radio operation."

While a "ham" radio operator can use more power and operate on a wider group of frequencies, Donielson explained, a citizens band radio operator is more limited in frequencies and power.

He said the violations included talking excessive distances, using nicknames instead of designated call letters, and using overheight antennas.

Donielson said the law provides 14 different penalties for the violations, ranging from two years imprisonment or a \$10,000 fine, or both, down to a \$500 fine.

Former Morse Operators Have International Club

When it became apparent that the whole telegram industry would go into automation, a number of active and former telegraph operators in the Western Union, railroads, brokers' offices, private wire systems, news bureaus and others decided to form an organization to perpetuate the achievements of Samuel F. B. Morse and the traditions of the great fraternity of "brass pounders" as they were called. The Morse Telegraph Club was formed in California in 1942 and spread to 60 chapters throughout the U.S. and Canada. Today it has over 4,000 members.

Among those members are many hams, and former commercial wireless operators. Anyone who telegraphed the American Morse code or the Continental code (which hams use) for at least one year was eligible for membership. The big event each year for each chapter is the annual dinner on the last Saturday in April to commemorate the birthday of Samuel F. B. Morse.

On that Saturday each year the Western Union Telegraph Co. of 60 Hudson Street, New York City, has set up a circuit to all the cities requesting contact with the network, so that upwards of 60 cities are on this vast circuit in the U.S. and Canada. The Morse Club appoints a chief operator who tries to maintain priorities on the big circuit, and it functions all that Saturday. Wires are cut into halls, hotel dining rooms, or wherever the chapter is gathered for the annual get-together.

The proceedings and other Morse Club news, including several columns of Morse Club's ham news are published five times a year in a tabloid-size newspaper, "Dots and Dashes." Last year the Morse Club opened its membership rolls to hams, too. Dues are small.

Those interested may write O. Hugh Braese, President, Morse Telegraph Club, 1501 West Shields Avenue, Fresno, Calif. 93705

Through Repeaters...

HAM FM BRINGS AID

by Peter Lascell W4WWQ

On October 3, Amos Rhames K4WQS came upon an automobile accident three miles south of the Virginia-North Carolina state line on US-29. At 11:40 AM, Amos put out a call through the Danville, Va. repeater (WB4QWP, 28/88) for any N.C. stations to make a call to the N.C. State Police. Hearing no reply from Carolina stations, W4WWQ, Lynchburg, Va., replied offering to call the Virginia State Police to see if they had contact with the N.C. authorities. The call was made but they didn't have interstate contact.

A call was then put out by W4WWQ via the Lynchburg repeater (WB4HCX, 34/94) for N.C. stations. A reply came from Bill WB4AXH in Smithfield, N.C. about 150 miles from Lynchburg and 100 miles from the accident scene. Bill contacted his local

police department who in turn put the information on the N.C. State Computer Network at 11:50 AM.

While Rhames was at the scene directing traffic on what has been said to be the most heavily traveled two lane road in N.C., he maintained contact with both repeaters.

The state police car arriving at the scene at 12:18 PM had been a few miles south on a radar assignment. It took ham radio FM ten minutes to establish and pass information over the 330 mile round-robin circuit and took the police thirty minutes to move a car about 15 miles.

As it turned out, there were no injuries but there were some hot tempers over the crinkled metal blocking both lanes of traffic. The following stations participated: K4LKQ, K4WQS/M, K4YZR, W4WWQ, WB4AXH, WB4MBO, WB4QXE.

News Pages

News of the World

73 MAGAZINE

GOLDWATER ELECTED PRESIDENT



Senator Barry Goldwater has been elected president of the Quarter Century Wireless Association for the 1972-1973 term. QCWA, which was founded in 1947, is a non-profit international organization of radio amateurs who have been licensed for 25 or more years. Current membership is over 5200 of which more than 450 have been licensed for 50 or more years.

Senator Goldwater operates station K7UGA in Scottsdale, Arizona and station K3UIG in Washington, D.C.

INTERNATIONAL HAM PHONE PATCH LINKS AILING SON, PARENTS

(Reprinted from the Columbia (MO) Missourian.)

The University ham radio station in Brady Commons reached Central America Saturday night to reassure a University professor whose son was critically ill.

Robert E. Bray, University assistant professor of economics, was contacted Saturday by the American Consulate in Tegucigalpa, Honduras. A spokesman said his son David, 23, was critically ill with meningitis. David was touring South Central America on foot.

"They (the consulate) told us very little, just enough to be alarming," Bray said. "They said he was very ill with spinal meningitis, and if we didn't send \$650 immediately he wouldn't receive proper treatment."

Wanting more information about his son's condition, Bray called a relative who worked in the State Department and a Jesuit priest in Maine who had worked in the State Department in Honduras as a missionary a few years ago. He asked them to try to make contact with his son.

Bray's problem was solved quite unexpectedly. Wally Grossman, a friend of Bray's, called him Saturday morning concerning another matter. When he heard Bray's problem, he

suggested Bray go to the ham radio station at the University Brady Commons, and attempt a hookup with Honduras.

Steve Kahle, a graduate student in engineering, took over the radio. Kahle, son of Louis G. Kahle, University professor of political science, had attended University High school with David Bray.

The hookup was complicated and took more than an hour, Bray said. Kahle first reached the Canal Zone, where an operator linked him with Miami. Miami completed the link to Tegucigalpa.

Kahle talked with David Bray and was able to ascertain that he was feeling better. But the Brays wanted more information, and a new link was made, this time through Coral Gables, Fla.

"We found our son quite ill with meningitis, but not as serious as we had believed," Bray said. "He has to be in the hospital for two weeks. We were concerned not only with the possibility of death, but also with the possibility of brain damage. My wife is a nurse and she realized the serious implications more than I. We realized he needed prompt treatment." The Brays sent the needed money through their local bank.

HOLLYWOOD ARC CONTEST

The Hollywood Amateur Radio Club announces its first annual Operation's Day celebrating the first anniversary of its club call, WB4TON. They expect to have at least two transmitters in operation for the full 30-hour period and offer special QSL's and certificates to participating stations.

Date: January 8 and 9, 1972

Time: 1700Z Sat. to 2300Z Sun.

Frequencies:	CW	SSB
	3570	3930
	7070	7230
	14070	14330
	21070	21430
	28070	28530

Exchange: RST, state, province, or country, and name of operator.

Awards: Special QSL's to stations making contact with WB4TON during the 30-hour period.

Certificates to stations working WB4TON on both CW and SSB.

Certificates to stations working WB4TON on 5 bands. (Any combination of CW and SSB)

Application: Send SASE to W4OZF along with your QSL and a list of all contacts made to WB4TON during Operation's Day to W4OZF, Contest Chairman, 2311 West Nassau Drive, Miramar FL 33023.

HOT GEAR

Starting this month, 73's Hot Gear listing will include a cumulative list, providing a running checklist for hams and dealers to check before buying used equipment. Items will be kept on this list for ten months. Each entry consists of the make and model of the stolen equipment, identification of type of gear if necessary, the serial number and the date of the issue of 73 in which a full listing, with owner's name and call, can be found.

Hallicrafters SR46A	Xcvr	#446100	9/71
Regency 2	Xcvr	#04-03505	11/71
Sonar FM-3601	Xcvr	#1003	11/71
Collins 75A-4	Rcvr	#804	12/71

Stolen from Marvin A. Mahre WØMGI, 2095 Prosperity Ave., St. Paul MN 55109:

Collins 75A-4 Receiver, Serial #804.



A 17-year-old ham in Japan is looking for a few ham pen pals around his own age. Kazuhiro Nakao (KH3IWT) lives about 5 miles east of Osaka and his mailing address is 196-9, Shimokosaka, Higashiosaka City, Osaka, Japan. This young man is interested in basketball and he wants to exchange notes of interest with other young adults. Please contact him right away if you are interested.

Attention DXers. ARRL has announced the addition to the Countries List of Annobon Island. Annobon Island is located off the west coast of Africa in the Gulf of Guinea. It qualifies as separate from Equatorial Guinea under point 2A of the DXCC Criteria. Confirmations for contacts with Annobon Island may be submitted starting October 1.

YO2RA



Stefan Rusu YO2RA, seventy-two years old, a ham since 1927, has held calls ER5AR, CV5AR and YR5AR. He worked all continents in 1938 with 3 watts; his present rig consists of a 13 tube receiver, Hertz antenna, and a 60 watt transmitter.

Hilary McDonald W5UNF/6

VIET NAM. Fred Laun W9SZR, HS5ABD, HI8XAL, etc., who is presently a Province Advisor in the Vinh Binh, along with Don Riebhoff K7CBZ, HS3DR, etc., are working hard to get permission for amateur radio operation in this country. They've had a lot of experience with that in other areas, so they just may make it where everyone else has failed. If you have any help to offer write to Fred Laun, JUSPAP/PPA Advisory Team 72, APO 96243 San Francisco.

Kure and Midway QSL cards for the W7UXP/KH6 DXpedition should go to KH6BZZ, no matter what else you may have heard. Bureau cards will not be accepted. Address 45-601 Luluk Road, Kaneohe HI 96744. Donations gratefully accepted.

KAMARAN ISLAND, VS9K, unavailable for about five years now, is expected to be in operation for a few days in early 1972 when Aldo ET3ZU visits there. The Labor Day operation from Jabal al Tair Island in the Red Sea netted over 7000 contacts... a very good score indeed.

AVES ISLAND, YV0 should be on in late October if the two radio amateurs accompany the scientific expedition to this remote island as expected.

JORDON, JY9DK was on for a few days from Amman. Darleen will be on from various spots around Europe during November and will be returning to the U.S. in December. SMSAEC is scheduled to be on from Jordan too, so it looks as if there will be no real shortage of JY calls on the bands. King Hussein JY1 still shows up frequently on the bands to reward the diligent DXers.

ZANZIBAR, 5H3LV is trying to get back there again in late December for those who missed Garth's last two visits there in February and April 1970. By now there should be a fair demand built up.

(Thanks to the West Coast DX Bulletin)

DX MAILBAG



Hi Wayne:

As per our contact the other night I am enclosing the shot of Gus Roblot FP8AP.

After some ninety 90 trips to the Newfoundland mainland with the ATTA BOY in which he brought ice cream to St. Pierre for sale on the Island, Gus has finally decided to retire his trusty little boat. To let the legend of the ATTA BOY live on, Gus has decided to move it up on the mountain side on St. Pierre on skids,



W2NSD/1 report!

On the morning of September 28th I noticed that the two meter band was unusually good. The WA1KGR repeater from Holyoke MA was pushing S-9 on the Standard, where it usually struggles in here about S-4 or so; good copy, but not overpowering. This perked in the back of my mind through the day and, when things went a little blah along about ten that night I headed for the top of Pack Monadnock in the Rover.

Sure enough, signals were excellent. I put the C.T. Power amplifier on the Standard, boosting it to about 80 watts output and made a try to get into WA2SUR 19-73 in New York City. I've tried them before, but never when they were as strong, running an S-2 with a lonng slooow fade, taking perhaps fifteen minutes to go through a valley and back up again. I made it this time and quickly found myself talking to a bunch of good old friends through that extremely popular repeater. The most exciting contact for me was with Larry WA2INM, who wrote a lot of articles for 73 back in the early days and spent a good deal of time haunting the 73 offices in Brooklyn. Further, he did a good deal of the work of moving us up here, and then visited any number of times while he was going to college in nearby Marlboro VT. Larry was sitting in a bar in Greenwich Village with a TR-22, with his wife Jackie WB2BXY!

and make a ham shack out of her, for visitor hams to use while on the island, as well as his own shack. Shown here with the ATTA BOY are left to right, George, Gus' son-in-law, Bridget, Gus' granddaughter, and Gus FP8AP.

Bill W1PFA

INTERNATIONAL AMATEUR RADIOCOMMUNICATION

The FCC has received notice from the Cambodian licensing authorities that pending government approval and eventual International Telecommunications Union notification, there would be no objection to communications between amateur Station XU1AA, Phnompenh, Cambodia, and U.S. licensed amateur stations.

The Commission has no objection to U.S. amateurs communicating with Station XU1AA.

Shifting to WA1KGGK in Trumbull CT I added more old friends to the log, plus Jim K3VJH down near Washington, almost 400 miles away, and John K3IBN in Harrisburg PA. I could hear a lot more chaps coming through the Philly repeater on 76, but they were busy with themselves and weren't as excited over working New Hampshire as I was in contacting Philly, so nothing came of it.

The car battery, my perseverance and the band all failed about 2 AM, so I pushed the car to start it and headed home to bed.

Would there be an interest in a repeater contest? I know I would enjoy it, but perhaps I'm in a great minority. Perhaps one which would give one point for every contact made through a repeater, with a multiplier for the number of repeaters used. I'd win, of course, but what better way to set up a contest, right? With a minimum of 22 repeaters available from my nearby mountain, even without a beam, I have quite an advantage. If someone gives me trouble from down in Massachusetts on Mt. Greylock we could throw in a state multiplier to push me back over the top again.

Ken and I discussed an FM contest, but he was violently opposed to it. FMers aren't interested in DX and contests, said he. Maybe not, but a lot of chaps sure tried hard to contact me when the band was open and the rest, with one or two exceptions, cooperated fully. If I get letters of encouragement from a dozen states we can start mulling over the rules for a short fun contest, perhaps 24 hours on a Saturday night through Sunday afternoon. It won't take as many negative letters to turn the whole thing off... I discourage easily

DXing The Repeaters

The late September effects of the hurricane sliding up the coast were most pleasant for old timers on two meters. The band went wild, with the FMers finding Ohio repeaters banging into Maine and most of New England, and openings all over the place from the midwest down to Virginia. I drove to the top of my local mountain on three different nights and had a wonderful time working the gang in New York through WA2SUR 19-73. The temperature inversion was so pronounced that I could even see lights reflected way up in the sky from what must have been New Haven, well over 100 miles away.

My old buddy Frank W2OCM was boiling through the New Hampshire repeater W1ALE from Long Island and I worked him on a half dozen different repeaters in short order. My best DX for the evening was K8WKE in Utica Michigan who was hearing me through W1ABI in Vermont and

coming through on 88 direct! My 34 receive channel was awash with signals from New York and New Jersey and I had better luck listening 34 and letting them hear me through one or more of the 34-94 or 34-76 repeaters.

Ernie W1FPT down in Bridgeport CT probably did the best of all with his 100 watts and beam. He worked all over the place. I wonder if we shouldn't think in terms of making a certificate available for working through 100 repeaters? Perhaps a tape cassette of the CW identifications coming back would be proof? I know I get a kick out of lifting a repeater out in Ohio or western Pennsylvania and hearing the identification come back.

CA	WA6SIN	Ventura Cty.	28-88
CA		Broomfield	01-61
		proposed	
CO	WA0VUO	Denver	04-64
CO		Denver RTTY	10-70
CO	WA0VTV	Colo. Springs	16-76
CO	W0IA	Boulder	16-76
CO	WA0BAG	Saginaw Peak	16-76
		proposed	
CO	WA0ZCI	Monte Vista	16-76
		proposed	
CO		Pueblo prop.	19-79
CO	WB0ERV	Buckhorn Mt.	25-85
		No. CO	
CO	WA0SNO	Pueblo linked	28-88
		to W0ENA	
CO		Denver simplex	88-88
CO		Denver prop.	31-91
CO	W0WYX	Denver Squaw	34-94
		Mt.	
CO	WA0SNO	Pueblo	34-94
CO		Denver prop.	37-97
CO	K0OVQ	Denver CD	
			146.82-147.30
CO		Arapahoe Cty. CD	
			147.06
CO		Prop. CO	58-88
		simplex	
CO		State RACES	
CO	WA0VVC	Denver	145.20
			444.35-449.35
CO	WA0FTM	Broomfield	
			444.40-449.40
CO	W0WYX	Squaw Mt.	
			444.45-440.45
CO	W0IA	Boulder	
			444.55-449.55
CO	WB0ERV	Buckhorn Mt.	
		proposed	
			444.85-449.85
CO	W0ENA	Pueblo	53.0-52.525
CO		Statewide simplex	
			52.525
CT	K1IGF	New London	19-94
FL	WB4KNQ	Merritt Island	34-76
			443.1-448.1
GA	WB4KLM	Augusta	34-94
HI	KH6EQF	Honolulu	
			449.15-444.15
HI	KH6FOX	Waikiki	16-76
HI	KH6EQK	Mt. Holeakala	
			444.15-449.15

IA	WA0VVA	Linn Co.	34-94
IA	K0JTU	Council Bluffs	22-82
IL	WA9DZO	Chicago	10-85
IL	WA9DZT	Chicago	52.76-52.64
IL		Chicago	46-88
IL		Chicago	147.40-147.81
IL	WA9ORC	Chicago	
			448.75-443.75
IL	WA9TEC	Decatur	34-94
IL	WA9SGJ	Graymont	16-94
IL	WA9EAT	Joliet	28-987
IL	K9CLW	Winnebago	
			82-147.30
IL	WA9LIV	Waukeegan	34-76
		(1950 Hz Wimot WI access)	
IL	WA9ORC	Chicago	34-76
IL	WB9AEF	Peoria	34-76
IL	W9DGV	Rock Island	34-94
IL	W9DGV	Rock Island	34-76
IL	K9CLW	Winnebago	
			82-147.30
IL	WA9LIV	Waukeegan	34-76
		(1950 Hz Wimot WI access)	
IL	WA9ORC	Chicago	34-76
		(1800 Hz no., 2000 Hz so.)	
IN	W9ZPP	Evansville	
			52.92-52.525
IN	K9JSI	LaPorte	22/34-76
KS	WA0VWV	Pittsburg	34-94
LA	WB5CDP	Monroe	
			52.827-52.525
LA	W5MLE	Morgan City	34-94
		(+440.0-146.94 & 444.5-52.525)	
MA	K1FFK	Mt. Greylock	
			52.78-52.525
MA	WA1KFZ	No. Adams	10-70
MI	WB8CSA	Benton Harbor	34-94
MI	W8MAI	Benton Harbor	94-76
MI	K8WKE	Utica	28-91
NH	WA1KGO	Peterborough	19-79
		(was 37-73)	
NJ		Oakland	16-91
NY	WB2BLU	Yonkers	31-91
OK		Oklahoma City	16-76
RI	W1HQV	Providence	16-76
SD	WA0VVG	Sioux Falls	34-94
SD	W0BXO	Brookings	34-94
TN	W4BS	Memphis	22-76
			444.0-449.0
TX	WA5SNJ	Pasadena	34-94
VA	WB4QDP	Arlington(DC)	31-91
WI	W9ROM	Milwaukee	34-76
		(2250 Hz Slinger; 1700 Hz Grafton)	
WI	WA9PBW	Madison	34-76
		(2100 Hz)	
WI	WA9WVE	Madison	46-88
WI	W9AIQ	Sturgeon Bay	34-76
CANADA			
BC	VE7ELK	Chilliwack	46-00
BC	VE7CAP	Kimberley	34-94
		Cranbrook	
BC	VE7BTU	Nelson	46-147.33
BC	VE7AFG	Prince George	
			58-147.33
BC	VE7CAQ	Trail	34-94
BC	VE7RPT	Vancouver	34-94
BC	VE7BEL	Victoria	22-147.54
ONT	VE3SAR	Sarina	34-94

Thanks to WB4EAB, WA9TKA, WB6MAY/VE7, WA0RLQ, K6YLQ.



BOSTON HAM AUCTION

Boston College ARC (W1PR) and Middlesex ARC (WIHEB) are jointly sponsoring an auction of radio and ham gear to be held Friday, November 26 at Campion Hall, Boston College, Beacon Street, Newton MA, at 7:00 PM. All area hams are urged to attend, bringing any gear they'd like to sell. There will be a raffle and refreshments will be available.

SEPTEMBER VHF CONTEST

The results of the Honeywell Radio Club (W1DC) effort in the September VHF contest are interesting to mull over. They operated on seven VHF/UHF bands, 50 through 5650 MHz, and made 881 contacts in 29 different sections. The most contacts were made, naturally, on 50 MHz, where they made 432 in 28 sections. Interestingly, 18 of those were on FM, 90 on AM and 324 on sideband and CW! On 144 MHz they made 106 FM contacts, 152 AM, and 107 sideband or CW contacts, for a total of 365 in 21 sections. The best distance on 2m was West Virginia, Virginia and Ohio. Ten contacts were made with Maryland—DC! On 220 MHz no AM was used so there were 17 FM and 18 SSB/CW contacts for 35 total in 13 sections. The 432 MHz results might have been better with some FM, but 31 contacts were made on SSB/CW and 6 on AM, thirteen sections contacted. There were seven contacts on 1296 with 5 sections, the furthest being New Jersey. Four neighboring sections were contacted on 2400 MHz and one on 5650 MHz. Would there be any interest in 73 providing a special certificate of merit for two-way contacts between any two stations on six VHF bands? That sounds like an interesting goal.

DELAWARE QSO PARTY

This contest runs from 2300 GMT Dec. 18 to 2300 GMT Dec. 19. The exchange will be QSO number, report and county (for Delaware stations) or state, province or country for non-Del. stations. Suggested frequencies: CW, 3560, 7060, 14060, 21060, 28060; phone, 3975, 7275, 14325, 21425, 28650; VHF 50.4 and 144 MHz. Novices on 3710 and 7170.

Awards: A certificate will be awarded the highest-scoring station in each state, Canadian Province and foreign country (with 3 or more contacts) and to the highest-scoring station in each

Delaware county. In addition, a W-DEL certificate will be sent to any station working all three Delaware counties. Logs showing required date will be accepted in lieu of QSLs. The mailing deadline is Jan. 1, 1972. Send your log to Mark Augustin WA3OYA, 2119 Barr Road, Wilmington, Del. 19808. Persons wishing the W-DEL certificate must apply to this address. No fee asked, but SASE is required.

CINCINNATI STAG



"Without mud it wouldn't be a Cincinnati Hamfest," as one astute observer so aptly phrased it. Nevertheless, quite a number of brave lads from the far corners of Ohio and the nation braved the forbidding muck to set up table and tent in pursuit of an unfrozen buck.

This year's Cincinnati Stag Hamfest boasted an added treat in the person of Bob Mathews, K8TQK, the notorious "voice" of "Miamisburg's Finest Repeater," WA8PLZ. Our enterprising cameraman caught Bob in festive cowboy hat and jovial mood at left in the picture above. This is the last known photograph of Bob, who was last seen sinking rapidly in a plate of roast beef.

At right in the photograph is Miss Floozie O'Toole, an agent of the Women's Liberation Movement, who successfully infiltrated the traditionally all male event by disguising herself as a set of Drake equipment.

..WB8LBV

WITH THE FCC



WA3NIL fined \$100 for operating on unauthorized frequencies.

WA30FK proposed revocation of license for not answering FCC mail.

WN4RGR revoked for failure to answer FCC mail and violations.

WA6GMR revoked for failure to answer FCC mail and violations.

WB4KGL proposed revocation of license.

This may seem like a lot, but it is miniscule amid the hundreds of CB fines and revocations.

NEW PRODUCTS

TWO NEW FM TRANSCEIVERS ANNOUNCED



The Icom IC-20 and IC-21, which have been coming back from Japan under the arms of returning servicemen, are now being imported by our old friends at Adirondack Radio in Amsterdam, New York. Both are 10 watt FM two meter transceivers, with the IC-20 having 12 channels and the IC-21 24 channels! In addition there is an accessory vfo for the IC-21 to permit continuous tuning of the receiver. The IC-21 has an S-meter, an SWR meter and even a discriminator meter built in. There is a protection circuit which turns off the final if the output is shorted, open or likely to damage the transistors. The IC-21 operates from either 13.6 volts or 115 V ac. Both use 18 MHz crystals for the transmitters and 15 MHz crystals for the receivers



For further information write to Adirondack Radio, Box 88, Amsterdam NY 12010 or watch 73 for a review of the IC-21 at an early date.

Automatic Alarm


Whether you have a rig in your car or not you need an alarm these days. The estimated life expectancy for a Corvette parked on the streets of New York is now about 17 minutes, average.

The Technical Product Development Company, Box 84, Nutley NJ 07110 has come out with an alarm system for cars which does just about all you could want. For \$50 it will set itself automatically and sound your horn, flash lights set off a siren, etc as well as prevent the car from being started if anyone opens a door, hood, trunk, or messes with the ignition. You have seven seconds after opening your car door to turn off the hidden switch to prevent all hell from breaking loose. They have other models for \$20, \$30 and \$40 with progressively fewer features. They claim that the gadget is easily and quickly installed.

The Immovable Key


How about a key with no paddle movement at all! With no keying contacts, and completely solid state, the Data Engineering key operates by touch alone. The key has two insulated electronic grids which, when touched, operate the ICs. With this system there can be no problems with contact adjustment or bounce since there are no contacts.

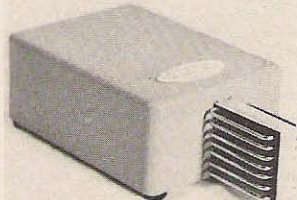The key operates from two C cells and uses two ICs and two transistors. It is carefully shielded against rf. Weighting prevents the key from walking.



How Data Engineering can turn out this remarkable key, with a 5-year guarantee, for only \$19.95 is surprising. You can get a spec sheet from them if you write to Box 1245, Springfield VA 22151.

16 Channel Scanning Receiver

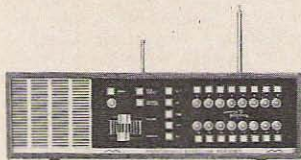

Regency Electronics, 7900 Pendleton Pike, Indianapolis IN 46226 now has a 16-channel scanning receiver available. This covers the 50, 146 and 450 MHz bands, enabling you to monitor repeater channels on all three bands. Push buttons activate the channels you wish to monitor. Manual switching of channels is also possible, naturally. The built-in antennas can be bypassed with outdoor antennas and the built-in speaker can be bypassed if an external one is preferred. Price? \$219. This would seem to be an excellent FM scanner for the serious FMers as well as the FM amateur with irons in other fires such as the need to monitor police, Apollo 16, the mafia, or whatever.

TELL OUR ADVERTISERS
YOU SAW IT IN 731
...even if you didn't

New BIRD Ham Wattmeter

Confirming rumors current during the past year, Bird Electronic Corporation has announced the debut of an RF Wattmeter designed especially for the ham market. There are actually three models, two of which cover the 1.8-30 MHz range (160 meter to 10 meter bands) and the third covering 50-150 MHz (6 meter and 2 meter band). The Model 4350 measures forward and reflected power in two ranges: 200W and 2000W, while the Model 4351 has ranges of 200W and 1000W. The Model 4352 has ranges of 40W and 400W covering the two VHF bands of six meters and two meters.



The new line of wattmeters are designated HAM-MATE™, and use the well known ThruLine® construction, made famous in the industrial field by the Model 43. The new 4350 Series Wattmeters emphasize dependable rf power measurement, in the tradition of Bird rf wattmeters. Special attention is given to the directivity of the Ham-Mate, which is the ability to differentiate between rf power flowing in opposite directions in a transmission line. The new Ham-Mate has a minimum of 20 dB directivity which assures meaningful reflected power (and vswr measurement).

It is anticipated that the Models 4350 and 4351 will be available for delivery beginning in October 1971, and the Model 4352 in December 1971. All three models are priced at \$79 user's net price.

Write Bird Electronic Corporation, 30303 Aurora Road, Cleveland OH 44139 for further particulars.

NEW NATIONAL TRANSISTOR CATALOG

A new 130-page Transistor Catalog is now available from National Semiconductor Corp. The catalog provides complete data on National's entire transistor line including NPN and PNP small signal transistors, Field Effect Transistors, and Pro-electron types. In addition to specifications, the catalog provides Process No. design/application data and test limit information. A glossary of terms and package outlines are also provided. For a free copy, write to National Semiconductor Corp., 2900 Semiconductor Drive, Santa Clara CA 95051, Attn: Marketing Services.

FM TRANSCIVER RECEIVES ANY 2-METER BAND CHANNEL... WITH CRYSTAL CONTROLLED PRECISION

Clegg Division of International Signal & Control Corp. has announced the immediate availability of its new completely solid state FM-27 mobile transceiver.

The principal feature of the transceiver is the CRYSTIPLEXER tuner, a new synthesizing system that allows any channel in the 2-meter band (146-147 MHz) to be monitored with crystal precision - but without the need for additional crystals. To monitor any specific frequency within this band, the operator merely sets the two receiver controls to numbers corresponding to the desired frequency. To monitor 146.94, for example, the operator sets the first control to 9, and the second to 4.

Receiver selectivity is rated at 70 dB of adjacent-channel attenuation. Sensitivity is rated at better than 0.35 μ V for 20 dB of quieting.



The transmitter portion of the FM-27 is a 10-channel solid state device with a power output of about 20 to 25W of rf.

Weighing less than three pounds, and measuring only 3½" H. x 7-7/8" W. x 9¾" D., the transceiver is packaged in a rugged anti-theft case with a special locking-clamp mounting. Two crystal controlled transmit channels and a PTT microphone are included in the suggested amateur net price of \$449.95.

Further information on the FM-27 mobile transceiver is available from Clegg Division, International Signal & Control Corp., Box 388, R.D.#3, Littitz PA 17543.

New Hep Catalog

Motorola has just announced their new cross reference guide to their entire line of semiconductors, publication HEP HMA-07 and it includes the type number, basing diagram index, packaging index, specs, maximum and minimum ratings, electrical characteristics, etc. This includes 168 new hobby devices just introduced. Replacements are listed for over 30,000 different semiconductor device numbers including 1N-, 2N-, 3N-, JEDEC numbers, Japanese, Dutch and other foreign numbers. See your Motorola HEP distributor for a free copy of this new catalog.



Meaningful Contacts

One of the more consistent complaints lodged against our hobby is that so little of our incredible communications capability is used for the exchange of more than superficial information.

Unfortunately the complaint is an all too legitimate one. Considering the reasons why this is so, I wonder if anything can really be done to reverse this pattern? Perhaps a look at some of the more basic reasons will help bring the problems into focus and give us some insight into solutions. Maybe not.

While the resultant lack of any real communication is the common result, there are several causes for this and each has to be considered separately. The chap on the two meter FM repeater has his trade-offs which limit the use he can make of that facility. The DX operator has his problems, some the same, others quite different. The Novice has his miseries, and so it goes.

Perhaps if we start with the more narrowly limiting factors and close in on the generally inhibiting situations we can best outline the whole problem. For instance, the operator working through an FM repeater has a whole bunch of cards stacked against him when it comes to opening up an interesting and meaningful conversation with someone else.

First of all, one or the other is probably driving a car. This means that a good portion of his attention is on the car driving and his radio contact has to take second place in his mind. If there is a second person in the car, this further divides his attention, and you will notice that little of what you say to this chap seems to have gotten across at all. You will be right.

Operating through a repeater could possibly work out well if two ops were putting good signals into the repeater, both had nothing whatever to do except pay attention to the other, both knew that there would be no interruptions, and both had lots of time and knew that they both had the time.

But it doesn't work this way at all. Few repeater users do not have the psychological feeling that they should get off the pot as soon as possible to make way for someone else. One, the

other, or both are preoccupied with something else. The signals often fade in and out, losing part of the conversation. One is wideband - the other narrow - and one therefore finds it difficult to understand the other, even when the signal is strong. And so it goes.

Add to this the fundamental difficulty of communicating with a person you don't know, whom you can't see, about whom you know little, if anything, a person you can't even hear except when you stand by for him, cutting off those conversation reinforcing grunts and uh-huhs which help keep two people talking with each other. The restriction of having to talk with no reinforcement, covering everything the other chap has said (as nearly as you can remember) and then originating new things to talk about is a very severe one. It is no wonder that such a large percentage of the radio amateurs stick pretty much to short recitations of their equipment and the weather.

The amateur radio type of contact is quite abnormal and has no counterpart in our learning process, so most of us are unprepared to tackle the difficulties it poses. Even on the telephone you can hear the reinforcing noises of agreement and be stopped when the other person has something to add or disagree about. Way back in the long-dead past of amateur radio this type of communication did develop for a while. Oldtimers will remember with great warmth the duplex contacts on 160 meters where it was possible to just leave your rig turned on and tune in to your contact on the other end of the band. Just like the telephone.

When sideband started and VOX became the way to go, this system looked as if it would partially bring back the old arrangement. But the clank of the relays was too much for most operators and, after uh-huhs between sentences to keep that con-flabbed VOX from tripping, they went back en masse to push-to-talk.

While a few of the DX brethren do indulge in interesting contacts, most of the exchanges are of little more value to anyone than the hasty hello over the local two meter repeater. The pressures of other stations trying to work your rare one, fading, other

contacts on frequency, and such jazz make long contacts rare. Even if you have the ability and experience to manage an interesting contact you would be hard put to bring it off.

I would dearly love to talk with YA1GNT for an hour, yet I have one devil of a time carrying on an hour contact with Chicago a good deal of the time. Oh, I can make it now and then, but I have to lose a lot of sleep waiting for the right conditions.

Are there any answers to the problem? Are there any changes that might be made so more of us could indulge in meaningful conversations via our incredible amateur radio bands? I think so.

There are no simple answers to such a complex set of problems, obviously. But we can all help out if we are first of all aware of what we are missing and make a determined effort to move in the direction of better use of our bands.

On the FM repeaters I would suggest that repeater owners seriously consider the installation of a second or third repeater. While the spectrum between 146-147 MHz is about full in many areas, there is still little going on in the 145-146 and the 147-148 bands. The emerging 220 units will make that band an invaluable addition to the two meter repeater setup. With enough repeaters we can afford the luxury of long-winded contacts. With both 146 and 220 repeaters we might even develop a duplex system of operating. The use of two- or three-minute timers on repeaters will aid the mobile operator in getting a word in when two long-winded ops are talking. Timers like that will also shorten some of the endless and pointless pontifications which drive ops off the air for weeks at a time when they get snagged.

I'd be very interested in what you, the reader, thinks might improve our ability to use amateur radio for true communication. Should phone patches be eliminated except for serious emergencies? Should nets be curtailed or encouraged? Should DX for QSL card purposes be channeled to a small set of frequencies? What can we do? Here we are, able to talk anywhere in the world, and what do we do?

When you consider that we have virtually the ONLY system for people-to-people contact around the world, perhaps you can appreciate the importance of our really making something of it. Tourists rarely get to meet the people in a country they are visiting. They meet the tour guides, hotel clerks, and taxi drivers, and that is about it. No wonder so many Europeans have incredibly distorted ideas of Americans... they know us from our movies and television ex-

ports, and an occasional camera-clad tourist who bumped into them on the street. How much do you know of Yugoslav people . . . their lives, interests, foods? Yet I doubt if any serious DXers have talked with less than a hundred YU stations.

What can we do? I think all of us are open for suggestions and ideas.

SAROC

A reader wrote to ask what it is about Saroc that we make such a fuss over it. Mostly I guess it is because this is one of the best run and most carefully planned hamfests in the country. I know I have a wonderful time there because I can get together with the amateurs who are making the news and the manufacturers with the newest products.

Like you, I'm interested in seeing and feeling the latest ham gear, whether it be FM, SSTV, or sideband. I enjoy talking with the men who design and make this equipment . . . to find out what they have in mind for the future . . . what problems they've had . . . how things are selling. I like to pass along reader questions about difficulties with the equipment and my own personal miseries that I may have had.

The 34-94 repeater allows me to talk the clock around with interesting FMers and meet the fellows who are designing the most sophisticated repeater installations.

The technical talks are usually fascinating and give me a lot to think (and write) about. The parties are even more fun, whether it be mass elbow bumps put on by manufacturers or bashes in the private rooms in the evenings.

The \$12 per double room at the hotel makes the visit relatively inexpensive as long as I stay clear of the gambling tables and devices. The expensive shops are a delight to look into if I am there alone, and a caution if my wife is along.

It's fun . . . and that is what amateur radio is all about, right?

Articles wanted...

Come on you fellows who are working with ICs, break loose with more articles for the rest of us. We know you can make up a frequency synthesizer now that will let the Novice use crystal control and still hit every kHz or even 0.1 kHz across the Novice band. We know you have worked out many ways to replace the dozens of crystals needed to hit all those FM repeaters with a synthesizer for the receiver and transmitter. We know you have some fabulous new RTTY converters and AFSK generators. We know you can build 24-hour clocks for the shack that count the Hertz arriving from Con-Ed and wink

at us with numbers. We know you can varactor yourself up through any of the UHF bands with substantial power. What we don't know is if you can write about these modern wonders.

You say you have a mini-repeater in your car so you can work through the local repeaters even with a hand unit? Details . . . give us details. You are proud of your remote base up on that mountain, complete with sophisticated controls . . . write about it so more of us can join the fun. You have a Touchtone system that is unusual? Let's go!

Status Quo of CB

The 1970 FCC annual report disclosed that a total of 886,951 stations were licensed to operate in the Citizens Band. During the year 26,327 new stations were added while but 951 were dropped. Perhaps that will put to rest some of the exaggerated reports circulating citing over a million CBers. That growth figure sure would look good in the amateur service, wouldn't it!

Scaling as a Way of Life

Several months ago we built up one of Heath's counters and it has seldom been turned off since its first test run. Normally it sat on top of the sideband rig, reading out the frequency a la the Signal One . . . "Hmmm, let's see there, Gus, I think I'm on about fourteen point two one eight three seven seven, how's that check with your receiver dial?" Heh, heh!

All this was a barrel of laughs, but it didn't help much with the mysteries of what is tuned where on two meters since this was a good bit above the range of the IB-101. And two, as you may have read, is where it's at these days. Particularly around here at the 73 pad, it's at.

Chancing to read one of the fascinating ads in 73 (I find the ads in 73 much more interesting than those in other magazines, don't you?), I noticed that Vanguard Labs was making a nifty little contraption designed to solve my problems. A Scaler. This gadget divides things by ten, which is just the ticket for counting down from 146 MHz.

Down in my cellar workshop I have one of the world's nicest old frequency meters, the Navy LR-1. This kluge weighs in a 98 pounds of hernia-inducing bulk and has about fifty tubes. It was built by General Radio, so you know it was the state of the art back when. The LR-1 has done well for me down through the years, I have to admit. With it I could read out most frequencies to a cycle or two if I made a project out of it. That's almost as good as the IB-101, which feels like it weighs about six ounces.

At any rate, today I have the IB-101 and the Vanguard Scaler on the desk and with them I can get the FM transceivers right exactly on channel instantly. I poke the prod over near the receiver oscillator and read out the 136 MHz frequency there (146.94 - 10.7 (i-f) = 136.24 MHz). A quick tweak and it's on channel. Then I probe near the coax output and tune up the transmitter. With the counter on the Hz position it counts in tens of cycles, which is closer than your quivering hand can probably adjust the trimmers. While it varies from rig to rig, I've found that several of them drop about 500 Hz when I put them back in the case. Now I know and you know that one half a kHz isn't going to make the slightest difference to anyone, but perfection is perfection and we have the means, so why not be perfect? Right, so we tune everything up a bit high and it all drops into place back in the box. For a while.

Quite a few FM rigs come and go here, so the counter is in, used almost every day. And of course, every time I am going to take a trip anywhere I have to get out my tray of crystals (I'll sure be glad when frequency synthesis is the order of the day) and re-crystal for the new area. In go the crystals and tweak, tweak, they are on channel, and I'm off to New York City or Chicago, ready to join the fun wherever I am.

Just going up on the local mountain, Pack Monadnock (where we keep the WA1KGO repeater), calls for a good deal of encrystallization. If you are on the go you could do worse than drive to the top of this lump, the highest place you can drive in Southern New Hampshire. From there you can work through so many repeaters it will make your head spin . . . WA1AE, WA1KGR, W1KOO, WA1NJR, K1MNS, WA1KGO, WA1KGP, W1ABI, WA1KFZ, WA1KGM, WA1IMO, W1QFD, WA1KRJ, WA1KFX, K1ZAW, K1ABR, WA1NEU, W1MTV, W1PRI, K2AE, WA2UYJ, and perhaps a few more if you wait for the squelch tails to stop and if too many fellows aren't on channel using closer repeaters.

Impressing Relatives

Or friends, for that matter. What amateur hasn't had to try and explain the hobby to some long-lost visiting aunt or cousin? It is difficult. They look puzzled and not very interested. Our hobby is a damned impressive one to us and we want them to appreciate what miracles we accomplish. The usual scene following the attempts to explain is one of demonstration . . . and it is frequently a disaster, leaving the aunt convinced her nephew is an idiot.

(Continued on page 10)

The chap with a DX-20 on CW has no chance and he knows it, so (unless he really is an idiot) he flips through a few choice QSL cards to prove his prowess and lets it go at that. The seasoned DXer may put his reputation on the line by turning on twenty meters and tuning for something better than average. I've tackled this with success at times, netting an interesting contact with an ornithologist in Finland on one important occasion.

The other day I was worried and I admit it. It was during my folks' wedding anniversary celebration up in northern New Hampshire and all I had with me was a little two meter Handie-talkie. There I was, sitting in the back seat of someone else's car trying to explain amateur radio to an aunt I hadn't seen in twenty years. I talked about working DX and then got into describing repeaters. She heard what I was saying, but it obviously wasn't making much sense.

I pulled the little HT-220 out of my jacket pocket and turned it on... silence. Hmmm, not so good. We were driving through the White Mountains about 50 miles from WIKOO in northern Vermont... could I make it? I flicked the button and the squelch-tail came back on cue. I announced myself on channel and hoped. Back came a VE2 mobile in Montreal! We talked for about five minutes and the effect was most positive. She was impressed. So was I, to be truthful. I wasn't at all sure I would be able to get through from the back seat of a car with a little two watt Handie-talkie over that difficult path. Needless to say I rested on my inflated laurels and didn't go on to prove that the contact was a fluke that might be difficult to repeat.

Thin 73 This Month?

We appear to have been taken to the cleaners by three of our trusted Massachusetts advertisers to the tune of an amount about equal to two complete issues of 73. This is not only frustrating since they ignored our suggestions for improving their advertising, but we bent over backwards to help them and got nothing for our efforts. We will have to cut back a little on the thickness of 73 for a month or two to make up for this royal rip-off.

...Wayne

**HELP STAMP OUT
MENTAL HEALTH
SUBSCRIBE TO 73
NOW**

ou goons don't ever proofr
lousy man scrips from bab
bunch of trocks preening an
you ignored my comments in
LETTERS
I insist that you print ev

The VU9KV DXpedition was organized by me in April (12th to 21st) and I was at Port Blair in Andaman Islands for 225 hours. During this time I must have been QRV for approximately 170 hours allowing for sleep(?) times, mealtimes and the times when the power was off or voltage too low (160) for the relay to operate (Surprisingly the FTDX works at even such low voltages as long as it is upside down and I have a pencil to push the relay!). During that period I made 4661 contacts mostly on 10, 15 and 20 meters. Had just a few contacts on 40 and 80 meters. Conditions were extremely poor, but I was glad that I was able to perform better than the other expedition that was being operated at the same time. Fortunately the band conditions were not too good during some part of the daytime and we were able to see some of the picturesque countryside and take some pictures. The XYL was also there for moral support and enjoyed the holiday. The QSL business was very ably handled by Clyde W6KNH.
**Venkat VU9KV
New Delhi**

I just received my copy of October 73 and was surprised that you published the article on page 79 by WA1FBH entitled "Back to mother earth the easy way." I have seen this type of article many times in the past, and if you only wanted to get the pipe into the ground this is okay, but if a good earth ground is what you want, then this is about the poorest one you could get.

No doubt the article was written in good faith, but you will find if the pipe is say 1/2 inch in diameter that you will end up with a hole in the ground about 1 inch or more in diameter and the pipe swinging in this only making contact a few inches at the bottom.

I have been an electrical worker all my adult life and in our work a good earth ground is often important. If you wish to test your ground take the XYL's electric iron and your ac meter (accuracy here doesn't matter so much) plug the meter into a duplex outlet and read the voltage, then plug the electric iron in the other of the outlets on the duplex outlet, read the voltage and make a note of the drop in voltage.

Now take a couple of pieces of wire (number 14 or larger) long enough for one to go to your ground rod, the other long enough to reach an ac outlet. Put a duplex outlet on these

two wires, fasten the one wire securely to the ground rod, then plug the other wire into the "HOT" side of the duplex outlet furnishing the current. Now use the duplex outlet you put on the two wires and make the same test as above using the ac meter and the electric iron.

If you get as many as two times as many volts drop in this last test as the first, you have a very poor ground.

**Harold D. Mohr K8ZHZ
Gahanna OH**

Have been waiting some time to read in the letters column something about the cover on the July issue of 73. Noticed a letter from a Texas ham offering to send you a Texas plate. I felt sure, by now, that someone would question the W6 plate from the state of Tenn. which I believe is the fourth call area, also holding fourth in a prominent position on the front cover of July 73. Anyway: Love your mag; read each copy over several times, even read the ads. Someday, please, how about some articles ABOUT FAST SCAN TV?

**Harry E. Neff W9UBF
Anderson IN**

Out of call area plates are particularly treasured. Though I am not a license plate collector, other than call plates, I do want to thank everyone who has kindly sent me plates. We will be metalling the barn wall with them... and hope someday to have enough for another picture. ATV? Come on fellows, let's see some articles on using the new ICs for TV.

Your magazine has gone VHF and I am not interested in the high meter bands. I do, however, like the books on the lower bands as those are the ones I work. The VHF equipment costs, the lack of range, the lack of CW, the FM, etc., just do not appeal to me.

**Thomas Piepenbrink WA9SRB
Fort Wayne IN**

Tom, what does it take to please you? In looking over the last few issues, in August there was not one single VHF article. In September there was ONE VHF article. In October there were only THREE! Now that comes to a total of four out of 47 articles, or less than 10%. Is it possible to please you? Being honest, it must be admitted that we have been underplaying FM and VHF a little for the last few months to bring the magazine back into balance and that the per-

centage of VHF will most certainly be higher in the coming months than it has been recently. Tom, you could do a lot worse than visit your local distributor and just listen in to the activity on the Fort Wayne repeater. Hundreds of amateurs are having the time of their lives with this, so don't sell it short... particularly without even looking into it. It does NOT have to be expensive at all. I like the low bands and would never give up my low band fun... but I am having a fantastic time on FM and I feel deep regret when I am unable to even get someone to try something that I find so much fun.

In the last few issues of 73, and in numerous issues of other ham publications, there has always been reference to the CB problem. We all know there IS a problem, and it is, in my opinion, definitely a threat to the existence of amateur radio, at least as we know it today.

I work for an electronics retail outlet, handling CB radio, along with stereo equipment, here in Dover, Delaware, and therefore am in daily contact with the CB world. For this reason I feel somewhat qualified to discuss them.

Needless to say, I am 100% against relinquishing any amateur band for use as a CB band. It happened once before, and anyone who cares to take the time to look, can see it was one tremendous mistake on the part of the FCC. It did not result in more hams, more legal CBers, or any other benefits to anyone but the electronics manufacturers. How can anyone, especially anyone who ever listens on the CB band, suggest that to give the CBers a legal "hobby license" is going to improve their operations, or is going to result in anything but double jeopardy?

I notice in literature from Antenna Specialists, they push the EIA proposal to allocate 146-148 MHz to CB hobby operations. While this newsletter is not up-to-date on the 220 Mgz proposals, it certainly shows where the amateur stands in relation to large antenna manufacturers. Shall we create even more of a market for CB equipment, further forcing the prices and availability of amateur gear out of our reach?

Here in this area the tremendous amount of illegal operation amazes me. I know of several companies using CB radio legitimately, say, five or six. The balance of the local CBers seem to have no idea of the content of the regulations, let alone have the desire to follow them. This includes the local REACT operation, with which I am familiar. I know personally several "good citizens" of the REACT, running linears, 40 foot towers, etc., in REACT operations. They say they have to have the linears in order to get through in times of emergency. Possibly true, but comparable to my stating I have to drive 60 miles an

hour in order to get through the local residential areas in self-defense, because a few others are. Bull. I sincerely doubt I could find 20 people in the Dover area who use CB radio as intended. How many are in the area? I don't know, but from my store window I can see 5 CB ground planes in one housing area of about 30 houses.

A week ago, a customer asked me for an rf wattmeter. I said sure, we had a real nice one, good for up to 15 watts. He laughed, saying he needed one to read 3000 (yes, three thousand) watts. Another wishes to trade his 300 watt (output) linear on a high-power one. They don't like our standard line of antennas, because they arc and melt at over 500 watts of rf. If this was the kind of customer I got once a month, or even once a week, I would be impressed with the integrity of CB radio, for I know of a few hams also running, 5, 10 or more kW. But this is the kind of customer I get once or twice a day on a slow day, and more often on busier days.

What is the solution? Can the FCC move CB to VHF where it belongs? I doubt it. Many do not have licenses, 98% do not use them (they just use pseudonyms - Poptart, Dumbell, Sandbox), and would pay zero attention to any FCC ruling saying "Ok, boys, be good and move up to VHF." Therefore, a reallocation of CB to VHF would result in two Citizens Bands, one legally allocated on VHF (but probably illegally used) and the other illegally retained by the ones who don't give a darn.

One solution would be to move them, and immediately reallocate 11 meters to international broadcasting, military point-to-point wideband multiplex, facsimile, multikilowatt AFSK, etc.

Another solution, one which might in the long run benefit amateur radio would be for special permission from the FCC for technically qualified amateurs, preferably holders of high class amateur and commercial tickets, possibly retired, who have the equipment, to act as volunteer monitors for the FCC. As most of us are aware if we sit and tape a conversation on CB and send it to the FCC, it is not admissible as evidence. But, for this special group of amateurs who wish to see amateur radio continue, they would be acting as official FCC monitors, on a voluntary, non-paying basis, and tapes and other evidence made by them would be acceptable to Federal authorities. This would cost the FCC nothing (one of their hang-ups), would multiply their monitoring manpower and efficiency tremendously (again at no cost) and would increase the chances of survival for amateur radio.

I would invite comments on this second solution, as to whether it would seem feasible to the majority of concerned amateurs, and be worthy of drafting into a formal proposal to the FCC. If worthy, I would gladly relinquish any "copyright" and hope

someone with the knowledge of legality and formal governmentese would draft and submit it.

I know of a couple of amateurs in the Dover area who would qualify (and I am not one as I do not have a commercial license), so I am sure there must be many in larger areas.

Opinions?

Ed Brooks Jr. W3GAB
Felton DE

The choice on 220, as I see it, is either you lose a good part of it to CB per the EIA proposals or else you share part of it with a hobby licensee. Which would you prefer, complete loss or sharing? I see no parallel between possible 220 use and the mess on 11 caused by skip operating and regulations which make almost every operator illegal. But, it's your choice... which do you like best?

Dear Wishy Washy Wayne Green, Anybody who prints the pages right instead of sideways can't be all bad! Let's get those other improvements implemented. 2m FM? Why? It's expensive, you get only one band, coverage is limited, you can't get anyone to talk to you on repeaters, costs a bunch to put up your own repeater, and try and use someone else's repeater while mobile.

XX

The above letter arrived unsigned, but I know who it's from... the postmark gave him away. The postmark was "Northern Virginia." How about that? What else but your favorite and mine, the CIA? Who else could have such a ridiculously ambiguous address. And who in the CIA but an old ham-Mensa buddy of mine named Brad would write such complete hogwash? Lordy, when you can buy a brand new transceiver for under two bills (like the Drake TR-22) and have an absolute ball, or even go the used Motorola route for less, they sure must not be paying much to the CIA agents these days. With his crummy attitude I don't doubt for a minute that the fellows in Washington across the river there won't let him into their repeaters. Good going, men, keep those cloak and daggers in their compound and let them put up their own repeater with a super secret tone burst entry. Considering the crowds on 2m FM these days, who needs another band? I have all I can do to keep up with the FM scene. Oh, I come down for some choice DX now and then on 20m, but the excitement is on 2.

73 is usually several months ahead of local info on the IC scene.

We have in operation at the moment a repeater on Mt. Tambourine with an input of 146.1 and output of 145.6. This gives us coverage of Brisbane and the Gold Coast extending into northern VK2.

146.0 is our main working frequency for simplex.

Graham Nixon VK4ZZG
Brisbane, Australia

David Morgan K6DDO
4747 Ambrose
Hollywood CA 90027

Convert Your 7 MHz Cubical Quad To All Bands

Why let your quad limit you to one band? This is one antenna that can be adapted to multiband operation.

160 Meters

Let's start with 160 meters, since nobody ever heard of a rotatable quad on that band. Theoretically, it should be quite feasible to put the quad on 160. It would be likely to even have 2 to 4 dB of forward gain. Once you have built the large supporting structure it would be very easy to try 160. Here is how to do it. The boom length on the quad is 30 ft or so. On 7 MHz the boom length is about 0.22 wavelength. On 3.5, this would give about 0.1 wavelength spacing and on 1.8 about 0.05 wavelength spacing. At this spacing the antenna will be very sharp in frequency response and should be tuned to a spot frequency. However, it will still work and should display considerable advantage over

the usual arrays. Generally about 0.1 wavelength is commonly used in close-spaced arrays.

For loading purposes, four coils of 3 or 4 in. diameter with about 4 to 6 windings per inch should be inserted in the center of the tops and bottoms of the element. (See Fig. 1.) The coils can be tapped and adjusted to tune the elements. The coil at the top of the element should be the same length as the one at the bottom. This will prevent imbalance.

The gamma match might be 15 to 20 ft long on 1.8 MHz; thus, the coils will have to be placed down toward the tips of the bottom wire. This can be worked out experimentally. The rule is to use the same number of turns on each of the two coils as close as you can get it. Also they must be the same distance from the center of the element. As you add one turn on the left coil, add one turn on the right coil and two

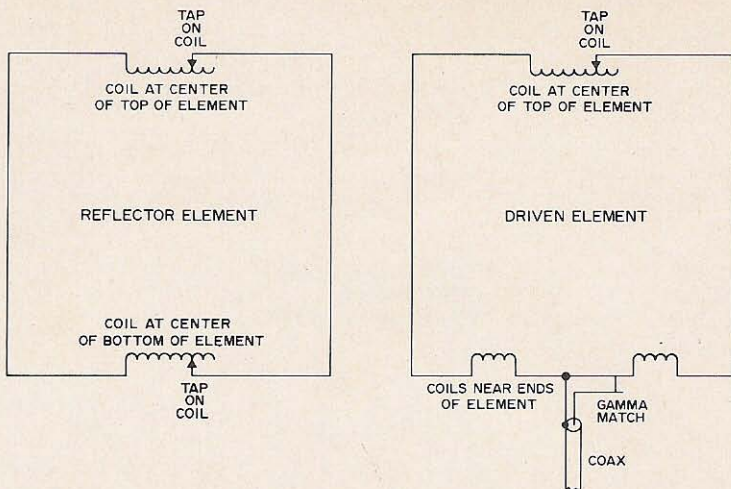


Fig. 1. Quad configuration, reflector and driven element.

turns on the coil at the top of the element. This way the array will stay in balance. There are other ways to accomplish the loading, but this is presented to give you the idea rather than an ultimate solution. Use a gamma match to feed the array. The electrical length of the reflector will probably be about 1.05 times that of the driven element. To tune the antenna first adjust the driven element coils and gamma to resonance at the desired frequency and then adjust the reflector coils for maximum gain or maximum front-to-back ratio.

80 Meters

If you can build a 160m quad then 80 should be easy. It is only a matter of loading. Use the coil system described for 160 but with less turns. The coils for 80 and 160 should be of rather heavy wire and widely spaced to prevent arcing under power. Long coils will be better and the diameter should be as large as convenient. The gamma match may come out around 10 ft long. The spacing of 0.1 wavelength is quite standard and will give excellent results.

20 Meters

From looking at the photographs of the original quad from which the multiband

one was derived (73, May 1967, pp 26-31), you will see that the boom has four spiders on it. It is a simple matter to add four more pieces of element and have the entire support system for a 4 element 20m quad. The standard procedures can be used with standard measurements.

An alternative method to the standard 14 MHz quad is to add arms on the two spare spiders in the center of the boom and build a 4 element extended quad antenna.

Some of you are familiar with the K6CT crossed yagis. What George discovered was that you could mount two multielement yagis on one boom at right angles to each other and get a diversity effect and enhanced gain. Now you will notice that in the 7 MHz quad article previously referenced there is about 30 to 36 ft of aluminum in the center of each of the quad element supports. These are actually parts of 4 element beams for 14 MHz. The inner two elements can easily be added to effectively yield considerable gain. There should be virtually no interaction with the 7 MHz elements. To build it, just add a driven element in the center and another parasitic element. The spacing of about 7 ft between elements is about 0.1 wavelengths.

15 Meters

The 15m band is easy. Use the inner

spiders and build a 4 el quad. The spacing is wider than 14 MHz but still quite workable. You could also put in some 15m yagis. You could also build an 8-element quad on 15 in the configuration shown in Fig. 2.

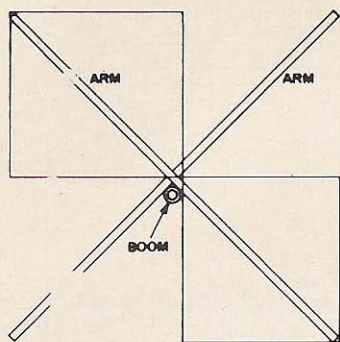


Fig. 2. Cross section of one spider and elements.

10 Meters

After all this you should have lots of ideas for 10. You can use any of the preceding and in addition you might try a quad-quad. This would give 16 elements or 28 elements with no more supporting structure than already described. A cross section of one spider is shown in Fig. 3. If you use four spiders like this you will have a total of 16 elements. However, on 10 meters the quad will have 0.2 wavelength spacing, which is sort of wide; this permits you to add three more elements between the existing four. There is no need to add more spiders because if you are clever you

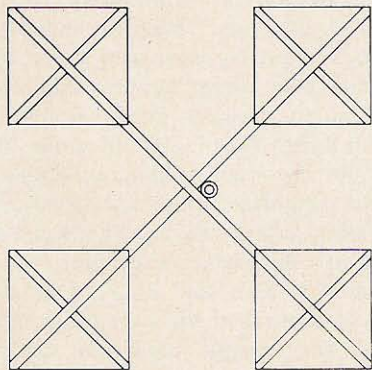


Fig. 3. The 28 MHz quad-quad.

can hang the extra ones on nylon cord in between, taking care to get the spacing right and avoid wind movement. This 28 element quad on 28 MHz would really put out a signal.

The cross arms are not actually needed as the elements can be tied back with nylon cord.


All Bands

What is a simpler way to put all bands on the quad? The methods mentioned work best for high gain on one or two bands since the elements get in the way of each other if you try to add too many fancy arrays. For all bands it would be advisable to use straight quads on 28, 21, 14, and 7 MHz with four elements on the three higher bands and two elements on 7. 3.5 and 1.8 would be connected electrical-ly by switching a relay.

Here is another idea for all bands. Suppose you buy two very strong oversize triband beams with sturdy elements. Then you mount them on the 4 in. boom and extend the tips of the four end elements with fiber glass or bamboo to 54 ft each. Hang your quad wires on for the lower frequencies and you will be ready to go. You would have a K6CT design for 14, 21, and 28 and a quad on 7. It might be necessary to build your own tribander to do this, since the commercial ones would not be sturdy enough. You can still add the coils for 1.8 and 3.5. What would be more practical on 3.5 and 1.8 would be to use traps in the quad elements and a multiband gamma with three gamma matches in parallel to cover all three bands. If you were to get a set of those traps used in trap dipoles you could probably work it out — maybe adding a few more coils as needed, here and there.

Switching

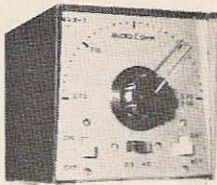One of the ways to handle the feedline and switching problem is to use a stepping relay such as used on TV antennas. I took one of these and rebuilt it with coax leads inside it and it has worked out well on control switching of quad feedlines. One line runs to the shack. The relay has four positions and there are four feedlines pos-



NOVICE DECLARATION OF INDEPENDENCE

We the People of MicroComm,
recognizing the **inalienable right** to **QSY**,
freedom to work DX and **independence**
to throw your crystals away, **do ordain and**
establish the Novice NVX-1 Variable Crystal
Oscillators. Fully approved by the **Constitu-**
tion and the F.C.C.

The NVX-1 works like a V.F.O. with your XMTR.

Coverage: 3702 - 3748 KHz

7152 - 7198 KHz

Declare your Independence and order today at the Intro-
ductory Price \$39.75, p.p.d., wired. Guaranteed and certified
for one full year. California residents add 5% sales tax.

FEDERAL COMMUNICATIONS COMMISSION

WASHINGTON, D. C. 20540

May 3, 1971

7324

Mr. James D. Shadlin
MicroComm, Inc.
P. O. Box 373
Berkeley Beach, California 90234

Dear Mr. Shadlin:

This is in reply to your letter of January 29, 1971, in which you
included a detailed test report on the performance of your proposed variable
crystal controlled transmitter for Novice Class amateur radio operation.

On the basis of the constructive test results submitted regarding the opera-
tion of the 3702 and 7152 Model Class amateur variable crystal controlled
transmitters, the equipment appears to be acceptable for licensing in con-
formance with Section 97.17(a)(1) of the Commission's Rules. Acceptability
is limited to factory assembled equipment operating in the 30 and 20 meter
Novice Class segments of the amateur band and each transmitter produced
shall carry on the chassis the warning forbidding unlicensed tampering
with the unit.

Sincerely yours,

J. E. Beer
James E. Beer
Chief, Safety and Special
Radio Services Bureau

Available ONLY factory direct from:

MicroComm

"... the birthplace of new ideas
in Novice Communications"

BOX 373

CUPERTINO, CALIF.

95014

sible to different antennas. Quite often the feedline of a second band can be ignored or phased out and a short length can be left in place with a relay 10 or 20 feet away. This is a matter for experiment with regard to the 3.5 and 1.8 MHz coils. The trap system might be the best for these low bands but what set of traps and coils to use if you try it is left to experiment. The point is that unwanted things can be disconnected with traps.

Feeding

Feeding a group of these antennas may be a problem. The standard types of matches will work well. But if you want to drive both a quad and a yagi on the same boom and same band this may be a situation requiring some thought to get the right impedances and good power transfer. I have found that gamma matches give the best feed for quads although many people don't use them. The idea of using coax baluns and calculated impedances does not give precise matching due to the reflections of nearby objects. It does work as a first approximation. The more bands and ele-

ments you add to the array the more important it is that you can tune and measure every part of the antenna.

Conclusion

What I have done is to give you some ideas that I hope will enable you to come up with some more interesting antennas and better use of a large supporting framework. The final method has not been described for there must be something left for experiment or we would not be doing much as amateurs. There are endless possibilities to getting more gain out of antennas and in a recent conversation with a professional antenna design engineer he told me that they could use some better ideas for the space tracking program. One of the important unsettled questions is how many arrays can actually be gotten to work on a design such as we have. Can you somehow cheat and squeeze in a few more elements and still raise the gain some more? Most people think you can't but they are the source of a new frontier.

...K6DDO■

The Indoor Quad

Ray Kasprzak K9RJO
4958 West Potomac Ave.
Chicago IL 60651

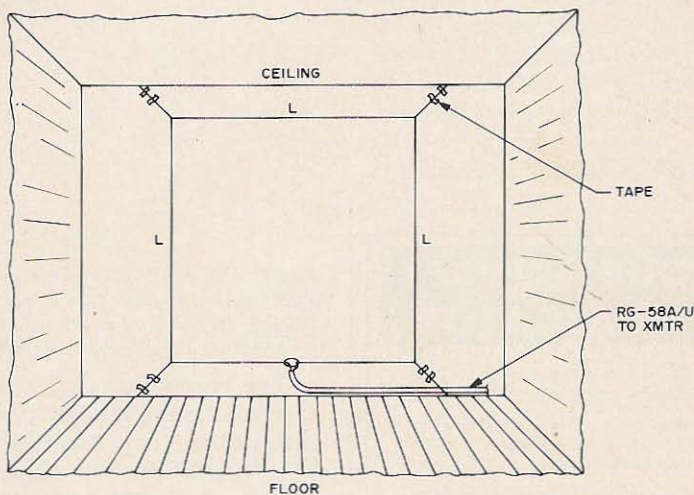


Fig. 1. Tie string at the corners and then tape to ceiling and floor. $L = \text{approx } 251/f(\text{MHz})$. I wound up with 8 ft 2 in. for each side after trimming for minimum swr.

After spending several hours on 15m with everyone telling me of the excellent openings on 10m, I decided to see if I could get some rf out on that band.

Being an apartment dweller, and having spent the entire summer erecting an inverted vee on the roof, I had my doubts as to whether or not my landlord would look kindly on my spending the winter putting up another antenna. (I would undoubtedly

be seeking permission to erect an antenna on top of the local Salvation Army Hotel had I made another trip to the roof.)

That's when I decided to try an antenna inside the shack. First I thought of trying a dipole, but since a dipole doesn't really do much for my low-power signal even when the dipole is outside, I dismissed it. My next idea was a quad and looking around the shack I found that my ceiling was 8½ ft

SPACE-AGE TV CAMERA KITS & PLANS



BE A PIONEER IN HOME TELECASTING! Build your own TV CAMERA. Model XT-1A, Series D, \$116.95 pp. Solid-State. Step-by-step construction manual. High quality. Connects to any TV without modification. Ideal for hams, experimenters, education, industry, etc.

PHONE or WRITE for CATALOG.

DIAL 402-987-3771

Many other kits, parts and plans available including starter kits, focus/defl. coils, vidicon tubes, const. plans, etc.

1301 N. BROADWAY

ATV Research

DAKOTA CITY, NEBR. 68731

high. Using the standard formula $L=251/f$, I made the driven element as shown in Fig. 1. I used string tied at the corners and taped the element to the ceiling and floor with the whole thing about 4 in. from the wall. Next, I made a similar element for the reflector and placed it $6\frac{1}{2}$ ft opposite the driven element (Fig. 2). I hooked up a 10 ft length of RG-58 to the driven element, and found I had an swr of 3:1. By trimming the driven element, I managed to

reduce this to 1.4:1. It's easy to keep the sides symmetrical by slipping the wire through the string. The string can be taped in place after trimming the antenna.

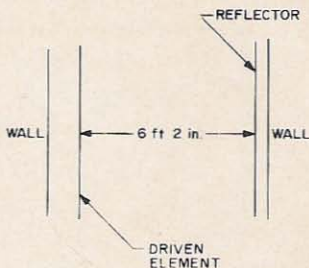


Fig. 2. The distance between the 2 walls of my shack was very close to the distance for optimum spacing. If you have room, you may experiment by trying various distances between elements.

The results were just a little short of amazing. During the first operating session with this antenna, I worked LUs, an HC, PY, 9Y4, XE and VE8. Signal reports were anything from S6 to S9+. I also worked a dozen W6s. Almost everyone said the band was on the poor side, and my signal compared favorably with others from the same area. The rig used was an HW-100.

The reflector is tuned to a frequency lower than that of the driven element. If you choose to have a director rather than a reflector, you should tune the element to a higher frequency than that of the driven element.

When switching from my inverted vee to the indoor quad, there is a 2 S-unit increase on the quad in all directions.

Incidentally, my operating position is right between the elements of the antenna.

...K9RJO

FM YOUR GONSET COMMUNICATOR

- New! Plug-in modulator puts the Communicator transmitter on FM.
- No modification or rewiring of your Communicator. Just plug into mike jack and crystal socket.
- Compact self-contained modulator measures 4" x 3" x 1½".
- Works with Communicator I, II, III, and IV.
- FM at a tenth the cost of a new rig.
- Frequency adjust for netting built in.
- Built-in tone burst available. Keyed by push-to-talk switch.
- \$34.50 postpaid U.S.A. Built-in tone burst \$10.00. Specify Communicator model and tone-burst frequency. 5% tax in California. (HC-17/U crystal and 9 volt transistor battery not supplied.)
- Send for free descriptive brochure.

PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025

Getting to know

TEE SQUARED ELL

The early RTL families of logic integrated circuits have been utilized for many ham-type circuits encompassing everything from rf amplifiers, oscillators, and other linear-type circuits to digital circuits for which they were originally intended. However, the commercial/industrial demand for RTL circuits has been on the downhill slide for the past few years so the availability, price, etc. are not as attractive as they have been; moreover, no new and exotic circuits have been added to the RTL families. But don't despair — get HEP with TTL, because this is where the computer industry demand is. And when you have big demand, you have high volume production which means low prices. In addition, you can do everything and a little bit more with TTL that you could do with RTL — and you can do it better, because TTL has much higher frequency capabilities. In fact, TTL is the fastest form of saturated logic made. MECL circuits which operate at higher frequencies are nonsaturating devices.

The basic gate of all TTL families is the *nand* gate; this is because all logic functions can be synthesized with only *nand* gates. A typical TTL gate circuit is shown in Fig. 1, and the typical transfer characteristic (input vs output voltage) is shown in Fig. 2. When all inputs are logic 0, the output is a logic 1. When all inputs are a logic 1 the output goes to a logic 0. Note, however, that the device goes through a linear region as it makes its transition from logic 1 to 0. By biasing gates in this linear region they can be used for amplifiers and other nondigital applications.

Notice from Fig. 2 that the permissible input voltage range for a logic 1 output is only a few tenths of a volt. This makes TTL a little more sensitive to stray voltages

(noise) than RTL. It is possible that with power applied (pins 14 and 7) and with pins 1 and 2 open (or any of the other gate inputs) that pin 3 would *not* provide a logic 1 output (it would be at 0) because of stray voltage pickup. Grounding both gate inputs immediately produces a logic 1 output. So, don't attempt to use TTL gates with the inputs left open or you will have problems. In normal operation, the gates would be connected to another device which would provide the permissible input levels.

Basic Functions Using *Nand* Gates

Since we indicated before that the *nand* gate is the universal logic element of the TTL family, let's start out by showing how six basic Boolean functions can be implemented with *nand* gates. These are shown in Fig. 3. Some additional basic applications for *nand* gates driving discrete devices are shown in Fig. 4. Several of these circuits use the HEP-C3001P which is a slight variation from the basic *nand* gate in that it has open collectors which permits increased versatility. See Fig. 5. Note that the output transistor's collector must be connected to V_{cc} through a resistor, bulb, etc. As shown in Fig. 4, the open collector gate is ideal for driving SCRs, the new light-emitting diodes, and low-voltage, low-current incandescent bulbs. These last two items are often used as readouts in frequency counters.

Note: In all of the circuits shown, the V_{cc} and ground connections (pins 14 and 7) are omitted to simplify circuitry.

Pulse Shaping and Generating

Pulse shaping involves forming a train of square waves from any periodic wave. If the original waveform is relatively fast, 1 kHz or faster, the circuit of Fig. 6 can be

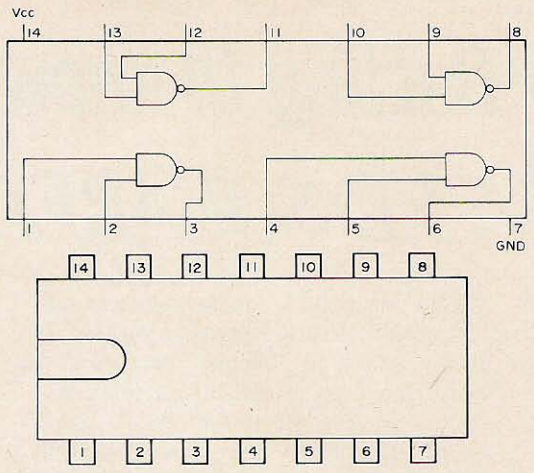
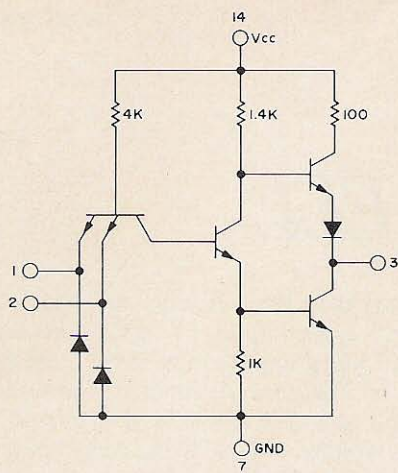


Fig. 1. Typical TTL gate (¼ of HEP-C3000P).

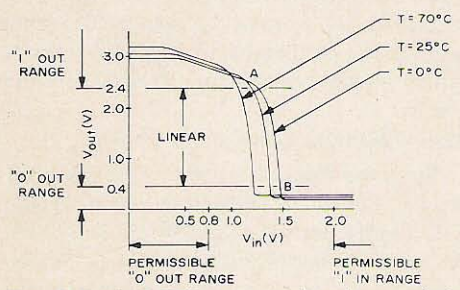


Fig. 2. Typical TTL gate transfer characteristics.

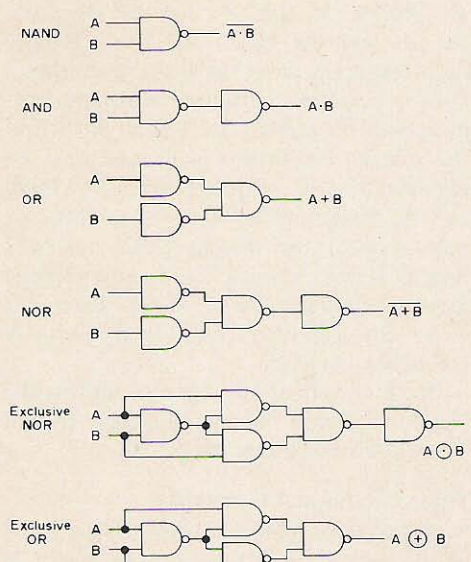


Fig. 3. Six basic Boolean functions as implemented with a NAND gate.

used to provide good square waves. Slower waveforms need the regenerative Schmitt trigger shown in Fig. 7. The accompanying table in Fig. 7 shows how the threshold voltages change with different values of R_F and R_{in} .

If the system already has an input square pulse, but of short duration, a wider pulse can be generated by using the input pulse to trigger a one-shot such as shown in Fig. 8. The chart gives values for C and R so that you can estimate the pulsewidth time in nanoseconds.

A square-wave generator with a fast risetime can be fashioned by connecting the HEP-C3001P as shown in Fig. 9. This is a ring oscillator with the external capacitor and load resistors controlling the frequency of oscillation. Frequency of operation for various values of R_L and C are given in the accompanying chart.

How To Linearize TTL Gates

The HEP-C3000P TTL gate can easily be turned into a linear amplifier; all you do is add some feedback. This is achieved by adding a 560Ω resistor between output and input, and a small resistor of about 220Ω in series with the input. This is shown in Fig. 10. The 560Ω feedback resistor biases the gates so that approximately 1V is provided at the output, which is in the linear region. A slightly smaller resistor will raise the output voltage level and a larger

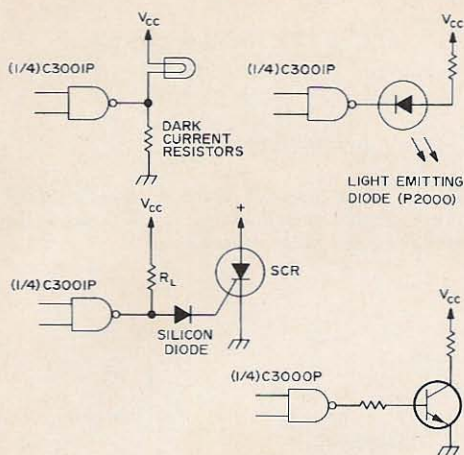


Fig. 4. Representative circuits of TTL gates driving readout lamps, SCRs and other discrete devices. The gate inputs would be connected to flip-flop or some other type of device to provide proper input levels.


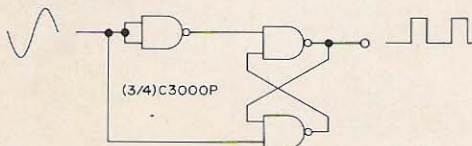


Fig. 6. Pulse shaper.

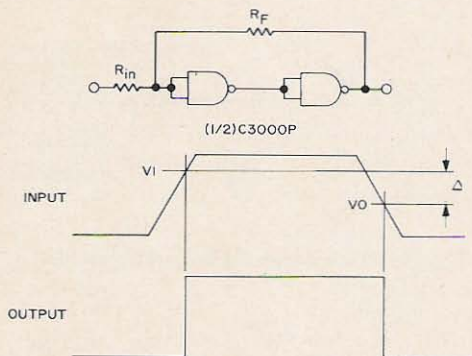

R_{in} (Ω)	R_F (Ω)	V_I (V)	V_O (V)	ΔV (V)
300	4.0K	1.07	0.84	0.23
300	6.0K	1.04	0.89	0.15
500	7.5K	0.94	0.73	0.21
500	10K	0.94	0.77	0.17
500	15K	0.93	0.83	0.10
1.0K	7.5K	0.77	0.32	0.45
1.0K	10K	0.74	0.41	0.33
1.0K	15K	0.71	0.48	0.23

Fig. 7. Schmitt trigger.

resistor (680Ω) will reduce output voltage to about 0.8V. With this simple arrangement, the TTL gate can be used as an amplifier for audio, video, and rf. As a broadband video amplifier this circuit provides fairly flat response over a bandwidth

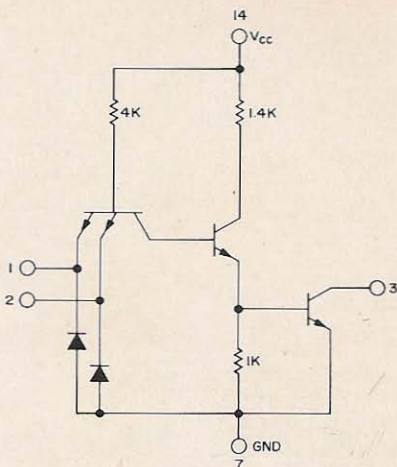


Fig. 5. Typical TTL gate with open output collector (HEP-C 3001P).

well into the megahertz region (around 9 MHz). With tuned circuits, it will provide useful gain to 30 MHz and beyond.

Two linearized gates connected in series provides a 360-degree phase shift which makes a perfect oscillator arrangement. As shown in Fig. 11, a crystal can be connected in a second feedback loop around both gates to provide an oscillator operating at the crystal fundamental frequency. This oscillator is good for use with crystals in the 1–20 MHz range.

A low cost square-wave generator that can operate from low audio frequencies up to rf in the 12 MHz range can be fashioned as shown in Fig. 12. The frequency of operation is controlled by C1 and R1. For fixed values of C1, the potentiometer can adjust frequency over a decade range.

Frequency Counters

The most widely used digital circuit is the flip-flop used as a counter. So, to provide a ready reference for all count functions from 2 through 10, we have developed the circuits in Figs. 13–21. Since the big reason for using TTL circuits is their improved speed over RTL, these are all synchronous counters. Synchronous counters require a number of interconnecting gates, but they are much faster than the ripple counter, which usually does not need the gates. The HEP-C3073P is a

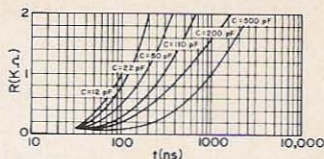
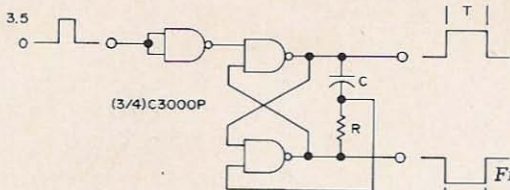


Fig. 8. TTL one-shot used to develop wider pulses. Chart shows values for C and R for various output pulse widths.

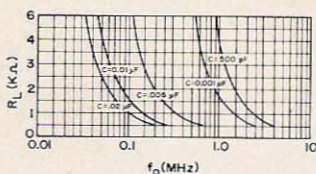
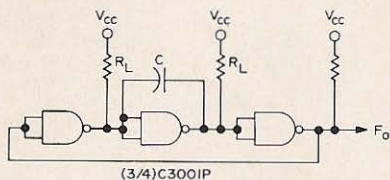


Fig. 9. Square wave generator (Ring oscillator). Frequency is determined by R_L and C as shown in the chart.

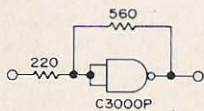


Fig. 10. How to linearize TTL gates with a feedback bias resistor.

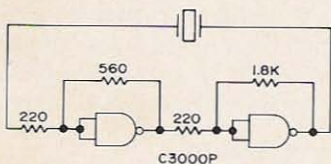


Fig. 11. Crystal oscillator using TTL gates.

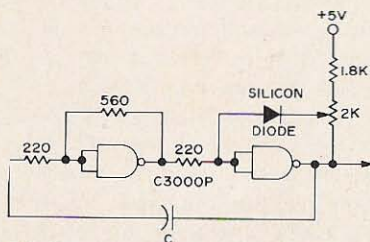


Fig. 12. Square-wave generator will operate over a wide frequency range from audio to RF. Capacitor and pot controls frequency.

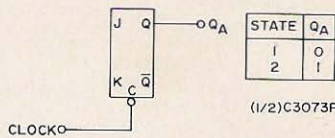


Fig. 13. Synchronous divide-by-2 up-counter.

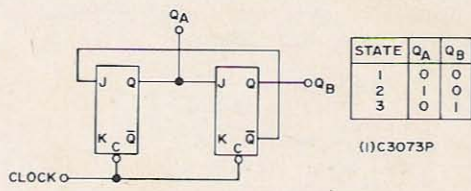


Fig. 14. Synchronous divide-by-3 up-counter.

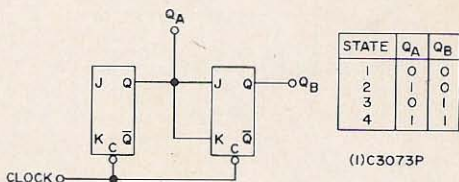


Fig. 15. Synchronous divide-by-4 up-counter.

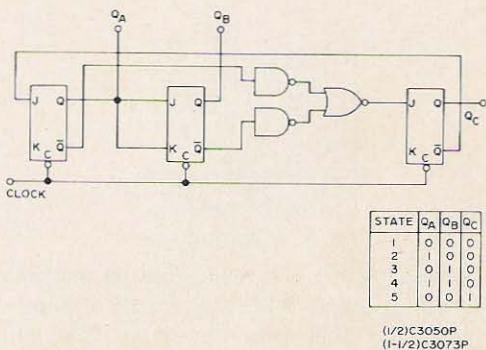


Fig. 16. Synchronous divide-by-5 up-counter.

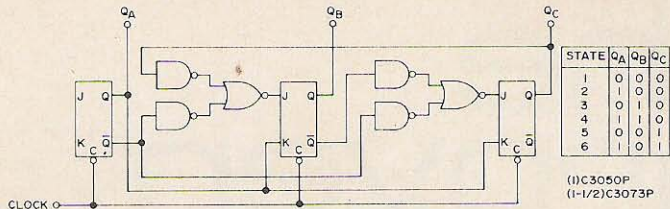


Fig. 17. Synchronous divide-by-6 up-counter.

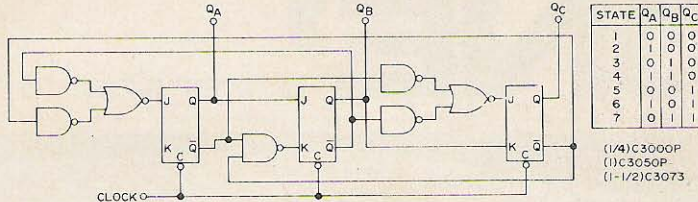


Fig. 18. Synchronous divide-by-7 up-counter.

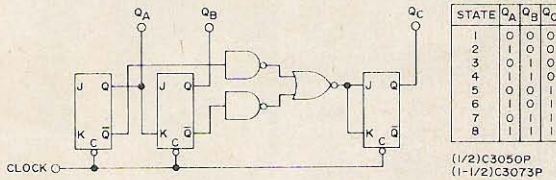


Fig. 19. Synchronous divide-by-8 up-counter.

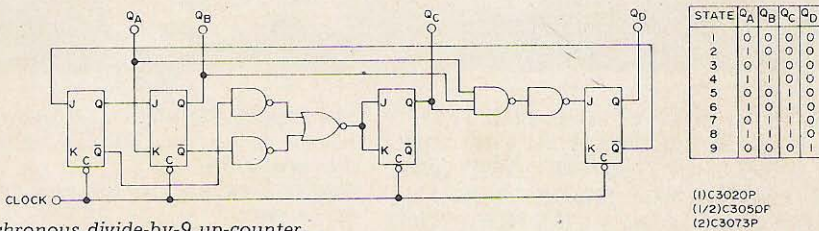


Fig. 20. Synchronous divide-by-9 up-counter.

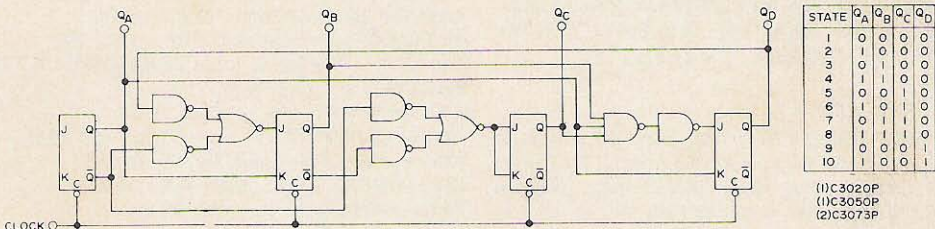


Fig. 21. Synchronous divide-by-10 up-counter.

dual JK flip-flop that triggers at frequencies up to 20 MHz. The HEP-C3050P is a dual 2-input *and-or-invert* gate.

All of the counters operate as follows: The counter starts in state 1 where all flip-flops are at zero. With each negative transition of the clock pulse, the counter steps to the next state in its table. From

the last state in the table, the counter cycles back to state 1. The frequency of the pulses out of the last stage of the counter is equal to the input frequency divided by *n*, the number of states in the table.

...Thorpe ■

Reference: TTL Design Ideas - Motorola Semiconductor Products Division.

the proven 'ONE'

a transceiver by Tempo



MORE THAN A YEAR AGO THE TEMPO 'ONE' WAS INTRODUCED TO THE AMATEUR WORLD AS THE NEW 'ONE'. NOW WITH THOUSANDS IN USE IT'S THE PROVEN 'ONE'. LOOK AT ITS PRICE AND THEN LOOK AT ITS SPECIFICATIONS. ADD TO THIS ITS RECORD OF RELIABILITY AND THE RESULT CAN BE SUMMED UP IN ONE WORD... VALUE.

SPECIFICATIONS

FREQUENCY RANGE: All amateur bands 80 through 10 meters, in five 500 khz. ranges: 3.5-4 mhz., 7-7.5 mhz., 14-14.5 mhz., 21-21.5 mhz., 28.5-29 mhz. (Crystals optionally available for ranges 28-28.5, 29-29.5, 29.5-30 mhz.)

SOLID STATE VFO: Very stable Colpitts circuit with transistor buffer provides linear tuning over the range 5-5.5 mhz. A passband filter at output is tuned to pass the 5-5.5 mhz. range.

RECEIVER OFFSET TUNING (CLARIFIER): Provides \pm 5khz variation of receiver tuning when switched ON.

DIAL CALIBRATION: Vernier scale marked with one kilohertz divisions. Main tuning dial calibrated 0-500 with 50 khz. points. Each revolution of tuning knob covers approximately 15 khz.

FREQUENCY STABILITY: Less than 100 cycles after warm-up, and less than 100 cycles for plus or minus 10% line voltage change.

MODES OF OPERATION: SSB upper and lower sideband, CW and AM.

INPUT POWER: 300 watts PEP, 240 watts CW

ANTENNA IMPEDANCE: 50-75 ohms

CARRIER SUPPRESSION: -40 dB or better

SIDE BAND SUPPRESSION: -50 dB at 1000 CPS

THIRD ORDER INTERMODULATION

PRODUCTS: -30 dB (PEP)

AF BANDWIDTH: 300-2700 cps

RECEIVER SENSITIVITY: 1/2 uv input S/N 10 dB

AGC: Fast attack slow decay for SSB and CW.

SELECTIVITY: 2.3 khz (-6dB), 4 khz (-60dB)

IMAGE REJECTION: More than 50 dB.

AUDIO OUTPUT: 1 watt at 10% distortion.

AUDIO OUTPUT IMPEDANCE: 8 ohms and 600 ohms

POWER SUPPLY: Separate AC or DC required. See AC "ONE" and DC "ONE" below.

TUBES AND SEMICONDUCTORS: 16 tubes, 15 diodes, 7 transistors

DIMENSIONS: 13 1/4"W, 5 1/2"H, 11"D

WEIGHT: 17.5 lbs.

TEMPO "ONE" TRANSCEIVER

\$315.00*

AC/ONE POWER SUPPLY

117/230 volt 50/60 cycle . . .

\$104.00*

DC/1-A POWER SUPPLY 12 volts DC

\$107.00

**Prices subject to import surcharge*

Designing or aligning...now you can afford lab-grade Heathkit instruments

The new Heathkit IO-105 Dual Trace Scope. Triggered sweep, DC-15MHz, x-y mode, 8 x 10 cm flat-face CRT. For a fantastic 399.95*!



New Heathkit IM-102 Digital Multimeter. 3½ digits, built-in calibration to 0.2%, lab calibration to 0.1%. At an amazing 229.95*

The new Heathkit IM-102 is a breakthrough in instrumentation — a true digital multimeter at a price that's about half what you'd pay for comparable wired DMM's! Measures AC and DC voltage, current, and resistance, with automatic switching for DC polarity. Five overlapping ranges show voltage from 100uV-1000V on DC; 5 ranges cover 100uV-500V on AC; 10 ranges measure 100nA-2A, AC or DC; 6 resistance ranges cover .1 ohm-20 megohms. Input impedance is 1000 megohms on the 2V range, 10 megohms on higher ranges, with overload protection on all.

Decimal point is automatically placed with range selection. Panel light indicates over-range.

A Heath-designed DC calibrator is furnished assembled with every IM-102. A unique transfer method, described in the manual, provides accurate AC voltage calibration. All solid-state circuitry incorporates cold cathode readout tubes and a "memory" circuit to assure stable, non-blinking operation. Kit includes standard banana jack connectors complete with test leads. Assembles in approximately 10 hours. Order yours, and step up to digital instrumentation at analog prices.

Kit IM-102, 9 lbs. 229.95*

Kit ID-1041, high-voltage probe accessory, 1 lb. 6.95*



The new Heathkit IO-105 is a true digital multimeter at a price that's about half what you'd pay for a comparable wired unit. Gives you full dual trace and x-y capability. Separate signal display in Channel 1 or Channel 2 mode, direct comparison of both signals in alternate or chopped modes, both signals as a function of each other in x-y. Both input channels are precision balanced for 5% or less phase shift of over 50 kHz. Has switch selected AC/DC coupling; automatic triggering; 18-position time base, 1, 2, 5 from 100 msec/cm-0.2 usec/cm; separate vernier control; 5x magnifier; DC-15 MHz bandwidth with 24 nsec rise time; flat-face CRT with mu-metal shield. The new Heathkit IO-105 expands your capability without stretching the budget, order yours today.

Kit IO-105, 35 lbs. 399.95*

HEATHKIT	
Schlumberger	
HEATH COMPANY, Dept. 11-12 Benton Harbor, Michigan 49022	
<input type="checkbox"/> Enclosed is \$ _____, plus shipping.	
<input type="checkbox"/> Please send model(s) _____	
<input type="checkbox"/> Please send FREE Heathkit Catalog.	
Name _____	
Address _____	
City _____	State _____ Zip _____
Prices & specifications subject to change without notice. *Mail order prices; F.O.B. factory. AM-257	

TEMPO IS
AVAILABLE FROM THE
FOLLOWING SELECT DEALERS
THROUGHOUT
THE U.S.

HENRY RADIO 11240 W. Olympic Blvd., Los Angeles, Ca. 90064 477-6701 • 931 N. Euclid Ave., Anaheim, Ca. 92801 772-9200 • Butler, Mo. 64730 679-3127

ADIRONDACK RADIO SUPPLY 185 W. Main St., Amsterdam, New York 12010 842-8350

ADVANCED ELECTRONICS 804 Dupont St., Bellingham, Wash. 98225 734-3400

ALLIED RADIO SHACK 230 S. Main St., Lombard, Ill. 60148 495-1234

AMATEUR ELECTRONIC SUPPLY 4828 W. Fond du Lac, Milwaukee, Wis. 53216 442-4200

AMATEUR ELECTRONIC SUPPLY 17929 Euclid Ave., Cleveland, Ohio 44112 486-7330

AMATEUR RADIO CENTER 2805 N.E. 2nd St., Miami, Florida 33137 374-4101

AMATEUR RADIO SUPPLY 6213 13th Ave. S., Seattle, Wash. 98108 767-3222

STAN BURGHARDT 315 10th Ave. N.W., Watertown, S.D. 57201 886-3767

COMMUNICATIONS WORLD 4788 State Road, Cleveland, Ohio 44109 398-6363

DERRICK ELECTRONICS 108 E. El Paso, Broken Arrow, Okla. 74012 251-9923

DOUGLAS ELECTRONICS 1118 S. Staples, Corpus Christi, Texas 78404 883-5103

ELECTRONIC CENTER 107 3rd Ave. N., Minneapolis, Minn. 55401 338-8461

ELECTRONIC DISTRIBUTORS 1960 Peck St., Muskegon, Mich. 49441 726-3196

ERICKSON COMMUNICATIONS 4657 N. Ravenswood, Chicago, Ill. 60640 334-3200

ELECTRONIC EXCHANGE CO., INC. 608 Papworth Ave., Suite "B", Metairie, La. 70005, 834-9000

FRECK RADIO & SUPPLY 38 Biltmore Ave., Asheville, N.C. 28801 254-9551

HARRISON Rt. 110 at Smith, Farmingdale, N.Y. 11735 293-7990 8 Barclay St., N.Y. City 227-7922

HAM RADIO CENTER 8342 Olive Blvd., St. Louis, Mo. 63132 993-6060

HAM RADIO OUTLET 999 Howard Ave., Burlingame, Ca. 94010 342-5757

INDUSTRIAL DISTRIBUTORS 1209 S. Industrial Ave., Dallas, Texas 75207 742-8570

JRS DISTRIBUTORS 646 W. Market St., York, Penn. 17404 854-8624

ED JUGE ELECTRONICS, INC., 3850 S. Freeway, Fort Worth, Texas 76110 926-5221

KASS ELECTRONICS 2502 Township Line Rd., Drexel Hill, Penn. 19026 449-2300

MADISON ELECTRONICS 1508 McKinney Ave., Houston, Texas 77002 224-2668

MANWILL SUPPLY CO. 2780 S. Main St., Salt Lake City, Utah 84115

PORTLAND RADIO SUPPLY 1234 S.W. Stark St., Portland, Or. 97205 228-8647

RADIO DISTRIBUTING CO., INC. 1212 High St., South Bend, Indiana 46624 288-4666


RADIO SUPPLY & ENGINEERING CO. 85 Selden Ave., Detroit, Michigan 48201 831-3175

SIMON SIDE BAND CO. Holland Mountain Road, Oak Ridge, N.J. 07438 697-4246

WESTERN RADIO 1415 India St., San Diego, Calif. 92101 239-0361

WORLD RADIO LABS 3415 W. Broadway, Council Bluffs, Iowa 51501 328-1851

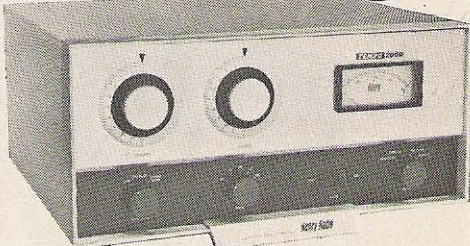an unbeatable value from Tempo...the "2000"



A LINEAR AMPLIFIER DESIGNED BY E.F. JOHNSON EXCLUSIVELY FOR TEMPO

The Tempo/2000 is the smallest self-contained, full-legal-limit kilowatt amplifier in its price range.

- Full kilowatt input on all modes. Grounded — grid input for maximum compatibility with modern transceivers and transmitters. Complete compatibility with most transceivers. Entirely self-contained, solid-state power supply. Instantaneous and silent T-R and Bypass switching incorporating power-reed relays. Self-contained T-R switching for separate transmitter and receiver — operates even with transceiver turned off. Band-switched to cover 80 through 10 meters. Internal dummy-load for exciter tuneup. Smallest desk-top kilowatt amplifier in its price range. Double interlock system to eliminate shock hazard. Circuit breaker power supply protection. Relative RF power meter reads exciter or amplifier power. Operational within 3 seconds from turn-on. All necessary inputs and outputs for either transceiver or transmitter/receiver operation.

SPECIFICATIONS: Power Input: 1000 watts DC on SSB, CW, AM, FM and RTTY — 2000 watts PEP capability for SSB • Duty cycle in all models: 50% at 1KW DC input, 15 minutes 'ON' and 15 minutes 'OFF'. • RF driving power required: 55 watts for 1000 watts in — 85 watts PEP for 2000 watts PEP in • T-R switching: Requires a closed circuit from the exciter in receive and an open circuit in transmit • Final tubes: Two rugged 3-400Z zero-bias triodes • Input: 50 ohms nominal, broadband • Output: Pi-network matches 30 to 100 ohms, minimum, on all bands (80-10 meters) • Internal blower: Provides a minimum air flow of 35 CFM upward around tubes • Self-contained, solid-state power supply: Provides 2500 volts or 1800 volts • Inter-modulation distortion: 35 dB below PEP output at full legal input • Cabinet dimensions: 7" high x 15½" wide x 14" deep

The TEMPO/2000..\$395

More Power from 6146s

E. John Labaj W2YW
12 Park Place
Elmsmere NY 12054

After some checking and minor circuit changes I found that I could run a pair of 6146s (A or B) at an input of 400 mA at a 1000V, and no sweat.

Observation and measuring indicated that some of the problem with the tubes was like one famous TV personality's drinking problem: He knew his limit but he always lost control before he reached it.

Same with the 6146s. Long before the input limit was reached the tube lost control, resulting in plate-current runaway and tube failure.

While the 6146 plate is about the same size as comparable sweep tubes, the 6146 seems more touchy, tending to gas and go into a catastrophic "spin" with very little provocation.

With the average circuit and biasing arrangement the 6146 tube will have about 20 to 30 k Ω resistance, plus the resistance of the bias supply between the grid and ground.

Now, with a minor tuning fluff, or even normal use, especially on the higher frequencies, and with a few loose electrons around, the 1 control grid will act as a cold cathode and set up a reverse grid current flow. This reduces the actual grid voltage from that coming out of the supply, which in turn causes more plate current, and thus more reverse grid current. In less time than it takes to tell about it, this cumulative action has cost you another pair of 6146s.

This is understandable when you see that the potential on the control grid is greater than that between the actual cathode and screen and plate.

To minimize the bucking effect of the reverse current I jumpered all resistors in the grid circuit with small low-resistance rf chokes. This reduced the voltage drop through the grid circuit string under cur-

rent flow conditions, either forward or reverse.

To make sure of a stable bias supply I bought some surplus zener diodes and clamped the bias supply at -82V. This fed the hot end of the bias potentiometer, and then, as close to the actual grid as possible but on the cold (rf) side of the grid feed I used another zener diode which was -68V; this happened to be the value that was needed to set the plate current to normal idling (Fig. 1).

To make sure of getting sufficient peak plate current flow, I jumpered the screen feed resistor so that screen voltage was clamped at 260V. The series feed resistor was 1.2 k Ω ; the B+ supply under load was 310V — this voltage was clamped by using two 10W zeners in series, as shown in Fig. 2.

To discourage the screens from getting into the secondary emission act, I wired in series with each screen lead a 1 kV, 1A silicon diode rectifier.

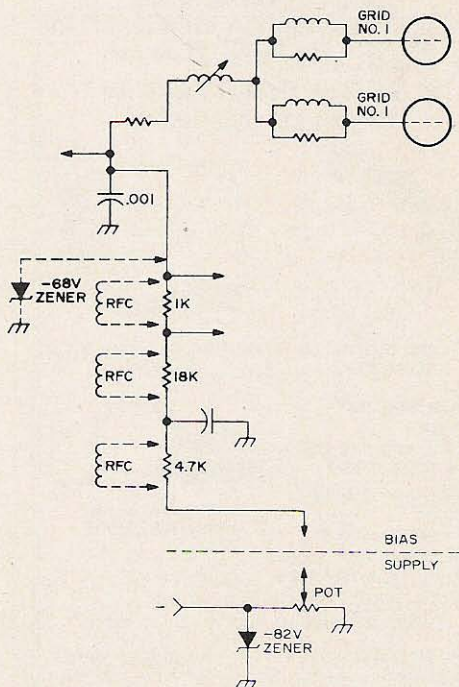


Fig. 1. The addition of zener diodes established a runaway limit. A -82V zener limits the bias output and a -68V zener clamps the grid potential.

72 PIECE TOOL KIT



A new 72-piece tool kit contains everything needed by amateurs, professional repairmen, servicemen, technicians, and field engineers. Each tool stores neatly in its own place in a handsome attache case: all are in clear view and always ready-to-hand.


Included are screwdrivers, pliers, wrenches, an alignment tool, burnisher, crimping tool/wire stripper/bolt cutter, knife, saw, instrument oiler, inspection mirror, spring tool, stainless steel rule, pick/scribe, scissors, tweezers, heat sink, voltage tester, soldering aid, and temperature-controlled soldering iron. Wrenches, pliers, screwdrivers, etc. come in a range of sizes and styles.

The attache case, finished in prestige-quality vinyl, has a lock; it measures 13 x 18 x 4-1/2 inches. A removable pallet in the lid holds many of the tools, each in its own pocket. There is also a pocket for service manuals and schematic diagrams.


K-77 Professional Tool Kit, complete with attache case, is \$139.50. The attache case alone is \$39.50.

Telvac Instrument Co.
14614 Raymer Street
Van Nuys, California 91405

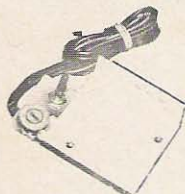AT LAST -- A SPEECH COMPRESSOR THAT REALLY WORKS!




RPC-3,3U Internal Unit
(\$24.95)

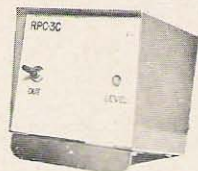

RPC-3C Cabinet Model
(\$34.95)

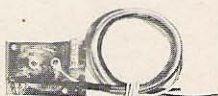- Low distortion circuit.
- Fully wired & tested. NOT A KIT
- Works with phone patch.
- Internal units & modules work mobile.
- FULL WARRANTY — ONE YEAR
- INTRODUCTORY LOW PRICES
(Illinois residents add 5% Sales Tax)



RPC-3M Module
(ONLY \$22.50)

Write for specifications and information sheets (Free). Demonstration Tape (cassette) available (\$2.00 deposit).

RP ELECTRONICS

Box 1201 B Champaign, Ill. 61820

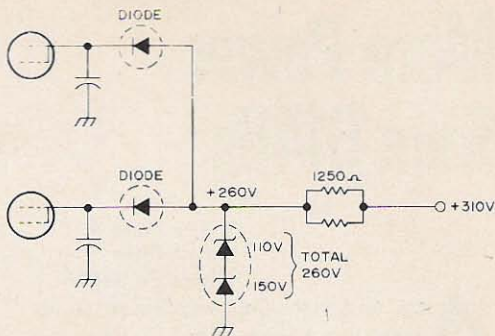


Fig. 2. Zeners can be used in series to help limit the B+. Make sure the diodes are rated to handle the dissipated power if you don't use resistors with them.

In case you need more drive, remember what Joe Namath says: You have to excite them to make them put out! You can juggle the bias and screen voltage on the driver tube — in my case, found that the 6CL6 had over 6V bias on the cathode — and for linear class A operation it should be less than 3V. I shunted the cathode bias resistor and also the screen feed resistor and again using a zener, I clamped the screen voltage at 150V. This gave me enough drive to get about 8 mA (maximum) grid current.

Before you start pouring on the coal, make sure the tubes are neutralized — and it helps if they are matched. Use a fairly sensitive rf indicator across a small 47Ω carbon resistor across the output.

Go over the neutralizing adjustment till you reach the best setting. That is, adjust for good grid current flow — then adjust the neutralizing capacitor for a dip — tune the plate for a peak — again adjust neutralizing capacitor for a dip — retune plate for a peak. By carefully observing the rf indicator you will find a neutralizing adjustment that results in the lowest peak when tuning the plate. That's the spot!

Do not load the 6146 too heavily without drive. In the CW mode at 400 mA it will take about 4 mA. In the SSB mode when kicking to 400 mA, the grid should wiggle 0.5–1 mA.

...W2YW■

Radio Direction/Range Finder

Gus Gercke K6BIJ
Box 143
Weimar CA 95736

Working ten years ago with loop antennas, I noticed that the so called "null" was rarely a null; in most cases it was just a sharp decrease in a signal strength. It was further noticed that by tilting the loop a real null became possible. The top of a hand-held loop had to be tilted toward you and away from the transmitting station.

This resulted in an interesting solution to the ambiguity problem; if you got the total null—you are facing the signal, if not—it is behind you.

This angle of tilt, necessary to produce a total zero signal, was and still is a mystery.

A direction finder consisting of aluminum aircraft loop, mounted on a small aluminum hand-held box, containing transistorized receiver (BC band, 80 and 40 meters) and batteries, was constructed. A pendulum was attached to the top of the loop to measure the angle of tilt.

Tests, including a 100 mile diameter drive around a known station, showed a definite dependence of the angle of tilt on the distance to the signal source. The measurements were however complicated by variations in the angle of tilt (time of day, frequency, and possibly some other unknown factors). As far as I could determine


(and I did not get very far) this is what probably happens:

A vertically held loop cannot produce a total null because *two* signals are present—direct and reflected from one of the heavy-side layers. Somehow these two signals can totally cancel themselves only when the loop is tilted, and in one direction only. It appears that the angle of tilt then is a function of two things—height of the reflecting layer and the *distance* to the station. If so, that distance can be found by a solution of a simple trigonometric problem involving a rectangular triangle with one side (height of the layer*) and one angle (angle of tilt) known.

Unfortunately it is not that simple. Which layer? What is its exact height at the moment? Is there a possibility of a third path?

I was able to calculate the distance with an average 40% error. The frequencies were BC, 4 and 7 mhz; all distances less than 100 miles.

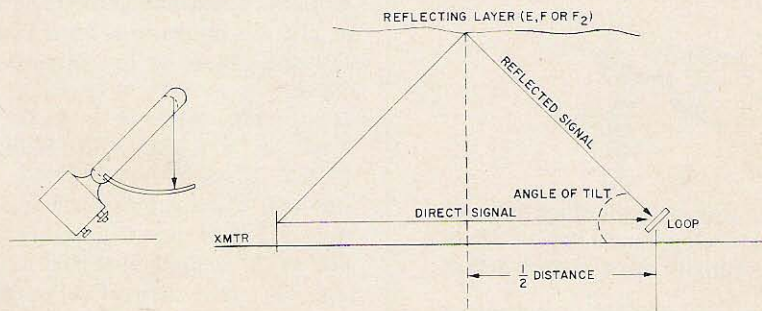All this was done ten years ago; I tried to get people interested in this project, but only one person showed up to look at it. When I explained that a lot of developing is yet to be done, his face produced an





ELECTRONIC FIST . . . THE PROFESSIONAL KEYSER

- Every feature you need for easy, accurate CW
- IAMBIC FOR SQUEEZE KEY'ers
- VARIABLE WEIGHTING FOR DX'ers
- MESSAGE GENERATOR FOR CONTEST'ers
- COLORS TO MATCH YOUR RIG
- KIT OR WIRED. PRICES START AT \$69.95
- WRITE FOR SPECIFICATIONS

CURTIS ELECTRO DEVICES

From your ham dealer or direct.
Box 4090, Mountain View, California - 94040

Custom Transformer Design & Manufacture

Write today for a free quotation on any transformer, choke, or saturable-reactor. Each unit will be designed and manufactured to your exact specifications. Standard E-1 and tape wound "C" cores are available. Quantities from single units to production runs may be accommodated. Custom rewinding services are also available.

PETER W. DAHL CO.

5325 Annette Ave., El Paso, Texas 79924
Tel: 915-751-4856

FRECK RADIO SUPPLY

38 Biltmore Ave., Asheville, N.C. 28801
(704) 254-9551

Serving the amateurs for 43 years

Large Stock of Used Equipment. FREE list upon request. We stock Collins • Drake • Galaxy • Kenwood • Signal One • Swan • Tempo • Hy-Gain • Newtronic • Several Others.

BEFORE YOU TRADE - TRY US!

Bank Americard - Master Charge

Tenny Freck W4WL - Sandy Jackson Mgr.
Harvey Nations W4VOV

HW12,22,32 OWNER


New three band modification kit delivers the performance of your transceiver on 5-200 Kc. band segments. 80/40/20 Mtr. SSB/CW coverage. New front panel and plastic dial included. Perfect for Civil Defense nets. Complete kit price only \$69.95 ppd. Complete assembly manual \$5.95 ppd. Send 50¢ for illustrated brochure.

DYNALAB RADIO CO.

215-28 Spencer Ave., Queens Village NY 11427

Vernier Dial Control

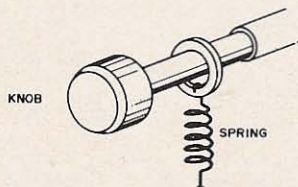Through constant use, eventually many vernier dial movements begin to slip. By putting the shaft into a slight "bind," control can be gained again.



A thin wire or washer on the shaft held under slight spring tension, inside the set where it won't show, will give good vernier action again.


Richard Mollentine, WAØKKC

expression of a man in whose mouth suddenly materialized a dead rat beamed down from the "Enterprise."

Anyone want to take over where I left off ten years ago, do some experimenting, and become immortal? I am busy with my radio controlled submarine models, and gave up on this one.

. . . K6BIJ

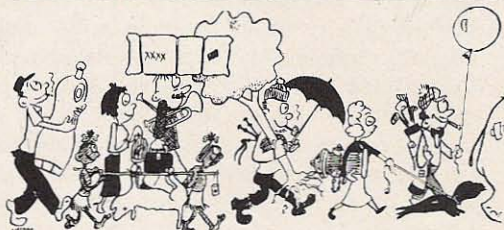*If my assumption that the "angle of tilt" is a function of the height of the reflecting layer is correct, then this height can be measured by solving the same trigonometric problem. In this case we measure the angle of tilt necessary to produce the "null" in a signal coming from a station located a *known* distance away.



Moving? Please let us know.

OOPS!

K6MVH's "Gain Antenna for VHF/UHF Repeaters" (73, July, 1971, page 42) is not really so non-critical that all dimensions can be left to the reader's imagination. Neither can it be said that we purposely deleted the dimensions to test how alert our readers really are. Actually, somebody goofed and forgot to put the dimensions onto Figure 1. The dimensions for this antenna are: 2 meters: A = 19", B = 13.3", C = 26.6". 450 MHz: A = 6.33", B = 4.44", C = 8.875". 220 MHz: A = 12.66", B = 8.88", C = 17.75". Note also that the bottommost coaxial section in Figure 1 is incorrectly identified as "C" length. It should of course read "B", as is clarified in the caption.

Curtis CW Identifier

When repeaters started getting very popular and manufacturers began to tool up their assembly lines for production of 2m FM transceivers, a representative of Curtis Electro Devices called me to ask what the potential might be for a repeater ID unit. Curtis has been manufacturing electronic keyers for some time, and the switchover to an automatic ID unit seemed logical enough. It seemed to me that the market could certainly afford at least one manufacturer in the identifier field, provided that the manufacturer could afford to produce the unit at a cost that was within the budget of the average repeater group.

The Curtis people were not too involved with repeater operation, but they wanted to make their identifier solve all the problems associated with automatically identifying repeaters; so the representative listened while I listed all the desirable features such a unit would have — which were considerable. Within two months, I opened a package that came in the mail and found what I consider to be the ideal identifier. Curtis had taken the ideas I'd given and combined them with some of their own, and the result was a working production ID unit that can be easily installed into any repeater within minutes. What's more, the Curtis identifier contains in its one small package all the control circuitry, tone oscillator, and relay contacts required to make the unit immediately operational.

When properly connected into a repeater, the identifier will send out a modulated CW signal when the first carrier appears on the repeater input. From that point on, it will identify at three-minute intervals as

long as the repeater is being used. When all the carriers drop out and the repeater is no longer being accessed, the Curtis identifier will send out one more ID at the end of 3 minutes, then it will keep quiet; and it will remain quiet until someone else comes along and uses the repeater.

The unit has a built-in speaker so that you can hear the ident when you are testing or installing the system. And an inside-mounted switch allows you to cut off the speaker when you're through making checks. The unit has a set of relay contacts built in, too. These contacts stay closed during the time the identifier is generating its signal; they are used to lock the repeater transmitter on during an ident so the identification signal won't get cut off in mid-sentence.

Other features include a volume control to adjust the level of the modulated CW signal into the repeater transmitter, a speed control to adjust the rate of the automatic identification signal, and various terminals to change the mode of operation from "automatic" to "manual" — or from periodic keying to keying each time a carrier appears.



The Curtis ID package. The terminal strip gives access to all control, voltage and ground points needed for fully automatic operation.

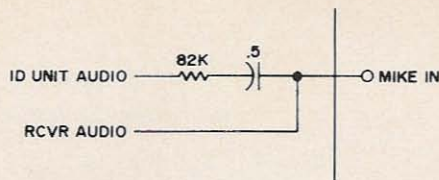


Fig. 1. A series resistor/capacitor network in effect increases the impedance of the ID unit's audio output, and prevents circuit loading.

The Curtis automatic identification unit should be compatible with most repeaters, because it uses a negative dc voltage (12–28V) for control. A ground signal, as from the carrier-operated relay, keys the identifier, but does not cause triggering of the ID until the required time period has elapsed.

When I connected the identifier into the WA1KGO repeater, I noticed that the audio from the Curtis unit tended to swamp the audio arriving from the receiver. This situation resulted in repeater users being jammed out by the identifier. I placed an 82 kΩ resistor and a 0.5 μF capacitor in series with the audio lead from the identification unit (Fig. 1), and that solved the problem.

I didn't do a great deal of thinking or planning before I connected the ID unit initially, and I ended up paralleling the ID unit's contacts with those of the transmitter PTT. This is an acceptable scheme, but it resulted in an automatic identifica-

tion every three minutes, day and night, even when the repeater was not in use. This was because of the small bias voltage on the PTT line. If you like to sleep with your monitor receiver on, you'd be driven quite mad with this sort of hookup. I know I was. So I raced up to the hilltop and made a few small control-circuit changes; the final interconnect circuit is shown in Fig. 2. This latter arrangement keeps the unit from generating an ID signal unless the repeater is actually being keyed, but it does not keep the unit from finishing its ID once it's started, even if the incoming carrier drops out.


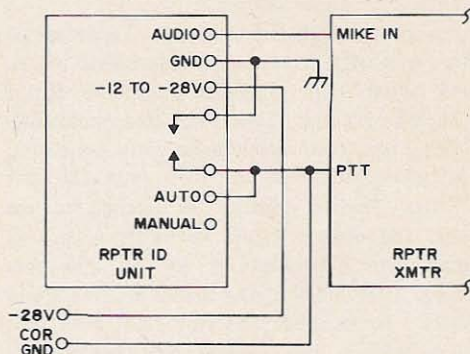


Fig. 2. This interconnect scheme allows identification only when repeater is in use.

Technical Aspects

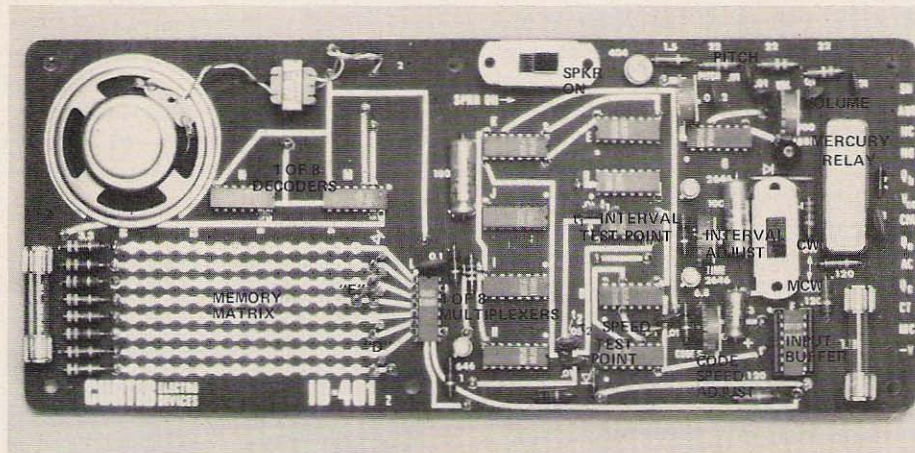The block diagram (Fig. 3) can be used to follow this operational description. When a signal from the carrier-operated



Inside the Curtis ID-401. A PC-mounted speaker (upper left) allows monitoring of the audio signal even before the ID unit is connected to the repeater. The memory matrix (below speaker) can be programmed or reprogrammed by amateurs in the field. The matrix shown is programmed for "DE" only, as indicated by the diode placement.

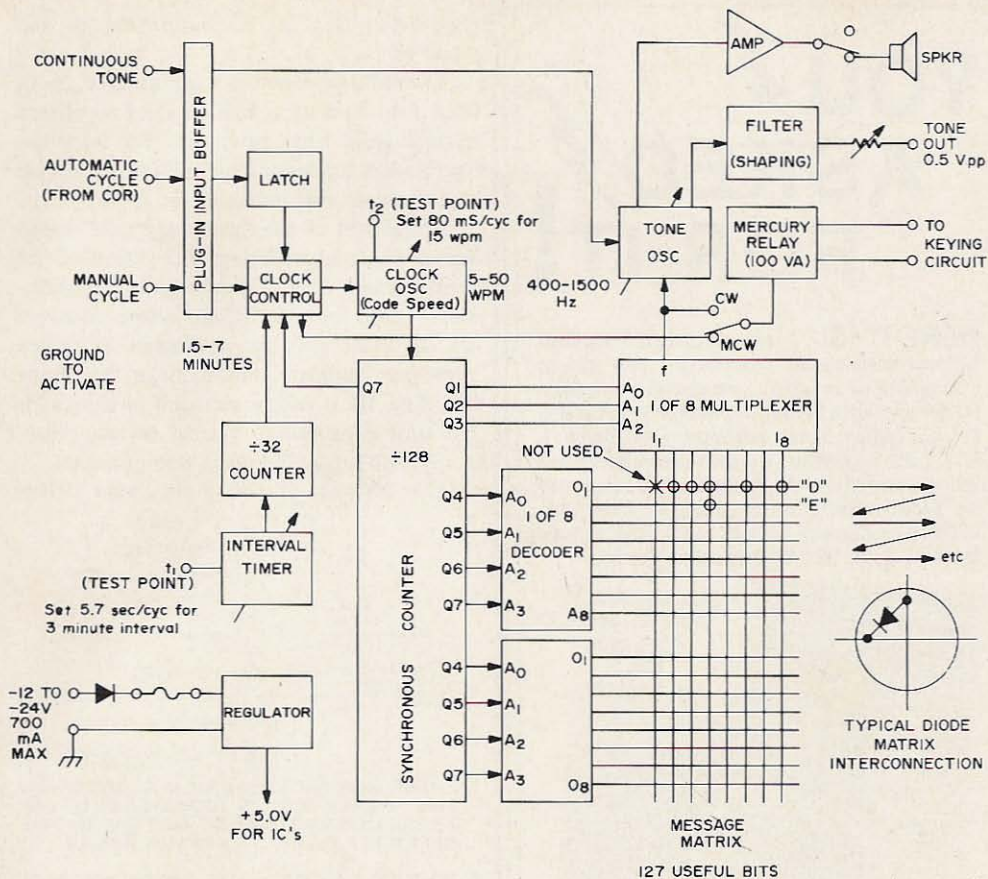


Fig. 3. Block diagram of Curtis ID-401 identification unit.

relay in the repeater grounds the "automatic cycle" input a latch is set indicating the closure regardless of duration. For the first closure after the repeater has been at rest, the clock control starts the clock which is fed into a +128 counter. This counter is fed to two 1 of 8 decoders and one 1 of 8 multiplexer. The decoders ground the horizontal matrix lines in sequence starting at the top and proceeding downward. Each line is held low for eight clock cycles.

At the same time, the 1 of 8 multiplexer is scanning the vertical lines - acting in effect like a single-pole, eight-position switch. In this manner the matrix is scanned bit by bit from the upper left down to the lower right.


Each intersection between the vertical and horizontal lines which is connected by a diode pulls the input of the multiplexer

low. Each "low" is interpreted as a dot; three in a row is a dash. Where a diode is not connected, the output represents a space. In effect, the memory plays out just like a paper tape. You can read the message by examining the diodes. Programming or reprogramming requires only a knowledge of Morse code and no knowledge of Karnaugh maps.

The memory plays out one time and stops until the interval counter counts out the set interval at which time the program will play out once more. If the repeater has been activated during the waiting period the timer will again count out a set interval and cause the unit to identify once more. Only when an interval passes without repeater activation will the unit cease identifying. And at the same time, the unit will not ID more often than the set interval

YOU ASKED FOR IT!

HERE IT IS! . . . one complete U.S. Callbook and one complete DX Callbook per year and no change in price. In addition you can keep your CALLBOOKS up-to-date through a subscription to the new Service Edition Series published each March 1, June 1 and September 1 — each one covering new licenses and all activity during the preceding quarter. Annual subscription to complete Winter CALLBOOKS plus 3 Service Editions only **\$14.95** postpaid for the U.S. and **\$11.45** postpaid for the DX.

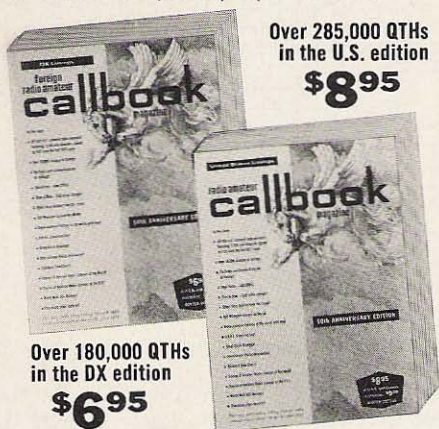

These valuable EXTRA features included in both editions!

- QSL Managers Around the World!
- Prefixes by Countries!
- Zips on all QTHs!
- Census of Radio Amateurs throughout the world!
- A.R.R.L. Phonetic Alphabet!
- Where To Buy!
- Radio Amateurs' License Class!
- Great Circle Bearings!
- World Prefix Map!
- International Postal Information!
- International Radio
- Plus much more!
- Amateur Prefixes

See your favorite dealer or order direct (add 25¢ for mailing in U.S., Possessions & Canada. Elsewhere add 50¢).

**50 YEARS OF SERVICE
TO RADIO AMATEURS**

GET YOUR NEW ISSUE NOW!

**WRITE FOR
FREE
BROCHURE!**



RADIO AMATEUR **callbook** INC.


Dept B 925 Sherwood Drive
Lake Bluff, Ill. 60044

regardless of what is happening at the repeater.

The interval timer is a unijunction oscillator followed by a +32 counter to obtain reliable long time intervals over temperature and independent of line frequency (in case the unit uses batteries for standby).

Activation of the "manual cycle" input causes continuous IDing. Activation of the "continuous tone" input gives a continuous audio output. These three controls are all buffered by a plug-in IC since improper hookup may damage the input ICs. The IC is easily changed in the field. The unit is protected against reverse polarity. A fuse (and a spare) is also provided.

The output of the multiplexer drives

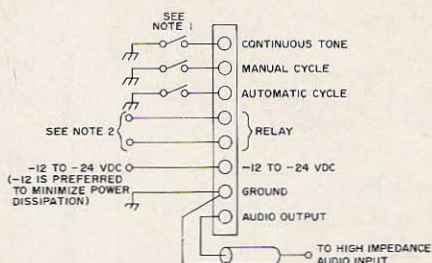

1. THESE CONTACTS SHOULD CLOSE WHEN THE REPEATER IS COMMANDED ON. THESE CONTACTS MUST NOT BE ON THE REPEATER CARRIER KEYING RELAY.

2. TO KEY CARRIER, USE DIODE ARC SUPPRESSION WHEN DRIVING RELAYS. ALSO R/C SUPPRESSION. SEE CHART.

Fig. 4. Terminal strip of the 401. Internal controls are set as follows at factory: Speed, 15 WPM; Time, 3 minutes; Pitch, 650 Hz; Volume, Full; Speaker, On. Relay Mode, MCW.

both the MCW oscillator and a mercury reed output relay. The relay may be switched to either a CW (keys the Morse) or MCW (key down during whole program) position.

The audio drives both a switchable internal speaker and is filtered and level controlled for directly modulating the repeater carrier.

The interval timer is variable between 1.7 and 7 minutes, the speed from 5 to 50 wpm and pitch from 400 to 1500 Hz.

The regulated power supply allows operation from -12 to -28V dc and draws about 700 mA.

The unit employs 14 ICs, three of which are MSI types. . . . K6MVH

DYCOMM offers MORE WATTS per \$\$\$

DYCOMM broadband, no tuning, ready to use boosters can increase your transmitted power up to 45 times. Fully automatic, hands off operation.


DYCOMM offers a booster for virtually every 2M FM rig.

DYCOMM boosters are reliable, inexpensive, straightforward, small in size and big in performance.

DYCOMM boosters all operate on 12V mobile power.

Over 2,000 satisfied users have never paid a cent for a repair; in fact, part of our warranty reads:

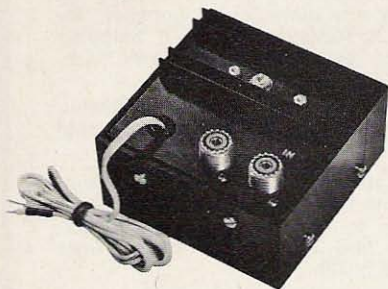
"... If you ever have a problem with your booster take it to any DYCOMM dealer and he will replace it free of charge; if it is out of warranty he will give you another booster and we will charge for repairs, if it seems appropriate..."



500C "FM Booster", 4-12W in, 15-30W out 10W input/output 25W. \$ 59.95




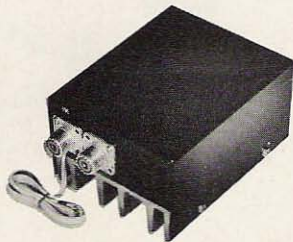500E "Brick" or TR22 Booster, one of the most popular, your 1-2W HT can push out 20-25W \$ 69.95



500ES "Super Brick/TR22 Booster", now you can have from 35-45W for .8-2 watts input. Typically 38W output/1W input. \$ 99.95

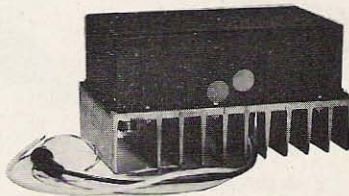500D "Block Booster", 8-12W in, 35-55W output, 16W of drive is FB, this outstanding bargain is still only \$ 89.95



10-0 The ultimate in solid state power 8-15 watts input will put out 80W min., 125W max. Typically 100W output/10W input, 90W min. \$185.00
 35-0 Provides 80-110W output for 25-40W input, typically 100W output for 35W input. \$165.00

All boosters have automatic low insertion loss in/out switching. All operate from 12-15V DC. Isn't it time you also went DYCOMM??

They are rugged: built to take vibration, load mismatch and over-voltage.

To order: See your nearest DYCOMM dealer, if none near you, order direct and add \$1.55 for shipment.

For more information, call or write:

JIM - W4MR1
 AREA CODE 305-844-1323
 844-1324

DYCOMM

Dynamic Communications Incorporated
 948 Avenue "E" Riviera Beach, Florida 33404

STEP UP TO TELREX

Professionally Engineered Antenna Systems

Single transmission line "TRI-BAND® ARRAY"

By the only test that means anything . . . on the air comparison . . . this array continues to outperform all competition . . . and has for two decades. Here's why . . . Telrex uses a unique trap design employing 20 HiQ 7500V ceramic condensers per antenna. Telrex uses 3 optimum-spaced, optimum-tuned reflectors to provide maximum gain and true F/B Tri-band performance.

ONLY TELREX GIVES YOU ALL THESE FEATURES . . .

- Power rating 4 KW PEP . . . rain or shine
- Wind rating survival 110 MPH
- Patented broad-band coaxial Balun
- Heavy-duty steel gusset mounting plate
- Aluminum boom 2 in., 2½ in. O.D. x 18 ft.
- Large diameter, .058 wall taper-swaged dural elements for minimum

weight and exceptional strength to weight ratio

- Stainless steel electrical hardware

With a Telrex Tri-band Array you get 49 lbs. of educated aluminum engineered and built to provide many, many years of performance unmatched around the world by any other make. Longest element 36 ft. Turning radius 20 ft. Shipping weight 65 lbs. Shipping container 13 in. x 5 in. x 13 ft.

Note: If not available from your dealer, order direct. You'll get fast, personal service.

Telrex Labs are design engineers, innovators and manufacturers of the world's finest ¾ to 160 meter communication systems and accessories priced from \$25 to \$25,000.

For technical data and prices on complete Telrex line, write for Catalog PL 71.

TB5EM **\$395**

Other
Multi-Band
Arrays Available


Elements shortened to show details.



BALUN



TRAP

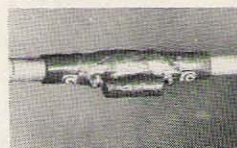

TYPICAL TELREX "MONO-BAND" ANTENNAS

15M317	- "Monarch", 10 DBD, 3 El., 4 KWP, 2-1/2" O.D., 17' boom	\$175.00
20M326	- "Monarch", 10 DBD, 3 El., 8 KWP, 3-1/2" O.D., 26' boom	\$355.00
2M609	- "Monarch", 14 DBD, 6 El., 6 KWP, 1" O.D., 9' boom	\$ 39.95
2M814	- "Monarch", 16 DBD, 8 El., 8 KWP, 1.375" O.D., 14' boom	\$ 59.00
6M516	- "Monarch", 13 DBD, 5 El., 8 KWP, 1.5" O.D., 16' boom	\$ 63.95

and ----- many, many more! send for PL-71 Dept. C

telrex LABORATORIES

TV And Communications Antennas Since 1921
Asbury Park, New Jersey 07712 201-775-7252

John H. Jerman WA6ATT
20434 Seaboard Road
Malibu CA 90265

MORSE MEMORY

All of the Morse code message sending devices which have been in the amateur radio magazines have been designed to send one short message over and over again, usually for repeater identification. They all have been useful for one limited application and have lacked the versatility that is possible using some of the newer advances in integrated circuit technology. The Morse Memory is capable of sending a message in code at any speed as many times as desired. The distinctive difference is that the message in the memory can be changed in a matter of seconds by a simple programming process.


With the encoding scheme used here, a message up to 30 letters long can be stored in the Morse Memory, depending on the length of the letters in the message. This is more than enough to handle any message needed in a contest-type operation and it is also sufficient to send messages during normal daily operation. For example, the Morse Memory can be used during a contest to send repetitive messages such as CQ FD CQ FD DE WA6ATT/6 K. With the simple addition of another integrated circuit memory, two different messages can be sent. For instance, the alternate memory can be used to store the message DE WA6ATT/6 599 LA LA K, sent directly after you send the call of the station which you had just contacted. To send either of these messages you must only push one button and the Morse Memory will do all the rest. On the last Field Day our group used the Morse Memory for every CW contact and it now seems difficult to imagine how we operated CW in contests before. It took care of about 90% of all situations which we encountered. Since the Morse Memory does not hold any message permanently, for the next contest two different messages can be programmed into the unit.

The Morse Memory uses an integrated circuit random access memory (RAM) instead of the large diode matrices used in many of the other projects. Each IC memory



The controls from left to right are memory select, speed control, audio volume, power. The speaker is at the far left, and two power supplies are mounted on the top.

can hold the same amount of information as a diode matrix containing hundreds of diodes. These memories were first produced less than 5 years ago and are now being used in the newest computer systems. The price for individual units has just dropped to the point where they are economical enough for amateur use. The particular memory element used in this project is the Intel type 1101 MOS large-scale integration device. It is capable of storing 256 bits of binary information in a 16-pin dual inline integrated circuit package. Unlike the rest of the logic in the Morse Memory which uses regular P and N type silicon construction as in regular transistors, the memory chip is constructed from silicon and silicon oxide such as is used in MOS FET's. To give some idea of the degree of miniaturization involved, there are over a thousand of these FET's in each memory chip.

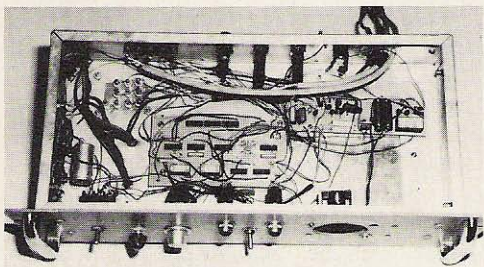

The main IC board is in the center with the transmitter interface in the upper right. The third power supply is mounted on the left wall.

Inside the 1101 there is a memory plane of 256 bistable latches arranged in a 16 x 16 matrix. Each latch must be in one of two possible states at any one time. These two states are normally abbreviated 1 and 0 to represent a high voltage or a low voltage. It is possible to *read* that is, to find out which state a particular location is in, and it is also possible to *write* which involves changing the information in the latch to that of the input signal. Since there are 256 bits of memory, any number from 0 to 255 will correspond to a different memory location. This number is put on the address leads to single out the memory location wanted. All of the necessary decoding is done inside the memory chip itself. For instance, if you wish to read the contents of location 157, you would

simply put that number on the address leads and observe the DATA OUT lead. Since the device can understand only binary information, that number must first be converted into binary. It takes eight binary digits to differentiate between 256 different locations; in this example location 157 corresponds to binary 10011101. Although it seems difficult to decode all of these numbers, it happens that there are relatively simple devices which take care of this problem.

All the rest of the circuitry in the Morse Memory is transistor-transistor logic or TTL. This type of logic is used far more in industry than the RTL devices which have been most common in previously published projects. TTL has many advantages over its RTL counterpart; these include high speed, reduced power dissipation, and lower output impedance. For instance, the entire IC portion of the project which includes over 2500 transistors requires only 1.7W and is capable of sending a message at around 1 million words per minute. The particular type of TTL used was the 7400 series. Each member of the series is designed to be compatible with the other members of the series. In addition, there are at least five companies which make their own versions of the 7400 series, each of which is designed to be compatible with units produced by another company. The larger companies producing a 7400 series are Texas Instruments, Sprague, ITT Semiconductor, Motorola, and Philco. Because of its completeness and availability, I used the TI series. The basic internal differences between TTL and RTL are that TTL inputs of *nand* gates are multiple emitter connections to a single transistor instead of connections to bases of different transistors in RTL, and the outputs of TTL gates are pulled up to plus and pulled to ground by different transistors instead of just having the output pulled to ground and a resistor to plus in RTL.

In order to understand the operation of the unit it is not necessary to understand the internal operation of each device. The only thing which must be considered is the truth table, or mathematical description of each chip. *Nand* logic is used in the system, and the only fact which must be remembered

about these devices is that a 0 signal on any input forces a 1 output. Whenever all inputs are 1's, the output is then zero. In addition, whenever any input pin on the TTL devices has no connection to it, that pin is considered to be in the 1 state.

The most common arrangement of *nand* gates in this project is called the bistable latch; there are over five hundred of these latches in the entire project. Three are outside the memory chips and must be wired, so they should be understood. They could be considered the digital equivalent of a child's seesaw. Just as one end of the seesaw must be in the air and the other on the ground, if one output of the latch is high then the other is at ground. To put a particular end of the seesaw in the air you must push on the ground. To put one output of the latch to a high state a negative pulse, that is, a pulse to ground, must be applied to the input of the *nand* gate whose output needs to be changed. If the pulse is applied while the output is already high then nothing will happen. If the seesaw has a weak center pivot, when both sides are pushed up the center will break, and both sides will go high. If both inputs are grounded, both outputs will go high.

Aside from the *nand* gates and inverters in the Morse Memory, there are three other different TTL devices: one-shots, divide-by-16 counters, and shift registers. The action of the one-shot is basically simple. It gives a pulse of a predetermined length at the output whenever there is a negative going edge of a pulse at the input. The one-shot will not fire again until the input signal goes positive and then goes negative. There is inverting action in the device so both a positive and a negative pulse is available at the two output terminals; the terminal with the positive pulse is Q, and the one with the negative pulse is \bar{Q} . There are two timing terminals to set the length of the pulse by a resistor and capacitor combination. With the values shown the pulse length is about a millisecond, long enough to detect easily, but short enough so that it will not conflict with the other signals.

Internally the one-shot is fairly simple with only a flip-flop and a pair of gates; the other two devices are a bit more complex

than the one-shot but not as complex as the memory. They are therefore known as medium scale integration or MSI devices. Each of the four chips contains four flip-flops internally wired in slightly different ways.

The divide-by-16 counters has each output of the flip-flops connected to the clock input of the next flip-flop. In this way each flip-flop divides by two for a total division of 16. Each of the outputs of the flip-flops is available at a different pin on the package, and with the divide-by-16 output of the first chip connected to the input of the next chip, a clock input to the first chip will be divided by 256 at the output of the second chip. These two chips have a total of eight outputs each at a frequency which is one-half of the preceding signal. If the counters are first reset and a clock signal applied, the devices will count from binary 00000000 to binary 11111111, that is, from 0 to 255. These signals are exactly what is needed to address the memory.

The four bit shift registers each have four flip-flops connected in a slightly different arrangement. The Q and \bar{Q} output of the preceding flip-flop are connected to the J and K inputs of the next flip-flop. With the clock leads all connected together the end result is that the information contained in the preceding flip-flop is transferred to the next flip-flop whenever the clock line is pulsed. With two of these devices connected together, information which is put on the input will be at the output of the last flip-flop exactly eight clock pulses later. This is the digital equivalent of a delay line. As in the counters, each flip-flop has its output available to use. If the input of the shift register is connected to the message output of the memory, and the address to the memory is changed at the same speed as the shift register is clocked, then the last eight bits of message are always contained in the register.

The Morse Memory simply contains the devices mentioned hooked up to perform the required functions. There are many ways to encode the message in the memory, and the peripheral circuitry of the memory will be entirely different with different coding schemes. Here perhaps the simplest method of coding was used. It is a simple time-based

code where a dah is represented by three ones, a dit by a single one, a space between dits and dahs by a zero, and a space between characters by three zeros. The space between words is a matter of personal choice; either 5 or 6 zeros will suffice. If the message is coded in the memory in ones and zeros serially from location 0 to as high as needed by the length of the message, when the address is started at zero and counted up toward 255, the message will be sent in perfect code. To signal the end of the message, eight zeros are added to the end of the message. For example, the message "DEI" would be coded: 0001110101000100010100000000. As the eighth zero has just been sent, the *nand* gate which samples all the outputs of the register will have all ones on its 8 input pins and the output of the gate will go to ground, pulsing the reset one-shot.

The basic sending cycle is therefore as follows. Assuming there is a message in the memory, and the address counter is reset, the start button is pushed. This puts a zero on one of the inputs of the start latch causing that gate to have an output of one. That one opens the clock signal gate allow-

ing the clock signal to go through to the next date. The \bar{Q} output of the one shot is normally high allowing the clock signal to go on to the counter and shift register. The counter begins to count from 0 to 255, sending the message in the process. The shift register keeps track of the last eight bits of message sent, and when the eight zeros signifying the end of the message appear, the *nand* gate fires the one-shot which both resets the counter to zero and closes the clock latch. The message is now ready to be sent again.

There are only four other parts of the complete unit; they are the programming circuit, the clock circuit, the transmitter interface, and the power supplies.

Of the four, the programming circuit is the most unusual. The particular memory device used, the 1101, has both a read/write input and a DATA input. The read/write, or R/W, input is normally low for the read cycle. When the R/W input is made positive, whatever signal is present at the DATA input is put into the memory location which is addressed at that time regardless of what was in that location before. During the write cycle two "bouncless" switches are used to

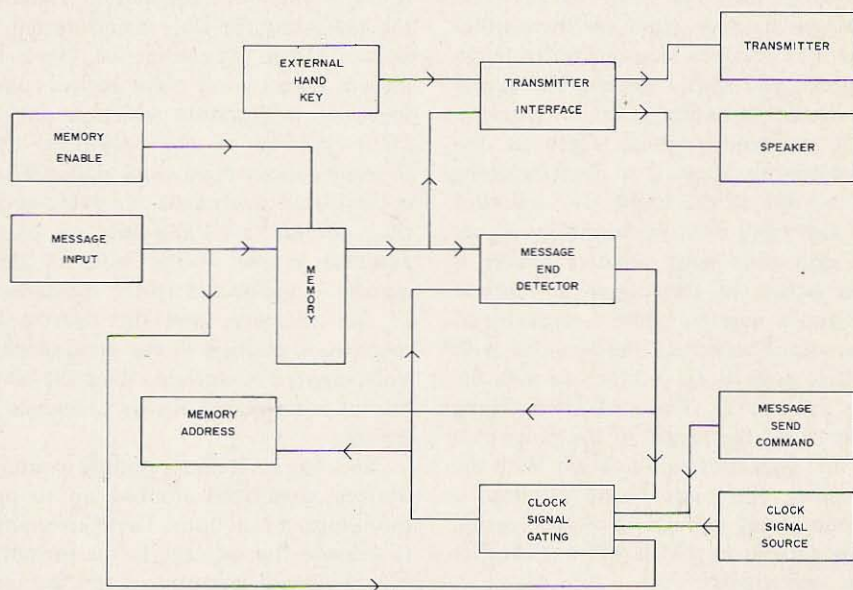


Fig. 1. The block diagram for the entire unit except power supplies. The signal paths are shown by the arrows.

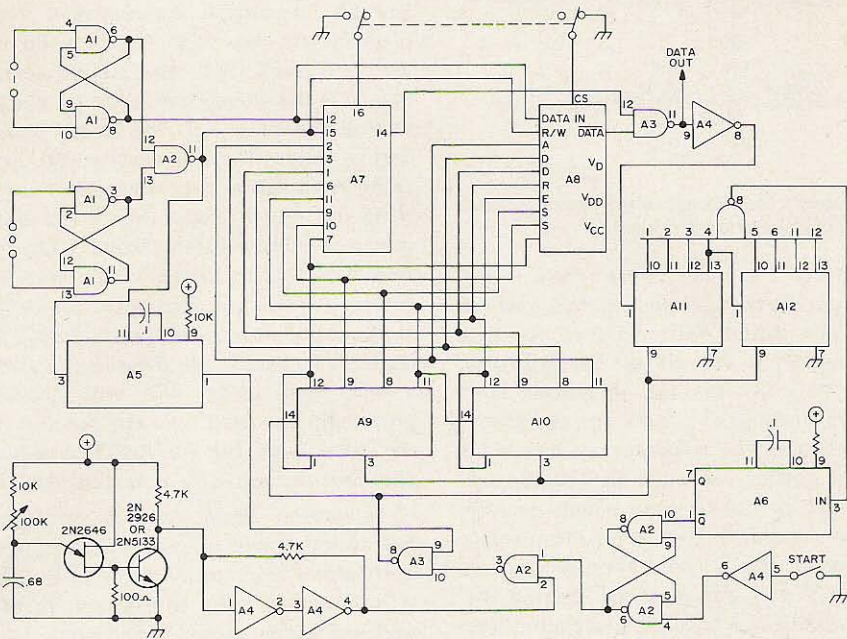


Fig. 2. The circuit diagram for the IC and clock portion of the unit. The numbers in parentheses refer to the 7400 series part numbers, and A, B, C, are three different type 7400 quad 2 input nand gates.

input the ones and zeros of the message. As each of these switches are pressed the R/W line goes positive, and the appropriate signal, either a 1 or a 0, is sent to the DATA input of the memory. As either of the input buttons is released, another one-shot pulses the clock line which advances the memory address one position so that it is ready to receive the next bit of message.

The clock circuit uses a unijunction transistor to provide a variable speed clock signal. With the resistor and capacitor combination shown, the Morse Memory will send Morse code at any speed from about 5 to 100 words per minute. A smaller capacitor could be used to increase the speed any more than this. The clock signal is further processed after the unijunction. Although the unijunction delivers a pulse with a very short fall time, the rise time was a bit too long to properly clock all of the devices. The transistor and two inverters are used to decrease these rise and fall times of the clock signal. The clock runs continuously and the output signal from the clock circuit is gated by the logic mentioned earlier. Since the

speed of the clock signal can be varied over about a 20 to 1 range, a ten-turn potentiometer and counting dial was used to give better control of the speed.

The transmitter interface circuitry contains the devices necessary to both key the transmitter and to provide a sidetone output for the operator. There is a phone jack to allow a hand key or an electronic keyer to operate in parallel with the Morse Memory. The output of the memory and the key are cross-coupled so that either drives both the audio output and the reed relay which is used to key the transmitter. The tone of the sidetone is set by the two capacitors in the multivibrator; to increase the frequency of the tone simply decrease the size of the capacitors. The reed relay which is used is capable of following the output over the full range of speeds with no detectable error, however its power handling capability is rather low, so use it with grid block keyed rigs only. If your transmitter has cathode keying another larger relay could be keyed either from the reed relay or a larger driver transistor.

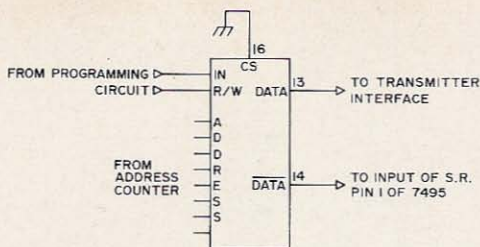


Fig. 3. These are the changes to the circuit diagram if one memory operation is desired.

The power supplies were constructed mostly from parts from the junkbox and are intended as a guide. Three different voltages are needed, +5.0 for all of the IC's and clock, 9.0 volts for the memories, and somewhere around +12 volts for the transmitter interface. The 5 volt supply should be capable of putting out close to 250 mA for an extended period of time which necessitates some type of heat sink on the regulating transistor. The -9 volt supply only has to handle 25 mA per memory chip so the power dissipation is reduced quite a bit. Try to make certain that the regulation is within $\pm 5\%$ and the ripple is less than .05 volts for both IC supplies.

Since it is fairly difficult to make a printed circuit board with the number of crossovers and with the extremely close spacing which is characteristic of large integrated circuit projects, the main parts of the Morse Memory were constructed on Vector-

board with the .1 inch hole spacing which exactly matches the pin spacing of the 14 and 16 pin dual inline packages. To interconnect the pins #26 tinned solid copper wire was used. This wire is thin enough so that there is plenty of room to work with around the pins, but it is heavy enough so that it doesn't break easily and holds its shape well. When the wires cross or come close to other pins the wires must be insulated. Plastic tubing which has an inside diameter slightly larger than the wire is perfect for this job, but some plastic tubing melts easily during soldering. Teflon tubing is ideal. To attach the wires to the pins form a small loop in the wire with needle nose pliers, slip the loop over the pin and tighten the loop with the pliers. Then solder the wire and the pin with a small soldering iron.

Integrated circuit sockets are useful but need not be used in excess. When the socket costs about the same as many of the cheaper IC's it seems silly to protect them with sockets. Each person can make his own decision about where to use the sockets; I used them only on the two memory units. Since the connections to the pins are made by wire, the IC's can be removed simply by taking the wires off pin by pin. On a printed circuit board the task would be much more difficult.

The entire project is housed in a surplus rack panel which seemed suited for the task

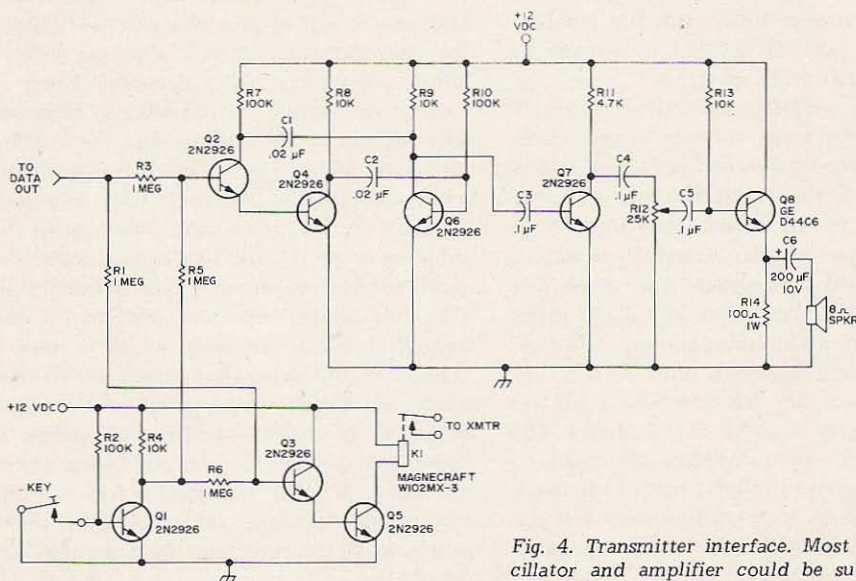


Fig. 4. Transmitter interface. Most any audio oscillator and amplifier could be substituted and many different reed relays are compatible.

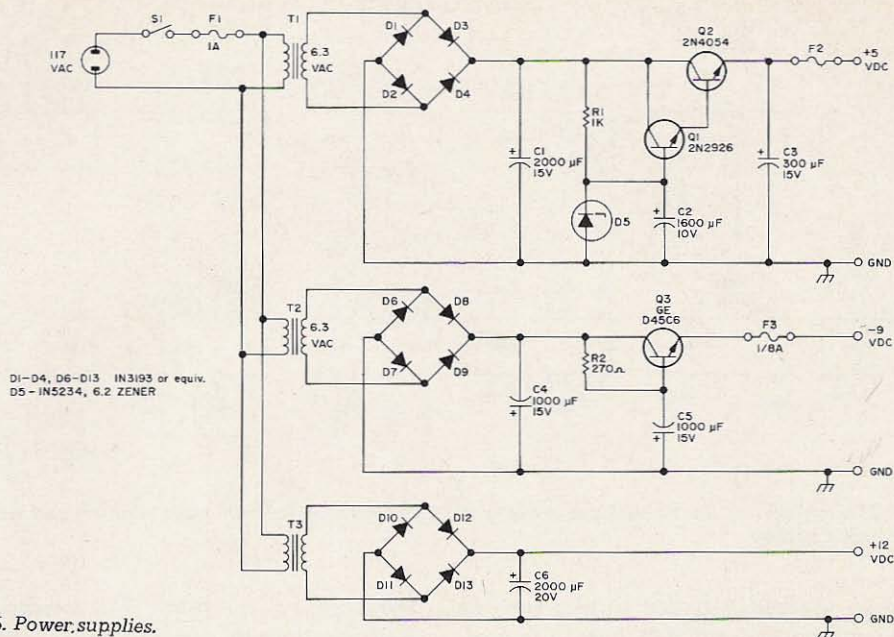


Fig. 5. Power supplies.

and was available on the day before field day. With all of the power supplies and controls the Morse Memory takes up a reasonable volume. With smaller transformers the weight and volume would be reduced by a large degree. I found no reason to label the controls; this job could, however, be done easily with the dry transfer type lettering. Make certain that the completed unit provides a reasonable shield against rf. This will prevent false keying by a nearby transmitter and will prevent false programming.

The operation of the Morse Memory will depend on the number of memory units used. With one 1101 most of the time some type of CQ message would be most useful. This will be somewhat shorter than the 10-minute CQ's heard often around the bands, but it can be repeated at a touch of a button. This message can be changed from CQ FD to CQ DX to TEST. With two memories full contest operation can be implemented. Of course an additional 1101 can be added at any time to increase the versatility of the unit. The wiring differences are minor between the two units. With one memory the chip select (CS) is tied to ground, DATA to the interface units, and DATA to the shift register. With two or

more units all the address and input leads are connected in parallel. The CS leads are connected so that only one lead is grounded at a time and the rest are tied to plus. All of the $\overline{\text{DATA}}$ outputs are put to different inputs of a *nand* gate, the output of this gate goes to the transmitter interface, and this signal is inverted and fed to the shift register.

Once the unit is wired the first job is to check the power supply, clock, and interface. Be absolutely certain that the IC supplies don't go more than a few tenths of a volt above the ratings, and be absolutely sure that the polarities are correct to all units. It takes only a few milliseconds for the IC's to be destroyed with wrong polarity supplies. It is a good idea to test the IC board with commercially built power supplies with current limiting which might save a chip. After these dc tests, pressing the start button will normally produce some output signal even without programming a message. This is the state which the memory takes whenever the power is turned off and turned back on. To hold a message the power must be continuously applied to the memories. If there is no message start tracing the clock signal through, make sure that the counter is counting, and see if the shift register is working. Watch for leads which must be

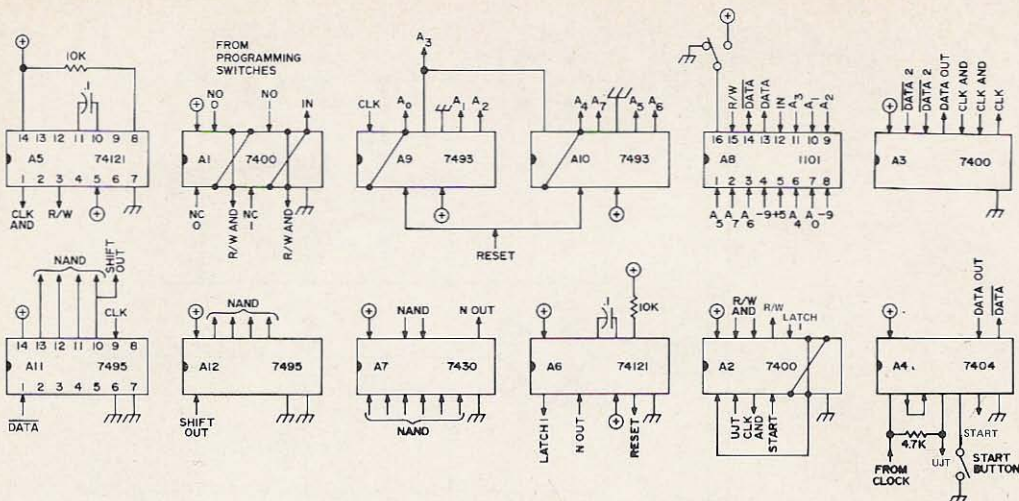


Fig. 6. The top view of the IC packages showing the interconnections of the pins. Wire the pins with the same names together.

normally grounded or tied to plus such as CS, counter reset, and R/W lines. The next job is to program a message and check the entire cycle. To put in a message code the Morse code into ones and zeros, and push the one and zero input buttons in the same sequence. To avoid confusion, turn the audio volume all the way down. Once the eight zeros are put in at the end of the message, turn the volume back up and push the start button. The code should be sent by the Morse Memory at a speed dependent upon the clock speed. With a little practice the programming will take very little time; it should take about two minutes to put in a 30 letter message in the memory. Once a message is put in one memory, if there is another memory chip in the unit switch the CS switch to the other memory and put another message in that chip. This will not affect the message in the first chip.

All of the TTL devices are readily available through any large supply house but prices can vary, so shop carefully. Be certain to specify the plastic dual inline package which is abbreviated as "N" or "P" after the device number. The Intel memory will be the hardest device to find although there should be no real problem. There was a recent price cut for the 1101 in a plastic package. The designation for it is the P1101A and the price is \$20 in single unit quantities. This works out to something like

two cents per transistor. The memories are available through Hamilton/Avent Electronics and Cramer Electronics. These two companies have offices in many of the larger cities in the U.S., but if there isn't a location in your area contact Hamilton Electro Sales, 10912 W. Washington Blvd., Culver City CA. There is a very complete data sheet for the 1101 which is very helpful in understanding the operation of the memory. This may be obtained from Intel Corp., 365 Middlefield Road, Mountain View CA 94040, or the local distributor in your area.

Aside from being a very versatile project and useful in many different areas, this project contains almost every type of integrated circuit device and will give a very thorough introduction to this rapidly expanding field. I would like to thank Dr. Carver Mead, Caltech, for his help on this project and the very thorough introduction to the field which he gave me.

...WA6ATT

Note: Devices and technical data are available from Circuit Specialists Co., Box 3047, Scottsdale AZ 85257. 1101A memory - \$20; 7493 - \$1.90; 74121 - \$1.80; 7495 - \$2; 7400 - \$.45; 7404 - \$.45; 7430 - \$.45; 2N2646 - \$1.20; 2N5133 - \$.30; 2N2926/HEP726 - \$1; 2N4054/HEP244 - \$1.75. Also available is 4" x 8 1/2" vectorboard with holes on .1" centers and instant printed circuit subelements for mounting and soldering to the integrated circuits. The cost of the board and the instant PC subelements is \$5.25. Please add a small amount for shipping.

ADVERTISING CAN PUT YOU OUT OF BUSINESS -

- ... if you advertise in the wrong place
- ... if you can't fill the orders that pour in
- ... if you spend more than you have to for ads
- ... if your ads don't sell for you



Aline

Is 73 the RIGHT place? Possibly. One company recently bit the dust largely because they wasted too much money advertising FM equipment in amateur magazines that had too few FM-interested readers. You can waste an awful lot of money finding this out for yourself when all you have to do is just look and see where the mail order advertisers are concentrated for your particular equipment... let them spend their money finding out which magazine sells best and then climb aboard, saving yourself a bundle. This works out to be 73, obviously, or we wouldn't bring it up.

Unless you are prepared to start shipping right away and in quantity, use one of the other magazines. They just may be able to hold your sales down to a small enough volume so filling orders won't be a problem. If you advertise in 73, be prepared.


The value of an ad depends upon one thing: the results you get from it. If you advertise in a magazine that reaches active amateurs and whose pages are all at least seen by these readers, then you have the best chance of having your ad read and acted upon. Polls show that ads bunched into a lump in the back of a magazine reduce readership by almost 50%, making the 73 system of spreading the ads through the magazine (or in a buyer's guide) far more effective. This factor alone would account for the remarkable sales results 73 has provided many advertisers as compared to a magazine with 30% greater circulation.

Speaking of circulation, what can you believe? Sworn statements? Post office statements? Or what? Are you buying 15,000 or 35,000 circulation? Or is it 30,000 instead of 98,000? Or is that even relevant? You are after sales, and that is all you are after. It makes little difference to you whether the copies of a magazine are mythical, are thrown away by newsstand distributors when they come back unsold, or go to old timers who have no intention of spending any money on equipment. What's the difference why your ad didn't pull? Only sales count. And that is what you will get when you advertise in 73.

73 is read by active amateurs. We don't lean toward the heavy duty engineers who build complicated projects... you will starve to death trying to sell to this elite group. We don't go after the fifty year ham who bought his last piece of ham gear in the 50's. Our construction projects, technical articles and flippant manner will get your ads into the hands of the active, on-the-air hams who are your customers.


Call me today and reserve space in the next issue of 73. 603-924-3873.

FRONT

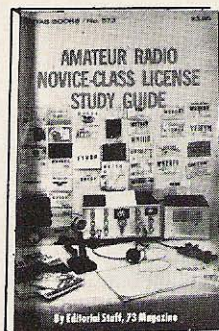

A The Novice Class License Study Guide has not yet been published in 73 or in any other magazine. This book contains all of the basic technical information needed to pass the Novice License with flying colors... and is invaluable as a basic text for understanding the General Class Study Guide. 154 pages and profusely illustrated. So clearly written that just reading it is enough to permit most applicants to pass their exam.

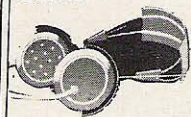
AMATEUR RADIO GENERAL CLASS LICENSE STUDY GUIDE



B The 73 General Class Study Guide has helped thousands to easily pass their General License the first time through. At \$9 a whack, isn't it foolish not to hedge your bet with this comprehensive and simple book? No other study guide is as complete or as easy to read. None. 320 pages.




C The Advanced Class Study Guide runs 192 pages and has proven to be the only complete text for preparing to pass the Advanced Class license exam. Never before has radio theory been made so simple. After just reading this book it is almost impossible to fail that exam. And remember that in addition to the trouble of going to the FCC to take that exam, there is a little matter of \$9 you have to ante up. Why take a chance on failing?

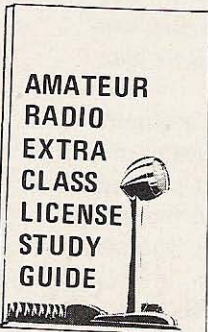

D The Extra Class License Study Guide makes all that complicated electronic theory seem simple. A little study with this book and you will be ready to face the FCC examiner with confidence. 220 pages.



E The 73 DX handbook has every DX aid you could hope for... QSL Bureaus, postage rates worldwide, DXCC and WTW country lists and record pages, maps of many areas of the world with prefixes, plus a complete wall-sized world map with each book! It is profusely illustrated with pictures of many of the top DXers, plus articles on working DX on the different bands. There are great circle bearing maps and charts, and more... more... more.

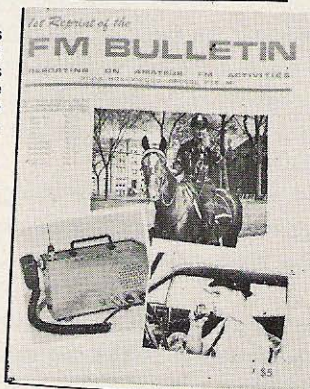

F The FM Anthology has reprints of all of the articles and technical data from the early issues of the FM Journal. No FM library is complete without this data, much of it just not available elsewhere.



G The BEST of FM is a compilation of the best articles that appeared in the FM Journal from March 1968 through June 1969, the last of the magazine. Read the extremely controversial Chronicles of 76. Plus dozens of technical and circuit articles available nowhere else.



H Transistor Projects for the Amateur is crammed with over 40 interesting construction projects covering receivers, converters, and transmitters, many in the VHF region. If you like to build you will blow your mind over this book.

Christmas Gifts - FROM 73 TO YOU!

Accept ONE BOOK FREE with our compliments for each \$6 subscription you enter.

Free Gift Books can be sent to each subscriber or to the donor. One gift book per \$6 subscription, wherever they go.

All subscriptions will be entered to start with the January 1972 issue unless otherwise noted. On renewal or extensions of subscriptions please include the address label from the magazine wrapper or renewal notice. This offer good for 1 year or life subscription only.

This offer good in North America only. Foreign readers may participate by adding one extra dollar per subscription.

Offer expires Dec. 31st 1971

Please enter subscriptions for the following, starting with the January 1972 issue.

73 Magazine, Peterborough NH 03458

New Renewal or extension

Name _____ Call _____

Address _____

City _____ State _____ ZIP _____

Circle book wanted: **A B C D E F G H**

1 year \$6

Life \$73

73 Magazine, Peterborough NH 03458

New Renewal or extension

Name _____ Call _____

Address _____

City _____ State _____ ZIP _____

Circle book wanted: **A B C D E F G H**

1 year \$6

73 Magazine, Peterborough NH 03458

New Renewal or extension

Name _____ Call _____

Address _____

City _____ State _____ ZIP _____

Circle book wanted: **A B C D E F G H**

1 year \$6

73 Magazine, Peterborough NH 03458

New Renewal or extension

Name _____ Call _____

Address _____

City _____ State _____ ZIP _____

Circle book wanted: **A B C D E F G H**

1 year \$6

25 Watts isn't everything, but with everything else it's GREAT!

GLADDING 25™

- 25 WATT • FM
- 6 CHANNEL
- 2 METER
- TRANSCEIVER



We loaded this rugged, new, two-meter radio with 25 watts of power and then packed it with desirable features that make it the most wanted two-meter amateur radio on the market. It's the Gladding 25™ from Pearce-Simpson, Division of Gladding Corporation and the World's largest manufacturer of marine communications equipment. Best of all, because of our unmatched marine volume, we could add a price tag to it that can't be matched by anyone, anywhere, and still give it custom quality. Great! 25 watts and a lot more, from Pearce-Simpson.

- 25 watts output • 0.3uv sensitivity for 12db SINAD • built in 12 volt power supply • matching AC power supply accessory • 6 separately switchable transmit and receive channels • Economical vacuum tube driver and final.
- Plus • 8 pole crystal lattice filter • Transistor sockets • Glass epoxy printed circuit boards • Quick disconnect power plugs • Mounting cradle • 1 watt output switch


\$249⁹⁵

mobile unit

\$295⁹⁵*

with accessory
AC Power Supply

Suggested List Price

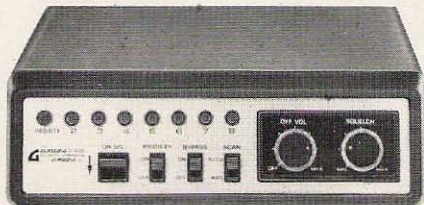

GLADDING HI-SKAN™

8 Channel VHF Monitor

- Automatically scans 8 pre-selected channels • Switch for manual selection of channel • Priority channel • Bypass channel • 115VAC/12VDC built in power supply • Mounting cradle • Can be tuned to 2 meters.


\$99⁹⁵*

*Suggested List Price

PEARCE-SIMPSON
DIVISION OF **GLADDING** CORPORATION
P.O. Box 800, Biscayne Annex, Miami, Florida 33152



73 Tests

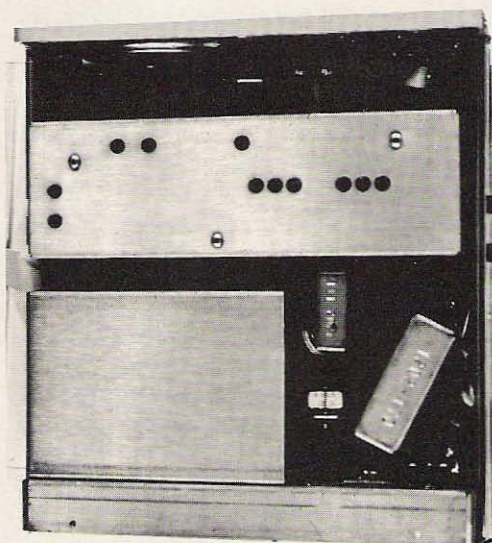


Though relatively new on the ham market, the Pearce-Simpson Gladding 25 transceiver is showing up on the air very rapidly.

The big difference between it and the other units is that "25" in the name, which means 25 watts output. Power has come to two meter FM. Surprisingly this power is available at a price that is remarkably competitive. The Gladding 25 sells for \$249.95 in the 12-volt model and for \$299.95 with a matching ac power supply.

The two meter model is almost identical with the famous Gladding marine transceivers, which are about the best selling in the world. This volume of business undoubtedly helps them to keep their price a lot lower than it might be if they were making units for amateur radio alone.

Those of you who have read the ads for

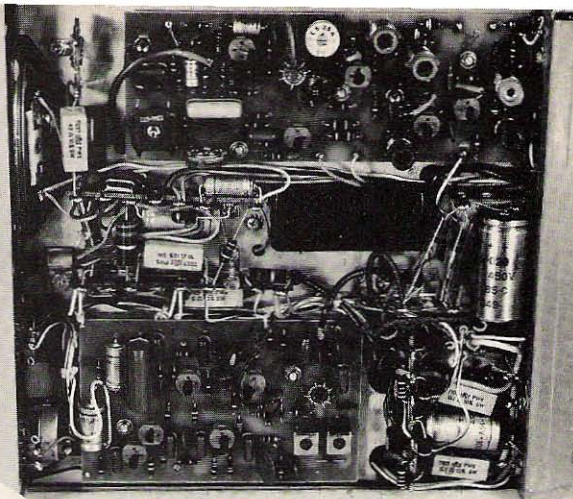

the GLADDING 25 FM TRANSCEIVER

solid state amplifiers recognize why most FM transmitters are limited to around ten watts. Transistors are available for up to 100 watts or more, but the price is a bit out of the average amateur pocketbook range, running up to over \$200! Gladding pulled a fast one with their rig by using tubes in the driver and final. Tubes may be old fashioned in some circuits, but for power amplification they are still the least expensive route.


The Gladding, like the Drake, Tempo, Telecomm, Sonar and Swan units, uses 12 MHz crystals for the transmitter. The receiver uses 78 MHz crystals, which is a departure . . . this being the only amateur FM rig we know that uses these. The transmitter crystals have air padding capacitors for zeroing in the channel. There are six separate channels.

The transmitter has a power level switch

WORLD RADIO
\$1⁰⁰ MICROPHONE
SALE!*

OUR BEST "HOME" MICROPHONE the
 "SOUND-OFF" and the 521 "MOBILE MIC."

BOTH \$25⁹⁵
FOR

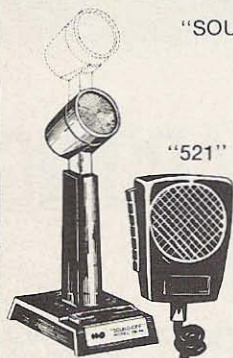

"SOUND OFF"

"521"

The "Sound-Off" is high impedance dynamic, with tailored high output, especially suited for SSB ham use.

Has great "talk-power Armo-Dur case has adjustable height; push-to-talk or VOX use. Complete with 7' cable. Regular price alone \$24.95.

The 521 is a rugged mobile hand mic. with big "easy-grip" PTT switch, high impedance, rugged ceramic element and convenient "coil-cord". Regular \$10.00 value. (*Order by # SB44/521 — on BankAmericard or Master charge and you get both for \$25.95 plus shipping; or send \$25.95 with your order and we'll send prepaid in the USA. Offer good starting Dec. 1, 1971, while stocks last.) Check with WORLD RADIO for a deal on: Galaxy-Drake-Hy Gain-Mosley and many other popular brands for your "ham" equipment & accessory needs.

WORLD RADIO

3415 West Broadway (C9)
 Council Bluffs, Iowa 51501

Ship a SB 44/521 package on (Bank-Americard) (Master Charge) my account is _____

and charge \$25.95 plus shipping cost. Ship a SB 44/521 package at \$25.95 PREPAID for which my check is enclosed in full.

Name _____

Address _____

City _____ State _____ Zip _____

which helps conserve your car battery when the 25 watts isn't really needed. The output is one watt in the low power position. There is a "monitor" position on the power switch which turns off the amplifier filaments and thus conserves battery power, if this is important.

The Gladding is surprisingly well made, particularly when you consider that price. The circuits are on boards, IC's are used, and there is a lot more shielding than you will see in most other rigs. The crystal compartment has its own shield, as does the receiver rf and i-f section and the final amplifier. The final is shielded both below and above the chassis!


The receiver is considerably better than some we've tested, probably due to the eight pole crystal filter in the 10.7 MHz i-f. We have an enormously loud repeater about 70 miles from here which runs about 15 hours a day average on 146.91. Many receivers are just about useless when this is on if we want to listen on 88 or 94, both among the most used channels in our area. If you have 60 kHz spacing to your nearest repeaters you probably won't have interference and a sharp i-f won't make that much difference, but if you've got a signal of substance just 30 kHz off channel, this may be an important factor to keep in mind. The advertised selectivity of the unit is 60 dB down at 15 kHz.

The receiver and transmitter crystals switch independently, so you can use the 34/94 pair or, if you happen to live in a run-down part of town where an old repeater is still grinding out 34/76, you are still set. By adding a 16 transmit crystal you will be on 16/76 for modernized repeaters. If you are uptight about your 34/76 repeater please try and ignore the sarcasm . . . but do let the idea of shifting to 16/76 perk somewhere in the back of your mind, even if it is way, way back.

All in all, we liked the Gladding 25 and think it is a remarkable buy. . . . Staff

Tell Our Advertisers
 You Saw It In 73
(Even if you didn't)

*73's Special
Christmas
Catalog*

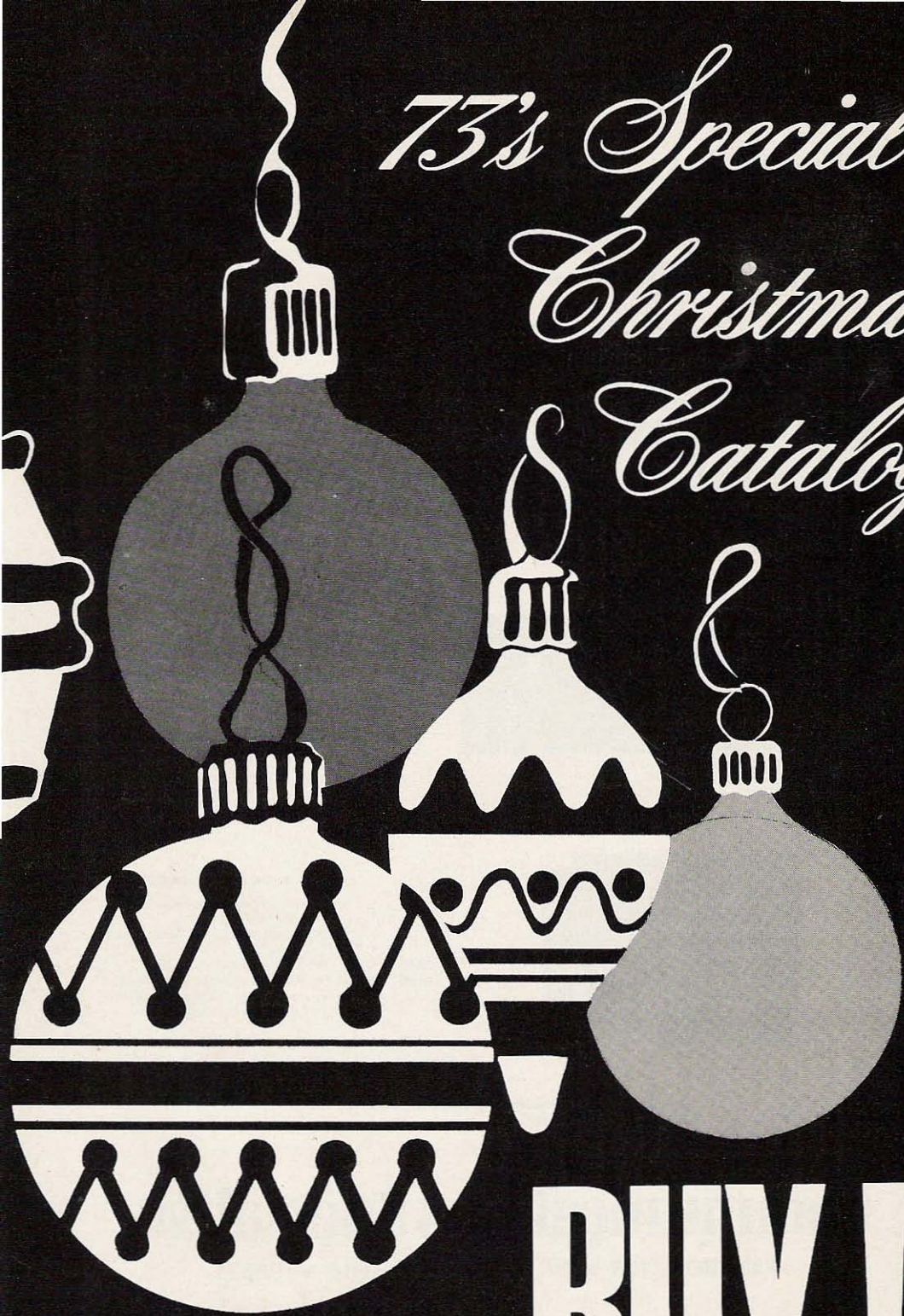

BUY!

SUB-AUDIBLE TONE ENCODER & DECODER KITS

- Compatible with all sub-audible tone systems such as Private Line, Channel Guard, Quiet Channel, etc.
- Glass epoxy PCB's and silicon transistors used throughout
- Any type reeds may be used: Motorola, G.E., RCA, S.D.L., Bramco, etc. except special dual coil types
- All are powered by 12 vdc
- Use on any tone frequency 67 Hz to 250 Hz



- ENCODER**
- Small size 1.5 x 4 x .75"
 - All parts included except reed and reed socket
 - Output 4v RMS sinewave, low distortion
- \$8.95 Kit
13.95 Wired-Tested



- WIRE-IN TYPE DECODER**
- Same small size as encoder 1.5 x 4 x .75"
 - All parts included except reed and reed socket
 - Output relay included, low profile sealed type
 - Driven directly off discriminator of any FM receiver
- \$9.95 Kit
14.95 Wired-Tested



- PLUG-IN TYPE DECODER**
- Circuit board plugs into 12 pin edge card connector
 - Driven directly off discriminator of any FM receiver
 - Small size 3.25 x 2.5 x .5"
 - All parts included except reed, reed socket, 12 pin edge card connector, and plug in relay
- \$8.95 Kit
13.95 Wired-Tested

All material shipped postpaid (Calif. residents add 5% sales tax)
Send check or money order to:

Communications Specialists

P.O. BOX 153 • BREA, CALIFORNIA • 92621

2 METER FM HEADQUARTERS

Rigs for every use . . .
for every pocketbook!

HIGH POWER STANDARD 851SH

25 Watt output
12 channels (4 with crystals)
All solid state
Separate 4x6" speaker

Only \$449.95



NEW! HANDY-TALKY STANDARD SRC-146

5 Channels — .94/.94 and .34/.94 supplied
.3 uV receiver — 1.5 W transmitter
Compact — 8" h x 3" w x 1½ d
Full line of optional accessories includes external
speaker-mike — desktop charger — "stubby" an-
tenna — and more!

Available NOW! — Only \$279.00

ALL PURPOSE STANDARD 826M

12 channels (4 with crystals)
10 Watt output
All solid state
Hot MOSFET receiver

Only \$339.95



And many more from Dycomm/Kenwood/Tempo/Antenna Specialists

Make ERICKSON your headquarters for all your FM needs . . .


ERICKSON COMMUNICATIONS

4653 N. Ravenswood Ave., Chicago, Ill. 60640 (312) 334-3200

SEND QSL FOR COMPLETE SPECIFICATIONS

PREAMP CATALOG

HIGH GAIN • LOW NOISE

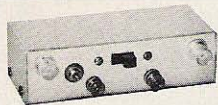


35 dB power gain, 2.5 – 3.0 dB N.F. at 150 MHz, 2 stage, R.F. protected, dual-gate MOSFETS. Manual gain control and provision for AGC. 4-3/8" X 1-7/8" X 1-3/8" aluminum case with

BNC receptacles and power switch. Available factory tuned to the frequency of your choice from 5 MHz to 350 MHz with approximately 3% bandwidth. Up to 10% B.W. available on special order.

Model 201 price: 5–200 MHz\$21.95.
201-350 MHz\$24.95.

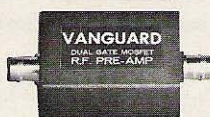WEATHERPROOFED AND D.C. POWERED THROUGH ANTENNA CABLE



Models 101 and 102 only are available enclosed in a die-cast weatherproof case for mounting at the antenna in series with the lead-in cable and includes a filter for sending 12 VDC through the cable. Can be used only for receiving unless you put a TR switch at the antenna. Available with your choice of VHF, BNC or type "N" receptacles. Especially useful for eliminating antenna line loss and thereby improving signal-to-noise ratio of weak signals such as those from weather satellites at 137 MHz.

Price: Add \$10.00 to pre-amps.

MINIATURE SIZE: 2 1/2" X 5/8 X 1" 20 dB GAIN • LESS THAN 3 dB N.F.




Single stage, R.F. Protected dual-gate MOSFET. 4 miniature trimmers for tuning and impedance matching. Aluminum case with feed-thru solder terminals. Provision for manual gain control

or AGC. Tuned to the frequency of your choice from 135 MHz to 250 MHz with 2–4 MHz bandwidth. Supplied with mounting kit for installing inside or outside your receiver.

Model 101 price:\$17.95.

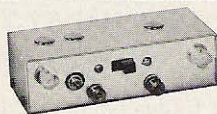UHF 3 TO 5 dB MAX. N.F. 20 dB MIN. POWER GAIN



The Model 202 uses 2 of T.I.'s super low noise J-FETS in our special circuit board design which gives a minimum of 20 dB power gain at 450 MHz.

Stability is such that you can have mismatched loads without it oscillating and you can retune (using the capped openings in the case) over a 15–20 MHz range simply by peaking for maximum signal. Available tuned to the frequency of your choice between 300–475 MHz. 4-3/8" X 1-7/8" X 1-3/8" aluminum case with BNC receptacles and power switch.

Model 202 price:\$31.95

SUPER LOW NOISE: LESS THAN 2 dB N.F. POWER GAIN: 24 dB @ 150 MHz. MINIATURE SIZE: 2 1/2" X 5/8 X 1"



Features a super low noise J-FET rated by T.I. as typically 1.2 dB N.F. @ 150 MHz (transistor data curves supplied with unit) and guaranteed by our lab to give under 2 dB actual N.F.

in our circuit. Transistor is mounted in a socket with gold plated contacts. 4 precision trimmers make possible tuning for optimum desired results over a wide range of conditions. We supply it tuned for minimum noise figure across 50 ohms input and output resistance. Fully shielded in aluminum case with feed-thru solder terminals. Supplied with mounting kit for installing inside or outside your receiver. Tuned to the frequency of your choice from 135 MHz to 250 MHz with approximately 2–4 MHz bandwidth.

Model 102 price:\$19.95

PREMIUM TESTED PRE-AMPS

All of our pre-amps are available with a certified test report stating the actual gain and noise figure as obtained on Hewlett-Packard test equipment and supplied with a nomograph that will give you the sensitivity you can expect with a given noise figure and receiver bandwidth.

Price:Add \$3.00 to pre-amp.

HOW TO ORDER:

All the pre-amps on this page are available only from Vanguard Labs. Include remittance in full plus sales tax if you reside in N.Y. State. Send money order or certified check for faster shipment. We ship at our expense by regular parcel post. Add 80¢ for special delivery or \$1.00 for air mail for up to 2 items.

NOTE:

All pre-amps on this page are for operation on 12 VDC and draw approximately 5 to 20 ma. Available for 6 volts on special order. Stated dB gain figures are for power gain across 50 ohms input and output load resistance.

VANGUARD LABS

196–23 JAMAICA AVE.
HOLLIS, N.Y. 11423

SELECTED CONVERTERS AND RECEIVERS

40 dB GAIN 2.5-3.0 N.F. @ 150 MHz



2 RF stages with transient protected dual-gate MOSFETS give this converter the high gain and low noise you need for receiving very weak signals. The mixer stage is also a dual-gate MOSFET as it greatly reduces spurious mixing products — some by as much as 100 dB over that obtained with bipolar mixers. A bipolar oscillator using 3rd or 5th overtone plug-in crystals is followed by a harmonic bandpass filter, and where necessary an additional amplifier is used to assure the correct amount of drive to the mixer. Available in your choice of input frequencies from 5-350 MHz and with any output you choose within this range. The usable bandwidth is approx. 3% of the input frequency with a maximum of 4 MHz. Wider bandwidths are available on special order. Although any frequency combination is possible (including converting up) best results are obtained if you choose an output frequency not more than 1/3 nor less than 1/20 of the input frequency. Enclosed in a 4-3/8" x 3" x 1-1/4" aluminum case with BNC receptacles, power and antenna transfer switch.

Thousands of our converters are now in use by satisfied customers, many of whom are government agencies and universities.

Model 407 price: 5-200 MHz \$42.95
201-350 MHz \$44.95

Prices include .005% crystal. Additional crystals \$5.95 ea.

VHF FM RECEIVER 11 CHANNELS • 135-250 MHz




- 11 crystal-controlled channels. ● Available in your choice of frequencies from 135-250 MHz in any one segment from 1-4 MHz wide. ●
- I. F. bandwidth (channel selectivity) available in your choice of +/- 7.5 KHz or +/- 15 KHz. ● 8-pole quartz filter and a 4-pole ceramic filter gives more than 80 dB rejection at 2X channel bandwidth. ● Frequency trimmers for each crystal. ● .2 to .3 μ volt for 20 dB quieting. ● Dual-gate MOSFETS and integrated circuits. ● Self-contained speaker and external speaker jack. ● Mobile mount and tilt stand. ● Anodized alum. case, 6"x7"x1 3/8".

Model FMR-250-11 price: 135-180 MHz \$109.95
181-250 MHz \$119.95

Price includes one .001% crystal. Additional crystals \$6.95 ea.

UHF 20 dB MIN. GAIN
3 to 5 dB MAX. N.F.

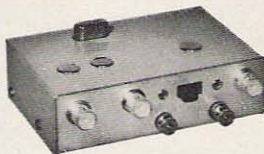

This model is similar in appearance to our Model 407 but uses 2 low noise J-FETS in our specially designed RF stage which is tuned with high-Q miniature trimmers. The

mixer is a special dual-gate MOSFET made by RCA to meet our requirements. The oscillator uses 5th overtone crystals to reduce spurious responses and make possible fewer multipliers in the oscillator chain which uses 1200 MHz bipolars for maximum efficiency. Available with your choice of input frequencies from 300-475 MHz and output frequencies from 14-220 MHz. Usable bandwidth is about 1% of the input frequency but can be easily retuned to cover more. This model is now in use in many sophisticated applications such as a component of a communications link for rocket launchings.

Model 408 price: \$51.95
.005% crystal included.

NOTE:

All the items on this page are for operation on 12 VDC. See back issues of 73 Magazine for some of our other products. Still available are our FMR-150-A at \$89.95 and a line of frequency scalars starting at \$99.50.

HOW TO ORDER:

State model, input and output frequencies and bandwidth where applicable. Remit in full, including sales tax if you reside in N.Y. State, direct to Vanguard Labs. Prices include postage by regular parcel post. For air mail or special delivery include extra amount, excess will be refunded.

COMING SOON: .0005% crystal control for 2 meter transceivers for less than 25¢ per channel! Watch for our ads in 73 Magazine.


VANGUARD LABS

196-23 JAMAICA AVE.
HOLLIS, N.Y. 11423

DRAKE



TR-22

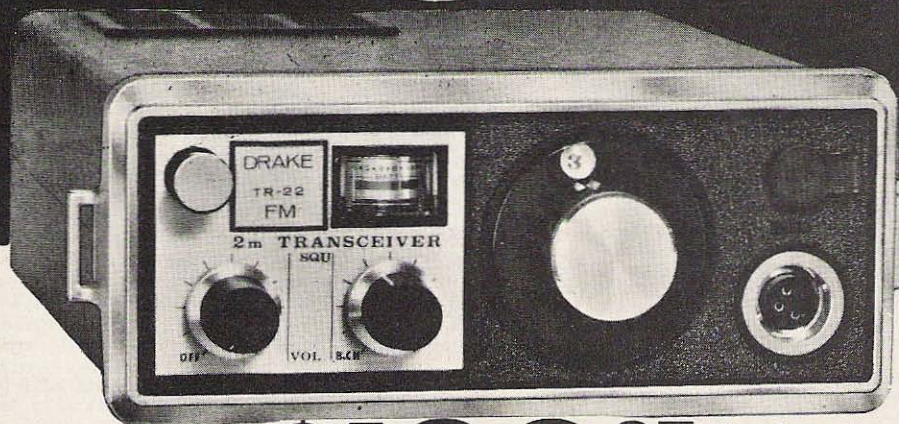

\$199⁹⁵ Amateur Net *

**6 CHANNEL • 1 WATT
.5MV SENSITIVITY
BUILT-IN ANTENNA
BUILT-IN BATT. CHARGER**

**INCLUDES: Dynamic Microphone,
Over-the-Shoulder Carrying
Case, 120 VAC and 12 VDC Power
Cords, Speaker/Headphone Plug,
and 10 Nickel-Cadmium Batteries**

**Add \$7.00 to cover part of new 10% import tax*

Most crystals between 145.830 and 146.970 (30 kHz channel spacing) in stock. \$3.95 each. We will install and set on frequency FREE before we ship your unit. Order today!!

on all in-stock items...

MAIL ORDERS SHIPPED IN 24 HOURS

OTHER DRAKE GEAR IN STOCK:

2C Receiver	\$255.00
2CS Speaker	22.00
2NT Transmitter	164.00
ML-2 2M FM	329.95
W-4 2KW Wattmeter	61.95

R4-B Receiver ..	\$475.00
T4X-B Transmitter ..	495.00
AC-4 Power Supply ..	99.95
L4-B Linear Amplifier ..	825.00
MS-4 Speaker for R4-B ..	22.00

WRITE FOR MORE INFO & USED GEAR LIST

Use Your BANKAMERICARD or MASTERCHARGE

ED




ELECTRONICS, INC.

**PHONE:
(817) 926-5221**

**3850 SOUTH FREEWAY
FORT WORTH, TEXAS 76110**

Semiconductor Supermart

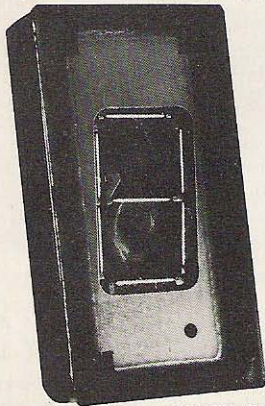• MOTOROLA • RCA • FAIRCHILD • NATIONAL • HEP •



DIGITAL READOUT

At a price everyone can afford

\$3.70

- Operates from 5 VDC
- Same as TTL and DTL
- Will last 250,000 hours.

SPECIAL OFFER

- Digital readout
 - BCD to 7 - Segment Decoder/driver
 - 7490 Decade Counter
- Only **\$8.50**

SUPER BUYS

709 Op. Amp59
741 Op. Amp	\$1.19
723 V. Reg.	\$1.75
Zener 9 V50
Zener 12 V50
Zener 6 V50

DIGITAL BARGAINS FACTORY FRESH TTL IC's

MSD047 decoder/driver for the digital readout	\$3.50
7400 gates35
7441 NIXIE driver	\$1.95
7490 decade counter	\$1.40
7475 quad latch	\$1.40
7495 shift Reg.	\$2.00
7493 divide by 16	\$1.90
74121 monostable	\$1.80
7473 dual flip-flop85

POPULAR IC's

MC1550	Motorola RF amp	\$1.80
CA3020	RCA 1/2 W audio	\$3.07
CA3020A	RCA 1 audio	\$3.92
CA3028A	RCA RF amp	\$1.77
MC1306P	Motorola 1/2 W Audio	\$1.10
MC1350P	High gain RF amp/IF amp	\$1.15
MC1357P	FM IF amp Quadrature det.	\$2.25
MC1496	Hard to find Bal. Mod.	\$3.25
MFC 9020	Motorola 2-Watt audio	\$2.50
MFC 4010	Multi-purpose wide-band amp	\$1.25
MFC 8040	Low noise preamp	\$1.50
MC1303P	Dual Stereo preamp	\$2.75
MC1304P	FM multiplexer stereo demod	\$4.95

TRANSISTORS


MPF102	JFET	\$.60
MPF105/2N5459	JFET96
MPF107/2N5486	JFET VHF/UHF	\$1.26
MPF121	Low-cost dual gate VHF RF85
MFE3007	Dual-gate	\$1.98
2N5188	79
3N140	Dual-gate	\$1.95
3N141	Dual-gate	\$1.86

PLESSEY INTEGRATED CIRCUITS GREAT FOR SSB RCVRs AND XMTRS

SL610	low noise 150 MHz RF good AGC	\$5.65
SL612	low distortion IF good AGC \$5.65
SL621	AGC generator for SSB rcvrs \$8.30
SL620	AGC gen. for SL630 Audio \$8.30
SL630	multipurpose audio amp \$5.35
SL640	top performing balanced mixer	\$10.88
SL641	low-noise rcvr mixer \$10.88

MOST MOTOROLA, FAIRCHILD, RCA, HEP & NATIONAL INTEGRATED CIRCUITS, FETS, OTHER TRANSISTORS AVAILABLE. WRITE WITH YOUR NEEDS.

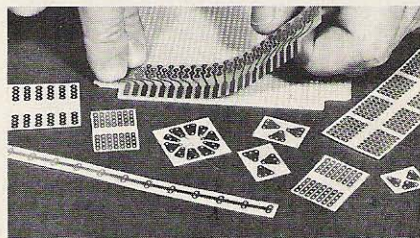HEK-2 FET EXPERIMENTERS KIT Contains HEP-801, HEP-802, HEP-50, HEP-51 and instructions for 9 Projects **\$3.95**



INSTANT CIRCUIT BOARDS

NO ETCH - NO MESS - NO FUSS CIRCUIT-STIK is a complete system of component sub-elements and materials designed to work together to produce instant circuit boards that are as durable as regular circuit boards. CIRCUIT-STIK ELIMINATES: drilling, photo work, and etching. Just stick the pressure sensitive sub-elements down on pattern G Vectorboard. They stick down firmly, withstand soldering temperatures, yet can be picked up and moved for circuit changes. In fact, they make building projects with integrated circuits and transistors a real breeze. Sub-elements are available for 8, 10, and 12-lead IC's, dual-in-line IC's, all transistors, plus pressure sensitive copper tape, etc. Applications data available. Three assortments are available:

CS20 \$5.50, CS30 \$7.95, CS40 \$9.95.



Please add 35¢ for shipping
CIRCUIT SPECIALISTS CO.
Box 3047, Scottsdale, AZ 85257
FACTORY AUTHORIZED
HEP-CIRCUIT-STIK
DISTRIBUTOR

Exciting New Products

.....FREQUENCY MARKER STANDARD

Advanced marker, with seven selectable outputs: 5, 10, 25, 50, 100, 200 or 400 KHz. Complete with highly accurate 400 KHz crystal. Buffered oscillator. Zero beat hold's on each marker position. Harmonics beyond 150 MHz. Low level logic used in divide chain. High noise level immunity output amplifier. Engineered to eliminate ghost markers. Adjustable to WWV. HF phono output jack.

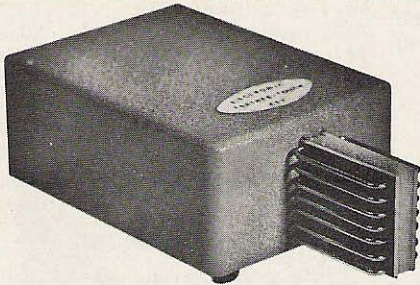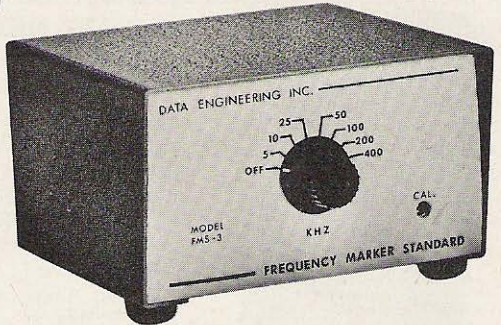- Wired, Tested & Calibrated \$32.95
- Wired, Tested & Calibrated \$22.95
(Less cabinet, switch & battery holder)
- Kit \$19.95
(Less cabinet, switch & battery holder)



.....SPACE-MATIC 21 KEYER

At last—a keyer that automatically sends all code elements: Dot, dash, dot space, dash space, character space and word space in an instant self-starting, self-completing mode. Advanced memories respond to momentary key closures or to closures extending to the end of the dot/dash space with a guarantee of no missed or extra dot or dash. Iambic operation. Dot and dash memories, adjustable weighting, jam-proof spacing, tone control, monitor/speaker, 3.5 to 85 wpm. Use any twin level (iambic operation) or single level key.



\$89.50 Complete

ELECTRONIC FEATHER TOUCH KEY....

Completely solid state key eliminates forever such mechanical problems as contact bounce, proper adjustments and dirty contacts. Designed especially for solid state keyers. A mere touch of your fingers provide instant keying of the twin level key. Finger touch is detected by a monolithic level detector. Transistor outputs. Not affected by damp or dry fingers. Weighted to prevent "walking". Can be battery operated.

\$19.95 Complete

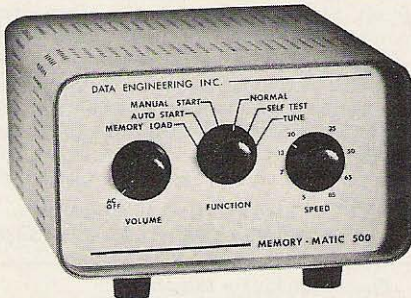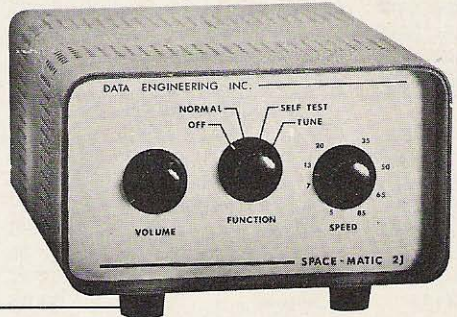\$22.95 With SPDT Switch (Required with Memory-Matic 500)



MEMORY-MATIC 500 KEYER.....

The newest and most advanced keyer. The keyer which gives you 500 bits of storage for automatic calling, contest operation, etc.—just right for on-the-air contacts. Instantly store any message, by keying the memory at any speed or weighting ratio. Stored characters can be automatically transmitted once, or on a repetitious basis. Complete with memory near-full and over load alarms. Indispensable for the serious code, contest or traffic operator. Also includes all features of the Space-Matic 21 listed above.


\$198.50 Complete

ALL ITEMS SOLD WITH A FIVE-YEAR GUARANTEE and are shipped prepaid.

SEND FOR FREE BROCHURES

DATA ENGINEERING INC.

Box 1245 • Springfield, Virginia 22151

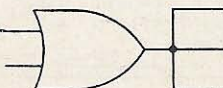

To Troubleshoot
FAST & EASY



use: Serviset
Model EC
PATENTED

FREE INFORMATION
Intro-Price
\$29.95 Postpaid

A precision engineered professional quality electronic test instrument. Ideal for field or bench servicing of all types of Communications gear.

CHECKS: sync, sweep, video, audio circuits, high voltage supplies (DC, RF or Pulse), low voltage supplies, coils, capacitors, resistors, tubes, transistors, diodes, transformers, speakers, etc. Will locate trouble to a particular stage, determine defective component and can actually be clamped in circuit to restore circuit operation temporarily in 80% of component or tube defects. Ideal for locating and confirming intermittents.

SPECIFICATIONS:

RF & AF Signal Tracer, RF & AF Signal Injector, AC & DC Voltage Indicator 0/60/550/20,000 DC Polarity Indicator 60/550/20,000 volts, Lo ohms 0-5. Hi ohms 0-500k-20 megohms. Tests Condensers, .00025-12 mfd., Tests Resistors 2 ohms-20 megohms, 2 Capacitance Sub ranges .01-.1 & 4-40 mfd., 3 Resistance Sub ranges 50-500 ohms, 5k-25k, 100k-1 meg.

SERVISSET MODEL E-C will outperform any tester of its size, weight, & price ANYTIME-ANYWHERE.

IDEAL for: Professionals, Amateur Repair men, Ham Radio Operators, **STUDENTS**, appliance repairmen, etc. Will complement your existing equipment and will outperform other testers costing many times more.

**30-DAY UNCONDITIONAL MONEY BACK GUARANTEE, 90 DAY PARTS WARRANTY
ORDER TODAY**

Manufactured by


LEE ELECTRONIC LABS, 88 Evans Street, Watertown, Mass. 02172

NEW CT-1

From



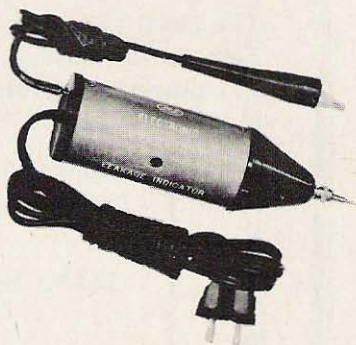Will allow you
to Dynamically test all
types of capacitors.



The Model CT-1 features a built-in electronic power supply providing BOTH AC and DC Test Voltages in a special circuit with highly sensitive NEON type leakage indicator. The CT-1 permits quick, accurate testing of condensers for leakage or shorts with actual DC voltage applied and readily indicates intermittent OPEN condensers with AC applied. Self-regulating power supply circuit provides tapered forming current to suit particular requirements of capacitor under test. Special circuit re-forms and polarizes electrolytic and tantalum capacitors under test. High sensitivity permits determination of condenser dielectric breakdown before leakage causes major shut-down.

ONLY \$16.95 postpaid
Capacitance Range: .00025 - 1000 mfd.
Sensitivity: Over 200 MEGOHMS
Dealer Inquiries Invited



LEE ELECTRONIC LABS., CO.
88 Evans Street
Watertown, Massachusetts 02172

\$1.00, off any
and ALL LEL equipment
(Limited time only)
Buy BOTH & SAVE \$2.00!!

Please rush me:

E-C at \$29.95

C-T at \$16.95

Free information

I enclose payment in full.

Send C.O.D. and I will pay postage.

Name _____

Street _____

City _____

State _____ Zip _____

G·A·M *presents*

The GAM Line
Famous for POWER
... powerful performance,

VHF/Antennas
BASE/MOBILE

144 to 160 MHz

3.7 db




TG-2-R



TG-2

3.7 db

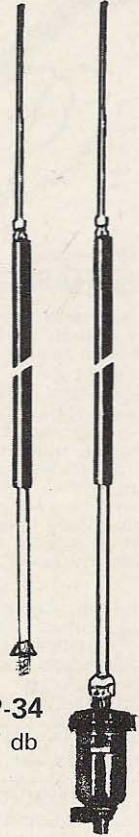

MP-34
6.7 db

TG-4-MS
6.7 db

Mobile

- TG-2-R List \$30.00
- TG-2 List \$20.50
- TG-4-MS List \$50.00
- MP-34 List \$33.50

TG-3 3.7 db
List \$35.20



TG-3-S 6.7 db
List \$66.00

14.9 db Omni-Directional Gain

In System Performance

MODEL
TG-5S



List
\$95.00
8.2 db

GAIN OVER ISOTROPIC RADIATOR

G·A·M *Electronics* inc.

191 VARNEY STREET
MANCHESTER NH 03102
TEL. (603) 627-1010

TWO NEW ENTRIES IN THE 2m FM FIELD

Adirondack Radio Supply, Inc. is happy to announce the introduction of the latest in 2 meter FM gear.

Model IC-20 with the following features:

Manufactured by a pioneer manufacturer of 2 meter FM gear.

2 outputs — 1 watt and 10 watt.

12 Channels — tweaking condenser on both transmit and receive crystals.

RF meter.

S meter.

Adjustable deviation control — 3 to 16 KHz.

Sensitivity — Better than 0.4 μ V 20 db quieting.

Matching power supply available with discriminator meter.

Current — Low power 1.2 amp. at 13.5 volts.

High power 2.1 amp. at 13.5 volts.

Crystals — supplied with 3 channels.



IC-3P power supply\$49.50 Net IC-20 (as shown above)\$299.00 Net

Model IC-21 with the following features:

24 Channel capability.

A new high — very useful in these days of new repeaters going on the air constantly.

Front panel — P.A. tune control — a real advantage to get maximum output.

Separate S and discriminator meter \pm 5 KHz — panel.

R.I.T. — control on receive — either 1 watt or 10 watt output.

S and SWR meter combined.

Remote VFO plug.

12 volt DC or 110 volt AC operation.

AC and DC cable supply.

Discriminator meter — a real addition.

Crystals — supplied with 4 channels.



IC-21 \$389.00 Net

Both of these superb units are manufactured by Inoue Communication Equipment Corp. of Osaka, Japan, already well known to 2 meter FM users.

Send your order today.

This is an entirely new approach in 2 meter FM gear. Just imagine 24 channel capability, SWR meter and S meter, plus netting condenser on each transmit and transceive crystal, plus many other features original with this unit.

ADIRONDACK RADIO SUPPLY, INC.

185 West Main Street, Amsterdam New York 12010

Mann

CHRISTMAS SPECIALS

GENERAL ELECTRIC MOBILES complete with accessories

ME 13	40-50MHz	30Watt	6/12 Vibrator Supply\$99
ME 16	40-50MHz	60Watt	6/12 Vibrator Supply119
ME 33	150MHz	30Watt	6/12 Vibrator Supply109
ME 36	150MHz	60Watt	6/12 Vibrator Supply129

WHILE THEY LAST

KAAR Model DT76 150MHz 120Watt Output Mobile all transistorized except 8624 Final Output

New in original factory cartons, no factory warranty

Complete with manual\$299
6 Channel Kit for DT7639

We thank you for your patronage during 1971, and we sincerely hope you will give us the opportunity to serve you in 1972.

We are going to move into larger facilities in 1972. Watch for our new address in coming issues.

WRITE FOR FREE CATALOG

Mann Guarantee

Money refunded without question if equipment is returned within seven days from shipment, undamaged, freight prepaid.

Conditions of Sale


Unless otherwise specified, equipment is used, and is sold as-is. All items shipped FOB Tarzana, California. Crystals, ovens, antennas not included unless specifically stated in catalog. All equipment is sold on a first-come, first-served basis.

Mann COMMUNICATIONS


18669 Ventura Blvd.
Box 138 Tarzana, CA 91356
(213) 342-8297

2837 North 24th Street
Phoenix, Ariz 85008
(602) 955-4570

*Merry
Christmas*

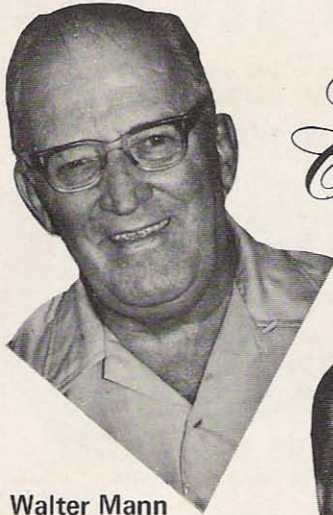

Walter Mann

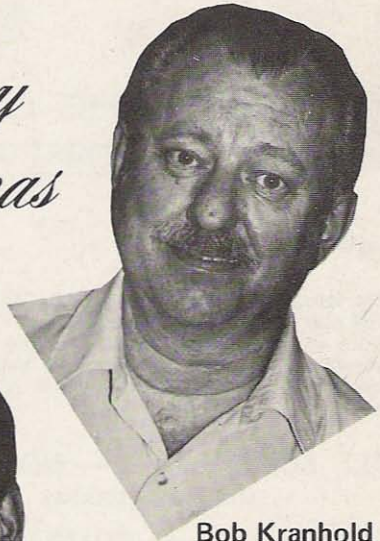

Bob Kranhold



Jim Mann



Jim Mann II




Tom Hicks

FROM *Mann* COMMUNICATIONS

18669 Ventura Blvd.
Box 138 Tarzana, CA 91356
(213) 342-8297

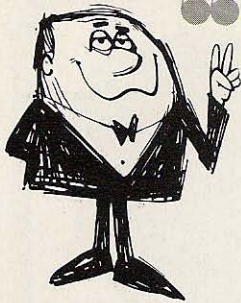2837 North 24th Street
Phoenix, Ariz 85008
(602) 955-4570



"2" Rigs in one!

THE CTR-144 by COMCRAFT FIRST AM-FM TWO METER TRANSCEIVER

No longer is it necessary to choose between AM and FM on two meters. Now you can have both in one compact unit. Join the gang on the new FM repeaters yet still be able to "rag chew" with old friends either AM or FM anywhere in the two meter band.



ALL SOLID STATE — NO TUBES
MADE IN AMERICA

\$389.95 SHIPPED POSTPAID†
INCLUDES 146.94 MHz CRYSTAL

COMPARE THESE FEATURES

TRANSMITTER:

- Built-in VFO (Frequency converted for stability*)
- AM and FM both crystal and VFO
- Four transmit crystal positions (8 MHz)
- 12 watt input AM and FM
- High level transmitter modulation on AM
- Bandpass coupled transmitter requiring only final tune and load
- Three internal transmit crystal sockets with trimmers for netting
- One transmitter crystal socket on the front panel

RECEIVER:


- Double conversion
- Crystal controlled first conversion
- MOS FET receiver front-end
- Integrated circuit limiter and discriminator for FM
- Envelope detector and series gate noise clipper for AM
- Built-in squelch for both AM and FM

GENERAL:

- Separate transmitter and receiver tuning
- Built-in 115VAC power supply
- Direct 12VDC operation for mobile or portable operation
- Optional portable rechargeable snap-on battery pack available
- "S" Meter also used for transmitter tune up
- Military style glass epoxy circuit boards
- Anodized lettering and front panel
- Baked epoxy finish on the cabinet

DIMENSIONS:

- 10 1/4" W x 6 1/4" H x 7 1/2" D

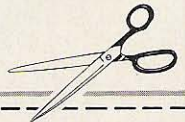

†U.S. ONLY

*VFO operates from 7 to 9 MHz and is converted to 72 to 74 MHz using a 65 MHz crystal oscillator. 72 to 74 MHz is then doubled to 2 meters.

THE CTR-144 IS AVAILABLE
FACTORY DIRECT



COMCRAFT COMPANY

P. O. BOX 266 — GOLETA, CALIF. 93017


- I enclose \$389.95. Please ship a CTR-144 and Manual.
- I enclose \$2.50. Please send CTR-144 Manual only. Calif. residents add 5% sales tax.
- Please send illustrated brochure and accessory list.

FROM: NAME _____
 73 STREET _____
 MAG CITY _____ STATE _____ ZIP _____

2 meter FM Mobility at unheard-of Savings

AVCOM FM-201 SOLID STATE TRANSMITTER MODULE

Starts You on Your Way!

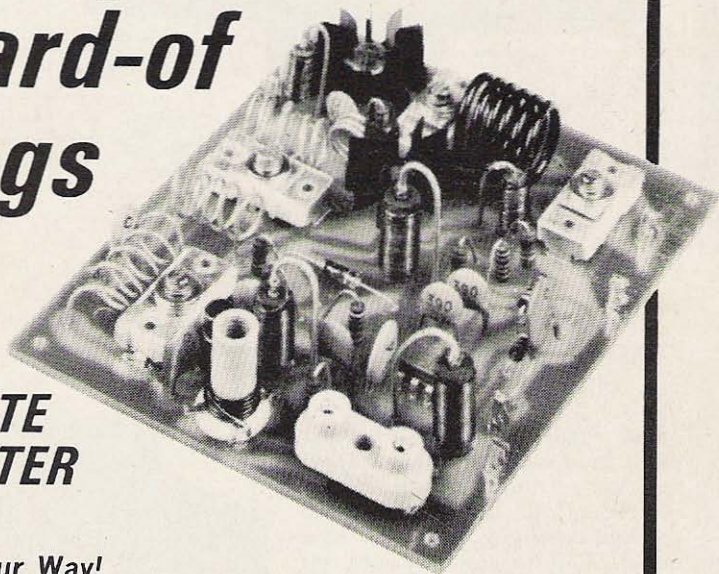

Only **\$49.95** COMPLETE — Not a Kit 90-Day Warranty

- Ideal for Repeater use! Just add ant., mike, Xtal and 12-16 volts DC.
- Cut Transceiver cost as much as 50%. Add police band receiver to AVCOM FM-201 Transmitter. Your rig can cost under \$100 while others are priced up to \$250.
- Already have a 2 Meter FM rig? Increase your fun, save installations and removals of your high priced mobile rig with a low-cost second rig.
- Walkie-Talkie compactness — glass epoxy printed circuit board is only 3" x 3½".

SPECIFICATIONS:

Mike Pre-Amp: high impedance input, integrated circuit.

Operates anywhere between 12 and 16 volts DC.

4.0 KHZ frequency deviation typical. 1-Watt DC input to final transistor

Order Your FM-201 Transmitter Module Today!

LM-210 10 Watt POWER Amplifier Module \$29.95

AVCOM, Inc.

P.O. BOX 29153 COLUMBUS, OHIO 43229

You Can't Buy These Exclusive Brands Just Anywhere — Only at Our 1200 Stores



Allied AX-190 Ham Receiver. The "professional" addition to any Ham Shack! 11-band crystal-controlled coverage of 3.5 to 30 MHz. "Blank channel" provision for specialized monitoring from 3.5 to 10 MHz. Every solid-state feature for AM/SSB/CW reception, user-designed controls for easiest operation anywhere! Has 25/100 kHz calibrators, 200-Hz visual dial accuracy, AGC, ANL, better than 500 Hz per hour stability. A honey.

WITH CRYSTALS
249⁹⁵

Plus Speaker

AX-190/SX-190 Speaker 19.95

Allied SX-190 Communications Receiver. Every feature of the AX-190 above, but for coverage of worldwide shortwave. Two "blank" channels!

WITH CRYSTALS **249⁹⁵** Plus speaker

Allied "Patrolman PRO-7" Automatic Scanning VHF Monitor. Check the "Action Airwaves" with the finest under \$100 rig on the market! Automatic scanning of up to 8 crystal-controlled channels between 148 and 174 MHz, crystal filter, latest FET/IC circuit. Automatic or manual selection, 2-second scan delay to prevent missed call-backs, DC gated squelch, special channel "lock-out" buttons, more. Dual-powered for car, home.

99⁹⁵



Realistic DX-150A Communications Receiver. Great for any Ham Shack, priced low enough for the beginning SWL. FET and mechanical filter pull in stations from all over with startling clarity, 11 front-panel controls for complete operating coverage of 535 kHz to 30 MHz; illuminated bandspread for 160-10 meters and separate logging scale. OTL audio and built-in speaker for really clear sound, fast and slow AVC, variable pitch BFO, and cascade RF stage. Battery, AC or 12 VDC operation—keep in touch with anywhere from anywhere!

119⁹⁵



Radio Shack and Allied Radio — The Nationwide Communications Supermarket!

A Antenna Tuner. Matches transmitter and antenna impedance between 10 and 1000 ohms. Handles up to 500 watts of RF power. Positive coax connectors.


B 2-Position Coax Switch. Perfect for dual antenna setups. Instantly switches from one antenna to another without changing leads. Handles up to 500 watts power. Compact, for any installation!

C Low-Pass TVI Filter. Interference-free transmission and reception. Attenuation starts at 41 MHz, is 3 dB down at 43 MHz, 6 dB at 45.5 MHz, 25 dB at 54 MHz. Insertion loss is only .25 dB. Metal housing.

D Code Practice Oscillator. Low-cost aid for beginners or experienced CW fans. Tone and light signals, self-contained speaker pitch control. Increases speed and accuracy — helps you become a "big-time" CW operator!


E Code Course. Easy-to-follow lessons designed to advance you quickly to a speed of 15 wpm. With basic code book. Take your choice of 12-lesson cassette or 10-lesson 33 1/3 rpm record.

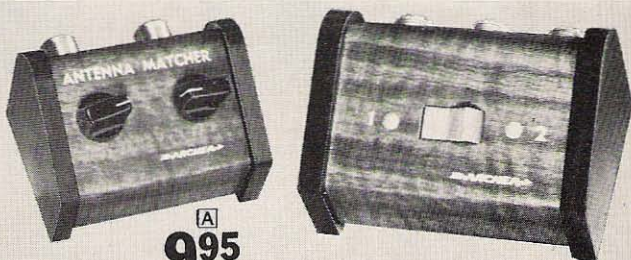F 6-Position Coax Switch. Rotary shorting switch handles up to 4000 watts peak envelope power. Lets you hook up six antennas to a single transmitter. Speeds band switching; simplifies antenna comparisons.



A
995

B
595

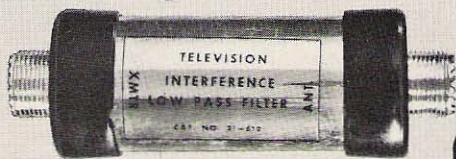

C
695




D
895

350
LP

E
495
Cassette



F
995

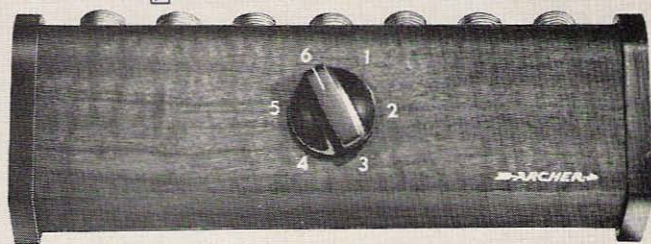

**FREE
Catalogs!**

See what's REALLY new in electronics!
Get your copies at our store near you... find us in the phone book.




RADIO SHACK
and

ALLIED RADIO STORES

TANDY CORPORATION COMPANIES

2725 W. 7th St. • Fort Worth, Texas 76107


Gated Calibrated Marker Generator

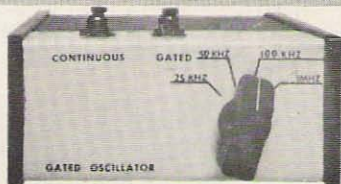

The K-OSC-G1 is a gated generator on and off 3 times per second making it easily recognized on today's crowded bands. Frequency — 1 MHZ, 100 KHZ, 50 KHZ, 25 KHZ. Accuracy — High Precision 1 MHZ xtal., 001%. Gate time — 3 Pulse per second. Harmonics — up to 200 MHZ. Output — Square wave 3.5 PP. Electrical Description — All solid state, printed circuit on 1/16" glass board. ICs 2 gates, 3 dividers, and 1 transistor. A ceramic trimmer allows zero-beating WWV. Physical description — The K-OSC-G1 Generators are small, structurally rigid yet light-weight instruments which are designed for portability. The instrument is enclosed in a 3 color vinyl covered metal & plastic cabinet. Dimensions are 2 3/8" x 5 1/8" x 6".

K-OSC-G1 Wired and Calibrated \$45.50
 K-OSC-G1K Kits all parts and case
 (less batteries) \$35.50

KD-10 PRESCALER

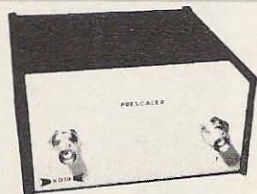

The model KD-10 is a sensitive prescaler with a divide-by-ten scaling factor. This prescaler is designed to extend the range of the many surplus 1 meg. counters. It has a front end sensitivity of .05 volts, and flip-flop speed of 20 MHz. Has a square wave output of 2.5 V PP. KD-10 has its own built-in power supply (regulated).

HEP 170 2.5A 1000V 10/\$3.50 20/\$ 6.00
 1N 914 Signal Diodes 10/\$3.00 20/\$ 5.00
 7490 Decade Counter \$2.10 5/\$ 1.00
 7441 Decimal Decoder/Driver . \$3.10 5/\$15.00
 UL 914 Gate \$.55 10/\$ 5.00
 UL 923 JK Flip-Flop \$1.50 10/\$ 8.00

KD-10-K kit — Board and all parts (except cabinet and coax connectors). \$22.50
 KD-10 Complete with case and tested. . . \$33.50
 Cabinet and coax connectors (Same type cabinet as K-OSC-G1). \$7.50
 KD-100-K kit — Board and all parts (except cabinet and coax connectors). \$25.50
 KD-100 Complete and tested. \$36.50
 KD-100 Divides by one hundred for use with 100 KHz counter.

DECIMAL COUNTING & READOUT KIT




K-DCU's are small readout kits which include amperex tubes, 7490 dividers, 74141 decoders and circuit board. The tubes and IC's may be plugged or

soldered in as you desire. Boards are 1 1/8" x 3", 5 1/8" x 3" and 8 1/8" x 3".

K-DCU-1 Kit 1 tube, Board and IC's \$12.50
 K-DCU-5 Kit 5 tubes, Board and IC's . . . \$55.00
 K-DCU-8 Kit 8 tubes, Board and IC's . . . \$80.00
 IC Sockets for above @ \$.50
 Amperex tube sockets
 (sold with board only). @ \$.60


KEO-4 & 5 Oscillator 100 KHz 50 KHz 25

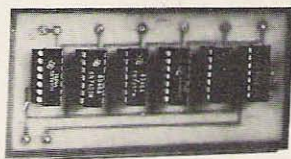

100 KHz 50 KHz 25 KHz RTL circuit followed by 1 stage amp. Used for band edge marker, clock driver for dividers below, Driver for 10 KHz divider audio frequency interperlation, etc. Power requirement 3-3.5 V 12 ma. deliver 2 V PP. Will operate as low as 2 V DC.

KEO-4 2 1/2" x 4" glass board wired, tested and Cal. \$15.95
 KEO-5 MHz 2 1/2 x 4" board Wire Test Cal. . \$15.95

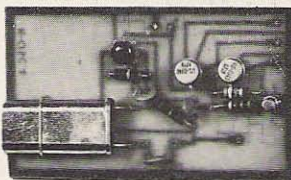KED-1 & 2 Divider Boards and Sockets Kits




TTL Divider board 10 MHz to 1 Hz designed to use with KEO-4 or 5 clock for counters or marker. Power requirements 4.75-5.5 VDC. 300 ma. uses SN7490 ICs.

KED-1 4 1/8" x 2" glass board 1 MHz to 1 Hz or 100 KHz to 1 Hz (without sockets or ICs) \$ 4.00
 Same as above with sockets & ICs \$18.50
 KED-2 4 1/8" x 2" glass board 10 MHz to 1 Hz (without sockets or ICs) \$ 4.50
 Same as above with sockets & ICs \$22.00

ENTERPRISES

1401 North Tucker, Shawnee OK 74801 Ph: 273-1598

IT'S ONE FOR THE ROAD!

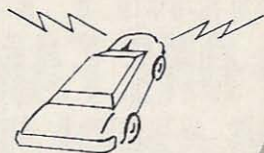

"MODEL A"


2-METER AMATEUR BAND
VHF-FM

Here's what the amateur operator has been looking for.

It's new, all new! It's a State-of-the-Art, all solid state 2-meter ham rig which we designed, we built, we tested and we priced the Simpson way. Low.

PUT THIS BABY IN YOUR CAR! THE EASY WAY!

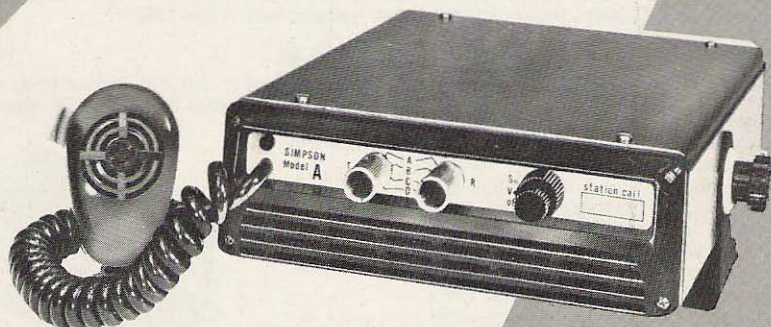Time was when you had to modify to go mobile. Not with the model A! It's as mobile as its name. Enjoy 2-meter mobile along with the thousands of others who are enjoying this fast-growing part of amateur radio.



- COMPLETE WITH MICROPHONE, MOUNTING BRACKET, CRYSTALS
- CHANNEL 1 - 146.34-146.94
- CHANNEL 2 - 146.94-146.94

AMATEUR NET PRICE

\$249

fob Miami

(INCLUDES 2 PAIR CRYSTALS)

- Over-size front mounted speaker
- Press-to-talk microphone with coil cord
- 8½ in. wide x 2½ in. high x 11 in. deep
- G-10 glass epoxy boards.

PRICES & SPECS SUBJECT TO CHANGE WITHOUT NOTICE

TUNING FREQUENCY RANGE: 144-148 Mhz.

FREQUENCY STABILITY: 0.001%
(from -30° to +60 C)

NUMBER OF CHANNELS: 4 Independent selector switch

USABLE SENSITIVITY: 0.5 uv or less for 12 db SINAD


SPIRIOUS RESPONSES ATTENUATION:
Greater than -60 db.

AUDIO OUTPUT: 2.0 watts with less than 10% distortion.

POWER OUTPUT: 6 watts into 50 ohm

SIMPSON ELECTRONICS, INC.
2295 N.W. 14th St. • Miami, Fla. 33125 • Ph: 633-3261

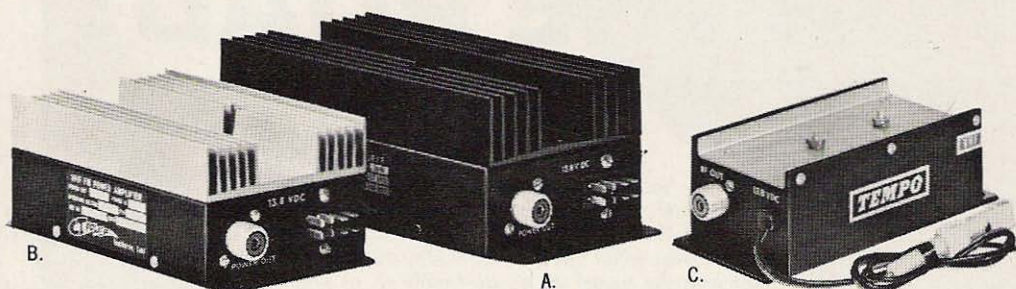TWENTY TWO STAR PERFORMERS IN ONE FAMILY... HIGH POWER FM AMPLIFIERS BY TEMPO



A. CT 1002-3

A true powerhouse. 10W input gives a guaranteed 120W output (In fact, typical output runs as high as 140W). Operates directly from a 12 VDC power source. Antenna switching is automatic when as little as 1.5W of RF drive is applied. The amplifier incorporates Balanced Emitter transistors and state of the art design practices, making it virtually immune to destruction due to high VSWR or misloading conditions. Features include THREE 40W output transistors plus one 40W driver transistor, low loss input coax connector (complete with RF cable), low loss solid state antenna switch (.5 db or less typical) and Spurious response: -60 db typ. All amps include a built in power output monitor for use with a Remote Control Head and may be used anywhere in the 2 meter band without the necessity of retuning. Only 9 3/8" x 4" x 3", the CT 1002-3 can be installed almost anywhere. Since there are no switches or meters, it may be mounted under a seat, in the trunk or in a desk drawer. Power output: 120W. Input voltage: 13.8 VDC. Current required: 15-17 amps. Drive required: 5-15W for 100-140W out. Price \$220.00

B. CT 802-2

A superior quality VHF FM two meter power amplifier.

Only 6 1/2" x 3 1/2" x 3", yet contains all the features of the CT 1002-3 and provides a minimum of 80W output and typically 90W. Price \$160.00

C. CT 252-A2

Unbelievably small... but outperforms many of the big ones. 1W input delivers an easy 25W power output. Only \$85.00

CT 445-30

1 or 4W input... minimum 30W output. 450 MHz UHF. Same features... same superior quality as CT 1002-3, including low loss solid state antenna switch. Ideal for use with 1 watt handi-talkie or other low power UHF transceivers.



TEMPO OFFERS THE MOST COMPLETE LINE OF 'SOLID STATE' AMPLIFIERS AVAILABLE

MODEL NUMBER	POWER INPUT	POWER OUTPUT min.	BAND	MODEL NUMBER	POWER INPUT	POWER OUTPUT min.	BAND
CT6-30	1 to 10 W	30 W	6 M	CT252-A2	1 W	25 W	2 M
CT6-60	1 to 10 W	60 W	6 M	CT352-2	8 W	30 W	2 M
CT6-100	1 to 10 W	100 W	6 M	CT 1250	25 W	100 W	2M
CT1202-2	25 W	125 W	2 M	CT 220-20	4 W	20 W	220 MHz
CT1002-3	5-10 W	100-120 W	2 M	CT220-40	4 W	40 W	220 MHz
CT602-2	5-10 W	60 W	2 M	CT220-80	4 W	80 W	220 MHz
CT 602-B2	1 W	60 W	2 M	CT445-1	100 mw to 300 mw	1 W	440 MHz
CT 802-2	5-10 W	80 W	2 M	CT445-5	200 mw to 1 W	5 W	440 MHz
CT452-2	5-10 W	45 W	2 M	CT445-15	1 to 5 W	15 W	440 MHz
CT452-B2	1 W	45 W	2 M	CT445-30	1 to 10 W	30 W	440 MHz
				CT445-50	1 to 10 W	60 W	440 MHz

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
 931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
 Butler, Missouri 64730 816/679-3127

Henry Radio

IT'S NEW...IT'S UNIQUE...THE TEMPO CT 220TR AM/FM TRANSCEIVER



CT 220TR


Don't let its small size fool you (it's only 7" wide). This little giant outperforms its big brothers. Look at these specifications... then look at the low price. Completely

solid state. 220 to 225 MHz operation. Transmitter: Positions for 5 internal crystals (not supplied). 1 external crystal position and VFO input. Power Output: 4W FM, 1½W AM. FM internally adjustable to 15 kc. Power Requirements: 13.8 VDC XMT 1.2 amps FM .5 amp AM, 25 ma Stby. Receiver: Tuning meter for AM and FM. .6 micro-volt for 20 db quieting. Tunable or pre-set to five internally adjustable frequencies. FM is detected by limiter discriminator, 6 db at 15 kcs.

1W audio output — 5% distortion. Double conversion, 10.7 MHz and 455 KHz. ACCESSORIES AVAILABLE: AC Power Supply & Speaker. Internal amplifier to increase output to 20W FM and 8W AM. External high power amplifiers for FM operation. (CT 220-40 or CT 220-80 suggested.) Introductory price: \$179.00

CT 220-20 AM/FM Amplifier

A truly significant new amplifier, the CT 220-20 measures only 6½" x 2" x 3". Operates from a 12 VDC power source. Antenna switching is automatic when as little as ½W of RF drive is applied. Incorporates Balanced Emitter transistors and state of the art design practices. 4W input provides 20W output on FM. 1½W input provides 8W output on AM. May be used anywhere in the 220 MHz band without the necessity of retuning.

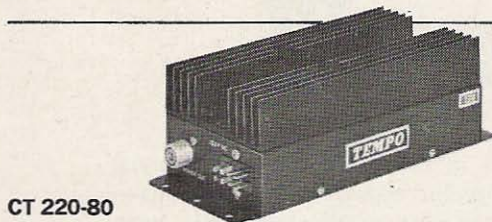

CT 220-80

Another fine 220 MHz FM amplifier. 4W input/80W power output.



CT 220-40

A superb little 220 MHz FM amplifier. 4W input/40W power output.

CT 100BP

High current regulated power supply. 17 amps at 12.8V, includes speaker.

More exciting items coming from Tempo CT

CT Solid State Repeater: 220 MHz, 110 VAC or 12 VDC

A superior quality repeater, priced well below all others... offering true emergency operation. A 12V battery is maintained at full charge, takes over automatically in the event of an AC power failure.

FEATURES: Transmitter power-20W output. Receiver sensitivity is .5µv for 20 db quieting, has 6 pole monolithic crystal filter, minimum spurious and image rejection 70 db. Front panel discriminator monitoring meter (calibrated in Kc). Provisions for local mike, local speaker included. Standard 19" rack mount, 8" high. Transmitter & receiver encased in separate shielded compartments. Requires 2 antennas and 12V storage battery. (available in spring)

CT 2 Meter Transceiver:

Same specifications as 220 repeater.

CT 2 Meter Repeater: 8W AM, 15W FM.

Crystal controlled and tunable receiver. .35µV sensitivity. Provision for toneburst. 10.7 MHz crystal filter results in 70 db spurious and image rejection, adjacent channel selectivity, 70 db at 30 Kc. 11 channel transceiver.

CT 450 MHz Transceiver: 4W FM Specifications essentially same as 2 meter transceiver.

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

Henry Radio

The only
monitor receiver
you'll ever need



\$139.95* WITH RF MODULE TO COVER ANY ONE BAND

\$159.95* WITH RF MODULES TO COVER ANY TWO BANDS

ALL-NEW ***Bearcat III***

LATEST FROM THE ORIGINATOR

Meets present and future needs in any locality • Scans any 8 frequencies in any one or two public safety/business bands—low, high, UHF • Interchangeable plug-in RF module for each band. • Complete band coverage without the frequency spread limits of other makes • Any mix of frequencies in two bands without wiring changes • Built-in 3" x 5" front speaker • American built and backed by Electra, originator of the scanning-monitor receiver. Fast factory service if ever needed • Complete with one or two RF modules, mobile mounting bracket and cord for 115 VAC and 12 VDC • See it! Hear it! Now at better dealers.


**Plus crystals at \$5 each. Additional RF modules \$20 each.*


Electra CORPORATION
CUMBERLAND, INDIANA 46229

G&G MILITARY ELECTRONICS CATALOG

24 PAGES, crammed with Gov't Surplus Electronic Gear — the Biggest Bargain Buys in America! It will pay you to **SEND 25¢** for your copy — Refunded with your first order.

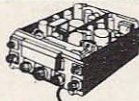BC-645 TRANSCEIVER 15 tubes, 435 to 500 Mc. Easily adapted for 2 way voice or code on Ham, Mobile, Television Experimental, and Citizens Bands. With tubes, less power supply in factory carton. **BRAND NEW** \$16.95



TRANSMITTER has 4 tubes: WE-316A, 2-6F6, 7F7
RECEIVER has 11 tubes: 2-955, 4-7H7, 2-7E6, 3-7F7
RECEIVER I.F.: 40 Megacycles
SIZE: 10-1/2" x 13-1/2" x 4-1/2". Shpg wt 25 lbs.

SPECIAL PACKAGE OFFER: BC-645 Transceiver, Dynamotor and all accessories, including mounting. UHF Antenna Assemblies, control box, complete set of connectors and plugs. **Brand New** \$26.95

TG-34A CODE KEYS, self-contained, automatic, reproduces code practice signals from paper tape, 5 to 12 WPM. Built-in speaker. **Brand new** with tech manual, take-up reel and AC line cord \$24.50
Code practice tapes for above P.U.R.



TG-5B TELEGRAPH SET for code communications or code practice. Portable, with hinged lid. Two or more units operate up to 25 miles apart. Bell call system, 1000 cycle howler, key, headpiece, canvas case, book. **Size** 5-1/2 x 5-1/2 x 10". **NEW** \$8.95



BC-603 FM RECEIVER converted for operation on 35 to 50 Mc. Checked out, guaranteed. **LIKE NEW**, with tubes \$39.50



RAY-3 NAVY RECEIVER Crystal controlled superhet with dyn. power supply. Audio system designed for modulation frequencies 20 Khz to 120 Khz; not for voice. Tubes: 6AC7, 6A8, 6SJ7, 12SR7. Weston output meter on front panel.
Model PR6N - 14V DC, like new, with tubes, dyn. . \$8.95
Model PR7NA - 28V DC, like new, with tubes, dyn. \$8.95



BC-223AX TRANSMITTER 25 Watt, CW, MCW, Voice, Crystal control on 4 pre-selected channels, range 2000 to 5200 Kc by use of 3 plug-in units, included. Complete with 5 tubes.
BRAND NEW in original case \$27.50



PE-125AX Vibrator Power Supply 12/24V DC for above, **NEW** \$12.95
PE-135AX Dynamotor Power Supply for above, **NEW** \$14.95

BC-605 INTERPHONE AMPLIFIER Easily converted to home or office intercom system! Uses pair of 1619 tubes, delivering 10 watts of audio power. Massive construction, suitable for shops, factories. Finest parts used. Conv. diagram and instr. included.
BRAND NEW, made by Western Electric **\$2.95**



DUAL AMPLIFIER has two input circuits each feeding a single 6SN7GT twin triode amplifier. Complete with 115V 60 cy. power supply using 6X5GT rectifier. **NEW** \$5.95



AM-26/A1C PHASE INVERTER AMP. 4-tube pushpull power amplifier. Carbon microphone input, hi- ω output. Works on 24V DC. Easily converted to dandy 9-watt amplifier. Complete with tubes and dynamotor.
LIKE NEW \$5.95



WILLARD 2-VOLT STORAGE BATTERY Rated at 20 Amp.-Hours. Model 20-2. Rechargeable. Compact nonspill construction. Lightweight polystyrene container, 3 x 4 x 5 1/2". Shipped dry, uses standard electrolyte. Shipping Weight 3 lbs. **NEW**, each \$2.79



AM-300/A1C PUSH-PULL AMPLIFIER 4-tube PP power amplifier with dynamotor, works on 28V DC. Automatic gain control.
Shpg wt 15 lbs. **LIKE NEW** \$3.95



AN/APR - 4Y FM & AM RECEIVER "FB" for Satellite Tracking! High precision lab instrument, for monitoring and measuring frequency and relative signal strength, 38 to 4000 Mc, in 5 tuning ranges. For 110v 60 cycle AC. Built-in power supply. Original circuit diagram included. Checked out. Perfect.
LIKE NEW \$88.50
All tuning units available for above. P.U.R.



TV-10 UHF TRANSVERTER 28V DC Made by Aircraft Radio Corp. Couples UHF Antenna to VHF transmitter and VHF receiver. Uses 6 tubes: 4/5763 and 2/620L. Includes 8 crystals ranging from 233.8 Mc to 257.8 Mc. **Size:** 11 x 4-1/2 x 4-5/8". **Wt** 5-1/2 lbs.
LIKE NEW, with tubes and crystals \$9.95



R-20 RECEIVER Made by Aircraft Radio Corp, works on 28V, includes 4 tubes: 2/12AW6, 12AX7, 12AT7. **Size** 6-1/2 x 4-1/2 x 4-5/8".
LIKE NEW \$7.50



HANDMIKE Rugged, heavy-duty carbon hand mike with press-to-talk switch. Equipped with 4-foot cord & phone plug.



NEW, boxed, Each \$1.88 2 for \$3.25


BC-604 FM TRANSMITTER 20 to 27.9 Mc. Output approx 30 watts. 10 crystal controlled channels. Complete with tubes.
NEW \$12.50



BC-1206-C RECEIVER Aircraft Beacon Receiver 200 to 400 Kc. Operates from 24V DC 1.5A. Continuous tuning, vol control, on-off switch and phone jack. Very sensitive. Compact.
Complete with tubes, **NEW** \$12.50



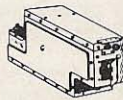ARC-5 VHF RECEIVER, TRANSMITTER, MODULATOR 100-156 Mc
R-28 Receiver, with tubes and crystal, exc. Used Cond. \$19.50
T-23 Transmitter, with tubes and crystals. **Brand New** in original carton \$21.50
T-23 Used, less tubes \$3.95
MD-7 Modulator, w/tubes, exc. used \$10.95



R48/TRC-8 UHF FM RECEIVER 230 to 250 Mc. Variable tuning, one band. 115/230 V 60 cy. Complete with speaker, phone jack, squelch circuit 2-1/2" meter for circuit testing; includes 15 tubes: 8/6AG7, 9002, 5U4, 6V6, VR-150, 6SN7, 6AL7. **Size** 20 x 19 x 16". **Weight** 75 lbs.
NEW \$44.50



HEADSET Low impedance. With large chamois ear cushions, 4-foot cord and plug. **Reg.** \$12.50. **OUR SPECIAL PRICE** \$2.95
Less Ear Cushions \$1.95
High impedance adaptor for above . . \$.69



2" DC VOLT-METER Mounts in 2-1/8" hole. Flange diameter 2-5/8". Two scales 0-15 and 0-600. Calibrated for use on steel panel. Standard brand. **SPECIAL**
NEW, boxed Each \$1.75 2 for \$3.00



SCR-274-N, ARC-5 COMMAND SET HQ!

Freq. Range	Type	Exc. Used	Like New	BRAND NEW
190 - 550 Kc	BC-453			
RECEIVERS, Complete with Tubes				
TRANSMITTERS, Complete with Tubes				\$19.50
4 - 5.3 Mc	BC-457		\$8.95	\$11.95
5.3 - 7 Mc	BC-458		\$8.95	\$11.95
3 - 4 Mc	T-19		\$10.50	\$14.95
4 - 5.3 Mc	T-20		\$6.95	\$11.95

TERMS: 25% Deposit with order, balance C.O.D.—or—Remittance in full. Minimum order \$5.00 F.O.B. NYC. Subject to prior sale and price change.

G&G RADIO ELECTRONICS COMPANY

47 Warren St. (2nd Fl) NYC, NY 10007 Ph 212-267-4605

LICENSE GUIDES

TRY ANY OF THESE MODERN, COMPREHENSIVE LICENSE BOOKS ON FREE 10-DAY TRIAL


Novice-Class License Guide



Getting a Novice license is just about as easy as falling off a log—with this new study guide. All the mystery and confusion is taken out of learning the theory involved in the FCC exam. It is simple and logical, taking the basics of electricity and radio and exposing them as the really simple things they are. This book was written by an average ham to be read by absolute beginners. It is not for engineers, nor for children, but for the reader with the equivalent of a high school education and the interest to think things through. The theory is simple, and there is no reason why anyone cannot get an amateur Novice license after a few days study. 160 pps.

Order No. 573 \$6.95 hardbound; \$3.95 paper

General-Class License Guide

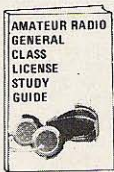

Teaches, in simple everyday language, the technical aspects of ham radio considered necessary prerequisites to passing the General-Class exam. The author takes a patient and personable approach, yet gets right to the heart of the technical questions the FCC will ask on the General-Class exam. Each question is dealt with individually, and the answers are explained in depth, but at a level that can be easily understood by relatively inexperienced, nontechnical readers. The text follows the philosophy that learning—not memorizing—is the key to successfully entering the higher grades of amateur radio. Pertinent facts are grouped into palatable doses.

Order No. 551 \$8.95 hardbound; \$5.95 paper

Extra-Class License Guide



Although written as a study course for the ham radio enthusiast, much of the content in this practical guide covers material needed to pass the FCC 1st-Class Radio telephone License Exam. Thus, it has a great deal to offer anyone desiring to advance his knowledge of all kinds of radio communications systems—modulation, bandwidth, spurious radiation, sidebands, transmission lines, etc. And for the amateur radio operator who aspires to become one of the elite, this book is a must! In fact, it's the only book entirely devoted to the subject. Begins with AC-DC theory and winds up with RF power amps, measurements, and RTTY. 224 pps., 162 illus.

Order No. 543 \$7.95 hardbound; \$4.95 paper

Advanced-Class License Guide



Tells all you need to know, with complete, thorough answers to all the questions you'll find in the advanced-class exams. The only book that covers transistors and sideband, and knowledge of both is positively required to pass the exam. Thoroughly prepares you to answer exam questions dealing with harmonics, parasitic oscillation, oscillators, feedback, and neutralization; antennas, transmission lines, and SWR; receiver circuits; transmitter operation; and transmitter circuits and adjustments.

The final chapter covers measurements of frequency, modulation, voltage, resistance, etc.—things you need to know to operate legally and efficiently. 192 pps., 73 illus.

Order No. 527 \$6.95 hardbound; \$3.95 paper

Ham Radio Incentive Licensing Guide



Get started in amateur radio—or advance to a higher class—with the aid of this new book. New FCC rules now in effect encourage radio amateurs to learn more about communications, electronics and therefore become eligible for higher class licenses with special operating privileges. This book contains the information needed to pass all the ham license exams—Novice, Technician, Conditional, Advanced, and Extra Class. Included are study sections for each class, from learning the code to equipment and operating rule requirements. Specific question and answer sections make it useful to all hams and would-be Novices. 160 pps.

Order No. 469 \$6.95 hardbound; \$3.95 paper

Commercial FCC License Study Guide



A new and unique study guide and reference manual, combining theory and applications with up-to-date questions and answers for 1st, 2nd, and 3rd class radiotelephone license exams plus broadcast and radar endorsements. Everything you need to know is included—complete detailed answers to questions on any subject you may be asked when you take your exam. Numerous practical examples are used to describe the various principles. In each case, the author painstakingly explains the answers to questions on all subjects included on the exams. Thus, the content not only thoroughly prepares you for any exam, but also for practical reference. 432 pps.

Order No. 582 \$8.95 hardbound; \$5.95 paper

OTHER HELPFUL AMATEUR RADIO BOOKS AVAILABLE ON FREE 10-DAY TRIAL

IC Projects for Amateur & Experimenter



Here's your opportunity to become knowledgeable on ICs, and have a lot of fun in the process. Here's a book of 35 integrated circuit projects that will strike the fancy of today's hobbyist with complete details on the construction of such items as a digital counter, audio mixer, signal and marker generators, code oscillator, audio filter, AC switches, converters, various generators, a 2-watt 6-meter transmitter, and many others. So grab your soldering pencil and a small sheet of styrofoam and get busy on some of these projects, wiping away a tear of nostalgia for those of us left with shelves full of power transformers and 4000-mfd capacitors and other worthless memorabilia. 192 pps.

Order No. 568 \$6.95 hardbound; \$3.95 paper

104 Ham Radio Projects



Here is a well-rounded assortment of devices, many you'll want to build and use in your shack. Particular emphasis has been placed on transmitting gear, including modulators, monitors, filters, BFOs, and converters. In addition, there are projects for the 80, 40, and 15 meter Novice; 6, 2, 1 1/2, 3/4 meter, and 1296 MHz for Technician classes. In all, the 10 categories include antenna devices, audio equipment, CW aids, interference suppressors and eliminators, power supplies, preamps and preselectors, receivers and converters, transmitters, and transmitter-receiver accessories. A lot of fun for little money. 192 pps.

Order No. 468 \$6.95 hardbound; \$3.95 paper

VHF Ham Radio Handbook



Explains how to make use of the many VHF-UHF techniques—hints and kinks, transmitters, antennas, equipment modifications, receiver and modulator circuits, etc. The final section describes 25 VHF construction projects, including transmitters, receivers, preamps, filters, RF amplifiers, a field strength meter, noise generator, and a VFO for all bands. Other chapters cover VHF propagation phenomena and power supply considerations. Written for the ham who takes pride in contributing to the advancement of the art. Truly a book every ham will want to own. 176 pps., over 100 illus. Scores of construction projects.

Order No. 460 \$3.95 paper

NO-RISK COUPON

TAB BOOKS, Blue Ridge Summit, Pa. 17214

Please send me the following books on FREE 10-day trial. (Please specify hardbound or paper cover.)

Please invoice on FREE 10-day trial I enclose \$_____ Send FREE Catalog
 573 551 543 527 469 582 568 468 460

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

SAVE POSTAGE by remitting with order

73-121

Professional Quality for the Professional Amateur!



AMATEUR—2 meters TRANSMITTER-RECEIVER

(from 144 to 148 MHz)

COMPLETE FLEXIBILITY FOR MOBILE
— BASE — HAND HELD
PORTABLE



Model FM 3601 (2 METER)

- 8 Channels with Instant Push Button switching • 10 Watts • Solid State. Finest quality silicon transistors • Netting trimmer for each receive and transmit crystal • High quality mechanical filter for adjacent channel rejection • Military-grade, glass-epoxy printed circuits • Rugged, serviceable design, compact construction • Diode protected Dual-gate FET mixer • 25 transistors, 1 IC, 1 MosFet, 16 Diodes • Overload protected receiver R.F. stage

Complete with microphone, mobile mounting tray and 2 pair of crystals, (146.94T/146.94R and 146.34T/146.94R)

\$299⁹⁵

Model PS-2923 AC Regulation Power Supply . . . \$39.95

SPECIFICATIONS

Frequency Coverage: 144—148 MHz
Dimensions: 6³/₄" W x 2⁵/₈" H x 9" D without tray
Weight: 5 lbs.
Microphone: Controlled Magnetic
Antenna Impedance: 50 ohms

RECEIVER

Sensitivity: At least 0.5 μ V for 20 db Quieting,
0.35 μ V for 12 db Sinaid
Selectivity: 16 KHz @ 3 db
Freq. Tolerance: .001% from -30°C to 60°C
Spurious Rejection: At least 60 db
Audio Power: 2 W, w/less than 10% distortion
Squelch Range: 0.2—0.8 μ V
Intermediate Freq.: 10.7 MHz & 455 KHz

TRANSMITTER

Emission: 16F3 (Frequency-Modulated)
Freq. Tolerance: .0005% from -30°C to 60°C
RF Power Output: 8 to 10 Watts
Spurious & Harmonic Attenuation:
More than 50 db below RF carrier
Deviation: Internally adjustable 0—10 KHz

POWER REQUIREMENTS

Receive: Squelch standby: 0.175 Amp.
Maximum audio: 0.500 Amp.
Transmit: 1.90 Amperes
Voltage: 13.8 VDC—Neg. Ground only



Model 2307 VHF-FM (144-148 MHz) TRANSMITTER 5 CHANNELS HAND HELD PORTABLE

- Provides immediate voice contact with Base Stations, Mobile Units and other portable transceivers • Compatible with ALL 2-way communications systems • Snap-in Nicad Battery Pack cartridge • Receiver and transmitter can be operated on independent frequencies • Electronic mode switching/no relays • Receiver and transmitter sections are individual modules for easy servicing • Sensitive adjustable squelch • Sensitive, noise immune squelch • Meets all EIA requirements.

\$450 compatible with collapsible antenna and shoulder strap. Less crystals & battery cartridge*

SPECIFICATIONS

Frequency Range: 144-148 MHz
Power Supply: Snap-In Nicad Battery Pack
Power Drain: Standby—10 ma
Receive—50 ma
Transmit—450 ma
Battery Life: 8-14 hours
Quick Charge: with 3 hours
Dimensions: 3¹/₄" W x 9" H x 2" D
Weight: 1¹/₂ lbs.

TRANSMITTER

Power Output: 1.6 Watts
Modulation: \pm 5 KHz
Stability -30°C to +60°C: \pm 0.0005%
Spurious & Harmonics: 46 db
FM Noise @ \pm 3.3 KHz deviation: 46 db
Audio Distortion: 10%
Audio Response (EIA): 6 db per octave
pre-emphasis from 300 Hz to 3 KHz

RECEIVER

Sensitivity: 12 db Sinaid—0.35 microvolts
20 db Quieting—0.50 microvolts
Modulation Acceptance: \pm 5 KHz
Spurious & Attenuation: 70 db
Squelch Sensitivity: 0.15 microvolts
Audio Output 65 ohm: 250 milliwatts
Stability -30°C to +60°C: \pm 0.0005%
Selectivity Adj. Chan.: 85 db
Channel Spacing: 30 KHz

Plastic Case

MIN.
1.6 WATTS
OUTPUT

SONAR RADIO CORPORATION


73 Wortman Ave., Brooklyn, N.Y. 11207

TELEVISION INTERFERENCE HANDBOOK

TELEVISION INTERFERENCE
CAN BE CURED

Is there a radio operator anywhere who has not had trouble with television interference? Unlikely!

**NEW,
UP TO DATE...
only \$1.50**

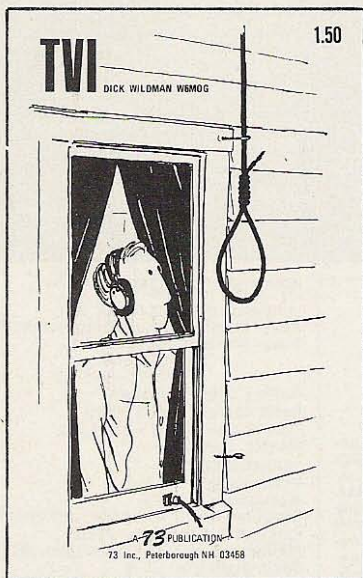

Television Interference Handbook

Send to:
73 Magazine, Peterborough NH 03458


Name _____

Street _____

City _____

State _____ ZIP _____

Want to know more
about Repeaters?

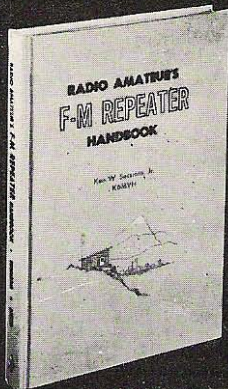

\$6.95

*Want to build a repeater?
Want to improve your
existing repeater?*

Whether you're a newcomer or an oldtimer, you'll find "The Radio Amateur's FM Handbook" to be the most valuable repeater aid you can get.

FOR THE OLDTIMER

- the Handbook tells . . .
- how to defeat desensitization
 - how to calculate attenuation according to frequency spacing, antenna separation
 - how to build sophisticated control systems, using ICs, timers, relays, steppers, or Touchtone
 - how to build automatic logging and identification devices
 - how to build automatic phone patches

FOR THE NEWCOMER

- the Handbook tells . . .
- how to prepare for a repeater
 - how to get a repeater site
 - how to build a repeater
 - how to keep a repeater on the air
 - how to determine a prospective repeater's range
 - how to get your repeater license

The Handbook contains 208 pages of useful, hard-to-come-by information, and it's written in an interesting, personal vein by Ken W. Sessions, Jr. (K6MVH) former editor of FM Journal, now managing editor of 73.

Order from:

73, Inc.

Peterborough NH 03458

73 tests the GAM TG-5-S Gain Vertical

Perhaps "tests" is a bit extravagant. To be honest about it we didn't run tests with the antenna, we just decided to use it and thought you might be interested in the rationale behind the choice.

The repeater here in Peterborough is on top of Pack Monadnock Mountain. To be precise, the receiver is on top of the mountain and the transmitter is down about 300 feet or so about one half mile away. There are two reasons for separating the transmitter and receiver. One is to prevent desensitizing the receiver every time the transmitter comes on the air, which can be a serious problem when the two are side by side, and the other was to get that little extra gain the very top of the mountain obviously provides.

The tower beside the transmitter shack is 100 feet high. We put the antenna on top of the tower . . . probably because antennas are always supposed to be on top of towers, not at their base. But this brought on the obvious problem of some of the rf getting lost on the way up to the antenna. Though we used RG8/U foam cable for the job, the spec sheets still let us know that we can expect to lose about 2.5 dB over that length. Figuring a few more feet into the rig from the tower we manage to lose 3 dB over the path. That's one half of the power! Zounds!

The logical solution to that is to run more power. This is logical and expensive. If you figure it out at all, you will see that the most

economical way to amplify your signal, within reason, is by putting up a gain antenna.

The specs on the Gam TG-5-S antenna tell us that it has a 10.5 dB gain over a coaxial antenna. That certainly would more than make up for the 3 dB feedline loss and might even make up a good deal of the difference between the transmitter and receiver heights. A repeater is working its best when it can be heard as well as it can hear. If it covers more area with its transmitter the mobiles can hear it clearly and not get into it, a most frustrating experience. If the receiver is better than the transmitter, then fellows go through the repeater who can't get the transmitter, a frustration to everyone who can hear the rig.

The first tests of the system, using a ground plane antenna on the receiver and the Gam TG-5-S on the transmitter, indicate that the coverage of both the transmitter and the receiver are fairly equal. Mobiles in Rhode Island have been able to work through the repeater to work mobiles in Maine, both over 100 miles away from the mountain.

The high gain of the antenna is achieved by placing and phasing the radiating elements one over the other. This squeezes the radiation pattern down toward the horizontal, giving the gain. Radiation at a high angle is wasted unless you want to do a good job on passing planes. . . . Staff

FM Schematic Digest

A COLLECTION OF

MOTOROLA SCHEMATICS

Alignment, Crystal, and Technical Notes
covering 1947-1960

136 pages 11½" x 17" ppd \$6.50

S. Wolf

1100 Tremont Street

Boston, Massachusetts 02120

A 2m Preamplifier

12 vdc powered.

27 db gain (approximately).

Noise figure 2.5.


Will take Regency HR-2
or Motorola to 0.1 μ v sensitivity
without appreciable noise.

Metal Case. ONLY \$17.95 ppd.

CRAWFORD ELECTRONICS

302 West Main, Genoa IL 60135

NEW! REPEATER ATLAS

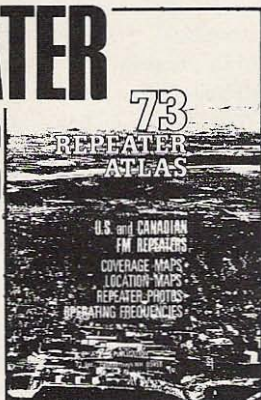

This is the book to have for your glove compartment in your car. When you are travelling now you will know what channels to use to get into the repeaters. Say you are driving along the New York Thruway . . . what repeaters can you use and over what range? Check the ATLAS.

Perhaps you are flying into Chicago for a business trip or convention . . . what repeaters can you use with the little rig you plugged into the rented car? Check the ATLAS!

Or are you just getting the FM bug and wondering whether there is a repeater which covers your town? Check the ATLAS.

Going on a vacation and want to route yourself through as many repeaters as possible? Check the repeater ATLAS.

Is your repeater group thinking of changing frequencies? Check the ATLAS!

HOT OFF THE PRESS

Order today **ONLY \$1.50!** postpaid

Repeater Atlas Order Blank

73 Magazine

Peterborough NH 03458

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

\$1.50 enclosed for one copy of the ATLAS.

\$10.00 enclosed for 10 copies of the ATLAS


(club special).

REPEATER CIRCUITS MANUAL

If you're into FM, you'll want to have this incredibly complete manual of FM circuits. You don't have your own repeater yet? Well, you've been thinking of it . . . admit it. Some fellows even have gone so far as to have a repeater in their car so they can extend the range of their hand units!

This book, over 300 pages long, has just about every circuit that you could possibly want. Many of these have been published elsewhere, but many haven't, too. And you can go out of your mind trying to find a circuit when you want it . . . so here they are, all in one handy place!

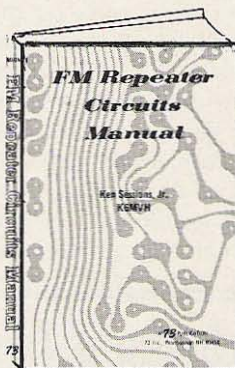This book will be selling for \$6.95 when it is published. For the next month it is available at the pre-publication introductory rate of only \$4.95 postpaid. Publication is expected in late November; however this offer is good until January 1st.



73 Magazine

Peterborough NH 03458

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

\$4.95 enclosed for FM Repeater Circuits Manual.

RADIO BOOKSHOP BIG DEALS

VHF ANTENNAS This handbook is a complete collection of up-to-date information about VHF and UHF antennas, with design hints, construction and theory. If you've been wondering what array you need, this book will give you enough background to make the right decision.
1003.....\$3

73 BINDERS

BUY BINDERS FOR YOUR 73 and win the love of a beautiful girl. Gorgeous red binders look great on your shelves and also keep the magazines from disappearing or breaking. Come with set of year stickers. Get enough binders to protect all those back issues too.
1205.....\$5

GUNSMOKE

GUNSMOKE? Blow your mind on our back issue bargain bunch, 30 (count 'em) assorted (we hope) back issues, all before 1968, for the incredibly low price of \$6 postpaid (hardly pays for the postage). These are packed by slave labor (to cut costs) so please ignore notes calling for help, etc., that may be slipped into the bundles.
1204.....\$6

TIRED OF CRUMMY LOG BOOKS?

Try a pad of W2NSD log sheets. Why use a 1931 log book in 1971? Do we guarantee that this is the best log ever devised by the mind of man? You bet we don't! It is a good one and you'll find it a tremendous improvement over anything you've ever seen before.
1210.....ppd USA \$2

DX CHART

You will use this DX chart every day that you are on the air. That's a guarantee. This is the fastest way to find the angle to swing that beam. These charts are made by a computer and are custom made for your location. The angle and distance to all of the countries of the world are on this chart. This chart should cost you \$50, but it doesn't... send only \$4 and thank your lucky stars that there is a ham who is offering this service more for fun than profit.

FM BOOKS

FM ANTHOLOGY Vol. 1. This book is largely a collection from FM Bulletin, edited by K67MVH and WA8UTB. The material is taken from the editions of February 1967 through February 1968.
1009.....\$3

FM REPEATER HANDBOOK K6MVH. Book is required for all repeater operators and must reading for all FM'ers. Only complete book on the subject. It is also one of the best selling books in amateur radio today.
1010.....Hardbound \$6.95

"THE BEST OF FM" A huge selection of FM Journal's finest technical and conversion articles, never before reprinted in any other magazine. The concluding segments of those controversial "CHRONICLES"! Selected FM editorials to show a broad view of the problems faced by FM'ers. This book comprises Volume II of the FM anthology, and includes an "Editor's Choice" selection of topflight articles from FM Journal, from March 1968 to May 1969.
1011.....\$4.95

EDITORS & ENGINEERS RADIO HANDBOOK Hardbound. W6SAI (17th edition) reduced for clearance, limited supply available for fast acting amateurs. Last chance to get this great book before it is gone forever.
1019.....\$10

You Need an ATLAS

Lucky for you we still have atlases. These are not cheap junky discount-house type trash atlases, these are the finest ever made, up to date, profusely illustrated, exquisite in appointment, a joy to behold, a pride to own, a king couldn't do better. Hammond spares

Don't you love your children?

Prove your love with a Hammond world globe. What kind of father are you, talking with people all over the world when your poor deprived child does not have a world globe? How can you live with yourself?

Wayne Green has had a Hammond globe for over 15 years and he uses it almost every day. And guess what Wayne is giving his #1 daughter for Christmas this year? Right, a great big lovely Hammond World Globe!



Tully Green, who will be receiving a Hammond World Globe for Christmas this year. Would you do less for your child?

13" globe.....\$10
19" globe.....\$15 (reg. \$25)

DX HANDBOOK Includes giant world country-zone wall map. Articles on QSL design secrets, winning DX contests, DXCC rules, DXpeditions, reciprocal licensing and many more. World postage rates, WAZ record lists, time charts, propagation, etc. Special ham maps and bearing charts. A must for the DXer. 1021...\$3

no expense to turn out the very finest atlases in the entire world. The only expense that is spared is the one we spare you by making these extraordinary books available. Where else can you buy a \$20 atlas for only \$9? Order now, we have a limited supply and can't get more before Christmas.

Mail To: **RADIO BOOKSHOP, Peterborough NH 03458**

NAME _____ CALL _____

STREET _____

CITY _____

STATE _____ ZIP _____

SCR Mobile Theft Alarm

Dominic Bottaro
36 Quirk Street
Watertown MA 02172

There is a very simple and inexpensive circuit ideally suited for the protection of ham gear, tape decks, and other car accessories.

The circuit, as shown, utilizes the car horn as an alarm, but it can likewise be used to energize a siren or other appropriate equipment.

The circuit components consist of a switch, one resistor, and a 90¢ SCR.

The circuit (Fig. 1) gets connected to the horn button side of the horn relay. Wire A, originating from the gate of the SCR, is connected to the grounded case of

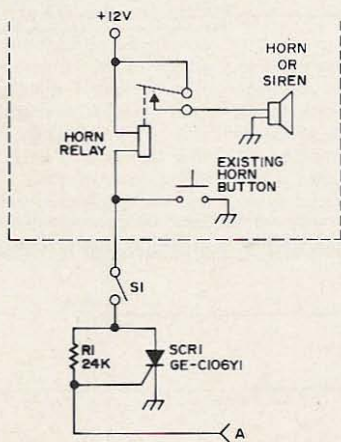


Fig. 1. Mobile theft alarm circuit.

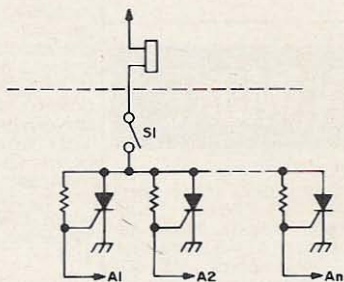


Fig. 2. Paralleling SCR circuits will protect several pieces of equipment, even though only one "safety" switch is needed.

the equipment to be protected. This prevents triggering of the SCR until the time that this wire is cut or disconnected. A thief, determined to steal a piece of equipment (ham gear, tape deck, radio, or outboard motor on a boat), by necessity must disconnect all wires leading to the equipment; in so doing he would unground wire A, allowing gate current to flow and trigger the SCR, which in turn would energize the horn relay (and, therefore, the horn or siren).

To protect several pieces of equipment, the circuit must be duplicated as many times as needed with the exception of the switch.

Figure 2 shows how to protect several accessories or pieces of equipment.

...W1BHD■

DX QSO's or CONTACTS

A recent Leaky Lines discussed the broader aspects of DX, and deplored that DX contacts were always so brief. Here we have the nub of the point.

DX is *not* synonymous with contests. It can be the opposite. A contest, as the name implies, is solely competitive and no attempt is made to get to know anything about one's opposite number, nor is there time to do any comparative tests of a technical nature. A DX QSO need not resemble a contest contact. In fact, it can be a QSO either devoted to learning about the other fellow, or trying out some technical test or other.

I have been on several minor DXpeditions such as ZD3F, G3BID/6W8, 9H1BN, and G3BID/CN down to more mundane calls such as G3BID/LX and others; and have studiously avoided making nothing but contest contacts. Occasionally for perhaps half an hour or an hour I have worked contest style, but never for long periods. One of my short bursts of contest operations was in Southern Morocco when near Zagora. I had driven up a hill called the Djebel Zagora. I found 10 meters open to the States and worked one hour of contest contacts to give a lot of Ws a mobile contact from Morocco. But that was enough.

Next morning I heard a VK2 on 40 meters, but failed to contact him because he was working a W7 and, therefore, listening outside our band. So, changing bands, I worked another VK2 on 20 meters and got him to inform the 40-meter VK2 to look for me next day at the same time on 40 on his own frequency.

This resulted in a QSO (not a contest). Having established communication on 40 meters with the VK2 from the car, I asked him to listen carefully while I rotated the car through 360 degrees, and note my report. He just copied me for about 45 degrees either side of the peak signals and then lost me completely for the other 270 degrees. This gave a clear indication of the directional properties of the car. But there were two Gs also on frequency, and they reported little or no change as I rotated the car.


So we began to establish the difference between the directional properties of the car for low angle radiation, about 12,000 miles (long path) and for high angle radiation, about 1,500 miles. That is a DX QSO, in my opinion.

In ZD3 and 6W8 I made a point of only working contest style contacts for a maximum of an hour at a time, but normally I had QSOs describing the scenery, the climate, the people I had met, as well as getting to know the people at the other end.

Because I have never worked in a contest even from the home station, and have always had QSOs, not contacts, I was able to meet many old friends on the air — amateurs I had worked frequently from England and elsewhere.

These personal QSOs even resulted in my being able to get a transceiver supplied by some very kind American friends to one of my friends in the Gambia and get a local radio club started under the auspices of the Prime Minister as first Patron. This club is

NEED CRYSTALS ?

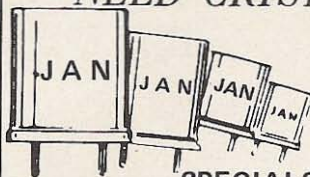

We can supply crystals from 2 KHz to 80 MHz in many types of holders.

SPECIALS

Color TV crystal (3579, 545 KHz) wire leads	\$1.60 4 for 5.00
100 KHz frequency standard crystal (HC 13/U)	4.50
1000 KHz frequency standard (HC 6/U)	4.50
Any CB crystal, trans. or rec. (except synthesizer crystals)	2.50
Any amateur band crystal in FT-243 holders (except 80-160 meters)	1.50 4 for 5.00
80 meter crystals in FT-243 holders	2.50

We have in stock over six million crystals which include types CR1A/AR, FT243, FT241, MC7, HC6/U, HC13/U, etc. Send 10¢ for our 1971 catalog with oscillator circuits, listing thousands of frequencies in stock for immediate delivery. (Add 10¢ per crystal to above prices for shipment 1st class mail; 15¢ each for air mail.)

ORDER DIRECT

with check or money order to
Special Quantity Prices
to Jobbers and Dealers

2400B Crystal Dr., Ft. Myers, Fla. 33901



now flourishing and took part in the Boy Scouts Jamboree in the air.

This is, I imagine, the different aspect of DX which you are seeking.

One of K2AGZ's articles refers to "Ugly Americanism" and looks forward to changing the opinions of foreign amateurs with respect to the overstressed image. May I as a Briton (not Britisher please) offer a suggestion or two?

May I make a plea for greater sincerity? Some amateurs put on a false and totally unconvincing friendliness, when clearly they are not genuinely interested. I have received printed QSL cards expressing great pleasure at this "personal" contact with friends overseas and thereby "helping to establish world friendship." If all this talk of "personal" contact and "friends" is printed, it smacks of insincerity. Few Europeans are likely to believe there is anything either personal or friendly if the whole thing is printed.

Of course, I use printed QSL cards. My call is printed. The type of rig is printed. The type of antenna is printed. The type of

receiver is printed. The mode of QSO, CW, AM or SSB is printed and the address is printed. These are not personal. These are the same for everyone and make no pretence of being personal. But to print one's appreciation of a "personal" contact and "friendship" is degrading the words themselves, like the word "personalized" which often means "produced by the thousand," and exposes the insincerity of the amateur who sends them.

Obviously no human being likes all the people he meets — he would not be human if he did. Likewise, no radio amateur is going to enjoy a QSO with every amateur he meets on the air. One must be peculiarly insensitive if one cannot feel within a few minutes whether the QSO is going to be enjoyable or not. If one is obviously talking with someone with whom one has clearly nothing in common, with someone with whom the conversation will be dull and uncongenial, one can always sign quite politely and move off, but one need not then indulge in fulsome phrases which are obviously insincere, such as, "Look forward to meeting you further down the log" when it is quite clear that the personalities do not fit and there will be no pleasure in having another QSO; nor in saying, "Whenever you hear me on, please give me a shout," when it is clear that one hopes never to repeat the dull QSO which one is gladly about to end.

Real international friendship is not established by stereotyped insincere phrases. Apparently many amateurs do not realize that the insincerity comes across quite clearly, except under conditions of the very worst QRM.

It is, of course, easier to conceal the insincerity on CW where the tone of voice doesn't come across quite so clearly. But even here I wonder if the fist doesn't indicate whether the other fellow is enjoying the QSO or is only anxious to end it.

But, above all, the QSL which has printed remarks about "personal" QSO, "enjoyable" contact, or "friendship" are so palpably insincere as to spoil any illusion of there ever having been a "personal" or "friendly" contact.

...G3BID

CODE SHORTHAND

After one has learned the twenty-six letters of the alphabet, the ten numerals, and approximately ten punctuation marks, and progressed to about ten words per minute in code speed, he generally finds himself on a "plateau." Progress to greater code speeds seems for a time to come to a halt.

Progressive learning of any art (and code is an art), according to psychological research, takes place in "steps." But there are actually ways of advancing many steps at a time. This article is devoted to one of the many methods which can be used to skip a few steps and hasten the process of acquiring superior code speed in a shorter time.

It is comparable to the shorthand used by stenographers for years to write a language in the form of symbols. One of the principal ingredients of any shorthand is the use of "word signs." Practically all of the *short*, frequently used *words* in any language are represented by simple "word-signs," which are actually simple, very short strokes used to represent a word rather than use a multitude of strokes to represent the characters forming that word.

If one wishes to accrue superior code-copying ability, he will have to learn to read and copy words and short phrases just as readily as he copies single letters. In short, he learns word forms instead of single letter forms.

Actually, one of the first word forms to learn is "the" because it is used most often in the English language. It is no more difficult to copy — than it is to copy the character 9 (-----); and really, in terms of time-space, the two are about equal. The word "the" takes up 17 time elements, and the character 9 takes up 17 time elements, if one cares to count them up. It takes the

same length of time to transmit the word "the" as it does to transmit "9."

In code, as in a lot of other arts, there is nothing quite like practice to make one proficient. Except, as herein noted, the time is spent in word-copy instead of letter-copy.

To facilitate the use of this system, a list of the short repetitive words used in the English language is given here for the student to practice. If you have a small, inexpensive tape recorder, it will pay to record these (each one at least five times) and then copy them back many, many times; and a good trick is to record them at the slow speed, then play the tape back for copy at double speed.

Two-letter words are more easily learned first:

OF TO OR ON AN HE NO DO
WE IN IT IS AM

Then, progress to three-letter words:

BUT THE AND WAS WILL SHE
HAS HAD NOT WHO FOR ANY

This will make progression to the four-letter words, as given below much easier, as a lot of the four-letter words are mere continuations of the two and three letter words:

WERE WILL THEY THAT HAVE
THEM WITH HERE FROM MORE THAN

The student can add many of these two-, three- and four-letter words to this list to record and copy at double speed.

Phrase Copying

The next step in speed-copying is to progress from simple words to phrases. In shorthand, phrases consist of combinations of word signs strung together.

Some of the simple, repetitive phrases found in common usage are listed herein as a guide to those that should be recorded and copied:

IT WAS	OF THIS	WITH THE	ILL	MOT	SUB	EX	MOT
I AM	WILL HAVE	THEY ARE	SEM	FER	WHE	CAR	PRE
THAT IS	FOR THE	IT WAS	UN	CON	MET	INF	ADD
TO THEIR	AND THEY	WE WILL	ED	MEN	PER	AD	BRO
FROM THE	IT IS	OF A	ALL	FOL	COM	TEN	INT
IN THE	SHE WAS	DO NOT	CO	POS	ANO	FOR	REL
WE ARE	IN AN	TO THE	DIR	ANTI	COL	EVE	TEM
HE IS	OF THEM	AND HE	REP	BOR	WE	BAR	PRO
HE WAS	WILL BE	THEY WERE	Following is a list of common suffixes (word endings):				
THAT WAS	ON THE	SHE IS	TION	ILY	AIN	ERT	
AND THE	TO THEM	THEY WILL	ONE	LY	DENT	CED	

It will take from three weeks to a month with copy at the rate of at least one hour per day for the student to become proficient at copying these two-, three-, four-letter words and phrases.

But one will notice that automatically his code speed is increasing in direct proportion to his facility in copying. If one wishes more of these phrases, he can consult a "shorthand" book which will list practically all the phrases in common usage.

Prefixes and Suffixes

There is one more device which can increase the student's code speed immeasurably. This is to become proficient in copying prefixes and suffixes.

There is no greater truism than that in code copying the long words become the stickers. After copying the first few letters of a long word, the mind seems to go into reverse, and a letter or two in the middle is lost—and one might as well forget the rest of the word, because in attempting to copy the lost letter or letters, the complete word is lost. This is a common state of mental confusion (or mind block) and anyone who copies code knows about it.

By thoroughly learning the prefixes and suffixes, and shortening the "automatic response" time when they are encountered, the student gains copy time going into the middle of a long word, and then he has a better chance of copying the central letters; and by thoroughly automatizing the suffixes, if the copier falls a letter behind, and the suffix phrase is recognized, the student will automatically be able to quickly complete the word correctly.

Here is a list of some of the common prefixes used in the English language (these will vary somewhat with other languages):

MINE	ALE	CAL	ASE
ALT	DAY	SED	DER
EST	ANE	ITE	ANY
TON	ICT	ULD	ERY
ALY	CED	AIL	DED
ABLE	NAL	ISE	TES
OULD	SIGN	TER	ERS
INE	ATE	ANE	IBLE
ISH	ELF	ORY	OTE
IVE	IAL	TED	IST
IST	ESS	SES	THING
ING	TOR	END	BLY

It must be emphasized that the more common prefixes and suffixes, such as pro, ed, in, and, tion, ing, must be so thoroughly imbued in automatic reaction that there is absolutely no hesitation in recognizing them, and copying them as such.

Prefix and Suffix Combinations

The reader should immediately recognize the fact that certain combinations of prefixes and suffixes actually form complete words—such as words like "promote," which consists of the prefix "pro" and the suffix "mote."

In longer words, such as the word "admission," here we have two suffixes following a prefix: "ad", the prefix and "miss," one suffix, followed by "ion," another suffix.

It should readily become apparent that once one becomes proficient in this type of code shorthand he will notice an immediate increase in his code-copying ability and his speed will jump from five to ten words per minute over any previous speed in a very, very short time. By the use of a trick system, the student has jumped a couple of steps, instead of struggling to take them one by one.

...K2EE■



Here is the simplest way of generating "almost SSB" on VHF. Avoiding the usual problems in generating SSB, this circuit shows how to build a Double Sideband Suppressed Carrier rig for 2 Meters. Why not start working real 2 Meter DX on groundwave!

Several years ago an article appeared in one of the amateur journals using tube types similar to those presented here, for DSBC operation. I duplicated that design, but with disastrous results! It simply wouldn't work right. Five or six months went into constructing the unit, all to no avail — until I tried using slightly different pentodes in the balanced modulator configuration, based upon intelligent use of self-bias and adherence to the tube data.

Now, with piles of nonworking drilled chassis, partially destroyed 8156s and a half-melted 7984, I feel I am the authority for workable DSB. I worked Canada from Kentucky, with 2 meters "closed" and no aurora prevalent. If there's anything "wrong" with double-sideband, disregarding the confusion with AM radiotelephony,

it is the operator's inability to tell which sideband he should tune. Operator error, plain and simple.

My ultimate goal is to provide fellow amateurs with a simple, reliable SSBSC generator using the phasing method as developed through my DSB efforts. DSBC is practical, simple, and the best way to get your feet wet on sideband. All of your friends become only "appliance operators" you might say, if it is pointed out that heterodyning a commercial rig is not the same as building a sideband *generating* unit where results depend upon the homebrewer. With the equipment shown here, the next step is "single-double sideband," to coin a catchy term.

This article is entitled *VHF Double*

2 METER PREAMP



NEW MODEL HP-2A

- SMALLER SIZE
ONLY 1 x 3 x 1/4"
FITS INSIDE MOST SMALL
TRANCEIVERS
- SAME SPECS 20db gain, NF 3
- SAME LOW PRICE

ONLY \$13⁹⁵

KIT MODEL \$9⁹⁵

POSTPAID U.S. & CANADA
MICH. RES. ADD 4% TAX.

Hale Electronics

803 17th Street

Bay City, Michigan 48706

TTL POWER SUPPLY

Input	115 VAC 50-500 Hz
Output	180 VDC @ 20 ma 5 VDC @ 500 ma
Line Reg ± 10%	30 mV
Load Reg	25 mV
Ripple (Full load)	1 mV
2 X 5" PC Board —	PC Transformer
LM309K IC reg —	Heatsink
Model PS-12 (Kit)	\$17.95
Model PS-14, 5 VDC @ 1000 ma less 180 VDC	\$17.95

Key Telemetry Products

3853 Garden Terrace, Owensboro, KY 42301



Radio Amateurs Reference Library of Maps and Atlas

WORLD PREFIX MAP — Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables postpaid \$1.25

RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles. postpaid \$1.25

RADIO AMATEURS MAP OF NORTH AMERICA! Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus informative information on each of the 50 United States and other Countries. postpaid \$1.25

WORLD ATLAS — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages, size 8 3/4" x 12" postpaid \$2.00

Complete reference library of maps — set of 4 as listed above postpaid \$3.50

See your favorite dealer or order direct.

**WRITE FOR
FREE
BROCHURE!**



**RADIO AMATEUR
callbook INC.**
Dept. B 925 Sherwood Drive
Lake Bluff, Ill. 60044

Sideband because it tells how pentodes can be successfully used above 50 MHz, dispelling the popular fable about high input capacity and circuit balance limiting use of higher powered balanced modulators above 6 meters. Our balanced modulator nulls the carrier by phasing and tunes out input reactance with an inductive divider. Differential capacitors are seen as being useful on 432 MHz and up, where strays force the designer to use "inductive" plate circuit symmetry.

Operating Class

"Class of operation" has been ignored by most authors when describing balanced modulators. Or maybe a quick appraisal as "pulse" has been thought adequate. I got a bit further. With the first high-level unit being made from 8156s I discovered some interesting things. First, plate voltage must be no higher than for normal class C operation. Second, fixed bias must not be used; resistor bias is adequate because there is no dc screen voltage present. And third, a swamped screen circuit is preferred for stability and development of audio voltage for generation of plate current pulses.

There was no need to place any dc voltage on the screen's centertap at any time. Plate voltage of about half of design maximum rating is plenty adequate with high perveance tubes, or consult the classified data for typical operation. If you should double the plate voltage, even within the design-maximum region, you'll find the distortion so high no one will know *what you're running*.

Getting back to our composite operating class — the grid circuit in my balanced modulator runs class C. You might say the audio-driven screens are running class B, since they're swamped but have some dc component on peaks, even though grounded like zero-biasing. The plate circuit is operating with large current pulses, however, so I guess we can call that portion "pulsed." So, the aggregate of these considerations might well be dubbed "class B, pulsed," as typical operation.

Plate Tank Circuit

Don't use excessively high-Q tanks on

VHF. A convenient way of avoiding this problem is by restricting your experimenting to a particular brand of split-stator "butterfly" capacitors, like the E. F. Johnson 160-series. The largest one they make in this M series is for 2 meters: The 160-211 is my choice.

Using ferrite or dust cores is not always recommended. Permacor X-7451 type IRN-9 material should find best application on 6 meters; but on 2 it is too lossy. IGC Ferramic Q3 material might find decent use above 100 MHz.

Another word on practical theory: Make sure an rf bypass is used for plate current pulses. It is not satisfactory to omit the bypass after an rf choke is used on a capacitive-split tank. The reason is that plate current rf pulses, at an audio rate, must be returned to ground. This speech-frequency pulsed energy can be strong enough to destroy a low-reactance button! Power supply filtering will help, but the lead reactance to the electrolytics can be so high as to result in lower DSB output and instability. In the next design I try I'm planning to use an *output* audio choke along with the electrolytics and silver mica 0.001s.

Turns Ratio

Turns ratio is interrelated with tank circuit considerations given earlier. However, the concept of matching a plate load impedance under pulsed conditions was attempted. We did this by using a reflectometer and driving the output tank backwards from the coupling loop. I was limited in achieving a perfect match by the output capacity of the tube and the LC ratio obtained. That is, the butterfly's capacity set this ratio and happily this seemed good for audio fidelity and not necessarily the greatest output. Presumably this is the sort of tradeoff that must always be made in an optimized design.

One and one-half turns for the coupling loop and at least 3.5 times this is okay for the total number of tank coil turns, depending upon size of coil wound. Tighter than usual coupling is sometimes desirable on VHF in cases where plate resonant load impedance is low. It should be remembered that plate power pulses are on a 4:1 duty

You can have the **TOP FM SIGNAL**

with our base station antenna. The AT-2FM offers you 6 dB Gain, 1.5:1 V.S.W.R. (or better) and 3 Mega-Hertz Bandwidth centered around 146.94 Mega-Hertz.

For full details write: **Box 357 R.R. 5**
AN-TEK INDUSTRIES Elkhart, Indiana 46514

NU SIGMA ALPHA

International Amateur Radio Fraternity. Memberships now available. Includes wall certificate, I.D. card, newsletter, and more. Send for free brochure.

BOX 310
DEPT. 73, BOSTON MA 02101

TELETYPE-RIBBONS-TOROIDS

Lowest prices anywhere!

88 mhy TOROIDS 40/\$10. ppd. -
Fresh RTTY Ribbons 12/\$3.50 ppd.
MACHINES - GEARS - SUPPLIES - TAPE
Stamp for **VAN W2DLT** 302X PASSAIC AVE.
CATALOG STIRLING, N. J. 07980

WE PAY HIGHEST CASH PRICE

for Electron Tubes & Semiconductors
Immediate Payment on Unused Tubes

H & L ASSOCIATES

Elizabethport Industrial Park
Elizabeth, New Jersey 07206
(201) 351-4200

HILLTOPPERS

INSTANT ERECTING

3 EL 6M . . . \$14.95
8 EL 2M . . . \$16.95

We also make Saturn 6 Halos -- 6 & 2 M Beams

HI-PAR PROD. BOX 88 FITCH. MA 01420

PARTS! **CORNELL** TUBES!

FREE Send For FREE
CORNELL'S
New Color
Catalog
48 Pgs. New Items

33¢ per tube

36¢ per tube

ORDER FREE
IF NOT SHIPPED
IN 24 HOURS!

4215 S University Ave. San Diego, Calif. 92105

VHF CONVERTERS

We manufacture a complete line of converters for 50 through 432 MHz. Models to suit all needs. DX, FM, ATV, MARS, etc. A postcard will bring our new FREE CATALOG with pictures, schematics, specifications and prices.

JANEL
LABORATORIES

P.O. Box 112
Succasunna, N. J. 07876
TEL: 201-584-6521

HELP STAMP OUT MENTAL HEALTH

SUBSCRIBE TO 73 NOW!

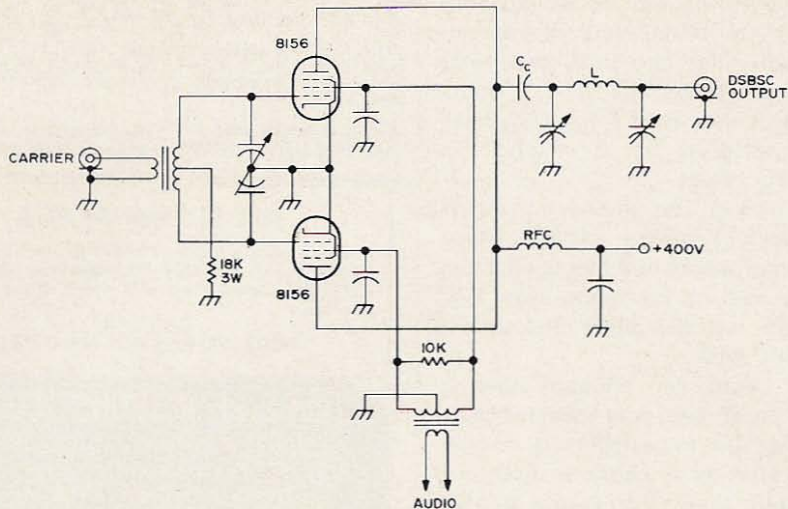


Fig. 1. Conventional method of generating DSB suppressed carrier.

factor with DSBSC (rather than 2:1, as with SSB).

Practical DSB Schemes

All DSBSC generators that do not result in high power losses utilize balanced modulators in one form or another. On VHF, with a commercially made exciter, the best way to go sideband is by using a high-level BM rather than a low-level one. The reasons are obvious: The TX-62 exciter in use at W4KAE already puts out 10-15W on

2m. And I drive much higher-power linears, which need additional watts PEP to push them to 500W average power output. Insertion amplifiers cannot be tolerated because of difficulty of obtaining adequate stability with very high peak powers. The several working circuits I recommend for stable operation follow:

Figure 1 shows the more conventional method of obtaining DSBSC on the HF bands. Usually, it is not necessary to add a differential capacitor, since the DSB gener-

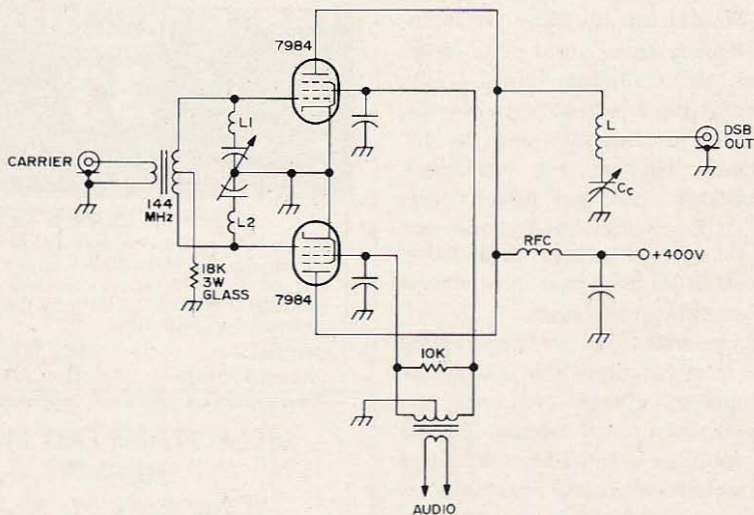


Fig. 2. W4KAE's original "divider input."

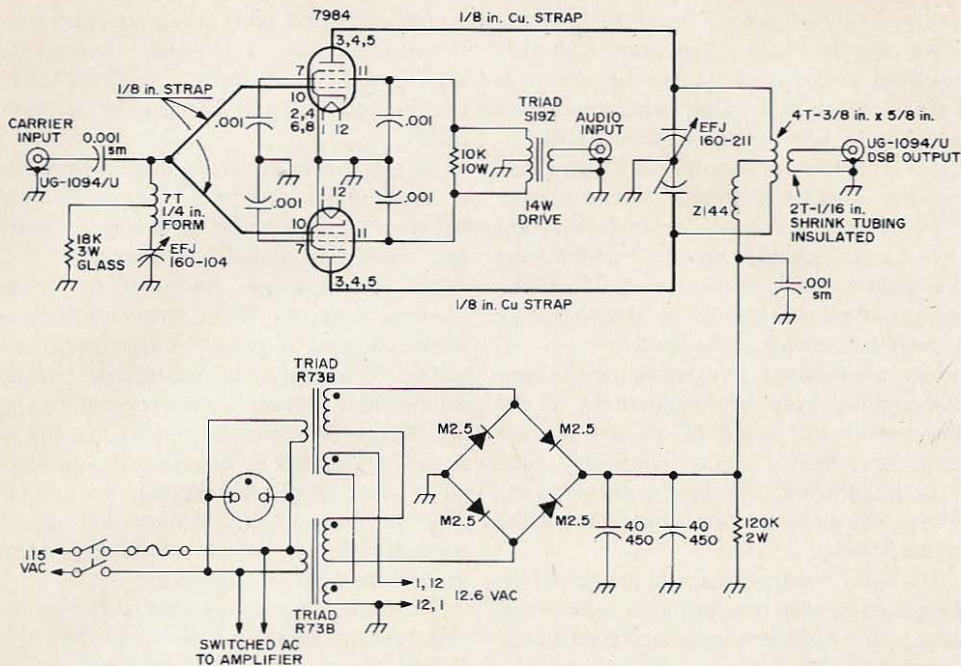


Fig. 3. Final 2m double sideband suppressed carrier transmitter and power supply.

ated results from 90° phasing either side of centertap. Quadrature phasing is simply half of 180° "push-pull."

Figure 2 shows a special push-pull "divider input," my own original design. This circuit is especially useful when very high capacities are encountered on UHF input circuits. The input transformer secondary is to be self-resonant with tubes in place and associated strays. Grid-dipping must be done before placing L1 and L2 in circuit. Once the broad-resonance condition exists, the two inductors should be peaked with the input butterfly so that *balanced series tuning* with both tubes' input circuits is obtained.

Figure 3 is a most successful medium-powered DSB ham rig. Featured is a high current supply made from two Triad 200 mA low-voltage power transformers whose windings conveniently series to provide 400-450V. A total of $80 \mu\text{F}$ is needed for filtering to get a T9 note on the nulled carrier. Carrier suppression is -36 dB , even so!

An inductive divider is used on input. The $10 \text{ k}\Omega$, 10W wirewound resistor is a swamper which provides increased stability when audio gain is opened up about $\frac{3}{4}$ turn. It also provides an impedance match to the hi-fi amplifier used in BM service.

Alignment and Adjustment

To tune the balanced modulator, all you need is about 5W of rf drive (from HW-17 or TX-62) and an swr bridge. The bridge is used as an output indicator. First peak the grid circuit for a small meter deflection, with sensitivity control at maximum and key down. The BM should be plugged-in and turned on, of course. Notice that the peak can be increased greatly by output tank adjustment - if it cannot, disassemble the unit and check to see if tank variables are within stator mesh. Grid-dipping can help greatly here, before firing up.

When both input and output peaks are obtained (with no audio feed), the swr bridge sensitivity can be turned back to about 10% full-scale and some audio can be

injected to the screens. Speaking into the mike should cause momentary full-scale readings. Driver must operate key down, as before. There is a point where increased audio gain will result in increased distortion (I listen on headphones while my receiver is partially muted). With a *dummy load* connected and vswr normal, the point can be determined visually by observing the erratic output meter indication. Eliminate residual shack noise by shorting mike input when setting audio level.


An oscilloscope can also be used to gage flat-topping; however, inexpert use of this instrument can result in disaster quicker than by reliance upon elementary auditory monitoring with headphones and the bridge. An itemized procedure without the scope follows:

1. After peaking the circuits as above, keep feedthrough indication no higher than about 10% highest momentary level (without speech, key down).
2. There should be no variation in feedthrough level with the microphone switched off.
3. Juggle the drive level so that enough excitation is present to allow maximum deflection on the output indicator, but not so *little* as to *not* allow whatever loud vowel sounds may be spoken to register full-scale momentary indication. Note: This rf driving range is quite broad, i.e., from 1 to 5W (estimated)

on the paralleled grids because resistor bias is self-regulating. 4. Repeat these steps until you're sure there's no instability, exciter (driver final) heating, or rf feedback.


Actual carrier suppression is much greater than merely 10 to 1! The difference between the indication of so-called "average" signal and nulled carrier is about 100 times. For example, most of the feedthrough is simply drive power or capacitively coupled in-phase energy that is rejected from balanced modulator output during those intervals when speech is present. Remember, in-phase energy like this is normally rejected by any voltage amplifier when used in power circuits, by normal 180° phasing. An exception would be the cathode follower current amplifier, or the grounded-grid power amplifier.

To finish adjustments I found it convenient to listen again on my receiver to the DSBSC signal, with upper sideband setting preferred. I do this with the rf gain all the way back. That sing-songy sideband sound is reassuring. Careful adjustment of tuning results in good-quality sideband. An oscilloscope might find use, now, as a final check. Calling a friend to check out your gear is an excellent way also. Experience will show you need *not* try for momentary-peak indications on a monitor to be

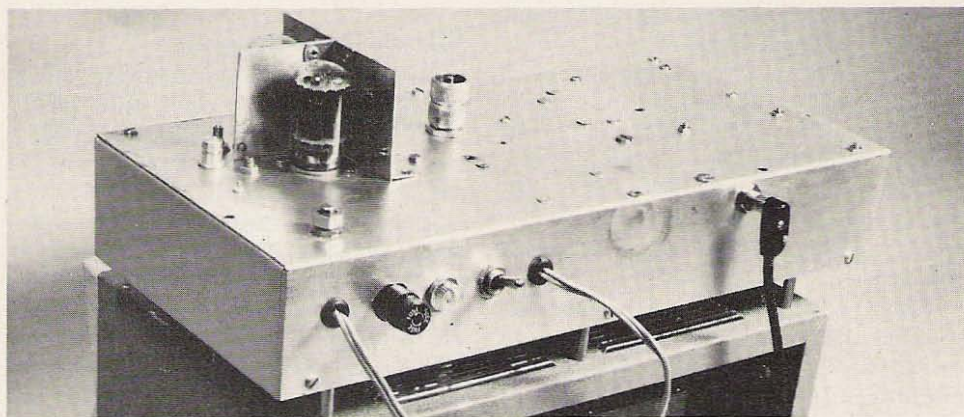

This photograph shows the completed DSB unit and its mounting upon the Heathkit AA-13 monophonic amplifier. The three-leaved interpartition shield is necessary to prevent oscillation and resultant instability. Two types 8156s are

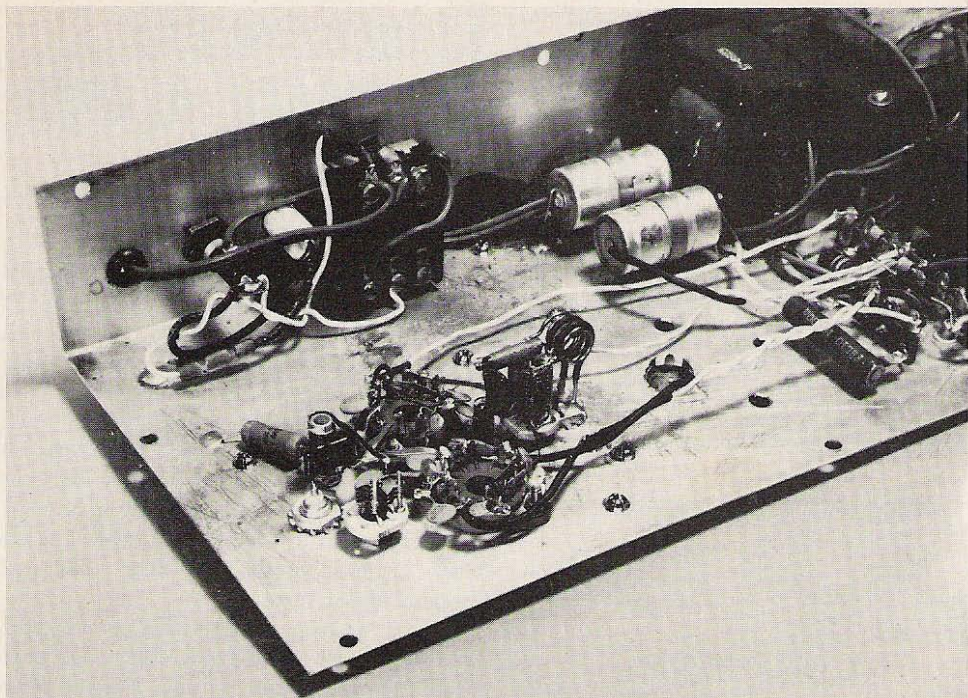depicted, although the final "4th generation" version uses 7984s. A screwdriver adjust pot is provided; however, this was abandoned when we went to self-bias as opposed to fixed.



Here's the final version (underside) of W4KAE's DSBSC rig. Note the inductive divider series tuned input made from an E.F.J. "M" capacitor and a ceramic form series coil, connected with 1/8th in. strap. The silver mica 0.001 capacitor

connects to the "Y" going to both control grids in parallel. Output tank has moderate L to C ratio, using a 160-211 butterfly variable which establishes rf ground.

the same as full carrier indication at the same power level: this is because the meter damping will not allow true "peak" readings. Because of this, don't "talk up" to the same level you used to run on AM.

Use and Conclusion

Using the 2m VHF double-sideband rig is fun. Most SSB stations in Cincinnati could not tell the difference between it and their mode. DX stations like VE3BIG could copy very well; however, the only problems (with DX) came when a multipath fadeout forced retuning on their part, and confusion resulted in which sideband to use. This is not as great a problem as might be expected, however, because we use the piggy-back method of DXing and everyone stays right on frequency (no tail-ending)!


Concern about wasted power in the other sideband is almost academic in practical operation, since duty cycle is quite

low for SSB or DSBSC. If "they" can hear you at all, chances are the lost energy is unimportant. If your linear can be run at slightly lower plate voltage than normal, you can get some increase in signal by overdriving it a little — getting rf clipping this way — but don't crank the audio up into the balanced modulator.

The one disadvantage to DSB is the operator confusion previously mentioned: It's not so bad on DX, but 80-mile Cincinnati stations tend to become relaxed in a long QSO and sometimes they forget which sideband to tune, winding up with a 3 kHz offset on alternate transmissions! I'm sure this problem can be overcome if operators learn to switch sidebands on their receivers, when hearing backward speech, instead of trying to retune for just one sideband. With DSB, you should always switch from UPPER to LOWER or vice versa, when hearing "backward" speech — then retune.

...W4KAE■

VIBROPLEX

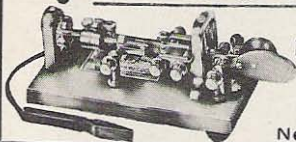


ENJOY EASY,
RESTFUL KEYING
\$21.95 to \$43.95
THE VIBROPLEX
CO., INC.
833 Broadway,
New York, NY 10003

WORLD QSL BUREAU

5200 Panama Ave., Richmond CA USA 94804
THE ONLY QSL BUREAU to handle all of
your QSLs to anywhere; next door, the next
state, the next county, the whole world. Just
bundle them up (please arrange alphabetically)
and send them to us with payment of 5¢ each.

SSTV COMPLETE STATION \$545

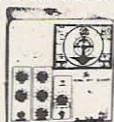

AVAILABLE IN
KIT FORM ALSO

E. K. Y. VIDEO VISION CO.
BOX 15, STOCKHOLM NJ 07460

HAL DEVICES

HOT CARRIER DIODES: HP2806...\$.90, 12/510 00 Matched by HAL...4/\$4.25

ZENERS: 1N4729(3.3v), 1N4733(5.1v), 1N4735(6.2v), 1N4738(8.2v),
1N4739(9.1v), 1N4742(12v), 1N4742(15v), 1 watt...\$.75

LINEAR ICs: 709N...\$.75 708L 710N...\$1.25 741N...\$1.50
MC1429G...\$3.75 MC1496G...\$3.25 MC1596G...\$5.60

DIGITAL ICs: F1L923...\$.90 MC767P...\$3.30 MC723P...\$.95

MRTL: MC788P...\$1.30 MC880P...\$3.50 MC890P...\$2.00
MC724P, MC725P, MC789P, MC792P...\$1.05

MC771P...\$1.75 MC970P...\$3.30 MC9760P...\$9.45



DIP TTL: 7400, 7401, 7402, 7410, 7420, 7430, 7440...\$.48

7404, 7405...\$.80 7407, 7409, 7496...\$3.00 7442...\$2.75

7472...\$.75 7473, 7474...\$1.05 7475...\$2.40

7486...\$1.15 7490, 7492, 7493...\$2.10 74121...\$1.40

FETS: 40673 MOSFET...\$1.80 MPF102...\$.60 2N3619...\$.95

TOROIDs: Indiana General CF102-06, CF102-01, CF101-02...\$.50
CF102-03...\$1.25 FERROXUBE FERRITE BEADS...10/\$1.25

CINCH IC SOCKETS: 8-ICS, 14-DIP...\$.60 10-ICS, 16-DIP...\$.70

MANY OTHER DEVICES AND COMPONENTS IN STOCK. WRITE FOR CATALOG.

HAL DEVICES

Box 365L, Urbana IL 61801 ● 217-359-7373

WE PAY CASH FOR TUBES

Lewispaal Electronics, Inc.
303 West Crescent Avenue
Allandale, New Jersey 07401

73 tests the 270 AUTOMATIC ALARM

And likes it . . . and likes it!

After having a nice brand new Standard FM transceiver ripped out of an assistant editor's car, and further to find that this multi-centibuck investment brought nothing from the assorted insurance companies (which are gradually bleeding us of as much green corpuscles as they can) but shrugged shoulders and polite letters of too bad but we don't feel that we covered you for this, nervousness set in every time I looked at the mass of two meter FM gear that had accumulated in my car.

Never one to go at anything in ham radio half way, I set about being able to get into all of the repeaters in W1- and W2-land from my car. This built up into three rigs and three antennas around the top and back of the car, making it look like a wounded porcupine scuttling down the road. I was able to hide two of the rigs in the large Rover glove compartment, thus keeping them out of sight when not in use, but this still left a third sitting up on the dashboard as a tempting prize for any enterprising youth. This isn't much of a problem in New Hampshire, of course, but then I do drive down to New York and other areas where the life of an exposed piece of gear is measured in minutes, and it is a drag to have to put the rigs in the trunk every time I park.

Being an avid reader of 73 magazine, I could hardly help but notice that ad in the November issue by Technical Product Development Company for an automatic alarm. I went the whole way and ordered one of their Model 270 Automatic alarms, complete with siren. The alarm gadget costs \$50, if you get it with all the options. This includes a recycler which turns off the siren after about two minutes and resets again automatically to guard against re-entry. The alarm is \$40 without this feature. A manual model is available for \$30 with the recycler and \$20

without. The siren is \$19 if you prefer that to using your regular car horn. There is something particularly alarming about a siren, so I went that route. I figured there would be no question if I heard my car sounding off in a distance that way.

So there was old fumble-fingers Wayne, armed with the alarm system, a set of instructions, and a pair of wire cutters. The whole operation took me just under two hours, and that included a couple of pauses for coffee, a long phone call from an author, and some hunting around the house for solder lugs and screws that I turned out not to really need. I think one hour would have done it if I could have kept my mind on what I was doing.

When the job was done there came the good old "smoke" test. I sat in the car, turned off the ignition, waited one minute and then opened the car door. Would it work? Ten seconds later the siren let loose and the whole east end of Peterborough knew that it worked.

You have about 40 seconds or so after you turn off the ignition to get out of the car and close the doors. Then the alarm arms itself and is ready to let out a howl that will panic anyone within a hundred yards. You have seven seconds or so after opening the car door to turn on that ignition key before all hell breaks loose. Imagine the panic some night when I get into the car and manage to drop the key. I am able to do this . . . I've proven it.

A few weeks ago I was getting out of the car and somehow the ignition key caught on the steering wheel and flipped out of my hand. Big deal, right? Well, Lin and I hunted for fifteen minutes trying to find where it went. We looked everywhere! We checked in the seats, under them, under the floor mats, glove compartments, and on and on and on. We checked outside the car . . . nothing! Was it an apport? Thank heavens I didn't have that alarm set up then.

Now, I'm ready for downtown Boston . . . even for New York! Perhaps I am being too smug. Knowing New York, they may well steal the alarm along with everything else. But they'll have to work for it and their eardrums will never be the same.

. . . W2NSD/1

oscillator/monitor^{mark 2}


- makes an audible tone to monitor the RF of any CW transmitter from 10Mw to 1 Kw & 100Kc to 1000Mc, using only an 8' pickup antenna.
- can be self-triggered for code practice or the testing of solid state components and circuits.
- aids in tuning up & testing RF oscillator and power circuits.
- 4 transistor, 2 diode circuit, speaker, tone adjust, AA pencil, test tips, 8" ant., & magnetic base.
- cabinet is 16 gauge black & clear anodized aluminum, 3.4 x 2.3 x 1.2" US made & guaranteed for 1 year.



14.95 complete,
ppd usa & can.
send a check or m.o.
sold by mail only

James Research company, dept: AR-M
20 willits road, glen cove n.y. 11542

LEARN RADIO CODE

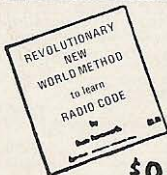

\$9.95

Album contains three 12" LP's 2 1/2 hr. instruction.

THE EASY WAY!

- No Books To Read
- No Visual Gimmicks To Distract You
- Just Listen And Learn


Based on modern psychological techniques—This course will take you beyond 13 w.p.m. in **LESS THAN HALF THE TIME!** Available on magnetic tape, \$9.95 — Cassette, \$10.95

EPSILON [E] RECORDS

508 East Washington St., Arcola, Illinois 61910

HAL DEVICES

HAL ID-1 REPEATER IDENTIFIER

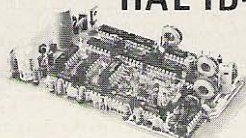

\$7500

Circuit board wired & tested.

TTL logic. Power line frequency counter for 3 minute or less timing and control. Easily reprogrammable diode ROM uses only 27 diodes (depending on call) to send DE "any call". Low impedance audio with volume and tone control. All circuitry including PS on small G10 glass PC board. Write for full details. HAL DEVICES, BOX 365, URBANA, ILLINOIS 61801

AT LAST!

THE ANSWER TO YOUR
AUTO THEFT WORRIES

SYSTEM 270 AUTO ALARM

FOR FURTHER INFORMATION CONTACT:

**TECHNICAL PRODUCT
DEVELOPMENT CO.**

P.O. Box 84, Nutley, New Jersey 07110

A revolutionary new solid state auto alarm system far ahead of its time. So advanced it even contains an electronic memory which AUTOMATICALLY arms the alarm system every time you leave your auto. By far the easiest installed, most convenient, most protective auto alarm ever.



BRAND NEW FREQ-SHIFT TTY MONITOR:
NAVY OCT-3: FM Receiver type, freq. range 1 to 26 MHz in 4 bands, cont. tuning, Crystal calib. Reads up to 1500 Hz deviation on built-in VTVM. Cost \$1100.00 each! In original box, with instruct. book & cord, fob Mariposa, Cal. 49.50

HIGH-SENSITIVITY WIDE-BAND RECEIVER
COMMUNICATIONS • BUG DETECTION
• SPECTRUM STUDIES

38-1000 MHz AN/ALR-5: Consists of brand new tuner/converter CV-253/ALR in original factory pack and an exc. used, checked OK & grid main receiver R-444 modified for 120 v. 50/60 hz. The tuner covers the range in 4 bands; each band has its own Type N Ant. input. Packed with each tuner is the factory inspector's checkout sheet. The one we opened showed **SENSITIVITY:** 1.1 uv at 38.4 mhz, 0.9 at 133 mhz, 5 at 538 mhz, 4 1/2 at 778 mhz, 7 at 1 ghz. The receiver is actually a 30 mhz IF ampl. with all that follows, including a diode meter for relative signal strengths; an atten. calibrated in 6 db steps to -74 db, followed by an AVC position; Pan., Video & AF outputs; switch select pass of ±200 khz or ±2 mhz; and SELECT AM or FM. With Handbook & pwr. input plug, all only 375.00

30 mHz Panadapter for the above 129.50

Regul. Pwr Sply for Command, LM, Etc.

PP-106/US Metered. Knob-adjustable 90-270 v up to 80 ma; also select an AC of 6.3 5A, or 12.6 v 2 1/2 A or 28 v 2 1/2 A. With mating output plug & all tech. cata. Shpg. wt. 50 lbs. 19.50
BARGAINS WHICH THE ABOVE WILL POWER: LM-(*) Freq. Meter: 125-20 MHz, .01%, CW or AM, with serial-matched calib. book, tech. data, mating plug. Shipping wt. 16 lbs. 57.50
 TS-323 Freq. Meter: 20-480 mhz, .001% 169.50

R23A/ARC5 Command Q-5'er 190-550 KHz, exc. cond. 16.95
A.R.C. R22 Command rev 540-1600 KHz, exc. cond 17.95
A.R.C. R15 (MIL R-509) Command, 108-135 KHz, new 27.50

NEMS-CLARKE #1670 FM Revr 55-260 MHz like new 475.00
 WVW Rcvr/Comparator 2 1/2 - 20 MHz, solid state 250.00
 SSB Converter CV-591A/URR (455 KHz) w/book 137.50
 Ferris #32 (*) Field Strength Meter is a red-hot receiver from 150 KHz to 20 MHz, only 95.00
 Empire Devices NF-114 RFT meter is a red-hot receiver from 150 KHz to 80 MHz 295.00
 Spectrum Analyzer Give-Away: Polarad TSA with STU-1 head: 10-1000 MHz. Looks good, sold as-is 350.00

We have the best test-equipment & oscilloscope inventory in the country so ask for your needs . . . don't ask for an overall catalog . . . we also buy, so tell us what you have.

R. E. GOODHEART CO., Inc.
 Box 1220 GC, Beverly Hills, Calif. 90213
 Phones: Area Code 213, Office 272-5707

Toroid core, reactor or inductor. Core size 1/2" thick 1 1/4" wide 2 3/8" od 1 3/8" id. Silicon steel spiral wound plastic covered core. This toroid core now has 296 turns of #18 wire wound around core. Core weight 13 oz. wire weight 1/2 lb. total weight 1 lb. 5 oz. Room for additional 12 volt primary and feedback windings. CAN be used for powering FM with voltage doubling circuit. Approximate D.C. output 500 volts. Power input up to 200 watts \$90 ea, 3 for \$250

Write to us for items available.

TOWER COMMUNICATIONS
 1220-22 Villa St., Racine, WI 53403

SIMPLE SQUELCH

As anyone who has monitored a receiver for any length of time knows, a squelch is worth its weight in gold. Especially mobile, nothing can seem more tiring than constant receiver noise.

A simple squelch arrangement can be added to most small transceivers, with minimum effort, to alleviate the problem. Two diodes and a few resistors are all that is needed to make this effective squelch.

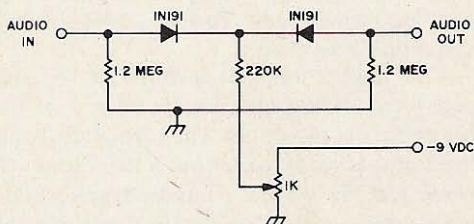


Fig. 1. Simple squelch circuit. Install before final audio amplifier.

The squelch circuit can be inserted between the last audio stage of the receiver and the final audio amplifier. The squelch level is set by varying the 1K pot. Power is most easily obtained from a 9V transistor battery.

...Larry Jack WA3AQS

PICKERING RADIO CO.
 Post Office Box 29 A
 Portsmouth R.I. 02871

IS IT EASY TO LEARN THE CODE?

Frankly, no. Neither was it easy to learn how to read without two things: Proper instruction, and practice. CODEMASTER tapes, proven in over five years of sales of thousands of tapes all over the world, give you that essential instruction. No other teaching system offers you a more proven method, more accurate sending, more complete guidance. Select your CODEMASTER tapes below!

CM-1: For the beginner. A complete course of instruction is on the tape. Practice material at 5, 7, 9 WPM. Prepares you for Novice exam. Includes code groups and punctuation.

CM-1 1/2: An intermediate tape, especially for General Class exam study. No instruction; just practice. 1/2 hr 11 WPM; 1 hr 14 WPM; 1/2 hr at 17 WPM. Includes coded groups and straight text.

CM-2: For Extra-Class license study. Mostly straight text, some code groups. 1 hour at 20 WPM, 1/2 hour each at 25 and 30 WPM. For real QRQ, play this tape at twice speed!

CODEMASTER tapes are 2-track monaural; available in two styles: 7 inch reel (3 1/2 IPS) and cassette. Be sure to specify both the program (CM-1, etc) and the style (reel or cassette). Any tape, \$6.95 postpaid USA 4th class. Any two tapes, \$13.00; all three, \$17.00 PPD. For air shipment in USA add 50¢ per cassette or 80¢ per reel. Immediate delivery. MasterCard and BankAmericard honored; give us your account number. CODEMASTER tapes are made only by Pickering Radio Company, P O Box 29A, Portsmouth, RI 02871. See your dealer or order direct. Satisfaction guaranteed.

JEFF-TRONICS

SOLA CONSTANT VOLTAGE TRANSFORMER, type CV, #22-962 5E93. 1000 Va, 108-132 volts input, 118 volts out, 8.48 amps, 60 Hz. Brand new. Shpg. Wt. 65 lbs.
\$35.00 each 3 for \$95.00

POWERSTAT, 230 v. input, 0-230 v. out, 35 amps max., 60 Hz. 14" wide, 6 1/2" high. No cover or dial. Used, exc. Wt. 75 lbs.
\$22.50 each 5 for \$100.00
(above 2 items ship by REA or motor freight)

Panoramic SB-8B T-1000 Spectrum Analyzer. 5 Mc. IF. With power supply \$200.00
APR-4Y receiver with CV-253 plug-in. Tunes 38-1000 MHZ. 115 v. 60 Hz \$200.00
H-P 100-D Frequency Standard \$135.00
H-P 524-B Counter, 10 Mc \$250.00
526-A Video Amplifier plug-in for 524-B, C, D. \$50.00
526-D Phase Unit plug-in for 524-B, C, D. Measures phase angle to 0.1 degree \$100.00
H-P 715-A Klystron Power Supply \$60.00

Send for catalog of surplus electronic equipment & parts. 25¢ for handling.

JEFF-TRONICS

4252 Pearl Rd., Cleveland, OH 44109

GATEWAY ELECTRONICS

6150 DELMAR BLVD., ST. LOUIS, MO 63112
314-726-6116

MOTOROLA 432 Mhz TRANSCEIVERS - Model T44-6A - Complete with all cables, control head, and mic. - ship wt. 75 lb. \$25.00

RCA 150 Mhz TRANSCEIVERS - Model CMC-30 CAR FONE - Complete with all cables, control head, and mic. - ship wt. 75 lb. \$85.00

12 VOLT A RELAY - ship wt. 1/2 lb. \$3.50
2C39 A (Ceramic version) - ship wt. 1/2 lb. \$6.00
6397 (final used in P-33 etc.) - ship wt. 1/8 lb. \$4.50
1AD4 - ship wt. 1/8 lb. \$2.50
5678 - ship wt. 1/8 lb. \$1.50

MOTOROLA 6 VOLT XTAL OVEN - ship wt. 1/2 lb. \$1.00
RCA 12 VOLT XTAL OVEN - ship wt. 1/2 lb. \$3.50
GE 12 VOLT XTAL OVEN - ship wt. 1/2 lb. \$3.50

4 COND. MIC. CABLE - Coil Cord - 2 shielded - 2 unshielded - 30" retracted - 15" extended - ship wt. 2 lb. \$6.50

BRUSH 4 CHANNEL CHART RECORDER - Model RD2341 with DC Amplifiers and cables - ship wt. 75 lb. \$250.00

See other ads for our IC prices and write for our catalog. Stop in and see us when you're in St. Louis.

ALLEN BRADLEY'S "MICRO-POTS"

Any 2 for \$1

Type G, 1/2" dia. x 1/2" high. Mounts 1/4" hole, with shaft, linear, immersion-proof high freq.



<input type="checkbox"/> 100	<input type="checkbox"/> 1.0K	<input type="checkbox"/> 10K	<input type="checkbox"/> 100K	<input type="checkbox"/> 1 Meg.
<input type="checkbox"/> 250	<input type="checkbox"/> 2.5K	<input type="checkbox"/> 25K	<input type="checkbox"/> 250K	<input type="checkbox"/> 2 Meg.
<input type="checkbox"/> 500	<input type="checkbox"/> 5.0K	<input type="checkbox"/> 50K	<input type="checkbox"/> 500K	<input type="checkbox"/> 5 Meg.

PIV	1Amp*	2Amp	3Amp	EPOXY SILICON RECTIFIERS
50	\$.05	\$.05	\$.08	
100	.06	.06	.12	
200	.07	.07	.15	
400	.09	.09	.22	
600	.12	.12	.28	
800	.15	.16	.39	
1000	.18	.22	.59	

LINEAR AMPLIFIER SALE!

Type	Function	Sale
<input type="checkbox"/> 709C*	Operational	.59
<input type="checkbox"/> 710C*	Hi-speed Dif. Comparator	.59
<input type="checkbox"/> 711C*	Dual Comparator	.59
<input type="checkbox"/> 723	Voltage Regulator	1.49
<input type="checkbox"/> 741	Freq. Comp. 709	.95
<input type="checkbox"/> 709-709	Dual 709's	1.49
<input type="checkbox"/> 741-741	Dual 741's	1.98

Buy Any 3 Take 10% Discount!

State case desired: DIP, TO-5, FLAT PAK

6-AMP FULL WAVE BRIDGES

PRV	SALE	400	1.50
50	\$.88	600	1.75
100	.99	800	1.95
200	1.25	1000	2.25



LIGHT EMITTING DIODES

Use as logic readouts, either on panel or right on cards. Infinite life. **\$1** Visible LED

- 2.5 AMP 1000 PIV SILICON RECTIFIER
 - 6 AMP 2000 PIV SILICON STUD RECTIFIER
 - EPOXY
 - Microminiature
 - Obsolete "bullets"
- 4 for \$1 Only \$1

GIANT SALE ON NEW TTL TEXAS & NATIONAL ICs

Buy Any 3 - Take 10% Discount!

*Factory Tested! *Factory Guaranteed!

Type	Function	Sale
<input type="checkbox"/> SN7400N	Quad 2 input NAND gate	\$.45
<input type="checkbox"/> SN7401N	SN7400 with open collect	.45
<input type="checkbox"/> SN7402N	Quad 2 input NOR gate	.45
<input type="checkbox"/> SN7404N	Hex inverter	.45
<input type="checkbox"/> SN7405N	Hex inverter, open collect	.45
<input type="checkbox"/> SN7410N	Triple 3 input NAND gate	.45
<input type="checkbox"/> SN74120N	Dual 4 input NAND gate	.45
<input type="checkbox"/> SN7430N	8 input NAND gate	.45
<input type="checkbox"/> SN7440N	Dual 4 input NAND buffer	.45
<input type="checkbox"/> SN7441N	BCD-to-Decimal driver	1.50
<input type="checkbox"/> SN7446N	BCD-to-7 seg. dec./driver	2.25
<input type="checkbox"/> SN7447N	BCD-to-7 seg. dec./driver	2.25
<input type="checkbox"/> SN7472N	J-K Master slave flip-flop	.69
<input type="checkbox"/> SN7473N	Dual J-K Master slave flip-flop	.88
<input type="checkbox"/> SN7474N	Dual D triggered flip flop	.69
<input type="checkbox"/> SN7475N	Quad bistable latch	1.50
<input type="checkbox"/> SN7476N	SN7473, with preset-n-clear	.88
<input type="checkbox"/> SN7481N	16-bit memory (scratch pad)	1.50
<input type="checkbox"/> SN7483N	4-bit binary full adder	2.25
<input type="checkbox"/> SN7490N	Decade counter	1.50
<input type="checkbox"/> SN7491N	8-bit shift register	1.98
<input type="checkbox"/> SN7492N	Divide by 12 counter	1.50
<input type="checkbox"/> SN7493N	4-bit binary counter	1.50
<input type="checkbox"/> SN7494N	4-bit shift register	1.50
<input type="checkbox"/> SN7495N	4-bit register right-N-left	1.50

- 15¢ CATALOG on Fiber Optics, 'ICs', Semi's, Parts

Terms: add postage. Rated: net 30, cod's 25%
Phone Orders: Wakefield, Mass. (617) 245-3829
Retail: 211 Albion St., Wakefield, Mass.

POLY PAKS

P.O. BOX 942 A
Lynnfield, Mass.
01940

READER SERVICE

Please either tear out this list of advertisers and send it in to 73 with as many boxes checked off as you would like to see brochures, data sheets or catalogs... or else make a copy and send that in. Do NOT fail to send for data on those products and services that interest you. Your magazine will be as large as the number of ads allow it to be... so the more you encourage the advertisers the bigger magazine you will have. When you send for information, the advertisers get encouraged. Send.

ADVERTISER INDEX *December, 1971*

- | | |
|---|---|
| <input type="checkbox"/> Adirondack 61 | <input type="checkbox"/> Jefftronics 95 |
| <input type="checkbox"/> Allied 66, 67 | <input type="checkbox"/> Juge 56 |
| <input type="checkbox"/> An-Tek Industries 87 | <input type="checkbox"/> K-Enterprises 68 |
| <input type="checkbox"/> ATV 18 | <input type="checkbox"/> Key Telemetry 86 |
| <input type="checkbox"/> Avcom 65 | <input type="checkbox"/> Lee Electronics 59 |
| <input type="checkbox"/> Callbook 34, 86 | <input type="checkbox"/> Lewispaul 92 |
| <input type="checkbox"/> Circuit Spec. 57 | <input type="checkbox"/> Mann 62, 63 |
| <input type="checkbox"/> Clegg Div. of I.S.C. Cover III | <input type="checkbox"/> Micro Comm 16 |
| <input type="checkbox"/> Comcraft 64 | <input type="checkbox"/> Nu Sigma Alpha 87 |
| <input type="checkbox"/> Comm Spec. 52 | <input type="checkbox"/> Palomar 18 |
| <input type="checkbox"/> Cornell 87 | <input type="checkbox"/> Pearce Simpson 48 |
| <input type="checkbox"/> Crawford 77 | <input type="checkbox"/> Pickering 94 |
| <input type="checkbox"/> C.T. Power 70, 71 | <input type="checkbox"/> Poly Paks 95 |
| <input type="checkbox"/> Curtis 30 | <input type="checkbox"/> RP 28 |
| <input type="checkbox"/> Dahl 30 | <input type="checkbox"/> Saroc Cover II |
| <input type="checkbox"/> Data Eng. 58 | <input type="checkbox"/> Simpson 69 |
| <input type="checkbox"/> Drake Cover IV | <input type="checkbox"/> Sonar 75 |
| <input type="checkbox"/> DyComm 35 | <input type="checkbox"/> Tab Books 74 |
| <input type="checkbox"/> Dynalab 30 | <input type="checkbox"/> Tallen 76 |
| <input type="checkbox"/> EKY 92 | <input type="checkbox"/> Tech Products 93 |
| <input type="checkbox"/> Electra 72 | <input type="checkbox"/> Telrex 36 |
| <input type="checkbox"/> Erickson 53 | <input type="checkbox"/> Telvac 28 |
| <input type="checkbox"/> Epsilon 93 | <input type="checkbox"/> Tower 94 |
| <input type="checkbox"/> Freck 30 | <input type="checkbox"/> Vanguard 54, 55 |
| <input type="checkbox"/> Gam 60 | <input type="checkbox"/> Van W2DLT 87 |
| <input type="checkbox"/> Gateway 95 | <input type="checkbox"/> Vibroplex 92 |
| <input type="checkbox"/> G&G 73 | <input type="checkbox"/> Wolf 77 |
| <input type="checkbox"/> Goodheart 94 | <input type="checkbox"/> World QSL 92 |
| <input type="checkbox"/> Hal 92, 93 | <input type="checkbox"/> World Radio 50 |
| <input type="checkbox"/> Hale 86 | |
| <input type="checkbox"/> Heath 26 | |
| <input type="checkbox"/> Henry 24, 25 | |
| <input type="checkbox"/> Hi Par 87 | |
| <input type="checkbox"/> H&L 87 | |
| <input type="checkbox"/> James 93 | |
| <input type="checkbox"/> Jan 82 | |
| <input type="checkbox"/> Janel 87 | |

- 73 Stuff
 Ad Letter 45
 73 Subscriptions 46, 47
 FM Repeater Atlas 78
 FM Rptr. Circ. Manual 78
 Radio Bookshop 79

Mail to: 73 INC., PETERBOROUGH NH 03458

Name _____ Call _____

Address _____

Zip _____

PROPAGATION CHART J. H. Nelson Good Fair (open) Poor

December 1971

SUN	MON	TUES	WED	THUR	FRI	SAT
			1	2	3	4
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30	31	

EASTERN UNITED STATES TO:

GMT: 00 02 04 06 08 10 12 14 16 18 20 22

ALASKA	14	7	7	3A	3A	3A	3A	7	14	21	21
ARGENTINA	14	7	7	7	7	7	14	21	21	21	14
AUSTRALIA	14	7A	7B	7B	7B	7B	7B	14	14	14	14A
CANAL ZONE	14	7	7	7	7	14	21	21A	21A	21A	21
ENGLAND	7	7	7	3A	7	7B	14	21	21	14	7B
HAWAII	14	7B	7	7	7	7	7B	7B	14	21A	21
INDIA	7	7	7B	7B	7B	7B	14	7B	7B	7	7
JAPAN	14	7B	7B	7B	7	7	3A	7	7B	7B	14
MEXICO	14	7	7	7	7	7	14	21	21	21	14A
PHILIPPINES	14	7B	7B	7B	7B	7	7	7B	7B	3B	7
PUERTO RICO	7	7	7	7	7	14	14A	14A	14A	14	14
SOUTH AFRICA	7B	7	7	7	7B	7B	14	21	21A	21	14
U. S. S. R.	7	7	3A	3A	7	7B	14	14A	14	7B	7
WEST COAST	14	7A	7	7	7	7	14	21	21A	21A	21

CENTRAL UNITED STATES TO:

ALASKA	14	7	3A	3A	3A	3A	3A	7	14	21	21
ARGENTINA	14	7A	7	7	7	7	14	21	21	21	21
AUSTRALIA	21	14	7B	7B	7B	7B	7B	14	14	14A	14A
CANAL ZONE	14	14	7	7	7	7	14	21	21A	21A	21
ENGLAND	7	7	7	3A	7	7B	14	21	21A	14	7B
HAWAII	21	14	7	7	7	7	7	7B	14	21A	21
INDIA	7	7A	7B	7B	7B	3B	8	8	7B	7B	7B
JAPAN	14	7B	7B	3A	3A	7	3A	3A	7	7B	7B
MEXICO	14	7	7	7	7	7	14	14A	14A	14A	14
PHILIPPINES	14A	7B	7B	3B	3B	7	3A	3A	7	7B	3B
PUERTO RICO	14	7	7	7	7	7	7A	21	21A	21	21
SOUTH AFRICA	14	7B	7	7B	7B	7A	21	21A	21	21	14
U. S. S. R.	7	7	3A	3A	7	7B	14	7A	7B	7B	7

WESTERN UNITED STATES TO:

ALASKA	14	14	7	3A	3A	3A	3A	7	14	21	21
ARGENTINA	14	14	7	7	7	7	14	14A	21	21	21
AUSTRALIA	21	21	14	7B	7B	7B	7B	14	14	14A	14A
CANAL ZONE	14	14	7	7	7	7	14	21A	21A	21A	21
ENGLAND	7B	7	7	3A	7	7	3B	7B	14	14	7B
HAWAII	21	21	14	7	7	7	7	7	14A	21A	21A
INDIA	7B	14	7B	3B	3B	7B	3A	3A	7	7	7B
JAPAN	21	14	7B	3A	3A	3A	3A	7	7	7B	14
MEXICO	14	14	7	7	7	7	7	14	21	21	14A
PHILIPPINES	21	14	7B	7B	3B	3B	7	3A	7	7	7B
PUERTO RICO	14	7A	7	7	7	7	7	14	21A	21A	21A
SOUTH AFRICA	14	7B	7	7B	7B	7B	14	21	21	21	14
U. S. S. R.	7B	7	3A	3A	7	7B	7B	14	7B	7B	7B
EAST COAST	14	7A	7	7	7	7	14	21	21A	21A	21

A = Next higher frequency may be useful also.
 B = Difficult circuit this period.