

\$1.00
JULY 1974

73

magazine
for radio amateurs



new

HUSTLER

the real performer! specifically for repeater

...or any TWO-METER FIXED STATION OPERATION

With **6** db—
db—

- Gain compared to ½ wave dipole
- FCC accepted for repeater application

mechanical

- Vertical element—117" long, 1-1/8" telescopic to 3/8" OD high strength aluminum
- Radials—four, 21" x 3/16" OD aluminum rod
- Connector—SO-239
- Wind load—26 pounds at 100 mph.
- Wind survival—100 mph.
- Completely self-supporting
- Mounting—fits vertical pipe up to 1-3/4" OD


The gain you gain—you gain transmitting and receiving—get both with Hustler!

Available from
all distributors
who recognize the best!

electrical

- 6 db. gain over ½ wave dipole
- Omnidirectional radiation pattern
- Maximum radiation—at horizon
- 50 ohm feed impedance
- Field adjustable—140-150 MHz
- SWR at resonance—1.2:1 measured at antenna
- Bandwidth—6 MHz for 2:1 or better SWR
- Power—one kilowatt FM
- Feed—Shunt with D.C. grounding
- Radiator—5/8 wave lower section, ¼ wave phasing, 5/8 wave upper section

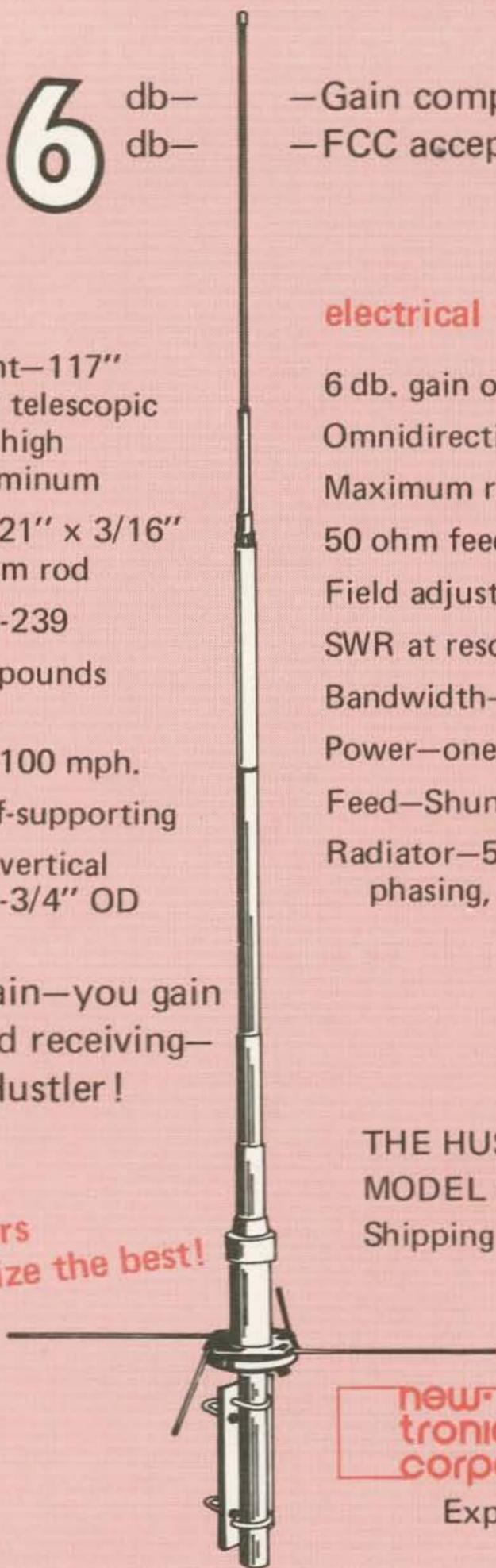THE HUSTLER MASTER GAINER
MODEL G6-144-A
Shipping Wt.: 6.8 lbs. Price: \$52.95



**new
tronics
corporation**

15800 commerce park drive,
brook park, ohio 44142

Exporter: Roburn Agencies, Inc.,
New York, N.Y.

FEATURES

- 2 W2NSD
- 4 SSTV Scene
- 6 Social Events
- 7 Looking West
- 8 Contests
- 8 Ham Help
- 9 New Products
- 10 Repeater Update
- 12 Traveling Ham
- 12 ATV Raster
- 13 New England Repeaters
- 13 FCC
- 14 Letters
- 15 Solid State
- 80 Circuits Circuits
- 90 Schematic of the Month
- 94 Hambuglar
- 95 Caveat Emptor
- 96 QSL Contest

EDITORIAL STAFF

Wayne Green W2NSD/1
Yvette Grimes WA8ULU/1

ASSOCIATES

Gus M. Browning W4BPD
Tom DiBiase WB8KZD
Terry Fox WB4JFI
Mike Frye WB8LBP
Dave Ingram K4TWJ
Joe Kasser G3ZCZ/W3
Bill Pasternak WA2HVK/6
Jonathan Tara WB8DBN
Bill Turner WA0ABI

PRODUCTION

Lenore DeLiguori
Lyman DeLiguori
Karen Hebert
Biff Mahoney
Lynn Panciera-Fraser
Bob Sawyer
Barbara Walker

BUSINESS

Knud E. Keller KV4GG/1

CIRCULATION

Barbara Block
Dorothy Gibson

TRANSPORTATION

Bill Barry
Marshall Raymond


DRAFTING

T. M. Graham W8FKW
Bill Morello
Wayne Peeler K4MVW

CONTENTS

- 17 **Modern 4-1000A Linear** K8UIR
At last — a use for that 4-1000A lying
around in your junkbox.
- 27 **"Free" Batteries for TT Pad Power** W3WTO
73 lands another great article.
- 31 **The Scotch Transistor** WA9UFG
Hoot Man, you don't have to throw it
away after all.
- 33 **Poor Man's Universal Frequency Generator** ... W2EEY
Only after you build it.
- 37 **Universal AFSK Generator** K6IQL/NØZIP
An article of cosmic importance.
- 47 **Cheap 10-minute Timer for the Shack** WB2VRW
Price does not necessarily indicate shoddiness.
- 49 **Low Frequency Phased Array** W2OZH
Here's one to satisfy all you 80m buffs.
- 55 **DC Isolation of RF Amplifiers and Modulators** . K1CLL
Another great one from Bill.
- 63 **Little Bill** W9WBH
A neat little transmitter.
- 69 **3000V DC Supply** K8VIR
Here's something to do after you finish
your 4-1000A.
- 73 **Diagrams** WB2PAP
At long last, an easy way to tell the difference
between a resistor and a tube.

73 Magazine is published monthly by 73, Inc., Peterborough, New Hampshire 03458. Subscription rates are \$7 for one year in North America and U.S. Zip Code areas overseas, \$8 per year elsewhere. Two years \$12 and \$13 overseas. Three years, \$15, and \$16 overseas. Second class postage paid at Peterborough, New Hampshire 03458. Phone: During office hours 603-924-3873, other times there is a tape recorder for messages on 603-924-3883. Microfilm edition of 73 available from University Microfilms, Ann Arbor MI 48106. Magnetic tapes available from Science for the Blind, 332 Rock Hill Rd., Bala Cynwyd PA 19904. Entire contents copyright 1974 by 73 Inc., Peterborough, NH 03458.

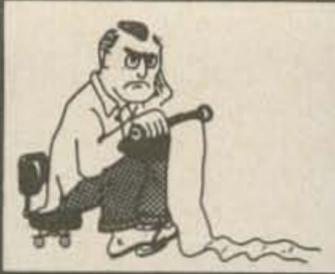

NEVER SAY DIE

...de W2NSD/I

THE IRS GOAL

The IRS works diligently to make sure that there will be stories in the newspapers, on the radio and on television telling of people who have been convicted of tax fraud — and they try very hard to see that these cases come off just before tax filing time. This is part of the IRS campaign of fear which helps keep taxpayers in line. They orchestrated my trial so the verdict would come out in time for national publicity just before tax return filing time. The IRS, with unlimited funds and the best of legal talent available from the Justice Department in Washington, virtually never loses a case.

IRS WIN?

While I expect that the next issue of Worldradio will headline that Green has been convicted by the IRS of income tax fraud — sentence suspended and probation for three years — the actual story is almost totally hidden by the IRS press release, as you might expect.

The whole purpose of many of the "trials" for tax fraud is to generate articles in the newspapers and magazines at tax time to frighten taxpayers into complete submission. If editors would refuse to give the IRS the PR they want, this whole program would fail and hundreds of people would be spared the trauma every year of being indicted, tried and found guilty of tax evasion — whether they have actually done anything wrong or not — a process that is helping to destroy faith in our government.

Yes, I sat through a trial, listening to a couple of people lie in order to protect themselves, and unable to say anything — to fight back — even to argue. I can see why the Chicago Seven let loose — the temptation was almost overpowering at times. Even so, there was never any testimony or evidence at all that I did anything wrong — nothing was hidden — books weren't altered — I had depended entirely on the accountants to prepare tax returns — I hadn't even read them over as Nixon did (he has a lot of tax experience — I haven't).

My lawyer felt that since no case had been made against me that we had nothing to worry about so he made virtually no defense or closing statement. Much has been written about

EDITORIAL BY WAYNE GREEN

having to prove oneself innocent in these courts and I can verify that. Even though the testimony of the accountants was that I depended on them to allocate all business and personal expenses, the jury of my peers (retired postal employees, housewives, etc.) decided that "I should have known that the tax returns weren't right." **GUILTY!**

So we're appealing the case.

There is so much to write about this that there is no way to present the material within the pages of 73. Those who are interested in getting the inside information on how the IRS works — how they defy constitutional protections with impunity — how they can win fraud cases even when the pidgeon is innocent (and they know it), should watch for the first of my books on the IRS.

May I ask that all readers keep your eyes peeled for newspaper clippings of IRS harassments and send them to me. My file is growing and the horror of the story the clippings tell is honestly beyond belief. I shall write this story.

In the meanwhile I am back at my regular stint, working at 73 day and night, and the magazine is doing well. There never was any serious problem as far as the magazine was concerned anyway since our carry-back losses for 1969 and 1970 more than cover any possible tax the IRS could come up with for the previous years. That's about the only benefit there is to losing money — and we did lose a bundle in those two years.

You didn't think the IRS was going to take my pressures on them lying down, did you?

OUT OF ONE POCKET THE IRS GETS THEIR CUT

Have you ever stopped to think of how come government employees have to pay income taxes? Does this make any sense at all?

The government salaries come from taxes collected, like from the income tax. So all that is happening is that Uncle Sam is giving with one hand and taking it back with the other. Unfortunately, the money doesn't just get from one hand to the other without going through a lot of other hands, each a little sticky.

The IRS charges for their collection service. In fact it costs more to keep

this den of thieves running than it does the whole postal system, as incredible as that may seem. In point of fact the Treasury (IRS) is the third most costly department of the government, with Defense and Health beating them out on expenses. The Treasury spends over 10% of the total government budget! It costs a lot to take the money from one pocket and put it back in the other when a government bureau is in the middle.

If all government salaries could be made tax free that would result in an immediate reduction of about 20% in the salary overhead of the government, but would reduce the income tax receipts by only about 7%, leaving a substantial net gain.

Considering the cost of the Treasury Department, perhaps more effort should be made to work out an alternative to the income tax. There has to be a more efficient way of paying for government.

DAYTON SMASH HIT! OVER 9000 REGISTERED

Trot out the adjectives — Dayton rated all of them. The exhibitors all went home smiling for most of the 9000 hams who attended the Hamvention brought money and spent it. One distributor claimed to have sold nearly \$30,000 worth of merchandise — one



Gordon West WB6NOA of Standard Communications took one look at the May Streaker cover and flipped! For that matter, this cover was the center of a lot of attention at Dayton, with fellows turning up every few minutes who had heard about it and wanted to get a copy before they ran out. For those readers who are not sophisticated enough to know a boy from a girl when they see one, the cover was a male type boy, despite the longish hair. Long hair seemed compatible with streaking. The streaking took place right here in Peterborough and the streekee was the brother of one of the lovely gals in the art department.

Gordon was in high humor after hearing how well his SC-R146A HT's were selling through his distributors. They were everywhere and you never heard such a mess as 94 during the Hamvention.

chap sold over \$3000 in batteries alone — and so it went. Exhibitors remarked that the crowd on Friday alone was better than any other ham-fest or convention has been able to turn out for an entire weekend.



The flea market (above) had over 700 displays and covered over seven acres. Dedicated scroungers were hard put to do the assortment of stuff even on the long weekend.



Wayne W2NSD/8 and Yvette WA8ULU at the 73 booth at Dayton. Subscriptions, code tapes and books all sold extremely well, keeping them busy for the whole weekend.



Bob Brown W2EDN of VHF Engineering had a chance to show and tell his new line of repeaters and his under \$100 HT's. The audience at the FM session ate it up.

The three day convention was decidedly a success. The complaints were few (there are always *some* complaints) and had to do with a need for better scheduling of tech sessions and an earlier closing on Sunday.

The FM sessions were most helpful in getting everyone up to date on the latest FCC twists and turns — bringing out needs for repeater council cooperation — and a solidifying of agreements on FM and repeater standards.

RESTRUCTURING AMATEUR RADIO

The FCC has a list of 43 petitions for rule making that have piled up — many of them contradictory. They probably have been putting off action on these (some for many years) because the changes which they would make are major ones and call for some basic rethinking of the whole structure of our licenses.

We have six different types of amateur licenses right now. Do we really need that many or can we simplify the structure a bit? Five of these classes have different frequency allocations. Do we really need that many? Should we continue the Technician license as it is — a sort of dead end for two meter FM? Should we open part of 10m for Techs as petitioned by the ARRL? Should we give Novice privileges to Techs so they can work some CW bands if they want to improve their code as petitioned by me? Should we have more phone bands? Should we get rid of AM on the low bands once and for all? If we do get rid of AM, should we then permit SSB and CW to use any frequencies they want, and go to an agreed sub-band setup rather than an FCC allocated one? How about a Communicator or Hobby class license, perhaps for 220 MHz, as a starter? Perhaps we need a CW Extra and a

Phone Extra license setup so phone ops won't have to pass a 20 wpm code test, which seems difficult to rationalize. Is it time to set up a whole new call sign arrangement so amateurs can just about have the call of their choice?

DON'T PANIC

If the FCC has any favorite restructuring plans for us they are keeping it quiet, and I was assured that they do have an open mind about all this and are more interested in the amateurs coming up with a plan that they want than in dumping one of their own making on us. Perhaps the trauma of the repeater license rules is fresh in their minds and they would like to try their best to avoid replaying that one. And in something as emotional as restructuring, the heat generated by Docket 18803 was just a candle next to a blast furnace.

The fact is that a great many amateurs are reactionary — they don't like change and will fight it, bitterly. Since change is inevitable (at least until immortality is discovered), I have always felt that we should accept the fact that there is going to be constant change and try to turn this to our advantage rather than fighting it.

The recent headlines in CQ about restructuring the licenses was not a reflection of FCC intent, but just a bunch of wishful thinking on the part of the magazine, bent more on promoting their own petition than on reporting news. There is a need for a good deal of thinking and planning before the FCC can come up with a notice of rule making — and the FCC is asking that you start working out your ideas for them. I would suggest that you bounce your ideas off the members of your local club before forwarding them to the FCC as this may help to weed out half baked schemes which will create more heat than light.

In case it does not go without saying, the letters pages of 73 are wide open for ideas on license structures and band plans.

CW?

One key concept you'll have to come to grips with has to do with the Morse Code. The present license structure is built around the code and the skill of being able to copy code is the single most important factor holding back advancement in license classes. In view of the almost total lack of use of CW for other than amateur radio, is this still important enough to hold this position?

We don't want to just throw open the gates, so to speak, for the mass input of CBers into amateur radio, complete with their disregard of the rules, which is frightening to consider. And on the other hand, with the number of amateurs steadily dropping, obviously something radical must be done to get things turned around. My own idea is to try to get the ARRL to spend some money (and they have a million dollars just sitting there unused) to get PR for amateur radio — and maybe even to advertise it. I prefer that to debasing the entrance exam because I feel that the less people have to work to get ham licenses, the less they will appreciate them. The Novice ticket is so simple a ten year old can hack it, so why go simpler than that?

I won't cover all of the arguments — you do that — okay?

OTHER PLANS

For argument more than a real proposal, the FCC has come up with an ultra-simple license plan — sort of an answer to CBers who want to get a ham license and talk with their buddies all over the country while sitting back with a cold beer after a day on the assembly line.

Entry
Form 1
Form 2
Universal Class License

(Continued on page 92)

SSTV SCENE

Dave Ingram K4TWJ
Rte. 11, Box 499, Eastwood Vil. 50N
Birmingham AL 35210

A Slow Scan milestone was recently accomplished when Johnny Bjornulf LA2BK, and Knut Gjertsen LA2PH/mm, successfully transmitted and received solid copy color SSTV pictures between Norway and the ship "Thorsage" which was in the South China Sea area. One of their best quality pictures, that of the newborn Prince Haakon Magnus, has appeared in magazines and newspapers throughout the Scandanavian area. Their QSOs were on 20m, and considering the distance involved, was quite a feat for our present band conditions.

Tic-Tac-Toe

On the lighter side of record setting events is W6EYY and WA7QBV's recent on-the-air tic-tac-toe game. Hal and Bob were located too close for a 15m QSO, and WB9GCS, hearing them both, acted as relay in this "3 corner event." No doubt that called for some lights, camera and tape recorder work! Who knows, today's games may point up tomorrow's possibilities.

Killer Tornadoes

The nationwide outbreak of killer tornadoes during April of this year pointed up the need for Slow Scan TV during emergencies. 2m autopatch operations have proved their merit during such times, now consider what an advantage SSTV coverage would be also. Pictures could be relayed back to TV stations, safety officials and newspapers immediately after a tornado, flood, earthquake or whatever. Concerned parties could see immediately the exact situation, and what steps should be instigated. Relief missions would have an idea of what awaited them. Just as 20m provides worldwide coverage, 2m provides local coverage. Obviously SSTV will soon fill this vital need. A camera and monitor would not necessarily need to be carried into the particular area. For example, Polaroid photos could be taken, then carried back a few miles to an SSTV setup. Or, a flying spot scanner might be carried in and the photos put into this. I have worked a couple of fellows mobile using Robot gear, and I'm sure if 15Hz sync lock is a problem, some of you could come up with a simple crystal time base counter for mobile operations. In fact, a SSTV camera is all that's really necessary in this type situation. Once you get familiar with your particular

camera, you can practically focus it by the lens calibration (which is not critical for distant shots, compared to "close-ups"). "F" stop adjustments can be "guesstimated" within close accuracy by listening for the swing of the camera's SSTV output on an earphone. Two SSTV operators working together over, say a 2m link, could focus a camera onto a scene within a minute or two; the "fixed" one observing a monitor and the "mobile" adjusting the lens. Sports photographers use a wire "sight" on their cameras for quick view finding. This idea could help you "view find" your SSTV picture easily. Use your imagination and consider these thoughts. SSTV is as useful (or useless) as we make it.

Have you ever noticed those little one dollar battery operated slide-viewers, you drop a slide in and it energizes a light for viewing? I couldn't help but think how dandy one of these would be for Slow Scan, so I bought one and mounted it beside my desk where the Robot Camera could be turned to look into it. Now, after marking the camera's lens settings for quick adjustment, the camera may view either the operating area or slides. The real advantage of this little "goodie" is that slides can be transmitted even in a very dim shack. (That's quite handy for tilting and IDs also.) After making a few slides using Datamark Letters, I dropped in some Instamatic 124 negatives and switched the camera to video invert. That worked so well I now use the Instamatic and have negatives only processed. (That is inexpensive enough to be worthwhile.) These little viewers are really hard to beat for a dollar "slide chain."

While on the subject, I might mention it's *definitely best* to place the viewer so the camera stays *horizontal*, not pointed down. Pointing a TV camera down can cause any impurities in the vidicon (or camera tube) to fall on the ultrasensitive target, permanently scratching it thus causing black spots or scratches to appear in all later televised pictures. Keep those camera's horizontal if at all possible!

Dayton

This year's Dayton convention was unquestionably the biggest milestone yet for SSTV. Although last minute problems prevented me from attending, Jerry W4CAH, provided a grand account of activities. The Digital Slow to Fast Scan converter made its debut in fine style. There were 2 or 3 of these scan converters displayed and although each use slightly different circuitry (recent SSTV Scene articles have briefly described these various units), they all use basically the same

principle; that of converting a Slow Scan picture into a digital equivalent, loading this into memory, then reading it out of memory at a regular Fast Scan rate. Variations were in methods of loading and unloading. I understand the Fast Scan converted pictures were quite outstanding due to their brightness and persistence. The pictures would appear in the familiar "window shade pull down" fashion for SSTV but less the bright initial trace. Further, newly received pictures erased previously displayed pictures completely on the first "sweep," whereas the conventional P7 phosphor monitor usually requires 2 sweeps. For example, if a frame is stopped in the middle, the "top" of the new frame and the "bottom" of the old frame were equally illuminated and equally visible. Also, the last frame received would continue to be displayed on the fast scan monitor until the "erase" mode was energized. Incidentally, the system I have just described (load on the fly technique) was that of Robert W0LMD, who also lectured and distributed descriptive information on his unit. It may be a while before Robert's unit appears in print, as there are other operation expansions planned, and memory IC costs are still prohibitively high (his 65,000 bit memory exhausted *known* surplus sources) for most individuals. However, Robert does have circuit information, descriptions, scope patterns, etc., available for his cost of processing, \$2.50. WA9UHV, has PC boards of the converter designed and built, but not completely tested. Availability is presently unknown, as other modifications may be added to the boards.

Another very interesting item, especially for those of you interested in APT weather satellite picture reception, was the converter unit Ralph WB8DQT, presented. This unit would permit either a scope or SSTV monitor to be used for direct readout of pictures. His unit is straightforward and relatively inexpensive and will probably come out in print very soon. If you really want to try something unusual, don't pass up the satellite idea. (Again, recent SSTV Scene articles had some information.)

Finally, for those of you building magnetically deflected monitors or FSS, I understand Brooks Radio and TV Corp., 487 Columbus Avenue, New York NY 10024, has a fairly large stock of 70° deflection yokes available for approximately \$2 each, and descriptive information is usually included. Possibly this will turn into another good source of SSTV "goodies."

K4TWJ

Six for less than Five!

Six channels at \$199 = \$33.16 per channel

Five channels at \$289 = \$57.80 per channel . . .

(think about it)



2m FM Transceiver

only \$199⁰⁰
(Amateur Net)

SMALL -- 8 7/8 x 1 7/8 x 2 7/8"

SIX CHANNELS! Six crystals are supplied. 94/94, 34/94, 16/76

LIGHT WEIGHT! Only 1 lb. 4 oz.

HIGH POWER -- 2 watts output (draws 15 mA on receive, 410 mA on transmit)

LOW INTERMOD -- operates near transmitters without interference.

accessories

12 Watt Amplifier


Includes steel case to hold the 1402. Plugs into cigarette lighter!

\$99⁰⁰

- Battery Charger, Model 14 BC \$29.95
- Speaker - Mike - SMI \$24.00
- Leather Case for belt - LCL \$12.00


SPEC SHEETS -- write Wilson for complete info on the finest hand transceiver on the market.

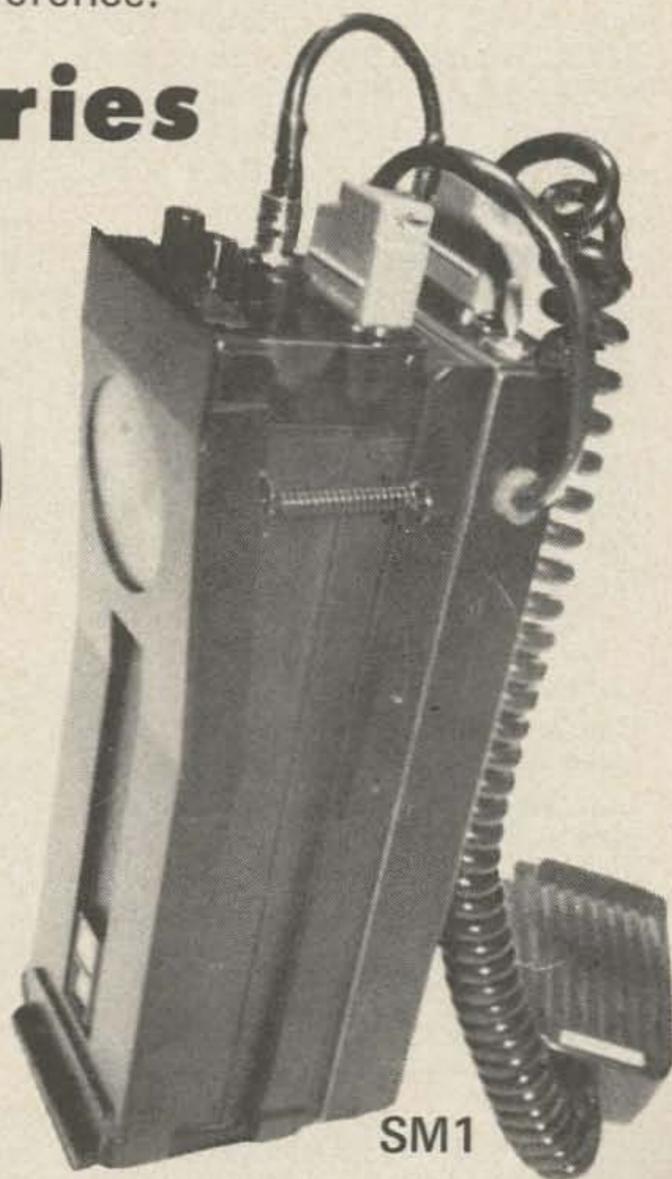DEALERS -- Call us about handling the Wilson Walkie-Talkies (commercial version available too), the Wilson beams, and other products.



WILSON ELECTRONICS

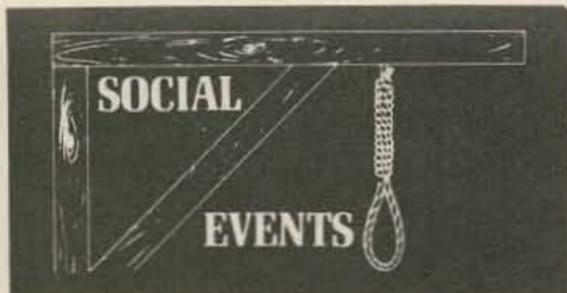Box 794, Henderson NV 89015 (702) 451-5791/6650



TURKEY RUN

The 27th Annual Turkey Run Hamfest and VHF Picnic, sponsored by the Wabash Valley ARA, Inc., will be held Sunday, July 28, at Turkey Run State Park near Rockville, Indiana. Don't miss the Midwest's finest fleamarket. Fun for the whole family: XYL Bingo and fleamarket; food and refreshments, camping facilities, and park recreation for the kids. First Prize: Genave GTX-10, Second Prize: Regency HRT-2, Third Prize: Drake WV-4 VHF Wattmeter; plus many more. Activities begin at 9:00 AM with free coffee and doughnuts. Talk-in 146.94 by W9UUU/9. For details, send SASE to WVARA Hamfest, Box 81, Terre Haute IN 47808.

WARREN 17TH

The 17th Annual Warren Amateur Radio Association Hamfest will be held at the Yankee Lake Amusement Park in Yankee Lake OH, on Sunday, August 18, from 9:00AM-6:00PM EDST. For more information contact: R. Drew Kelley W8GFG, 822 Moore Street, Hubbard OH 44425. Phone: 216-534-3376. Bus. Ph. 216-448-6801, Ext. 393.

HAMILTON - HAMILTON

Q.T.H. - Holiday Inn, Hamilton, Ontario, Canada. Dates - October 25, 26, 27, 1974. There will be eight forums, extensive ladies program, fleamarket, banquet. Everything under one roof. For registration forms write: P.O. Box 836, Burlington, Ontario, Canada.

STRICTLY CINCY

This year the 37th Annual Cincinnati Hamfest will again be sponsored by the Greater Cincinnati Amateur Radio Association and will be held on Sunday, September 15, 1974, at the new Stricker's Grove located on State Route 128, two miles west of Ross (Venice), Ohio, north of Cincinnati. For more information contact: Greater Cincinnati Radio Association, 3965 Harmar Ct., Cincinnati OH.

MONTREAL '74

The 1974 Montreal Hamfest will be held August 4, at the MacDonald College Farm, Ste Anne de Bellevue. Prizes, Giant fleamarket, technical sessions, family fun, \$2.50/adult. For more information contact: VE2RM, Box 201, Pointe Claire-Dorval, Quebec H9R 4N9.

OH! ADRIAN

The Adrian Amateur Radio Club will hold a Hamfest on October 13, 8:00AM - 3:00PM at the Lenawee County Fairgrounds in Adrian MI. Tickets \$1 in advance, \$1.50 at gate. Flea market, trunk sales, large display area - table \$3 - half \$1.50. Ample parking. prize drawing every hour. Grand prize drawing 3:00PM. Talk-in 146.46-.52-.94MHz For more information contact: Adrian Amateur Radio Club, Box 26, Adrian MI 49221.

ANGOLA FEST

The original FM hamfest Sunday August 4, 1974, near Angola, Indiana. Free flea market, entertainment for ladies and kids. Picnic grounds, campsites, boating, food, soft drinks, available, rain or shine. For information contact: Fort Wayne Repeater Assoc., Box 6022, Fort Wayne IN 46806.

20TH VHF

The 20th Annual VHF Conference will be held at Western Michigan University, Kalamazoo MI, on October 19, 1974. There will be Swap 'n Shop, Technical Forums, Evening Dinner, etc. For details please write: VHF Conference, S.M.A.R.S., P.O. Box 934, Battle Creek MI 49016.

GRAND EVENT

The Grand Rapids Swap and Shop will be held Saturday, September 21, 1974 at the Hudsonville Fairgrounds, M-21 at 40th Street, three blocks west of the Hudsonville traffic light. Admission is \$1.75 at the gate, no charge for tables or trunk sales. Talk-in on .16/76 and 146.94. For more information contact: Grand Rapids Amateur Radio Association, Inc., P.O. Box 1333, Grand Rapids MI 49501.

LOUISVILLE BASH!

The 4th Annual Greater Louisville Hamfest will be held at the Oldham County Fairgrounds, LaGrange KY, on Sunday, August 25, 1974, from 8:00 AM until 6:00 PM. For more information contact: Denny Schnurr K4GOU, 1022 Sylvia St., Louisville KY 40217 or telephone 502-634-0619 (home); or 502-774-7549 (work) leave message.

THE L'ANSE CREUSE ARC

The L'anse Creuse Arc will open the fall season for swap 'n shops in the Detroit area on September 22, 1974, EDT 9:00 - 3:00 at L'Anse Creuse Central Jr. High School, main drawing 3:00, 3800 Reimold Rd., Mt. Clemens MI. Free parking, good food, prizes, tables \$1.00. Admission \$1.00. Talk-in on .94; For more information contact: L'anse Creuse Arc, 38024 N. Bonkay Dr., Mt. Clemens MI 48043.

MILWAUKEE FEST (Bastille Day Celebration)

South Milwaukee Amateur Radio Club 4th annual Southeastern Wisconsin Swapfest will be held Saturday, July 14, 1974 at Shepard Park (American Legion Post 434), 9327 South Shepard Avenue, Oak Creek WI. Activities begin at 7:00AM and will run to 5:00PM or later. Parking, picnic area, hot and cold sandwiches and liquid refreshments will be available on the grounds. Admission is \$1.00 and includes a "Happy Hour" with free beverages. Prizes will be awarded. Talk-in on 146.94MHz. More details available from: So. Milwaukee Amateur Radio Club, S.F. Schreiter W9AKF, Secretary, 104 Brookdale Drive, South Milwaukee WI 53172.

INTERNATIONAL HAMFEST

The 11th Annual International Hamfest will be held July 13 and 14, at the Canadian Pavilion in the International Peace Garden between Dunseith ND, and Boissevain, Manitoba. Camping excellent. Party - Contest - Prizes - Meetings. For information contact: Ken Larson K0PVG, 807 Kelly Ave., Devils Lake, ND 58301, or Ron Samchuk VE4SR, 834-9th St., Brandon, Man.

"INDY" 14

(Another Bastille Day Bash)

The Greater Indianapolis Hamfest will be held on Sunday July 14, 1974 at the Marion County Fair grounds on the South East side of Indianapolis at the junction of Interstates 465 and 74. All events including the giant flea market will be under roof. Thirteen area amateur radio clubs combine to bring central Indiana an outstanding convention of technical forums, commercial displays and fellowship. Complete food facilities. Free coffee and donuts in the morning. Gates open at 6:00AM. \$2.00 at the gate entitles the bearer to hourly and main prize drawings. There will be a presale ticket drawing for a Genave transceiver. The main prizes consist of an impressive array of low band and 2m Drake gear. There is a good restaurant on the grounds. Free prizes for the kiddies and a full schedule of women's activities.

UPPER PENINSULA HAMFEST

August 3 & 4, 1974, Negaunee Township Hall, Negaunee MI. Hiawatha Amateur Radio Association host. Registration \$2. Swap n' Shop, Program for XYL's, Door prizes. Mobiles talk in on 3.920 and 146.94. Reservations and info: Frank K4CGQ/8, 322 Fortress, Sawyer AFB MI 49843. 906-346-5501.

MAPLE RIDGE

The Maple Ridge Amateur Radio Club is sponsoring a hamfest in honor of the Centennial of Maple Ridge, British Columbia, Canada, on July 13-14, at the Exhibition Grounds in Maple Ridge B.C. Registration \$2, 12 and under free when accompanied by parents. D.D.C. providing Enforcement Van for frequency checks, and lecture on topical subjects; Swap & Shop, CW, Bingo, 2m Bunny Hunt on 147.33, Ladies program, Kids games, Prizes and more. Talkin on 3.755, 147.33, 146.76 and 34/94. Limited on site camping or trailering. For more information or advanced registration or assistance with accomodations write to Bob Haughton, President M.R.A.R.C., 20623 114 Ave., Maple Ridge, B.C.

WARREN HAMFEST

Largest family style hamfest in the east. Sunday, August 18th at Famous Yankee Lake Park. Giant Fleamarket, swimming, picnicing: all free. Details QSL W8VTD.

"INDY" 14

Greater Indianapolis Hamfest, Sunday, July 14, 1974, rain or shine, Marion County Fairgrounds, all activities under roof. \$2 covers gate fee and prize drawing. For information write: Wm. J. Evans, 8104 Crest Hill Drive, Indianapolis IN 46256.

McKEESPORT SOCIAL

The Two Rivers Amateur Radio Club of McKeesport PA will hold its 10th annual Hamfest on Sunday, July 21, 1974, at the Green Valley Fire Department grounds off the East Pittsburgh-McKeesport Blvd., near U.S. 30. Check in on 29.000MHz. For information contact: Jim Hill WA3FSH, 2500 Banker Street, McKeesport PA 15132.

OKLAHOMA HAM HOLIDAY

The Oklahoma Ham Holiday will be held Saturday and Sunday, August 3 and 4 in Oklahoma City. In addition to the largest fleamarket in the Southwest the program will include special speakers, technical seminars, equipment displays, MARS meetings and unique activities for the XYL. Overnight parking for recreational vehicles is available. For more information and advance registration write Central Oklahoma Radio Amateurs, Inc., P.O. Box 15013, Oklahoma City OK 73115.

ZERO-BEATERS A.R.C. HAMFEST

August 4, 1974, Washington MO City Park. It starts at 10AM CDST, Auction at 11AM. Attendance prizes and other goodies. Auction, free bingo for XYL, cake walk, candy scramble - gigantic traders row. For Hamfest information and tickets write or contact Zero-Beaters ARC, Box 24, Dutzow MO 63342.

FT. WAYNE ORIGINAL

The original FM Hamfest sponsored by the Ft. Wayne Repeater Association WA9EAU, will be held Sunday, August 4, 1974 at the Steuben County 4H Fairgrounds off the Lake James Crooked Lake interchange of I-69 3 miles of Ind. Tool Rd. 80-90. Gate and flea market, open 0600-1600, free coffee & donuts 0600-0800. Admission \$2.00 includes main prize drawing. Children under 12 - free. Talk in - 16/76-94/94.

NINTH SWAPFEST

The ninth annual Northwest Texas Emergency Net Picnic & Swapfest will be held at the City Park in Levelland, Texas on Sunday, August 11, 1974. Bring your own picnic basket. Free registration begins at 0900. Lunch at 1300. Swapping all day. This event is for the entire family. Mobile talk in frequency is the net frequency 3950kHz and 28/88, 34/94 on 2m.

MELBOURNE HERE I COME

The 9th annual Melbourne Hamfest is September 7-8. All air conditioned, \$1.50 at door. Tables \$2/day. PCARS, P.O. Box 1004, Melbourne FL 32901.

GLACIER FEST

On the weekend of July 20 and 21, 1974 the WATERTON GLACIER INTERNATIONAL HAMFEST will be held in the beautiful Waterton Lakes National Park. For more information contact: John A. Fyke VE6AIV.



Bill Pasternak WA2HVK/6
14732 Blythe Street #17
Panorama City CA 91402

I believe it began: "Space, the final frontier." Memorable words from a memorable television program, "Star-Trek." I guess that I am what is known in SF (science fiction) circles as a "trekkie," one who tried never to miss an episode or rerun of that "series" that took one's mind into the future on voyages light years from home. I guess that I was not alone if the reports about ECLICON '74 are what I hear. ECLICON is the yearly convention held in LA where devotees of the world of Star Trek gather much like our "HAMventions." We swap rigs and look at all the new goodies; they

swap stories about what's what in the SF world and browse through the memorabilia of this now almost historic television series. I wanted to attend this year almost as much as I want a new HT220, but neither were possible. Thanks, though, to Pacifica radio station KPKF, a show thereon called "Hour 25" and its host Mr. Mike Hodel, I was there at least in spirit. Through Mike's eyes and voice, I was able to browse a bit while driving my mobile up the San Diego freeway; one of those times when the rig was turned off and the other FM radio was in use.

Well, Star Trek is gone except for the stations that still carry it in syndication. Perhaps it was killed off by the real thing; live television from space and from the moon. And, even more recently, those marvelous pictures sent back to old mother earth by NASA's Mariner Venus/Mercury probe. Amateur radio had its small part in the success of this mission; namely in those hams at the Jet Propulsion Laboratory here in Pasadena and at Boeing Aircraft in Renton WA who were part of the team of scientists, engineers and technicians working the project.

To celebrate the success of this mission, amateurs belonging to the Boeing Employees Amateur Radio Society and the Jet Propulsion Laboratory Radio Club offered a special QSL to any amateur worked by either WS6MVM or WS7MVM respectively. I was one of those lucky ones who worked Warren Andresen WA6JMM, under the WS6MVM callsign via the Mt. Lee Repeater, WR6ABN. So that we VHFers could partake of the festivities Warren supplied both the time and the 2m rig. In the process he handed out to we VHFers a considerable number of these "Special Event" QSLs; a job to which we here in LA thank him and the JPL club for their efforts.

Since we started discussing the media (i.e. television & radio) I would like to put my two cents in at this time about the February 7, "Chopper One." First, why wait till now? Simple, the first time around I did not see the program. I share something in common with that date in that February 7 is my birthday and though I had read the TV Guide blurb on the show, we had other plans for that evening. However, I knew if I waited long enough, ABC would run it again.

I was not to be disappointed. Last Thursday it was repeated and I sat glued in front of my TV watching the plot unfold. I have but one question for ABC and the producers of *Chopper One*. Why with as many hams working for ABC in LA was it not possible to ask one to act as technical advisor for the episode? Now if K6XEG were running a 450 MHz Base Radio, some of us might have believed that he had procured crystals for the Chopper's frequency and as Wayne put it "zapped onto the police radios." I've yet to see a dc Band station that can pull that trick. And that was a neat stunt hearing the bad guys on their CB walkie talkies halfway across town in a city where every 11m channel is 25 layers thick 24 hours a day. My advice to the media is use us, but don't abuse us. If you ask our help in producing something dealing with amateur radio many of us would consider it an honor to participate. But, for heavens sake don't make us out to be demented nitwits and foolish children. If one wants to figure numbers, that little fiasco probably cost ABC some 280,000 amateurs and God knows how many million CB operators as potential future audience. Let's face it, in the ratings game that's quite a hunk of viewership.

Therefore, I take it upon myself to make the following offer to ABC, NBC, CBS or any other LA station planning productions that involve amateur radio. If you need technical advice as to what will look right please contact me. If I cannot help you myself, I will do my best to put you in contact with an amateur; perhaps one working for your station or production company that can fulfill your needs. That particular *Chopper One* episode is a thing of the past and best forgotten by all concerned, but none of us want a repeat of this type of thing somewhere else next season. Well, one good thing, at least the "bad guys" were on the band where they belonged.

The "oops we goofed department" or to err is human to forgive devine. In May we mentioned a repeater in the Stocton area under the call WR6ACB. Well, that was a 3AM typographical error on my part. In a letter from Bill K6ZQ, I learned that my writing that column at that absurd hour had put WR6ACB about 400 miles north of where it belongs in La Habra Heights and on the wrong channel. WR6ACB is a Los Angeles area repeater on 19-79, owned by the Anaheim Amateur Radio Association of which Bill is president, and serves the Orange County area. With my buddy John WA2FMF/6, now a resident of Brea it might just pay to dig

out my 19/79 rocks and put them back in the Sonar 3601 mobile. It's a good hour ride from here in the SF Valley to that area. I will give you the correct call for the Stocton machine next month. In the interum my apologies to both groups.

WA2HVK/6



Tom DiBiase WB8KZD
708 6th Avenue
Steubenville OH 43952

Contest Calendar

July 27-29	CW County Hunter's Contest
Aug. 3-5	Kentucky QSO Party
Aug. 17-18	New Jersey QSO Party
Aug. 17-18	QRP ARC Contest
Sept. 14-16	Pennsylvania QSO Party
Sept. 14-16	Washington State QSO Party
Sept. 28-30	Delta QSO Party

This Month

CW County Hunter's Contest

From 0000Z July 27 to 0600Z July 29. Call CQ CH, exchange QSO number, category (portable or mobile, P or M), RST, State or province or country and county. Stations may be worked once per band and again if a county change was made. Scoring — QSOs with fixed stations are one point, with P or M stations — three points. Multiply points by U.S. counties worked. P&M stations calculate score on basis of total QSOs within a state. Frequencies 3575, 7055, 14070, 21070 and 28070. Appropriate awards. Logs must show category, date/time GMT (UTC), stations worked, exchanges, band, QSO points, location and claimed score. 100 or more QSOs require check sheet (of counties worked). SASE for results. Must be postmarked by September 1, and sent to CW County Hunters Net, c/o Jeffrey P. Bechner W9MSE, 64 North Pioneer Parkway, Fond du Lac WI 54935.

August

New Jersey QSO Party

From 1900Z August 17, to 0600Z August 18. Second period is from 1200 to 2300Z, August 18. Phone and CW are same contest. Stations may be worked once per band/mode. Frequencies — 1810, 3535, 3735, 3905, 7035, 7135, 7265, 14035, 14280, 21100, 21355, 28100, 28600, 50-50.5, 144-146. Exchange QSO number, RST and QTH (ARRL section or country). New Jersey stations send county. Multiply total QSO

points by total different QTHs worked. New Jersey stations score one point for W-VE QSOs, three points per DX QSO. Non-New Jersey score one point per New Jersey QSO. (For New Jersey, the KP4, KH6, KL7, KZ5 count both as DX and ARRL sections (4 points). Appropriate awards. Logs should include GMT (UTC) date/time, band, mode, and must be received no later than September 14. The first QSO for each claimed multiplier must be numbered and check list of QSOs and multipliers should be attached. Multi-operating stations include all calls of participating operators. Comments welcome. Send to Englewood ARA, Inc., 303 Tenafly Road, Englewood NJ 07631. #10 SASE for results. Stations planning active participation in New Jersey are requested to advise EARA by August 3, so they can plan for full coverage from all counties. Portable/mobile operation encouraged.

WB8KZD

J.O.T.A. '74

The 17th Annual Jamboree-on-the-Air, will be held October 19-20. Suggested starting time is 0001 hours LOCAL TIME on Saturday, October 19, and terminating 48 hours later, i.e., at 2359 hours LOCAL TIME on Sunday, October 20. Note that these are only suggested times, if it is more convenient for your stations to operate on the Friday evening, then you are perfectly free to do so.

HAM HELP

This column is for those needing help in obtaining their amateur radio license.

If you are interested, send 73 your name, address and phone number. Don't be bashful — remember, it's always easier when you have someone to give you that added bit of confidence.

73 would appreciate amateurs and clubs looking this list over and helping whoever they can. Do you remember when you needed help?

Aaron Jackson Jr.
P.O. Box 123
Clinton NC 28328

James D. Guy K7UAN
5818 S. 21st Dr.
Phoenix AZ 85040

Robert Bryan
P.O. Box 71
Cockeysville MD 21030
Telephone: 301-666-8453

Bishop L. Ellison
P. O. Box 631
West Branch IA 52358



DYCOMM SUPER "D"*

Some months back, Dycomm ran a full page ad in several of the ham journals advertising a special "while they last" kit offer for their Super "D" amplifiers at an amazing low price of \$49.95, which is less than the commercial price of the transistors supposedly used in the device alone. Apparently Dycomm had a goodly supply of these units stashed away, for the price was recently raised to \$59.95 and they are still being offered. Dan WA1EYX, got one of these units, and I hoped for a chance to see it, and evaluate what appeared to be one of the better deals in a long time. The opportunity soon came, for shortly after completing the kit, Dan was having troubles in tuning it up, and we both set it up on the bench for a few measurements.

Technically, the amplifier is self-contained, requiring only 13.6 VDC and rf drive to operate. It is automatically switched into the line when it senses rf, and does not need an external keying line. Two transistors are used in a parallel arrangement. The transistors supplied were unmarked and manufactured by Dycomm. They were supposedly equivalent to the excellent Motorola 2N6084 types which are each rated at 40 watts out and have ballasted emitters for infinite VSWR protection. All parts, including a nice glass epoxy board were supplied with the kit. This unit has no low pass filter after the amplifier stage, an obvious shortcoming since with typical low-Q circuits used in the low-impedance high-current output network, harmonic content is probably no better than 25 dB down referenced to the carrier. This amp will be best used if installed in a fast mobile with an inconspicuous antenna.

Several other design shortcomings were evident. With more than 20 watts of drive, the ferrite beads used in the DC return chokes for the transistor base biasing saturated, overheated and smoked. The ordinary dipped silver-mica capacitors were originally used in series with the inductors feeding the extremely low input impedance of the transistors; these high rf currents caused dielectric heating of the capacitors, resulting in continual shift in tuning and eventual breakdown. The diode supplied to sense rf turned out to be a silicon power type and would not detect two meter rf energy; this had to be changed. The relay used for rf switching is an open frame type, and is

apparently quite reactive at 146 MHz. Dycomm uses a series capacitor on the rf output circuit to tune out the reactance, but we were unable to obtain less than a 2 to 1 SWR between the exciter and amplifier. When operating straight through the amplifier, the relay is still in the circuit, and the capacitor must be re-tuned to obtain reasonable SWR.

Dycomm claims over 80 watts out with 30 watts drive, and 70 watts out with 20 watts in as being "typical" figures. Using two Bird 43 Wattmeters, our figures showed 50 watts out with 30 watts in. The heatsink used is minimal, and short transmissions must be the rule. We were unable to make further evaluations due to the failure of one of the output transistors, and sent the unit back to Dycomm along with their fifteen

dollar "we'll fix it for ya" fee, and a letter describing the problems. It came back with better caps and new transistors, and was now putting out 60 watts with 30 in, still below advertised claims. After one week of mobile operation, it is again out of service with defective transistors.

We must give this amplifier an unfavorable report; this is regrettable for it had the makings of a real good deal. Perhaps these design and manufacturing flaws were caused by component substitutions at Dycomm in order to meet demand, and if the problems are resolved we will report it in a future issue of INTERMOD. We understand several others have had experiences closely in line with ours with their "Super Dud" also.

Reprinted from Intermod.

John K1ZJH

NEW CDR ROTOR



The new CDR Ham-II antenna rotating system has an important advantage over the older Ham M units in that the new control unit has a separate switch for operating the brake.

The inertia of larger antenna systems is a force that has to be considered. The sudden stopping of the brake action on the Ham-M units put severe stresses on the rotors, the towers, the tower guys, the antennas themselves.

Something has to give eventually when repeated stresses like this are present. The new control unit permits the antenna to be turned and allowed to coast to a stop rather than slammed to a halt, whipping the tower and beam around.

The amateur net price of the complete Ham-II system is \$150, with the control unit being available separately for about \$80 — and it will work with any of the Ham-M rotors.

SAVE THAT RIG

The life expectancy of a good ham mobile rig left unattended in a car on the streets of New York is about 20 minutes. In Chicago it is about 40 minutes — and almost an hour in Boston, on the average. It is prudent to make every effort to protect your investment, not only with some sort of alarm system, but with the best locking device you can get — something that will keep the rig in the car even if a burglar manages to get into it — and they can manage.

Keeps-It Kit has a new bracket for your rig — a tamper-proof one. Normal tools such as screwdrivers, vise

grips, allen wrenches, etc., are ineffective against the mighty grip of the Keeps-It. Models are available for the SBE, the Regency, and the Genave so far — with more to come. The price is only \$16.

Before you take this lightly, call your insurance agent and see if you are insured against the loss of your mobile rig — and to what extent — and how about the second and third theft? Lordy, they even rip the rigs out in parking garages these days.

Details on Keeps-It Kit are available from *Jim Wallace K5SOY, Box 13249, Ft. Worth TX 76118.*


repeater update

Revision of Recently Published Repeater Atlas

AL	WR4AEJ	Birmingham	6.28-6.88	GA	WR4AED	Stone Mt.	6.16-6.76	NM	WR5ACM	Mt. Taylor	6.34-6.94
AL	W4MWF	Montgomery	DELETE		(Formerly: W4BOC)				(Formerly: WA5JDZ)		
AL	WR4AGA	Mt. Cheaha	6.10-6.70	HI	KH6EQF	Honolulu	6.28-6.88	NM	WR5ACE	San Antonio Mt.	6.16-6.76
AL	WR4AGN	Opelika	6.34-6.94				449.15-444.15	NM	WA5VKY	Sandia Crest	6.13-7.06
	(Formerly: W4ZBA)		W1.8 52.760-52.525	HI	KH6EQR	Lualualei	DELETE	NY	WB2GDF	Brooklyn (CLOSED)	7.96-7.36
AL	WR4AEH	Tuscaloosa	6.22-6.82	HI	WR6ACL	Waikiki	6.16-6.76	NY	WR2ABH	Dick's Hills (CLOSED)	7.90-7.30
AZ	WR7ACK	Sierra Vista	6.16-6.76		(Formerly: KH6FOX)			NY	WR2ABL	Elmira	6.10-6.70
	(Formerly: WA7KYT)			IL	KH6NLH	Waipahu	DELETE	NY	W2AWG	Flushing	DELETE
AR	WR7ACT	Eagle River	6.10-6.70	IL	WR9ACE	Aurora	CLOSED	NY	WR2ACK	Gloversville	6.10-6.70
			6.16-6.76	IL	WR9ABY	Chicago	6.16-6.76	NY	WR2AAA	Manhattan	7.73-6.73
			449.2-444.2				448.75-443.75	NY	WR2ACV	Manhattan	7.43-6.43
AR	WR5ADI	Little Rock	6.34-6.94		(Formerly: WA90RC)			NY	WR2ACU	Rochester	6.07-6.67
	(Formerly: W5DI)			IL	WR9AOZ	Chicago PL	7.15-7.45	NY	WR2ADG	Rochester	449.25-444.25
CA	W6IWI	Canoga Park	7.66-7.06	IL	WA9WJG	Danville	DELETE	NY	WR2ABO	Rome	7.78-7.18
CA	WR6AAA	Catalina Island	7.69-7.09	IL	WR9AAA	Joliet	6.22-6.82	NY	WR2ADN	Saratoga	6.40-7.00
	(No PL)				(Formerly: WA9EAT)			NC		Asheville	6.31-6.91
CA	WR6ACJ	Crestline	6.25-6.85	IL	WR9AAD	Murphysboro	6.25-6.85	NC	WR4AGF	Asheville	6.22-6.82
	(Erroneously listed as WR6ACI)			IL		Springfield	6.28-6.88		(Formerly: WA4NUO)		
CA	WA6LNU	Los Angeles (AM)	222.20-223.00	IL	WA9WVB	Urbana	T2.25 6.34-6.76	NC		Burlington	6.07-6.67
CA	WA6NTW	Los Angeles	222.34-223.94	IN	WA9EAU	Ft. Wayne	6.16-6.76	NC	W4NBR	Goldsboro/Kingston	DELETE
CA	WR6ABI	Los Angeles PL	7.60-7.00				6.31-6.91	NC	WR4AFV	High Point	6.19-6.79
	(Hollywood Hills)		223.26-224.86	IN	WR9ABN	Ft. Wayne	6.28-6.88	OH	WR8ABT	Cheviot	DELETE
CA	W6NWX	Orange Co.	6.13-6.73	IN	WB9FHD	Freemont	DELETE	OH		Cincinnati	6.16-6.76
	(Mt. Palomar)			IN	WB9RAI	Indianapolis	DELETE	OH		Cincinnati RTTY	7.69-7.09
	(Erroneously listed as W6NQG)			IN	WR9ACU	Indianapolis	6.28-6.88	OH		Cincinnati	7.75-7.15
CA	WR6ADR/6	San Bruno Mt.	7.90-7.30	IN	WR9ACZ	Lafayette	6.16-6.76	OH	WR8ABT	Cincinnati	6.07-6.37
CA	WA6ILA	San Joaquin	DELETE		(Formerly: W9EJV)			OH		(Formerly: K8SCH)	
CA	WR6ACM	Vacaville	6.55-7.57	IN	WR9ACX	Marion	6.19-6.79	OH	WR8ACB	Cincinnati	6.115-6.70
			52.760-52.525	IN	WR9ABO	Muncie	6.13-6.73	OH		(Formerly: WB8NON)	
			449.85-444.85	IN	WR9ABO	Pittsburg	DELETE	OH	WR8ACC	Cincinnati	7.99-7.39
	(Formerly: WB6WYI)			IN		Wabash Valley	6.25-6.85	OH		Cleveland	6.25-6.85
CO	WA8BAG	Colorado Springs	DELETE	KY	W4YWH	Covington	6.13-6.73	OH	WR8ABD	Cleveland	6.34-6.94
CO	WA8VTV	Colorado Springs	6.16-6.76				6.19-6.79	OH		(Formerly: K8MMM)	
CO	WA8NVU	Denver	444.90-449.90	KY	WR4AEM	Independence	7.86-7.26	OH	WB8CRP	Cleveland	6.22-6.82
CO	W8TX	Denver	444.35-449.35	KY	WB4RYX	Louisville		OH		(Formerly: W8TTO)	
	(Formerly: WA8VVC)			LA	W5MCC	New Orleans	T1.8 6.16-6.76	ON	WR8ACR	Cleveland	6.13-6.73
CO	WR8ABB		444.45-449.45		(Formerly: W5UK)		6.34-6.94	ON	WR8ABV	Columbus	6.16-6.76
CT	WR1ACZ	Norwalk	7.99-7.39	LA	WR5ADB	Rayville	6.16-6.76	ON		(Formerly: W8WTB)	
CT	WR1ABC	Torrington	223.06-224.66		(Erroneously listed as Bayville)			ON	WR8ACZ	Dayton	442.85-447.85
DE	WR3ABA	Wilmington	6.13-6.73	LA	WR5ACV	Shreveport	6.16-6.76	OH	WA8GEC	Fairfield	6.13-6.73
	(Formerly: WA3FRH)			LA	WR5ACV	Shreveport	6.16-6.76	OH	WB8ABW	Galion	6.25-6.85
DE	WR3ACV	Wilmington	7.75-7.15	MD	W3EHT	Baltimore	DELETE	OH		(Formerly: K8ZES)	
FL	WR4ACV	Boca Raton	6.22-6.82	MA	WR1ACP	Agawam	6.40-7.00	OH	WR8ACW	Lima	6.34-6.94
			6.34-6.94		(Formerly: WA1HDS)			OH	WR8ACQ	Mansfield	6.34-6.94
	(Formerly: WB4KVV)			MA	WR1ACB	Bellingham	7.66-7.06	OH	WR8ABM	Marietta	6.28-6.88
FL	W4LRH	Ft. Myers	6.28-6.88	MA	WR1ADF	Bridgewater	7.78-7.18	OH		(Formerly: W8HH)	
FL	WR4AAF	Jacksonville	6.16-6.76	MA	W1ACM	Stoughton	6.775-6.175	OH	K8PWL	Miamisburg	DELETE
			52.760-52.640	MI	WA8BDD	Clarkston	6.25-6.85	OH	WR8ABS	Middletown	6.01-6.61
	(Formerly: WB4QFL)			MI		Detroit RTTY	6.22-6.82	OH		(Formerly: WB8ATD)	
FL	WR4AEG	Melbourne	413.8-448.8	MI	WR8ABN	Detroit	449.00-444.00	OH	WR8ABX	Newark	6.28-6.88
FL	WB4KBG	Melbourne	6.25-6.85		(Formerly: WB8CRK)			OH	WB8CQO	Toledo	DELETE
FL	WR4API	Merritt Island	6.28-6.88	MI	WA8PUD	Grand Rapids	DELETE	OH	WR8ACT	Toledo	6.19-6.79
			6.34-6.88	MI	WR8ACN	Grand Rapids	T2.25 6.16-6.76	OH		(Formerly: K8ALB)	
	(Formerly: WB4KNQ)			MI		Howell	7.63-7.63	OH	WR8ADC	Toledo	6.01-6.61
FL	W4MKD	Miami	CLOSED	MI	WB8CSU	Jackson	DELETE	OH		Troy	DELETE
FL	WR4AFO	Orlando	6.16-6.76	MI	WB8CQM	Lansing	6.22-6.82	OH	WR8ACX	Warren	6.37-6.97
			6.34-6.76				6.34-6.94	OH	W8100	Youngstown	DELETE
	(Formerly: WB4QEL)			MI	WB8CRQ	Manistee	6.19-6.79	OK	WR5ADE	Oklahoma City	6.34-6.94
FL	WR4AEQ	Orlando	6.58-7.18	MI	WR8AAA	Milford	6.19-6.79		(Formerly: WA5YTI)		
			7.78-7.18	MI	WR8ACS	Rochester		OK	WR5ADF	Oklahoma City	6.06-6.67
FL	WB4QER	Panama City	6.10-6.70	MI		Tawas	6.34-6.94	PA	WR3ABC	Allentown	6.34-6.94
FL	WR4ADL	Pensacola	6.07-6.67	MI	W8FGB	Trenary	6.16-6.76		(Formerly: W3OI)		
FL	WB4KNS	St. Petersburg	CLOSED	MS	WR5ADC	Gautier	6.28-6.88	PA	WR3ACD	Churchville	6.40-7.00
	(Formerly: WB4IES)				(Formerly: WA5RMS)						222.98-224.58
FL	WB4AFJ	Tampa	CLOSED	MO	WR8ABW	Kansas City	448.10-449.10	PA	K3ZTP	Coatsville	DELETE
GA	WR4ABJ	Athens	6.13-6.73		(Formerly: K8OKI)			PA	WA3KXD	Erie	DELETE
GA	WB4NST	Atlanta	DELETE	MT	W7YB	Bozeman	6.28-6.88	PA	WR3ACO	Harrisburg	6.16-6.76
GA	WR4ABI	Atlanta PL 103.5	6.04-6.64	NE	WR8ACD	Beaver Crossing	6.16-6.76	PA	WR3ACS	Johnstown	6.34-6.94
GA	WR4ADB	Atlanta	444.50-449.50		(Formerly: WA8VWD)			PA	WR3AAB	Lehigh Valley	6.10-6.70
	(Formerly: WB4QGF)			NE	K8YRL	Lincoln	6.34-6.94	PA		(Formerly: W3OK)	
GA	WR4AED	Atlanta	6.16-6.76	NJ	WR2ABJ	Cedar Grove	7.78-7.18	PA	WA4BJS	Pittsburgh	6.16-6.76
	(Formerly: WB4WST)										
GA	WR4AEW	Atlanta	7.96-7.36	NJ	WR2ADV	Paramus PL 141.3	6.19-6.79	PA	WA4BJS	Pittsburgh	DELETE
	(Sandy Springs)				(Formerly: WA2UWR)		443.1-448.1	PA	WR3ACH	Pittsburgh	6.22-6.82
GA	WR4AFC	Atlanta	6.01-6.61					PA	W3QV	Philadelphia	7.63-7.03
GA	WR4AFR	Atlanta	7.66-7.06	NJ	K2GCL	Waldwick	DELETE				29.640-29.493
GA	WR4AGD	Augusta	6.34-6.94	NM	WA5QLZ	Albuquerque	DELETE				
			7.90-7.30	NM	WR5ACX	Albuquerque	6.10-6.70				
	(Formerly: WB4KLM)			NM	WR5ABV	El Capitan	6.34-6.94				
GA	K4DVJ	Dallas	6.25-6.85		(Formerly: WA5DMQ)						
GA	WR4AEK	Gainesville	6.07-6.37	NM	WR5ABU	Los Alamos	6.28-6.88				
	(Walka Mt.)				(Formerly: W5PDO)						
GA	WB4CNC	Griffin	DELETE								
GA	WR4AEA	Griffith	6.43-7.43								
GA	W4RRW	Smyrna	DELETE								


MORE NEXT MONTH

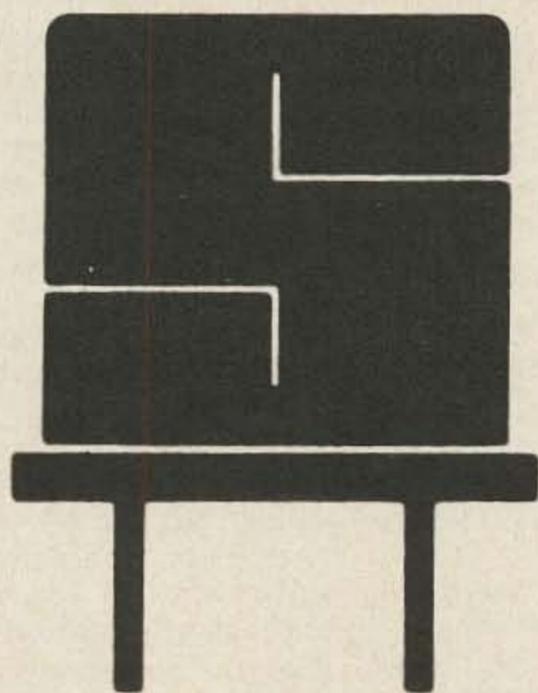Send any and all corrections, updates or new listings to 73 Magazine, Peterborough NH 03458.




REPEATER OWNERS

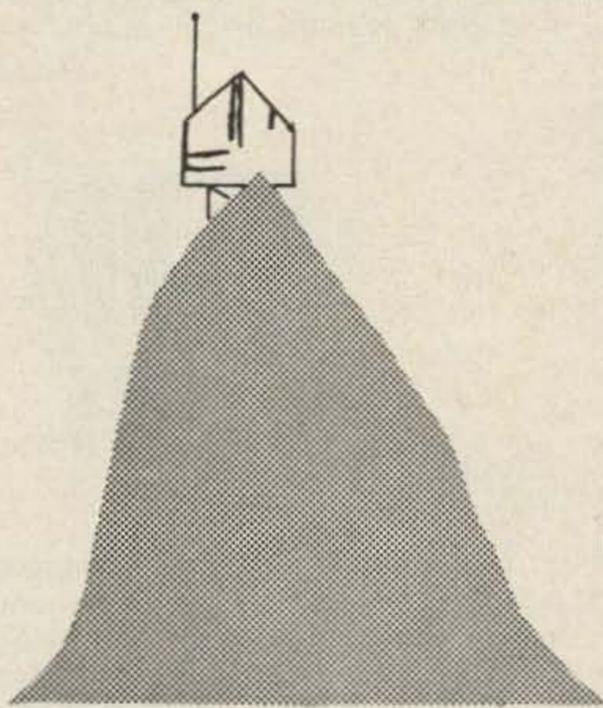Don't Take Chances. SENTRY offers custom made crystals made exactly to your specifications. When it comes to crystals for your repeater, BUY THE BEST - SENTRY.



REPEATER USERS

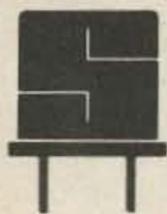If you want reliable access to the repeaters in your area, you want and need SENTRY CRYSTALS. SENTRY CRYSTALS are custom made for your rig. We don't stock a large quantity of crystals for a certain frequency and hope you can tweak them to frequency in your rig. We do offer FAST service on crystals made especially for you and your rig. If you want reliable, on-frequency operation, INSIST ON SENTRY.



SENTRY MANUFACTURING COMPANY
Crystal Park, Chickasha, Oklahoma 73018

PHONE: (405) 224-6780

TWX-910-830-6425



Joe Kasser G3ZCZ
1701 East West Highway, Apt. 205
Silver Spring MD 20910

For a country at war, everything appears to be normal. There are one or two minor differences noticeable from peacetime, such as a lack of young men in the streets and no ham operation. The lack of ham operation does not seem to be by government decree, but because all the operators are away in the desert on active service.

The country that I am writing about is Israel, better known as 4X or 4Z. It is an ideal location for ham operation, since it lies right where Europe, Asia and Africa all come together. It is thus possible to work three continents and over sixty countries without any effort at all on the HF bands. The VHF bands also have extremely good propagation conditions particularly in the summer. Evidence of this is clearly demonstrated by the multitude of TV antennas sprouting from nearly every rooftop in sight. TV reception in Haifa and Tel Aviv is such that viewable pictures can be seen from Cyprus, Lebanon, Syria, Jordan and Egypt.

Most of the locals, hams or otherwise, speak some English and they are all very friendly. For those of you who would like to work into 4X without or before going there try listening on or around 21360 MHz after 1600Z. That is the time that I have been able to get through from Washington DC.

If you are like me when mobile with a TR-22 you will have to keep changing crystals when mobile in different parts of the country. I usually talk myself on frequency with the help of one of the locals using the copper bronze clip that holds the plastic cover in place to warp the frequency. WB4JFI who writes the ATV column has a neat modification for putting 12 channels in the TR-22. He uses a switch and strip of crystal sockets obtained from Lafayette CB rig spares. I'll write some more after I've put it in my rig.

There seems to be more and more QRP rigs on the HF bands now. These rigs are ideal for the traveling ham. I worked a DX station the other day on 15, he was using an Argonaut transceiver and a 3 element beam. I worked a number of Europeans that day and

his signal sounded just as good as the others. I even heard him in there calling through the others. QRP can do good things for the traveling ham.

If you are going to use QRP it is very important that you also use an efficient antenna such as a matched long wire or a dipole or a beam. Read some of the published material on QRP operation and see what the "pro's" use. You never know, you may end up using QRP at the home station. In fact while I am writing this I am also calling CQ on 80m RTTY using 8W output as indicated on my Heath HM-102 Power Meter. I haven't worked anyone yet but I'm hopeful.

Still for those of you who want to use big rigs, take care when you plug in the line cord, because the rest of the world does not necessarily use 60Hz/110VAC lines. In fact more countries use 50 Hz/220V lines than 60/110V. I've found that a shaver transformer is an ideal device for interfacing my TR-22 to 220V lines for recharging.

Next month I'll present a list of line voltages and frequencies for the most commonly visited countries of the world. Until then keep those letters coming, for its only by such reader/writer feedback that I can determine if anyone actually reads this column.

G3ZCZ



Terry Fox WB4JFI
3612 Barcroft View #302
Baileys Crossroads VA 22041

This month I would like to bring up a few questions to all ATVers, and they have to do with that now familiar word: standardization. I feel that it would be very advantageous to our particular mode if we could standardize frequencies and antenna polarization wherever possible. If all of us were on the same frequencies with the same polarization, new hams wouldn't have to worry about what's in use in their particular area, and ATV DX would be feasible. Some people may not like this idea at first, but I know how frustrating it can be to look night after night after night for some ATV activity, only to lose interest simply because of too many variables. Having to move the antenna is bad enough, but when tuning a converter and worrying about polarization are thrown in, well, you need a lot more patience than most of us have. So let's get right down to the meat of the matter.

First of all there is antenna polarization. If we standardize on this and I hope we do, will it be vertical, horizontal or circular? I think that we can drop circular right away, because it's harder to build, not commercially available, and not in widespread use today. So now it's down to horizontal or vertical. Let's start by asking a few questions. Which, if either, has more gain under the same conditions? Which is cheaper and easier to build or buy? Does vertical or horizontal have the most overall advantages? I will have to admit right now that I am biased toward vertical polarization because of my own answers to the above questions.

As far as which works better under identical circumstances, rumor has it that above 300MHz neither out performs the other. I have heard of tests conducted by a branch of the military that showed this, but I haven't seen the results myself yet so I may be wrong. If anyone does have info on this I would appreciate it if they could send me a copy.

From which is easier to get gain? This turns out to be kind of a tricky question. If you're talking about directional gain, it's just as easy in either plane. Most antennas that are available will work both ways, you just have to rotate it 90 degrees if you're not right. The stickler is omni-directional gain. The repeater is what really prompts this question, although omni-directional gain is also advantageous for roundtables, nets and mobile operation. There are many, many vertically polarized antennas with gain on the market today, mostly because of the FM boom. Horizontal antennas are not only harder to make with gain and omni-directional coverage, they are also much harder to find commercially. That has also answered my question regarding price and availability. Another advantage is that commercial television runs horizontal polarization, so if we went vertical, the chances of TVI would be reduced. In case you're wondering why all the fuss about this, 450MHz isn't like 40 meters where often the difference in using cross-polarization isn't too noticeable. At UHF the difference can be as much as 20dB, or more. That is a lot to make up elsewhere.

I think that says what I feel about polarization, now I would like to hear from you, pro or con, because you are where it counts.

I'm sure this is a very touchy subject to some people, but as I mentioned earlier, it would help us and others getting interested in the long run, particularly if it is done now, before the 450 band gets as busy as 2 meters. Also, again I have my own feelings, which I'll bring up.

When we were first discussing putting up WR4AAG, we had a talk with our area frequency coordinator (he was set up as a mediator because of local 2 meter foul ups), and he told us that two frequencies had been sort of set aside all along the east coast for ATV. They are 439.25 and 427.25MHz. Since there wasn't any local ATV activity, we told him that we were going to try to put up a repeater on them. As it turns out, those are the best frequencies we could have gotten. Between 420 and about 425 MHz, there is some AM and CW activity, around 432 to 435 is some moonbounce and satellite work, and above 445 MHz is mostly FM, so we really lucked out, and got out of everyone's hair.

WB4JFI

NEW ENGLAND REPEATERS

-as of June 1, 1974

146.49	WR1AAF ¹	CT	Oxford
146.61	WR1AAH	MA	Marlboro
	WR1ABT	CT	New Haven
146.64	WR1ABV	MA	Waltham
	WR1ADK	CT	Hartford
146.665	WR1ABR	CT	Stamford
146.67	WR1AAI	MA	Boston
	WR1ABD	CT	Groton
146.70	WR1ACW	RI	Providence
	W1MTV	MA	Westfield
146.73	WA1KHC	MA	Mt. Lincoln
	WA1KGP	ME	Sanford
146.745	WR1ACR	MA	Somerville
146.76	WR1ACA	VT	Ascutney
	WR1ACE	RI	Lincoln
	WR1ADB	MA	Fall River
146.775	W1ACM	MA	Stoughton
146.79	WR1ACO	MA	Malden
	WR1ABI	MA	Fall River
	WR1ADJ	CT	Vernon
146.82	WR1ABA	CT	Simsbury
	WR1ABJ	MA	Weston
146.835	WR1ACD	CT	Monroe
146.85	WR1ABQ	NH	Derry
	WR1ADL	CT	Torrington
146.88	WR1AAC	MA	Salem
	WR1ABM	CT	Avon
	W1ABI	VT	Killington
	WR1ABG	MA	Webster
	WR1ACJ	RI	Providence
	WA1KGZ	ME	Buckfield
146.895	WR1ABE	CT	Bridgeport
146.91	K1FFK	MA	Greylock
	WR1AAA	MA	Malden
146.94	WR1ABU	NH	Concord
	WR1ABX	MA	Holyoke
	WR1ACI	ME	Bangor
	W1KOO	VT	Mansfield
	WR1ADD	RI	Providence
146.97	WR1ABF	NH	Salem
	WR1ABO	MA	Worcester
	WA1KGB	CT	Farmington
146.99	W1UQ	MA	Boston

147.00	WR1ACP	MA	Agawam
	WR1ACQ	NH	Deerfield
147.03	W1QFD ²	MA	Marlboro
	WA1KFZ ³	MA	N, Adams
147.06	WR1ACB	MA	Bellingham
	WR1ACN	NH	Londonderry
147.075	WR1ACU	MA	Reading
147.09	WR1ABN	MA	Walpole
	WR1ACY ⁴	CT	Glastonbury
147.12	WR1ABP	MA	Maynard
	WR1ADN	CT	Fairfield
147.15	WR1ABB	MA	Framingham
147.165	WR1ACL	NH	Salem
147.18	WR1ADF	MA	Bridgewater
	WR1ADM	CT	Naugatuck
147.21	DL2AA/WR1	MA	Medway
147.27	None		
147.30	WR1ACT	MA	Scituate
147.33	None		
147.36	WR1ACH	MA	Newton
	WR1AAD	CT	Canton
147.39	WR1ACC	MA	Oxford
	WR1ACZ	CT	Norwalk
147.42	WR1ADC ³	MA	Somerset
	1. 147.49 input		
	2. 147.87 input		
	3. 146.43 input		
	4. 145.47 input		

All input frequencies are 600 kHz (0.6 MHz) below the output channels listed here from 147.03 to 147.39 MHz. I.E., you transmit on 146.01 MHz to use a repeater you can hear on 146.61 MHz.



FCC NEWS

Adopted: April 2, 1974
Released: April 4, 1974

1. Because of recently adopted changes in the Table of Frequency Allocations in Part 2 of the Commission's Rules certain variances exist between the information contained in the Table of Frequency Allocations in Part 2 and the Authorized Frequency list, Section 97.61, of the Amateur Radio Service Rules.
2. This Order is issued to conform the information in Part 97 with the information contained in Part 2 relating to frequency allocations.
3. Because this amendment relates to editorial revisions to effect consistency among the Commission's Rule parts, prior notice of rule making public procedure and effective date

provisions are unnecessary, pursuant to the Administrative Procedure and Judicial Review provisions of 5 U.S.C. 553.

4. Accordingly, IT IS ORDERED, pursuant to Sections 4(i), 5(d) and 303 of the Communications Act of 1934, as amended and Section 0.231(d) of the Commission's Rules and Regulations, that effective April 16, 1974, Section 97.61 of the Commission's Rules is amended as set forth in the attached Appendix.

Frequency band	Emissions	Limitations
kHz		
1800-2000	A1, A3	1, 2
3500-4000	A1	
3500-3775	F1	
3775-3890	A5, F5	
3775-4000	A3, F3	4
7000-7300	A1	3, 4
7000-7150	F1	3, 4
7075-7100	A3, F3	11
7150-7225	A5, F5	3, 4
7150-7300	A3, F3	3, 4
14000-14350	A1	
14000-14200	F1	
14200-14275	A5, F5	
14200-14350	A3, F3	
MHz		
21.000-21.450	A1	
21.000-21.250	F1	
21.250-21.350	A5, F5	
21.250-21.450	A3, F3	
28.000-29.700	A1	
28.000-28.500	F1	
28.500-29.700	A3, F3, A5, F5	
50.0-54.0	A1	
50.1-54.0	A2, A3, A4, A5, F1, F3, F5	
51.0-54.0	A0	
144-148	A1	
144.1-148.0	A0, A2, A3, A4, A5, F0, F1, F2, F3, F5	
220-255	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5	5, 6
420-450	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5	5, 7
1215-1300	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5	5
2300-2450	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	5, 8
3300-3500	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	5, 12
5650-5925	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	5, 9
GHZ		
10.000-10.500	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5	5
24.000-24.250	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	5, 10
48.000-50.000	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	
71.000-84.000	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	
152.00-170.00	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	
200.00-220.00	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	
240.00-250.00	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	
Above 275.00	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	

ou goons don't ever proof
loasy men... from bab
bunch of trooks pre... in
you ignored my... in
I insist that you print ev

LETTERS

Dear Counsel:

In a recent column, you said tax rebels are "thoroughly convinced" that the federal income tax is unconstitutional. Is there any basis for this conviction?

Yes. Perhaps the strongest support is found in an article published in the December, 1972 issue of the American Bar Association Journal. It forcefully indicates that the present internal revenue code is so discriminatory as to violate the uniformity principles of the U.S. constitution.

I urge you to read this article. It was written by a top-rated lawyer, William G. Halby, formerly the tax partner in a very substantial law firm, now with Equitable Life in New York City. His analysis merits careful study by every American.

The 16th amendment to the constitution permitted congress to tax "incomes, from whatever source derived," without apportionment among the states. Still, any income tax law must be uniform, and must not deprive people of their property without due process.

The present federal income tax was enacted in 1913. In 1916, the U.S. Supreme Court held that it did not violate the uniformity and due process requirements of the constitution. But the present code bears little resemblance to the 1913 law, and judicial views have changed a lot in the last 58 years.

By implication, the Pennsylvania Supreme Court in 1971 said the present federal income tax is unconstitutional. The state had enacted an income tax law that adopted federal "taxable income" as its standard. Federal taxable income is the figure a taxpayer arrives at after taking exemptions, credits, deductions and other preferences to which he's entitled. It's line 48 of the 1973 form 1040 return.

This Pennsylvania law was challenged quickly. In a 1971 decision, *Tilghman v. Kane*, the Pennsylvania Supreme Court held that it violated the uniformity clause of the Pennsylvania constitution. Why? Because it used "federal taxable income" as its standard.

The court found that Pennsylvania, by adopting this federal standard, created widespread tax preferences. Taxpayers with the same amounts of income were required to pay different amounts of taxes, depending on whether they were wage earners, in-

vestors, home owners, tenants, or something else. Result: "Unequal burdens" were imposed "in violation of the uniformity clause" of the Pennsylvania constitution.

So what? Does the Pennsylvania uniformity clause mean the same thing as the uniformity provision of the federal constitution? The Pennsylvania Supreme Court said "yes" in *Pennsylvania v. Girard Life Insurance Company*, a 1932 decision.

In this case, the court found that the Pennsylvania uniformity clause, as applied to tax matters, was parallel in meaning with the equal protection and due process clauses of the federal constitution. What would violate one generally would violate the other, the court said.

So, if the Pennsylvania Supreme Court were to pass on the federal income tax today, in all probability it would find the law unconstitutional. And if the question were squarely presented, the U.S. Supreme Court easily could reach the same conclusion.

Unfortunately, congress and treasury officials have muffed the Tilghman message, just as they have turned deaf ears to other solemn warnings of a coast-to-coast taxpayers' revolt. Time is running out. Let's shelve Watergate and get on with fundamental tax reform, before it's too late to head off impending disaster.

E. Edward Stephens
815 King St. 3rd Floor
Alexandria VA 22314
(703) 683-3900

WHY I HATE WAYNE GREEN

1. I suppose I hate Wayne Green mostly because he *thinks*. He thinks that a QSO should consist of more than just an exchange of signal reports, names, QTH's and type of equipment. He thinks that amateurs should do more than just try to see how many countries, counties, states, or whatever, they can work. He thinks that amateur radio is more than just a hobby, and that an amateur license imposes special responsibilities such as public service, making contributions to the advancement of the state-of-the-art, and spreading international goodwill.

2. I hate Wayne Green because he thinks that, even in these days of

Watergate, there should be a sense of morality in our government. After all, what is so wrong for the FCC to take away 2MHz of the amateur 220 band just so the EIA can sell more radio equipment?

3. I hate Wayne Green because he refuses to be humbled by the dictates of the State. He thinks that since the government is supposed to be "of the people, for the people, and by the people," and since the IRS is a branch of that government, that "we the people" should be their bosses.

4. I hate Wayne Green because he is constantly needling the ARRL to become more activist. He should realize that due to the many League accomplishments over the past 50 years, the League should now be allowed to rest on its traditions and laurels.

5. I hate Wayne Green because he wants his readers to write his publication for him. He constantly asks in his columns for contributions of articles. He should realize that then any idiot could write an article for his publication. Too much readership participation is a dangerous thing!

6. I hate Wayne Green because of his interest in VHF. He thinks that just because the entire history of radio is one of moving to constantly higher frequencies, amateurs should follow that trend.

7. I hate Wayne Green because of his interests in other fields besides amateur radio. Kirlian photography, science fiction, and IRS troubles have nothing to do with my hobby! When I open an amateur publication, I want to shut out the world around me.

8. I hate Wayne Green because he sometimes disagrees with some of the regulations proposed and adopted by the FCC. He should realize that the FCC and its Amateur and Citizens Division always knows what is best for our hobby.

9. I hate Wayne Green because he is controversial. He should know that there is never any controversy in amateur radio. It should always be hushed up or committed to death.

10. I hate Wayne Green because the prize for winning this crazy contest is a trip to the Bermuda Triangle! If you all don't mind, I'd prefer to travel to someplace a bit safer, like Vietnam, Cambodia, or the Middle East!

Phil Sager WB4FDT
3827 N. Abingdon
Arlington VA 22207

EDITORIALS HELP?

Wayne, I hope your editorials in 73 create enough activity by the taxpayers to force the IRS to change its policies.

Name Withheld
Toronto OH

SOLID STATE NEWS

In a recent editorial Wayne asked if there was anyone out there in Hamdon who would like to write a solid state column for us. The result: We were inundated with sample columns. Our minds were boggled and we couldn't reach a decision on which column to run. So we've decided to let you make the decision for us. Here are two columns. Next month we'll run more. Write and tell us which column you liked the best. We'll tally up the results and use the column that gets the best reader response.

Waller M. Scott K8DIZ

Through this new column we will try to keep you informed of new developments in the fast moving field of solid state electronics, with ham type applications in mind. As new products become available the ones of greatest interest to hams will be described along with suggested applications. We hope to give hints as to where the products can be obtained and for how much.

New ICs for receivers continue to pop up. Fairchild's μ A720, primarily intended for AM car radios, can be put to many different uses at frequencies up to 30MHz. This device contains an rf stage, oscillator, mixer, i-f amp, AGC circuit and voltage regulator. The detector is not included in the IC so you are free to choose either a simple diode detector, product detector, or even add additional i-f or mixer circuits. RCA has introduced its CA3123 which is an identical IC. Sprague has their ULX-2137, National, the LM1820 and Motorola plans to announce an equivalent later this year. With all these sources, availability for the ham receiver-builder should be quite good. Mention should also be made of the RCA CA3088 receiver IC. It also is useful up to 30MHz and performs well as a receiver without an rf stage. The 3088 contains built-in i-f AGC and has an AGC amplifier for use with an outboard rf stage. An excellent choice for the rf would be a dual-gate FET using the 3088 AGC for gate No. 2. Additional features of the CA3088 include a built-in 30dB gain audio pre-amp and a drive circuit for an S-meter. The distributor prices of all these radio receiver ICs range from \$2 to \$3, but some of 73's advertisers may give you a better deal.

Quad op amps are very useful building blocks for an endless variety of circuits including audio, control, oscillators, voltage regulators, active filters, sweep generators, etc. Of course, all these can be built with single op amps too, but the convenience of having four amps on one chip makes circuit layouts smaller and more versatile. An added bonus is closely matched operating and temperature parameters since all of the op amps are processed under identical

conditions. Texas Instruments' new SN72L044 is the first quad op amp designed for low power operation. When powered from a $\pm 2V$ supply, it consumes only 340 microwatts! A natural for battery powered or portable equipment. All four amplifiers draw a total of 0.25 mA at $\pm 15V$ supply voltage. This is idle current. Of course, your circuit design will determine how much load current will be added to the idle current. These low noise amplifiers are grouped into two sections so that power can be applied to only two of the op amps, if desired, further conserving power. Other features include internal frequency compensation, high slew rate, and output short circuit protection. For applications requiring only two low power op amps, TI also makes a dual device, the SN72L022. The quad is offered in a 16-pin DIP and the dual in both 8-pin DIP and metal packages.

If your interest is in ultra low power op amps, Siliconix has the L144 tripple. The three op amps draw only 150 microwatts (50 each) when operated from $\pm 1.5V$. This device features supply voltage to $\pm 15V$, internal compensation, programmable bias current, programmable power dissipation, single programming resistor and 80dB gain.

Single supply voltage op amp quads have been around for over a year. There have been some new additions, however. These devices have become unusually popular with the electronics industry, especially with the auto manufacturers. The performance, versatility and low cost make these ICs a must for anyone interested in experimenting with solid state circuits. The National LM3900 and new LM2900 have an open loop gain of 2800, unity gain BW of 2.5MHz, and operate over the voltage range of +4 to +35V. The Motorola MC3301 has a gain of 2000, BW of 4MHz, range of +4 to +28V. The Motorola MC3401 and new RCA CA3401 have a gain of 2000, BW of 5MHz, and a range of +5 to +18V. All these ICs have internal frequency compensation, require low input bias currents, and have output short circuit protection making them easy devices to use. Distributor prices for all these devices are just over \$1, although some suppliers are selling them for 50¢. One of the best application notes ever written is available for the LM3900 from National Semiconductor (AN-72). It applies, in principle, to all the other types mentioned.

Timer circuits are finding their way into many ham designs these days: repeater timers, electronic keyers, delay circuits, and station ID timers to name a few. National Semiconductor has a couple of new precision timers, the LM3905 and LM322. Both of

these timers operate over the wide range of +4.5 to +40V and maintain constant timing periods from milliseconds to hours. The LM322 provides excellent repeatability down to 3 microseconds. A minimum of outboard components are required. An RC network sets the timing, which is begun by the leading edge of an externally generated trigger signal. The timer output is a floating transistor with current limiting and can drive either ground or supply referred loads up to 40V at 50mA. You can program the output transistor to be either off or on during the timing period. The LM322 has two additional features not in the LM3905. One is the accurate short interval timing already mentioned. The other is an input to allow a 50:1 ratio adjustment in the timing cycle with a given RC by varying a voltage applied to that terminal. This feature allows use of the IC as a switching regulator, voltage comparator, or voltage to pulse rate converter. The low input current requirement allows use of a smaller timing capacitor for long time-outs, lessening the need for precision low leakage capacitors. These timers are available in several environmental temperature ranges. The LM322 is in a 14-pin DIP and the LM3905, an 8-pin DIP.

While talking of timers, we should mention the new Exar XR-2340CP programmable timer-counter. This IC is capable of producing ultra long time delays without sacrificing accuracy. Programmable time delays from microseconds to five days are available. Two ICs in cascade can generate time delays up to 3 years! Other applications of this IC include operation with an external clock, use as a frequency synthesizer (programmable), a staircase generator, 8-bit analog to digital converter, etc. The IC consists of an RC controlled time base, a binary counter (8-bit), and a control circuit. The basic time unit is set by choice of the RC network. The binary counter counts each output pulse from the time base. The desired time-out is selected by appropriate connections to the counter output pins. The timing cycle is programmed to be between 1T and 255T where $T=RC$. Accuracy of 0.5% and excellent temperature stability are claimed. In quantities of 1 - 24 the price is \$4.50.

If you do not know of a local distributor who sells the devices mentioned, a letter to the appropriate manufacturer should get you a list of distributors and possibly data sheets and application info on the circuit of interest. 73 advertisers who specialize in solid state components can possibly supply you parts even though they are not currently advertised.

Addresses of manufacturers mentioned this month are: Fairchild Semiconductor, 464 Ellis Street, Mt. View CA 94043; RCA, Solid State Division, Box 3200, Somerville NJ 08876; Sprague Electric, Semiconductor Div., 115 N.E. Cutoff, Worcester MA 01606; Motorola Semiconductor, Box 20912, Phoenix AZ 85036; Texas Instruments, Box 5012, Dallas TX 75222; Siliconix, 2201 Laurelwood, Santa Clara CA 95054; National Semiconductors, 2900 Semiconductor Drive, Santa Clara CA 95051; Exar Integrated Systems, 750 Palomar, Sunnyvale CA 94086.

We would be pleased to hear from you as to what type of solid state developments you want to hear about in this column.

K8DIZ

Vern Weiss II WA9VLK

I would like to invite you to become a part of this column. If you have a technical problem, jot it down and mail it to me. If you have a recent solid-state success in your life and you're busting at the seams to tell someone about it, write! Even if you have run across a newsy vacuum tube gadget, don't keep it from the masses. While the emphasis of this column is on the ham radio applications of solid state electronics, I have always felt that a well rounded ham shack is a hybrid ham shack. When pulling ourselves away from our own established prejudices we must admit that many electronic applications perform better with transistors while others simply lend themselves better to the good old valve parameters.

A LITTLE BLAH THEORY

If you are an average ham you probably feel that transistors are cute, nifty and wowee-Mama-watch-this. You also probably have a good knowledge of electron tube theory, but for now prefer to satisfy your solid state knowledge void by buying a Heathkit and worrying about theory later. Therefore, we are going to give you a shot of theory each month - in small doses - to ease the pain.

Tubes and transistors perform many of the same jobs, but in construction are entirely dissimilar. The first and most obvious difference is that they do not look alike. Tubes and transistors are made of different recipes. Nowadays, transistors are made of silicon-crystal or germanium metal materials. Most transistors presently used are of the silicon type. To complicate things even more, there is some experimentation taking place with semiconductor production involving the combination of the two elements, silicon and germanium. But for the most part, Germaine and Si have the market cornered.

Tubes as you will recall (get out the license manuals) are voltage-operated devices while transistors are current

operated. Ah-Hah! You've got me there, right? I wince at the thought of you sitting there prepared to hit me with, "OK stupid, how do you explain the presence of current in tubes and voltage in transistors?" H-m-m-m. Let me think a minute. For now, let's just say that in a tube you can have the presence of voltage but not of current. Alternately, in a transistor, there can be current present but no voltage. Therefore, the tube must get its minimum daily requirement of volts if it is going to exist and live a happy life producing many, many happy little milliamps. In transistors the whole process is reversed. To further illustrate; how many times have you been trouble-shooting that final amplifier and was baffled because the 6146 had voltage but no plate current? This gets into specific conditions which will be dealt with later.

Often transistors, which thrive only because of the current within, are wrongly compared to tubes. The comparisons and "interchangeability" stem from nothing more than ever anxious marketing techniques and sales pitches and has little basis. The only parallel that should be drawn is that tubes and transistors can be harnessed to perform similar results in a circuit.

To dissect the "guts" we see that a tube (with its ohhh so warm glow on a cold New England night) grid controls the electron flow between the cathode and plate. Likewise, a transistor (with its cold, silent...almost standoffish personality) base controls the current flow between the emitter and collector. We also see that in a tube, the cathode shoots them thar little electrons off to the plate, which in turn, sucks 'em up. In the transistor, the emitter (so named because of its station in life) shoots the electrons over to the collector which catches them, like a solid-state Yogi Berra.

A mnemonic device to help remember these two component's inner-operations in relation to each other might be: Cathode - cathode; Grid - glow; Plate - proudly; Emitter - Emitter; Base - be; Collector - cool; ...oh well.

THE DYNASCAN B&K 162 TRANSISTOR/FET TESTER

Those seeking an excellent transistor tester should seriously consider the B&K 162 TRANSISTOR/FET TESTER. The unit is accurate, fairly inexpensive, attractive and I consider it one of the better pieces of electronic test equipment available.

The unit displays a complete analysis of all bipolar transistors, field effect transistors, diodes, unijunctions, SCR's and triacs, whether tested in the circuit or out.

Since a transistor tester capable of monitoring every transistor com-

ponent condition would be well beyond the financial grasp of many, the B&K does a nice job of diagnosing a component's state of being from a few universal tests which are sufficient to determine good-bad and current gain. A sequential switching procedure is involved in checking all solid state devices, therefore, no time consuming or confusing tester set up is required. With two rotatable switches (that 'click' so solidly) one can perform three leakage tests and a beta test. FETs may be tested with their own one-switch-to-test steps, measuring conductance (Gm), gate control and leakage. Even beginners would have no problem with operating the 162, and they probably would pick up a basic understanding of what solid state is all about. The instruction pamphlet is a storehouse of information in itself.

The B&K 162 has a METER! I mean...a *real* meter! It's a large, clear, easily read and highly responsive indicator and ohhh, what fine precision meter movement.

The only drawback is that the 162 is run on flashlight (D) batteries. This factor, coupled with its lightweight, makes it super-doooper for field service, but I have always preferred good 'ol 110 when it comes to test equipment. There's really no worry about inaccurate tests due to failing batteries as the B&K people built in a nifty battery test circuit, so I guess I have no real cause to gripe. Those with big fingers might do well to practice clamping the small test leads onto small component leads in small areas. It takes some diligent finger-gymnastics and a lotta hope to get the leads clipped onto the device under test in today's jam-packed circuit boards.

The B&K is a professional piece of gear through and through and any ham who has one is ready for serious solid state construction and repairs. The tester is one of those electronic devices you naturally want to put back into its box after each use. Cost is the same as 200 packs of cigarettes...and well worth every pack.

It looks as though space is running out, but again I want to emphasize that I would like to hear about those projects of yours...and problems. The idea of awarding a handsome award each month for THE homebrew project has been proposed, so get out the junk box and set out to dazzle and amaze us. Next month I have a handy little transistor aircraft band receiver for those of you frequently in the "hanger-flying" situation, desiring something on VHF that works from the innards of a Band-Aid box.

See you on the circuit!

WA9VLK

4-1000A GROUNDED GRID LINEAR

Featuring:

*Solid state alc
Shielded module construction
Plate vacuum tuning
80 through 10 meters
Thyrector protection
4-1000 technical summary*

Simplified module construction incorporated with up-to-date features including high plate dissipation make this linear amplifier an excellent choice for reliable contest, rag chewing or SSTV applications.

Construction

The following tools were used in the construction of the amplifier: metal munching tool, pop rivet gun, electric drill, various hand tools and a good soldering gun.

The main chassis 43.18 x 43.18 x 10.16cm (standard) and the front and back of the amplifier is constructed from 43.18 x 43.18 x 7.62cm (standard) and 33.02 x 17.78 x 7.62cm (standard) chassis respectively. The front and back are mounted to the main chassis by pop rivets around the perimeter. The cover is manufactured by hand bending a 48.26 x 121.92 x .16cm (standard) sheet of aluminum to tightly fit chassis assembly and is held in place by sheet metal screws at 3cm intervals.

Bending can be accomplished with two pieces of angle iron. The material to be bent is clamped between the angle irons using C-clamps and a vise. Use a piece of flat wood as a protector between the hammer and the material to be bent to avoid unsightly

hammer marks. A commercial metal bending brake will no doubt do a better job in far less time provided you have or can borrow one.

The air is exhausted by mounting home air vent assemblies on the sides of the cover and perforated aluminum sheeting over holes on the top and back. A total of six holes are covered by the perforated aluminum.

To achieve proper shielding, the screen in the air vent is removed and replaced with perforated aluminum eave trough screen, available at most hardware stores. When properly installed it provides excellent shielding but it is too weak to be installed without a frame. Attach the air vents a minimum of every 2 cm around the perimeter of your cover to provide adequate shielding. Small aluminum pop rivets really come in handy here but make sure each rivet is fitted tightly. Before I attached aluminum to aluminum I roughed each contact surface with extra fine sand paper to assure a good electrical connection. Also, each chassis was electrically connected together by lengths of copper braid.

The front of the amplifier contains a relative output meter (lower left), plate current meter (upper right) and grid current meter (upper left). The high voltage reading

The Ultimate F.M. Transceiver

Here it is, the FMer's dream, a fully synthesized transceiver that'll cover the entire two meter band, PLUS a built-in scanning receiver that'll locate any repeater frequency in your area that's in use.

And get a load of these other features that make the ultimate rig:

- Operates on FM, AM or Modulated CW
- Built-in DC and AC power supplies
- Frequency Range of 143.5 to 148.5 MHz in 5 KHz increments
- Autoscans in 5 KHz steps across entire band, with adjustable speed and frequency limits.
- Synthesizer flexibility that offers choice of 600 KHz up or down, 1 Meg up or down, simplex, frequency split, or any nonstandard split (programmable) all from a single function switch.
- Receiver Sensitivity of 0.35 Mv for 12 db SINAD on FM
- Dual power output of 20 watts or 5 watts across entire band
- Adjacent channel rejection (30 KHz) 100 db minimum
- Image spurious and intermodulation (EIA) 80 db minimum
- 10 pole, 13 KHz crystal filter
- Receiver Superhet, single conversion
- Frequency stability of 0.0005%
- Built-in tone burst and PL encoders and decoders
- Built-in touch tone pad
- Full LED Digital readout
- Built-in S Meter also serves as VSWR bridge, power output meter, battery indicator, deviation indicator and discriminator meter.
- Audio output 4 watts @ 10% THD
- Speaker built-in to left side of cabinet for maximum mobile reception
- Headphone jack for noise-free mobile operation
- Independent selectable priority channel
- Built-in Auto CQ
- Temperature range from -20° to 170° Fahrenheit
- Size: 4" H x 8" W x 10" D Weight: 10 pounds
- One million channels (1000 Rec. x 1000 Trans.)



\$1495 00

A \$100 deposit will insure early delivery and guarantee price

You owe it to yourself to go first class. Try an EBC 144 —
You deserve it !



**emergency
beacon corp.**

15 MM River Street
New Rochelle NY 10801 (914) 235-9400

AMATEUR PRODUCTS DIVISION

was taken from a voltmeter mounted directly in the power supply.

The three controls on the front in the lower left are cathode tuning, relative output level and alc level. Also included is a turns counter in the upper right for the vacuum variable capacitor and a vernier dial for the loading capacitor. The band switch is located in the middle and ganged to the cathode circuit via two right angle drives, providing single switch band switching. Once drives were properly adjusted I soldered them to the shaft to prevent slipping.

The bottom plate is made from .32cm (standard) aluminum or steel with one caster at each corner. It should be held in place by sheet metal screws placed a distance of 3 cm to insure adequate shielding.

To provide safety and stability, many sub-chassis are used. The alc and relative output circuit are shielded in the final enclosure. The sub-chassis are relatively inexpensive if purchased, but could also be hand formed.

The alc and relative output circuits are enclosed in aluminum miniboxes. The plate and grid current meters are enclosed in a 12.7 x 25.4 x 7.62cm (standard) chassis with steel or aluminum bottom plate attached. The relative output meter was a shielded meter and provided low measured leakage with no enclosure. The loading capacitor has an added frame enclosure but it is not critical in the design. The rear of the amplifier is designed with safety in mind. The B+ and B- connections are in a 12.7 x 10.16 x 7.62cm (standard) chassis with two grommetted holes in the bottom. High voltage cables should have a minimum rating of two to three times the voltage expected to be encountered. The blower is fused and the blower solder connections and fuses are located in a small minibox. The ac line is terminated in a small sub-chassis and at this point the thyrector attenuates line transits providing protection to your solid state devices. The ac is fed into the bottom chassis through two feedthrough capacitors and is fused in the plug with two fuses, one on each side of the line. This places all but one fuse externally and readily available. Located on the back are three shielded banana outlets for vox, alc and the high voltage

FREE IC

With Every \$10 Order*

- REDUCE YOUR PROJECT COSTS
- MONEY-BACK GUARANTEE
- 24-HOUR SHIPMENT
- ALL TESTED AND GUARANTEED
- LINEAR IC's:

709	Popular OP AMP (DIP/TO-5)	.39
723	Adjustable Voltage Regulator (DIP/TO-5)	.75
741	Freq. Compensated OP AMP (DIP/TO-5/MINI-DIP)	.45
747	Dual 741 OP AMP (DIP)	.95
LM305	Postive Voltage Regulator (TO-5)	1.25
MC1458	Dual 741 OP AMP (MINI-DIP)	.95
Assorted Linears-741/709/723, etc. (4)		2.00
- FET's

N-CHANNEL (LOW-NOISE):		
2N4416	TYPE RF Amplifier to 450 MHz (TO-72)	2/\$1.00
2N5486	TYPE RF Amp to 450 MHz (plastic TO-106)	3/\$1.00
2N5163	TYPE Gen. Purpose Amp & Sw (TO-106)	3/\$1.00
2N4091	TYPE RF Amp & Switch (TO-106)	3/\$1.00
Assort. RF & GP FET's, 2N5163, 2N5486, etc. (8)		\$2.00
P-CHANNEL		
2N4360	TYPE Gen. Purpose Amp & Sw (TO-106)	3/\$1.00
- TRANSISTORS

NPN:		
2N3563	TYPE RF Amp & OSC to 1GHz (TO-106)	6/\$1.00
2N3565	TYPE Gen. Purpose High Gain (TO-106)	6/\$1.00
2N3904	TYPE GP Amp & Sw to 100mA (TO-92)	6/\$1.00
Assort. NPN GP TYPES, 2N3565, 2N3641, etc. (15)		\$2.00
PNP:		
2N3638	TYPE Gen. Purpose Amp & Sw (TO-106)	4/\$1.00
- DIODES:

1N914	TYPE Gen. Purpose 100V/10mA	10/\$1.00
1N3600	TYPE Hi Speed SW 75V/200mA	6/\$1.00
1N4608	TYPE GP & SW 80V/400mA	6/\$1.00
RECTIFIER Stud Type 400V/5A		2/\$1.00
1N749	ZENER 4.3 Volt 400mW	4/\$1.00
1N753A	ZENER 6.2 Volt 400mW	4/\$1.00
1N755A	ZENER 7.5 Volt 400mW	4/\$1.00
1N757A	ZENER 9.1 Volt 400mW	4/\$1.00
1N758A	ZENER 10 Volt 400mW	4/\$1.00
1N965B	ZENER 15 Volt 400mW	4/\$1.00
LN968B	ZENER 20 Volt 400mW	4/\$1.00
VARACTOR 1-3W @ 432MHz 2-10pF		\$1.00

*MAIL NOW! With every order of \$10 or more, postmarked prior to 8/30/74, FREE IC of our choice included.

ORDER TODAY—All items subject to prior sale and prices subject to change without notice.


WRITE FOR FREE CATALOG offering hundreds of semi-conductors not listed here. Send 10¢ stamp.

TERMS: All orders prepaid. We pay postage. \$1.00 handling charge on orders under \$10. Calif. residents add 6% sales tax.

ADVA

ELECTRONICS

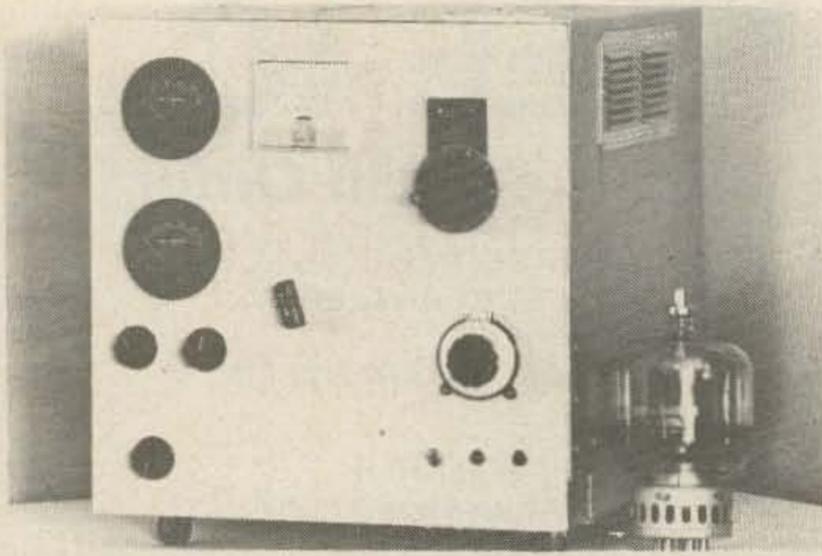Box 4181-D, REDWOOD CITY, CA 94062
Tel. (415) 851-0455



Front view. Meter upper left grid drive, lower left relative output, center plate current. Three controls in lower left. Alc far left, relative output sensitivity right, cathode tuning lower left. Front center control band switch. Upper right turns counter. Lower right loading control. Switch, on and off. Green filament light left. Red high voltage light right. Note: air vents on side.

light. Located below the banana plugs is a heavy-duty ground connector which should be utilized to recude possibilities of electrical shock. The rf is fed directly into the lower compartment and output is taken directly from the upper chassis to eliminate the problem of feedback. Shielding between input and output circuits of a grounded grid amplifier reduces the possibility of parasitic oscillations. The large opening in the rear of the amplifier where air enters the pressurized bottom chassis from the blower must be adequately shielded. An aluminum screen mounted over the hole and bolted in place at a minimum of every 2 cm insures good electrical connection between the screen and chassis. Be sure to clean the screen occasionally as it will clog up with dust, decreasing air volume. Place the blower a good distance away from the tube socket and seal any undesirable air leakage points in the bottom chassis with silicone rubber sealer to provide a good pressurized system. Cutting the lower flange off the tube socket will also provide better unrestricted air flow if you use the standard SK-510 socket.

To protect the operator, metal shafts that protruded out the front were equipped with insulated shaft couplings. All shafts at ground potential were connected directly to ground via flexible copper cable. This was done as double protection even when the shafts were already at ground potential, as in

the case of the loading capacitor. I took great care in these connections to guarantee they were electrically and mechanically strong.


Wiring

The wiring of the amplifier is straightforward. If you are contemplating construction and have not built a linear before, I would recommend the reading of construction techniques, as applied to rf amplifiers, in the handbooks — particularly the section on preventing radiation from the transmitter.

The input circuit is a tuned cathode circuit. The 4-1000 requires a substantial amount of drive; therefore a cathode tuned circuit is a must. This reduces drive requirements and also provides improved distortion products. When constructing this circuit, keep in mind that 10 meters may be a problem in respect to drive — therefore align coil and capacitor combination to provide short connecting leads on ten. Silver plating the cathode coil and leads also provides measurable improvement on ten. I had no problem with drive, but if your exciter is marginal it could make the difference.

Grid drive is monitored with a 0-1 mA meter utilized as a millivolt meter. *Be sure to calibrate meter before soldering the screen.* As the screen is operated in parallel with the control grid it must be disconnected from ground so that you are reading control grid current only. To calibrate the meter you must determine the proper value of the series resistor Rx. This is found by placing a regular milliammeter with a scale of 200 mA or more from the vox terminal to ground. Carefully apply excitation with no plate voltage and substitute resistors at Rx until both meters have the same deflection at 100 mA. My meter required 82Ω but this is variable depending on meter characteristics. Another meter may require a larger or smaller value. As the 4-1000 has no plate voltage at this time, the control grid dissipation can be easily exceeded. Therefore be extremely careful and work quickly during periods of excitation.

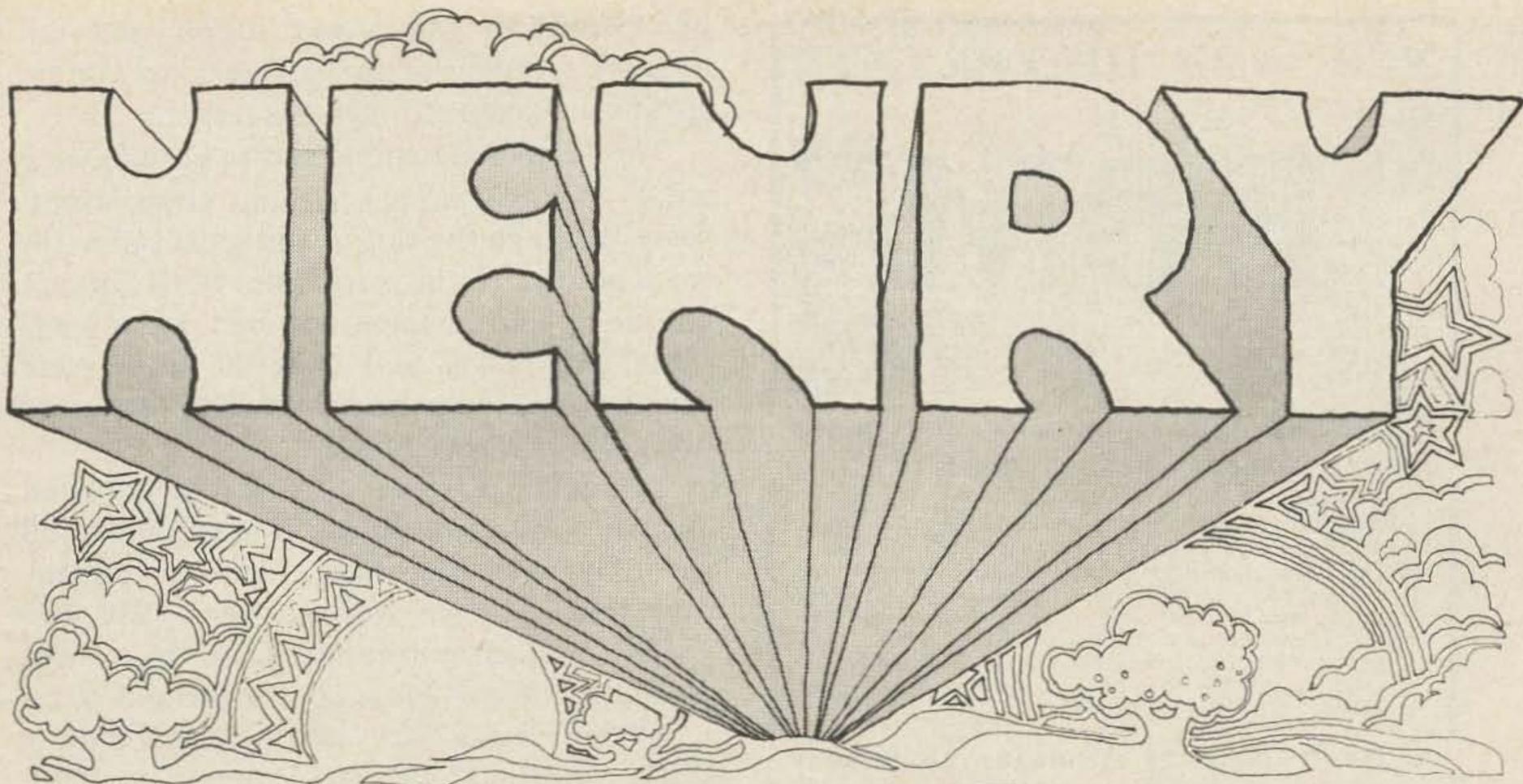The plate current is measured by the meter being shunted across a 10Ω resistor in the negative high voltage lead. The resistor




ONE NAME GROWS STRONGER YEAR BY YEAR

When you buy a Henry Linear Amplifier, you buy quality, performance, reliability.. all the features that have made Henry amplifiers world famous. But most of all you buy the integrity of the Henry name.

Other brands have disappeared from the amateur scene...names that were familiar to all amateurs. Now those companies are gone and their equipment is orphaned.

But one name has grown steadily throughout the years. Today Henry amplifiers stand preminent throughout the entire amateur world...symbols of the finest equipment you can buy.

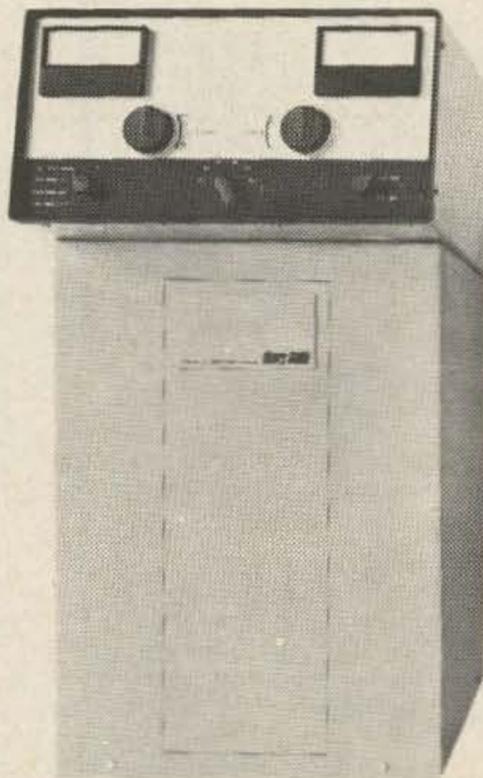Join the great family of happy Henry amplifier owners. Treat yourself to the best.



2K-4... THE "WORKHORSE"

The 2K-4 linear amplifier offers engineering, construction and features second to none, and at a price that makes it the best amplifier value ever offered to the amateur. Constructed with a ruggedness guaranteed to provide a long life of reliable service, its heavy duty components allow it to loaf along even at full legal power. If you want to put that strong clear signal on the air that you've probably heard from other 2K users, now is the time. Move up to the 2K-4. Floor console or desk model... \$895.00

2K-ULTRA Small, rugged and reliable. Loafs along at full legal power without even the sound of a blower. Uses the best components available, including a pair of Eimac 8873 tubes. \$895.00

TEMPO/2001 Small, reliable and inexpensive. Two Eimac 8874 grounded grid triodes, full kilowatt of output for SSB, built-in solid state power supply, antenna relay, internal blower, relative RF power indicator and full amateur band

coverage from 80-10 meters. \$595.00

3K-A Superior quality linear amplifier for commercial and military use. Two Eimac 3-500Z grounded grid triodes, three kilowatts PEP input on SSB with efficiencies in the range of 60%. PEP output in excess of 2000 watts. Provides a power supply capable of furnishing 2000 watts of continuous duty input for RTTY or CW with 1200 watts output. \$1150.00

Henry offers a line of superb commercial high frequency amplifiers including the 4K-Ultra and 1K-4A Channelized Amplifier. Also solid-state Vhf and Uhf amplifiers up to 120 Watts.

Please call or write for full technical specifications. Henry Amplifiers are also available at select dealers throughout the U.S. Export inquiries invited

Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

Prices subject to change without notice.

NEW AND DIFFERENT!!



The all new T_{doc} manual for electronics experimenters and hobbyists ---

More than two years in the making, T_{doc} has gathered the most practical and usable data from industry, the U. S. Patent Office, DOD, NASA, NTIS (National Technical Information Service) and others. Jam-packed with all the data needed by the hobby experimenter at the bench. From theory refresher to applications diagrams, device characteristics, tables and formulas, charts and graphs -- hundreds upon hundreds of illustrations.

A High-Density Modular Document

No wasted space or words. Separate sections are removable in loose-leaf fashion -- books within a book -- mounted in a rugged binder, big enough to hold other T_{doc} publications -- or your own notes.

Just by way of example, the section on hand soldering was boiled-down from the practices of the American Welding Society -- Committee on Soldering and Brazing; NASA, USN, solder manufacturers, the Bell Telephone System and others. The section contains everything you need to know about solder, fluxes, soldering tools and techniques.

There are over 100,000 words covering theory and application of semiconductor devices -- diodes, transistors, the SCR/TRIAC, digital and linear integrated circuits, operational amplifiers, voltage regulators, counters and decoders, and much, much more.

Sections also treat the vacuum tube and CRT, capacitors and electrostatic devices, relays and switches, electromechanical devices and mechanical movements, energy sources, cable and wire, +++++

Update Without Annual Replacement

No need to buy a whole new book every year to keep abreast of information in the field; the "book within a book" style permits you to update only as needed.

There has never been another manual like it. That's why we undertook to put it together!! Once you have had a chance to put the manual to use, you'll start enjoying electronics as a hobby, with fewer unfinished projects that could have been completed had there not been an information gap!

Electronics Bench Manual

**Introductory Price: \$17⁹⁵ Postpaid
In U.S.A.**

Send check or money order marked "EBM" with your name and address to:

**TECHNICAL DOCUMENTATION
BOX 340
CENTREVILLE, VA 22020**

703-830-2535

Virginia residents please add 4% sales tax.

was placed at the power supply and the negative terminal of the supply must not be grounded except through the resistor.


The screens are connected to ground via a .64cm flexible copper ground strap which passes through the slot of the socket directly from ground to the screen pin. Both pins are grounded in the same manner. Keep leads short! All power and metering leads were shielded and bypassed according to good construction procedures.

The entire plate circuitry was silver plated and the connecting output lead from the coil assembly was of silver plated .65 cm (standard) copper tubing. The plate and vacuum capacitor lead are made from silver plated flexible 1.27cm copper ground strap.


Silver plating was accomplished with a small electroplating unit powered by flashlight batteries. It was simple and required no special skill. There are different units available from various electronic outlets with prices starting at a few dollars.

Adjustment

Before applying any potentials recheck all wiring. Set the sensitivity of the output indicator to minimum, that is, maximum resistance with the slider of the 25K pot at ground. Connect a dummy load of 52 to 72Ω. Select the proper band with S1 and apply plate voltage. Apply a small amount of excitation. Peak up C1 for maximum reading. Resonate the output circuit with C3, making sure the loading capacitor is set at full capacity. Adjust C3 and C2 to increase

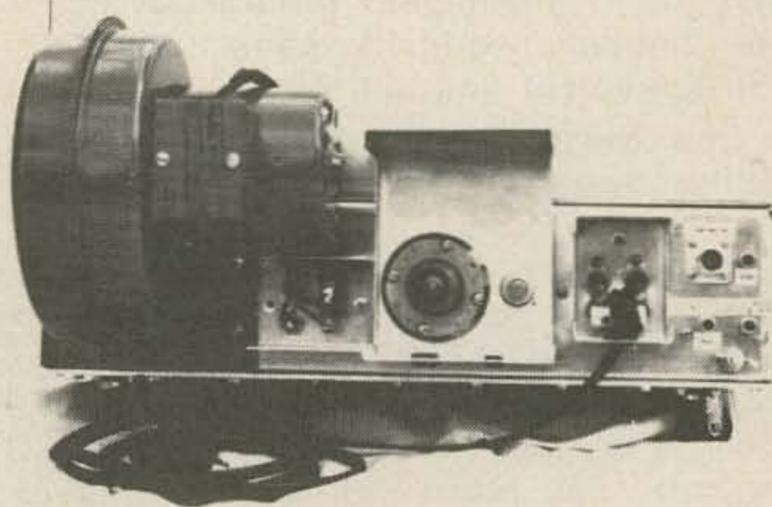

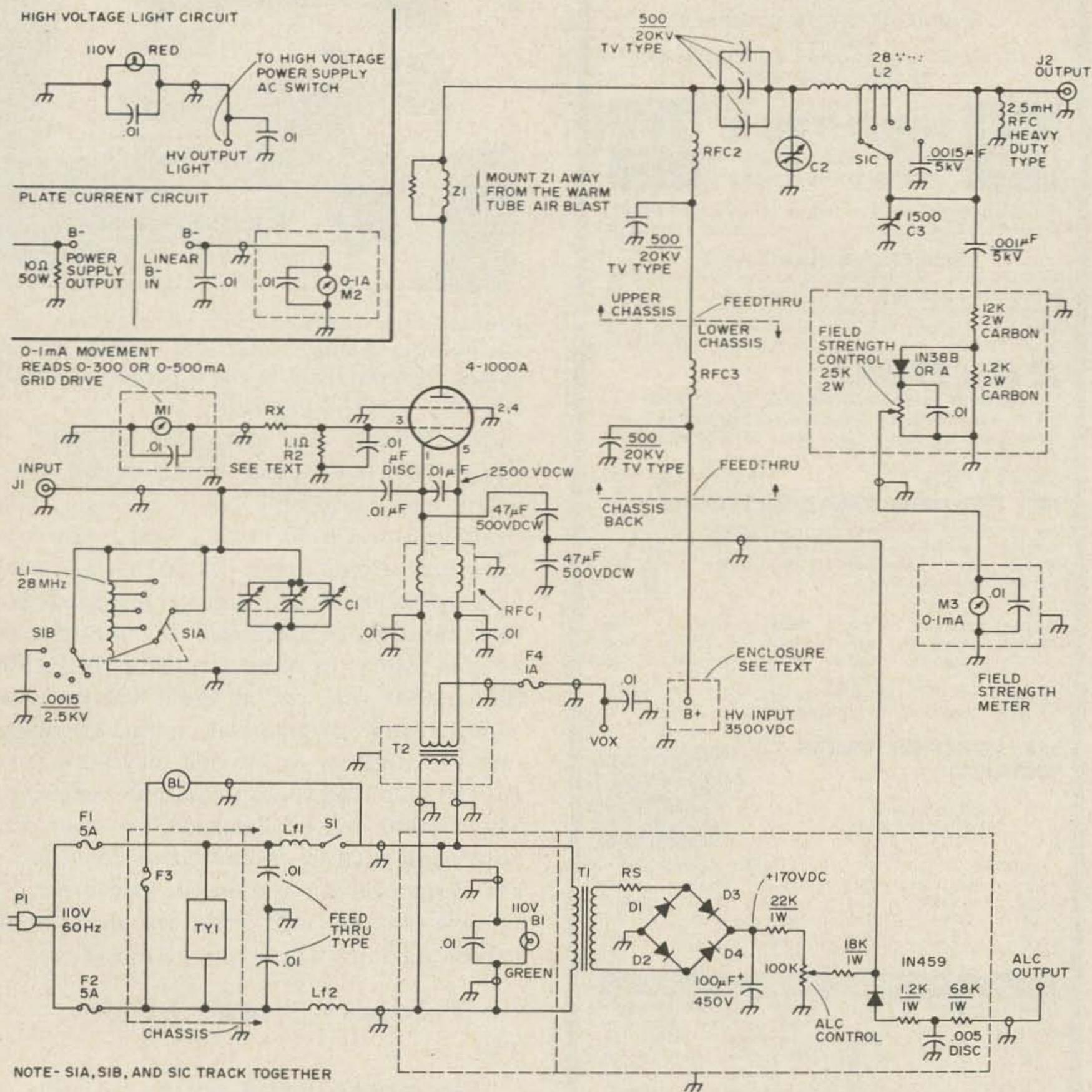Right to left: Rear view showing ground, alc, H.V. indicator, vox terminals, rf input terminal, ac input showing feed-through capacitor, thyrector and enclosure. Middle enclosure B- and B+ terminals. Left enclosure blower ac supply and fuse. Far left blower.



Schematic diagram of the modern 4-1000A, Class B, grounded grid, linear amplifier.

the plate current to the input power level you desire while increasing drive to 120 to 150 mA. You will probably note that the rf output meter and plate current meter conflict somewhat. Maximum output does not always occur at the point of resonance. Don't let this alarm you, adjust your drive and loading to a point where for a given drive, the output drops off slightly at your desired input. This is the point where you will generally achieve the best linearity. Once you have established your tuning for a band, record turns and loading for future reference.

To utilize the alc properly, connect the exciter to the linear via the alc connector on the rear of the amplifier. Once connected you may adjust your alc to achieve the maximum limitations you desire. The alc section, if properly utilized, can increase the average power output while maintaining the linear within the amateur power-input limit, providing that extra punch to communicate under adverse conditions.

Operation

The operation of the amplifier has been excellent. It provides adequate efficiency

NES

NURMI ELECTRONIC SUPPLY

Department 48
1727 Donna Road • West Palm Beach, Florida 33401
PHONE — (305) 686-8553



HEP 170's
THE "DO EVERYTHING"
2 1/2 AMP, 1000 VOLT DIODE



Motorola is catching up on the backlog and we've got thousands of them back in stock. 10/\$2.50 — 100/\$20.00

BELDEN TEST LEAD WIRE

20KV breakdown, 5KV Working, 18 ga, super flexible, Available in Red, Black, Gray, Blue, White, Yellow, Green. Designed for meter leads, test leads, clip leads, etc. Cut to your length. Minimum of 10 feet per color. Factory Fresh! Belden No. 8899. 6 cts. Foot - 100 Ft./\$5.00

RG - 174/U

WE WENT THROUGH 20 MILES OF IT LAST TIME!

We are authorized Belden Distributors and new shipments have come in from the factory. Split a 500' spool with a friend and save \$\$\$\$

BELDEN NO. 8216 100'/\$5.25 — 500'/\$19.30

RF POWER TRANSISTORS

We did it again - All brand new with standard markings and most were manufactured this year. A major manufacturer dropped his RF power line and we bought his inventory.




2N5589	3 Watts Out	\$ 3.50	2N6080	4 Watts Out	5.00
2N5590	10 Watts Out	6.00	2N6082	25 Watts Out	10.00
2N5591	25 Watts Out	12.00	2N6084	40 Watts Out	15.00

All are Silicon NPN and power output ratings are good to 175 MHZ. Hurry! Some quantities are limited.

KEYSTONE PERF BOARD

G-10 Glass Epoxy
Perf Board 3/64" Thick.

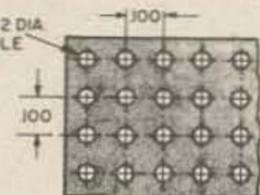


--UNCLAD--

No.	Size (in.)	Price
4229	2 x 4 1/2	\$.85
4230	2 x 6	1.09
4231	4 1/2 x 6	1.55
4232	17 x 6	5.75

--COPPER CLAD ONE SIDE--


No.	Size (in.)	Price
4238	2 x 4 1/2	\$1.35
4239	2 x 6	1.85
4240	4 1/2 x 6	3.20
4241	17 x 6	6.70

PUSH-IN TERMINALS For .042 DIA. HOLES

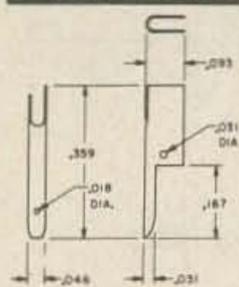


Cat. No. 1495 \$1.50/C
MATERIAL: .008 thick Beryllium Copper.
FINISH: Fused Tin Plate

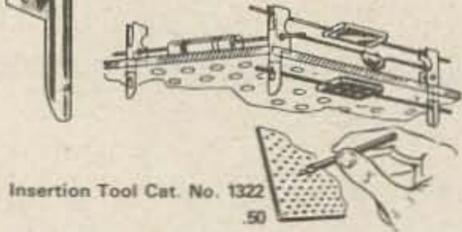The terminal is easily press-fit into a .042 dia. hole without staking or the base may be flared for permanent installations. Ideally designed for use in micro-circuitry to support components when space is at a premium.



Insertion Tool Cat. No. 1322

RF RELAY

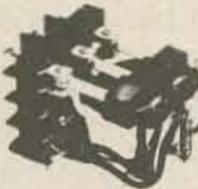

Designed to handle 200 watts to 450 MHZ. 12 VDC coil, DPDT. The nicest RF relay we have ever had. Only about 1-1/4" cube. Super low VSWR. Satisfaction guaranteed.

Only \$4.95 or 4/\$17.00


ARCO/EL Menco TRIMMERS

400 \$.55	421 \$.55	428 \$1.26	464 \$.69
402 .55	422 .55	429 1.26	465 .89
403 .67	423 .64	460 .37	466 .97
404 .81	424 .80	461 .32	467 1.04
405 1.01	425 .85	462 .52	468 1.20
406 1.04	426 1.01	463 .64	469 1.22
420 .58	427 1.12		



WE GUARANTEE WHAT WE SELL!!!!

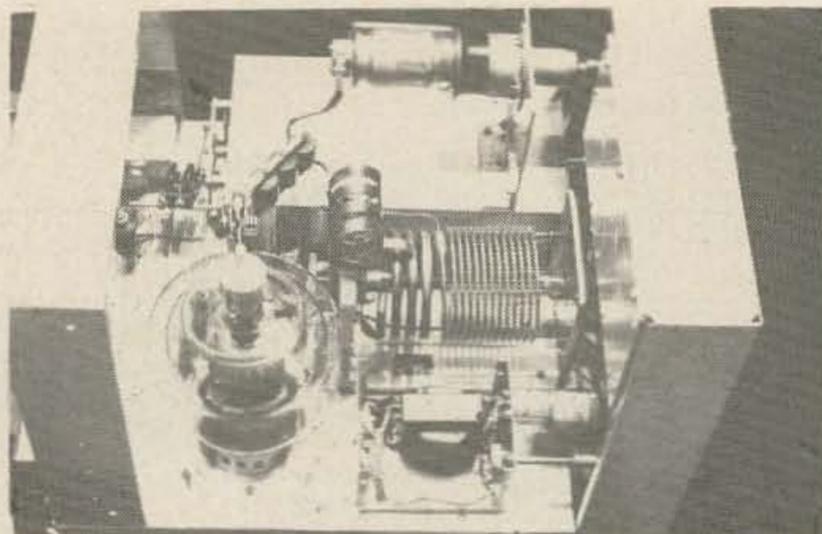We ship UPS whenever possible. Give street address. Include enough for postage, excess refunded in cash. Florida residents include 4% Tax.



Looking down on amplifier's alc enclosure cover removed for photo. Note: also vacuum variable mount. Relative field strength enclosure and 2.5 mH rfc is located in upper left.

and it is built with long-term reliability in mind. The multi-band linear circuit compared most favorably with a single band configuration on 80 meters which would be expected. Comparison of harmonic levels with commercial ham linears provided data that equalled or exceeded the commercial designs tested. In respect to tube operation, the 4-1000 will loaf at the 1 kW dc level, whereas some commercial circuits are operating the finals at or beyond maximum level which could lead to unpredictable reliability. The 4-1000 can be damaged, however. The control dissipation is limited to 25 watts — therefore keep an eye on the grid drive. Do not exceed 200 mA drive, and *never* apply full excitation without any plate voltage.

Technical Summary 4-1000A

TVI

The 4-1000 proved not to be guilty of rampant TVI. The circuit described was compared with commercial amplifiers at the same power level, 1 kW, dc, and it provided equal or better results. Circuits designed, constructed and operated according to good engineering practice should provide excellent results. Persons experiencing severe TVI problems with the 4-1000 should review their design and operating parameters for possible errors. This is not to discount problems due to rectification or overload. However, these problems are not the fault of the linear.


Drive requirements

The 4-1000 does require a fair amount of drive. Most commercial exciters should drive

GET TO THE FAST TOP!

NOW YOU CAN CHANGE, ADJUST OR JUST PLAIN WORK ON YOUR ANTENNA AND NEVER LEAVE THE GROUND!

ROHN manufacturers towers that are designed and engineered to do specific jobs and that is why we have the FOLD-OVER TOWER . . . designed for the amateur. When you need to "get at" your antenna just turn the handle and there it is. Like other ROHN big communication towers, they're hot dip galvanized **after** fabrication to provide a maintenance free, long lived and attractive installation. ROHN towers are known and used throughout the world . . . for almost a quarter century . . . in most every type of operation. You'll be in good company. Why not check with your distributor today?

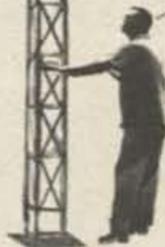

ROHN **MANUFACTURING**

DIVISION OF



P.O. Box 2000 / Peoria, Ill. 61601

the amplifier to 1 kW dc up to 15 meters, however.

Ten meter drive requirements may be a problem for two basic reasons: (1) Some excitors fair poorly when it comes to output on 10. They provide substantially less output on 10 as compared with 15 meters. A check of your exciter's output efficiency would be advised before selection of this tube for 10 meters. (2) When building the multi-band input cathode circuit, much energy can be lost in this configuration. Normally the majority of loss is at the highest frequency of operation.

Parasitic oscillations

If the 4-1000 circuit is wired according to good engineering practice with proper preventive measures taken, you should have no unusual problem with parasitics. Before you place your amplifier on the air, you should completely check it for parasitics on all bands. When first constructed, a parasitic may well occur but once the amplifier has been stabilized, it should provide excellent results. Parasitics are generally the result of the layout and wiring and not the tube per se. Keep in mind that it is indeed a lucky ham who builds a linear with any type tube who has a completely stable amplifier to begin with.

Negative aspects

Tube cost is considerable. Although I used new tubes in my circuits, used or pull-out tubes have in some cases been used to advantage. But beware, a pull-out tube may have very low emission, causing a change in plate load impedance requiring changes in loading parameters for maximum efficiency.

The air flow required causes irritating noise. Even if a low noise blower is used, air whistles as it flows through the perforated holes in the shielding. If you are using a great amount of audio processing the noise level may be prohibitive.

The tube is large physically, which requires a large enclosure.

Component Modifications


To prevent the possibility of high voltage breakdown due to moisture at the base of

the B&W 800 a fiber screw replaced the metal one supplied. Also, the B&W 800 was not mounted directly on the chassis. A 2.54 x 5.08 x .32cm (standard) piece of plexiglass was cut and the choke was mounted to it. The plexiglass was mounted 1.27cm above the chassis on two 1.27cm insulated stand-offs.

An extra switch position is required for the B&W 850A so that the .0015 μ F mica capacitor can be switched in on 80 meters. An extra contact for constructing the switch is available from Barker & Williamson in Bristol, Pennsylvania.

A note on the B&W 850A

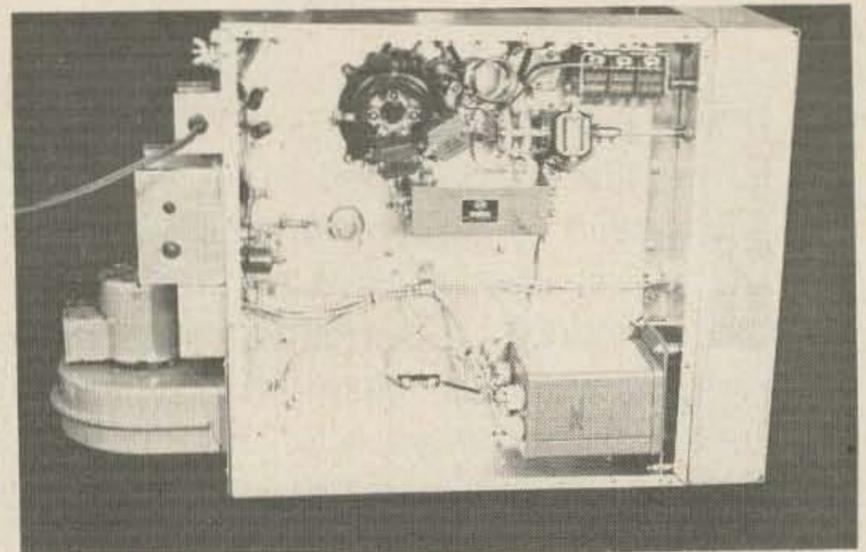The B&W 850A multi-band inductance does an adequate job of impedance transformation considering it covers 80 through 10 meters. It does not, however, provide the



Bottom wiring view.

optimum results that a well-designed single band linear can provide.

In essence, if you are a band hopper and prefer convenience, the B&W 850A will fill the bill. But if you are basically a one-band man, critical about efficiency, you would probably be happier omitting the B&W 850A, saving a few bucks and going single band by replacing L2 with a single band inductance. For further details see pi-network design in the various handbooks and journals.

Credits

I would like to thank the countless amateurs who generously gave their time and advice, which helped in the design, construction and testing of this circuit.

...K8VIR

FREE TT BATTERIES

By now, most everyone is aware of the new Polaroid SX-70 color camera. If you don't have one yet, you probably have a friend that does, and in any event you consequently know that the camera system contains sophisticated IC circuits (containing more than 200 transistors) which provide automatic exposure settings, an electronic shutter, flashbulb sequencing and firing circuits, and a special high speed motor to expel the exposed photograph from the camera

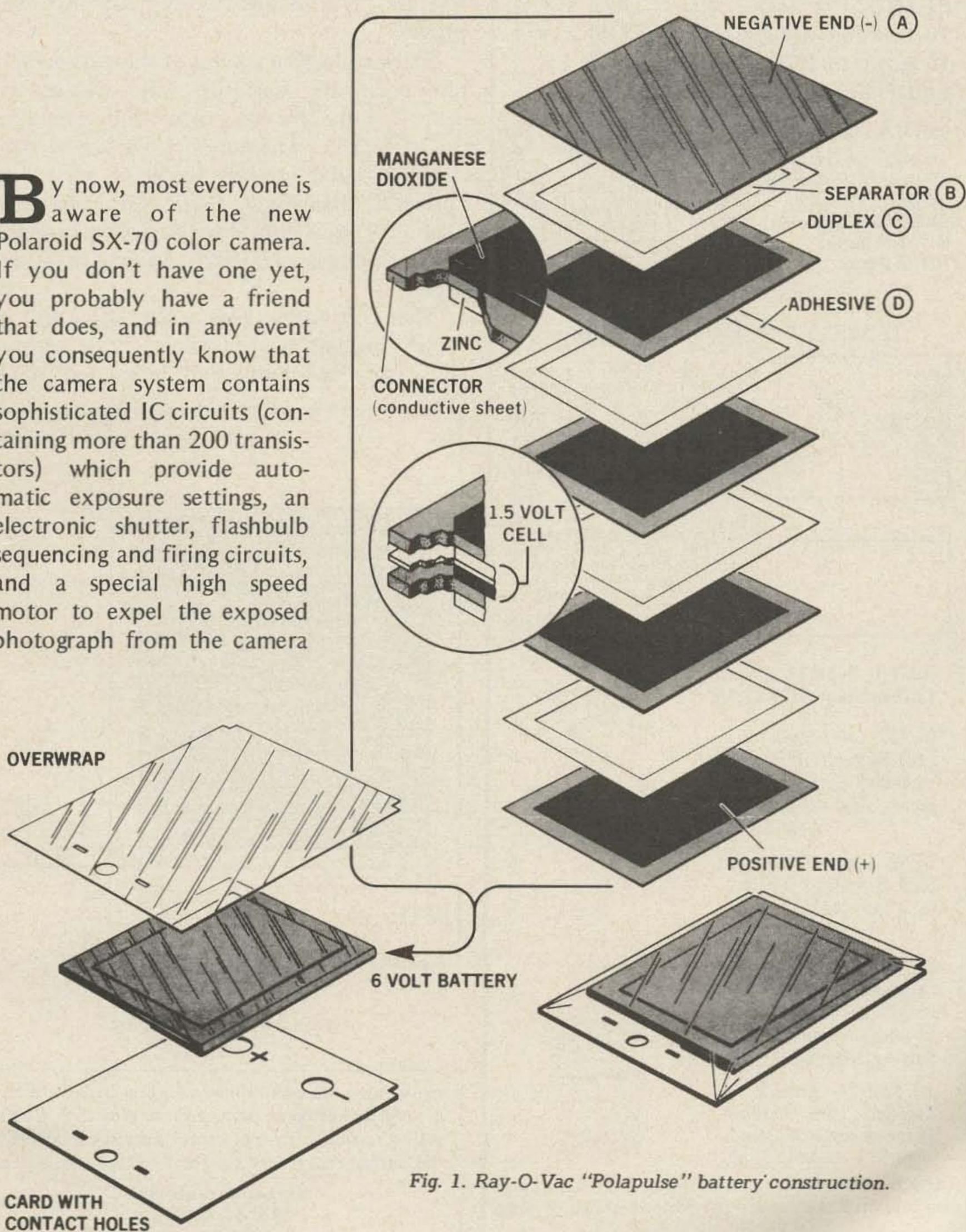


Fig. 1. Ray-O-Vac "Polapulse" battery construction.

GATEWAY ELECTRONICS

8123-25 PAGE BOULEVARD
ST. LOUIS, MISSOURI 63130
(314) 427-6116

THUMBWHEEL SWITCHES

STANDARD SIZE - 0.5 x 2.125 x 1.78

10 position decimal **\$3.00**

10 position BCD & compl. **\$4.00**

End Plates (per pair) **\$1.45**

MINIATURE SIZE - 0.312 x 1.3 x 1.3

10 position decimal **\$2.50**


10 pos. BCD & comp. **\$4.00**

10 pos. BCD only **\$2.75**


End Plates (per pair) **\$1.00**

Divider Plates **\$1.25**

Blank Body **\$.30**

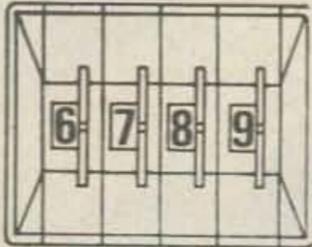


12 Volt 1.5 A. Regulated Supply

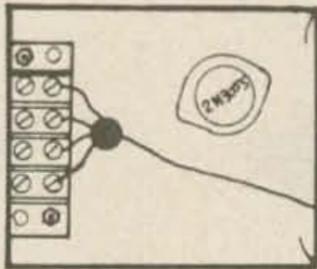

A handy little regulated supply. Voltage adjusts from about 9 to 13 volts. Its short proof and will make an ideal bread-board or general purpose power supply for the bench. At this

price buy two for dual voltage needs. A diagram is included that will make output adjustable from 0 to maximum supply voltage with a pot and a 2N3055.

\$6.00

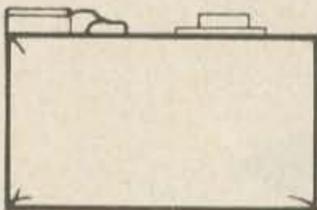




MAN 1- Type 7 Segment LED Readout **NEW \$2.75**

DL707- Later Style 7 Seg. LED Readout- Improved Visibility- Same specs, socket, size, etc. as MAN 1 **NEW \$2.75**

DL62- Larger 7 Segment LED Readout - 0.6 in. - same specs as MAN 1 **NEW \$3.95**

DL33B-3- Triple 7 Segment LED Readout used in calculators W/Built-in magnifier for better clarity. **NEW \$2.95**

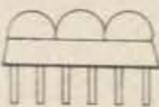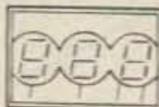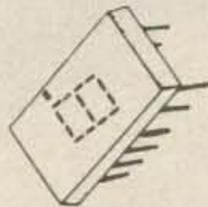DL33B-2- Double 7 Segment LED Readout (same as above W/Minus sign) **NEW \$2.95**



PACKAGE DEAL - 2 DL33B-3 & 1 DL33B-2 will give you an 8 digit readout w/minus sign all 3 - **\$8**

\$5 Minimum Order. Visit us when in St. Louis. Please include sufficient postage.

body. To insure adequate power to perform all of these functions, the Polaroid people took no chances and built an internal battery into each film pack. This means that after only a few seconds use an almost new power source is disposed of! This is more than my frugal "don't throw it away...it may be good for something" glands could tolerate, as a glance at my junk box will prove.

After collecting several of these discarded film packs my curiosity was satisfied by dissecting the plastic holder and removing the battery... whereupon I discovered that it was manufactured by RAY-O-VAC and is known as their model P-70. A note to their Technical Sales and Service Section brought quick response and the following information.

The P-70 battery is a new concept in battery packaging. Four 1.5 V zinc carbon cells in a 3.2 mm thin laminated stack

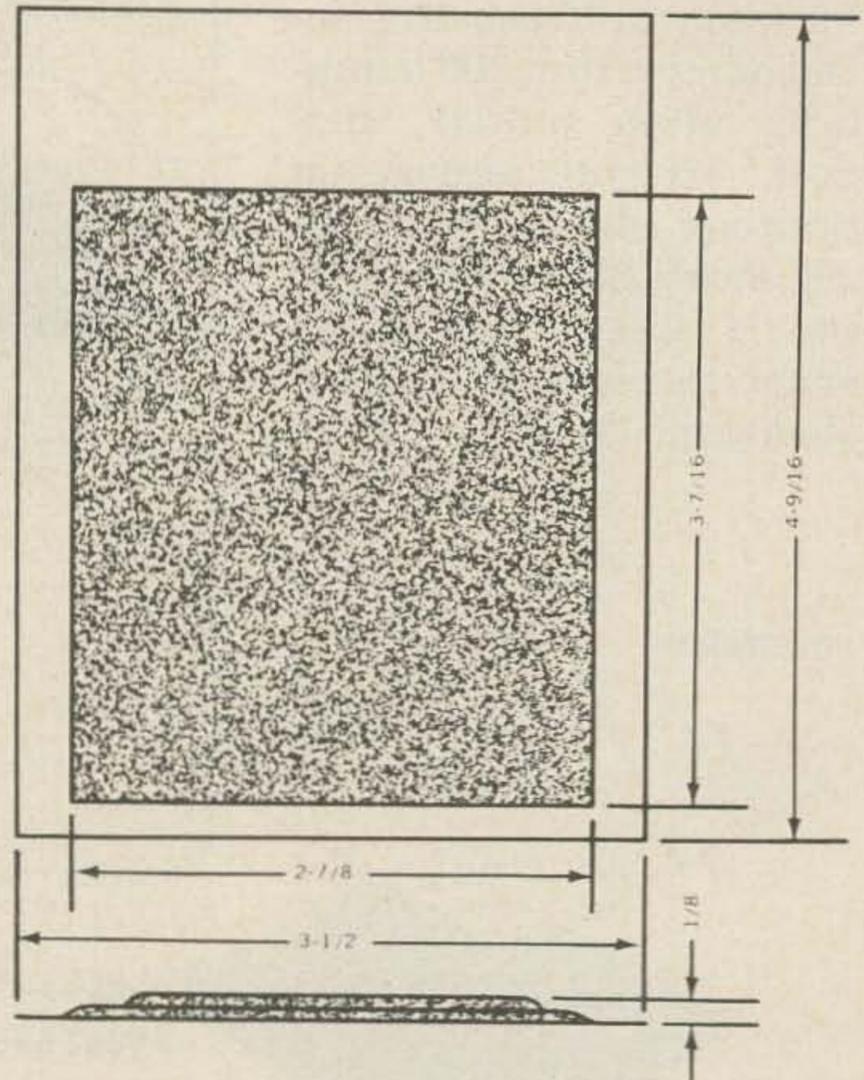


Fig. 2. P-70 dimensions.

How does the possibility of going to hamfests, or any gathering of hams and making over \$100 sound to you? For more information on becoming a local representative for 73 Magazine, write

Marketing Manager
73 MAGAZINE
Peterborough NH 03458

At ICOM
... the benchmark is quality.

IC-21



ALL ICOM RADIOS HAVE

- 5 Helical Resonators
- 0.4UV Sensitivity
- High and Low I.F. Filters
- Extremely Low Spurious TX
- Transmit and Receive Trimmers
- ESP
- 5KHz Freq. Deviation
- "S" Meter

INOUE'S NEW PLL SYNTHESIZED

IC-230



- 24 Channels
- Discriminator Meter
- Wide Range — 144 - 148 MHz + MARS
- SWR Bridge
- AC Supply Built In
- DC Supply
- Modular Construction
- \$429.00

- 5 Channels Included
- 22 Channels Total
- No Relays
- Large Speaker
- Carrier Operated Light

- 67 + Channels (Direct or ± 600 KHz)
- 30 KHz Steps (Optional 15 KHz)
- 146-148 MHz PLL Synthesized
- Modular Construction
- Socket For Tones or Dial
- Digital Readout (No Tuning)
- P.L.L. Lock Indicator
- \$489.00



\$289.00

IC-22



ICOM

IS DISTRIBUTED BY

ICOM WEST
 Suite 232 - Bldg. 2
 300 120th Ave. N.E.
 Bellevue, Wa. 98005
 206-454-2470

ICOM EAST
 13777 N. Central Expwy.
 Suite 501
 Dallas, Tx. 75231
 214-235-0479

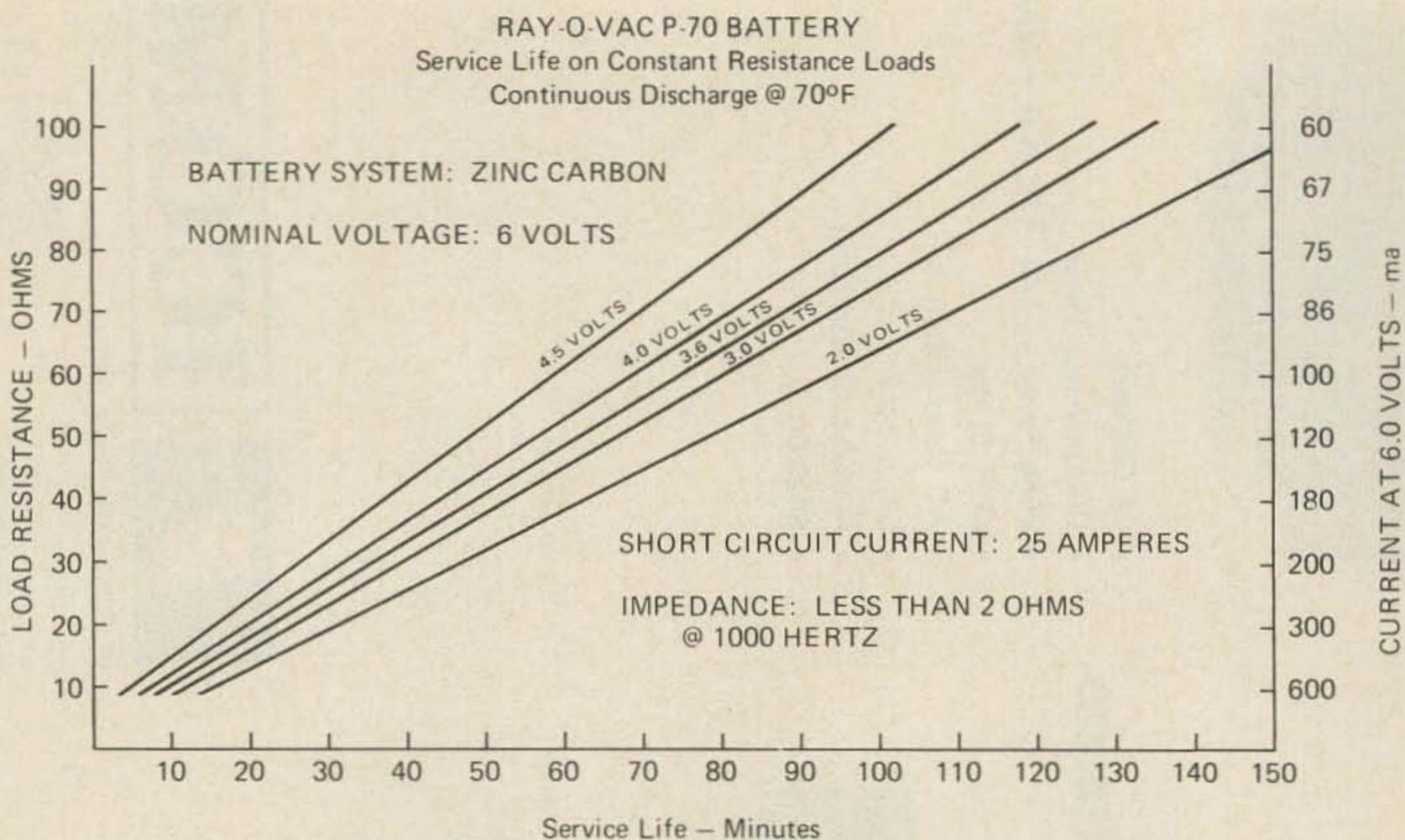


Fig. 3. New battery performance.

produce a 6V battery that is protected by steel and mounted on a card for easy handling. This type of construction provides a large electrode surface area capable of producing high current with a small battery volume. Each individual cell is composed of a top sheet (A) of steel coated with zinc on its underside, a separator (B) and a conductive sheet (C) coated on the top side with manganese dioxide and coated on the bottom with zinc, see Fig. 1. The individual cells are electrically connected by the conductive sheet. When the cells are stacked, an adhesive perimeter (D) on each separator fastens the cells together. The steel top sheet wraps around to the bottom of the stack to permit the minus and positive terminals to be on at the same side. The pack is mounted on a cardboard sheet, insulated and sealed with a clear plastic film overwrap. The overall dimensions are shown in Fig. 2.

What we have to work with is a small, thin, flexible battery capable of producing high current rates for short durations. An application for these batteries which immediately comes to mind is power for touch tone pads. Most pads are designed to operate from 9 to 15V, so two of the P-70 batteries


in series would do the trick. A standard Western Electric pad draws about 12 mA when producing a tone. The power output capabilities for a new battery are shown in Fig. 3. I ran a series of tests with a used pack under a continuous 200 ohm resistive load, while monitoring current and voltage, and observed a nominal 5.8V at 26 mA for several hours. Then the voltage rapidly fell off to about 2V. Some rejuvenation was observed after an overnight rest but the voltage gradually and steadily dropped under load to the point of uselessness. However, with the intermittent type of operation we will be subjecting the battery to it should hold up for weeks.

Stacking several of these battery packages can produce many combinations of desired output voltages and current capabilities to power experimental ICs or other solid state devices where current requirements are only a few mils, or for higher current-short duration applications, such as the aforementioned TT pad.

Well, happy picture taking. . .and save those film packs!

... W3WTO

THE SCOTCH TRANSISTOR

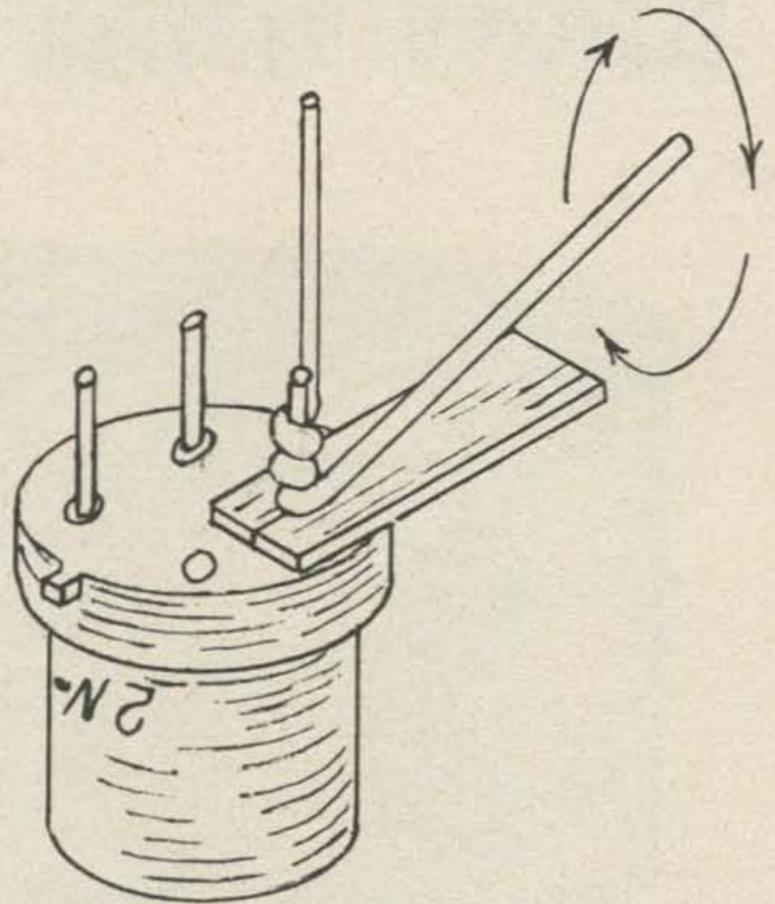

Don't throw away those transistors on printed circuit boards. They can be salvaged at a very low cost. A good transistor can be had for less than a nickel by the method described here.

Some circuit boards are so thin and the leads cut so short, that the removed transistors are nearly useless. I have tried soldering leads to these transistors many ways without too much success. The leads either short to the case after mounting, or come loose when being soldered to the other components.

The method that I have found best is to take a small piece of cardboard and cut it down the middle for about 1/8 or 3/16 of an inch. This cardboard is then slipped onto the transistor lead. This cardboard will, in most instances, block solder from running down the lead into the transistor case. It will also space the new lead from the transistor. The new lead is a piece of 24 gauge tinned wire. The transistor is held upside down in a vise. The cardboard is added to one lead at a time. The tinned wire is started at the bottom of the transistor lead at the surface of the cardboard. A leader of approximately 2 inches is left on to aid in the wrapping of

the tinned wire around the old transistor lead. I have found most transistor leads are long enough to get at least 2 full turns of wire around the lead. Now is the time to solder the transistor lead and the new lead together. Fasten a heat sink to the two inch leader. After the solder has cooled, hold the new lead taut, and twist the 2 inch leader off, using an upward pull. Remove cardboard and repeat for all leads. Inspect work, then cut all leads the same length. To mark the emitter lead, cut it 1/4 inch shorter. After the leads are dressed up, they are ready for potting.

A mini-cube plastic ice tray is used as the mold. The transistors are carefully placed into the ice tray. The epoxy is mixed and poured in. After setting, the new transistors are removed. The new leads can now be handled in the same way as leads on a new transistor. They will now be insulated from the transistor case, and will not affect the old leads, as they are held rigid by the epoxy. The little cubes look nice on a vector board. I was surprised to see just how neat they really looked.

...WA9VFG

THE NEW ITC AR-2000 RECEIVER. IT'S SO SELECTIVE IT DOESN'T KNOW WHAT INTERFERENCE IS.



The AR-2000 is a completely solid-state, dual-channel communications receiver with 0.15 uV sensitivity (10 dB S+N/N) and selectivity that renders it virtually interference-proof (more selective than you ever thought a receiver could be). Blocking, intermodulation, adjacent-channel and crossmodulation rejection characteristics are better than any other receiver on the market and are typically beyond the scope of measurement.

This plus: modular construction; digital frequency readout; all bands (160m-10m) in 1 MHz ranges; two independent channels for dual receive, transceive-plus-receive or split-frequency operation; adjustable IF Passband (to within 100 Hz);

*Warranted to be free from defects in materials and workmanship.

Factory or authorized dealer repairs at no cost to owner for two years from date of purchase.

16-pole filter for over 200 dB skirt selectivity (standard 2.1 kHz BW, shape-factor 1.4:1); adjustable-Q/adjustable-frequency Notch and Peak Filters; adjustable-threshold noise-blanker; Receiver-Incremental-Tuning; and many other features found in no other receiver. Introductory price: \$1,250 with **two-year** warranty.*

The AT-2000 matching transmitter is completely solid-state, provides adjustable output power from 1W to 175W, requires no tuning, can be remotely operated by the AR-2000, has a built-in RF Speech Processor, VOX, Sidetone and Heavy-Duty Power Supply. Introductory price: \$945 with **two-year** warranty.*

**The ITC AR-2000 Receiver and AT-2000 Transmitter—
performance that challenges your imagination.**

INTERNATIONAL TELECOMMUNICATIONS CORP.

P.O. Box 4235, Torrance, Calif. 90510 • (213) 375-9879

POOR MAN'S UNIVERSAL FREQUENCY GENERATOR

John J. Schultz W2EEY
 c/o RLC Inc.
 30 East 42nd Street
 New York NY 10017

As precise frequency control and measurement becomes more and more a part of the amateur radio game, the need develops for test instruments that deliver a wide range of both rf and af signals of high accuracy. It would be ideal if everyone could have a frequency counter and a synthesizer type rf and af generator but that is hardly the case. Most amateurs must utilize their basic station gear along with selected accessory items to test out and adjust equipment. This article describes a very useful accessory item that for a modest cost goes a long way toward having some of the expensive test equipment just mentioned. The item to be described is somewhat like a grid-dip meter in that it is basically a simple type of oscillator but as one gets to know and use it, new uses for it are found and its versatility constantly expands.

Circuit Description

Figure 1 shows the circuit diagram of the test generator. Basically, it consists of a

string of SN7490 decade counters which are used to divide down a selected input signal by a factor of 10 or 2. The input signal can come from a 1 MHz master oscillator, a special crystal oscillator for externally used crystals or from any external sine-wave source. The special crystal oscillator which uses a SN7400 will operate with almost any basic or overtone crystal in the hf range. It can be used for crystals in the low frequency and lower VHF range also by a simple modification. One gate of the SN7400 crystal oscillator is used to drive a LED which will indicate that the crystal is oscillating so it serves as a crystal activity indicator as well. When an external sine-wave source is used, it is first coupled through a SN74121 multivibrator. This stage squares off the sine wave so it can better drive the subsequent frequency divider chain.

The frequency divider chain is fixed, although one could easily switch the individual SN7490 units to divide by different ratios when desired. This should be obvious

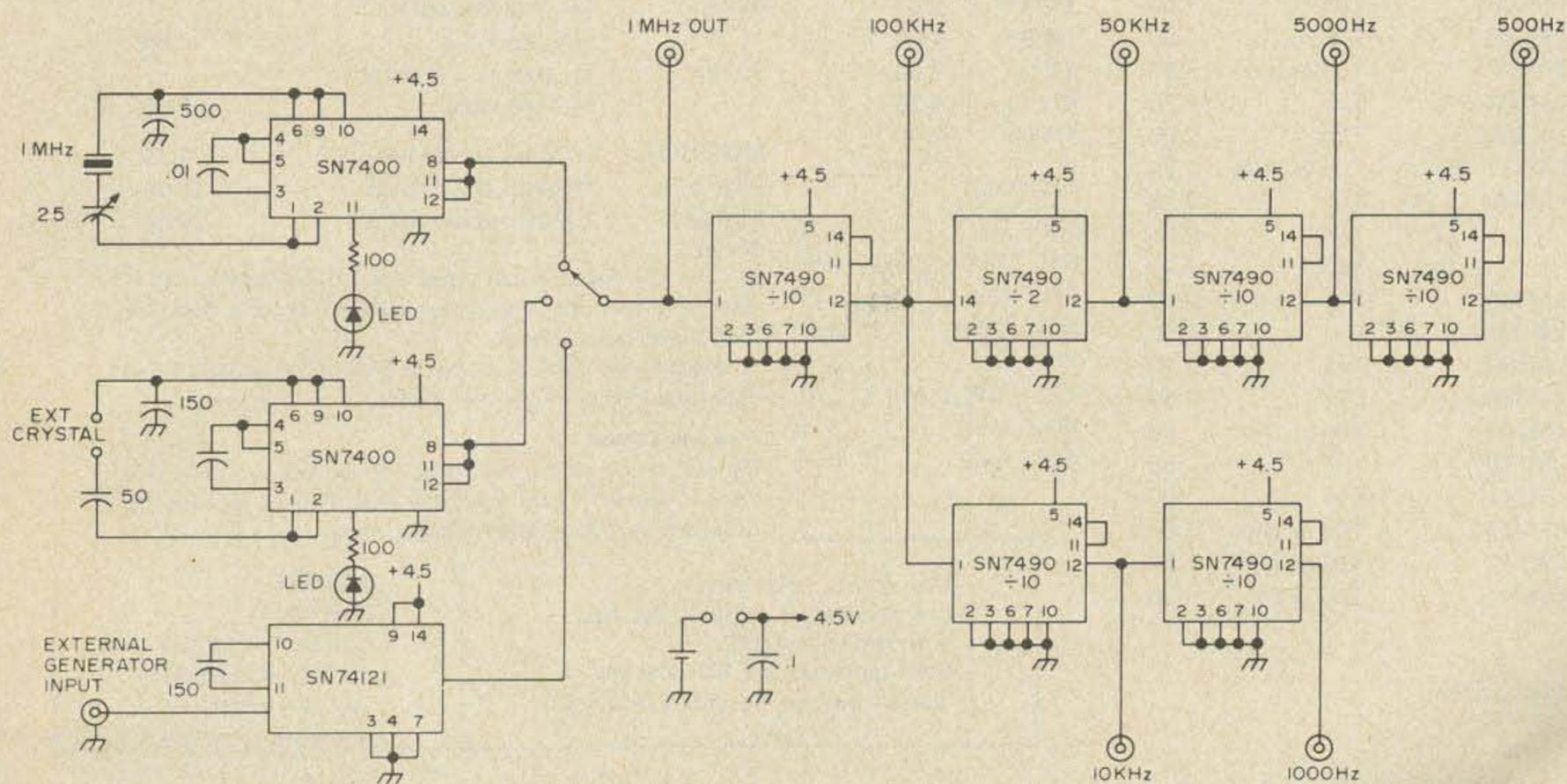


Fig. 1. Diagram of universal frequency generator. Output frequencies shown are for using 1 MHz oscillator.

WEIRNU IN ELECTRONICS AND CHARGING FAIR PRICES FOR GOOD DEVICES

Win up to \$500.00 in cash prizes. —we just bought 80,000 prime house marked devices at a low low price. But OOPS! Somebody goofed. We can't figure out what they are! All we know is that they are Fairchild ECL & that all of them are good. Sooooo we're gonna put all of you hams to work out there with an offer you can't refuse. \$100.00 to the first person sending us information leading to the arrest of our dismay; \$1 per type entry fee covers postage, handling & 5 units to experiment on. type A, type B, type C, type D, type E, try one type! try all types! but go go GOOO—

7400 series b Price Schedule

00	.30	41	1.50	95	1.25	165	3.00
01	.30	42	1.25	96	1.25	166	2.50
02	.30	45	1.25	100	9.99	170	4.25
03	.30	46	2.00	107	.60	173	2.50
04	.30	47	2.00	121	.75	174	3.25
05	.30	48	2.00	122	.90	175	3.50
06	.50	50	.30	123	1.25	176	1.00
07	.70	51	.30	125	.75	177	1.00
08	.30	53	.30	126	.75	180	1.25
09	.30	54	.30	132	4.25	181	6.25
10	.30	60	.30	141	4.50	182	1.25
11	.30	70	.40	145	1.75	184	3.25
12	.70	72	.45	150	3.25	185	3.50
13	1.00	73	.60	151	1.25	190	4.50
16	.70	74	.60	152	4.50	191	5.00
17	.70	75	1.50	153	1.50	192	2.25
20	.30	76	.60	154	2.00	193	2.50
23	.50	83	1.25	155	1.50	194	2.50
25	.50	85	1.50	156	1.50	195	1.25
26	.50	86	.50	157	1.50	196	2.50
27	.80	88	5.00	158	4.50	197	2.50
30	.30	89	4.00	160	2.00	198	4.25
32	.40	90	1.50	161	2.00	199	4.25
37	.50	91	1.50	162	2.00		
38	.60	92	1.25	163	2.00		
40	.30	93	1.25	164	3.00		

Linear Price Schedule

National*

LM301	T05 or mini	.50
LM302	T05	1.00
LM304	T05	1.50
LM305	T05	1.50
LM307	T05 or mini	.50
LM308	T05	1.25
LM309	T03	2.00
LM311	T05 or mini	1.25
LM320	-5.2V T03	2.25
	-12V T03	2.75
	-15V T03	2.25
LM380	Dip	2.00
LM381	Dip	2.50
LM382	Dip	2.50
LM3900	Dip	1.50
LM709	T05 or Dip	.50
LM710	Dip	.50
LM711	Dip	.50
LM723	T05 or Dip	1.00
LM741	T05 or Dip	.50
LM747	T05 or Dip	1.00

*or equivalent

74H00 series

H00	.50
H01	.60
H04	.60
H05	.80
H08	.60
H10	.60
H11	.60
H20	.60
H30	.60
H40	.60
H50	.60
H51	.60
H72	.80
H73	.90
H74	.90
H76	.90
H78	.90
H106	2.00

74S00 series

S00	.80
S03	.80
S04	.80
S10	.80
S11	.80
S15	1.00
S16	1.00
S20	.80
S22	1.00
S64	1.00
S65	1.00
S74	2.00
S153	3.00

74L00 series

L00	.50
L02	.50
L03	.50
L04	.50
L06	.90
L10	.50
L20	.50
L30	.50
L51	.50
L71	.75
L73	.80
L74	.90
L78	.90
L85	2.00
L86	.75
L90	2.00
L93	2.00
L95	1.75

odd devices at low low prices. . . .

81L22	low power 74157	1.00
8130	10-bit comparator	4.00
8288A	presettable divide by 12 counter	2.50
8822A	dual MS jk binary	1.00
8836	Bus receiver (SP380A)	.80
8837	Hex unified bus transceiver	1.75
8838	Quad transceiver	1.50
1303	Stereo preamp	2.25
1304	FM Multiplex Stereo Demod	4.25
1305	FM Multiplex Stereo Demod	5.00
1307	FM Multiplex Stereo Demod	2.25
8095	Tri-state hex buffer	2.00
8096	Tri-state hex inverter	2.00
8097	Tri-state hex buffer (4-2 grouping)	2.00
8098	Tri-state hex inverter (4-2 grouping)	2.00
MM5013N	1024-bit accumulator SR	9.25
P2102	1024-bit static RAM	18.00
N2602B	1024-bit static RAM	15.00

Notes . . .

a. even the factory can't test the 1103 properly, so, if you get a bad one please bear with us, send it back for immediate replacement.

b. 7400 series parts available at 25% of list untested. No guarantee! 10 pcs/type min. order.

Request Orders

We sell many items not listed, & can obtain many not kept in stock. If you need any odd or hard to find ICs, odds are we can get them. Please write.

—spec sheets .25¢ each
 —our complete catalog \$2.00, free with order of \$100.
 —Calif residents add 6% sales tax
 —add \$1 postage on orders under \$10

WEIRNU
 Box 1307
 Colton, CA 92324
 ph # (714) 882-5387
 (ask for FANNIE!)

MTWF 5-8 pm P.S.T.

Satisfaction guaranteed. All items except as noted have been precision tested by the latest equipment. We're so certain you'll keep coming back once you've tried our quality that we make this amazing first order offer: BUY \$100.00 worth of merchandise, choose \$100.00 worth free.

by noting the wiring of the divide by 2 SN7490 with that of the divide by 10 units. However, the variety of frequencies which can be generated then with different input sources becomes confusing and more than would normally be needed.

The fixed divider chain follows the sequence: divide by 10, divide by 2, divide by 10, divide by 10. A separate branch after the first divide by 10 unit goes through two other divide by 10 stages. In the case of the divider chain being driven by the 1 MHz master oscillator, this results in the following output frequencies being simultaneously present: 1 MHz (basic oscillator output), 100 kHz, 50 kHz, 10 kHz, 5000 Hz, 1000 Hz and 500 Hz. With any other frequency input source you can easily calculate what frequency outputs the divider chain will bring in both the rf and af regions. Many surplus crystals will produce interesting frequencies of high stability in the af region that can be used for test purposes.

When using the special crystal oscillator,

tor required in picofarads is 500 divided by the frequency of the crystal in MHz. This value need, however, to be only approximate unless you require an absolutely square wave output from the unit.

When using the multivibrator input about a 1½ to 2V peak input, either sine-wave or approximate square wave is required.

Construction

The whole unit can be constructed on a piece of perforated board about 3 x 2 in. and made completely portable if powered by a 4½V battery (Burgess No.532) or just three D cells in series. This arrangement does not provide the absolutely best stability for the 1 MHz master oscillator but unless you intend to use the unit for marker frequency generation in the VHF range, it is a perfectly satisfactory arrangement. Alternatively, one could power the ICs from any standard 5.5V regulated supply used for IC digital circuitry.

I constructed my unit for battery powered operation and enclosed the unit in

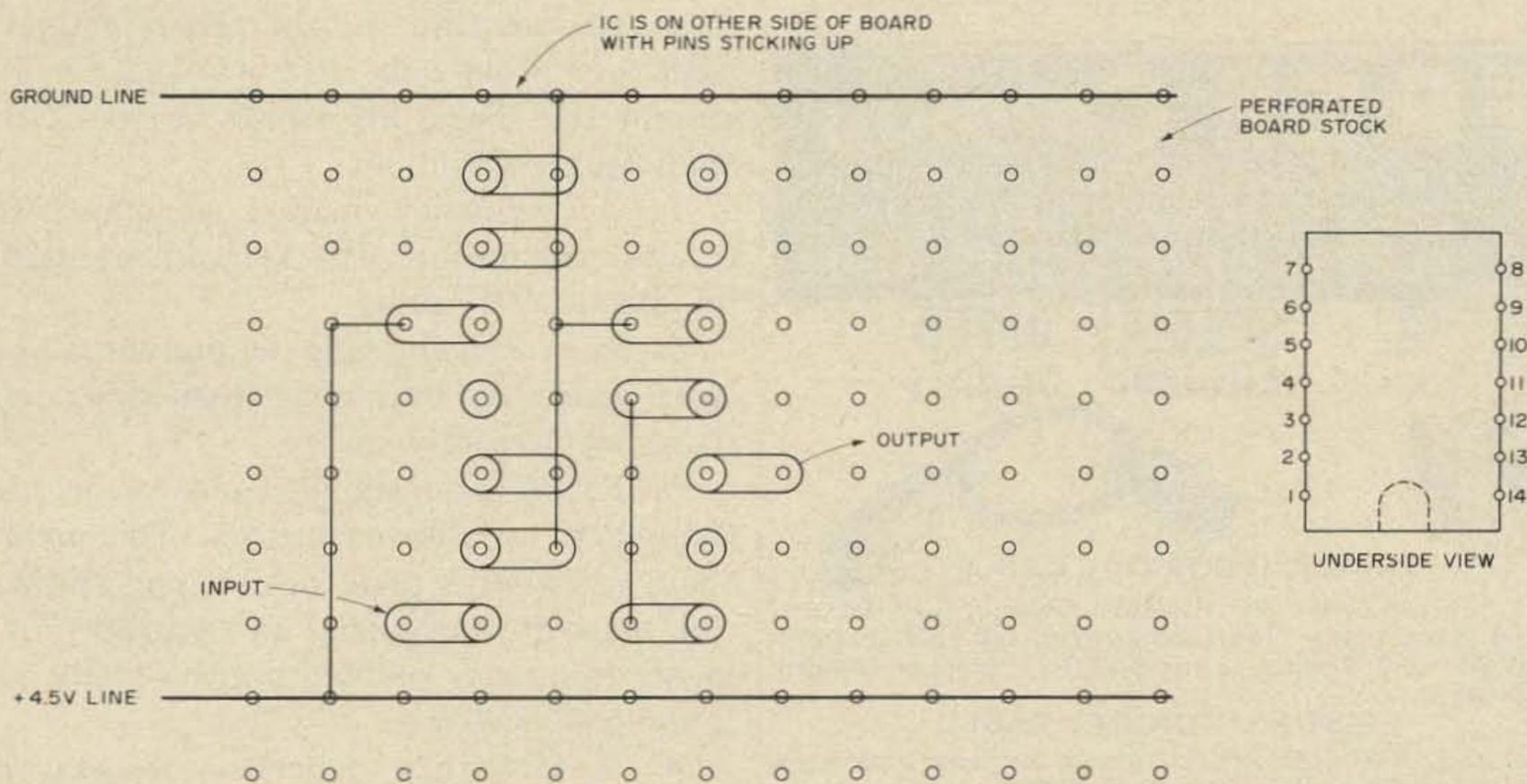


Fig. 2. Perforated board wiring of ICs. One SN 7490 divide by 10 unit is shown wired.

the LED will glow to indicate that oscillation is taking place. As shown with a 150 pF capacitor from one side of the crystal oscillator circuit to ground, the oscillator will work satisfactorily with hf crystals. Its range of oscillation can be extended to lf as well as high frequency overtone crystals by changing this capacitor. The value of capaci-

a small aluminum mini-box. The output of each divider was brought to a pin jack on the front panel of the unit.

One simple way to wire the relatively small number of ICs involved is to purchase perforated board which has hole spacing to fit standard DIP and preferably with a copper pad still left around each hole. The

SLEP ELECTRONICS COMPANY
 NOW SHIPPING NEW BOXED
 1974 MODELS

DRAKE DRAKE DRAKE

- TR-4C TRANSCEIVERS
- R-4C RECEIVERS
- T-4XC TRANSMITTERS
- TR-22, TR-72 FM TRANSCEIVERS
- C-4 STATION CONSOLES
- RV-4C REMOTE VFO, W-4
- WV-4 WATTMETERS
- TV-1000LP LOW PASS FILTERS
- R-4C IF FILTERS
- DC-4 MOBILE POWER SUPPLIES

Top trades given on Collins, Drake, Swan, Hammarlund and Military Surplus Airborne, Ground and Test Equipment.

Write or phone today Bill Slep
 (704) 524-7519.


Slep Electronics Co.

Highway 441, Franklin South
 P.O. Box 100
 Otto, North Carolina 28763

FREE Catalog

OF THE WORLD'S FINEST
 GOVERNMENT SURPLUS
 ELECTRONIC EQUIPMENT

SPECIAL OFFER
Limited Supply

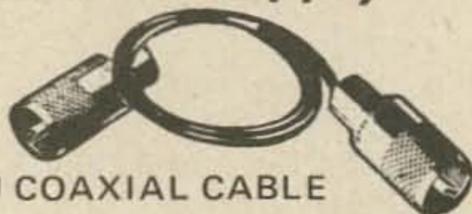

RG-8 A/U COAXIAL CABLE

52 ohm. Two (2) PL-259 Coaxial Connectors included. Used, Good Condition: 68 Foot Length \$5.50 - 50 Foot Length \$4.50 - 25 Foot Length \$2.50

RG-54 A/U COAXIAL CABLE

58 ohm .250 O.D. Polyethylene. Unused. 370 Foot Roll \$10.00 - 185 Foot Roll \$6.00

Prices are F.O.B., Lima, Ohio • Order Dept. 73
SEND TODAY FOR BIG FREE CATALOG !

FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

Isolated - Pad - Drill - Mill


Precision circuit board construction without etching. Fits hand drill, electric drill. Simple, fast, economical, safe.
 Sizes .20, .15, .10 inch dia.
 With replaceable #60 drill.

\$6.95 ea.

Calif. residents add 5%.

A F STAHLER Co

P.O. BOX 354 CUPERTINO, CALIF 95014

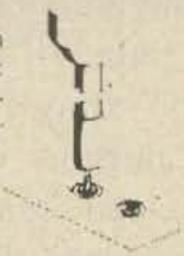

ICs are then placed on the board and the appropriate pins which either go to ground or to the 4.5V line bent in different directions. The ground line is run along one side of the IC and the 4.5V line along the other side and bare wire used to connect the appropriate pins to either line. Figure 2, illustrates the wiring for one of the divide by 10 ICs. When one starts this process on the board, it will be surprising how fast the wiring is completed. Individual insulated wire jumpers are used to make the input/output connections between ICs. The wiring is not critical and using a receiver to hear the markers, or an audio amplifier for the lower frequency outputs, one should be able to determine quickly if the circuit is working. The frequency of the 1 MHz master oscillator may be brought exactly on frequency using the 25 pF trimmer in the circuit and checking against WWV with a harmonic of the oscillator or by using a counter.

Applications

As I mentioned before, the applications that you can find for the generator really begin to unfold only after you have had it around the shack for awhile. Some of the applications would be:

1. A frequency marker generator for receiver calibration. The markers are usable up into the VHF range.
2. To extend the range of present rf or af signal generators into lower frequency ranges than they presently cover.
3. To perform stability checks on high frequency variable oscillators. The divider chain will always perform precisely and you can monitor the change in frequency of a higher frequency oscillator with a stable low frequency receiver.
4. A frequency generator to generate precise rf or af square wave signals at any frequency desired by choosing the proper crystal.
5. A crystal activity checker.
6. By taking two or more of the simultaneous outputs together via mixing diodes and a series tuned circuit resonant at the desired frequency, you can also mix the divider outputs to generate a variety of intermediate frequency outputs.

...W2EEY

UNIVERSAL AFSK GENERATOR

This article describes an AFSK tone generator which should interest any RTTY operator. It will work without modification in almost any local loop or with any terminal unit.

I have always felt that the two greatest shortcomings of most AFSK circuits have been cumbersome methods for adjustment of the tones to the correct frequencies and difficulty in adapting a particular circuit to an existing terminal unit. While some of the circuits based upon the Signetics 566 function generator have proved easy to adjust, the loop interface problems still exist. Many

of these circuits do not produce a sinusoidal output waveform. This can mean severe adjacent channel interference if the transmitter audio bandpass allows transmission of tone harmonics. I believe that this circuit solves all of these problems and in addition is simple to construct. Circuit features include:

1. Plug-in operation in any RTTY loop independent of loop polarity or grounding.
2. Independent adjustments for each tone.
3. Constant amplitude sine wave output.
4. Excellent tone frequency stability.

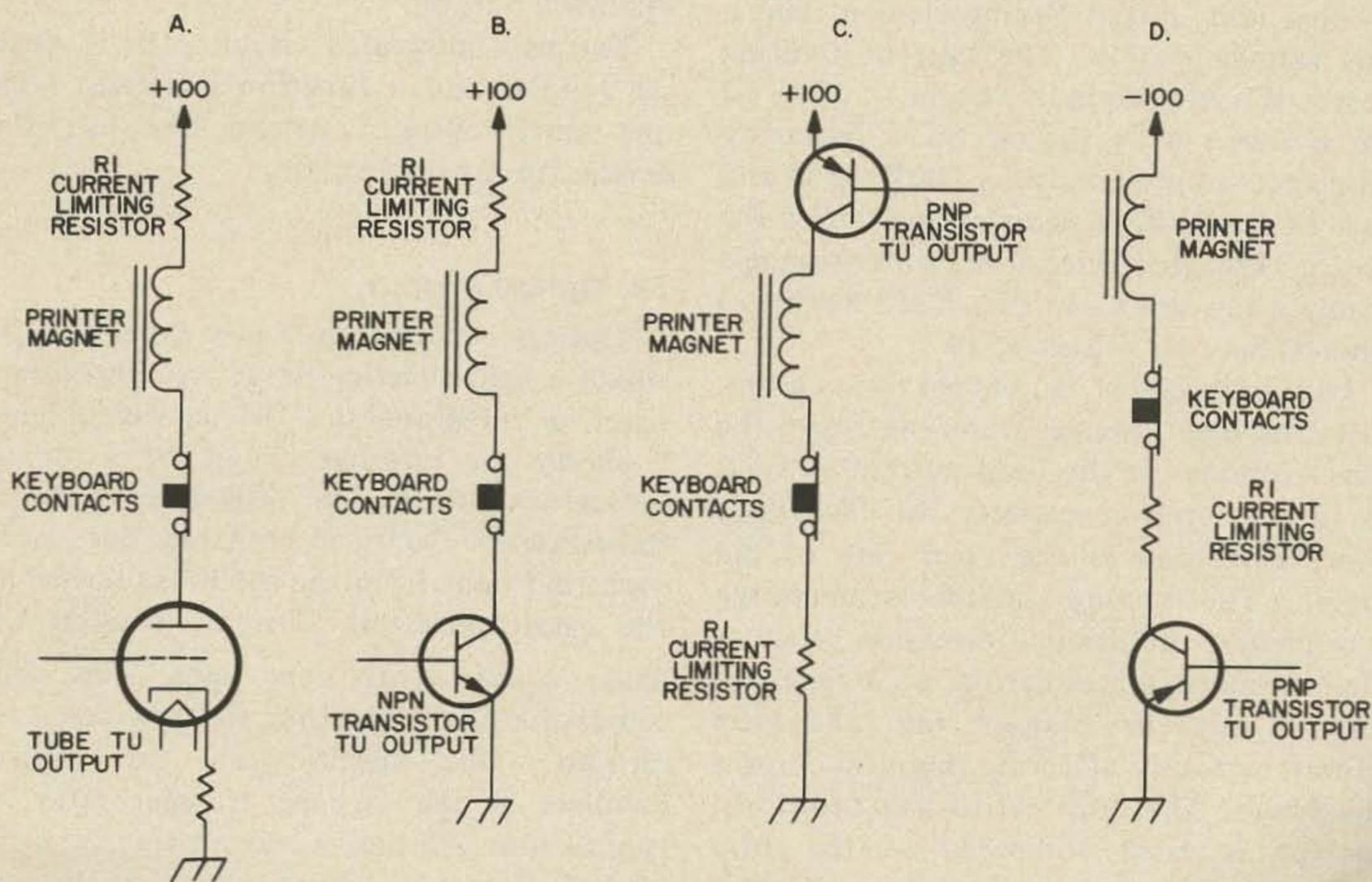


Fig. 1. Typical RTTY loop circuit: a - TU with tube output and positive loop supply. b - TU with NPN transistor output and positive loop supply. c - TU with PNP transistor output and positive loop supply. d - TU with PNP transistor output and negative loop supply.



Front view of the AFSK generator. Controls include the shift selector switch and the power switch. The loop input jack is isolated from ground with shoulder washers.

5. 850 or 170 Hz shift operation with narrow shift ID.
6. Output adjustable from 20 millivolts to 2 volts peak to peak.

The RTTY Loop-AFSK Oscillator Interface

Most amateur RTTY loops are some form of Fig. 1. The machine keyboards and printer magnets are placed in series with the terminal unit output keying element and a high voltage supply. The current limiting resistor R1 sets the loop current to 20 or 60 mA as required by the machines. Normally the power supply voltage is 100V or so and most of the voltage drop occurs across the resistor. The drop across the printer magnets is only a few volts and the closed keyboard contacts have no voltage at all.

This arrangement is used for two reasons. First, the high voltage source decreases the time required for the loop current to build up in the printer magnets for each code pulse. This reduces the error rate of the printer. The second reason is operating convenience. Additional machines such as other printers, reperforators, or a tape distributor may be plugged into the loop without seriously affecting the loop current adjustment. The drop across any additional machine is small compared to the drop across R1 and therefore the loop current change is negligible.

The high voltage loop is all good and well for the machines themselves, but can cause

real difficulty when an AFSK oscillator containing tender semiconductors must somehow be connected into the system. Further, each fellow's station is different. Depending on the particular operator, there may be one or more local loops and several terminal units. It is not uncommon to find that the serious RTTY operator has a Mark IV, a Mainline, an ST-6, plus some old military gadget such as a CV-57... all operational and powering one or more machine loops. Because of the differences in the various pieces of equipment, the AFSK oscillator design must contend with systems in which the loop voltage may be of either polarity. The machine end of the loop may or may not be ground referenced, and the loop supply may be anything from 24 to 200V. Thus, a special interface circuit is required to allow operation of the typical AFSK oscillator with each terminal unit.

Having encountered all of these problems when hooking up RTTY systems for myself and for friends, I decided to design a circuit which, like any other piece of RTTY equipment, just plugs into the loop and works. In addition I wanted the circuit to have good frequency stability and a constant amplitude sine wave output.

Two new integrated circuits, the IC optical coupler and a function generator with sine wave output, seemed like just the devices for my application.

The Optical Coupler

Optical couplers are a new type of IC in which a light-emitting diode and phototransistor are integrated in a DIP package. Figure 2 shows the internal circuit of a typical optical coupler IC. The LED and the phototransistor are electrically isolated, but placed such that light from the diode is focused on the phototransistor. Current through the diode causes it to emit light. This light causes the phototransistor to draw collector current. One specification for optical couplers is the current transfer ratio. A typical unit will have a current transfer ratio of 60%. For every 10 mA of current through the LED 6 mA will flow from the emitter to collector of the phototransistor. Couplers are also specified for the maximum voltage

allowed between the LED and phototransistor; 1000V is not unusual. The optical coupler is the ideal device for coupling current pulses from the RTTY loop to the AFSK oscillator without any electrical connection between the two. All voltage, polarity, and grounding problems are eliminated with this simple method.

The Intersil 8038 Function Generator

The tone generator portion of the AFSK oscillator uses the new 8038 function generator IC from the Intersil Corporation.

Operation of this circuit is similar to the Signetics 566 function generator which has been used in previous amateur AFSK circuits. There is one important difference, in addition to the triangle and square wave outputs obtainable from other circuits, the 8038 also produces a *sine* wave output.


The basic RC oscillator portion of the chip generates a triangular wave form. This is transformed into a sine wave by means of a triangle-to-sine converter integrated onto the same chip. Special trimming adjustments are provided so that the distortion may be reduced by optimization of the converter circuit. Harmonic distortion is about 5% without trimming. Careful adjustment of all of the optional controls will reduce this to less than 1%.

If all of the trimming pots are not used, only three external components are required to make a basic voltage controlled oscillator. The VCO control range is such that a frequency shift of up to 100:1 may be obtained by changing the control voltage input. The output amplitude remains constant as the frequency is shifted.

The chip is available in six versions which are graded on the basis of frequency stability and operating temperature range. The 8038BC used here has a maximum drift of 100 ppm/°C and is usable from 0 to 70°C. This version costs about \$8.40 in single quantities.

AFSK Generator Circuit

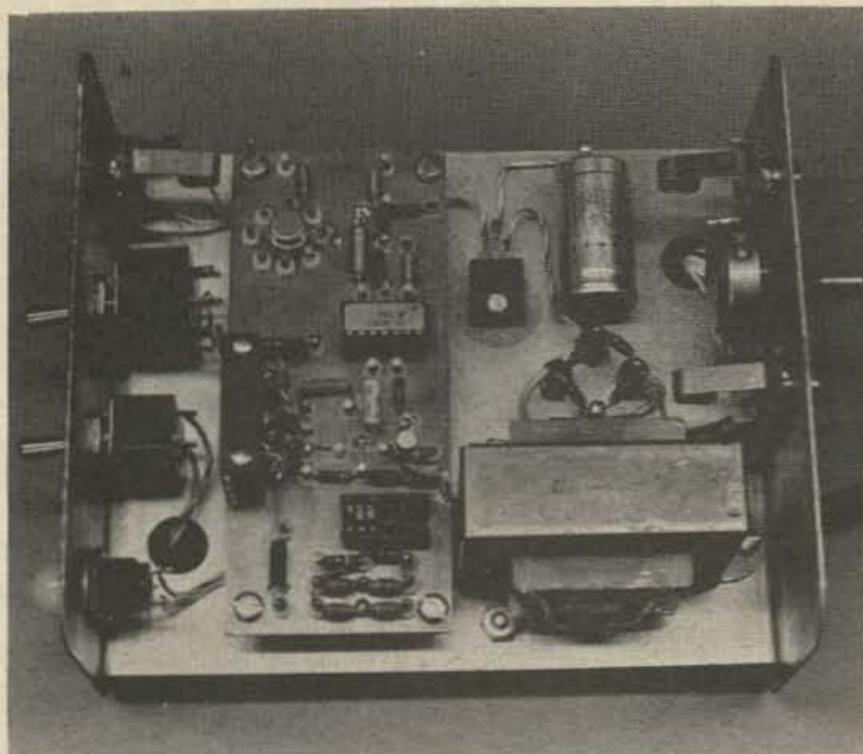The AFSK generator circuit is shown in Fig. 3. It is connected into the RTTY loop via a phone jack. In order to make the



Interior view of the AFSK generator. The tone frequency adjustment pots are positioned so that they may be adjusted through the vent holes in the side of the case. The tone output and narrow shift key jacks located on the rear panel with the tone level adjustment pot.

circuit truly independent of loop polarity, the current first flows through a bridge rectifier consisting of CR1-CR4 and then through 6V zener diode CR5. The bridge supplies the zener with current of the proper polarity such that a constant voltage drop occurs across the zener which is independent of both loop current and loop polarity. A $\frac{3}{4}$ W zener is used so that the circuit will operate with loop currents from 10 to 100 mA without damage. The bridge-zener diode combination then drives the optical coupler from an essentially constant voltage source.

The optical coupler is a Motorola MOC 1003 and is operated at an input current to the LED of 10 mA. This is set by R5. The phototransistor or output side of the coupler is grounded to the AFSK generator while the entire input circuit consisting of the bridge, zener and the LED are floating. The voltage difference between the loop and the AFSK circuit can be up to 500V before the coupler would be damaged.

The phototransistor drives the tone generator circuit via Q1 which operates as logic inverter to cause the frequency shift to be in the correct direction. Normally, the MARK (or closed loop) tone is 2125 Hz and the SPACE (or open loop) tone is either 2295 or 2975 Hz. The frequency shift is upward when the loop current is broken or

K-ENTERPRISES



PRESCALER MODEL PD-301

\$55.50 plus \$1.50 postage

Model PD 301 is a 300 MHz prescaler designed to extend the range of your counter ten times. This prescaler has a built-in preamp with a sensitivity of 50 mV at 150 MHz, 100 mV at 260 MHz, 175 mV at 300 MHz. The 95H90 scaler is rated at 320 MHz. To insure enough drive for all counters, a post amp. was built-in. The preamp has a self contained power supply regulated at 5.2V \pm .08%. (Input 50 Ohms, Output Hi Z)

All prescalers are shipped in a 4" by 4" by 1 1/2" cabinet. All are wired and calibrated.

K-ENTERPRISES

1401 NORTH TUCKER
SHAWNEE, OK 74801
405-273-1598

ECM 5A FM Modulation Meter

**NEW
FOR 74**

- Reads 0-15 kHz
- Operates 30-500 MHz
- Crystal controlled for fast and easy operation
- Peak reading
- Accurate within 1 kHz at 15 kHz



Only \$85.00

Phone or write "Skip" W9HAK for complete information Dial 812-476-2121 *less batteries/crystals*

Order Info: Send check or money order for \$85.00 plus \$1.50 for shipping. Indiana residents add 4% sales tax. Crystals for 146.94 MHz at \$3.95 each. All other freqs: \$7.10 each.

GIVE YOUR P/C BOARDS THE PROFESSIONAL TOUCH!

Professional plating solution - Plate your p/c boards with a shiny coating of tin and lead. Used by major manufacturers. Easy to use. Enough to plate 438 sq. in. only \$3.50.*

Professional cleaning solution - Solder flux left on your completed p/c boards is unsightly. Wash away excess flux, grease, wax, etc. Completely safe. 16 oz. bottle, at least a one year supply only \$3.50.*

*SAVE S S S S - Order more than one and deduct 50¢ from each. NO LIMIT.

TRY THESE ONE EVENING PROJECTS FOR FUN!

• **ECM-100 Module Kit**
100 kHz crystal oscillator with super harmonic intensifier produces useful harmonics to 500 MHz. Makes excellent frequency standard or clock for digital projects. TTL compatible. Complete kit with crystal \$14.95, wired and tested \$19.95

• **ECM-105 Power Supply Module Kit**
5 volt, 1 amp regulated power supply module with automatic current limiting and thermal shutdown protection. Complete kit \$12.95, wired and tested \$15.95

ORDER INFO FOR CHEMICALS AND KITS: ADD \$1 for shipping
SATISFACTION GUARANTEED

ECM

ECM Corporation
412 N. Weinbach Ave.
Evansville, Indiana 47711

keyed by the keyboard pulses. An upward frequency deviation is obtained from the VCO chip by decreasing the control voltage input at pin 8. This is done in the following manner: When the machine is at rest, loop current flows and the LED in the coupler is driven on. The light from the LED causes the phototransistor to be driven into saturation such that the collector-to-emitter voltage drop is about 0.5V. Q1 is turned off because its only source of base drive is via the 33K resistor, R6, and about 1.4V are required to overcome the forward drop of CR6 plus the turn-on threshold of Q1 itself. Because Q1 is off, the control voltage input to the tone generator IC is determined only by the voltage divider of which resistor R1 is

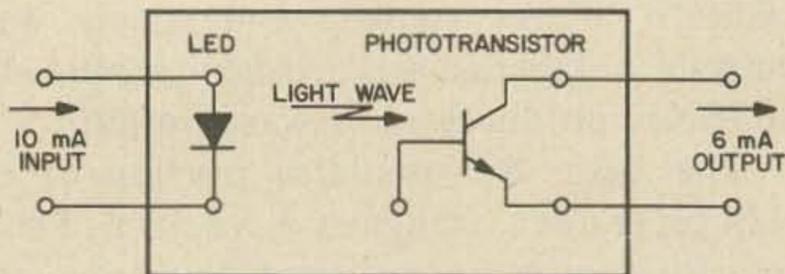


Fig. 2. Internal circuit of optical coupler IC. The input and output devices are completely isolated from each other. 10 mA through the light emitting diode will produce a current flow of about 6 mA from collector to emitter of the phototransistor.

a part. R1 sets the MARK frequency to 2125 Hz.

Each machine code pulse reduces the loop current to zero. The LED no longer has a source of current so the phototransistor in the coupler no longer conducts. The collector voltage rises until base current flows into Q1 causing it to saturate hard; the collector-to-emitter drop is less than 0.3V. The collector current for Q1 is obtained from the frequency setting pot R1 via resistors R3 or R4. This pulls down the voltage at pin 8 of the function generator IC and causes the frequency to shift upward. Switch S1 selects either R3 and its associated fixed resistor for 850 Hz frequency shift or R4 for 170 Hz shift.

Adjustment of the 100 cycle shift for CW ID is provided by R2, which is switched to ground by the key jack.

The basic frequency range of the function generator IC is set by R7 and C1. Other

INCLUDED WITH EACH GTX

At No Extra Charge

... are quality and features that can be derived only from considerable experience.

What Experience?

The experience of producing outstanding 2-Way **Land Mobile** business radios.

The experience of manufacturing FCC Type-Accepted VHF-FM **Marine** radio-telephones.

The experience of building TSO'd **Avionics** for General Aviation.

What Quality?

The quality that comes from working within necessarily high engineering and production standards.

The quality that results from applying Avionics and Marine Q.C. specifications to each GTX.

The quality that comes from manufacturing in a U.S. Government inspected facility.

What Features?

Higher RF output than other radios in the price range.

One-watt switch for economical repeater operation.

A clean layout that's easy to maintain (and modify).

A painfully thorough Owner's Manual that gives you answers instead of leaving you with more questions.

And lots more.

Please write for additional information and specifications, or . . .

made in U.S.A.



SEE THE GTX's

AT YOUR LOCAL AMATEUR DEALER

SOMETIME THIS WEEK

General Aviation Electronics, Inc., 4141 Kingman Drive, Indianapolis, Indiana 46226



GTX-600
6-Meter FM

\$309.95
(Incl. 52.525 MHz)



GTX-100
1 1/4-Meter FM

\$309.95
(Incl. 223.5 MHz)



GLH-100
P.A./Siren

\$159.95
(horn optional)




GTX-200
2-Meter FM

\$299.95
(Incl. 146.94 MHz)



GTX-10
2-Meter FM

\$239.95
(Incl. 146.94 MHz)

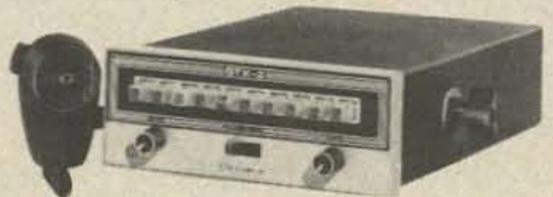

GTX-2
2-Meter FM

\$299.95
(Incl. 146.94 MHz)


values may be used. The sine wave output terminal of the chip is pin 2. The triangle is present across C1 at pin 10. The sine wave output is AC coupled to the output level adjustment pot, R8, and then to the output buffer amplifier which is a 741 operational amplifier. The 82K resistor, R9, is used to trim the sine converter in the chip for lowest distortion and is a nominal value.

The level set pot, R8, is 250K because the sine converter should not be operated into less than 100K if lowest distortion is to be obtained.

The output buffer, IC2, is operated from a single polarity supply so the inputs must be biased between the supply voltages. R10 and R11 accomplish this for the non-inverting input at pin 3 while the inverting input, pin 2, is biased with feedback from the output at pin 6. This is a unity gain buffer connection which enables the tone generator to drive loads of less than 1K. The output voltage may be adjusted from 20 mV peak to peak to 2V peak to peak. Inclusion of the buffer is a bit of a luxury, but it does assure that the unit may be used with just about any transmitter and the low impedance output is nice if a long cable must be driven.

Power Supply

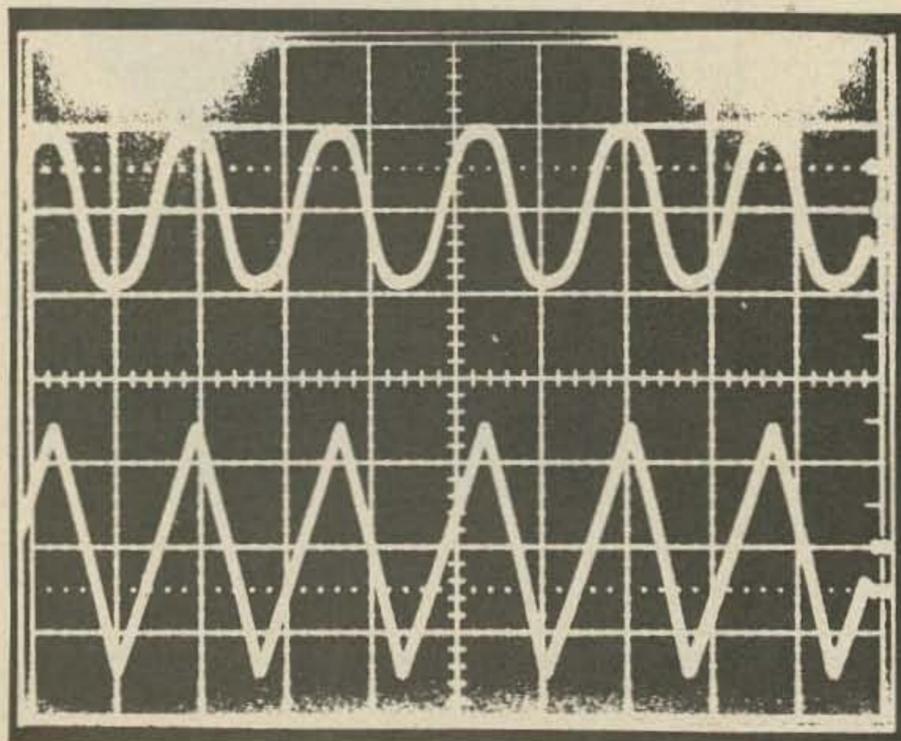The power supply section of the AFSK generator is conventional with the exception



Function generator waveforms. The bottom trace is the triangle wave generated by the RC oscillator portion of the 8038 function generator. The upper trace shows the sine wave obtained from the triangle to sine converter without optimization of the external trimming adjustments.

of the voltage regulator. The transformer and bridge provide about 24V unregulated across the filter capacitor. The regulator is a new single voltage regulator IC from Motorola. This chip, type MC7818CP, is a fixed 18V regulator capable of up to one ampere of output current. It is one of a series of low cost regulators available in standard voltages such as 5, 12, 15, etc. Only three connections are required: input, ground and output. A bypass at the input is a good idea if the lead from the rectifier filter capacitor is long. While the one amp capability of the supply is much more than this circuit required, the ease of application and good performance of the regulator more than justified its use. Particularly since it costs less than \$2!

Construction

I intended this circuit to be a stand-alone unit which could be used with any terminal unit or local loop. Consequently, it is packaged in a small sheet metal case and has its own ac power supply. Others may wish to build it into an existing system from which power may be obtained. Anything from +15 to +20V regulated will work.

The majority of the circuitry is constructed on a small PC card sub-chassis which may be seen in the photograph of the interior. The most frequently used inputs and controls are located on the front panel and include the loop input jack, the shift selector switch, the ac power switch, and a pilot light. Rear panel controls include the narrow shift ID keying jack, the tone output jack, and the tone output level adjustment pot. Be sure to isolate the loop input jack from ground with insulated washers! The power supply is located on the main chassis.

Care should be taken in installation of the regulator IC in order to assure that it is not shorted to the chassis by the mounting screw or a sheet metal burr.

Starting from the bottom of the card, components are arranged in the following order: First is the input bridge rectifier and the zener diode. Just above is a DIP socket containing the MOC 1003 optical coupler which is in a 6 pin package. The pins are counted around the package starting with

Morse and RTTY from one keyboard?



Meet the two and only.

The HAL DKB-2010 Dual Mode keyboard is one of the most sophisticated products ever offered to the radio amateur. It's an all solid state keyboard that allows you to send either RTTY or CW — with more ease, more versatility than anything you've ever seen before.

In the RTTY mode, you can transmit at standard data rates of 60, 66, 75 or 100 WPM, as well as an optional 132 WPM, 100 baud. In addition to the complete alphanumeric keys, you get 17 punctuation marks, 3 carriage control keys, 2 shift keys, a break key, 2 three-character function keys, a "DE-call letters" key and a "Quick brown fox . . ." test key.

In the CW mode, you can send at speeds anywhere between 8 WPM and 60 WPM. You can also adjust dot-to-space weight ratios to your liking. For CW, you have all alphanumeric keys, plus 11 punctuation marks, 5 standard double-character keys, 2 shift keys, a break-for-tuning key, error key, "DE-call letters" key, plus

2 three-character function keys. Output interfacing is compatible with cathode keying or grid-block keying. A side tone oscillator and built-in speaker allow you to monitor your signal — with adjustable volume and pitch controls.

The DKB-2010 also has a three-character memory buffer which operates in either the RTTY or CW mode, allowing you to burst type ahead without losing characters. A 64-character memory buffer is also available as an option. Key function logic in either mode is governed by LSI/MOS circuitry. All key switches are computer grade.

The DKB-2010 is available assembled or in kit form. Should you choose the kit, you'll find construction easy — the unit consists of three assemblies: power supply board, logic PC board, keyswitch PC board, and pre-assembled wiring harness.

Any way you look at it — as an easy-to-build kit, a complete assembly, as a CW keyboard, or an RTTY keyboard, the HAL

DKB-2010 is a real breakthrough for every amateur. It adds a whole new dimension to the exciting world of amateur radio. Once you've used the DKB-2010, you'll wonder how you ever got along without it!

Prices: \$425 Assembled;
\$325 Kit



HAL Communications Corp.
Box 365, Urbana, Ill. 61801
Telephone: (217) 359-7373

- Enclosed is \$ _____ (Assembled)
\$ _____ (Kit)
Call letters _____
- Charge Master Charge # _____
- Charge BankAmericard # _____
M/C Interbank # _____
Card Exp. date _____
- Please send me the HAL catalog.

Name _____


Address _____

City/State/Zip _____

All prices include U.S.A. shipping.
Add \$10 for air shipment.
Illinois res. add 5% sales tax.

NEW! Build and test circuits as fast as you can think! No soldering or patch cords!

Four new Continental Specialties Proto Boards let you make all circuit and power interconnections with common #22 AWG solid hook-up wire, while power distribution buses make wiring a snap. Aluminum base plates offer solid work surfaces and perfect ground plane. Rubber feet prevent scratching. Each Proto Board features one or more 5-way binding posts to tie into system or power supply gnd. All are compatible with ICs (digital or linear), in TO5s, DIP packs and discrete components. Each is completely assembled, ready-to-use.

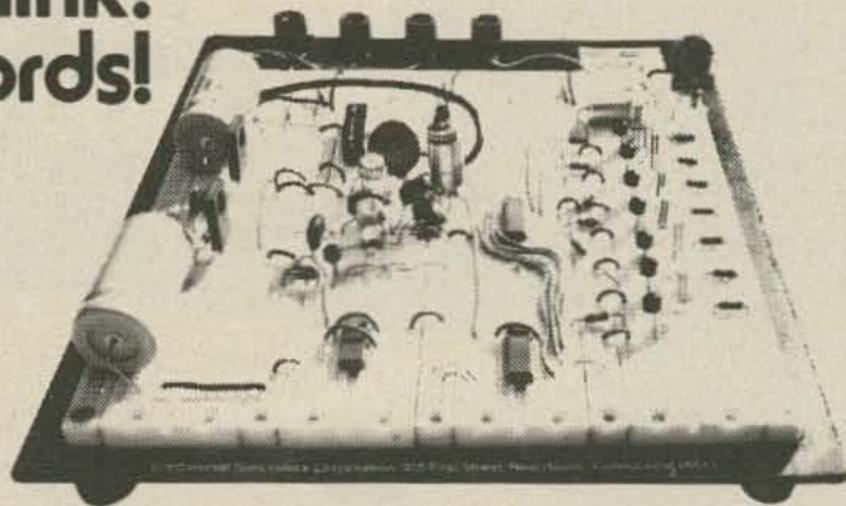

Proto Board Model No.	14 Pin DIP Capacity	Size (L"xW")	Price (U.S. only)
101	10	5.8"x4.5"	\$29.95
102	12	7.0"x4.5"	\$39.95
103	24	9.0"x6.0"	\$59.95
104	32	9.5"x8.0"	\$79.95

Order today — or send for free selection guide, with applications, photos, specs and more.




Continental Specialties Corp.


325 East St., Box 1942
New Haven, CT 06509
Telephone (203) 624-3103

CANADA: Available thru Len Finkler, Ltd., Downsview, Ontario

PAT. PENDING

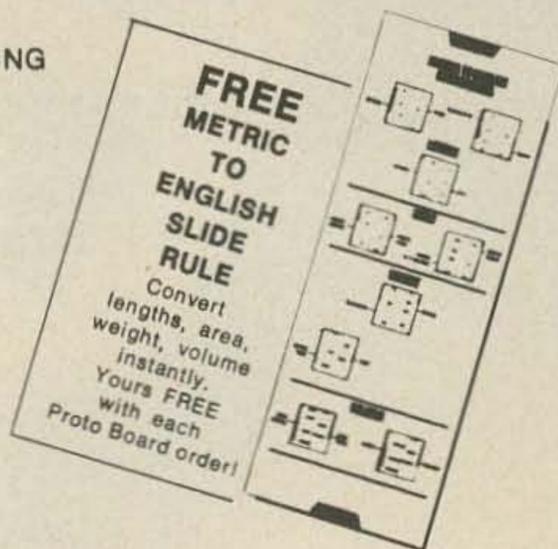

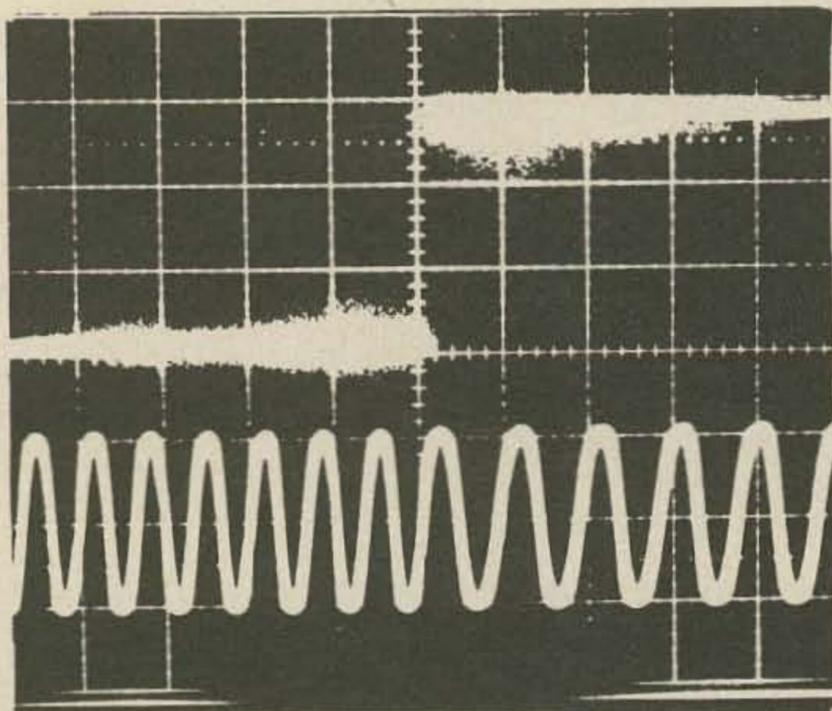pin 1 at the index dot and are sequential as in the case of a standard 14 pin package. That is, they go 1 to 3 down one side, then jump across to pin 4 through 6 going back up the other side. Q1 is located just above



Frequency shift waveforms. Top trace shows input current waveform switching from SPACE to MARK. Bottom trace shows AFSK generator tone output switching from 2975 to 2125 Hz. No transients are present and the amplitude remains constant. Output is 2V peak to peak.

the coupler socket while the frequency adjustment pots are just to the left of Q1.

All of the resistors associated with the frequency adjustments are stable metal film types such as the MIL RN60 series. Conventional carbons may be used but the stability just won't be as good.

I used surplus wirewound trimmer pots for the frequency adjustments. The 20 turn resolution is a real help in setting up the circuit, but again, single turn pots will work if you have a steady hand!

The function generator IC is located above Q1. A 14 pin socket is required for this circuit also. The timing components are located around the function generator socket. I bring the pins on the IC socket through the board via wires to push-in type feedthrough standoff terminals. The components are mounted on top of the card and are easily accessible. In addition, the larger terminals are easier to connect to than the tiny IC socket pins.

The 741 output buffer amplifier is located near the top edge of the card as shown in the picture. All input, output, and power

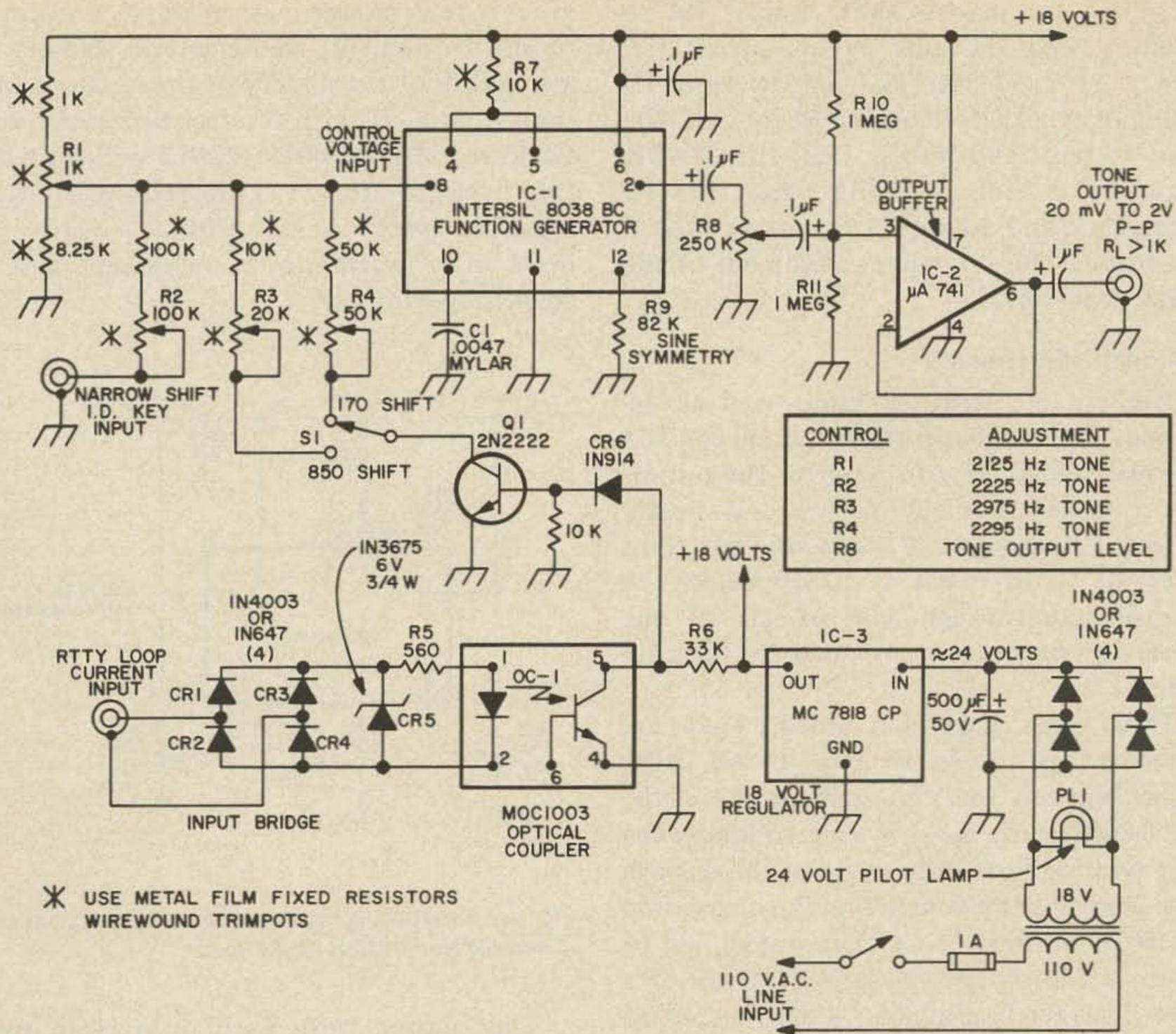


Fig. 3. Circuit schematic of the universal AFSK generator.

connections are made to the feedthrough standoffs on the underside of the card. The card itself is mounted above the main chassis on half inch spacers.

Circuit Alignment

After assembly, take a minute and check the wiring, particularly the connections to the two ICs. More chips are ruined from counting the pins from the wrong side than probably from any other cause.

Remove the 8038 function generator from its socket. Apply power and verify that the IC regulator output is 18V. Then check to see that this voltage is present at pin 6 of the 8038 function generator socket. Also check that R1 adjusts the voltage at pin 8. This voltage should never be less than three-fourths of the supply voltage. Remove power and install the 8038 chip in its socket. We are now ready to set up the tone

frequencies. Provide a 20 to 60 mA constant current source such as a RTTY loop. Connect this to the loop input jack. Do not attempt to drive the loop from a constant voltage source such as a lab supply without providing a current-limiting resistor. A small increase in input voltage will cause a large current to flow through the bridge and input zener CR5, since the circuit contains no internal current-limiting resistor.

Set the output pot, R8, to maximum and connect a counter, TU, or other frequency measurement device to the tone generator output.

With loop current applied to the input jack, set the MARK frequency adjustment, R1, so that a 2125 Hz output is obtained.

Set S1 for 850 Hz shift and remove the loop current. Now set R3 for a SPACE frequency output of 2975 Hz. Leave the loop current disconnected.

Set S1 for narrow shift. Adjust R4 to obtain a 170 Hz shift or an output frequency of 2295 Hz. The narrow shift ID setting is all that remains. Reconnect the loop current and verify that the MARK frequency is still 2125 Hz. Short the ID keying jack and adjust R2 to obtain a 2275 Hz output. This completes alignment of the AFSK generator.

Optional Adjustments

The circuit performs quite well as described. The experimentally inclined can add optional adjustments to improve the output distortion so that the sine wave is nearly perfect. I have reduced the second and third harmonic to as much as 50 dB below the fundamental through use of all of the trimming adjustments provided by the chip design.

Three pots must be added. They are connected as shown in Fig. 4. All other connections to the chip remain the same. The 1000 Ω pot, R12, is used to adjust the time symmetry or duty cycle of the triangle wave generator by controlling the charge and discharge currents of C1. The pot should be set for a 50% duty cycle using a scope. If a wave analyzer is available, it may be set to null out the second harmonic. This null is quite sharp.

R13 and R14 are used to adjust the amplitude symmetry of the sine converter. One pot adjusts each half cycle. Start with each pot at center position and adjust carefully for best wave form symmetry or minimum third harmonic distortion. This circuit is recommended by the IC manufacturers, but should be used with care so that the pot wiper does not go completely to the end. It might be possible to damage the sine converter by sinking or sourcing too much current to the chip from the supply or ground. Used with care it works fine.

Performance

Like most anyone, I like to make a few tests to see if my brainchild works as well as I think it will. The AFSK generator was subjected to several tests to verify performance. The frequency stability is quite good. The unit is about 5 Hz low when first turned on from cold, stabilizes within 1 Hz

after a few minutes warm up in a normal room environment. The long-term stability is a function of the quality of the resistors and capacitors used with the function generator IC. I used MIL RN60D resistors with a mylar film capacitor for C1. Long-term drift after some six weeks is still within a couple of hertz after warm up as measured with a frequency counter.

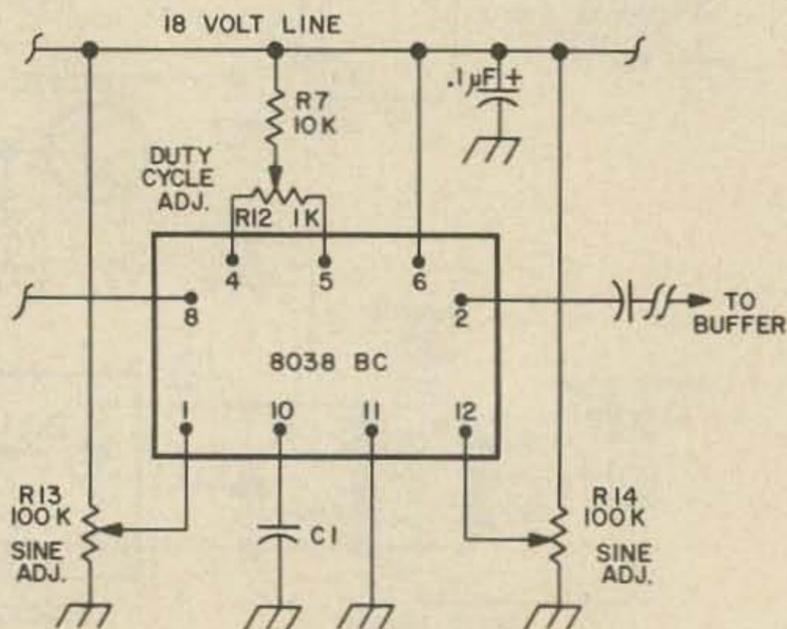


Fig. 4. Function generator with optional controls to reduce sine output distortion.

The output wave form is a clean sine wave and no clicks or transients are present when the circuit shifts from MARK to SPACE. The scope camera photograph shows the input switching waveform on the top trace and the resulting frequency shift on the bottom trace. This particular picture shows the shift from 2975 Hz back to 2125 Hz. There are no transients present and the sine wave amplitude does not change at all.

I also measured the harmonic distortion present in the output sine wave. Without adjustment of the 82K resistor, it is about 5%. Careful trimming will reduce it to below 3% which is good enough for most amateur RTTY applications.

The optically coupled input circuit worked quite well. The shift from MARK to SPACE occurs as the loop current drops below 5 mA which leaves plenty of margin for the fellows with 20 mA loop systems. The unit is truly universal. It does work with any local loop or TU, provided there is sufficient loop current.

... K6IQL/NØZIP

A CHEAP TEN MINUTE TIMER FOR THE SHACK

In his editorial for the month of August, W2NSD/1 commented on the amateurs' habit of identifying every two minutes. Not only is this habit unnecessary, but it's annoying, as well. Fortunately there's an easy solution in the form of a timer using one IC (Signetics NE555) and a handful of other components. Practically every repeater control circuit recently appearing uses some NE555s in the timing line, but relatively little has been said about its use by the average amateur. There's certainly nothing novel or original about the circuit that follows, as a similar circuit appears in Signetics' catalog. But many hams don't have access to catalogs and the like, and this article is meant for them.

The circuit is shown in Fig. 1. In the wiring configuration shown the NE555 acts as a monostable multivibrator. The timing is determined by R1 and C1, where the length of the timed interval is equal to $1.1 R_1 C_1$. It should be mentioned at this point that it's necessary to use a low-leakage capacitor for C1, or else the length of the interval will differ considerably from the value given in the equation. Also, be sure that R1 is less than 20 meg-ohms.

When S1 is pushed, pin 3 of the output goes high, and remains so until the end of the time period. If S1 is pressed during the

time period, the timer resets and begins counting a new interval. Pin 3 can source or sink 200 mils, which means that any device which draws up to 200 mils at 9V can be attached to the pin. If it's desired to have the device on during the timed interval, hook it up to points A and B, and to points A and C if the device is to turn on at the end of the interval.

In my set-up, an LED is used as the indicator. Most LEDs operate on two or three volts, so it's necessary to add a

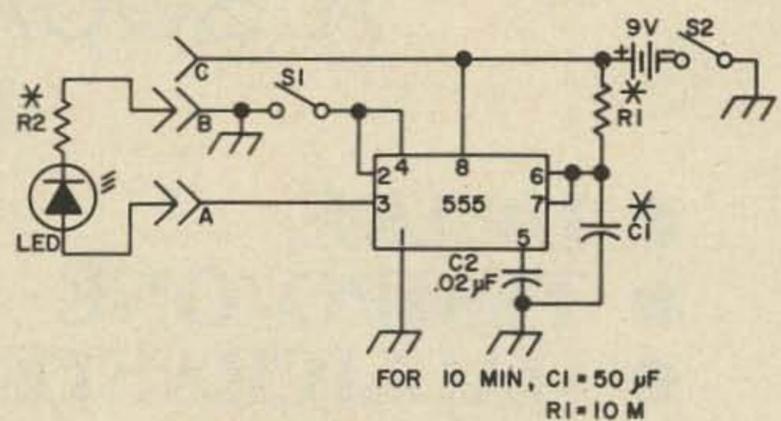


Fig. 1. Schematic of the 10-minute timer. See text for a discussion of R1, C1 and R2.

dropping resistor, R2, the value of which is equal to $\frac{9 - V_{led}}{I_{led}}$; where V_{led} and I_{led} are the LED's operating voltage and current, respectively. The same formula holds true for any device which operates on 9V or less.

...WB2VRW

CHARGE IT
ON



CHARGE IT
ON



DIAL-A-DEAL HAM RADIO CENTER

**CALL
FREE**

**TOLL
FREE
NUMBER**
(Continental 48 States)

**CALL
FREE**

**800
325-3636**

MO CUSTOMERS CALL
314-993-6060
COLLECT

**TRADE
ON
NEW**

CALL

**TRADE
ON
USED**

Bill Du Bord, WØKF

(9 A.M. – 5 P.M. Central, Closed Sunday and Monday)

**FOR
A SQUARE DEAL
ON**

- **DRAKE**
- **TEMPO/ONE**
- **HALLICRAFTERS**
- **CLEGG**
- **STANDARD**
- **YAESU**
- **SWAN**
- **COLLINS**
- **KENWOOD**
- **REGENCY**

*We carry all major brands and a large
stock of used reconditioned equipment*

SEND STAMP FOR USED LIST

HAM RADIO CENTER INC.

8342 OLIVE BL.

ST. LOUIS, MO 63132

A LOW FREQUENCY PHASED ARRAY

As a confirmed 80m type I have always resisted the urge to put up a truly superior antenna system for that band. Finally, last summer I decided to respond to the creative urge by constructing a system which would offer advantages over a simple dipole and which would also include sufficient flexibility to permit direct experimental comparison of a number of antenna configurations which are of interest. This article reviews the approach, the results and the current status of those experiments.

This antenna system provides effective gain and front to back ratio on 80m with switch-controlled directivity and angle of radiation.

The Approach

Consideration of space limitations (2/3 acre) and other practical constraints led to the choice of two parallel dipoles as the basic elements of the array. Since it was desired to switch to a unidirectional pattern and also to control the angle of maximum radiation, direct feed, rather than a parasitic array, was chosen.

Reference to the radiation patterns in the handbooks shows that a unidirectional cardioid (heart-shaped) pattern can be obtained in an end-fire array of two parallel elements, with a spacing of $\lambda/4$ and fed with a 90° phase difference. The radiation pattern in this case is a reversible cardioidal pattern

with maximum gain in the direction of the lagging dipole element. This cardioidal arrangement was chosen as the basic horizontal directional array with other related options available by switching.

It is of interest to provide, in addition to the reversible cardioid, a 45° lag (higher radiation angle), a 0° lag (highest radiation angle — 90°), and 180° lag (8 JK configuration — low angle, bi-directional) and, for comparison purposes, each of the two dipoles separately. This is a total of eight different pattern options!

Still in the experimental stage is an attempt to achieve the same options using $\lambda/4$ vertical radiators. Thus far, with the ground system available, the performance of the vertical system is uniformly inferior by about 10dB.

The Circuitry

The circuitry for the horizontal and vertical phased arrays is shown in the schematic diagram, Fig. 1. Instantaneous switching from one pattern to another is achieved by only three switches: a main selector switch S, the reversing switch X, which permits 180° phase reversal, and the 4PDT switch for changing between the horizontal and the vertical arrays.

For purposes of description the system will be treated under the following headings:

**We're
overwhelmed!
...but not surprised by your acceptance of
the new
TS-520**



**WE KNEW THIS NO-COMPROMISE, DO EVERYTHING, GO EVERYWHERE
TRANSCEIVER WOULD BE POPULAR. NOW WE ARE DELIVERING THEM IN
RECORD NUMBERS. PLEASE BE PATIENT...WE HAVE ONE FOR YOU.**

Here are 30 special reasons you will want to own a TS-520. After you have operated one, you will doubtless give us 30 more why you're glad you own one.

- | | | |
|--|---|---|
| <ol style="list-style-type: none"> 1. Built-in AC power supply 2. Built-in 12 volt DC power supply 3. Built-in VOX with adjustable gain, delay and anti VOX 4. 1 KHz dial readout 5. Ultra stable FET linear VFO 6. Built-in noise blanker 7. Built-in RIT circuit and RIT indicator light 8. 8 pole crystal filter 9. Built-in 25 KHz crystal oscillator 10. Provisions for optional CW filter 11. Break-in CW with sidetone 12. Completely solid state except final section. Compact, low current, | <ol style="list-style-type: none"> 13. Built-in cooling fan 14. Accessory external VFO & accessory external speaker 15. Built-in speaker 16. Modern styling & functional design. Modular construction. 17. Amplified ALC 18. TUNE position increases tube life 19. Maximum TVI protection 20. Built-in fixed channel operation (4 channels) with indicator light 21. Provisions for use with a VHF transverter | <ol style="list-style-type: none"> 22. Full metering 23. Selectable SSB 24. Selectable AGC operation for different modes 25. VFO indicator light 26. Built-in selectable ALC action for speech processing 27. Carrying handle 28. Rugged 6146 type final tubes 29. Internal cross-channel operation. 30. Push button WWV reception |
|--|---|---|

**Proven Kenwood quality
and reliability**

The price..\$629.00
subject to change without notice.

Accessories: External VFO-(VFO-520), External speaker - (SP-520), CW Filter - (CW-520)

**Available from
Kenwood dealers
throughout the U.S.**

Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

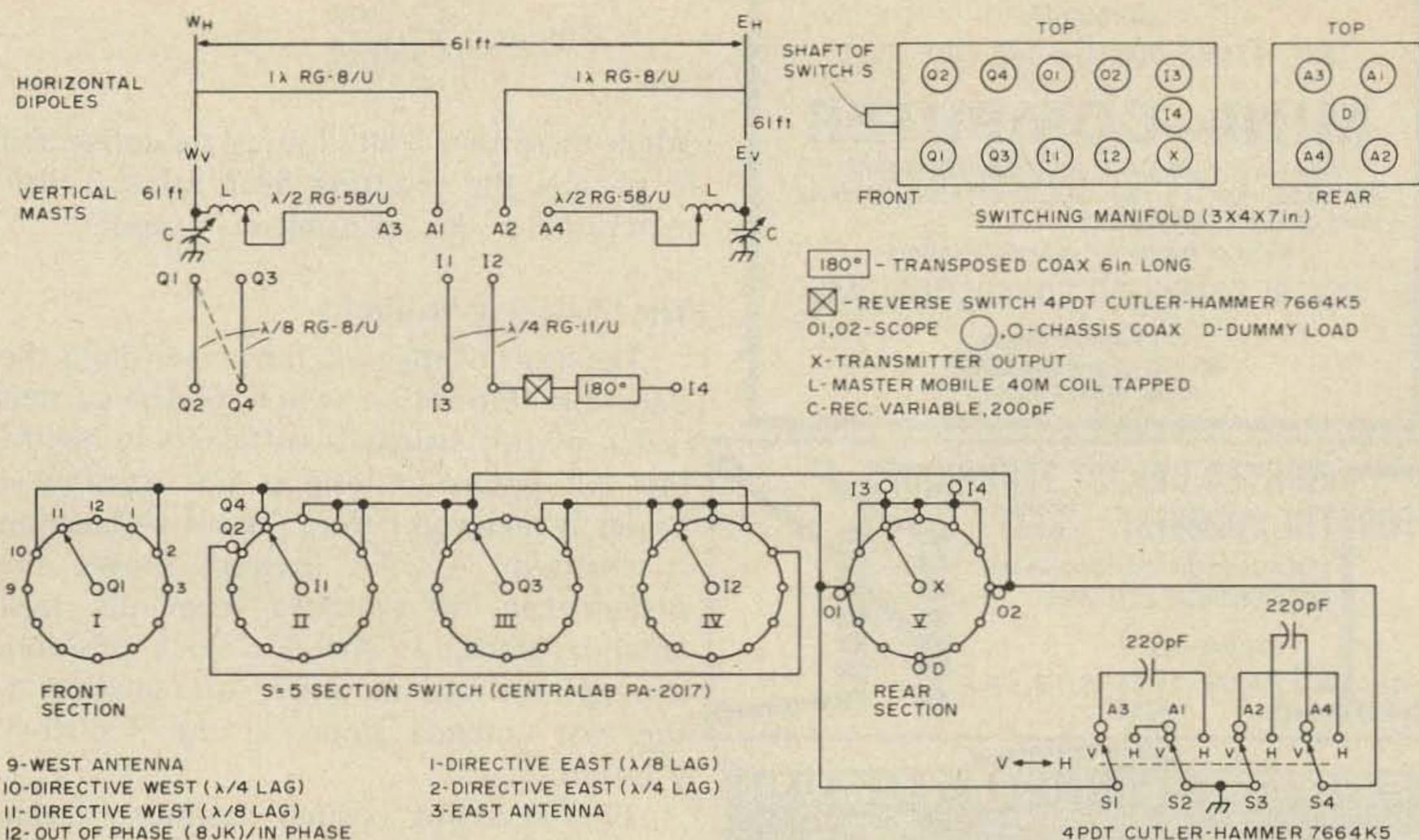


Fig. 1. Horizontal and vertical phased array circuitry. Only three switches need be used for instantaneous switching. See text for details.

The Horizontal Dipoles; the Verticals, Impedance Matching and the Switching Manifold.

The Horizontal Dipoles

The original installation utilized two dipoles as described previously.¹ The centers were 14.02m above the ground with a horizontal spacing of 18.6m. The RG8/U feedlines, one wavelength long, were inside the masts with the balun action and lightning protection as previously described. This original arrangement gave very good operation.

However, since it was desirable to have the lowest possible angle of radiation the centers of the two dipoles were raised to 18.6m ($\lambda/4$). This was accomplished by lengthening each steel mast by the addition of 9.14m length of 7.62cm diameter aluminum irrigation pipe at the bottom end of the mast. The steel mast is inside this pipe and the overlapping portion is bolted securely by use of .64cm plated bolts through the pipe and mast in perpendicular pairs. (No. 8 self-tapping screws in the steel mast served

to space the mast within the pipe radially before the bolts were put in place.)

No data could be taken for comparison of these two heights but it is assumed that the 18.6m height yields a somewhat lower angle of radiation for each pattern option.

The Verticals

The 18.6m foot masts are fed as top-loaded verticals. The horizontal dipoles are connected to the top of each mast and the two halves of each dipole are connected together by shorting the opposite end of the 1λ feedline.

Referring to the diagram, all of these connections are switched by means of the 4 PDT switch. This permits the selection of all of the vertical phasing options by the selector switch S just as for the horizontal system.

The resonating and impedance matching of the verticals is accomplished by the capacitors C and the inductors L. A noise bridge was used to insure adjustment to 52Ω resistive input at 3.955 MHz.

SCELBI COMPUTER CONSULTING, INC.

ANNOUNCES

THE TOTALLY NEW AND THE VERY FIRST

MINI-COMPUTER

DESIGNED FOR THE ELECTRONIC/COMPUTER HOBBYIST!
Kit prices for the new SCELBI-8H mini-computer
start as low as \$440.00!


Write or phone for detailed literature.

SCELBI COMPUTER CONSULTING, INC.

125 Edgefield Avenue
Milford, Connecticut 06460
Phone: (203) 874-1573

PRINTED CIRCUIT TECHNIQUES
FOR THE HOBBYIST booklet \$2.00
cutting-cleaning-drilling-layout
SUSPENSION ETCHING

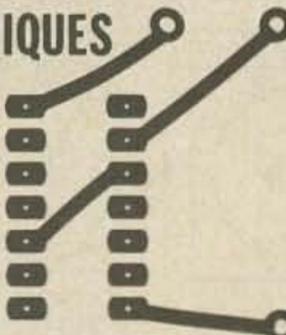TRUMBULL
833 BALRA DR., EL CERRITO, CA. 94530



PARTS! CORNELL TUBES!

FREE Send For FREE
CORNELL'S New Color Catalog
48 Pgs. New Items

33¢ per tube
IN LOTS OF 100

36¢ per tube
ORDER FREE IF NOT SHIPPED IN 24 HOURS!

4215 S University Ave. San Diego, Calif. 92105

The 220 pF fixed mylar capacitors connected across the feedlines of the verticals, during use of the horizontals, serve to tune out residual reactances for optimum SWR to the horizontals.

When full lightning protection is desired the bottoms of the masts are connected directly to ground by means of copper jumper cables. With this connection the horizontal array can be used with dc paths to ground from both sides of each dipole, giving full protection against build-up of static charge.

Impedance Matching

The feedline input impedances are 52Ω resistive at the resonant frequency (3.955 MHz). It is necessary to switch-in phase lag by inserting a length of 52Ω line in either of these feedlines, as desired, and to feed equal currents to both dipoles while maintaining a 52Ω match at the transmitter output.

This is accomplished by use of two $\frac{1}{4}\lambda$ transformer sections of RG11/U (75Ω) coax. These serve to transform the 52Ω antenna input impedance up to 108Ω by the

relation:

$$Z_{\text{input}} = \frac{Z^2_{\text{Line}}}{Z_{\text{output}}}$$

When these two 108Ω inputs are connected in parallel the resulting 54Ω value is well matched to the transmitter output.

The Switching Manifold

The heart of the switching manifold is the 5-section 12-position switch, S. The current rating of this switch is sufficient to handle the full power as long as the transmitter power is removed before the switch position is changed. As the diagram shows, the system can be switched from the west antenna alone, at the 9 o'clock position, through the various angles of radiation to the east antenna alone, at the 3 o'clock position.

The reversing switch permits instantaneous switching of patterns, for example, from east to west, without having to turn the selector through the intermediate positions.

Only four of the twelve switch positions are not used: 4, 5, 7 and 8 o'clock. The 6 o'clock position is used for a dummy load.

The switches are mounted in the $7.62 \times 10.16 \times 17.78$ cm aluminum chassis box with the sixteen coax sockets as shown. The box is mounted under a projecting top of the operating desk. The four lengths of coax used for matching and delay lines are wound on a wooden reel and placed inconspicuously behind the desk.

The connectors 01 and 02 provide inputs to the vertical and horizontal plates of an oscilloscope for a lissajous display of the inputs to the two antennas. (The integral scope in the CE 100V transmitter is used at W20ZH). Thus, the phasing and the amplitudes of the rf voltages can be continuously monitored, allowing any change in either antenna to be immediately noticed.

The scope shows a circle for the cardioidal patterns, diagonal lines for in phase or out-of-phase, and a flattened ellipse for either antenna alone. (This pattern is elliptical rather than a straight line due to the rf energy picked up by the non-energized antenna).

Performance


The performance of the array has been all that was hoped for, both for transmission and for reception.

The SWR is consistently low (under 1 1/2:1) for all configurations. The array shows a broadband behavior typical of coupled resonant circuits. The SWR remains low throughout a bandwidth of some 400 kHz — only the phasing varies.

The measured front-to-back ratio is of the order of 15dB and the gain is about 4dB, for both transmission and reception. The improved operation for low angles of radiation is sometimes spectacular — as net of California stations on .3952 kHz could be repeatedly heard and worked during the winter at 9:30PM E.S.T.!

One of the most pronounced characteristics noted has been the great reduction of QRM for reception. The combination of the high front-to-back ratio and the low angle of radiation serves to reduce the level of some signal strengths while increasing the level of others. Thus, there is often at nighttime, a sort of single-signal performance which is very gratifying. (It should be gratifying to the stations off the back of the pattern too!). This single-signal selectivity of the antenna system is particularly impressive when the station being worked also has a low-angle directive antenna system. In this case the directivities complement each other with spectacularly strong signals at either end.

For the type of operation prevalent at W20ZH the two cardioid patterns are used more than 90% of the time. Frequently the out-of-phase (W8JK) bi-directional configuration is used for calling CQ and the proper cardioid pattern is used for the ensuing contact. Under normal conditions there is little need for a linear amplifier, once contact has been established. The principle directivities are in the east and west directions so stations to the north or south are seldom worked. The 0° or 45° phase shifts and the single dipole patterns seldom show consistent superiority over the cardioids. It is interesting to listen to two stations on the same frequency which have about equal signal strengths, when one is to the east and

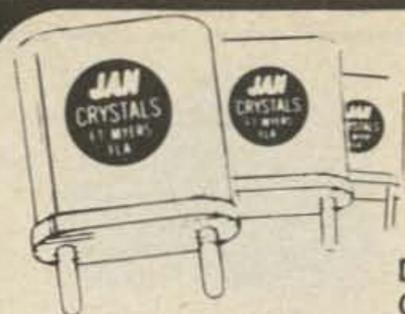

For FREQ. STABILITY

Depend on JAN Crystals. Our large stock of quartz crystal materials and components assures Fast Delivery from us.

CRYSTAL SPECIALS

2-METER FM for most Transceivers ea. \$3.75
144-148 MHz — .0025 Tol.

Frequency Standards
100 KHz (HC 13/U) 4.50
1000 KHz (HC 6/U) 4.50

Almost all CB Sets, Tr. or Rec. 2.50
(CB Synthesizer Crystal on request)

Any Amateur Band in FT-243 1.50
(80-meter, \$3.00 — 160-meter not avail.) 4/\$5.00

For 1st class mail, add 20c per crystal. For Airmail, add 25c. Send check or money order. No dealers, please.



Division of Bob Whan
& Son Electronics, Inc
2400 Crystal Drive
Ft. Myers, Florida
33901

All Phones
(813) 936-2397

Send 10c for new catalog with 12 oscillator circuits and lists of frequencies in stock

FREQUENCY STANDARD



Only
\$37.50



(less batteries)
POSTPAID USA

- Precision crystal
- Fully guaranteed

- Markers at 100, 50, 25, 10 or 5 kHz selected by front panel switch.
- Zero adjust sets to WWV. Exclusive circuit suppresses unwanted markers.
- Compact rugged design. Attractive, completely self contained.
- Send for free brochure.

PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025

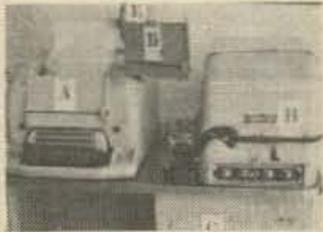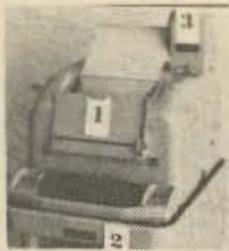

BARGAINS!

KLEINSCHMIDT TELETYPE EQUIPMENT

(1) TT-100 Page Printer, as is 60 or 100 wpm	\$59.95
(A) TT-117 Page Printer or (B) TT-179 Reprint & TD, as is	\$59.95
Above checked out, oiled & adjusted, each	\$119.95
(2) Table ... \$19.95 (C) Table ... \$34.95 (D) Copyholder ... \$3.95	
(3) Paperwinder ... \$14.95 TT-107 Reprint (not shown), only	\$59.95
TH-5 Converter Trans/Rec 100 cycles adjust to 170 shift	\$49.95




Andy Electronics Co., Inc.

6319 Long Drive / Houston, Texas / 77017 / Phone: (713) 641-0576
ALL PRICES FOB HOUSTON, TEXAS

vhf uhf CONVERTERS

START
HEARING the
WEAK ONES

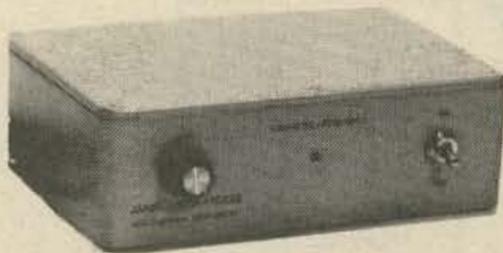

Very sensitive crystal controlled converters for receiving the VHF bands with your present receiver or transceiver. Ideal for DX, FM, Satellite reception or for just talking to the gang. All have built-in supplies for operation from either 117 VAC or 12 VDC. 10 Meter output is standard. Beautifully built and carefully tested with modern equipment.

50 CA, 50 - 52 MHz	\$85.00
144 CA, 144 - 148 MHz	\$85.00
220 CA, 220 - 225 MHz	\$85.00
432 CA, 432 - 436 MHz	\$85.00

JANEL can also supply a wide variety of receiving equipment for industrial applications. Write or call for details.

All items are postpaid and guaranteed. Please order direct or write for our free catalog.

ALSO - We stock a full line of sensitive PREAMPS!



JANEL laboratories

BOX 112, SUCCASUNNA, NJ 07876
Telephone: 201-584-6521

Cash for any Collins military or commercial equipment or parts, especially 618 T Tranceivers. 490 T antenna couplers. AN/ARC-102. AN/ARC-94.

CASH

AN/MRC-95. SPACE ELECTRONICS CO.,
76 Brookside Drive, Upper Saddle River, N.J. 07458
(201) 327-7640

Nasty Cryptogram
for non-FMers

RGUERT BWQ EWOWLRWEA OWE QWWJ
- LEW TIY IB DN? FUCW UR RET.

the other to the west. Either signal can be selected at will by switching the cardioid patterns and the unwanted signal is barely audible in the background!

Such an array would be a great boon to stations located on the coasts as the 3dB of power wasted out over the water could be largely utilized.

The only disappointment thus far has been the consistent weakness of signals from the vertical antennas. The separate vertical antennas are typically down about 10dB compared with the horizontals and this inferiority carries over to the vertical array, regardless of direction or distance. The poor performance of the verticals is attributed to ground losses, with attendant high radiation angles, in spite of the fact that a parallel grid of about 1066.8m of ground wire is used. Perhaps this explains why so many writers describe their 80m vertical constructional features at great length with hardly any space devoted to results. Maybe the results were unprintable!

Weather and motivation permitting, I plan to experiment further with improved radial grounding and I hope to get some meaningful quantitative comparisons. Meanwhile I will be skeptical when I hear of a "superior" 80m vertical with only a modest ground system.

Conclusions

A 2-element horizontal phased array for 80m has been constructed with a total of eight pattern options available by direct switching. Operating results have confirmed the expected gains and front-to-back ratios. The performance of the unidirectional cardioid patterns has been particularly effective, especially when the station being worked also has a directive antenna system.

Preliminary results using a vertical array with similar pattern options have not been encouraging, apparently due to high ground losses. Further experimentation on this system is planned.

W2OZH

¹ "Construction of a Balanced Dipole Antenna;" 73 Magazine, October 1972; P. 57ff. James E. Taylor.

DC ISOLATION

It is best to plan ahead a little for the dc organization of your complete solid state portable UHF station so that you don't find yourself connecting a negative battery terminal to a box that already has the positive wire on it. It happened to me!

There are a few units involved you know, like a low-noise rf stage, a second rf stage for image reduction, a mixer, a local oscillator, first i-f, tunable i-f, selective i-f, af amplifier, crystal-controlled exciter, rf power stages, and modulator. These are taken up and examined in turn as we deal with the bypassing and dc ground question. Good working examples of dc isolated 432 MHz amplifiers are detailed.

The dc question. Nowadays, with solid state devices, we're right back at the old stand where the 201A tubes used to have us — \$5 each, 6V directly-heated filaments, and storage batteries. With solid state converters, rf stages, i-f strips, exciters, rf power amplifiers, modulators, and cables, you've got to make up your mind before you start building whether you're going to use a positive or negative ground. The dc ground

deal is further complicated by the bypass question as you go up through UHF toward microwaves.

The low frequency units can be arranged pretty well with those little electrolytic and high K ceramic bypass capacitors (see tests on same later), but where trouble really starts is in the transition range near 432 MHz. Here, and increasingly so as you go on up through to 1296 MHz, no leads can be tolerated on the bypasses. You *must* use flat built-in capacitors.

We will take you through the whole bypass and isolation story, from 135 kHz up into microwaves, so that you can plan your dc ground and modulation affairs *on paper* first.

A list of some of the specific problems follows:

1. The value and size of bypass capacitors, beginning at 135 kHz, because you would like a good low-cost selective receiver, I'm sure.
2. When to use electrolytics and when you can do without them.
3. The UHF transition region, where you

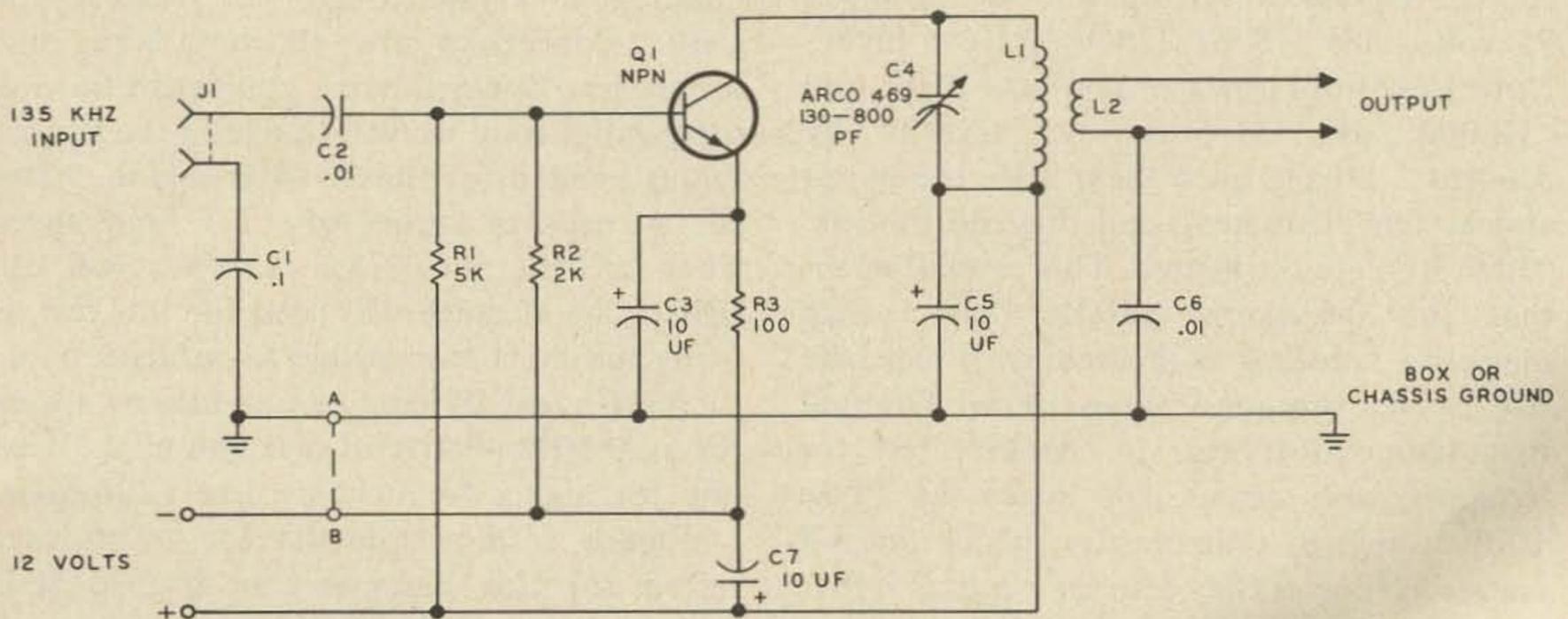


Fig. 1. VLF test circuit. I-f stage, 135 kHz.

— WE GOT 'EM —

CLEGG, COLLINS, DRAKE, SWAN,
YAESU, TEN-TEC, and many more in
stock. See us first for quick, courteous
service. Est. 1928 — MASTERCHARGE —
BANKAMERICARD W4WL

FRECK RADIO & SUPPLY CO.


40 Biltmore Avenue
P.O. Box 7287
Asheville NC 28807
Telephone: 704-254-9551

8220 MEMORY. 8 bit (4x2) content addressable memory. TTL and DTL compatible. For use in data-to-memory comparison, pattern recognition, cache memory, auto correlation, virtual memory, learning memory. New, house numbered. With data.
IN 16 PIN DIP \$6.00 each, 10/\$45.00

8038C VCO WAVEFORM GENERATOR
New, factory parts, full specs.
\$5.75, 2/\$10.50, 10/\$50.00

MM5314 CLOCK CHIP. Full specs. **\$9.50**

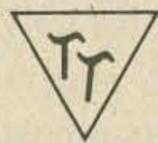All orders postpaid. Minimum \$5 U.S.,
\$15 foreign. Latest lists — \$.10 stamp.
Please add insurance.



TRI-TEK, INC.

P.O. BOX 14206, DEPT 7
PHOENIX, ARIZONA 85063

should begin to build your own lead-less capacitors.

4. The connecting cable outer conductor dc question.

5. How to build 432 MHz amplifiers whose groundplane-baseboard, box, and connecting cables don't have dc on them.

6. A word about 1296 MHz and up.

High-K, real small bypass capacitors are invaluable. Lafayette Radio has done a good job on bringing in low-priced subminiature ceramic bypass capacitors. I quote, "500 pF, 75 volts, size 1/8 by 1/8 by 1/16th inch." Now, I ask you, how can you beat that? And "10,000 pF, 5/16ths by 5/16ths by 5/64ths." I have used these little things for almost ten years now, and they do the job. "High-K" ceramic is used. This simply means that the insulation material has a high dielectric constant compared with air. Like five or six thousand times more! Granted that temperature-wise it changes, but for bypasses who cares? The specs say "Plus 100%" on high temperature, which doesn't matter as long as they also say "minus zero," which means that they don't drop *below* the initial rating. That is, they may increase, but

they don't go down, in pF.

Some checks and a test run here on VLF, 10 meters, 2 meters, UHF, and into microwaves may help you to decide what bypass to use at what frequency. It already has helped me with my work.

These tests also tend to answer the question of overall circuit design of a crystal controlled, selective, portable station, for UHF in particular.

VLF. A low frequency i-f stage was checked to see just how much emitter and collector bypassing was actually needed in the kHz range. Figure 1 shows the test circuit, forming part of a low-cost i-f stage on 135 kHz, with a selectivity of a few kHz.

In Fig. 1, C3, the emitter bypass, and C5, the collector return bypass, are the units requiring attention. It was found that C3 needed the largest amount of capacity, working all right with 1 μ F, but showing an increase of 5 to 10% in gain with 4 μ F. Eight to ten μ F was the value finally decided on for both C3 and C5. Subminiature electrolytic capacitors are available from Lafayette Radio which can be used for these purposes. Remember that you do not have the full battery voltage across the emitter resistor. A 6V rating will suffice here for C3.

There are some extremely tiny electrolytic capacitors made in the USA, but they run to more money, and will be taken up at another time.

The ten meter region. This can be of considerable importance because it is a good frequency to use for a tunable i-f when building a crystal-controlled receiver for UHF. Converters are all very well, but somewhere down the line you've got to tune something! Here we will touch on the bypass values needed for the 30 MHz region. After all, no need of taking up a 1/2 x 1/2 in. space when a little job 1/8th x 1/8th will do, right? The rf stage was used for this test as being the most susceptible to oscillation due to insufficient bypassing and also as a base for a 30 MHz i-f strip in case you might need one for higher frequencies, like 1296 MHz.

Figure 2 shows details for an rf stage tested for this parameter in the 30 MHz region. Checking for both rf and i-f usage, because there can be a difference between a

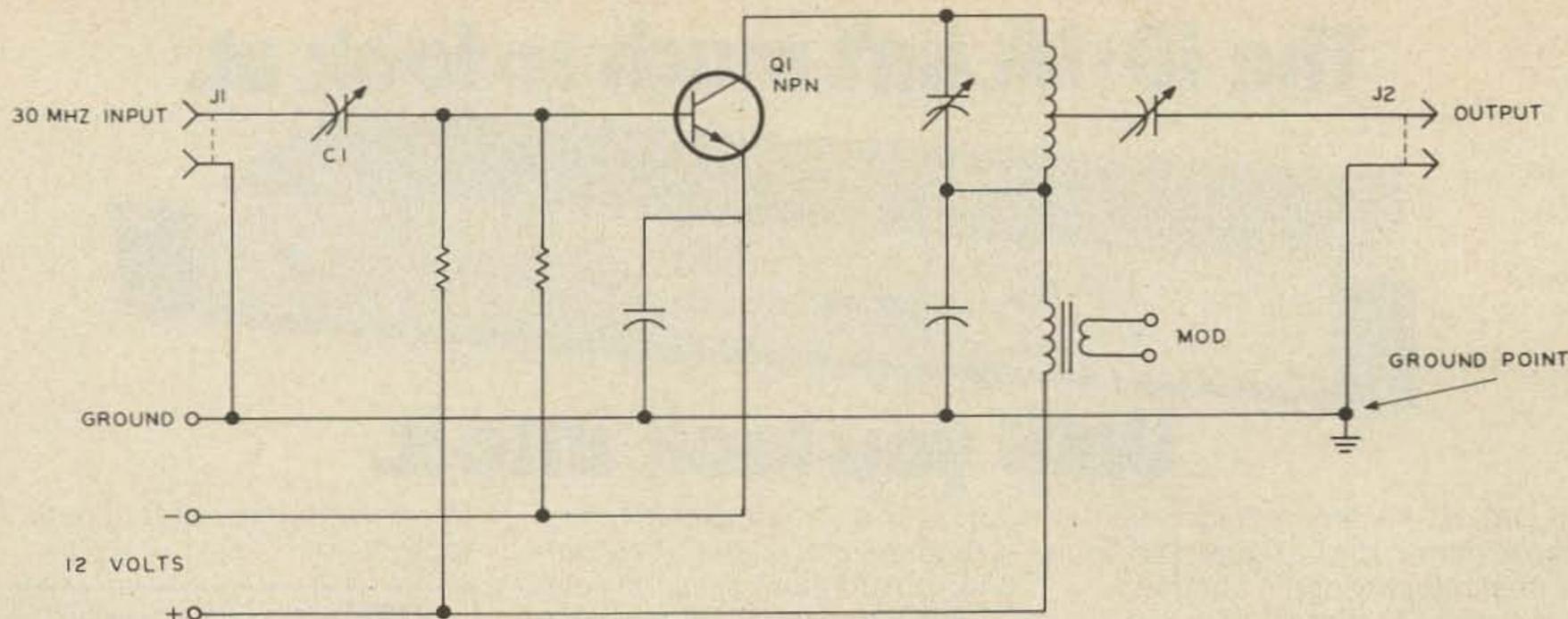


Fig. 2. Test circuit, 30 MHz region. Note. The "ground" point may be connected to either the positive or negative battery terminal, or left open dc-wise.

and up to 144 MHz for rf, that I've included details on the circuit for you. Four variable trimmer capacitors are shown and they are all useful. C1 matches the input cable, along with the tap on L1. C2 tunes L1 and the base tap on L1 completes the input circuit.

The collector coil L1 is tuned by C5, and tapped down for C6, the output matching capacitor. Excellent loading and control of feedback is obtained, with high gain and good stability.

single tunable rf stage and multiple fixed-tune stages as in an i-f amplifier, it appears that the value of .001 which is 1000 pF is sufficient for both C2 and C3. If you want to be absolutely sure, use 5000 pF. They are almost identical in size and price.

VHF, 120 to 144 MHz. I was going to jump from ten meters to UHF, but just couldn't let my old favorite two meters go by because I have ideas on a general purpose i-f strip to follow microwave front ends for

NASEM

COMMUNICATIONS INTEGRATED CIRCUITS

IC TYPE	DESCRIPTION	CASE	Price, Ea.
NA555	Versatile Timer	8-DIP	0.99
NA555-2	Dual Timer	16-DIP	1.55
NA370	AGC/Squelch/VOX	10-TO5	1.20
NA371	Versatile rf/i-f	10-TO5	1.29
NA3018	4-Trans. Array	12-TO5	0.89
NA3026	Dual Diff. Array	12-TO5	0.99
NA3086	5-Trans. Array	14-DIP	0.45
NA3039	Diode Array	10-TO5	0.75
NA3036	Dual Darlington	10-TO5	0.75
NA1595	Analog Multiplier	14-DIP	1.90
NA8038	VCO/Sine/Sq./Tri.	14-DIP	4.50
NA1596	Bal. Mixer/Mod.	10-TO5	1.20

SPECIAL - MICROTRANSMITTERS !

NA2000 100mW AM on 10 Meters \$9.95
 NA2001 250mW AM on 10 Meters \$14.95

in stud mount package

Both types usable at reduced output at 6 Meters and above. Requires external crystal & 2 tuned circuits. With data/applications.

NASEM Box AI
 Cupertino CA 95014

- 24 Hour COD—Phone Answering Service
- Our Data/Application Sheet Enclosed with Each Type Shipped
- Every Unit 100% Parameter and Function Tested to our Guaranteed Limits on the same Fairchild Computer-Type High Speed Tester Used by Major Semi Companies

"HOBBYIST-EXPERIMENTER" TRANSISTORS

TYPE	DESCRIPTION	CASE	Price, Ea.
HNP50	NPN RF 250MHz	TO18	0.49
HNP52	PNP RF 200MHz	TO18	0.59
HNP55	NPN RF 200MHz	TO92	0.59
HNP715	PNP GP RF/Audio	TO92	0.59
HNP716	PNP Med. Curr. SW.	TO92	0.59
HNP724	NPN GP Audio	TO92	0.49
HNP736	NPN GP Audio	TO92	0.59

TERMS

Prepaid U.S. orders over \$10.00, we ship.
 Prepaid U.S. orders under \$10.00, add \$1.00.
 Prepaid foreign orders over \$10.00, add postage.
 Prepaid foreign under \$10.00, add \$1.00 plus postage.
 COD U.S. orders over \$10.00, add \$1.50.
 COD U.S. orders under \$10.00, add \$2.50.
 No Foreign COD orders.
 California residents add 6% sales tax.

Confused? Please read again before ordering . . .

COD PHONE (408) 867-5900

Automatic recorded 24 hour COD telephone order service — supply full information concerning order and shipping instructions. Requested return calls — Collect only . . .

The ID-1A isn't much to look at.



Until you look into it.

The HAL ID-1A repeater identifier was designed and engineered for commercial service, in compliance with FCC identification requirements. But its price is so attractive that radio amateurs interested in FM are buying it, too.

The heart of any repeater identifier is its Read-Only-Memory. And inside the HAL ID-1A is a unique ROM — one you can easily re-program yourself, should you need to change the call sign. The ID-1A's ROM capacity holds 39 dots, dashes and spaces — enough for "DE" plus the call sign. But there's a lot more inside the ID-1A than that. TTL IC's are used for high noise and temperature immunity. Accurate timing is assured from the 60 Hz VAC line

source, or an internal oscillator — when the unit is operating on 12-VDC. And there's a wide selection of ID time intervals available to you (the factory-assembled set is programmed for 3, 6, 12 or 24-minute ID intervals). Code speed is adjustable. The keyed audio oscillator includes volume and tone controls, with a low-impedance output for driving the transmitter microphone line and a 2" monitor speaker. And there's a rugged transistor switch to actuate the transmitter keying relay or other controller.

The HAL ID-1A is available factory assembled for \$115 or as an assembled board/kit, including all parts external to the board except the cabinet for \$75. Look

into it. Better yet, order yours today.



HAL Communications Corp.
Box 365, Urbana, Ill. 61801
Telephone: (217) 359-7373

- Enclosed is \$ _____ (Assembled)
\$ _____ (PC Board/Parts)
Call letters _____ I.D. Interval _____ min.
 Charge Master Charge # _____
 Charge BankAmericard # _____
M/C Interbank # _____
Card Exp. date _____
 Please send me the HAL catalog.

Name _____

Address _____

City/State/Zip _____

All prices include U.S.A. shipping.
Add \$3 for air shipment.
Illinois res. add 5% sales tax. **L**

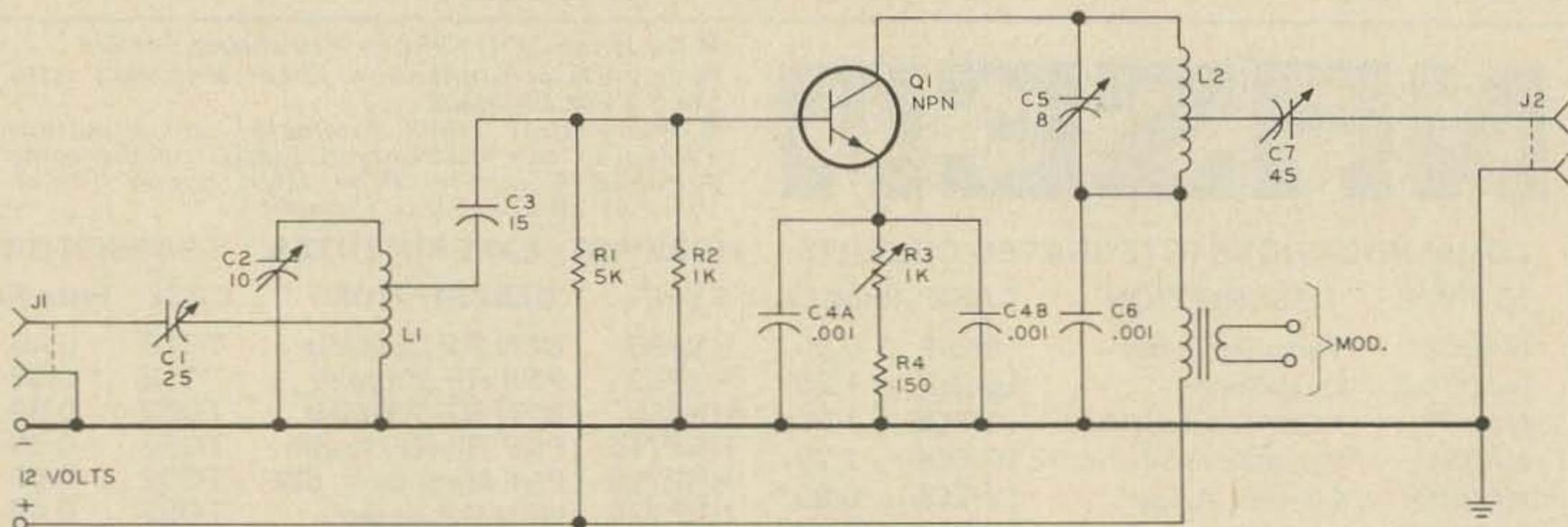


Fig. 3. Excellent 120 — 144 MHz amplifier.

amateurs somewhere in the 100 to 200 MHz region. Very useful.

Fig. 3, shows an excellent general purpose amplifier around six and two meters with emitter and collector return bypasses suitable for use with a negative ground. This turned out to be such a fine job for the region of 120 MHz as a microwave i-f strip, and up to 144 MHz for rf that I've included details on the circuit for you. Four variable trimmer capacitors are shown and they are all useful. C1 matches the input cable, along with the tap on L1. C2 tunes L1 and the

base tap on L1 completes the input circuit.

The collector coil L2 is tuned by C5, and tapped down for C6, the output matching capacitor. Excellent loading and control of feedback is obtained, with high gain and good stability.

The emitter bypass showed the preference for more than one capacitor. This business of a jump in gain when bypassing the emitter with a second capacitor is not new. However, a brass plate capacitor such as I use on 432 MHz and up did not help on this 120 MHz amplifier. This is evidently the beginning of a transition region where the

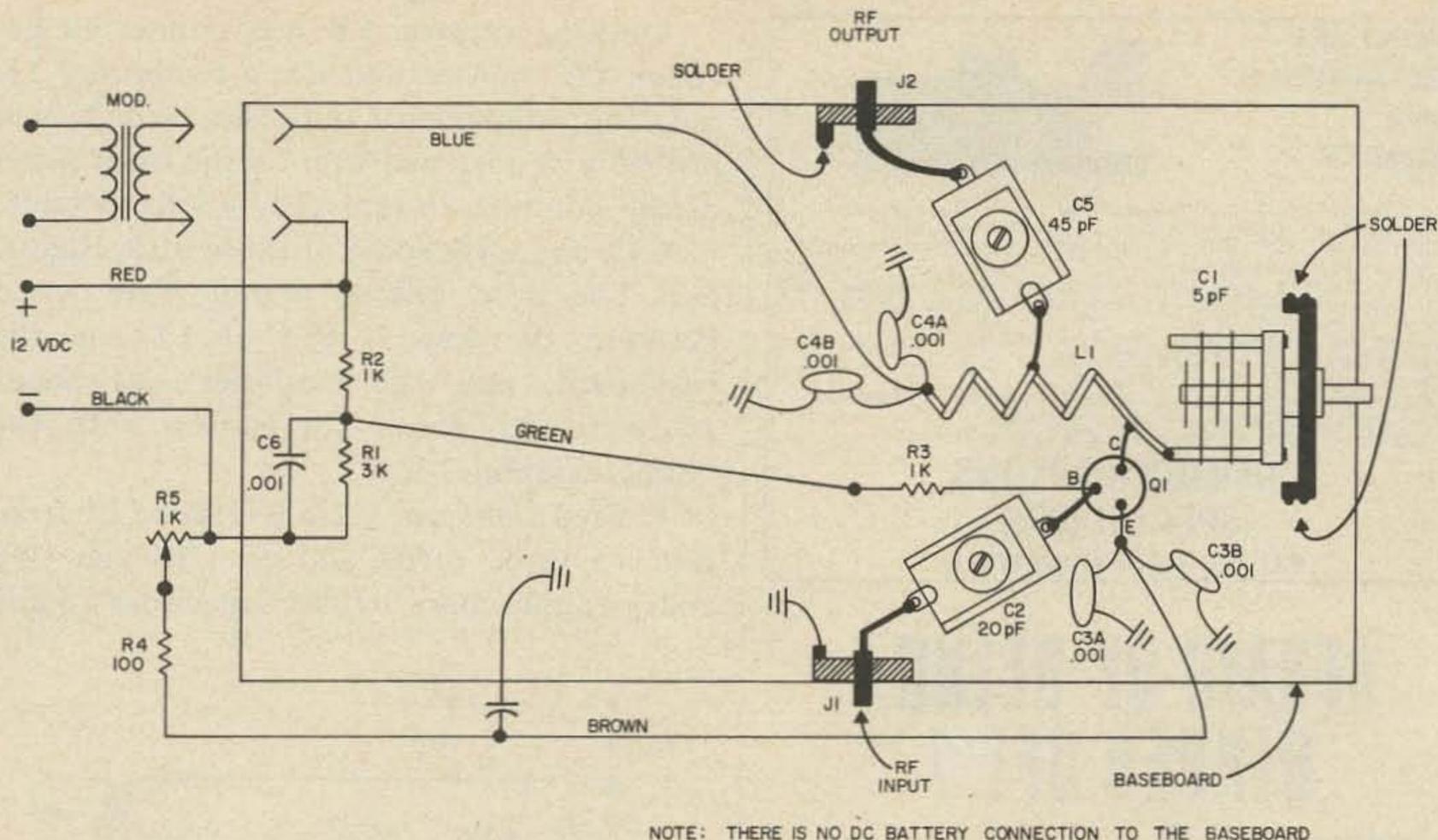


Fig. 4. 432 MHz amplifier using coil and capacitor. Top view.

inductance of the leads needs to be paralleled, but the total capacity still needs to be up in the hundreds of pF.

The collector return bypass did not show this effect as strongly. Only about 2% gain was obtained by the use of a second parallel capacitor. Of course it was installed, because 2% here and 2% there all add up. Retuning the collector is advisable after each such change.

UHF, with coils and boughten capacitors. Now we get to a transition region again, where even those tiny 1/8 x 1/8 capacitors begin to fall down.

Figure 4 shows a UHF amplifier for 432 MHz using a coil and variable capacitor, (see Fig. 7) and regular bypass capacitors, that is, capacitors you can buy retail, with leads on them. Success with an oscillator and a diode receiver using a coil and variable capacitor made me wonder about using them in an amplifier, so back to the bench I went and I'm glad I did; it worked fine. Figure 4 shows the result. As usual a copper-clad baseboard 1 3/4 wide x 3 3/4 in. long that fits into a minibox formed the base of this little UHF firecracker.

Collector circuit. Nothing to this one. A brass angle strap to hold the Johnson type "M" model No. 160-102, 1.5 to 5 pF, five

plate variable capacitor, was soldered to the baseboard as in Fig. 4 and Fig. 5. Next L1, a three turn coil, yes, even at 432 MHz a coil, was mounted as in Fig. 5, side view.

The KMC \$5 H104 was then connected, collector to the coil L1, emitter to rf ground through C3A9 (later C3B), and the base to R3, a 1K resistor, tenth watt. An additional

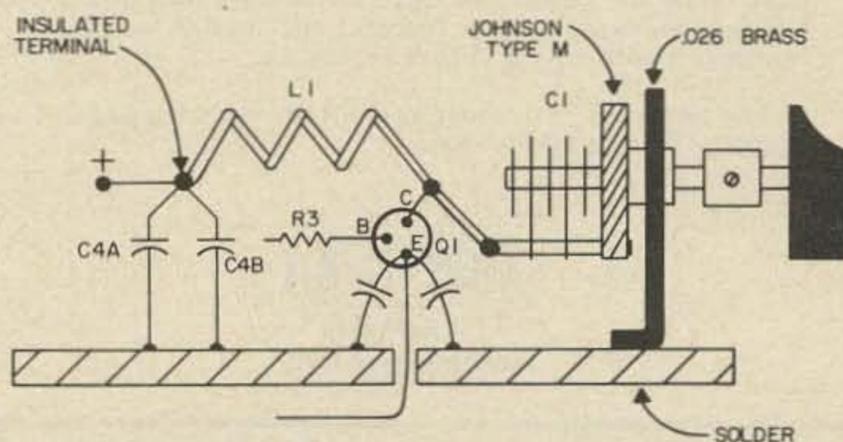


Fig. 5. 432 MHz amplifier using coil and capacitor tuning. Side view, layout of rf components.

ground strap of soft thin copper was soldered from the ground tab of C1 to the baseboard. The input jack J1 was soldered directly to trimmer C2, and J2 was soldered to the output cable matching trimmer C4.

The dc base bias resistors R1 and R2 were connected to the plus and minus battery lead pins, and R3 from the base to the center point.

**MINIATURE
SUB-AUDIBLE
TONE
ENCODER**



- Compatible with all sub-audible tone systems such as Private Line, Channel Guard, Quiet Channel, etc.
- Glass Epoxy PCB, silicon transistors, and tantalum electrolytics used throughout
- Any miniature dual coil contactless reed may be used (Motorola TLN6824A, TLN6709B - Bramco RF-20)
- Powered by 12vdc @3ma
- Use on any tone frequency 67Hz to 250Hz
- Miniature in size 2.5x.75x1.5" high
- Wired and tested \$14.95
- Complete less reed (Available in 33 freqs. for \$17.50 ea)
- Output 3v RMS sinewave, low distortion
- Postpaid - Calif. residents add 5% sales tax

**COMMUNICATIONS
SPECIALISTS**

P.O. Box 153, Brea CA 92621

**AFRAID OF BEING
RIPPED OFF?**

PROTECT your mobile transceiver with attractive, quickly installed, modification package using new unique concepts. Does not require bells, sirens, horns, or wires.


YOUR existing mounting bracket will be used but greatly improved with a custom designed "Keeps-It-Kit". Keys, pliers, allen wrenches, screw drivers, etc. are not used, and are not effective in theft attempts.

RIG is still easily removed **BY YOU** whenever desired, but risk of theft by others is drastically reduced.

NOW avail for your Linear, SB144, SB450 TRC, Regency, HR220, HR6, AR2, HR2B, HR212, HR2MS, and Genave, GTX2, GTX200, GTX600, GTX100, GTX10, GTH100. Others soon.

ECONOMICALLY priced at only \$15.95, post-paid. Because the specific, tamper-proof concepts have planned variations (even amongst identical transceiver types), your specific Kit profile will be registered with us for future reference.

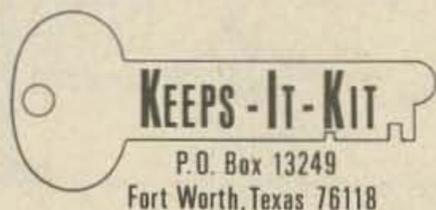Order today — quantities limited. Specify exact model. Texans add 5% tax.




**ARNOLD'S ENGRAVING
Personalized**

**ELECTRIC
ON-THE-AIR
SIGN
WITH CALL**



Works on
110 VAC
\$12.95

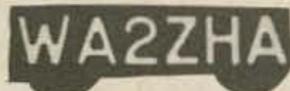

Metallex Lapel Bar - \$1.50 Metallex Tie Clip - \$2.25

ARNOLD'S ENGRAVING

2041 Linden St.

Ridgewood, N.Y. 11227

Limiting resistor R4 was connected between the emitter and R5, a temporary 1K pot for adjustment purposes, which will probably be fastened later on the front panel of the minibox, or replaced by a fixed value.

C4A and C4B, some of those little High-K jobs I've been talking about, were wired between the low rf end of L1 and the baseboard, and the amplifier was about ready to go, for a comparison with the "Super-strapline" unit.

It fired right up. I had to reduce L1 from four to three turns, add on C3B and C4B and a couple more bypass capacitors C5 and

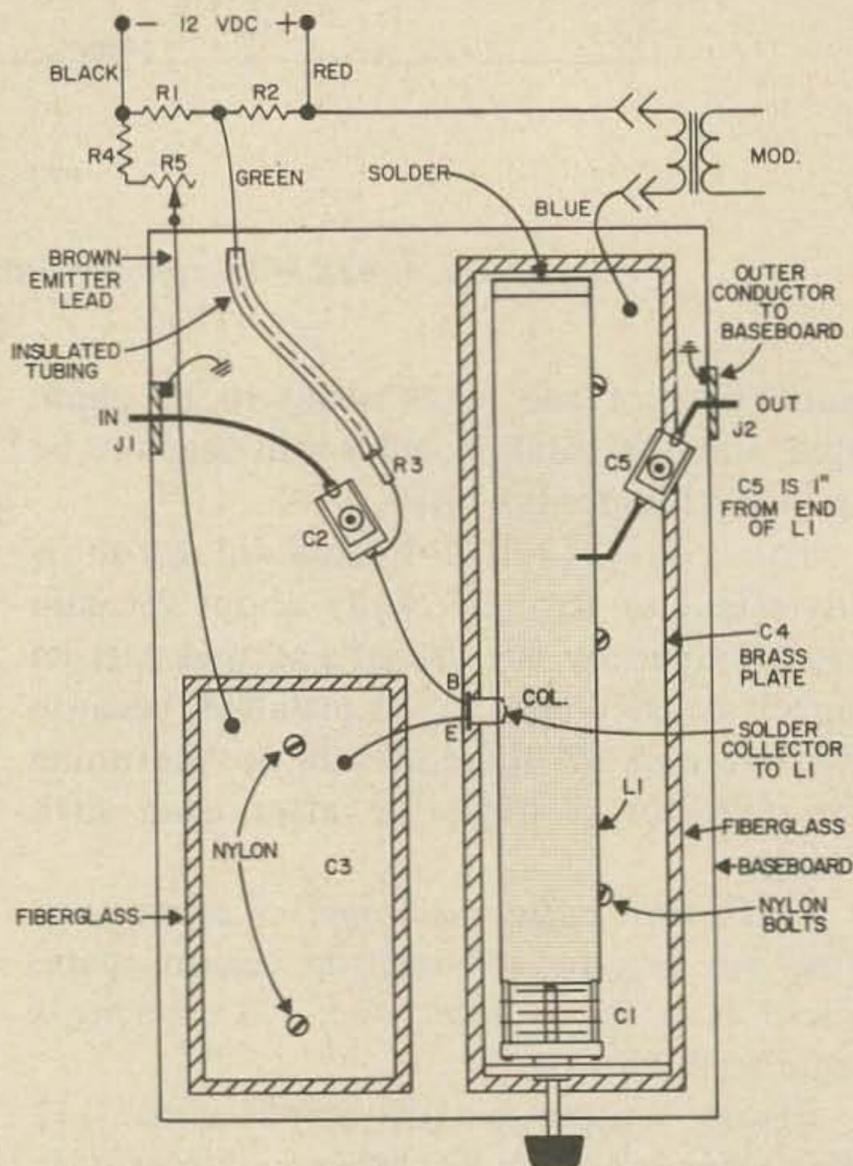


Fig. 6. "Super strapline" 432 MHz amplifier. Top view.

C6 on the terminal strip, and away she went on 432 MHz for an 18 mW output from the doubling type crystal controlled exciter. It also takes 20 mA of current nicely.

Special circuit notes on the use of the additional bypasses. C3B, in parallel with C3A on the emitter, brought the gain up some 4%. The same treatment at the collector return with C4B increased the amplifier gain by about 2%. Don't ignore all these little one or two percents. They can add up

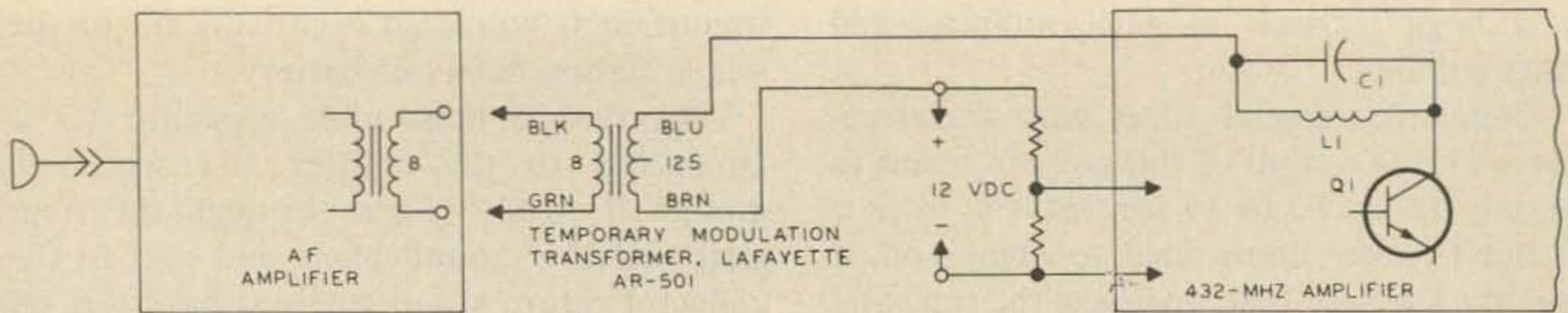


Fig. 9. Modulation test. 432 MHz.

This particular amplifier is intended to be driven by just a few milliwatts from a crystal controlled exciter, so the base has considerable dc bias on it. If it is used as a second stage amplifier with more drive you may operate it without any dc bias other than the positive swing of each input cycle, and some charge on C2, the base input coupling capacitor.

The output capacitor C3, along with its position on L1, matches the output cable to L1, and you will also find this one very useful, as it varies the working output load on L1.

I find something like 20 mW output from this amplifier for about 1 mW input, which is enough from today's \$5 device at 432 MHz.

1296 MHz and up. Figure 8 shows the proposed dc isolated collector circuit for the "1296'er" amplifier. No further details as yet available, because I haven't built it yet. I will soon, though!

Modulation voltages. There isn't too much to say here so far because I've been listening to it and the modulation "sounds like broadcast," as they say on the air. This is using the tried and true method of a diode detector, a high gain transistor af amplifier, and a pair of well-padded earphones. This keeps the sound of your own voice from reaching your ears through the air which would drown out the desired voice channel which for this test should come through the microphone, modulator, modulated rf power amplifier, and over through the air to the diode receiver, af amplifier and headphones.

Figure 9 shows the modulation hookup which is very straightforward as it was planned to be when the rf amplifiers were designed. Note the dc isolation available between the two windings of the modulation transformer. This is good because the modu-

lator secondary has to be connected to the plus battery terminal.

The Lafayette AR-501 has an 8Ω secondary which connects to the 8Ω speaker output winding of the modulator. This modulator is a temporary one because when the proper modulation transformer is installed the two transformers will not be needed. Remember we are probably going to climb in rf power at 432 MHz by several stages, each of which will call for a lower impedance winding on the modulation transformer, so it is handy to have transformers with several values of impedance around. I also have a three watt af amplifier waiting to modulate that extra power coming soon.


There are also now on the market some ten or twenty watters for less than \$20 which will make good modulators for some real power. That real power on UHF will also cost you real dough so save your pennies if you insist on it. Personally I'm just going to drive up Mt. Monadnock, 2000 plus feet of elevation, which I can see out of the window as I'm writing. I am of course interested in more power and am pestering the semiconductor lads all the time to divert or otherwise make available to us amateurs some devices for a watt or two at UHF at a price that we can afford. Maybe some mass market will do it for us.

Winding up the modulation story, there is also the business of modulating one or more driver stages ahead of the final. This will lower the modulating impedance seen by the modulator still further. But that's all right because the lower the impedance the lower the cost of the transformer. You can get ten watt transistor modulation transformers for less than \$5 retail right now. After all, there's not much copper wire in them.

"CQ, CQ, any station on 432 . . ."

. . .K1CLL

LITTLE BILL

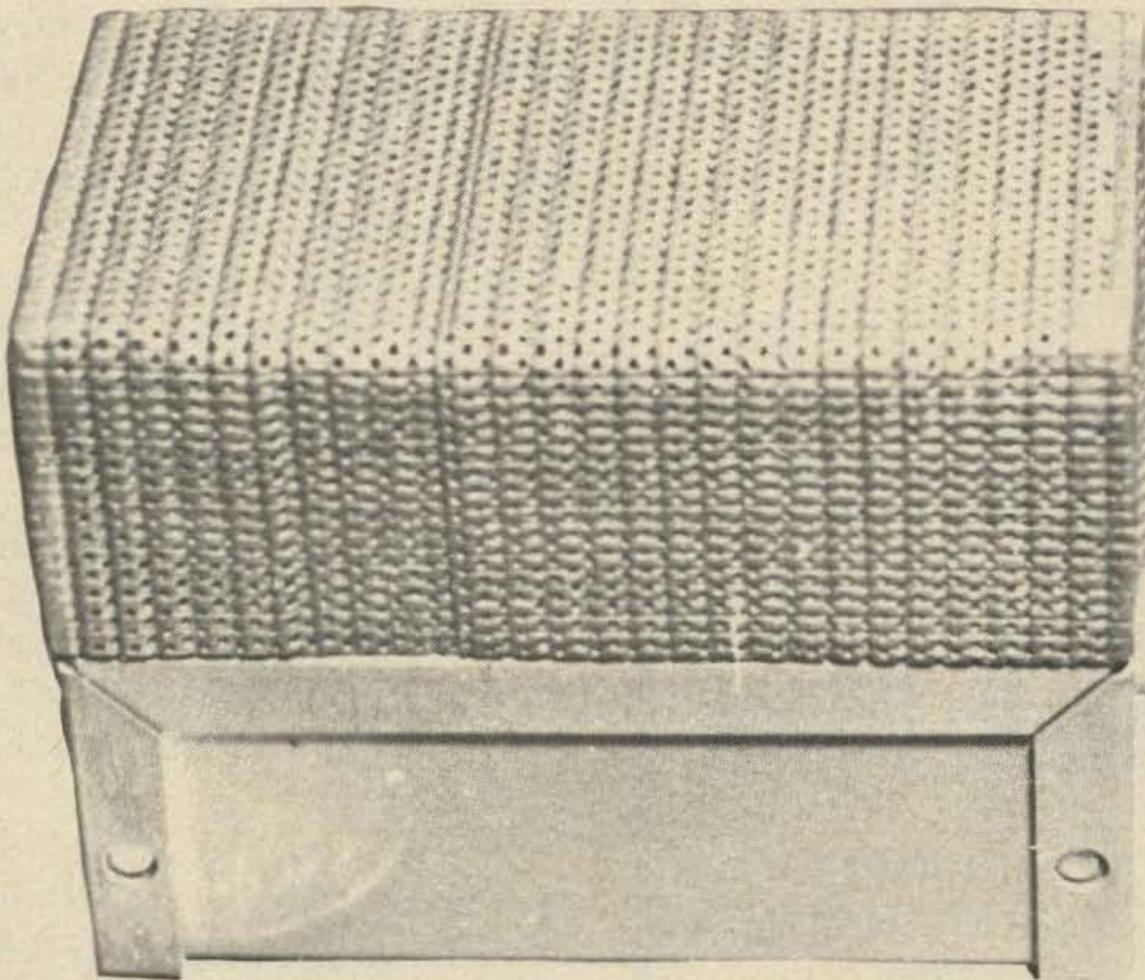

Overall view of the little transmitter with the homemade shield in place.

In these days of rising costs on practically everything, it is indeed a pleasure to construct and operate an efficient piece of radio equipment for pennies, and that is the reason for "Little Bill."

Circuit Description

The rf section of the transmitter, which consists of a crystal controlled Motorola HEP 53 oscillator followed by an RCA 2N4427 rf power amplifier running class C, develops about 1.25 watts output at 28 MHz.

The oscillator stage is a Colpitts type, providing excellent frequency stability with

respect to supply voltage and temperature and delivers over 100 milliwatts to the input of the rf amplifier stage.


The power amplifier stage uses a class C common emitter configuration and is modulated through the collector circuit.

A pi-network is used in the output resonant circuit to provide a measure of harmonic suppression, and the photographs show a double pi-network which was later changed to a single pi. A Drake lo-pass filter is used for additional harmonic suppression,

CW FILTER



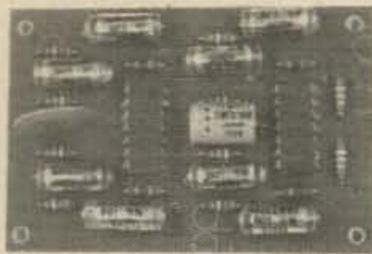New Model CWF-2BX—\$19.95.
Ready to use. Please include
\$1.00 postage.



Model CWF-2—\$12.95, Kit.
\$14.95 Wired, tested, guaranteed.
Please include 55c postage.

- Get Razor Sharp selectivity from any receiver or transceiver.
- Extremely high skirt rejection.
- Drastically reduces all background noise.
- No audible ringing.
- No impedance matching.
- Ultra modern active filter design uses IC's for super high performance.

We have what we think is the finest CW filter available anywhere. The 80 Hz selectivity with its steep sided skirts will allow you to pick out one signal and eliminate all other QRM and QRN. Simply plug it into the phone jack or connect it to the speaker terminals of any receiver or transceiver and use headphones, small speaker, or speaker amplifier. Better yet, connect it between any audio stages to take advantage of the built in receiver audio amplifier.

Build the 2"x3" CWF-2 PC card into your receiver or get the self contained and ready to use CWF-2BX and plug in!

SPECIFICATIONS

BANDWIDTH: 80 Hz, 110 Hz, 180 Hz (Switch selectable)
SKIRT REJECTION: At least 60 db down 1 octave from center frequency for 80 Hz bandwidth
CENTER FREQUENCY: 750 Hz
INSERTION LOSS: None. Typical gain 1.2 at 180 Hz BW, 1.5 at 110 Hz BW, 2.4 at 80 Hz BW
INDIVIDUAL STAGE Q: 4 (minimizes ringing)
IMPEDANCE LEVELS: No impedance matching required
POWER REQUIRED: CWF-2 . . . 6 volts (2 ma.) to 30 volts (8 ma.); CWF-2BX standard 9 volt transistor radio battery
DIMENSIONS: CWF-2 . . . 2"x3" PC board; CWF-2BX . . . 4"x3 1/4"x2 3/16" (black winkle steel top, white aluminum bottom, rubber feet)

TRY this fantastic CW filter. If you don't think it is the best you have ever used, ask for your money back. We will cheerfully refund it. These filters carry a full one year warranty.

Write for FREE brochures and magazine test reports. Other IC active filters available: CW mini filter (1 1/2"x2 1/2"), low pass, high pass, and wide bandpass filters. Audio amplifiers: 1/2, 1, 2 watts. Crystal calibrator.

MFJ ENTERPRISES

P. O. Box 494, Mississippi State, MS 39762

FM Schematic Digest

A COLLECTION OF
MOTOROLA SCHEMATICS
Alignment, Crystal, and Technical Notes
covering 1947-1960
136 pages 11 1/2" x 17" ppd \$6.50

S. Wolf
Box 535
Lexington, MA 02173

Slightly blemished tools from a top U.S. manufacturer. Assorted needle nose and cutters, 4 1/2" to 6 1/2". Send \$16.00 for 10 tools. Specify needle nose, cutters or assortment.

GREENE'S ELECTRONICS
P.O. Box 626
St. George SC 29477

WORLD QSL BUREAU

5200 Panama Ave., Richmond CA USA 94804
THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next county, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 6¢ each.

as solid state finals are noted for putting out many harmonics of quite healthy levels.

Other types of transistors may be substituted for the particular ones used here, but remember that the final amplifier impedance might be different. This would have to be taken into consideration for modulator impedance matching purposes.


The modulator section starts out with a FET microphone amplifier (HEP 801) to obtain a high impedance input for the crystal microphone used. The output stage is a HEP 593, a 1W output IC having an 8Ω output impedance.

Other audio amplifiers may be used here, such as the Amperex TAA-300, and these IC modules are preferred to standard audio boards for their compactness that lends itself readily to miniaturization.

The output of the audio stage is fed to an 8Ω input modulation transformer that steps this up to the required modulating impedance, being about 75Ω in my particular case.

I wound my own modulation transformer according to formulas given in the Handbook. If an output transformer is available with a primary impedance of 75–80Ω and a secondary of 8Ω this can be used reverse connected.

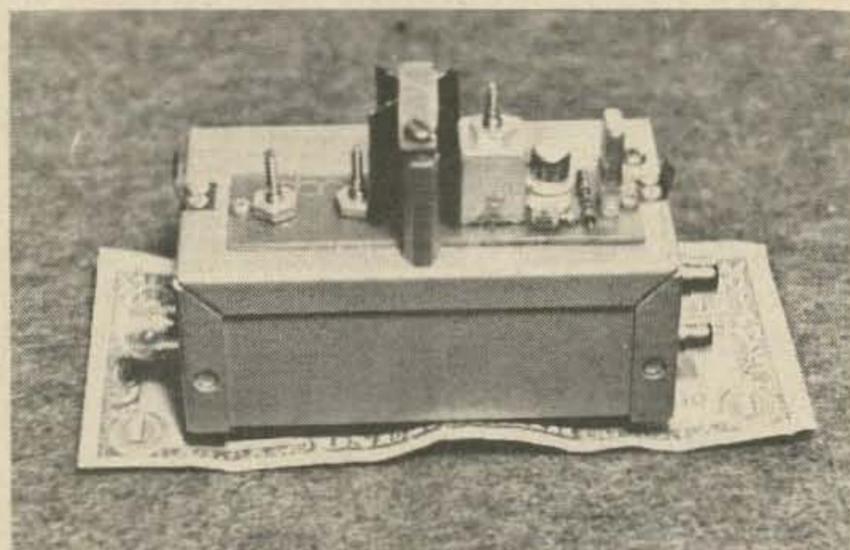If you elect to wind your own transformer, then a few words are in order here to assure good modulation results.



Top view of transmitter with shield cover removed to show general layout of components. Finned heatsink on final transistor is home made from aluminum sheet and painted flat black. Stand off supports small strip of plastic to hold heatsink in place and keeps transistor from being damaged if jarred accidentally. Crystal oscillator on right with its coil mounted in an old i-f can and amplifier on left with pi-network. Note small spring clips to hold shield cover in place on each end of mini-box.

2 METER FM HEADQUARTERS

Only STANDARD
sells more STANDARDS
than ERICKSON!

and here's
ANOTHER
ERICKSON
SPECIAL

SRC-826 MA



A better BEST BUY than ever

YOU GET Standard's 826MA, the best 12-channel 10-watt solid state rig on the market, factory set up on four channels plus crystal coupons for eight more channels (16 of Standard's lifetime Astropoint crystals!) of your choice; with helical-resonator front end receiver, built in provision for tone-coded squelch, rear panel test point/monitor/control sockets — all in one compact, reliable package — at a GIANT \$119 ERICKSON saving !!

Shipping prepaid for cashier's check or MO.

OUR DEAL:

826 MA list	\$398.00
+ 16 extra xtals	80.00
Package list price	\$478.00
You pay only	\$359.00
YOU'VE SAVED	\$119.00

Handheld Special

SRC-146A with:

- Deluxe basecharger
- "Stubby" antenna
- Leather case
- Ni-cads
- 94/94, 34/94 and one other channel of your choice

List Price	\$369.00
Our Price	\$319.00
YOU SAVE	\$50.00 !!

Another Best Buy from Erickson



Make ERICKSON your headquarters for all your FM needs

SEND QSL FOR COMPLETE SPECIFICATIONS

ERICKSON COMMUNICATIONS

3501 W. Jarvis, Skokie, IL 60076 (312) 677-2161

Be sure that the core that you use to wind this transformer has enough iron in it so that the core cannot saturate during modulation, and also that there is ample space for the windings. I mention this because the wire sizes used for transistor modulation transformers are larger than for comparable tube devices due to the current demands of the transistor and thus needs more room on the bobbin.

I used an old 5W output transformer and wound 70 turns of No.26 enamelled wire for the 8Ω primary and about 210 turns of the same size wire for the 75Ω secondary.

The final in my particular unit draws about 180 mA. The supply voltage is regulated at 13.5V so my final impedance is about 75Ω (collector voltage divided by collector current). The transmitter runs about 2W input and readily delivers 1W plus output.

With this modulation system, reports have been excellent. Running such low power you need good modulation for de-

pendable contacts. This probably seems like much ado about modulation, but even when the signals dropped to S-zero on someone's meter the report was still Q-5 and that is what really counts. Incidentally, the microphone used here is one of the imported lapel types and cost only 67¢.

Construction

This little transmitter was constructed in a small mini-box measuring approximately 10 x 5 x 4 cm, and a top cover was fabricated from an aluminum front grill from an old transistor receiver, with the sides folded to form a shield and the seams were epoxy cemented and when dry the corners were filed smooth and then given a coat of metallic green spray paint for a pleasing appearance.

The ends of the box are used for mounting the receptacles for the dc power input and microphone and the rf output to the antenna. Two phone jack types are used for microphone and power input and a bnc type

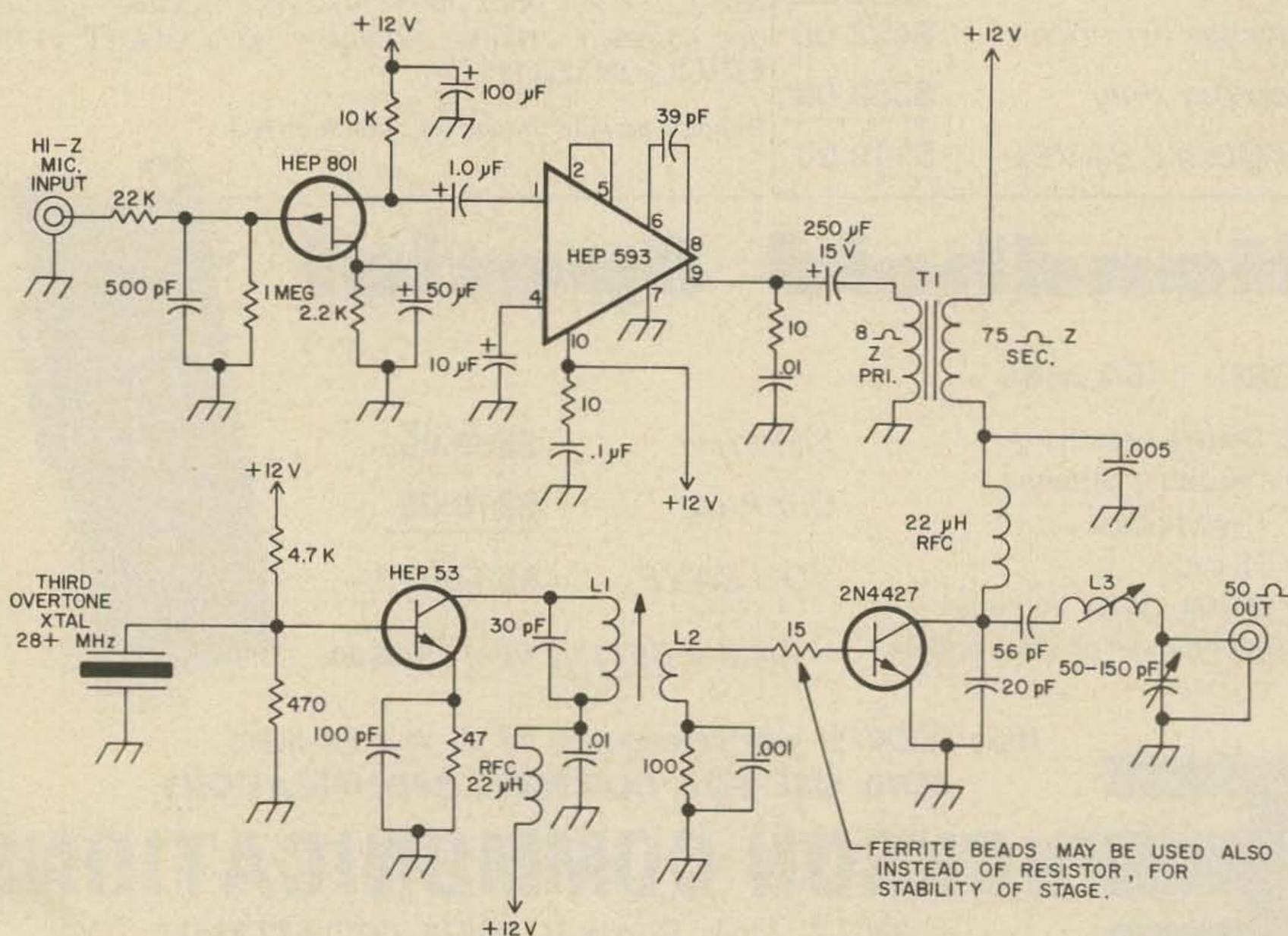


Fig. 1. Schematic of "Little Bill" transmitter. L1 - 13 turns No.28 P.E. CW, L2 = 2 turns link on cold end, L3 = 13 turns No.28 P.E. C.W.. All coils close wound on 6 mm diameter slug-tuned ceramic forms.

connector is used for the antenna to readily accommodate coax cable.


I made two small clips to hold the shield cover in place from scrap pieces of phosphor bronze stock strips, and these not only keep the cover in place but serve as grounding connections for the cover helping to keep harmonic energy from flowing out on the coax and creating unnecessary interference.

The coil forms used were ceramic surplus, just over 6 mm in diameter and tuned with a powdered iron slug. All coils were close wound with No.28 enamelled wire and given a coat of clear household cement.

Tuning Up


The tune up procedure is very simple and there should be no difficulty in obtaining proper output providing that all parts are good and the circuit has been wired correctly.

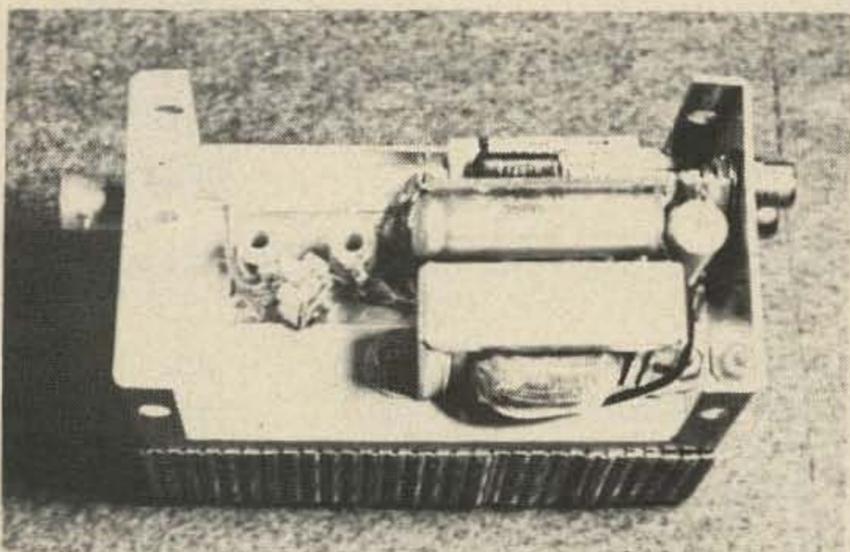Connect some sort of dummy load to the transmitter output, such as a 51Ω resistor (carbon) and a diode and voltmeter, or use a QRP wattmeter as I do.



Bottom view of transmitter showing mounting of audio board and modulation transformer. Capacitor at extreme right near power connector is 100 μF unit across power input used to provide good filtering and low impedance when batteries are used. Parts layout is not critical here but try to keep audio stages away from final rf stage as much as possible to avoid rf pick up.

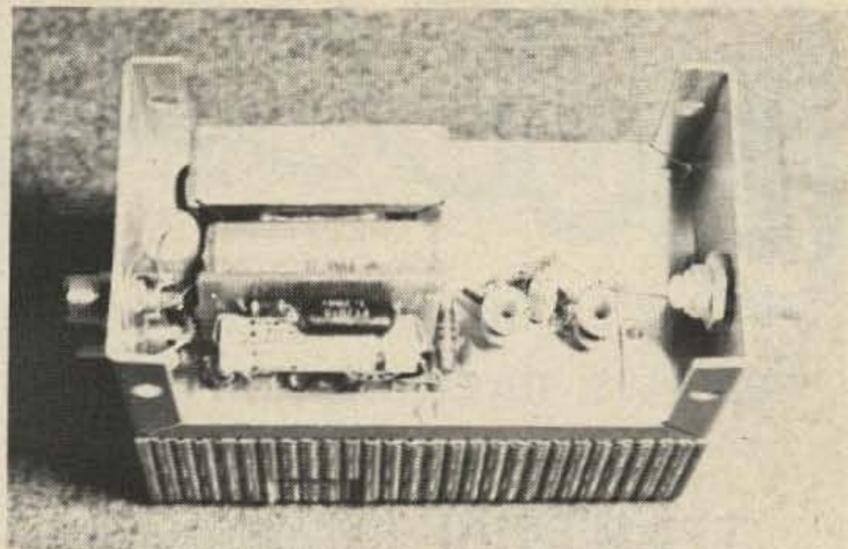Starting with the oscillator slug and with power applied adjust the slug with an alignment tool for output indication on the meter and turn the circuit on and off several times to make sure there is reliable starting of the oscillator each time. Then adjust the amplifier slugs and the pi-network capacitor for maximum output. Be sure to use heat-sinks on the rf amplifier. I also use one on



Bottom view of transmitter showing parts placement. Note antenna connector on left apron to allow very short lead to pi-network. Photo shows double pi-network originally used but later revised to single pi output, see text. Modulator components shown on right side with board containing all audio parts except transformer which is fastened to box directly.

the audio amplifier in the interests of cool operation and efficiency.

For the final touch-up in the alignment procedure, install the lo-pass filter in the line from transmitter to the dummy load and repeak all stages for maximum. The harmonic content will now be the lowest level and will not influence the output reading.

Transistor output stages are not as tolerant of high standing wave ratios as tube circuits, so be sure that your SWR is kept to a low level at all times.

Results

On the air results were most gratifying. I used a variety of antennas and modulation reports were very good indeed.

Using a $\frac{1}{4}\lambda$ whip attached to the side of the house about fifty to sixty contacts were made from both coasts and Canada with reports ranging from S-zero to S-9 plus. Always noted was Q-5 copy, attesting to the modulation capability.

With a 2-element beam, South American contacts were made as well as Central America and even the Windward Islands on a CQ!

It has been a real pleasure to operate this little unit. I should like to express my sincere thanks to Sam W9BDM for his patience during all the tests that were made, and for his incessant nagging to make the modulation as good as it now is.

...W9WBH

GODBOUT

JULY SPECIAL

BILL GODBOUT ELECTRONICS

BOX 2673, OAKLAND AIRPORT, CA 94614

74143 Decade Counter — LED Driver
with DL 707.3" readout \$6.00

- TTL SPECIAL** 7440 dual 4 input NAND buffer, same pin out as 7420
5/\$1.00
- MOS DYNAMIC MEMORY** 1 x 1024 bit MM5260 \$5.00
- LINEAR SPECIAL** MC 1496 balanced modulator IC \$1.00
- DTL SPECIAL** 936 Hex inverter, TTL compatible plug in replacement
for 7404 in many applications 5/\$1.00
- 12V 8A Regulated Power Supply Parts Kit.** Ideal for powering FM rigs.
Everything except the chassis \$17.95
- LM 309K 5V 1A REG** \$1.75
- LM 320K NEG Reg** available in 5V 12V & 15V \$2.25
- LM 340K POS Reg** available in 6V, 8V, 12V, 15V, 24V \$2.25
- 4194 TK adjustable dual tracking reg** TO66 \$3.90
- 4195 TK dual tracking reg** ±15V TO66 \$3.40
- SUPER MEMORY** Static N MOS 1 x 1024 bit. Runs on single 5 Volt
supply, with data sheet, type 2102 \$16.50
- 8008 PROCESSOR** 8 bit on a chip \$50.00

ICs, most TTL & LINEAR in stock — Send stamp for FREE catalog

CMOS DIGITAL

74C00	.60	CD4011	.60	CD4042	2.95	741M	.45
74C02	.60	CD4012	.60	CD4044	2.95	741T	.50
74C04	.85	CD4013	1.25	CD4049	1.25	741 Mini	.45
74C10	.60	CD4014	4.00	CD4050	1.25	747D	.90
74C20	.60	CD4015	4.00	CD4116	1.50	748M	.65
74C73	1.65	CD4016	1.25			1595	1.50
74C74	1.25	CD4017	3.20	LINEAR		1596	1.75
74C76	1.75	CD4018	5.00	LM318	1.75	CA3028	.75
74C107	1.75	CD4019	1.35	LM339	2.00	CA3065	.75
74C151	3.30	CD4020	5.50	LM370	1.25	CA3086	.45
74C160	3.25	CD4021	4.00	LM371	1.25	3900	.75
74C161	3.25	CD4023	.60	LM372	1.25	4136	2.00
74C162	3.25	CD4024	3.00	LM374	2.00	4250T	2.25
74C163	3.25	CD4025	.60	LM380	1.75	5558	.90
74C195	3.15	CD4027	1.75	LM381	2.00		
CD4001	.60	CD4029	6.00	LM382	1.75		
CD4002	.60	CD4030	1.20	555	1.00		
CD4008	4.00	CD4035	2.95	556	1.60		
CD4009	.95	CD4037	2.95	723T	.95		
CD4010	.95	CD4040	5.00	723D	.75		

ALL ITEMS IN STOCK and will be shipped within 24 working hours of receipt of order!

Include 50¢ postage and handling on orders under \$10.00

Sorry, NO C.O.D.'s. CALIFORNIA RESIDENTS ADD sales tax.

3000V dc SUPPLY

Building that new linear for CW, SSTV, or just everyday SSB, you'll find this one whale of a supply built to take it.

Have you ever built a piece of gear with available parts and done an immaculate job, only to have a transformer or component go bad after a period of time? When you go to purchase a replacement you usually find it is sold out or no longer available. So you shop and shop, trying to find something that will do the job and also fit into your cramped dimensions. Perhaps you'll be lucky. I usually am not and end up rebuilding.

The described 3000V power supply incorporates rugged design specifications

coupled with generous dimensions that provides versatility in accommodating transformers and related components found on the surplus market.

Construction

The high voltage power supply shown was easily constructed, as all mechanical work can be performed with a metal munching tool, pop rivet gun, good soldering gun, and ordinary hand tools. An electric drill with variable speed control will save much time.

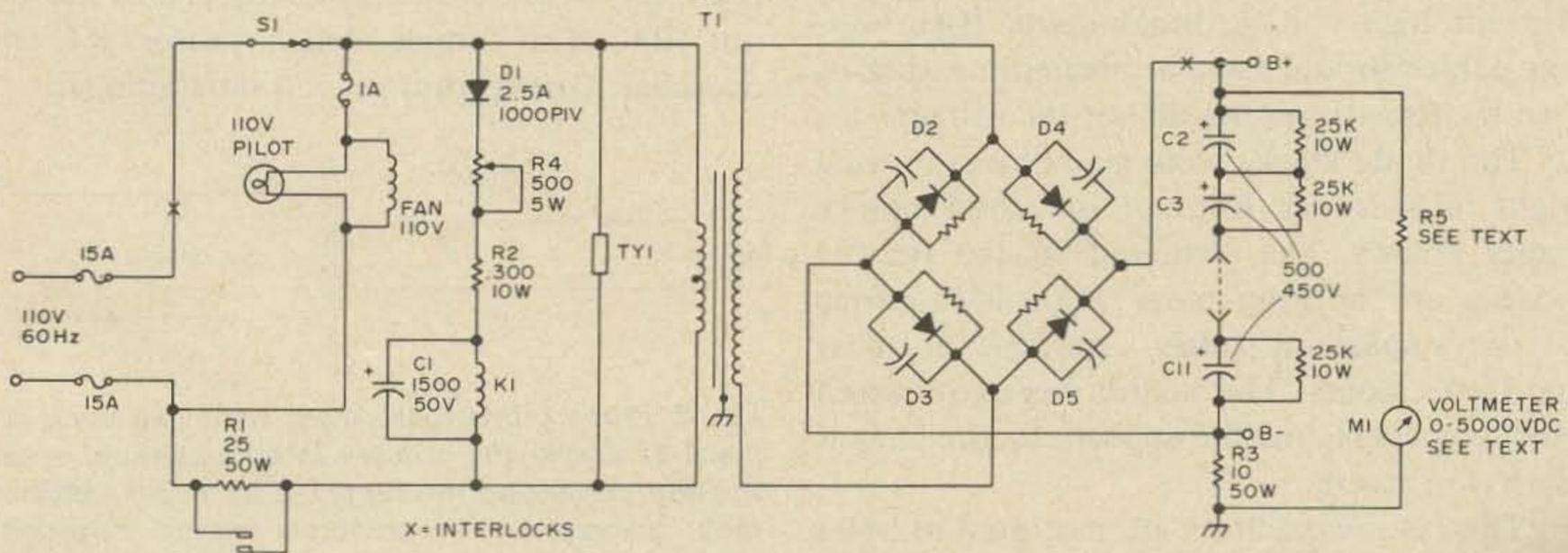


Fig. 1. Schematic of the 3000V power supply. The diode stacks D2–D5 are constructed of 8–2.5A 1000 PIV series connected diodes each. Shunted across each diode is a 470K 1W resistor and a .01 1000V disc capacitor. C2–C11 should be 500 μ F with a minimum voltage rating of 450V dc. K1 is a P&B type PR3DY, 24V dc coil with 25 amp contacts. T1 has a 2200V rms secondary with a 500 mA minimum rating. The thyrector is a G.E. 6R520SP4B4.

The main aluminum chassis and front are 33.02cm x 43.18cm x 7.62cm (standard) and the back aluminum wall has a 2 cm inside lip at the top and bottom for attachment to the main chassis and cover. The front chassis and rear wall are attached to the main chassis by generous use of pop rivets. The main chassis is reinforced on the bottom with a thick steel plate with one caster at each corner and one in the middle to support the weight. The line cord is fed to the rear through a steel conduit.

The cover is manufactured by hand bending a sheet of aluminum to tightly fit the chassis assembly and is held in place by sheet metal screws. Right angle aluminum brackets were installed on the back plate along the sides to accommodate the fastening of the cover. Air is exhausted by mounting home air vent assemblies on the sides of the cover. The local lumber yard had the vents.

Before attaching aluminum to aluminum I roughed each contact surface with fine sand paper to assure a good electrical connection. I also connected each chassis and the back together electrically with copper braid.

The front of the supply contains a voltmeter, on-off switch and pilot light. The rear of the supply is designed with safety in mind. The B+ and B- connections are in a minibox with two grommeted holes in the bottom. The large insulated feed-through was fitted on a small plexiglass sheet and the hole in the aluminum made extra large to prevent high voltage breakdown. High voltage cables should have a minimum rating of two to three times the dc output voltage.

The diode stacks were made by mounting eight diodes on four pre-punched epoxy paper boards. The insulated spacers for the boards are nothing more than self-tapping plastic expansion tubes, available at most hardware stores. The boards were connected to the spacers and the spacers to the chassis by nylon screws.

The filter capacitors are mounted in holes drilled in plexiglass with a hole saw. The hole was too small to begin with, requiring some filing. The plexiglass is held in place by self-tapping plastic expansion tubes and nylon screws. To prevent the capacitors from

arcing to the chassis the area below the capacitors has a sheet of punched epoxy paper board cemented to it – also the cut-out plastic circles were cemented to the bottom of each capacitor.

To keep air circulating a small fan was mounted in the rear of the supply. The fan is fused and the fuse is located in the front under chassis where it can be changed without removing the cover. The ac line is terminated in the front chassis at the switch and at this point the thyrector is also located across the line.

Located at the lower right of the rear chassis is a heavy duty ground connector *which should always be utilized for maximum safety.*

All lettering was accomplished by the application of white dry transfers over black wrinkle paint.

Circuit

The circuit utilizes a full wave bridge rectifier circuit with a capacitor filter of 50 μ F. This provides approximately 5% regulation with a 3 K Ω load. Ten 500 μ F, 450V capacitors provide a total voltage rating of 4500V.

The high voltage diodes, capacitors, and transformer are protected from excessive current when the power supply is first turned on by a series limiting resistor R1. The time delay for relay pickup is determined by R4, which adjusts the time required for C1 to charge and energize the relay K1 which closes its contacts and shorts out R1. Too much delay causes R1 to overheat. One second proved satisfactory.

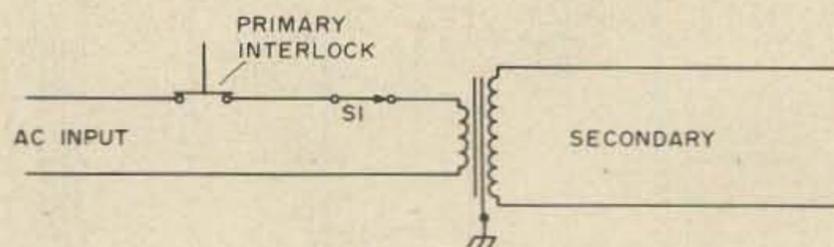


Fig. 2. Primary interlock. When removing cover or panel of supply the primary interlock should open thereby preventing the supply from being accidentally energized. A homebrew spring operated switch or commercial pressure switch works well. The primary interlock must have ample current carrying capability.

The supply also incorporates a voltmeter that measures the output voltage. An inex-



best BUY SURPLUS

DIGITAL MILITARY RECEIVER R-392 URR 24VDC VERSION OF FAMOUS R-390

A great surplus buy. Just released at a small fraction of government cost. Specifications: 500kHz to 32 MHz in 32 bands. Continuous tuning. Frequency is read directly on counter type frequency indicator. Receives CW, MCW, Voice, Frequency Shift Keying and SSB in BFO position. Triple and double conversion. BFO. Selectivity, I.F.: 8, 4, and 2 kHz. Built-in crystal calibrator every 100 kHz. Accurate to 300 cps. 25 tubes. Operates on 24 to 30 V.D.C. at only 3 Amperes. Rugged. Compact, size: 11½" x 14½" x 11". Used but fully guaranteed. Prices FOB Upper Saddle River. Limited quantities. Act now.

Prices: Complete, repairable with schematic \$150. Tested, OK with schematic \$195. Power Conn. \$2.00. Tech Manual \$10.00.

SPACE ELECTRONICS

division of

MILITARY ELECTRONICS CORP.

76 Brookside Drive, Upper Saddle River

New Jersey 07458 / (201) 327-7640

Another great buy. AN/URR-27 Receiver.
105-191 MHz. Continuous tuning. 115 V.A.C.
Like new. \$190.00 FOB Upper Saddle River.

pensive meter can be utilized as the supply incorporates a resistor multiplier string to increase the range of the basic meter movement, *but never use a meter with a metal zero adjusting screw in high voltage circuits!* To choose the correct value of R5 for your meter, use the following formula:

$$R5 = \frac{\text{full scale desired}}{\text{meter reading in amps}}$$

In my power supply I used a 500 μ A meter and wanted to read it to 5000V. The full scale value of .0005 was divided into 5000 and the solved value equaled 10 M Ω .

A resistor is not a high voltage device; therefore to achieve the desired resistance of R5 many series resistors must be used to handle the voltage. I used 10 1M Ω , 1W resistors in series, mounted on a strip of epoxy board, thereby distributing the voltage equally across ten resistors. The epoxy board was mounted to the front chassis on two ceramic insulators.

Before final soldering of my multiplier string, I substituted 1 M Ω resistors as needed

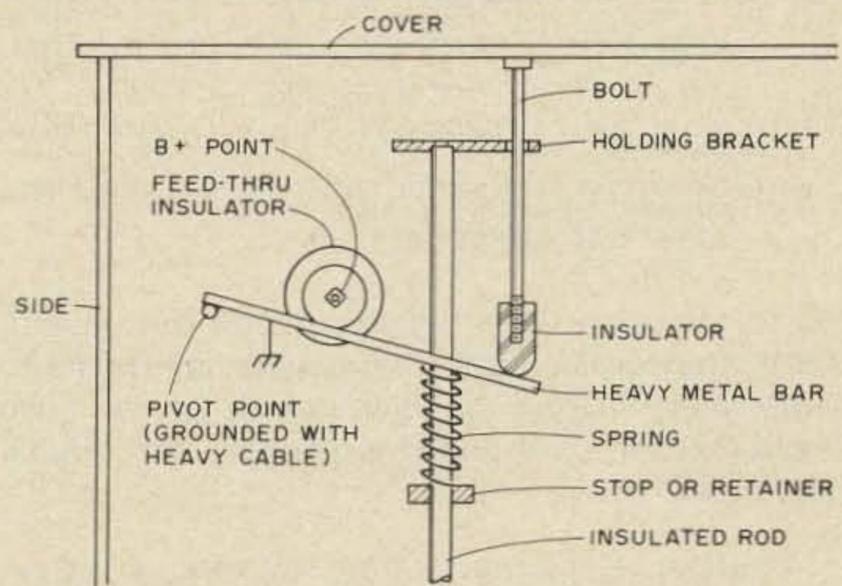


Fig. 3. Secondary interlock. Removing the cover permits the metal shorting bar to move up and contact the B+ point, thereby shorting any dangerous voltage to ground. As long as the cover is removed the B+ point will be grounded. This assembly must be mechanically strong and not subject to movement or bending.

until I had a measured 10 M Ω total resistance. The total resistance must be 10 M Ω in order for the meter to read accurately.

To protect the supply diodes from transients a thyrector-diode assembly is installed at the line input. Also, each side of the line is fused to provide adequate protection to the supply and station line circuits.

Interlocks

All high voltage power supplies should contain an interlock or interlocks. Basically there are two types: the primary interlock and the secondary interlock.

The primary interlock is similar to the power cord assembly on a television receiver. When you remove the back of the set you open the ac line and the television cannot be energized by unauthorized personnel without a special line cord. See Fig. 2.

The secondary interlock (Fig. 3) normally shorts the secondary out thereby discharging any residual charge on the high voltage capacitor string, thereby also protecting the amateur from electrical shock due to an open bleeder or equalization resistor.

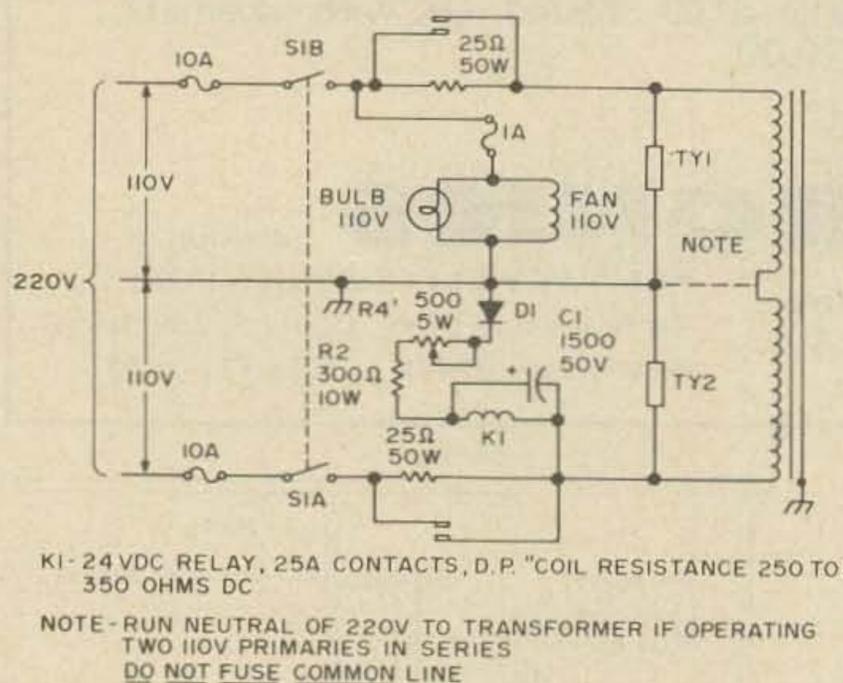


Fig. 4. Alternate 220V primary circuit for use with 220V transformers. The components are similar to those used in the original circuit except two thyrectors are used and the relay K1 is a double pole type.

Neither a primary nor secondary interlock alone will give 100% protection, but utilization of both in one supply will come close.

In essence, in respect to safety, it can be said that a power supply that does not break down requires minimum service - therefore the best protection is to build high voltage supplies with generously designed safety factors.

Transformers

This supply can accept transformers with a secondary voltage of up to 2500V rms with no design changes. A 2500V rms secondary will give an unloaded output of

3500V dc. Even at this dc level there is an ample power supply design safety factor. For a transformer with a 220V primary, see Fig. 4 for wiring details.

Testing

When the circuit was completed I checked the wiring and looked for any possible short circuits. Between ground and any positive voltage points I looked for a minimum of 3 cm separation when the insulation was solely air.

I also inspected each electrolytic capacitor to make sure none of the exhaust ports were obstructed by construction. A defective electrolytic or an electrolytic with a plugged or blocked exhaust port can explode violently.

Before energizing the circuit I reviewed the basic rules of safety.

1. Never bypass an interlock.
2. Fuse the circuit properly.
3. Never operate or test the supply with the cover removed or high voltage terminal exposed.
4. Make sure others in the household are aware of the location and operation of the master power cut-off switch so they can disconnect circuit from line in an emergency.
5. Label *all* high voltage points and equipment as such: DANGER - HIGH VOLTAGE."
6. Voltmeter should read zero and main ac line should be disconnected before removing cover or changing high voltage leads.
7. Make sure the family members know the basics of artificial respiration. Many shock victims die of suffocation before professional help arrives.
8. If you don't understand something, get the facts before proceeding.
9. Properly connect the power supply to a good and permanent earth ground.

Even when the circuit has been inspected and rules followed, there is the potential danger of defective new or used components. I cannot overemphasize that a 3000V dc supply with a 50 μ F filter is a lethal device. Always assume that *all* points in a circuit of this type are dangerous and proceed with that in mind.

...K8VIR

DIAGRAMS

Do you have problems reading a schematic? Here are some obvious and not so obvious hints on how to do it . . .

If you know some fundamentals and are willing to learn a few conventions, reading circuit diagrams is as easy as pie. You can look at a fairly complex print and say, "From what you have told me, the trouble is here!" and point to a certain component. In a few cases you can't be wrong, and generally it will turn out that you are right if you use care and don't back yourself into a corner.

Back when radio was *wireless*, the connections were shown by a drawing that was photographic in character. If you had an antenna (aerial) and a lead-in and a ground rod and a 2-slide tuner and a crystal detector and a bypass condenser and a pair of headphones, you just drew these things as much like they actually appeared as you possibly could (Fig. 1).

Soon it became apparent that the supporting trees were irrelevant, and that the drawings were uselessly detailed. Down through the years a kind of shorthand

evolved which depicted the etherial "soul" of the gadget instead of the fins and tailfeathers.

This was not imposed by some international authority, but evolved through natural growth, and therefore the development has been sound and practical. Occasionally even now a magazine will introduce some innovation in an attempt to outstand their rivals. If it is clear, and helps, everyone will take it up. If it is in the least confusing they get plaintive and abusive letters until they desist and reform.

It is the same with typefaces; they all differ slightly, but they're all clear and easy to read. But you don't, as a rule, examine printing with a magnifying glass. And you just as seldom examine a good print for style and makeup — you are far more interested in what it says.

Figure 2 can be taken in at a glance by any experienced radioman. A is the antenna (the trees are not indicated). G is ground, L

HOT NEWS! for hams...



The premier issue of the 73 HOTLINE, which will be published every other Friday, is scheduled for April 5th. This newsletter will cover all the up-to-the-minute happenings in amateur radio... FCC news... new petitions filed... new actions... DXpeditions... new products... propagation flashes... Hotline Classified ads... job opportunities in the ham field... hamfest and convention news... contest news... all those things hams want right now and not the usual two months late magazine schedule. The 73 HOTLINE will be chock full of last minute news since it will be in the mail just a few hours after deadline closing.

HOTLINE will be mailed to all subscribers (at \$8 per year) by first class mail, marked Rush - Time Value. Our tests have shown that this class of mail seldom arrives later than airmail and often even sooner! HOTLINE will not be a simple typewritten sheet, as some newsletters are, but will be similar to the format of newspapers, with many times the information you might get elsewhere. Use the handy order form below and start getting the news you need to know while it's still news.

NAME _____ CALL _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP _____
 Yes, start sending me one year of HOTLINE for the price of \$8.
 BankAmericard
 Master Charge Card No. _____ Expires _____
 Bill me
 Check enclosed Signature _____
 Mail to: 73 MAGAZINE, Peterborough NH 03458

is the 2-slide tuner. It is just a coil of wire with two sliding contacts on it - the picture doesn't show this too clearly but the diagram does. D is the detector, now called simply a diode. C is the bypass capacitor and the two connected circles are the headset - and doesn't it *look* like one!

But if you have a little background experience, the diagram implies even more than it says. The left-hand slider on L is in series with the antenna, and tunes the set. This slider is adjusted first, usually. The right-hand slider is a step-down auto-transformer arrangement to match the diode impedance which is fairly low; this slider peaks up the signal a little. With only a diode and no amplification whatever, the volume is also low, even with a "good" antenna, 60 ft or more, as high as you can get it. Also, a lightning-switch is a prudent part of the antenna system, all implied in A. As against the low level, this crystal receiver had a startling clarity and lack of distortion that largely made up for the rather faint signal. For some applications it remains a practical circuit to this day. You never need batteries for it.

Later, radio magazines began to diagram transmitters backwards, with the antenna on the left just as it is in the receiver diagram in Fig. 2. To trace the signal path from the master oscillator through amplifiers and harmonic generators, you read from right to left. The receivers were still read from left to right, from the antenna to the loudspeaker or headphones. As the brotherhood became more sophisticated and did more signal tracing, they howled about this just before WWII and now all radio diagrams are scanned from left to right, just as you would read a line of printing.

Figure 3 is a simple example of a transmitter. The X is the Piezo crystal that determines the frequency. Oscillations here are amplified in the triode tube and passed on to the tank circuit at the right; this tank comprises a tuning capacitor and a coil. The antenna lead is tapped on the coil for proper loading.

The triode tube shows a grounded cathode, and a plate element at the top, with the control grid between them. A battery and a telegraph key are also shown. Simple as it is, hams have sent thousands of miles with just such transmitters. Now notice one thing - here it is *assumed* that you know that the

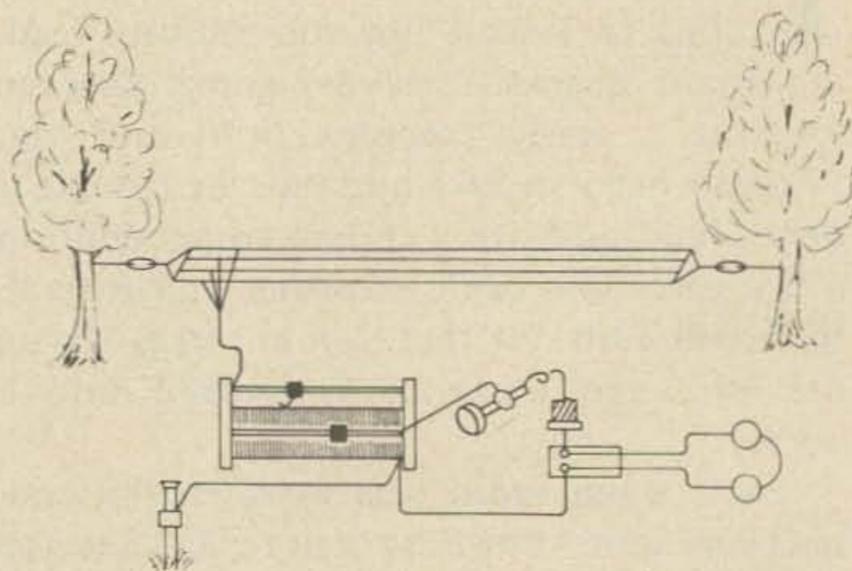


Fig. 1.

cathode must be heated for the tube to operate. The heater circuit, which could be a battery with an on-off switch in one lead is often implied but not shown. The plate circuit plus and minus terminals could be connected to a battery for portable work, but in practice is far more likely to take some kind of power pack: ac supply, transformer with a high-voltage winding, rectifier,

filter, and a low-voltage heater winding for the tube heater. You could use a tetrode or pentode screen-grid tube if you wanted, just by adding a screen voltage supply through a resistor to the plate voltage. The rest of the circuit was essentially the same. I built just such a transmitter in the early 30's.

Figure 4 is a simple receiver. Notice that you still scan it from left to right, just as the signal goes. First the input tuner, then the tube — ah, regenerative, see the little tickler coil in the plate circuit? The regenerative feedback control is that variable capacitor connected from tickler to ground. Hmmm. Makes a very sm-o-o-o-th regeneration control. What's this? A filament-type tube, probably dry-cell operated. The text will say what it is — a 1E4G or a type 30 or 99, probably. Pretty vibration — sensitive, but okay if you don't jar the table. Very quiet and sensitive; no ac hum.

Of course any transmitter operating on any frequency in the same town will overload it, so this circuit is good only in isolated areas. Nowadays it usually doesn't make it as a receiver for serious work.

How could a beginner know all this? A beginner couldn't. But if he actually built either of these circuits, he could tell us many things about them not mentioned here. After he experimented with them a little, he'd no longer be a beginner. When he talked to more experienced hams about his problems, they would no longer have to explain their explanations; the conversation would be enjoyed by both parties.

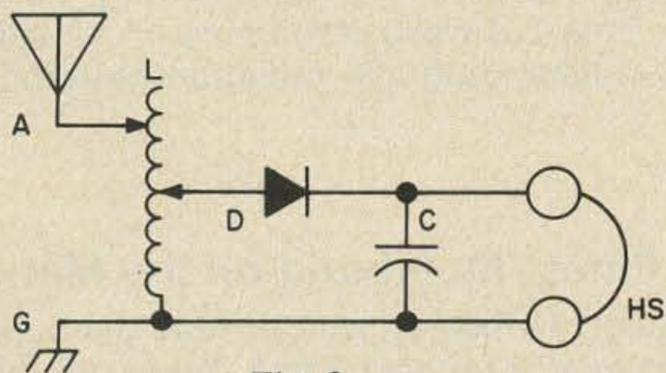


Fig. 2.

It is a curious thing that no one ever pointed out that circuits now follow the signal path, and are drawn from left to right.

Not all of us have visual imaginations, but technicians often do. Take a large complex circuit — a digital computer, a telephone carrier system, transmitter, receiver — and ask the expert a question about something

near the beginning of the chain, something else near the middle, and a third thing near the end. The first he will answer before you finish asking. The second takes a pensive stare and a lengthy pause. The third requires time out for a cigarette.

It's actually funny to watch his mind work, because you can easily follow his line of thought if you know the network yourself. He does not necessarily trace the entire path of the signal; he considers groups and sections where this is possible. But in the main he starts at the beginning and follows the signal path at a good clip until he arrives at the point in question, and then, Bang! — your answer. The hesitation is for travel time to the point of interest; once there he can answer a clear question instantly.

Okay, we know that the signal path goes from left to right. But often there are dc potentials to consider, such as plate voltages.

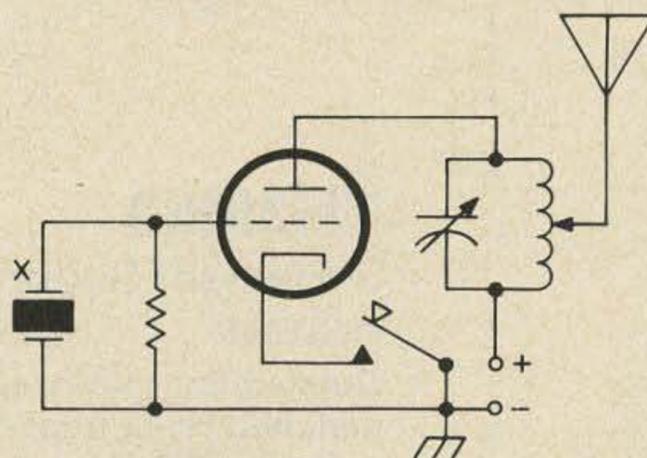


Fig. 3.

Here is another convention that has become a fairly rigid rule, and once again no one has ever mentioned it in print as far as I know. The highest plate voltage is indicated by a bus-bar drawn along the top of the drawing, and this voltage (+250?) drops through the plate load resistance (drawn vertically) to +125V at the plate terminal, down through the tube to maybe +10V at the cathode terminal, and the rest of the way down to zero at the ground bus through the cathode-bias resistor. The whole business is shown more or less vertically. When it isn't, when the plate bus is shown at the bottom with leads going up to the tube, it becomes noticeably more confusing and hard to read.

The vertical potential-concept is particularly helpful in the case of voltage dividers — you just look to see where the voltage tap is, and you know instantly whether it is higher or lower than some other tap.

Don't settle for second. Get the best...

hy-gain Antennas!

TH6DXX

6-Element Super Thunderbird DX
Superior Performance TriBander!

Impressive coverage 10-15-20 meters. Separate, improved Hy-Q traps for each band...SWR less than 1.5:1 on all bands. Takes maximum legal power, up to 1 kw AM, 2 kw PEP. Exclusive Beta Match. Factory pre-tuned. Feeds with 52 ohm coax.

TH3Mk3

3-Element Super Thunderbird Popular TriBand Beam Improved!

Outstanding performance 10-15-20 meters at reasonable cost. Separate, matched Hy-Q traps for each band. Exclusive Beta Match for tapered impedance, DC ground. SWR less than 2:1 at resonance. Accepts maximum legal power and feeds with 52 ohm coax.

18AVT/WB

The Great Wide Band Vertical Super Performer 80 through 10 meters!

Superb omnidirectional capabilities. Automatic band switching. Beefed-up Hy-Q traps. Top loading coil. True 1/4 wave resonance on all bands. SWR 2:1 or less at band edges. Outstanding low radiation pattern. Entirely self-supporting.

18 HT

Incomparable Hy-Tower Finest Multiband on the Market!

Automatic band selection 80 through 10 meters. Unique stub decoupling system isolates electrical 1/4 wavelengths for each band. Takes maximum legal power. Feeds with 52 ohm coax. 24' tower is entirely self-supporting, virtually indestructible. Requires only 4 sq. ft. for installation.

*GECC revolving credit available
Use your BankAmericard or Master Charge*

ELECTRONIC DISTRIBUTORS, INC.

• Communications specialists for over 35 years.

1960 Peck Street, Muskegon, MI 49441 616/726-3196 Telex 228-411

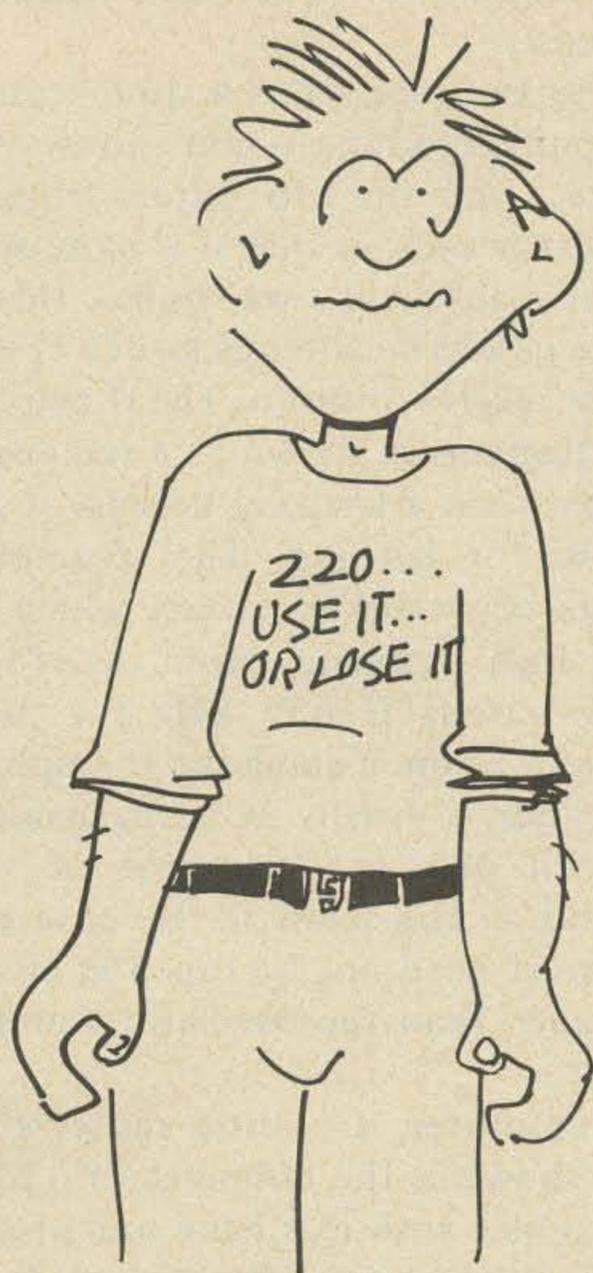


Figure 5 shows the now-forgotten Loftin-White audio amplifier circuit. It is a direct-coupled, wide-band audio amplifier with a high gain. It did require a power pack with about twice the normal voltage output since the two tubes are essentially in series for dc.

When this circuit first appeared, it was invariably drawn with the big voltage-divider resistances (its main feature) shown horizontally, and many of us built them by-the-numbers without really knowing what we were doing. But see how much more plain and obvious a vertical disposition, such as Fig. 6, makes it! The tetrode (or pentode) at the left has its cathode tapped a little way up on the voltage divider, making it slightly positive for the proper operating grid bias (the grid will be correspondingly negative, class A, low distortion.) The screen grid of the input tube is at much higher potential, around 100V. The plate of the tube 1 is connected directly the the grid terminal of tube 2, the output tube.

This is the whole point; what this circuit is all about. It does away with frequency-

limiting coupling condensers (capacitors) and transformers, but places a very high positive voltage from tube 2 grid to ground. If the cathode of the output tube were at ground potential or anywhere near it, the tube life would be measured in seconds. But

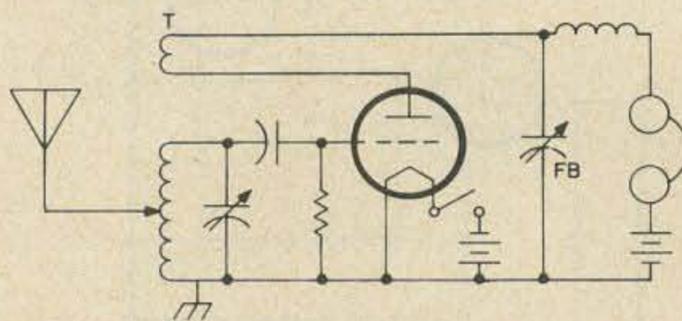


Fig. 4.

it isn't. Instead, it is tapped just under the plate/grid voltage tap for the two tubes, so that the cathode is a few volts more negative (less positive) than the plate/grid tap.

Isn't this wrong? It is certainly different from the input tube, number 1. But don't forget the voltage-drop across the plate load resistance of the input tube! This makes the plate/grid voltage actually applied to them somewhat *less* positive than the cathode tap of the output tube, never mind that the latter is tapped further down on the string. This one little point threw a lot of experimenters in the good old days! It would throw some now, but remember that in a voltage-divider you climb up the ladder and the voltage gets higher as you go. You know what dc voltages you need, so work them out.

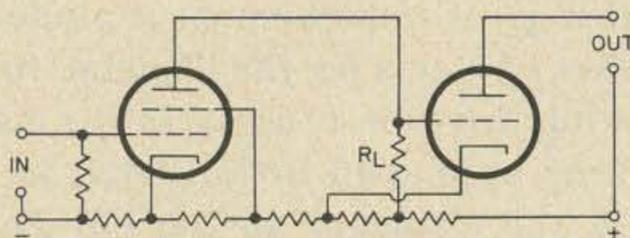


Fig. 5.

Power companies are little interested in circuit theory diagrams, so power diagrams are all but unintelligible to communications men. Their contacts look like capacitors to us, and the wires are a senseless tangle that goes to and from every which-way. But they know the conventions they use, as we do ours, and their diagrams give them the information they want. To each his own, and they can have it!

As the years went by, circuits became ever more complex. At first when we thought of an amplifier, we visualized tubes,

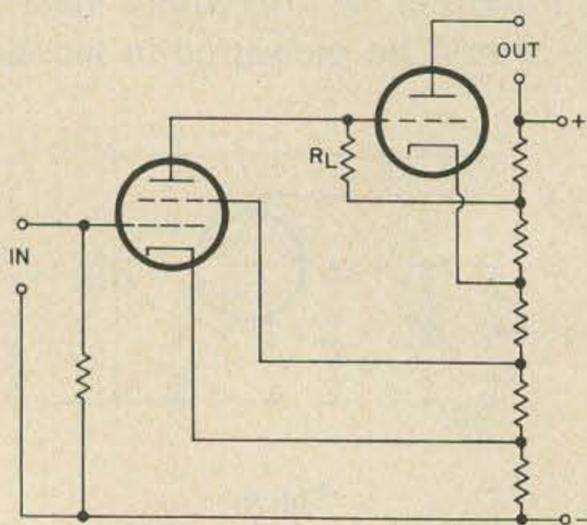


Fig. 6.

coupling transformers, filament rheostats and all the rest of the junk. The modern way is with block diagrams.

Nowdays, an amplifier is not a bunch of things, it is their total, an entity or thing in itself. We draw it as a triangle (to point direction) with the output from the apex. This amplifier (Fig. 7) may have vacuum tubes, transistors, or it may even be an integrated circuit full of microbic (well microscopic, then) amplifiers, diodes, stabilizers, and all sorts of esoteric stuff. You just accept it as such and such an amount of gain and let it go at that — there's plenty more to consider without dissecting the amplifier besides. If you want to know how to connect it, or the exact internal working, you look up the IC in the book.

Another great improvement is numbering tube-socket contacts on the diagram, to save you looking the tube type up in the manual and making your own little sketch to help you trace the elements. In the old days all tubes had four prongs, all were surface wired, and the filaments were always the thick pins 1 and 4, the grid was 3 and the plate 2. But Noval tube bases may be connected any way at all, depending on the particular type. So I'm grateful to the character who started numbering tube elements, bless his little heart.

Now let's pick a real dilly — a modern (more or less) transceiver. It has only one tuning control which acts as a variable frequency oscillator (vfo) to tune the receiver

and the transmitter to the same frequency simultaneously.

Actually, the receiver is a quite conventional superheterodyne — you know how that works — and the vfo differs from the usual oscillator only in that it is more stable and better calibrated, we hope, than is usually the case. The antenna switch (Fig. 8) rests in the receive position. The rf amplifier in block diagrams is shown as a rectangular block rather than a triangle, because it gives more room for labeling. The rf amplifier goes to the converter or mixer, which also gets some high frequency from the vfo and the mixer output is 455 kHz for the i-f amplifier and so on. Tuning the rf amplifier? Good question — usually it is mechanically ganged with the vfo capacitor in usual fashion, but if the band to be covered is narrow, the rf need not be tuned at all. It is a lot broader than the oscillator tuning in any case.

The transmitter is a little more tricky. The band shown is the 80-meter or 3.5–4.0 MHz, so to mix with this band and produce 455 kHz for the i-f amplifier, the vfo tuning range must be offset 455 kHz one way or the other, i.e., 3.955 to 4.455 — fine for the receiver, but plenty no-good for the transmitter. Because most of this oscillator range is completely out of the band. In the receiver, we subtract the *signal* from the

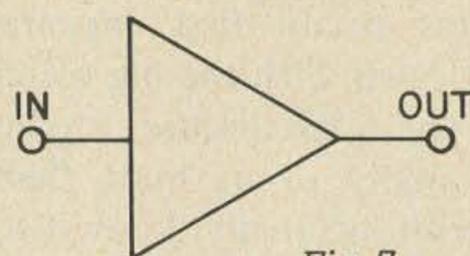


Fig. 7.

oscillator frequency to give 455 kHz which the i-f amplifier will accept. In the transmitter, we *subtract* 455 from the *oscillator* signal to get the proper transmitting frequency band, 3.5–4 MHz.

To make this a bit plainer, suppose you were receiving an AM signal on 3.950 MHz. This would mix with the vfo frequency tuned to 4.405 and the difference frequency, or lower sideband if you like, would be 455 kHz.

When you want to transmit — the vfo, still putting out its tuned 4.405 kHz mixes with 455 in the *transmitting* converter, and



THE OUTSTANDING 20 METER MONOBAND BEAM

ANTECH LAB gives you :


- QUALITY CONSTRUCTION
- OUTSTANDING PERFORMANCE
- REASONABLE PRICE

THE BELIEVABLE FEATURES OF THIS QUALITY BEAM ARE:

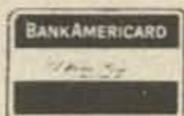- 8.5 Dbd Gain
- 22 Db FB RATIO
- 6061-T6 ALUMINUM THROUGHOUT
- 20 FOOT 2" OD BOOM w/.065" WALL
- 1.1 to 1 SWR
- CORROSION PROOF HARDWARE
- TURNING RADIUS 21' 6"
- LONGEST ELEMENT 36'
- WIND SURFACE AREA 4.3 SQ. FT.
- HANDLES MORE THAN LEGAL POWER
- COAXIAL GAMMA MATCH
- FULL CIRCLE CLAMPS FOR ALL ELEMENT TO BOOM CONNECTIONS
- WIND LOAD FACTOR 129 LBS AT 86 MPH
- WEIGHT 40 LBS.

PRICE
\$114.95
 FOB ST. LOUIS

WRITE FOR COMPLETE SPECIFICATIONS AND FACT SHEET



ANTECH LABS
 8144 BIG BEND BLVD.
 ST. LOUIS MO 63119

ANTECH LABS, PEOPLE WHO CARE ABOUT THE PRODUCTS THEY SELL

TOP QUALITY ANTENNAS AVAILABLE FOR 6 THROUGH 40 METERS

comes out the difference frequency of – surprise! – 3.950 kHz. This goes through a filter to eliminate other frequencies and harmonics and upper sideband and such like, is amplified, modulated with your voice and connected to the antenna by operation of the antenna switching relay. Thus, the transmitter itself is also a kind of superheterodyne, and in the case of SSB, the similarity between transmitter and receiver is still more striking.

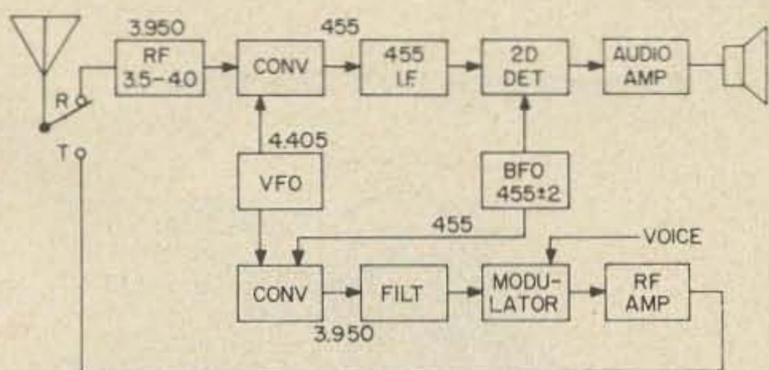


Fig. 8.

The British invented this thing in World War II, and we built one version for them, known as the "Tank Set" because it was used for communication between tanks. It had weird-looking dials with adjustable de-

tents for pretuned settings, which dials had Russian characters on them for the benefit of our Eastern Allies, who used the sets, too. The set had an 807 in the output which loafed along with +350V or so on it. It also had a tank-to-tank high-frequency transmitter and receiver in it, a superregen deal which the hams on this side of the water promptly discarded to make room for the power pack. They discarded it on the other side of the water too – nobody ever said the British aren't good radiomen! The receiver is an excellent one, and is often used in the British Isles as a DX broadcast receiver. It is even used for hamming, where low power suffices.



Transistor circuits follow the same lines as tube circuits as regards signal path and dc potentials. They have the benefit of tube experience to build on, and present no special difficulties as far as the diagrams are concerned. If you have a reasonable command of the fundamentals, you should now be able to read a diagram nearly as fluently as a comic strip!

...WB2PAP


CIRCUITS, CIRCUITS, CIRCUITS...

The following circuits have appeared in the referenced books, magazines, application notes, etc. While we try to reproduce all of the information that should be needed by an experienced constructor, readers may want to avail themselves of the original sources for peace of mind.

Readers are requested to pass along any interesting circuits that they discover in sources other than U.S. ham magazines. Circuits should be oriented toward amateur radio and experimentation rather than industrial or computer technology. Submit circuit with all parts values on it, a very brief explanation of the circuit and any additional parts information required, give the source and a note of permission to reprint from the copyright holder, if any, and the reward for a published circuit will be a choice of a 73 book. Send your circuits to 73 Circuits Page, 73 Magazine, Peterborough NH 03458.

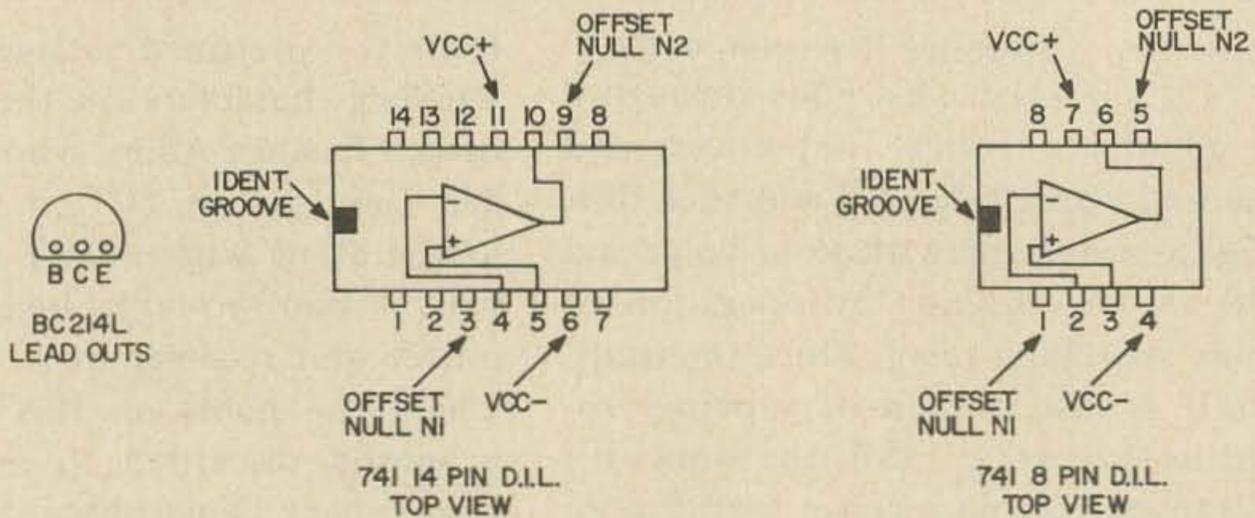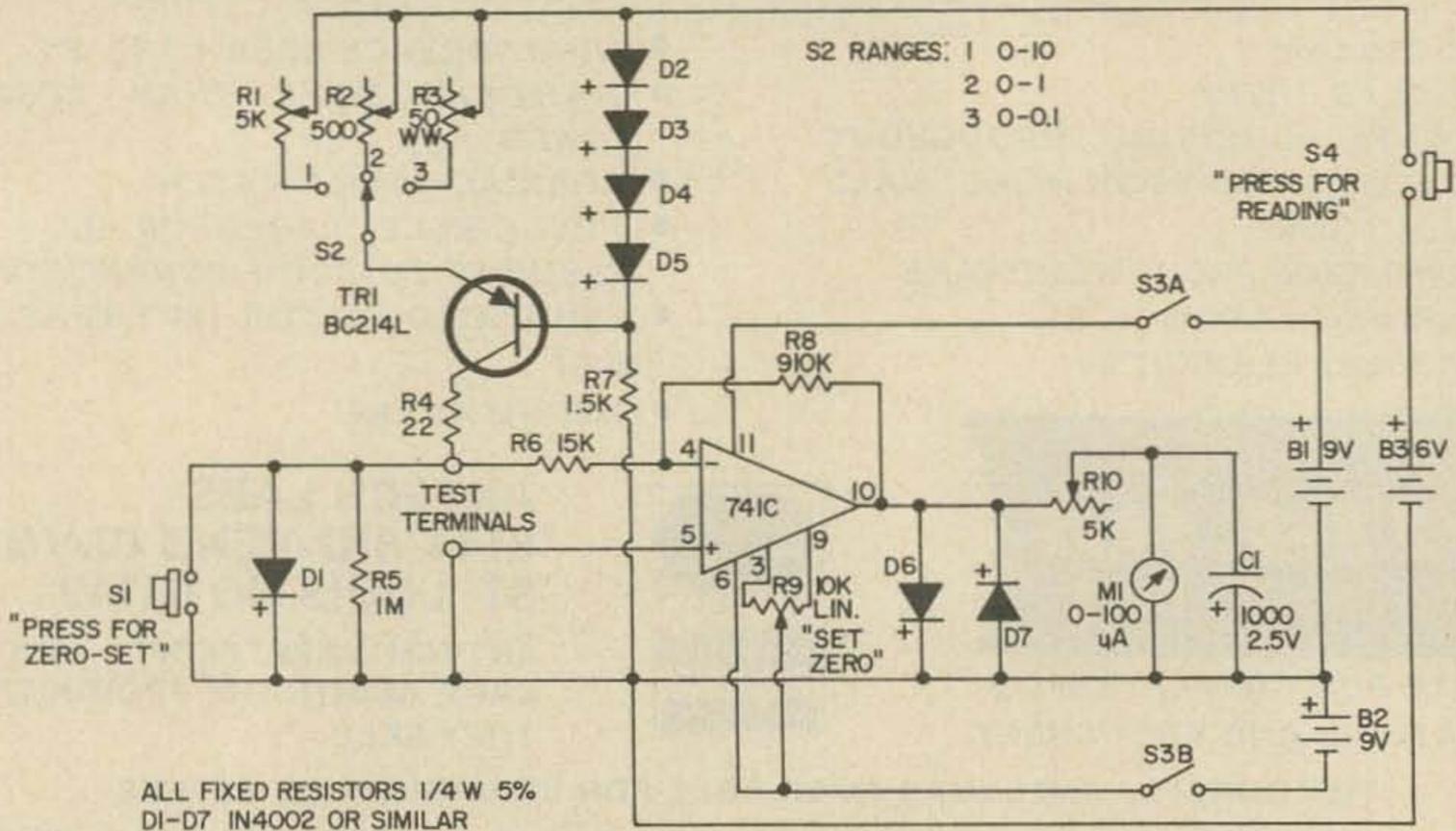

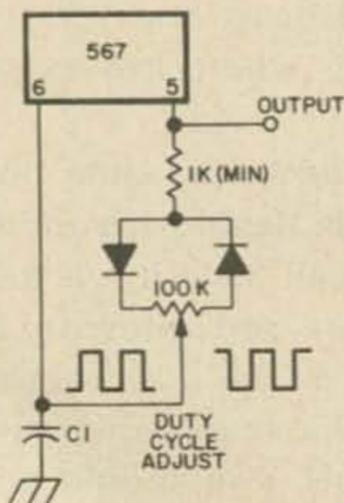
Full circuit diagram for the ohmmeter. It is capable of measuring resistance down to less than 0.01Ω . The two circuit points marked 'A' are wired directly together.



PULSE GENERATOR

Courtesy of Signetics Catalog


PATCHWORK FOR THE HW-101

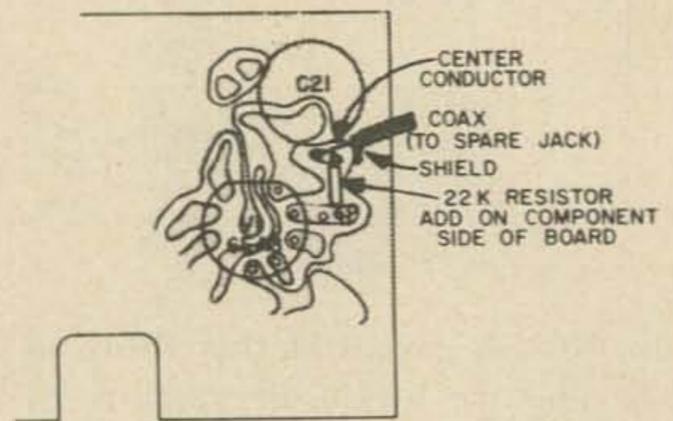

MODULATOR CIRCUIT BOARD (Foil Side)


CB Channel Assignments

Channel Number	Frequency (MHz)	USE			
1	26.965	Voice, same licensee only	Yellow (27)	27.145	R/C & walkie-talkies
2	26.975	As above	16	27.155	Voice, same licensee only
3	26.985	As above			
Brown (24)	26.995	R/C & walkie-talkies	17	27.165	As above
			18	27.175	As above
4	27.005	Voice, same licensee only	19	27.185	As above
			Green (28)	27.195	R/C & walkie-talkies
5	27.015	As above			
6	27.025	As above	20	27.205	Voice, same licensee only
7	27.035	As above			
Red (25)	27.045	R/C & walkie-talkies	21	27.215	As above
			22	27.225	As above
8	27.055	Voice, same licensee only	A	27.235	Business Radio Only (HELP?)
9	27.065	Emergency use only	B	27.245	As above
10	27.075	Voice, any CB licensee	23, Blue (C)	27.255	Voice, any CB license, also R/C & walkie-talkies, also Business Radio
11	27.085	As above			
Orange (26)	27.095	R/C & walkie-talkies			
12	27.105	Voice, any CB licensee			
13	27.115	As above	D	27.265	Business Radio Only
14	27.125	As above			
15	27.135	As above	E	27.272	As above

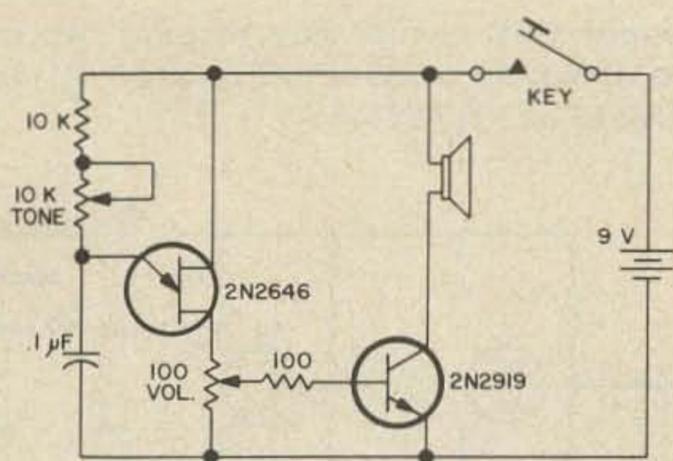

CODE PRACTICE OSCILLATOR

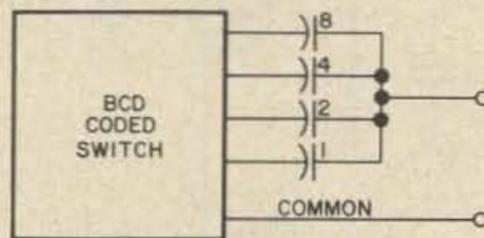Here is a code practice oscillator with variable tone and volume. Thanks to WB9IDI for this circuit.



SIMPLE DECADE CAPACITANCE

Using a BCD coded switch capacitor in parallel can be switched in or out. Thus by using 4 capacitors any value from 1 to 16 can be obtained, however since most BCD switches are from 0 to 10 a decade is obtained. Capacitors used are in the relation 1, 2, 4, 8 with the proper multiplier 1µf, 2µf, 4µf, 8µf. Keep all leads as short as possible. Thanks to L. S. Naguiney WA3GBC/1, for this circuit.

wanted

YOUR GEAR...

We pay top dollar or trade...

Tell us what you have — Here's a partial list of what we want:

- RT-742/ARC-51BX ... RT-662/GRC-106
- RT-743/ARC-51A ... RT-698/ARC-102
- RT-823/ARC-131 ... Magnavox FM-622
- RT-857/ARC-134 ... RT-859/APX-72
- RT-524/VRC ... RT-246/VRC
- R-442/VRC ... R-390A/URR
- RT-648/ARC-94 ... AN/TRC-68
- AN/VRC-24 ... AN/URC-9
- CU-1669/AR ... 490T-1 ... 618T-1-2-3
- C-6287/ARC-51BX ... AN/PRC-25
- AN/PRC-77 ... Wilcox 807

We buy all types of military test equipment ... radios, etc. Do you have a HAMMAR-LUND SP-600, H-P, or TEKTRONIX equipment? If you hate money ... we'll trade for NEW HAM GEAR!

COLUMBIA ELECTRONIC SALES, INC.
 Box 9266-A; No. Hollywood, CA 91609
 Phone: (213) 764-9030

LOOKING FOR A NEW CHALLENGE?



... then build a TV camera!

ONLY SOLID-STATE CAMERA AVAILABLE IN KIT FORM OR FACTORY ASSEMBLED COMPLETE KIT WITH VIDICON TUBE ONLY \$157.70. POSTPAID DELIVERY ANYWHERE IN USA, CANADA and MEXICO. OPTIONAL AUDIO SUBCARRIER \$18.95 WRITE or PHONE NOW FOR COMPLETE CATALOG OF KITS, PARTS and PLANS. DIAL 402-987-3771

1301 N. BROADWAY ATV Research DAKOTA CITY, NEBR. 68731

T.R.I.

Frequency Counter 1 KHz-60 MHz

(130-160 MHz with optional converter)

Reg. \$299

See Nov. '72 CQ & April '73 QST Reviews



A frequency counter with a range of 1 kHz to 60 MHz (or 130-160 MHz when used with our TRI-160 converter). With a resolution of 1 kHz or 1 Hz (at 1 ms. or 1 s. gate times). It can be operated on either AC or DC, with complete overload protection. Plus a stability aging rate of 1 part in 10⁶/week. And the whole unit is a mere 7" deep by 2 1/2" high! Superb laboratory precision quality at LESS THAN KIT PRICES. Call or write for literature and trade in or our LOW INTRODUCTORY PRICE.

One year warranty — NO ONE ANYWHERE BEATS OUR DEAL!!!

AMATEUR-WHOLESALE ELECTRONICS


8817 S.W. 129 Terrace, Miami, FL 33156

Days (305) 233-3631


Nights-Weekends (305) 666-1347




MORE CIRCUITS...

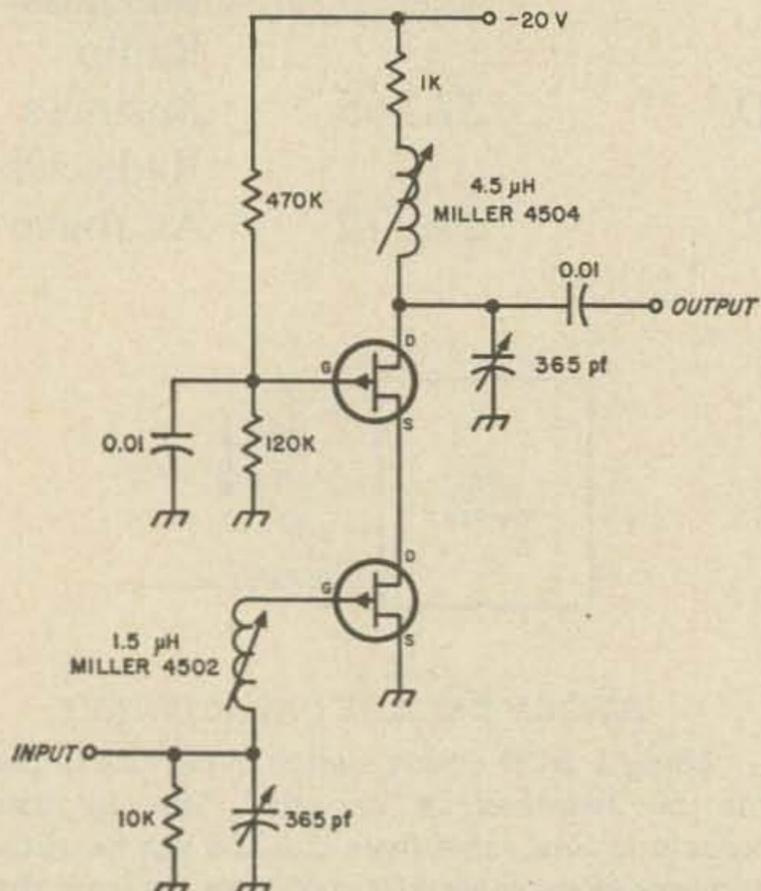

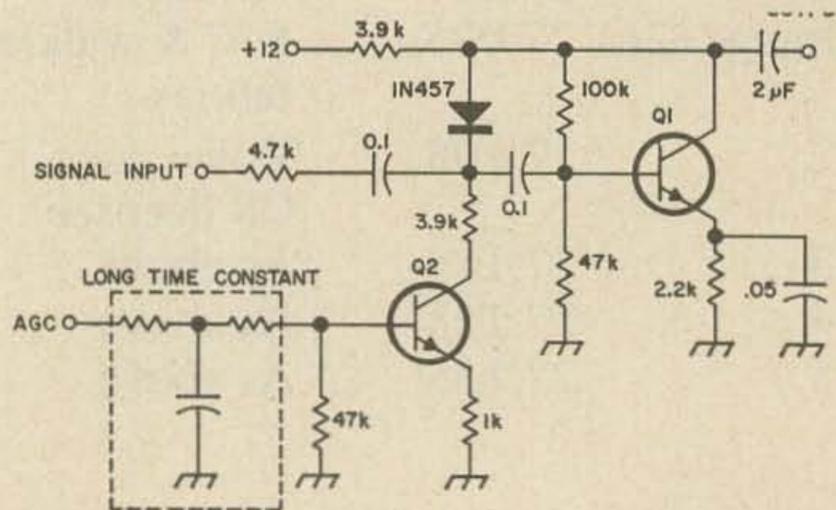This 30 MHz if stage uses two FET's connected in the cascode arrangement to provide 20 dB gain without neutralization; the bandwidth is 4 MHz. Both FET's in this circuit are 2N3819, MPF105 or TIS34. With a negative supply voltage, the 2N4360 or TIM12 would be suitable.




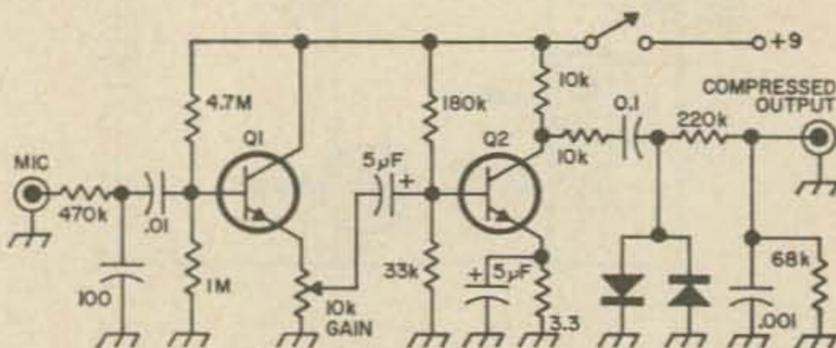This super AGC circuit only requires two transistors to obtain up to 60 dB of control. Q1 and Q2 are 2N1613 or HEP-254.




Two stage clipper/preamp will increase the talk power of your rig. Transistors Q1 and Q2 are 2N1304, 2N2926, 2N3391, SK3011, or HEP 54. The diodes are IN456 or HEP-158.

INTEGRATED CIRCUIT CHANNEL SCANNER

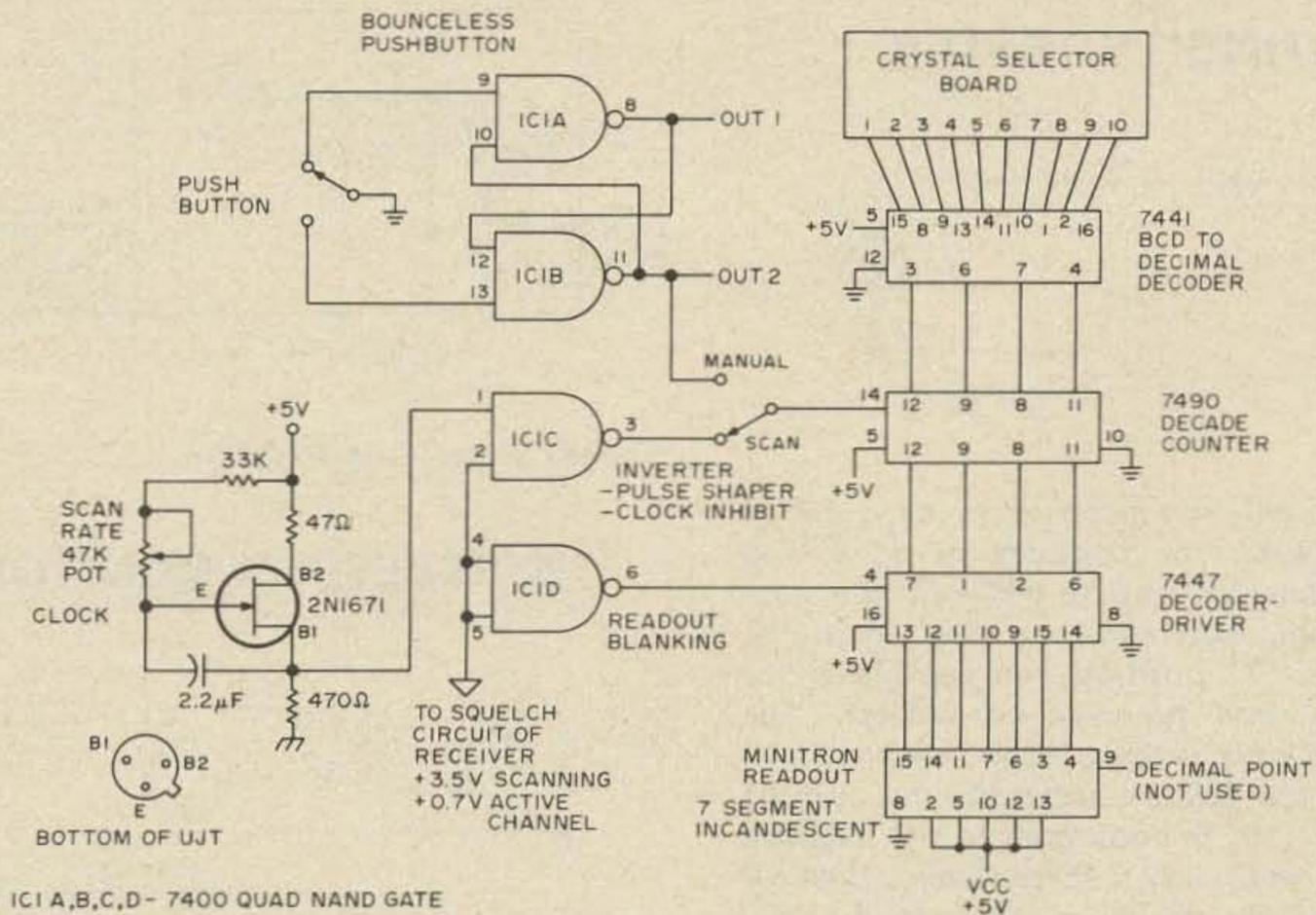


This unit is capable of scanning a series of channels in a receiver by switching crystals in and out of the first oscillator. It works like this. A UJT is used as a clock to produce a series of pulses. This particular UJT is fairly expensive (\$2-\$4) but it operates well on 5V. The pulses are of the wrong polarity and quite noisy. To correct both situations, they are fed into one gate of a quad two-input NAND gate, a 7400. The output of this gate is connected through a switch and thence to the counter. Note: Bypass 5V supply frequently .01-.1μF. Thank you George Cserenyi and Brian Hyndman VE7BHY.

ANTI-TIMEOUT TIMEOUT TIMER

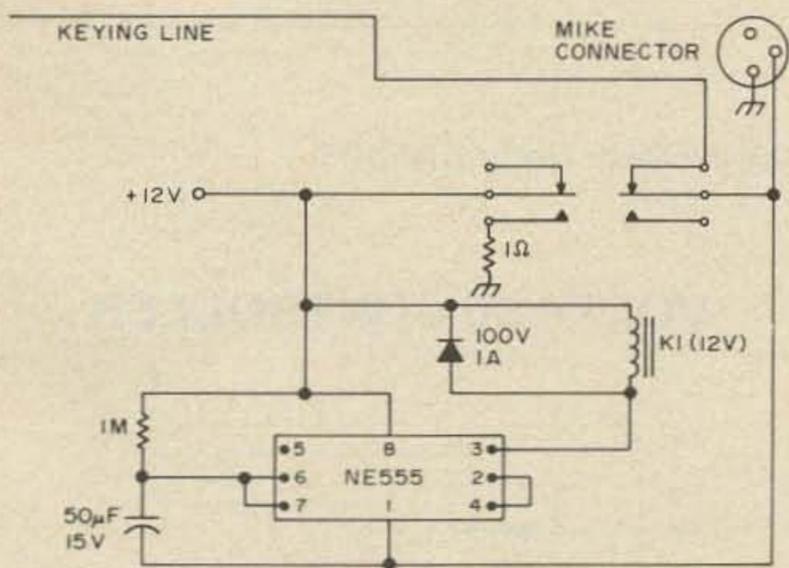


This circuit is designed to timeout your rig before it times out the repeater. It uses a simple 1 minute 59 second timer. It is shown wired for a TR22 but can easily be modified to work with any rig. Total cost about \$5. From the 31/91 KaChunker.


12 MHz VFO FOR A TR22

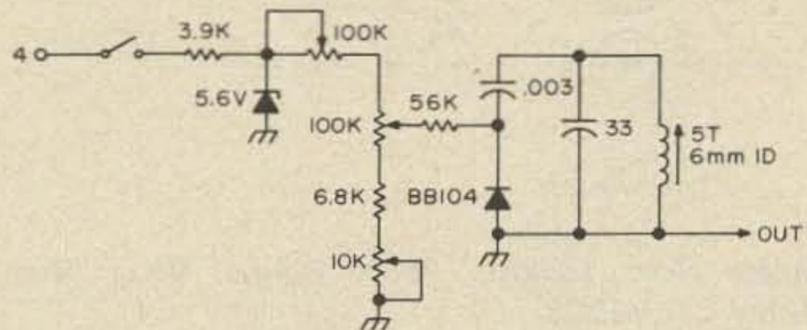

S-METER FOR REGENCY

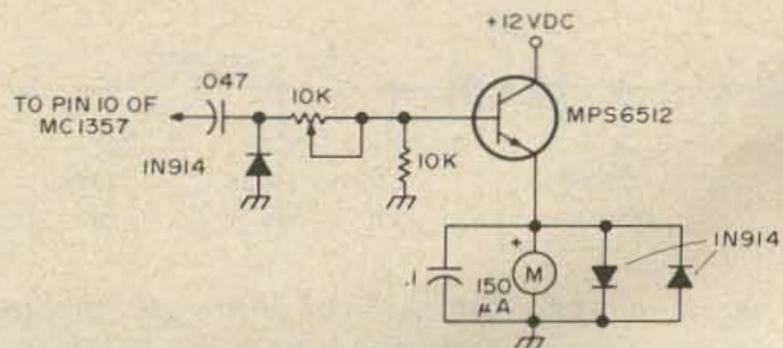


LED VOLTAGE AND CONTINUITY TESTER

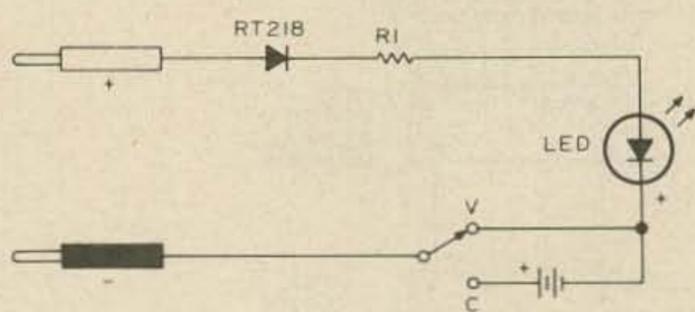


This tester will tell you polarity (+ or -, 6V or 12V). It will check for presence of dc at any terminal or connector and it will test the continuity of a bulb, fuse, cable or wire. When the switch is in the "V" position you can check for voltage polarity and presence of voltage. The ED150 will light only if the positive (red) test lead is connected to the positive voltage source and the negative (black) lead is connected to the negative terminal. It will work only if there is more than 3V present, and will be ruined at 15V. In the "C" position a 9V battery is added to the circuit. The ED150 will light when the test leads are connected to anything that will carry current provided that the "anything" is electrically OK. Parts needed are: R1 = 470Ω, 1/4W, LED = Sprague ED 150 (or 155), diode = RT218, 9V battery, SPDT switch, miniature box, grommets, battery connector, two 3-terminal strips. Thanks from the Sprague Products Co., No. Adams MA 01247.

SUPER SIMPLE DIODE CHECKER

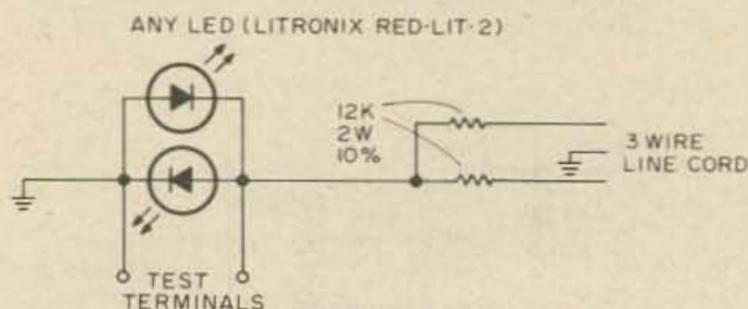


Thanks Noel Calvin, 2683 Buena Vista Way, Berkley CA 94708.

AM or FM CLIPPER

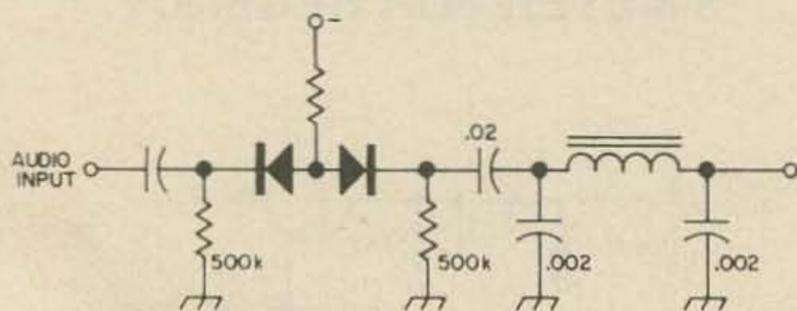


A good clipper for AM or FM use includes adjustable clipping level and a harmonic filter.

SIGNAL INJECTOR

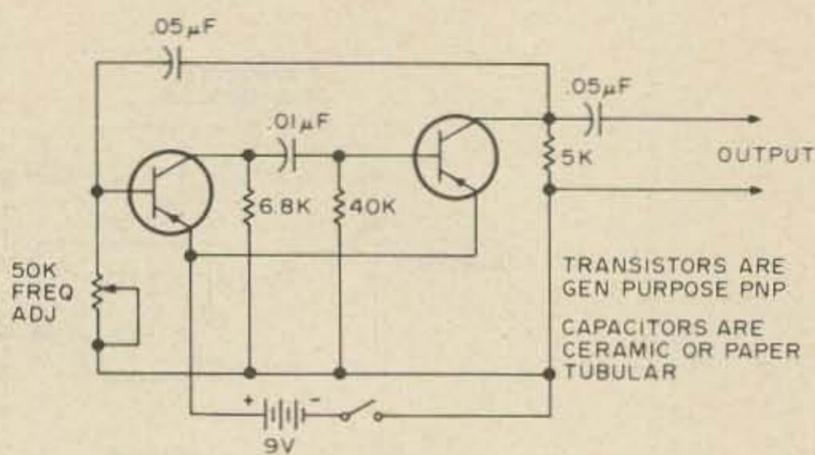


Thanks Steve Uhrig WA3SWS.

WIRELESS CW MONITOR

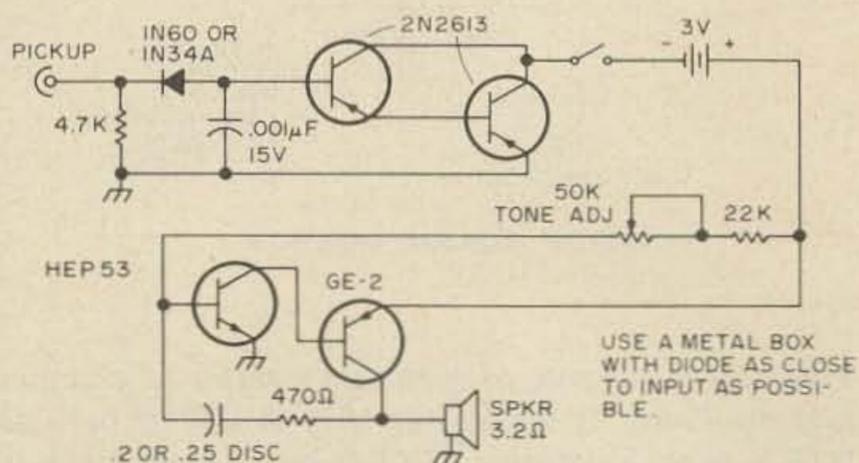


USE A METAL BOX WITH DIODE AS CLOSE TO INPUT AS POSSIBLE.

FIELD STRENGTH METER

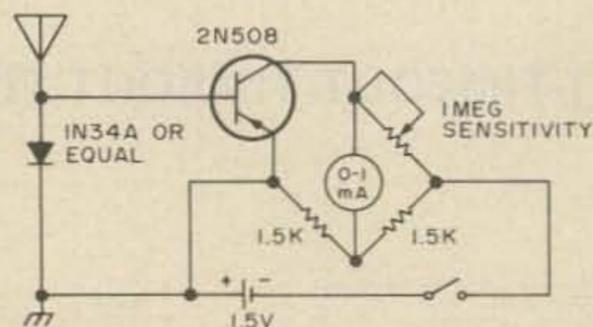

Thanks Steve Uhrig WA3SWS.

VOLTAGE CONTROLLER

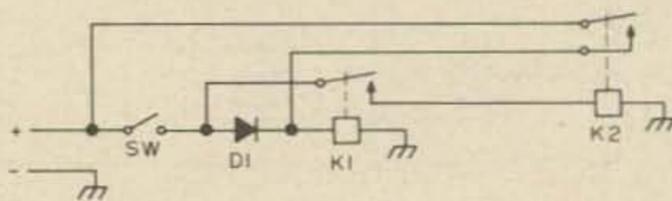

K1 on first and off last. K2 on last and off first. Handy for Pentode or Tetrode power amplifiers where K1 controls plate volts and K2 controls screen volts - overload dekeying, etc. Thanks W8UFN.

73 Books & Stuff

the Books

NOVICE CLASS STUDY GUIDE

\$4

The world's easiest to understand book on the theory required for the Novice amateur radio license exam. Frustrated by fundamentals? Read this book. One simple reading should carry you through the exam.

GENERAL CLASS STUDY GUIDE

\$6

This book will help you to really understand the theory and enable you to easily pass the FCC exam. This is not a Q&A manual for memorization. Study this book and go into the exam with confidence.

ADVANCED CLASS STUDY GUIDE

\$4

Thousands have used this book to help them breeze through the Advanced exam with no strain. This is the ONLY study guide published which covers ALL the material you will have to know.

EXTRA CLASS STUDY GUIDE

\$7

Does the theory required for the

Extra Class exam panic you? No need, for this book reduces it to easy comprehension. Many amateurs find that a quick reading through this book is enough to get them through the tough Extra Class exam. Face that exam with confidence.

1974 FM REPEATER ATLAS

\$1.50

Listings by states (or countries) and cities of all repeaters, both open and closed, in the world. Periodically updated. Handy size for mobile use.

FM REPEATER CIRCUITS MANUAL

hardbound \$7
softbound \$5

Contains almost every conceivable circuit that might be needed for use with a repeater. All circuits explained in detail. All aspects covered, from the operator to the antenna. Also contains chapters on setting up a mobile station, plus much more.

HOW TO USE FM

\$1.50

This book presents the basics of two meter FM operation and repeaters in short form with the end in mind of getting you on FM quickly and easily.

It is easy to make some blunders when you are getting started with anything new. It is also embarrassing. A fast reading of this book should help you avoid the pitfalls.

VHF PROJECTS FOR AMATEUR AND EXPERIMENTER

\$5

A must for the VHF op. Opening chapters on operating practices and getting started in VHF, both AM and FM, followed by 58 chapters on building useful test equipment, modifying existing and surplus gear, building complete stations, both fixed and portable, linears, converters, control units, preamps, band scanners, antennas, noise suppression, plus many more.

FASCINATING WORLD OF RADIO COMMUNICATIONS

\$4

All about broadcast band DXing, tuning the tropical DX bands, DXing radio amateurs, antennas for short-wave, radio licenses, pioneers in electricity and radio, commercial broadcast stations, WWV, etc.

TVI

\$1.50

Discusses all types of interference problems in great detail with recommended steps to cure these problems. Good for both the amateur and citizens band operator. Try this cure and suffer no longer.

IC PROJECTS

\$4

This book tells how to understand and use ICs, with numerous construction projects.

COAX HANDBOOK

\$3

All about coaxial cables, connectors and applications. It's all here — pictures, part numbers and specifications for all types.

SOLID STATE PROJECTS

\$4

More than 60 projects of interest to anyone in electronics. The devices range from a simple transistor tester to a ham TV receiver. This collection will help you become more intimately acquainted with zeners, ICs and varactors, etc.

TRANSISTOR PROJECTS

\$3

Crammed full of home construction projects, from receivers to transmitters and all in between. Chapters include such articles as zener diodes, how they work, how to use, test and buy them; integrated circuits; how to design transistor amplifiers; and many more.

DX HANDBOOK with MAP

\$3

How to work DX, how to get QSL'S, country lists, award lists, QSL bureaus, maps of the world, great circle maps centered on major U.S. cities, DX bearing charts for major U.S. cities, how to go on your own DXpedition, and much more. Wall size DX map of the world included.

more Books

INTRODUCTION TO RTTY

\$2

In this book the world of radio-teletype is explained in an easily understood manner for the beginner. There's also a chapter on RTTY Art which will teach you everything you need to know in order to be a RTTY Artist. The last part of this book contains a bibliography of everything published about RTTY since 1952.

RTTY HANDBOOK

\$6

A comprehensive book covering all areas of radio teletype, from getting started with the basic principles, what equipment to procure and how to make it work. The only up-to-date book available on the subject. Well written, easy to read and understand.

73 USEFUL TRANSISTOR CIRCUITS

\$1

Useful transistor circuits for audio, receivers, transmitters and test equipment. 47 chapters with circuit diagrams for each, complete with component values, etc. A must for the solid state home brewer. Easy to read and to understand.

SLOW SCAN TELEVISION HANDBOOK

hardbound \$7
softbound \$5

This excellent book tells all about it, from its history and basics to the present state-of-the-art techniques. Contains chapters on circuits, monitors, cameras, color SSTV, test equipment and much more.

DIODE CIRCUITS HANDBOOK

\$1

115 diode circuits including power supply application, regulators, ac meter applications, receiver detectors for AM-FM-SSB, noise limiters, squelch, AGC, varicap tuning, audio clippers, compressors FM modulators, RTTY keying, varactor multipliers, noise generators,

VHF ANTENNA HANDBOOK

\$3

Would you believe that the secret to success in VHF/UHF is in the antenna system? This is no earth shaking discovery, but it's true. A complete, detailed book with descriptions, dimensions, tuning data, diagrams and photos. Antennas from the instant coathanger to the giant collinear beam can be found here.

DIGITAL CONTROL OF REPEATERS

hardbound \$7
softbound \$5

Here's a book for the FMer who wants to design and build a digital repeater control system. Contains sections on repeaters, basic logic functions, logic circuit design, control systems, support circuits, mobile installations, touch-tone, plus a special section on a "mini" repeater control system.

CONVERTING COMMERCIAL FM GEAR

\$2

General information on commercial FM gear with specific conversions for Motorola equipment.

108 QUESTIONS AND ANSWERS

\$2

Discussions of transmitting, receiving, antennas, power and audio measurement devices, etc.

the Stuff

73 CERTIFICATES

WAAS

\$1

Worked Almost All States — Proof of your having worked 49 of the 50 states. It is for those who are just unable to get that last state confirmed.

RRCC

\$1

This Real Rag Chewers certificate is awarded only for the feat of a non-stop QSO for a period exceeding six hours with no time out for anything. Order must be accompanied with date/time (GMT) of start/end of contact, station contacted, and your call sign.

DXDC

\$1

Available for those who present proof of contact (copy of log) with 10 different countries. Awarding this certificate makes you a member of the DX Decade Club.

RTTY-DXDC

\$1

Frame and hang this one above your machine. All operating award for those who have submitted proof of 2-way teletype communications with 10 countries. Endorsement provisions for different bands.

SSTV-DXCC

\$1

Dress up the shack with this award for 2-way Slow Scan Television communications with 10 countries. Endorsement provisions for separate bands.

ALL MODE DXDC

\$1

How many can qualify for this one? An award for 2-way communications with 10 countries using CW-SSB-RTTY-SSTV modes.

UNDERSTANDING XYL/OM \$1

An unusual certificate — get one and keep your mate happy. An award to those who have the good fortune of having an understanding partner who appreciates all good things about amateur radio (staying up all night, spending money for rigs, etc.).

CHC

\$1

Presented to those who submit a sworn statement that they have never received a certificate for radio operating and if they ever receive one, they will hate it. This certificate should be your first before you accidentally do something and receive a certificate for it. This attests to your membership in the Certificate Haters Club.

Be certain to enclose sufficient postage for the return of your QSLs.

73 BACK ISSUES

VOL.1

\$4

This is an assortment of twelve different back issues of 73 from the years 1960 through 1964. Normally these back issues would cost you \$1 or more each, but since this assortment is our choice instead of yours you benefit with a big bargain. Here is a good way to build up your technical library with hundreds of interesting and valuable technical articles and construction projects.

VOL. 2

\$4

Twelve different back issues of 73 from the years 1965 through 1967. These are the real vintage years of 73 for home builders of transistorized gear. Lots of VHF projects and gadgets galore. See for yourself what 73 was doing back when QST was

more Stuff

the Stuff

(continued)

still bringing you only tubes. At this price you get our choice of back issues. This is an excellent way to fill in missing back issues, if you like to gamble.

VOL. 3 \$4
 Twelve different back issues of 73 from the years 1968 to 1972. These bundles are already made up so you have to accept our choice at this price. Individual issues for most months are still available for \$1 each for these years.

MAGNETIC CALL SIGNS \$4

Let the world know that you are proud of your ham call. These magnetic call signs will adhere to the side of your car, and they won't fall off at high speeds.

U.S. MAPS \$1

These wall sized maps show the states and call area. They are specially designed for coloring to show your progress toward the Worked All States award of ARRL or the Worked Almost All States award put out by 73 (for proof of contact with 49 states). Since you will probably be wanting to work for the award on several bands you will want several maps. They come in groups of four.

WORLD DX MAP \$2

This is the same wall-sized DX map that is included with the DX Handbook except it comes to you rolled up instead of folded. This is so you can put it on the wall or have it framed. The map is designed with all country prefixes indicated and space for you to color in the countries as

you work them. Visitors can see immediately how much of the world you have contacted! The zones are on the map as well as prefixes. Maybe you need several maps.

CUSTOMIZED DX BEARING CHART \$4

An amateur who works for a big computer company has a program which permits him to plug in your location and have it print out the bearings of all the countries of the world from your shack. Once you have this list you will use it for every DX contact. The chart gives the bearing and distance to all major cities and countries. Be patient when you order for these have to be run through in groups so that we can offer them to you at such a low cost.

73 BINDERS \$5

These binders are a gorgeous red and come with the nicest set of year stickers you've ever seen. The perfect thing for storing your issues of 73 so that they won't get lost or spilt on, or into the hands of the Jr. Op. Dress up your shack with these binders.

LAPEL BADGES \$1

Name and call identifies you at club meetings, hamfests, busted pot parties. Hand engraved by skilled New Hampshire craftsman with loving care. Only one lousy dollar. Send first name and call.

CALL LETTER DESK PLATE \$2

How about dressing up your operating table with a desk plate showing your first name and call? These embossed desk plates are nice — and inexpensive. No zero available, sorry. There is room for twenty letters and spaces total.

 
 NAME _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP _____
 SEND ME: _____
 SIGNATURE _____
 CARD # _____
 EXPIRATION DATE _____
 TOTAL ENCLOSED _____
 PRICE: _____

73 Magazine, Peterborough NH 03458

the String

73 DUZZII

REASONS TO SUBSCRIBE:

One Year Sub Saves

A one year subscription is only \$7 — 58¢ per issue. That's a 42% savings. (Egad!)

Two Year Sub Really Rips Us Off

A two year subscription for \$12 saves you 50% — each issue costs only 50¢. (We must be nuts!)

Don't Read This Paragraph

A three year subscription takes us for a bundle. It's only 42¢ an issue — a savings of 68%. (We certainly won't make much money off you. Come to think of it, what kind of person are you, reading this paragraph and thinking of subscribing for three years?)

OUR RATES ARE REASONABLE

We have managed to hold our subscription rates at a reasonable level despite a host of rising costs: postage rates (our nemesis, due to go up again), staff salaries (itinerant apple pickers are making more every year and the chimpanzees are asking for more and more bananas), rising printing costs and increased costs in just about everything else.

WHAT WE GIVE YOU:

- More articles on every facet of amateur radio than any other publication.
- We're usually a couple of steps ahead of our competitors in publishing articles you want to read about.
- More ads than any other Ham magazine—that means you can keep up on what's new in your hobby.
- NEWS PAGES: Read about how hams are aiding people during times of crisis. Read our special interest columns which will keep you up on what's new in your facet of ham radio — contests — SSTV — 50 MHz — Solid State — and more, more, more!
- An open forum for you in our letters to the editor column. Here you can sound off on your likes and dislikes (about us or anyone else). We publish both sides.
- Wayne's Editorials — never boring, sometimes controversial. They're a great conversation starter at ham clubs and on the air.
- IRS Report: Does an average ham pay more in taxes than a multi-million dollar company? Find out how the IRS is out to screw you and what you can do about it.

MORE

FOR YOU!

NAME _____ CALL _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP _____
 Sign me up for a money-saving 1-year subscription for \$7.
 Here's my \$12 to rip you off for a 2-year subscription.
 YEAH! I'm mean enough to sign up for a 3-year subscription for \$15.
 BankAmericard MasterCharge Account No. _____ Expires _____
 Check enclosed
 Bill Me Signature _____

Schematic Of The Month

WILSON

2m FM Transceiver

The basic circuit of the Wilson transceiver has evolved from the Ken unit a year ago to the Henry Tempo FMH — and now it is the Wilson. But there are changes — substantial changes — and all for the better. The Ken was a lot of transceiver for its price, but some amateurs wanted a hotter receiver and wanted a little more poop in the output. The Wilson has a new front end and it is a hot one. It also has a better rear end for more poop on transmit.

There are some other benefits to this rig when compared with other HT's on the market — things like the netting capacitors on all of the crystals, both transmit and receive. This makes it a lot easier to get the unit right on channel. And all of the crystals are plugged in too, not just some. The earlier Ken units had two channels soldered in — which was not serious where you had a use for both 34/94 and 94/94 — but these days, with no 34/94 repeater in New York, Chicago, Washington, Boston, Los Angeles, etc., that turned out to be a rather serious wasted channel. And in the 34/94 areas, the 94/94 pair wasn't all that valuable. Better that all crystals can be plugged in as in the Wilson. The fact is that a five channel HT with two soldered in channels is a three channel radio.

The Wilson has six channels — and that is none too many in most areas. It is none too few either, for seldom are you in an area where you can reach more than six repeaters with an HT. Considering the size of the HT — and there is more than a little resistance to the larger HT's such as the Unimetrix — more than six channels would begin to crowd things inside so the unit would have to be bigger. You want a unit that is comfortable to hold in the hand — that will fit in the pocket — or on the belt.

Speaking of holding in the hand — one of the really annoying things about most HT's is that if you have any kind of noise level you have to

hold the speaker up to your ear and then quickly swing the HT down to speak in the loudspeaker when it is your time to transmit. This little maneuver usually takes longer than the time between transmissions on the repeater, so you are aced out. With some ops you have to be mighty fast of finger to break in and that part of a second it takes you to swing the HT from your ear to your mouth you'll lose out. The Wilson has thymike mounted toward the bottom of the unit, right where your mouth comes when you put the speaker to your ear.

The use of the separate mike (such as you'll find on the late Motorola HT's) results in considerably better audio. You'll find that reports are most gratifying on your audio.

Another big hassle with the Motorola units are those incredibly expensive nicad battery packs they use. The Wilson uses those low cost AA size nicads (you can put in regular AA flashlight batteries in an emergency) — these batteries sell at every Radio Shack or Lafayette store for peanuts — or you can even catch someone like Hal Babylon (advertised in 73) with surplus nicads for a fraction of the Radio Shack price!

When you use your HT on your belt — for instance at hamfests — you want a remot mike that plus into the unit. The Wilson has a plug for this — and it also feeds out the audio from the loudspeaker which you can hear from a small speaker which is mounted right in the mike case!

The S-meter is handy when you are in a weak signal area and want to peak up a repeater in order to be sure to get the best signal back into it. It doubles as a battery indicator so you won't run your nicads down too far and reverse them. Nicads don't like that.


The circuit board for the Wilson is the size of the case — and this means that everything is easy to get at for servicing. If you've ever tried to fix a Motorola HT-220 you will appreciate the room in the Wilson for work —


and the use of small, but not invisible parts.

One problem with the earlier Ken units was a weakness of the internal molded track for the battery pack — it often broke when the HT was dropped — and who doesn't drop one now and then? The Wilson may break if you try hard enough, but it will take an incredible beating before giving up.

Obviously the Wilson is quite a rig — and one would expect it to come through at around \$280 or so. Wilson is selling them for only \$199 for reasons best known to themselves. It would seem prudent to get one of these radios before the folks at Wilson wise up.

...STAFF

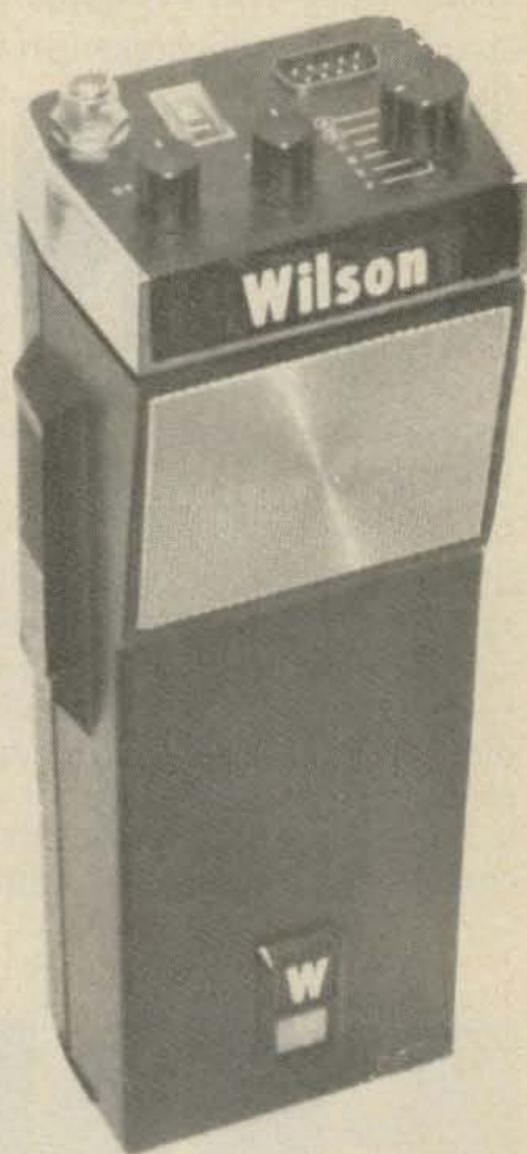

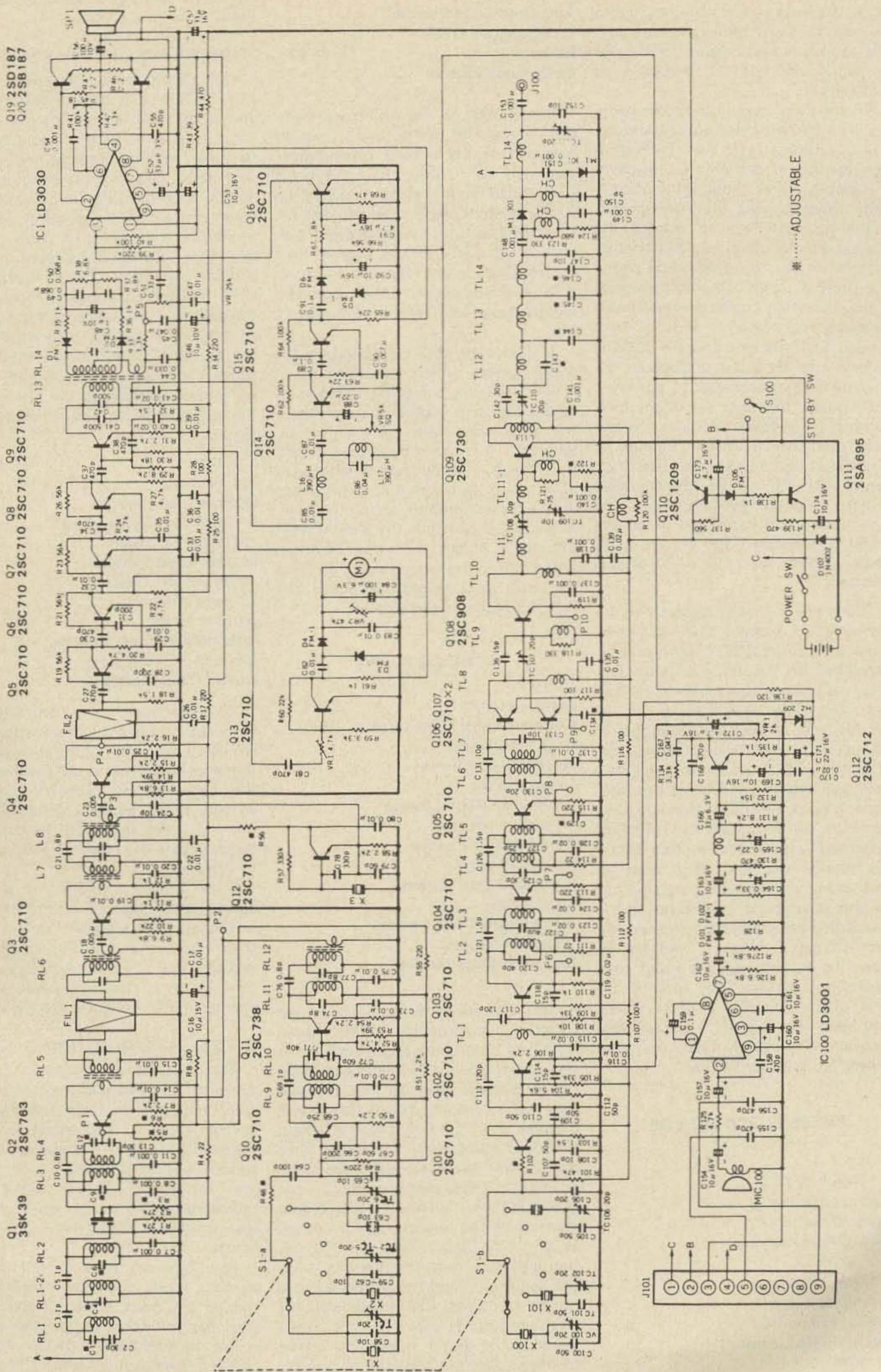

*.....ADJUSTABLE

Form 1 would require the applicant to write out his name and address. Form 2 would require him to sign a promise to learn the code someday. The license would permit him to use all ham bands with all modes — no subbands.

This system would have some benefits. The current trend toward extinction of amateur radio via a 3-1/2% drop per year would certainly be reversed. It is possible that it might be substantially reversed and that the growth might be sufficient to attract the interest of manufacturers big enough to help us get more bands and widen our present bands. One million amateurs pressuring congress could work wonders, particularly with a well funded EIA amateur division pouring money into the right pockets in the appropriate government agencies. With power like that we might look forward to grabbing off some of the lesser used UHF television channels. It is difficult not to see what has happened with CB, where totally illegal activity is enthusiastically supported by industry and permitted to go virtually unrestrained by the FCC, all because there are millions of dollars involved.

There are a few drawbacks to be considered. I suspect that we would see a lot of the W2OY syndrome — remember his calling CQ first class only, no lids, no space cadets, no ten meter ops? The CBers have an answer for this, too, as they have demonstrated recently when a woman complained to the FCC about CB interference. They got together and killed her dog, threw a brick through a window, and called her on the phone and threatened her with rape and mutilation. When this didn't stop her, they went to beating her up on a bus, stealing her car and smashing it, hitting her in the face with a brick when she opened the door to get a telegram, and ten or more obscene phone calls a day, plus threats on her life. They sent her all sorts of merchandise collect — sent plumbers, electricians, ambulances, taxis and fire trucks. There *are* ways to keep CB complaints down.

PRESENT STRUCTURE

Usual Entry
5 wpm code test
General/Tech exam
Tech Class License
or
Usual Entry
5 wpm code test
Novice exam
Novice Class License
13 wpm code test
General exam

General Class License
Advanced exam
Advanced Class License
20 wpm code test
Extra exam
Extra Class License

Since 95% of the amateurs never get to the end of the line, it would appear that the system leaves something to be desired. It is anyone's guess as to what the results would be if the system were changed. Predictions of the future have always been chancy at best, so we should take claims that certain changes in structure would be disastrous or would be greatly beneficial with a truckload of salt.

It does seem as if we should try for some system which would result in more amateurs achieving the top license. My own suggestions on this in the past have been almost totally ignored — I felt that incentives should be offered — while others, who were able to win out, felt that punishment was a better method of forcing compliance. The carrot or the stick choice. My ideas might not have worked either, of course, so perhaps I can't be as smug as I might be about the ARRL plan failing so totally.

THE CQ PLAN

Entry
Novice exam
Communicator Class License
5 wpm code test
Novice Class License
General exam
Technician Class License
13 wpm code test
General Class License
Advanced exam
Advanced Class License
Extra exam
Extra Phone Class License
20 wpm code test
Extra CW Class License

This has seven different classes of license, presumably with seven different sub band allocations. It is not clear why more Techs would go on to General than do now, so that may be misleading chartwise and in practice the Tech ticket would remain the dead end street it is today. This means that there are just two basic changes to the present structure — the communicator license — this would seem to be the same thing I proposed as a Hobby Class license for 220 use, though I have some reservations about the scheme — and the separate Extra Phone and Extra CW licenses which I also petitioned the FCC for some years ago. It didn't make sense to me to have a 20 wpm code test to operate phone — and there seems to be general

agreement about this. I do appreciate CQ adopting my petitions and pushing them as the new CQ plan.

THREE LEVEL LICENSE SYSTEM

One plan that is attractive to the FCC because it is simpler than the six and seven level license schemes is the three level idea which would have a beginner, an intermediate and an expert level. This is a bit closer to the system used back in the 30's and 40's where there was the Class A with all privileges, the Class B with fewer privileges, and the Bootlegger with no official privileges. The Bootlegger Class had the advantage of no exams, the call of your choice, and the use of all bands — obviously a forerunner of the current CB operating system. For those readers who have had their sense of humor amputated or atrophied, the preceding was not seriously presented.

Entry
Novice exam
Learner Class License
Endorsement by licensed amateur for code
Learner Class License with CW privileges
13 wpm code test
General exam
Intermediate Class License
Advanced/Extra exam
Expert Class License

This obviously isn't a lot different from our present system either. It would lump the Tech and Novice together and either the Advanced and the Extra or the General and Advanced. They might keep the Extra Class separate and let it die a natural death, rather than demote Extras back to Advanced.

Since I have a petition in already asking that Techs be granted Novice privileges, and another asking that there be an Extra Phone License without that 20 wpm test, this structure is very close to what would emerge if my petitions were granted.

OTHER RESTRUCTURING IDEAS

The FCC is up against a lot of decisions in restructuring — such as what emissions to allow each class of license — what frequencies — what transmitter power — eligibility for the various station licenses — station call sign format — call sign prefixes — honorariums for old timers — volunteer examiner eligibility — length of license terms — etc.

For instance, there is considerable thought being given to a substantial change in power limits. If the three level system were to be used and a power differentiation of six dB between powers, this might allow the Learner to use 125 watts, the Inter-

mediate 500 watts and the Expert 2000 watts output. Yep, that's output, not dc input or PEP input. Our 1 kW limit has been around for a long time and it may be time to take a closer look at it.

In my travels I have found that there are definite advantages to running high power, no matter how avid the QRPers may be. When you operate from YA, VU, 9N and other remote areas like that you hear the high power boys almost nightly — the medium power boys a few times a month — and the low power boys a few times a year. The lack of a substantial number of high power signals invites commercial invasion of our bands.

Time was when a kilowatt was so prohibitively expensive that only the most wealthy amateurs could afford to build one. Now you can tuck a kilowatt into a car — almost under the dash! It used to take racks (six feet each) of equipment for a rig like that, and now you can carry it around and set it on the table. CBers have shown us that 3000 watt transmitters are not all that expensive to buy or use. Shouldn't we be able to work out as well as CBers?

The FCC is about ready to throw out all previous restrictions on call signs and are thinking in terms of things like W1A for some club stations — which would be a 1x1 call. They would keep the present 1x2 (W1AW) and 1x3 (W2NSD). Add to that possible 2x1 such as WA1A and 2x2 like WA2AA, plus the current 2x3 calls. This would give some nice privileges for incentives. They are also thinking in terms of more prefixes, and the U.S. has many we haven't been using. They might open up the AA-AL, KA-KZ, NA-NZ and WA-WZ. What turns you on?

With such a wide selection of call signs available the FCC could set up their computer to give you the call of your choice. How about that?

There is much, much more to be said on restructuring, so let's think about it and we'll have more next month. In the meanwhile, if you come up with any ideas that seem inspired, why not send them in for exposure in 73?

FCC VS NETS

The complaints of some of the amateur nets — in particular the Wescars net — complete with pressures via Congress — about interference from jammers has the FCC seriously concerned. Wescars and the jammers have their own version of the mideast conflict.

There is no question that some of our nets do serve very valuable purposes, at least some of the time. They

do tend to give us better use of our frequencies since they keep large numbers of stations all on one single channel instead of spread out all up and down the band. Other nets are for fun.

While there are undoubtedly amateurs with severe psychological problems who are just looking for people having fun that they can spoil and who delight in clobbering a net, many of the problems encountered by nets have more to do with the way the net gets started on a channel. Few amateurs take well to the flat demand that they get off a frequency because it is the net's and the net is going to start in a few minutes. I will never forget the day I was operating from PJ3CC, happily working fellows around the states, when a woman came on channel and told me to get off the channel — that I had no right to be there — this was the YL International SSB Net frequency and the net was about to start and I certainly was a trouble maker for even daring to use the channel. Wow!

Amateurs who feel that the interference to a net is serious enough to warrant a complaint to the FCC should keep in mind that there is a petition on file now by K6BX to officially license and regulate all nets.

Every complainer should be sentenced to read this petition — he would never complain again.

The FCC position is that first of all the regulations prohibit deliberate interference. This is probably one of the least heeded rules on the books — every DX pileup is testimony that dozens to hundreds of amateurs are intentionally interfering with each other — but maybe pileups don't count? Frequencies are supposed to be available on a first-come first-served basis — and this is supposed to include nets, even if they are registered with the ARRL and are thus "official" nets, whatever that means. The FCC feels that it is up to amateurs to work out a solution to the net problem — or else they will do it. And all we have to do is remember the recent "solution" to the repeater problem to know that the chances are good that the very worst solution to the problem is FCC action.

If the FCC continues to get complaints about or from nets, it is quite possible that some system of net licensing, with one to two year delays, license fees, and allocated channels and times, with the usual delays in changes in times or channels, might be established. This prospect — and again I suggest you get a copy of the K6BX petition and read the complete thing (I think copies of it can be had for \$20 each or perhaps a bit less). This

prospect should help nets do some self-examing to see if there isn't some way to solve their problems with public relations — better techniques of getting the net started, etc.

There is a lot to be said for leaving the FCC alone. Remember, when you feel that there is something you want to do that is not specifically permitted that the FCC works on the other side of the coin — if it is not prohibited, then it obviously is permitted. The basic rule when dealing with the FCC — and all government — is, when in question, don't ask.

NEW FCC EXAMS COMING

The Commission has been working on an update of all of the amateur radio exams and it is being helped in this by some amateurs who are expert in the fields to be covered by the exams.

The material to be covered in the exams has been broken down to the following categories:

1. Rules and regulations
2. Radio phenomena
3. Operating procedures
4. Emission characteristics
5. Electrical principles
6. Practical circuits
7. Circuit components
8. Antennas and transmission lines
9. Radio & communication practices

It will be a while before the new exams are ready for use. The study material will not be substantially different from that which appears in the 73 license study series. The main changes that the new exams and study material will bring about will be a complete revising of the ARRL license study manual, which will be made obsolete. Some feel that it is just about irrelevant right now, but it does sell well and is responsible for helping thousands of prospective amateurs to pass the present license exams — and helping thousands of others to fail.

The 73 Magazine license study guides have been broken down pretty much as the FCC has done it, with each chapter covering a technical aspect of radio in depth and not, as the ARRL manual does, just giving questions and answers. The benefit of this in depth study system has been proven lately by the high percentage of successes of amateurs using the 73 system on the Conditional exam, which is a lot tougher than the FCC administered General exam now.

The recent FCC figures show that about 50% of those taking the Conditional exam are passing it as compared to 75% passing the General exam! What is the difference between them? Well, they cover about the same

material, but the General exam is the usual multiple choice exam with five statements, four of them wrong, and you have to pick out the correct answer. On the Conditional there are four right answers and one wrong — you pick out the wrong. It's a lot harder.

STRIKE

A strike of most of the unions at the printers of 73 Magazine delayed the mailing of the June issue by about ten days. This issue (July) might possibly have been delayed too. If so, then we apologize for a situation beyond our control.

WOODEN CIRCUIT BOARDS

A recent phone call from K3CMZ, who builds a lot of stuff but doesn't write much, explained some short cuts he has developed which may be of interest. For instance, he uses some of that thin balsawood for mounting ICs — you carefully shove the IC pins through the wood and you're in business. The balsawood makes a light servicable chassis. He makes little boxes for gadgets out of those brass strips they sell in hobby shops (where he went for the balsawood). The strips come to an inch wide and are 12" long, cost 25¢. He cuts these up and solders them to make small brass boxes. A small strip of hard wood along each side of a box, routed out to slide the balsawood chassis in, and you can stack up a number of the little chassis in one box.

VISITING BOSTON?

FM'ers visiting Boston may wonder which are the best repeaters to be ready to use. There are a couple of dozen repeaters in and around the Boston vicinity, but not all of them are close enough for low powered rigs, and a few are not friendly to visitors sad to say.

For starters you should be ready for 146.04-64, the Waltham group. This is the busiest repeater in greater Boston, and one of the most friendly (when you can get through to it). If you're toward the north end of town, from Route 128 on out, you'll do well to be set for 146.25-85, the Derry New Hampshire club. You won't find a more friendly group anywhere in the country. If you prefer a more businesslike and get off the pot machine, one which handles a lot of patches, you'll want 146.22-82 in Weston, one of the vast complex of MMRA repeaters.

If you have the weird crystals or a Clegg 27B, you'll be able to say hello on one of the most sophisticated repeaters in the area on 146.39-99. This is W1UQ, a closed repeater, but peopled by friendly and interesting ops.

A new repeater in Malden is on 146.19-79. You may get in a contact or two on it if you can get K1VTE to stop playing with his autopatch. In the same town you can also use WR1AAA 146.31-91. This is a strictly local repeater and will take you from downtown Boston out to about Route 128 (the highway which circles Boston. Say hello to Mel W1BHD.

Up on the north shore is WR1AAC on 146.28-88. It is also a local repeater and not too strong even in Boston. Out in Billerica at the Honeywell plant is WR1ABP on 147.72-12. It isn't as active as a lot of the others, and watch out for a zing from Lew, but there are a lot of first rate fellows that do hang out there. The 147.84-24 repeater covers that northern area pretty well too, but they generally don't seem to like visitors and have been known to turn off the repeater if you try to call in.

Off to the west of town you'll run into a repeater on 146.01-61 — not too active, but a nice group. There is also one on the ridiculous pair of 147.87-03, but it is kind of closed, and very inactive. If you can get them to talk with you, the fellows are fun to meet. Ask them about W1PRI and then stand back for the blast! It's almost worth the trouble of waking them up. If you have crystals for 146.07-67 you can exercise them out that way too. Out Worcester way you can call in on 146.37-97 and say hello to Charlie. Same pair works north out of Salem (NH), but not used a lot. Very nice guys when they are available. Also to the west is DL2AA/WR1, the only reciprocal licensed repeater.

That should hold you in and around Boston.

REPEATER WARS

The FCC has been quite outspoken on one point: if we cannot solve our own problems they will try to solve them for us. I think we have all had far more than we need of FCC solutions to ham problems and from the exciting experiences we have had we should learn that it is time to stop turning to the Great White Father for help whenever we get into trouble — and realize that we must work out our own problems.

Repeater wars are problems and they need solutions — better solutions than higher and higher power — deliberate interference — kerchunking — and the usual silliness. I remember the reaction of a repeater owner in Holyoke MA, when Ken Sessions first put a repeater on 34/94 up here in New Hampshire — RTTY on the input by the hour. War. Not a visit to see what could be done to solve the problem.

With difficulty I will restrain myself from giving specifics, using a certain cretin in Connecticut as a horrible example of the war-prone repeater op.

In most areas we have an excellent start toward peace with the organization of repeater councils and frequency coordinating groups. But that is just the first step. One thing that became very clear during the FM forum at Dayton was that there is a serious need for some way to get repeater councils together to solve intermural problems. Whether this will turn out to be a national council meeting or a council newsletter remains to be seen. Communications is badly needed at this level.

W2NSD



The Hamburglar STRIKES AGAIN!

List from Past Issues: Mfr., Model, Ser. No.	Owner	Issue
AF68 No. 10888	K5LKL	1/73
PMR8 No. 10918		
M1070 pwr supply		
Trio TR2200 No. 241969	WA2ZBV	1/73
Clegg 22er No. 1900-578	W1DHP	2/73
Standard 826M, No. 112007	WA8PCG	3/73
FM27B No. 27013-1141	W2LNI	4/73
FM-144-10L No. F459	WA6WOA	4/73
NPC 107m pwr supply		
2, 5AJ-IPL Onan Gen., No. 327885		
HR-2 No. 04-C2879	W6GSR	6/73
SB-34 No. 21 1828		
STD 826 No. 011268	WA2FSD	6/73
HT220 No. GJ7327	State Univ. of NY (Albany)	6/73
	W4GF	7/73
Yaesu FT-101		
No. 82G 12279/CW		
HR-2 No. 0302030		
Clegg 27B No. 72013-1068	W3BXL	7/73
STD. 826 MA No. 208078	WB2DEW	7/73
Drake ML-2 No. 10582	W3MSN	8/73
Sonar FR-2528 No. 21-4250	Doherty	12/73
STD SRC-851-SH No. 9725		
STD SRC-707C No. 2833		
TPL PA-6-IDE No. 1092		
RP MEA-22 No. 212		
Two Larsen antennas		
Swan 270 No. M-252616	W4NTB	12/73
STD SRC-146A No. 208070	W7DKB	12/73
Marker Luxury No. 2296	W7BVP/6	2/74
Regency HR-2A 2m FM No. 04-05632	W88NSU	3/74
Collins Model KWM-2 No. 13551	W9JS	3/74
Regency HR-2A No. 04-0787	WA3TVI	4/74
Kenwood TS-520 No. 840092	W7JFR	5/74
CW-520/511S filter		
Inoue EC-20 No. 1161	W1PVF	7/74
1-RF Communications RF-403-2 VHF-FM XCUR No. 1277	K3YHR	7/74
Sonar 3601 No. 1416	K1UXD	7/74
SBE Model SB-144 No. 46316 \$25 reward \$25 for information for arrest and conviction of thief	K4KVF/5	7/74
Clegg 27B No. 27103-2891	WA1ECF	7/74

Caveat Emptor?

Price - \$2 per 25 words for non-commercial ads; \$10 per 25 words for business ventures. No display ads or agency discount. Include your check with order.

Deadline for ads is the 1st of the month two months prior to publication. For example: January 1st is the deadline for the March issue which will be mailed on the 10th of February.

Type copy. Phrase and punctuate exactly as you wish it to appear. No all-capital ads.

We will be the judge of suitability of ads. Our responsibility for errors extends only to printing a correct ad in a later issue.

For \$1 extra we can maintain a reply box for you.

We cannot check into each advertiser, so Caveat Emptor.

GREATEST of them all! That's the ARRL 1974 National Convention, sponsored by Hudson Amateur Radio Council. Remember the dates - July 19, 20, 21 at the Waldorf-Astoria, New York City. Three days of exciting events! Wide array of demonstrations, exhibits and forums featuring latest in FM, SSTV, ATV, RTTY, FAX, Satellites, Antenna design, Transistors, Integrated Circuits, DX, MARS, ARPSC and much more. Something to do every exciting minute for YLs & XYLs - Tours, New York sightseeing, visits to popular TV shows, Parties, Fashion Shows. Meet the ARRL President, Vice-presidents, and all 16 Directors! Famous-name Speakers at Saturday Night Banquet! Everything for the Non-Ham, New Ham and Old Timer. For info, Contact: ARRL Convention, 303 Tenafly Road, Englewood NJ 07631.

DANVILLE HAMFEST at Douglas Park in Danville IL on September 1, 1974. Take Bowman Avenue Exit off I-74 and follow the signs. Prizes will include a low-band rig and VHF gear, antennas, electronic keyer, wattmeters, SWR bridges, and many others. Camping and motel accommodations nearby. Food and plenty of parking available. Huge flea market and commercial displays. Tickets are \$2 or three for \$5. Advance tickets available from Dave WA9PDS, Dolan Rd., Catlin IL 61817. Send check or M.O. and SASE. Talk-in on 22/82 and 94 simplex.

BUY-SELL-TRADE write for monthly mailer, give name, address, call letters. Complete stock of major brands new and reconditioned equipment. Call us for best deals. We buy Collins, Drake, Swan, etc. SSB & FM. Associated Radio, 8012 Conser, Overland Park KS 66204. 913-381-5901.

EQUIPMENT FROM 73

The following list of gear, unless otherwise noted, consists of brand new equipment purchased for testing purposes only. Some have been tested, some remain unopened in original cartons. We are offering this gear at a considerable discount on a first-come-first-served basis. Please send Money Orders or Certified Checks only to 73 Magazine, Peterborough NH 03458.

MITS 908M Calculator w/p.s./case (\$143) new	\$ 90
Heath IB-101 counter (\$170) - 5 figs	\$ 140
Vanguard Scaler - by 10 - to 200 MHz (\$120)	\$ 75
Regency 16ch scanner TME-H-LMU (\$300) - new	\$ 245
SBE Scanvision, complete, like new (\$900)	\$ 500
Pickering CW keyboard KB-1 (\$265) - tested	\$ 175
Gladding Hi-Scan - 8ch scanner - tested (\$180)	\$ 99
Motorola KW 2m amplifier - used	\$ 350
Heath IC-2009 calculator - brand new (\$92)	\$ 88
Standard 1400 2m 22ch xcvr 10w (\$550) - used	\$ 250
Signal One CX7-A - tested - perfect - like new - fantastic	\$1990
Kenwood Twins - Tested - like new (\$900)	\$ 750
Standard 146 2m HT - used (\$289)	\$ 190
Fannon intercom - exec - 6 ch master - (\$60) tested	\$ 35
Concord video monitor VM-12 - tested (\$400)	\$ 250
Concord all channel TV tuner Dem-911 (\$600)	\$ 250
Bell & Howell 2965 portable VTR - new (\$1595)	\$ 475
Batteries for B&H 2965 - like new (\$36)	\$ 25
Regency 450 MHz scanner - (\$200) - like new	\$ 140
Varitronics PA-50 2m amp (\$110) - brand new - 10w in 50 vout	\$ 75
RP tone burst gen - 5 freq - TB-5 - exc (\$37.50)	\$ 25
Hitachi stereo cassette recorder - exc - (\$120)	\$ 75
Hitachi AM-FM cassette recorder - exc - (\$90)	\$ 50
Antenna Spec rubber ducky antennas HM-4 2m	\$ 4
SWR meter - exc (\$25) KW	\$ 12
Test Labs - 10 in 1 - SE-400 (\$25) as is	\$ 10
Radio Shack Code cassette - new (\$6)	\$ 4
Regency HR-6 (\$240) six meter 10w xcvr 12ch	\$ 199
Standard SR-C826M (\$360) 2m 10w xcvr 12 ch	\$ 299
Regency ACT-R8H/L Scr (\$160) VHF/UHF 8ch scr receiver	\$ 136
Standard SR-C826MA (\$398) Latest model 10w 12ch 2m xcvr	\$ 339
Regency HR-2MS (\$319) 2m 15w xcvr with 8ch scanner	\$ 269
SBE SB-450TRC (\$180) 450 MHz transverter	\$ 149
SBE SB-1PA (\$190) 10w in 40w out power amplifier 2m	\$ 159
Regency Pocket scanner 4 channel ACT-P4H (\$120)	\$ 99
Cobra 220 MHz Transceiver 10w 12ch (\$300)	\$ 255
Amphenol RG-8/U Polyfoam 100' w/PL-259 connectors (\$24)	\$ 19
Standard 14U 2m 22ch superfantastic rig, VOX (\$510) demo	\$ 439
Pacificom 2m HT - brand new - (\$250)	\$ 199

All Prices fob: UPS collect.

73 Magazine - Peterborough NH 03458

462.60MHz FM 6/12V mobile tube transceivers; 15 complete GE 4ES14A1 450-470MHz 20 watt units for sale, \$50 each. Additional specs upon request. Tony Hogg, WHLM Radio, Bloomsburg PA 17815.

FREE BARGAIN CATALOG. Transistors, Relays, ICs, Puts, Leds, Readouts, Resistors, Capacitors, Thermocouples, Transducers, Circuit Boards, Unique Components. Chaney's Dept. A, Box 15431, Lakewood CO 80215.

THE 27th ANNUAL Turkey Run Hamfest and VHF Picnic, sponsored by the Wabash Valley ARA, Inc., will be held Sunday, July 28, at Turkey Run State Park near Rockville, Indiana. Don't miss the Midwest's finest fleamarket. Fun for the whole family: XYL Bingo and fleamarket; food and refreshments, camping facilities, and park recreation for the kids. First Prize: Genave GTX-10, Second Prize: Regency HRT-2, Third Prize: Drake WV-4 VHF Wattmeter; plus many more. Activities begin at 9:00 AM with free coffee and doughnuts. Talk-in 146.94 by W9UUU/9. For details, send SASE to WVARA Hamfest, Box 81, Terre Haute IN 47808.

GREATER Indianapolis Hamfest, Sunday, July 14, 1974, rain or shine, Marion County Fair Grounds, all activities under roof. \$2.00 covers gate fee and prize drawing. For information write: Wm. J. Evans, 8104 Crest Hill Dr., Indianapolis IN 46256.

FREE Crystals with the purchase of any 2m FM radio. Write for our deal on the rig of your choice. Factory-authorized dealers for Regency, Drake, ICOM, Alpha, Tempo, Kenwood, Genave, Swan, Clegg, Ten-Tec, Standard, Midland, Telex, Halli-crafters, Venus, Hy-Gain, Galaxy, CushCraft, Mosley and Hustler. For the best deal around on VHF or HF gear, see us first or see us last, but see us before you buy. Write or call us today for our low quote and become one of the many happy and satisfied customers of Hoosier Electronics, R.R. 25, Box 403, Terre Haute IN 47802. 812-894-2397.

HAMFESTERS 40th Annual Hamfest and picnic, Sunday August 11, 1974, at Santa Fe Park, 91st and Wolf Road, Willow Springs IL (southwest of Chicago). Exhibits for OM's, XYL's. Famous Swappers Row. Information - contact, Vince Pronites WA9EOM, 7206 So. Damen Avenue, Chicago IL 60636. Tickets write - Jos. Paradyla WA9IWU, 5701 So. California Avenue, Chicago IL 60629.

THE ORIGINAL FM Hamfest Sunday August 4, 1974, near Angola IN. Free flea market, entertainment for ladies and kids. Picnic grounds, campsites, boating, food, soft drinks, available rain or shine. For information contact: Fort Wayne Repeater Assoc. Box 6022, Fort Wayne IN 46806.

ANTIQUÉ RADIO BUFFS. Do you need a schematic for your radio? For information send SASE showing make and model number. Joseph C. Crockett K3KUL, 762 S. Gulph Road, King of Prussia PA 19406.

TELETYPE EQUIPMENT For Sale: Models 14, 15, 19, 28, 32, 33. TD's, Reperfs, KSR's, ASR's. Parts or complete machines. Write needs and send SASE for complete listing and prices. Larry Pflieger, 10615 W. Ridge Rd., Apt. 54, Hales Corners WI 53130.

"73 MAGAZINES" in binders. First thru latest, make offer on complete set only. Wm. Coldewey Jr. WA8DJS, 5733 Linden Drive, Milford OH 45150.

UPPER PENINSULA Ham fest, August 3 & 4, 1974, Negaunee Township Hall, Negaunee MI. Hiawatha Amateur Radio Association host. Registration \$2. Swap n' Shop, Program for XYL's, Door Prizes. Mobiles talk in on 3.920 and 146.94. Reservations & info: Frank K4CGQ/8, 322 Fortress, Sawyer AFB MI 49843. 906-346-5501.

FOR SALE 2 each EIMAC 4CX1000A with sockets and filament transformers, \$200. Also RCA 7094 with sockets, \$18 each. Write: Dave Kiech, 3615 Harrison St., Riverside CA 92504.

WARREN HAMFEST, largest family style hamfest in the East. Sunday, August 18th, at Famous Yankee Lake Park. Giant Fleamarket, Swimming, Picnicing: All free. Details, QSL W8VTD.

KIRLIAN photography kit: Complete, with instructions, \$19.95 + \$1.50 postage. BOOK: "The Kirlian Aura," \$3.95 + \$.75 postage. Systecon, Department 21, Box 417, West Hyattsville MD 20782.

WANTED TO BUY Scott Philharmonic XXX or McCurdo Silver Masterpiece VI. David Singer, 10301 Alpine Drive, Cupertino CA 95014.

BCD Adder-Subtractor Experiment. Complete instructions tell how to build, add, subtract, multiply and divide for \$2.00. Sollee Enterprises-T, Box 41283, Los Angeles CA 90041.

FOUNDATION for Amateur Radio Annual Hamfest Sunday, October 20, 1974 at Gaithersburg Maryland Fairgrounds.

MIX PLEASURE with pleasure at the Hamburg International Hamfest on September 21. For information contact Lin Brownell WB2HCL, 210 Buffalo, Hamburg NY 14075.

TECH MANUALS for Government surplus gear — \$6.50 each: R-390/URR, R-220/URR, URM-25D, CV-591A/URR, CV-278/GR, TRM-1, TS-382D/U, TS-497B/URR, TT-63A/FGC, URM-32, W3IHD, 7218 Roanne Drive, Washington DC 20021.

MOBILE IGNITION shielding gives more range, no noise. Everything from economical suppression kits to custom shielding. Literature estes engineering, 543-A West 184 Street, Gardena CA 90248.

SELL Drake 2C Receiver with matching noise blanker crystal calibrator speaker \$150 postpaid, George Konnick, Apt. P2, 1750 West Main Street, Riverhead NY 11901.

VIDIO RECORDER Ampex VR6500 like new with vidio monitor and cables \$475. Sam Wood 12648 La cresta Ct, Los Altos Hills CA 94022. Telephone 415-941-8000.

MOTOROLA PORTABLES — Expert repairs, reasonable prices, fast turn-around time. More details and flat rate catalog FREE. Ideal Services, 6663 Industrial Loop, Greendale WI 53129.

FOR SALE: — TV7B Tube Testers. Some need repairs. \$16.95 shipped UPS collect. NJ residents include 5% sales tax. Capacitor materials Inc., P.O. Box 413, West Long Branch NJ 07764.

WANTED: HT200 2 meters, any condition. State price and condition. Ron Dierkens WA6QVE, 3367 Ellington Dr., Altadena CA 91001.

FOR SALE: All issues of 73 Magazine. All reasonable offers considered. Prefer local buyer. D.S. De Armond W6MSD, 100 Glen Eyrie #2, San Jose CA 95125.

SELL: Drake TR4, AC4, MS4 Speaker, Heath HD-10 Keyer, HM-102 Wattmeter, HD-15 Phone Patch, Eico Model 460 DC Wide Band Oscilloscope 2KW Linear Homebrew. All Mint, Best Offer. Knud E. M. Keller c/o 73 Magazine, Peterborough NH 03458.

VERY INTERESTING! Next 5 issues \$1. "The Ham Trader," Sycamore IL 60178. (Ask about our "HAM EQUIPMENT BUYERS GUIDE" covering Receivers, transmitters, transceivers, amplifiers 1945-74. Indispensable!)

CRAMPED for antenna space? Slinky Dipole for 80/75, 40 & 20m operates efficiently at 24 feet long on 80m. Money-back guarantee. Complete kit \$30.95 ppd., COD \$1 extra. Teletron Corp., Box 84-S, Kings Park NY 11754.

MONTREAL HAMFEST 74, August 4, MacDonald College Farm, Ste Anne de Bellevue. Prizes, Giant fleamarket, technical sessions, family fun, \$2.50/adult. Info contact: VE2RM, Box 201, Pointe Claire-Dorval, Quebec H9R 4N9.


AUTOMATIC TELEPHONE Answering Computer. The best available. List \$239.95. I have two new and still in boxes for \$150.00 each. Warranty is still good. First check takes one or both. WB8CTA, 1000 Moore Road, Conway MI 49722.

NOW PAYING \$1750.00 and up for 618T/ARC-102 — \$1200.00 and up for ARC-51 — \$1500.00 and up for GRC-106, also parts for these sets. D & R Electronics, R.D.#1, Box 56, Milton PA 17847 after 6:00 1-717-742-4604.

WYOMING RANCH LAND. No QRM-QRN. Wild horses, antelope, deer. 10 acres — \$25 down, \$25 month. Owner — Michael Gauthier K6ICS, 9418 Florence, Downey CA 90240.

HERE IT IS — Heathkit 10-105 — still in the box unassembled. List \$400 — our sensational price \$379.00. 73 Magazine, Peterborough NH 03458.

QSL CONTEST

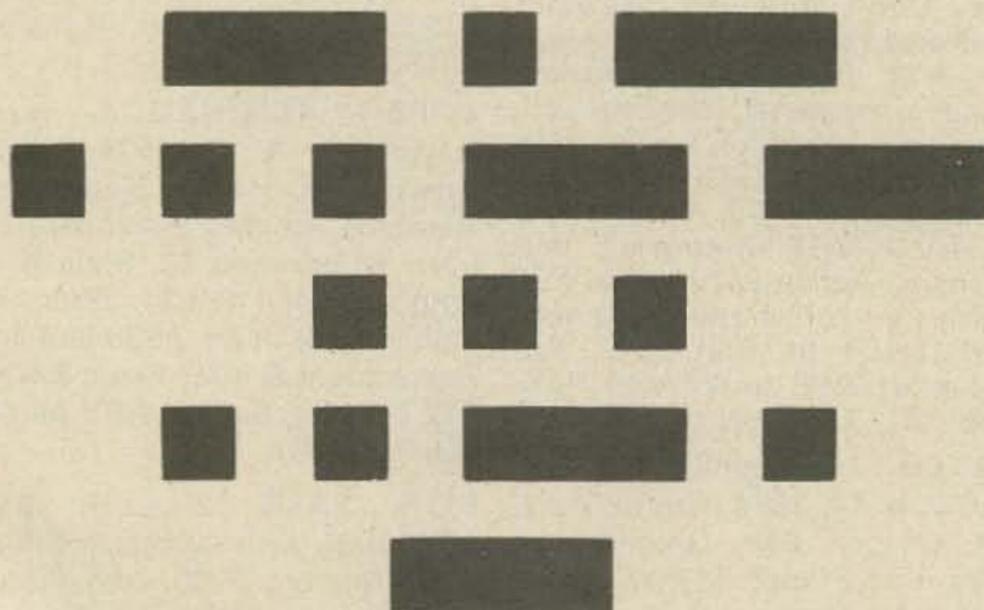

"A stark representation and realization of the universal unimportance of everything. A deeper understanding of the unrealized self revealing all of the traumas and hidden meanings of the inner self." Those were just a few of the comments we received from a well known art critic when he was shown this card. When we told him that it was an amateur radio QSL card and not a work by one of the newer artists around he went away muttering to himself.

However, putting all of the above aside, we proudly announce this month's winner, William W. Ehlers K3SFT, of Sykesville MD. Congratulations.

Even if your card doesn't reveal a message of cosmic importance you have a chance to win a one year subscription to 73. Enter your card today. Send it to 73 Magazine, Peterborough NH 03458.

NEW

30 WATTS OUTPUT




2-meter FM amateur band mobile transceiver
- 30 watts, 12 channels **MODEL 13-505**

(1) Midland 13-505 (built-in DC PS) . . \$299.95
(2) DELUXE REGULATED 12 AMP AC SUPPLY
69.95

(3) 5 crystals: Tx 34, 16, 94; Rx 94,76 . . . N/C
REGULAR . . . \$369.90

OUR SPECIAL PACKAGE PRICE . . . \$299.00

- 30 WATTS OUTPUT, ALL SOLID STATE (NO TUBES)
- MOTOROLA FINAL TRANSISTORS • SUPERB PROFESSIONAL LEVEL QUALITY AND CONSTRUCTION • TRIMMER CAPACITORS XMIT AND RCV XTALS • SEPARATE CHANNEL SELECTORS GIVE SIMULTANEOUS OR SELECTIVE CONTROL OF TRANSMIT AND RECEIVE FREQUENCIES-144 CHANNEL COMBINATIONS • DISCRIMETER SHOWS FREQUENCY SHIFT OF RECEIVED SIGNALS, ACTS AS CALIBRATION METER FOR RECEIVER AND TRANSMITTER • S/R/F/SWR METER SHOWS RECEIVED SIGNAL STRENGTH, RF POWER OUTPUT, SWITCHES TO SHOW ANTENNA SWR-D'ARSONVAL METERS • HI/LO TRANSMITTER POWER: 5 WATTS OR 30 WATTS • FULL SHORT OR OPEN SWR PROTECTION • PRIORITY CHANNEL • DYNAMIC MICROPHONE • SUPERB UNEQUALED EMPHASIZED EFFECTIVE HI-FI AUDIO QUALITY • MOBILE MOUNT • ACCESSORY JACK FOR TONE PAD, ETC. • EXTERNAL SPEAKER JACK • TEST POSITION TO MONITOR OWN SIGNAL • AND MUCH, MUCH, MORE. SIZE: 9 1/2 X 8 1/2 X 3. ALL CORDS, PLUGS, MOBILE BRACKET, MICROPHONE HANGER, ETC., INCLUDED.

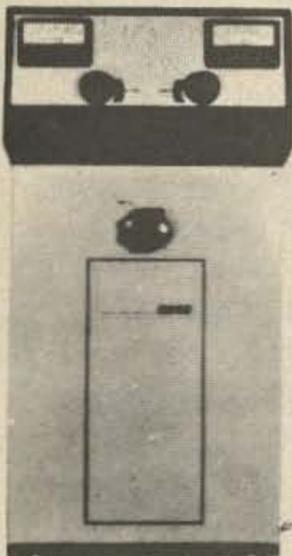


HENRY 3K-A

Cool and Easy Max. Legal Power • SSB, CW, RTTY or SSTV ratings • 3.5 to 30 MHz • Continuous duty • Silver plated PI-L plate tank • DC relays • ALC • built in SWR bridge • Output power 2 KW min, in commercial service.

The Finest Commercial Grade Amateur Linear Amplifier Available Anywhere in the World at ANY Price for ONLY \$1150 - The HENRY 3k-A.

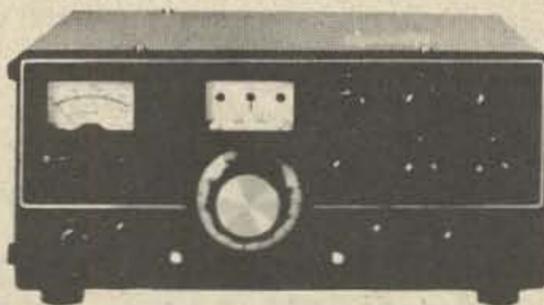
You will never know how little it costs to own THE incomparable HENRY 3K-A until YOU write or phone us and let us know the trade in deal YOU WANT. We usually say yes! NO ONE ANYWHERE BEATS OUR DEAL.



KENWOOD TS-520

The new TS-520 is the transceiver you have wanted, but could not buy until now. It is a no-compromise, do everything, go everywhere 5 band transceiver for SSB or CW that performs equally well at home, in an automobile, airplane, boat or trailer. The TS-520 features built-in AC power supply, built-in 12 volt DC power supply, built-in VOX with adjustable gain delay and anti-VOX . .

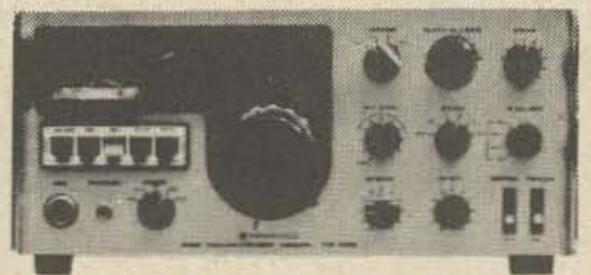
PLUS A HOST OF OTHER IMPORTANT FEATURES AND PROVEN Kenwood reliability. All at a price most amateurs can afford. The price . . . \$629.00



KENWOOD TS-900

. . . the ultimate transceiver. The promise of the transistor has been fulfilled. Here is the transceiver you will want to own . . . whatever you have now, get ready to trade up. Its important features are far too numerous to list. Its specifications are superb. The TS-900 is unquestionably the best transceiver of its kind ever offered. The price . . . \$795.00

PLEASE WRITE FOR COMPLETE INFORMATION

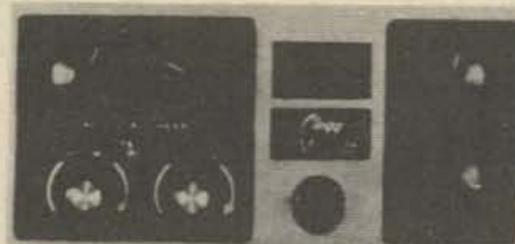

MIDLAND 13-520


NEW!! 4 way switch -
Provides 146T&R, 146
T-147R, 147T-146R

- SUPERB QUALITY
- 2 watts, 6 channels with carrying case and 16/76, 34/94 & 94/94.
- Please write for special packages with NI-CAD pack, charger, etc.

Reg. **\$229.95**
WRITE FOR SPECIAL DEAL!



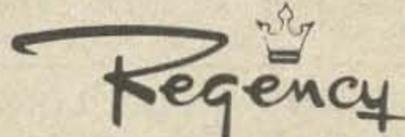REGENCY, CLEGG, SBE, INOUE, CUSHCRAFT, DATA ENG., BIRD, OLIVER SWAN (KLM), HY-GAIN, B&K, KENWOOD, TEMPO, TEN TEC, DX ENG., MINI PRODUCTS, SWAN, MIDLAND, ETC., IN STOCK - PLEASE WRITE FOR QUOTE.



WRITE FOR SPECIAL DEAL



HR-2MS

8 Channel Transcan
2 Meter FM Transceiver



HR-212

12 Channel-20 Watt
2 Meter FM Transceiver



HR-2B

UNEQUALED AT ANY PRICE

NO ONE ANYWHERE BEATS OUR DEAL!


AMATEUR-WHOLESALE ELECTRONICS

8817 S. W. 129 Terrace - Miami, FL 33156

Telephone - days (305) 233-3631 - night and weekends - (305) 666-1347

Kentucky Branch Store
Ashland, Kentucky
Telephone: (606) 325-0005

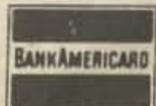We carefully and professionally service everything we sell. An employee always answers our night and weekend phone - not an answering service.



\$1.00 Telescoping Antennas \$1.00

25¢ 50¢ \$1.00 SALE

Part #	Sections	sections		dia.	Swivel	Hinge
		open	closed			
A	11	56-1/2	6	7/16		
B	8*	32-1/8	6	5/16	X	X
C	10	47	6-1/2	11/32	X	X
D	11	26-3/8	3-3/4	3/8		
E	8*	26-3/4	5-1/4	5/16	X	X
F	7	29-3/4	5-1/2	9/32		
G	6	19	5	1/4		X
H	8	30-3/4	6	5/16		
I	*9*	26	5	11/32	X	X
J	8	32-5/8	5-1/8	5/16		
K	8	32-1/2	6-7/8	9/16	X	X
L	8*	32-1/2	6-1/4	5/16	X	X
M	6	19	4-1/2	1/4		
N	7	24-1/4	4-1/2	1/4		
O	6	27-1/2	6	7/32		
P	Assortment 3/\$2.00 No Choice					

*Bottom section used inside case for mount

*Brass base and top hat

SPEAKERS

8Ω 80mW 2" Round
11Ω 200mW 2 1/4" Round

50¢ each

8Ω 3W 5x7 Oval
8Ω 3W 4x6 Oval
8Ω 2W 4x4 Square
8Ω 2W 2 1/2x7 Oval
8Ω 800mW 3 1/2 Round

\$1.00 each

Standard Size 15/16" body 5/16" thread 1/4" shaft 20K, 100K 25¢. 10K, 500K, 1meg—w/sw 50¢. 5K/10K concentric w/sw 75¢. Miniature size 3/4" body 1/4" thread 1/4" shaft 50K 25¢. 5K s/sw 50¢. Miniature size 5/8" body 7/32" thread 3/16" shaft 2.5K 25¢. 5K, 10K w/sw 50¢. Ultra Miniature Transistor Radio Volume Controls s/switch 2K, 2.5K, 5K, 7.5K, 15K. Your choice 25¢ ea. — 5/\$1.00.

ANOTHER TON OF GOODIES
Over 50 types of audio driver & output transformers for transistor circuits. Micros, minis, "CB" radio size, etc. \$.25 each, 5/\$1.00

PLASTIC BATTERY HOLDERS
Your choice 4'C' or 4'AA' or 4'A' w/leads. \$.25 each, 5/\$1.00

WE GOT A TON OF 'EM Transistor radio tuning caps for AM, AM-FM. Micros, minis, sealed, open. Over 40 types. \$.25 each, 5/\$1.00

TRANSISTOR RADIO EAR-PHONES — your choice mini or micro plug, long cord — \$.25 each, 5/\$1.00.

4 PDT RELAY Miniature pcb enclosed in clear plastic. Gold contacts \$2.00

VIDEO TAPE BONANZA New American made 1/2" cobalt energized video tape 2400' on 7" reel in nice box. \$21 each, 5 & up — \$15 each.

RUBBER TAPE RECORDER Drive Belt assortment \$1.00

6 FEET LONG! cord, not shielded with female connector on one end only \$.25

CAR LIGHTER PLUG w/5 foot cord! \$.50

RADIO & INSTRUMENT KNOBS over 100 types. \$.05 each.

TRANSISTOR TAPE RECORDER 1/2 track mono head assembly for 1/4" tape. Consists of erase, R/P heads, pressure pads mounted on base plate as used in MAYFAIR 1802. A steal at \$1.00 each.

RECORD/PLAY tape heads for 8 track stereo cart & 2 track mono cassette. Your choice \$1.00 each

LV BRIDGE & 1/2 BRIDGE RECT. Fine for meters other LV 500 mA. Your choice \$.25

MINI & MICRO JAX for mic or earphone your choice. 2 circuits w/nc sw. \$.25, 5/\$1.00

4P 3 POS ROTARY SW 5/16" thread 1/4" diameter shaft. \$.25

JUNK BOX SURPRISE All good parts. Quantities too small to advertise. \$2.50

ASSORTED TRANSISTOR RADIO 455 kc & 10.7 i-f transformers & osc. coils. Over 100 types. Micros, minis, etc. 4/\$1.00. Specify 1st, 2nd, 3rd i-f or osc. & size, 455 or 10.7.

GET A GRIP! Handles — use for mobile mounts. Chrome, 4" x 11", large hole in end \$.25

SUPER SMALL TRIMMER CAPS — rotational, singles — \$.20, duals — \$.25, quads — \$.50. Terrific for xtal netting. Multis have common "GND"

ASSORTMENT of 110V AC phono, tape, fan motors. Also some DC phono and tape motors \$1.00

ASSORTED FERRITE ANTENNAS & RODS. Over 50 types. 4/\$1.00, 1 of each \$10.00

ELECTROLYTICS

40/20/20	50WVDC Upright Tab MT
40/20/5	150/150/25 1-7/8L x 7/8Dia.
1200/1200	15V Can 50¢ ea.
1000/1000	20V Can 50¢ ea.
3300	16V Tubular 25¢ ea.
500	15V Tubular 25¢ ea.
500	50V Tubular 25¢ ea.
500	10V Tubular 25¢ ea.
470	10V Tubular 25¢ ea.

Assortment other values 4/\$1.00

Over 1/2 million parts on hand! The boss says get rid of 'em. 50% off if you'll buy all we have of an item! Top that \$1 a pack people.

All sales cash with order, include estimated UPS charge for shipping. \$2.00 minimum order. No COD under \$10.

COMMUNICATIONS UNLIMITED

9519 MAIN STREET P.O. BOX 463
WHITMORE LAKE, MICHIGAN 48189

STORE HOURS
NOON-6pm TUES.—SAT. (313) 449-4367



The Hybrid Analog TONE GENERATOR

MH8913J \$18.00



DATA and APPLICATION SHEETS FURNISHED WITH ORDER



general specifications


- Frequency Drift(1): < 1.5%
- Group Amplitude Stability: ±25%
- Total Distortion (Harmonic + Intermodulation): < 5% (relative to level of fundamental frequencies)

- Typical Rise Time to Specified Output and Frequency:
- 1) Frequency selected, power supply switched < 5ms
 - 2) Power applied, frequency selector switched < 2ms
 - 3) Power applied, frequency within same group changed < 2μs


features

- Dual Frequency Capability
- Standard Telephone Tone-Dial Frequencies: Low Group - 697, 770, 852, 941 Hz; High Group - 1209, 1336, 1477, 1633 Hz
- Specification Ratings Exceed CCITT Recommendations

typical circuit connection diagram

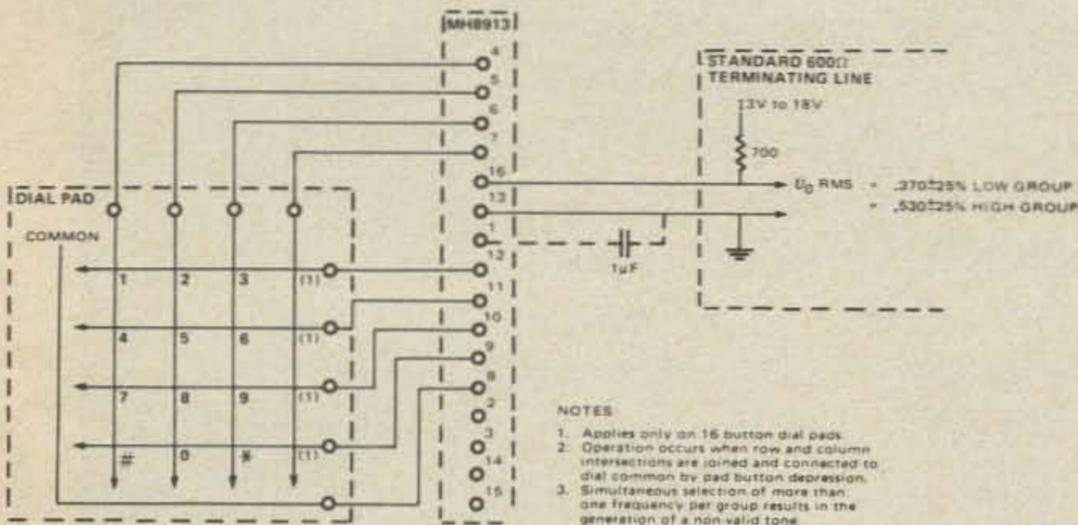

block diagram and pin configuration

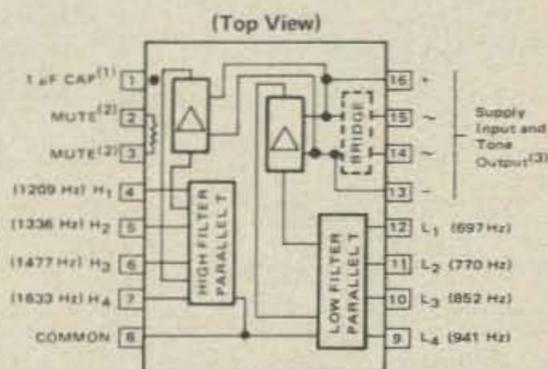


MH8913J CAN BE USED WITH CHOMERICS #ER21624 TOUCH TONE KEYBOARD




QUICKEY® TACTILE KEYBOARDS

FORMATS
Standard legends are black and white set in Standard Medium type.

CALCULATOR FORMATS

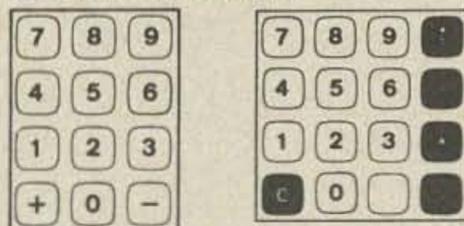


TOUCH TONE FORMATS

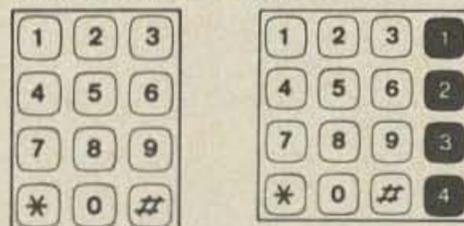

CODING


Touch Tone 12 Key

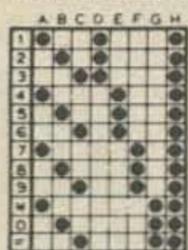


BCD 12 Key




Single Pole 12 Key

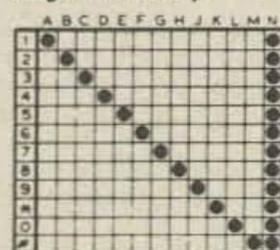

Touch Tone 16 Key

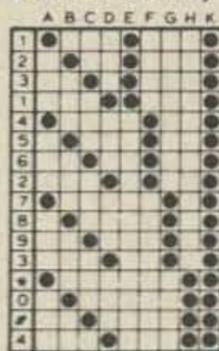

Single Pole 16 Key

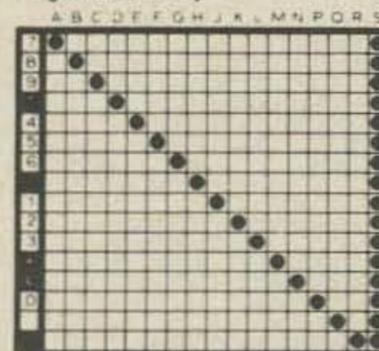

1/2" centers		3/4" centers		Format	Coding	# of Keys
Model #	Price	Model #	Price			
ER 21622	7.15	ER 21605	7.70	Touch tone	Single pole	12
ER 21623	8.70	ER 21606	9.25	Touch tone	Touch tone	12
ER 21624	9.25	-	-	Touch tone	Direct to MH8913	12
-	-	ER 21607	7.70	Calculator	Single pole	12
-	-	ER 21608	11.00	Calculator	BCD	12
ER 21625	8.70	ER 21609	9.25	Calculator	Single pole	16
-	-	ER 21610	9.25	Touch tone	Single pole	16
-	-	ER 21611	11.15	Touch tone	Touch tone	16

KA CATALOG 25¢ OR FREE WITH ORDER

ELECTRONICS FOR THE HAM and EXPERIMENTER

KA ELECTRONIC SALES (214) 634-7870
1220 MAJESTY DR DALLAS, TEXAS 75247 TWX 910-861-9028

The New Hy-Gain 270 brings state-of-the-art design to 2 meter mobile.

The Hy-Gain 270 is specifically designed to solve the problems common to 2 meter gain antennas...hard tuning, high VSWR, poor pattern due to irregular ground plane, and "picket fencing" from whip flex. The 270 develops outstanding gain through use of two stacked $\frac{5}{8}$ wave radiators and operates completely independent of car body grounding by utilizing a self-contained, $\frac{1}{4}$ wave decoupling system. There is no irregular ground plane, so there's minimum pattern distortion and fading due to whip flex. This all-fiberglass design can be used anywhere, fixed, land-mobile or marine, with the 271 mount.

- 250 watt rated.
- 6.0 db gain.
- 144-148 MHz.
- VSWR less than 1.5:1 at resonance.
- 96" whip height.
- No pruning required, completely factory tuned!
- 50 ohm input.
- $\frac{3}{8}$ x 24 standard mobile thread.
- Comes with 18' coax and PL-259 connector.

Order No. 270

Mounts—Universal No. 271
Flush Body No. 499
Bumper No. 415

Get maximum range...get a Hy-Gain 270!

**hy-gain**


Hy-Gain Electronics Corporation; 8601 Northeast Highway Six; Lincoln, NE 68507; 402/464-9151; Telex 48-6424.
Branch Office and Warehouse; 6100 Sepulveda Blvd., #322; Van Nuys, CA 91401; 213/785-4532; Telex 65-1359.
Distributed in Canada by Lectron Radio Sales, Ltd.; 211 Hunter Street West; Peterborough, Ontario.

2 METER F.M. portable

4 CHANNELS 2 WATTS
DUAL CONVERSION

HT-144

ONLY **\$99.95** *KIT*

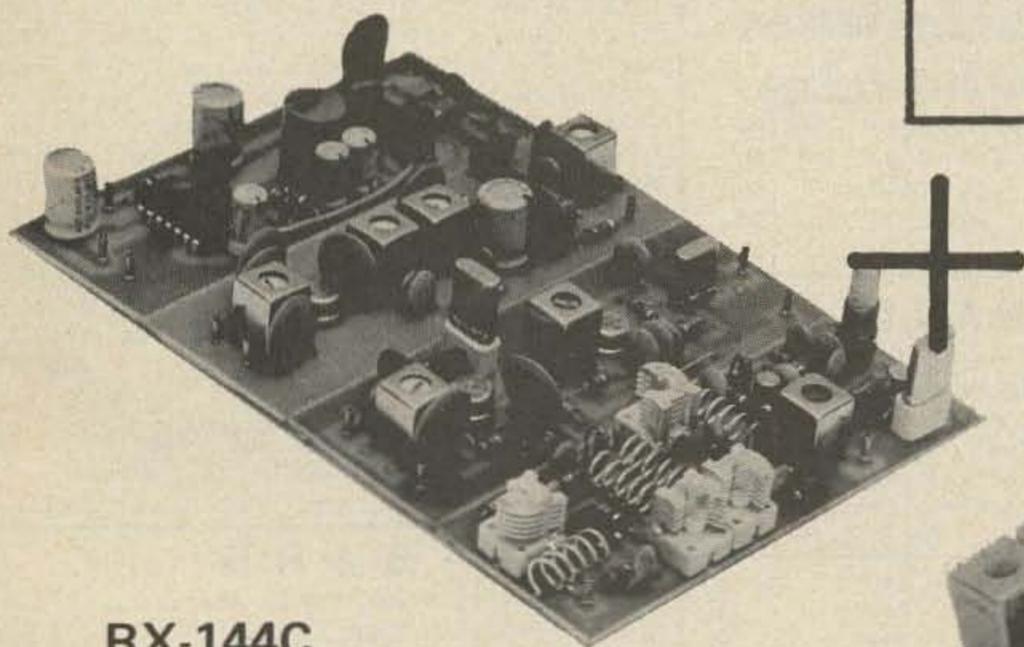

RX-144C

\$69.95

KIT



TX-144

\$29.95

KIT

= BASE OR MOBILE STATION



VHF ENGINEERING

- DIV. of BROWNIAN ELECT. CORP. -

320 WATER ST. POB 1921 BINGHAMTON, NY 13902 607-723-9574



7-SEGMENT READOUT 12-PIN DIP

- Three digits with right-hand decimal
 - Plugs into DIP sockets
 - Similar to (LITRONIX) DL337
 - Magnified digit approximately .1"
 - Cathode for each digit
 - Segments are parallel for multiple operation
 - 5 - 10 MA per segment
- EACH \$3.00 4 (12 Digits) \$11.00

BRAND NEW

RCA NUMITRON

EACH.....\$ 5.00

SPECIAL: 5 FOR \$20.00

DR2010



Potter & Brumfield

TYPE KHP RELAY 4 PDT 3A
CONTACTS

24 VDC (650
coil)....\$1.50

120 VAC (10.5 MA
coil).... 1.75



Power Supply SPECIAL!

723 DIP variable regulator
chip 1-40V, + or - output @ 150
MA 10A with external pass trans-
istor--With diagrams for many
applications.

EACH....\$1.00 10 FOR....\$8.95

CT5005 CALCULATOR

This calculator chip has a full four-
function memory, which is controlled
by four keys, +M (adds entry into
memory), -M (subtracts entry from
memory), CM (clear memory, without
clearing rest of registers), RM (read
memory or use as entry).

12-Digit display and calcu-
late

Fixed decimal at 0, 1, 2,
3, 4, or 5

Leading zero suppression

7-Segment multiplexed output

True credit sign display

Single 28-pin chip

CHIP AND DATA.....ONLY \$14.95

DATA ONLY (Refundable)..... 1.00

5001 CALCULATOR

40-Pin calculator chip will add, sub-
tract, multiply, and divide. 12-Digit
display and calculate. Chain calcula-
tions. True credit balance sign out-
put. Automatic over-flow indication.
Fixed decimal point at 1, 2, 3, or 4.
Leading zero suppression. Complete
data supplied with chip.

CHIP AND DATA.....ONLY \$9.95

DATA ONLY (Refundable).... 1.00

5002 LOW POWER CHIP AND DATA..12.95

All ICs are new and fully-tested;
leads are plated with gold or solder.
Orders for \$5 or more will be shipped
prepaid. Add 35c for handling and
postage for smaller orders; residents
of California add sales tax. IC or-
ders are shipped within 2 workdays--
kits are shipped within 10 days of
receipt of order. \$10.00 minimum on
C.O.D.s (phone in).

MAIL ORDERS:

P. O. Box J 4811 Myrtle Ave.
Carmichael, CA Sacramento, CA
95608 (916) 334-2161

MONEY BACK GUARANTEE ON ALL GOODS!

SEND FOR FREE FLYER LISTING 100's OF
MONEY-SAVING BARGAINS!

**BABYLON
ELECTRONICS**

CTμL SPECIAL:

Complementary Transistor Logic

This logic family is unique in
that both NPN and PNP transis-
tors are combined in the same
package. Unlike TTL and DTL,
the outputs are current sour-
ces (in the high state) as
well as sinking current in the
low state. Those are brand new
units, some of which are mis-
marked with DTL numbers.



CTL 9956 dual 2-in-
put AND buffer
CTL 9953 2-2-3input
AND/OR gate
CTL 9952 dual 2-in-
put NOR gate

Data supplied; all parts are
dual-in-line.

MIX OR MATCH 5 FOR \$1.00

LED's

MV50 red emitting \$.20
10-4 ma @ 2V 10 FOR 1.25

MV5024 red TO-18 \$.35
high dome 10 FOR 2.95

MV10B visible red \$.30
5-7 ma @ 2V 10 FOR 2.50


CMOS

CD4001 \$.75 74C20 .75
CD4002 .75 74C160 3.25

3-Amp Power Silicon Rectifiers Marked Epoxy Axial Package

PRV	PRICE	PRV	PRICE
100.....	\$.10	800.....	\$.30
200.....	.15	1000....	.40
400.....	.18	1200....	.50
600.....	.23	1500....	.65

MAN 1

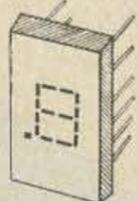

7-Segment, 0-9 plus
letters. Snaps in 14-
pin DIP socket or Mo-
lex. Operates with IC
voltage requirements.
Long operating life.
ONLY \$3.25

7400	\$.25	74L51	\$.30
74H00	.35	74H51	.35
7401	.20	7453	.20
74H01	.35	7454	.25
7402	.35	74L54	.35
7403	.30	74L55	.35
7404	.28	7460	.20
74H04	.35	74L71	.30
7405	.28	7472	.40
7406	.70	74L72	.50
7408	.35	7473	.60
74H08	.35	74L73	.75
7410	.25	7474	.65
74H11	.35	74H74	.80
7413	1.25	7475	1.40
7417	.40	7476	.60
7420	.25	74L78	.80
74L20	.35	7480	.65
74H20	.35	7483	1.00
74H22	.35	7489	4.00
7430	.25	7490	1.20
74H30	.35	7492	.90
74L30	.40	7493	1.15
7440	.25	7495	1.15
74H40	.35	74L95	2.00
7441	1.25	74107	.70
7442	1.20	74121	1.25
7446	1.75	74154	2.30
7447	1.50	74193	1.50
7448	1.50	74195	1.00
7450	.25		
74H50	.35		
7451	.25		

7400 Series DIP



RECTIFIERS

VARO FULL-WAVE BRIDGES

V5447 2A 400V \$.90
V5647 2A 600V 1.10

MR810 Rect. 50V 1A .10

Special 811: Hex Inverter


TTL DIP Hex Inverter; pin interchangeable
with SN 7404. Parts are brand new and are
branded Signetics and marked "811."

Data Sheet Supplied EACH.....\$.30
10 FOR..... 2.50
100 FOR.... 23.00
1000 FOR... 220.00



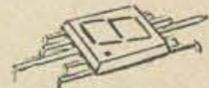
0-9 plus letters. MAN 3

Right-hand decimal point.
Flat-pack type case. Long
operating life. IC vol- EACH \$1.25
tage requirements. Ideal 10 OR MORE 1.00
for pocket calculators!



MAN4 Seven-segment, 0-9 plus let-
ters. Right-hand decimal point. Snaps in
14-pin DIP socket or Molex. IC voltage re-
quirements. Ideal for desk or pocket calcu-
lators!

EACH.....\$2.75
TEN OR MORE 2.50 EACH

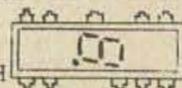


CD-2 Counter Kit

This kit provides a highly sophisticated
display section module for clocks, counters,
or other numerical display needs. The unit
is .8" wide and 4 3/8" long. A single 5-volt
power source powers both the ICs and the
display tube. It can attain typical count
rates of up to 30 MHz and also has a lamp
test, causing all 7 segments to light. Kit
includes a 2-sided (with plated thru holes)
fiberglass printed circuit board, a 7490, a
7475, a 7447, a DR 2010 RCA Numitron display
tube, complete instructions, and enough
Molex pins for the ICs . . NOTE: boards can
be supplied in a single panel of up to 10
digits (with all interconnects); therefore,
when ordering, please specify whether you
want them in single panels or in one multi-
ple digit board. Not specifying will result
in shipping delay.

COMPLETE KIT, ONLY \$11.95

FULLY-ASSEMBLED
UNIT \$15.00

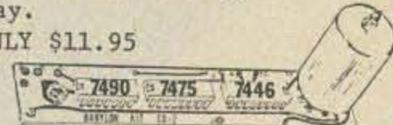

Boards supplied separately @ \$2.50 per digit.

LINEARS

NE540	70-Watt power driver amp.....	\$2.00
NE555	Precision timer.....	1.50
NE560	Phase lock loop DIP.....	3.25
NE561	Phase lock loop DIP.....	3.25
NE565	Phase lock loop TO-5.....	3.25
NE566	Function generator TO-5.....	4.00
NE567	Tone decoder MINI DIP.....	4.00
NE567	Tone decoder TO-5.....	3.00
NE5558	Dual 741 op amp MINI DIP.....	1.00
709	Popular Op Amp DIP.....	.45
710	Voltage comparator DIP.....	.75
711	Dual comparator DIP.....	.40
723	Precision voltage regulator DIP.	1.00
739	Low noise op amp DIP unmarked...	1.00
741	Op amp TO-5/MINI DIP.....	.55
747	Dual 741 op amp DIP.....	1.00
748	Op Amp TO-5.....	1.00
CA3018	2 Isolated transistors and a Darling- ton-connected transistor pair...	1.00
CA3026	Dual differential amp.....	1.00
CA3045	5 NPN transistor array.....	1.00
LM100	Positive DC regulator TO-5.....	1.00
LM105	Voltage regulator.....	1.25
LM302	Op amp voltage follower TO-5....	1.25
LM308	Op Amp TO-5.....	2.00
LM309H	5V 200 MA power supply TO-5....	1.00
LM309K	5V 1A power supply module TO-3..	2.00
LM311	Comparator TO-5.....	1.75
LM370	AGC amplifier.....	2.00
LM380	2-Watt Audio Amp.....	1.75
LM1595	4-Quadrant multiplier.....	2.00
MC1536T	Op Amp.....	2.00

ANOTHER SELECTRONIC SPECIAL

For This Issue Only

RADIO RECEIVER R-392/URR

Freq. Range: 500 KC to 32 MC in 32 bands. Types of Signals Received: CW, MCW, Voice (AM) and Freq. Shift Radio Teletypewriter. Type of Tuning: Continuous: Freq. Read Directly on Counter—Type Freq. Indicator. Method of Calibration: Built-in crystal Calibrator. Calibration Points: Every 100 KC. Nominal Input Voltage: 28 Volts DC; will operate on an input of 25 to 30 V, will operate at reduced gain.

PRICE: \$195.00 F.O.B. Philadelphia, PA

Shipping Wt. 50 lbs. (with schematic)



FOR THIS ISSUE ONLY

We will include with every purchase the following accessories for the above receiver — **FREE**

- 1 Whip Antenna _____ \$4.95
- 1 Speaker _____ \$4.95
- 1 Mike _____ \$2.95
- 1 Set Connecting Cables _____ \$2.50
- 1 Head Set _____ \$4.95
- 1 Telegraph Key _____ \$1.95

ADJUSTABLE PRINTED CARD BOX

For Rack Mount

5" to 7 1/4" — 16 slides and sockets — includes 30 double contact position edge connector type
PRICE \$9.95

MODERN ALUMINUM BENCH RACK CABINET

11 1/2" H x 18" D x 19" W. 8" panel openings w/rubber feet and disappearing handle.
Lt Blue **Price: \$7.95 ea.**

Triad transformers F-21A 115 Volts 60 cycles 6.3 VCT at 10 Amps.

Price: \$4.95.

R-508 VHF RECEIVER

118-148 MHz, part of ARC-60 aircraft radio set. Front panel tuning 118-148 MHz, lightweight, compact, 5" x 6" x 12". 28 VDC input, 250V, 50mA, dynamotor.

Price: \$14.95

HELIPOT DIGITAL

Turns counting digital dial model 201 3 digit direct reading w/10 turn 5k/5% pot.

Price: \$2.50 each, 5/\$10.00

DIGITAL READOUTS SETS

Make your own counter, frequency meter, digital voltmeter, readouts, etc. Includes 6-B 5031 mixes w/sockets (6" character height), 1 transformer, 1 p/s board with socket.

Price: \$12.95, 2/\$20.00

Small B-5031 nixies no board w/socket 4/\$5.00

**ANOTHER SPECIAL
LARGE ALPHA NUMERIC READOUTS**

Two B7971 tubes in sockets, driver transistors and components all on one board — can be used for clocks, counters, numerous other uses. . . .

Price: \$2.00 a board, 3/\$5.00

SOCKETS

Sockets for 4 x 150's — 2 sockets with chimney, mounted on aluminum chassis

Price: \$7.00

Lighted switches 2 pdt push pole panel mount 5/8" hold.

Price: \$1.00 each, 6/\$5.00

MODULE TYPE P/S

AC input 95-125 VAC-60Hz-100 watts.

+12VDC^a .375A

- 12VDC^a .3A

- 6VDC^a .375A

Regulation 1%. Front panel adj. ±10%. 5 1/8" x 7 3/8" x 7"

Price: \$14.95, 2/\$25.00

ALL PRICES ARE F.O.B. OUR WAREHOUSE, PHILADELPHIA, PA. ALL MERCHANDISE DESCRIBED ACCURATELY TO THE BEST OF OUR KNOWLEDGE. YOUR PURCHASE MONEY REFUNDED IF NOT SATISFIED. TERMS ARE CASH. MIN. ORDER \$5.00. ALL MERCHANDISE SUBJECT TO PRIOR SALE. RFE — REMOVED FROM EQUIPMENT.

SELECTRONICS

1206 South Napa Street
Philadelphia, PA 19146
215-468-7891 215-468-4645

IT ONLY HAPPENS ONCE IN A LIFETIME!



NORELCO VIDEO TAPE RE-
CORDER-PLAYBACKS

tape

*YOUR FAVORITE TV
SHOWS...*



build

*AN INEXPENSIVE
LIBRARY OF THE TV
SHOWS YOU LIKE BEST...*

- *WEIGHS ONLY 26 POUNDS
- *LONG LIFE FERITE HEADS
- *EXTREMELY QUIET
- *USES INEXPENSIVE 1/2" TAPE
- *HORIZ RESPONSE 2½ MHz
- *OPERATES FROM 110 VOLT AC.
- *SOME MODIFIED WITH LIGHT TO INDICATE UNIT IN USE.
- *STANDARD AUDIO-VISUAL SIGNALS

BRAND NEW, AS IS...\$399.00

ALSO, SHIBADEN FP-707 VIDICON CAMERA, WITH CRT VIEWFINDER AND LENSES 12 VOLT D.C. REQUIRED AND EXTERNAL SYNC...NEW COST \$750.00, NOW **\$325.00**

AC POWER SUPPLY AND SYNC GENERATOR FOR THE ABOVE...NEW: **\$65.00**

HUNDREDS OF ADDITIONAL VIDEO ITEMS, WRITE FOR LIST, SASE

COMMUNICATIONS UNLIMITED

9519 MAIN STREET P.O. BOX 463
WHITMORE LAKE, MICHIGAN 48189

Store hours, noon to 6PM, Monday thru Saturday. (313-449-4367)

hy-gain

REPEATER LINE

All you need to know about
2 meter mobile antennas!

263 Special no-hole trunk lip mount. 3 db gain. 130-174 MHz. 5/8 wave. 16' coax. DC ground. Base matching coil for 52 ohm match. 17-7 ph stainless steel whip.

264 High efficiency, vertically polarized omnidirectional roof top whip. 3 db gain. Base matching coil for perfect 52 ohm match. DC ground. Coax and connector furnished.

265 Special magnetic mount. 3 db gain. Performance equal to permanent mounts. 12' coax and connector. Base matching coil for 52 ohm match. 17-7 ph stainless steel whip. DC ground.

Rugged, continuously loaded, flexible VHF portable antennas. Completely insulated with vinyl coating. Bend at all angles without cracking or breaking. Cannot be accidentally shorted out.

723N With UHF connector.

269 With 5/16-32 base for Motorola HT; Johnson; RCA Personafone; Federal Sign & Signal; and certain KAAR, Aerotron, Comco and Repco units.


723A With BNC connector.

260 Commercial duty, 1/4 wave, claw mount, roof top whip. Precision tunable to any discrete frequency 108-470 MHz.

261 Same as above, with 18' coax and connector.

262 Magnetic mount whip, 108-470 MHz. 52 ohm match. Complete with coax and connector.

Write for details

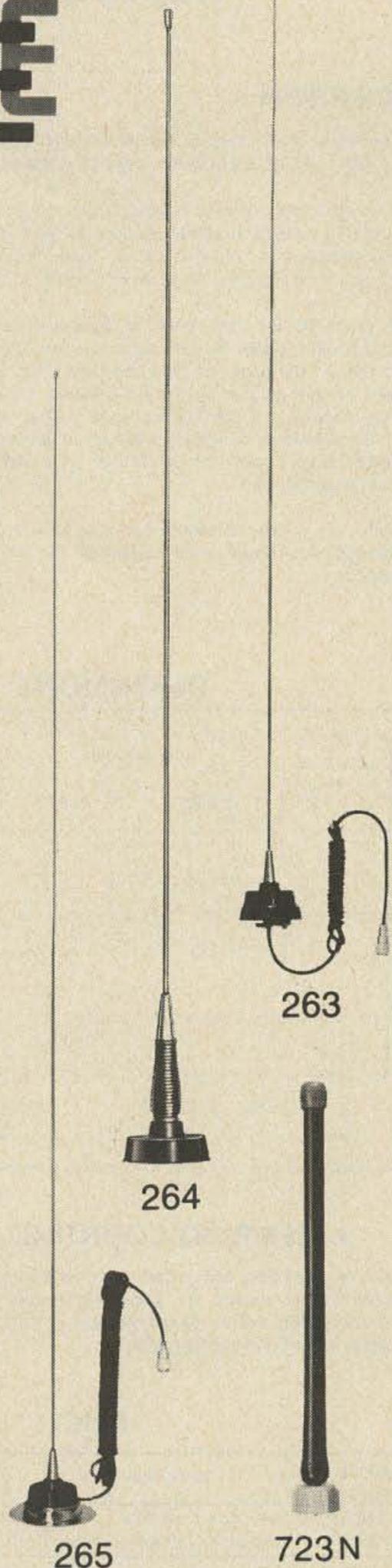

hy-gain

ELECTRONICS CORPORATION

Dept. CB, 8601 Northeast Highway Six, Lincoln, NE 68507
402/464-9151

Telex 48-6424

Distributed in Canada by: LECTRON RADIO SALES, LTD. 211 Hunter Street West, Peterborough, Ontario

"REAL GOOD STUFF"

RGS ELECTRONICS

SPECIAL - THIS MONTH ONLY:

MAN3 4 for \$2.00
MAN4 4 for \$4.00

TTL

7400 S	.25	7475	1.00
7401	.25	7476	.65
7402	.25	7483	1.25
7403	.25	7485	1.40
7404	.30	7486	.50
7405	.30	7489	3.25
7406	.50	7490	1.00
7407	.50	7492	1.00
7408	.30	7493	1.00
7409	.30	7495	1.00
7410	.25	7496	1.00
7411	.30	74107	.60
7413	.90	74121	.60
7416	.50	74122	.60
7417	.50	74123	1.10
7420	.25	74125	.65
7430	.25	74126	.65
7432	.30	74141	1.25
7437	.50	74151	1.10
7438	.50	74153	1.40
7440	.25	74154	1.70
7442	1.10	74157	1.40
7446	1.45	74164	2.00
7447	1.45	74165	2.00
7448	1.45	74166	2.00
7450	.25	74176	1.60
7451	.25	74177	1.60
7453	.25	74181	4.50
7454	.25	74192	1.75
7473	.50	74193	1.50
7474	.50	74195	1.15
74200	9.00		

WIRE WRAP SOCKETS

14 pin	\$.50
16 pin	.60
24 pin	1.25
28 pin	1.35
40 pin	1.80
wire-wrap socket pins	.05

\$4/100

1/4 WATT RESISTORS

\$.05
\$4/100

We have most 10% values.

1N914 EQUIVALENT DIODES

\$.10 \$8/1.00

NEW - REAL GOOD STUFF

PS 25-1 Zero to 25 volt 1 amp power supply with adjustable current limiting; has remote sensing & remote programming for voltage and current. Instructions included. All parts supplied except chassis & meter(s).

Kit of parts with schematic \$14.95

LT-1 Digital logic tester, uses 5 volts, will test TTL, DTL and CMOS. Has internal slow clock. All parts supplied except power supply, chassis, panel & board.

Kit of parts with schematic \$19.95

PS 5-1 5 volt 1 amp regulated power supply kit with p.c. board and instructions. Board measures 2" x 6"; completed kit is 2" high. Transformer has internal r.f. shield.

\$8.00

OP AMPS

301T	\$.50
301M	.45
307T	.70
307M	.65
318T	1.50
709D	.20
709T	.30
709M	.25
739D	1.00
741D	.35
741T	.50
741M	.45
748M	.40
747/5558T	1.05
5558M	1.00
4131M	1.00
4132M	1.25

LEGEND

T = TO-5
D = DIP
M = miniDIP

JUNCTION FETs, TO-18 case

N-CHANNEL: SIMILAR TO:	
NJF10	2N4416, MPF102 3/\$1.00
NJF11	2N4091-93 4/\$1.00
NJF12	2N4338-41 4/\$1.00
NJF13	2N3089 3/\$1.00
NJF14	2N4221-22 4/\$1.00
P-CHANNEL:	
PJF11	2N3382-86 4/\$1.00
PJF14	2N2608 4/\$1.00

All FETs come with data sheets.

TRANSISTORS

NPN TO-18 general purpose	
silicon	.15
10 or more,	.10
PNP TO-18 general purpose	
silicon	.15
10 or more,	.10
2N2222 (NPN) TO-18	.25
10 or more,	.20
2N2907 (PNP) TO-18	.25
10 or more,	.20

LEDS

LED 10R - Pack of 10 discrete red lens LEDs, various MV5020-series types. \$1.50
LED 10C - Pack of 10 discrete clear lens LEDs, various MV5020-series types. \$1.50
Application note included.

RGS ELECTRONICS (408) 247-0158
3650 Charles St., Suite K, Santa Clara, CA 95050

TERMS OF SALE: All orders prepaid; we pay postage. \$1.00 handling charge on orders under \$10.00. 10% off on orders over \$25.00. California residents please include sales tax. Please include name, address and zip code on all orders and flyer requests.



RT-70/GRC \$20 each, 3/\$50


Latest government release. Transmitter-Receiver RT-70/GRC covers 47 to 58.4 mc FM. Requires only 90 Volts dc and 6 volts dc. Used, visually OK, supplied with schematic. **1 MC crystal used for calibration \$4.00**
116 page maintenance manual for GRC \$2.00

TRANSFORMERS

BRAND NEW, 115 volt AC input. OP . AMP XFMR, out puts: 16 VCT 1/2 amp, 17 VCT 1/2 amp. \$3.50


FILAMENT or BTRY CHARGER XFMR

output of 18 volts at 4.5 amp \$3.50

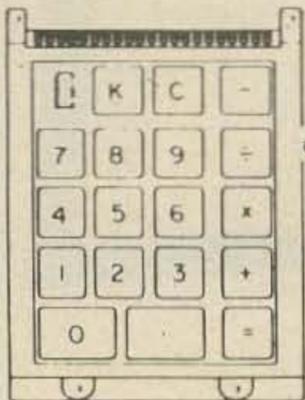

CALCULATOR KEYBOARD

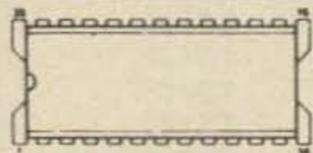Brand new keyboards for hand held calculators. Two styles available. One for use with calculator chip CAL TEX 5001-5002-5012 or MOSTEK 5010-5012. Another for use with Gen. Inst. chip C500. Priced at ~~\$8.00~~ each or two for ~~\$15.00~~ ^{\$5.00} ^{2/\$9.00}



CT 5005 CALCULATOR CHIP

Single MOS chip with all logic required for 12 digit 4 function desk top calculator with extra storage register for memory or constant. Multiplexed 7 segment outputs for LED, Incandescent, Fluorescent, or Gas Discharge displays. Brand new, bargain priced, with specs. \$8.00 each, 2 for \$15.00

AM-FM RADIO \$5.50

Due to the West Coast ship strike they came in too late for the customer. Now it's your bargain. Use it as is or build it into your own cabinet, desk, wall, etc. All built, ready to use, with AC supply. To make it portable all you do is power it with a couple of "D" cells. Fully assembled solid state chassis with AC power supply, less speakers. Covers full AM as well as FM broadcast. The price. . . an astounding meager \$5.50

313,344 CORE MEMORY \$125.00

From SPECTRA computer, visually OK. 64 x 68 x 4 x 18 core stack. Figures out to 35K Byte.



CLOCK/CALENDAR ALARM CHIP

These large scale integrated (LSI) chips eliminate literally thousands of components or hundreds of chips in the construction of a clock. For most applications only a single supply and a minimum of components are required. 7001 Chip - Features 28/30/31 day calendar, 12/24 hour clock, 24 hour clock, 24 hour alarm, snooze alarm, 6 digit display, direct drive to luminescent anode tubes or LL segments, single transistor interface with Sperry displays. Segment and digital outputs can be "wire or "D" to share calculator displays. \$9.95 each, 2/\$18.00

IC SALE YOUR CHOICE 3 for \$1.00

- μl 900 BUFFER TO-5
- μl 914 DUAL 2 INPUT GATE TO-5
- μl 923 JK FLIP FLOP TO-5
- μl 926 Hi speed JK FLIP FLOP TO-5
- μl 931 JK/RS FLIP FLOP (DIP)
- 10 pin socket for TO-5 IC 3/1.00



GIANT NIXIE B7971

Used \$1.00 Brand New \$2.00
 With schematic for GIANT clock.

COMPUTER TAPE DECK \$75.00

Takes 1/2 inch tape, made by Computer Entry Systems. Visually ok, with electronics, no data available.

Calculator Chips

5001 LSI (40 pin) Add, subtract, multiply, divide 12 digit. With data \$6.95
 Data alone 50 cents

CMOS 4814 HEX INVERTER

CMOS HEX INVERTER, dual inline package. 3-18 volt range, dual diode protection against static charge. Dielectrically isolated complimentary MOS. \$1.00 each 12 for \$10.00

DUAL 16 BIT MEMORY

Dual 16 bit memory, serial MOS by Philco TO-5 case, brand new with 2 page specs. #PLR 532 \$1.00 each \$10/12

2048 BIT MOS MEMORY

2048 bit MOS LSI random access memory NEC 6003. All inputs except clock are TTL compatible. 2048 word by 1 bit. 22 pin ceramic dual-in-line. With specs. \$5.00 EACH ~~\$9.00~~ each 2 for \$9.00

RCA INJECTION LASER DIODES

Another SUPER SCOOP by Meshna. Brand new RCA packaged, considered obsolete by RCA but what an exotic opto-electronic device for the sophisticated experimenter. Only several hundred on hand. Values shown are approx. as each diode characteristic varies. Each is marked with correct value.
 6 WATT \$10.00
 10 WATT \$15.00

Meshna

Postage extra on above. MESHNA PO Bx 62 E. Lynn Mass. 01904



ASCII KEYBOARDS W/ENCODER


From Raytheon, new or like new. 5 extra function buttons each side. Open faced, no cabinet. Schematic provided. Price is postpaid world wide.
\$46.00

AUTOMOBILE REVERB

Brand new fully assembled, ready to install in your car to give 3rd dimension concert hall effect. Complete with instructions, rear seat speaker, grill, wires, plugs.
05 \$7.00

15 AMP BATTERY CHARGER

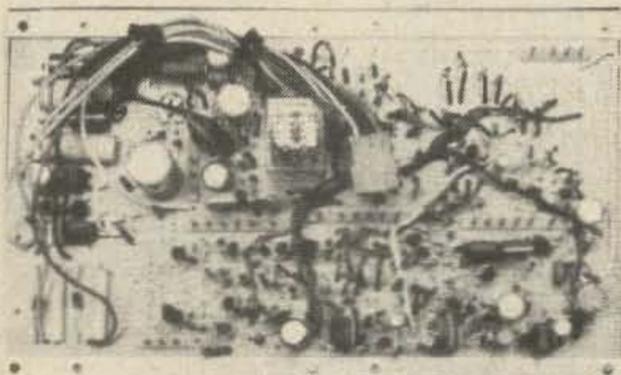Brand new GE transformer, 25 amp fullwave bridge. Output approximately 15 volts up to 15 amps. Ideal battery charger or DC source for general use. With instructions , assembled in minutes.
PK-4 \$10.00



TV POWER SUPPLY & TRANSPORT CIRCUIT

A complete assembled PC board, spares from a video tape machine. Many many fine components to be found. One section of the board used as a 12 volt and 24 volt regulated power supply. You add the transformer and output will be 24 volts transistor regulated as well as another output of 12 volts transistor regulated. 3 amps on the 12 volts and 1 amp on the 24 volt section. Full schematic of the complete board included. These are unused and cost in excess of \$200.
B74-1 \$6 or 3/\$15

8 TRACK STEREO TAPE DECK

With built-in stereo pre-amp, 115 volt drive motor, channel indicator lamps. Unused, original boxed, less cabinet. Customize your stereo music center with one of these tape decks.
46 \$14.00

UNDERWATER LISTENING

Brand new by OLIN. Use it for a swim pool monitor-alarm, use it on lake or ocean listening to underwater noises, fish, etc. Complete with hydrophone, 50 ft. mike cable, speaker-amplifier console. Operates from 115 volts AC or 15 volt dry cells. 12 lbs.
\$25.00

RCA TD-2 TUNNEL DIODE

Original packaged, each factory marked, with spec sheet.
\$1.25 each, 5/\$5.00.

CALCULATOR KIT

Includes 8 digit LED readout, Keyboard, Calculator Chip – all for **\$15.00**

RCA INJECTION LASER DIODES

Another SUPER SCOOP by Meshna. Brand new RCA packaged, considered obsolete by RCA but what an exotic opto-electronic device for the sophisticated experimenter. Only several hundred on hand. Values shown are approx. as each diode characteristic varies. Each is marked with correct value.

6 WATT \$10.00
10 WATT \$15.00

2N2152	45 volt	170 watt	PNP-G	\$1.00
*2N3713	80	170	NPN-S	1.00
*2N3789	60	150	PNP-S	.75
2N5301	40	200	NPN-S	1.25
*2N5301	40	200	NPN-S	1.00

*Removed from used equipment

Postage extra on above. **MESHNA PO Bx 62 E. Lynn Mass. 01904**

Meshna

NEW 96 PAGE CATALOG NOW READY

**NATIONAL BUY ANY 3 — TAKE 10%
LINEAR OP AMPS**

<input type="checkbox"/>	LM-300	POS V.R. (super 723) TO-5	\$.91
<input type="checkbox"/>	LM-301	Hi-performance op amp (A)	.41
<input type="checkbox"/>	LM-302	Voltage follower TO-5	.91
<input type="checkbox"/>	LM-305	Pos. Voltage Reg. TO-5	1.19
<input type="checkbox"/>	LM-307	Super 741 op amp (A)	.41
<input type="checkbox"/>	LM-308	Hi-Q fet type op amp TO-5	1.19
<input type="checkbox"/>	LM-309H	5V Volt-Regulator TO-5	1.19
<input type="checkbox"/>	LM-309K	5V Volt-Reg. 1 Amp TO-3	1.85
<input type="checkbox"/>	LM-310	Voltage-Follower TO-5	1.25
<input type="checkbox"/>	LM-311	Hi-perf. Volt. Comp. (A)	1.19
<input type="checkbox"/>	LM-319	Hi-speed Dual Comp. DIP	1.50
<input type="checkbox"/>	LM-320	MINUS 5, 12 or 24V V.R. TO-3	1.50
<input type="checkbox"/>	LM-339	Quad Comparator, DIP	2.50
<input type="checkbox"/>	LM-324	Quad (4-741's in DIP)	2.50
<input type="checkbox"/>	LM-350	Dual peripheral driver	.41
<input type="checkbox"/>	LM-370	AGC Squelch op amp, TO-5	1.19
<input type="checkbox"/>	LM-373	AM-FM SSB I.A.D. TO-5	3.50
<input type="checkbox"/>	LM-374	AM-FM SS IVAD TO-5	3.50
<input type="checkbox"/>	LM-377	Dual 2-watt audio amp	3.00
<input type="checkbox"/>	LM-380	2-watt audio amplifier TO-5	1.69
<input type="checkbox"/>	LM-381	Low noise dual pre amp DIP	1.95
<input type="checkbox"/>	LM-382	Low noise dual pre amp DIP	1.95
<input type="checkbox"/>	LM-703	RF-IF amp, TO-5	.55
<input type="checkbox"/>	LM-709	Operational amplifier (A)	.36
<input type="checkbox"/>	LM-710	Differential amplifier (A)	.45
<input type="checkbox"/>	LM-711	Dual Differential Amp (A)	.36
<input type="checkbox"/>	LM-723	Voltage Regulator (A)	.69
<input type="checkbox"/>	LM-725	Instrument Op Amp	.95
<input type="checkbox"/>	LM-733	Differential Video	1.75
<input type="checkbox"/>	LM-741	Freq. Comp. 709 (A)	.41
<input type="checkbox"/>	LM-741CV	Mini DIP 741C	.45
<input type="checkbox"/>	LM-747	Dual 741 (A)	.89
<input type="checkbox"/>	LM-748	Freq. adjustable 741C (A)	.44
<input type="checkbox"/>	LM-1303	Stereo pre amp DIP	.95
<input type="checkbox"/>	LM-1304	FM Stereo Multiplexer	1.25
<input type="checkbox"/>	LM-1305	FM Multi. Stereo Dem. DIP	1.25
<input type="checkbox"/>	LM-1307	FM Multi. Stereo Dem. DIP	.91
<input type="checkbox"/>	LM-3028	Differential RF/IF amp	1.50
<input type="checkbox"/>	LM-3900	Quad "current mirror" amp	.95
<input type="checkbox"/>	LM-4250C	Programmable op amp	2.50
<input type="checkbox"/>	LM-75451	Dual peripheral driver	.44
<input type="checkbox"/>	LM-75453	Dual peripheral driver	.44
<input type="checkbox"/>	LM-75491	Quad seg. driver, LED (DIP)	1.65
<input type="checkbox"/>	LM-75492	Hex digit driver, 250ma, DIP	1.85

(A) TO-5 Dip or mini Dip

LINEAR Op Amps *FACTORY MARKED
*FACTORY GUARANTEED *FACTORY TESTED

<input type="checkbox"/>	531	Hi slew rate op-amp (TO-5)	\$2.50
<input type="checkbox"/>	532	Micro power 741 (TO-5)	2.50
<input type="checkbox"/>	533	Micro power 709 (TO-5)	2.50
<input type="checkbox"/>	536	FET Input op amp (TO-5)	2.95
<input type="checkbox"/>	550	Precision 723 voltage reg. (DIP)	1.17
<input type="checkbox"/>	555	Timer 2 u Seconds to 1-hr. (A)	1.25
<input type="checkbox"/>	556	5 Times faster than 741C	2.10
<input type="checkbox"/>	558	Dual 741 (DIP)	1.00
<input type="checkbox"/>	560	Phase lock loops (DIP)	2.95
<input type="checkbox"/>	561	Phase lock loops (DIP)	2.95
<input type="checkbox"/>	562	Phase lock loops (DIP)	2.95
<input type="checkbox"/>	565	Phase lock loops (A)	2.95
<input type="checkbox"/>	566	Function generator (TO-5)	2.95

<input type="checkbox"/>	567	Tone decoder (A)	2.95
<input type="checkbox"/>	702C	Hi-grain, DC amp (TO-5)	.49
<input type="checkbox"/>	704	TV sound IF system	1.50
<input type="checkbox"/>	711C	Dual diff. comp (A)	.33
<input type="checkbox"/>	723C	Voltage regulator (A)	.69
<input type="checkbox"/>	741CV	Freq. comp 709 (Mini DIP)	.44
<input type="checkbox"/>	748C	Freq. adj. 741C (A)	.44
<input type="checkbox"/>	753	Gain Block	1.75
<input type="checkbox"/>	739-739	Dual stereo preamp	1.98
<input type="checkbox"/>	741-741	Dual 741C (TO-5)	.89
<input type="checkbox"/>	PA265	5-Watt voltage regulator	1.00
<input type="checkbox"/>	ULN2300M	Op amp with SCR	1.00
<input type="checkbox"/>	CA3065	Video Audio system	1.00
<input type="checkbox"/>	RC4195	Dual 15V Tracking V.R.	2.50
<input type="checkbox"/>	4136	Quad 741's (DIP)	1.95

(A) TO-5 or DIP Buy any 3 — Take 10%

WRIST WATCH LIQUID CRYSTAL DISPLAY

*3-1/2 digit. 7 segment *Only 1-1/16 x 11/16 x 1/4"

See POPULAR ELECTRONICS (Jan., 1974) for building your own electronic digital wristwatch using the Liquid Crystal Display (LCD) as its basic. Easy to see, 3 1/2 digit display, requires less than 1/1000 of power as LED'S. Visibility increases with ambient light. Difficult reading of LED'S in light. Pulsates SECONDS in center of display. NO NEED OF TRANSISTOR-RESISTOR interface, as LED'S, thus smaller package. Chip contains holder, tiny connecting terminals, and "slide-in-place chrome spring face plate". Size of display in holder: 1-1/16 x 11/16 x 1/4". Operating freq. 32 hertz. 45-microwatts of power. Operates from 1.5V hearing aid cell. Uses the new and latest CMOS micro-circuitry. We include copy of write up from PE magazine.



Only \$19.95



"THE PRO" — HI-Q DYNAMIC PENCIL MIKE

Sold elsewhere for over \$10. All metal construction, with stand, 6-ft. cord, and standard mike plug. By General Electric. NO IMPORT! Highly polished with chrome trim. Omni-directional, 20,000 ohm imp., 60 to 100Khz freq resp. Crisp, ultra-sensitive, high quality, hi-fidelity. Ideal for PA, CB, and all HAM equipment. May be hand-held too! Mike 5" long 1" dia., with taper. Heavy-duty grey metal stand, 2 1/2" x 2 1/4" x 1 1/2". Ideal for our 60w stereo Amp, wt. 1-lb.

Only \$6.95

OVER 1,000,000-PC INVENTORY

Brand New


POLY PAKS SMASHES IC PRICES

* Factory Marked Order by type number! Spec sheets on request "ONLY" Buy 100 — Take 20%

<input type="checkbox"/>	SN7400	\$0.30	<input type="checkbox"/>	SN7432	.55	<input type="checkbox"/>	SN74108	.95	<input type="checkbox"/>	SN74160	1.95
<input type="checkbox"/>	SN7401	.30	<input type="checkbox"/>	SN7437	.55	<input type="checkbox"/>	SN74112	.95	<input type="checkbox"/>	SN74161	1.75
<input type="checkbox"/>	SN7402	.30	<input type="checkbox"/>	SN7438	.55	<input type="checkbox"/>	SN74113	.95	<input type="checkbox"/>	SN74163	1.95
<input type="checkbox"/>	SN7403	.30	<input type="checkbox"/>	SN7440	.30	<input type="checkbox"/>	SN74114	.95	<input type="checkbox"/>	SN74164	2.95
<input type="checkbox"/>	SN7404	.35	<input type="checkbox"/>	SN7441	1.40	<input type="checkbox"/>	SN74121	.60	<input type="checkbox"/>	SN74165	2.10
<input type="checkbox"/>	SN7405	.35	<input type="checkbox"/>	SN7442	1.50	<input type="checkbox"/>	SN74122	.95	<input type="checkbox"/>	SN74166	2.05
<input type="checkbox"/>	SN7406	.45	<input type="checkbox"/>	SN7443	1.50	<input type="checkbox"/>	SN74123	1.20	<input type="checkbox"/>	SN74173	2.50
<input type="checkbox"/>	SN7407	.55	<input type="checkbox"/>	SN7444	1.50	<input type="checkbox"/>	SN74125	.71	<input type="checkbox"/>	SN74175	3.20
<input type="checkbox"/>	SN7408	.35	<input type="checkbox"/>	SN7445	1.50	<input type="checkbox"/>	SN74126	.71	<input type="checkbox"/>	SN74176	2.10
<input type="checkbox"/>	SN7410	.30	<input type="checkbox"/>	SN7446	1.65	<input type="checkbox"/>	SN74140	1.25	<input type="checkbox"/>	SN74177	2.10
<input type="checkbox"/>	SN7411	.35	<input type="checkbox"/>	SN7447	1.45	<input type="checkbox"/>	SN74141	1.95	<input type="checkbox"/>	SN74180	1.20
<input type="checkbox"/>	SN7413	.95	<input type="checkbox"/>	SN7448	1.50	<input type="checkbox"/>	SN74145	1.55	<input type="checkbox"/>	SN74181	3.95
<input type="checkbox"/>	SN7416	.55	<input type="checkbox"/>	SN7450	.30	<input type="checkbox"/>	SN74148	4.50	<input type="checkbox"/>	SN74182	1.20
<input type="checkbox"/>	SN7420	.30	<input type="checkbox"/>	SN7451	.30	<input type="checkbox"/>	SN74150	1.61	<input type="checkbox"/>	SN74185	2.50
<input type="checkbox"/>	SN7421	.55	<input type="checkbox"/>	SN7453	.30	<input type="checkbox"/>	SN74151	1.25	<input type="checkbox"/>	SN74192	1.95
<input type="checkbox"/>	SN7422	.35	<input type="checkbox"/>	SN7455	.55	<input type="checkbox"/>	SN74152	4.95	<input type="checkbox"/>	SN74193	1.95
<input type="checkbox"/>	SN7425	.50	<input type="checkbox"/>	SN7462	.35	<input type="checkbox"/>	SN74153	1.60	<input type="checkbox"/>	SN74194	1.95
<input type="checkbox"/>	SN7426	.55	<input type="checkbox"/>	SN7464	.30	<input type="checkbox"/>	SN74154	2.10	<input type="checkbox"/>	SN74195	1.25
<input type="checkbox"/>	SN7430	.30	<input type="checkbox"/>	SN7465	.50	<input type="checkbox"/>	SN74155	1.55	<input type="checkbox"/>	SN74196	2.50
<input type="checkbox"/>			<input type="checkbox"/>			<input type="checkbox"/>	SN74156	1.45	<input type="checkbox"/>	SN74197	2.50
<input type="checkbox"/>			<input type="checkbox"/>			<input type="checkbox"/>	SN74157	1.55	<input type="checkbox"/>	SN74198	2.65
<input type="checkbox"/>			<input type="checkbox"/>			<input type="checkbox"/>	SN74158	1.55	<input type="checkbox"/>	SN74200	9.95
<input type="checkbox"/>			<input type="checkbox"/>			<input type="checkbox"/>			<input type="checkbox"/>		

* "DIP" Packages

7-SEGMENT LED Readouts

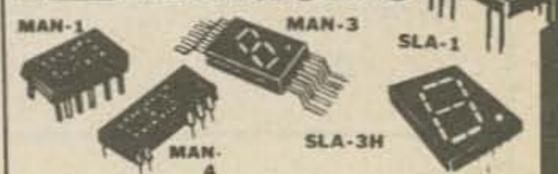


(All "LED" TYPES)

Type	Char.	Each	Special
<input type="checkbox"/> MAN-1	.27	\$3.75	3 for \$9.
<input type="checkbox"/> MAN-3	.12	1.49	3 for \$3.
<input type="checkbox"/> MAN-4	.19	2.50	3 for \$6.

REFLECTIVE BAR TYPES

<input type="checkbox"/> 707*	.33	2.50	3 for \$6.
<input type="checkbox"/> 704*	.33	2.50	3 for \$6.
<input type="checkbox"/> SLA-1**	.33	2.10	3 for \$5.
<input type="checkbox"/> SLA-3**	.70	4.95	3 for \$13
<input type="checkbox"/> SLA-11**	.33†	3.50	3 for \$10
<input type="checkbox"/> SLA-21**	.33††	3.95	3 for \$10.

*By Litronix. **By Opcoa, equal to MAN-1 or MAN-4 specs. Color - RED. †Green. ††yellow

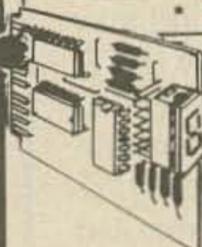

Buy 3 — Take 10%
Only \$9.99

LED MITY DIGIT "DCM'S"

Scientific Devices "Digital Counting Modules" outperform any other DCM on the market today. More features than ever before! Not gaseous, not incandescents, not nixie but the modern LED. Choose from such famous manufacturers as Monsanto's MAN-1, MAN-4, Litronix 707 and 704, Opcoa's SLA-1 (the last 4 having character heights of 0.33 at no extra charge). Each kit includes 3x2" p.c board with fingers for a FREE edge connector, side-mounting dip socket, LED readout of your choice, resistors, 3 IC's, and Molex connectors (this ELIMINATES SOLDERING YOUR IC'S) and booklet. INCLUDES P.C. EDGE CONNECTOR — FREE!

READOUT	Char.	Maker
<input type="checkbox"/> MAN-1	.27 h.	Monsanto
<input type="checkbox"/> MAN-4	.19 h.	Monsanto
<input type="checkbox"/> 707*	.33 h.	Litronix
<input type="checkbox"/> 704**	.33 h.	Litronix
<input type="checkbox"/> SLA-1*	.33 h.	Opcoa

Pin-for-pin MAN-1, ** Pin-for-pin MAN-4, elec. char. same



METAL-ENCASED

\$3.50
3 for \$9

6.3 VOLT 3 AMP
Heavy-duty, 110VAC to at 3 amps filament transformer. 3 x 2 1/2 2 1/2 With color-coded wires.

SILICON TUBES

<input type="checkbox"/> 5U4	\$1.49
<input type="checkbox"/> 5R4	3.95
<input type="checkbox"/> 866	7.95

HIGH VOLT 1AMP

PIV	SALE
2000*	1.00
3000	1.35
4000	1.65
5000	2.25
6000	2.96
8000	3.50
10000	3.95

SANKEN HYBRID AUDIO POWER AMPS

Mfgr's Type	Watts	Sale
<input type="checkbox"/> SI-1010Y	10	\$ 8.88
<input type="checkbox"/> SI-1025E	25	18.88
<input type="checkbox"/> SI-1050E	50	29.95

Used extensively in hi-fi systems, tape decks, FM tuners, record players, stereo components, musical instruments, P.A., etc. All amplifiers, flat within 1/2 db from hz to 100,000. Each unit properly heat-sinked, with heavy-duty connecting tie lug connections. Single-ended pushpull output. Power supply required 24VDC Output to 8 ohms.

Order by Stock No.

POLY PAKS BLUE RIBBON Policy

20-Years of Business INTEGRITY
20-Years of Prompt SERVICE
20-Years of Money-Back GUARANTEES
20-Years of Economy! LOWEST PRICES!

Terms: add postage Rated: net 30
Phone Orders: Wakefield, Mass. (617) 245-3829
Retail: 16-18 Del Carmine St., Wakefield, Mass. (off Water Street) C.O.D.'S MAY BE PHONED

15¢ CATALOG on Fiber Optics, 'IC's, Semi's, Parts

POLY PAKS

P.O. BOX 942A LYNNFIELD, MASS. 01940

EPOXY FULL WAVE SILICON BRIDGE RECTIFIERS	PIV	2 Amp	6 Amp
<input type="checkbox"/>	50	\$.69	\$.88
<input type="checkbox"/>	100	.79	.99
<input type="checkbox"/>	200	.95	1.25
<input type="checkbox"/>	400	1.19	1.50
<input type="checkbox"/>	600	1.35	1.75
<input type="checkbox"/>	800	1.59	1.95
<input type="checkbox"/>	1000	1.79	2.25

Code: 2 amp TO-5 case
6 Amp 1/2 x 1/2 x 3/16 sq

10-AMP PLASTIC "POWER TAB" SCR'S

PRV	Sale
<input type="checkbox"/> 50	\$.75
<input type="checkbox"/> 100	.95
<input type="checkbox"/> 200	1.25
<input type="checkbox"/> 300	\$1.50
<input type="checkbox"/> 400	1.98
<input type="checkbox"/> 500	2.50




Money-Back GUARANTEE on all items

CALL BOOK 74

When you want an authoritative, up to date directory of licensed radio amateurs

It's the CALLBOOK

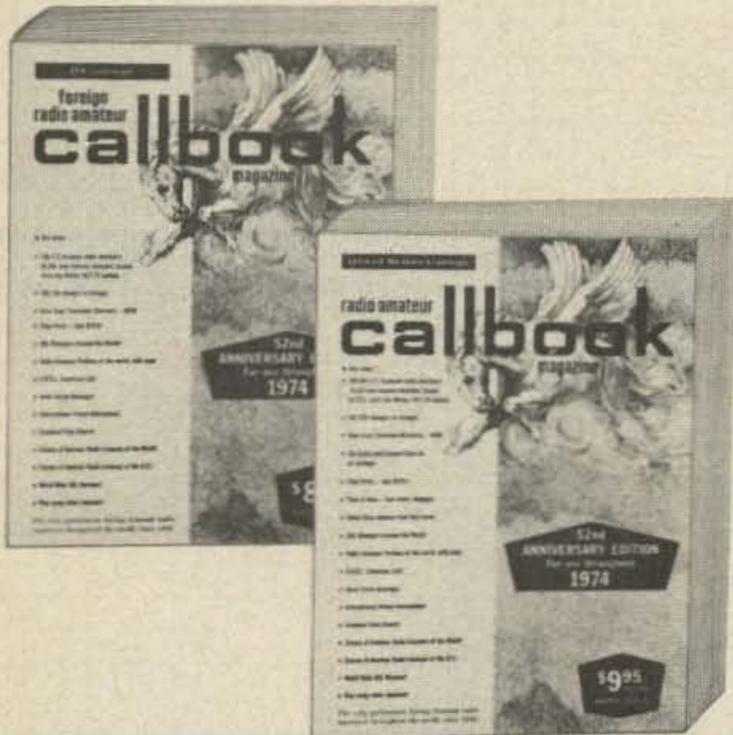Over 210,000 QTH's in the DX edition
DX CALLBOOK for 1974
\$8.95



Over 285,000 QTH's in the U.S. edition
U.S. CALLBOOK for 1974
\$9.95

See your favorite dealer or Send today to
 (Mail orders add 50¢ per CALLBOOK for postage and handling)


WRITE FOR FREE BROCHURE

RADIO AMATEUR



callbook INC.

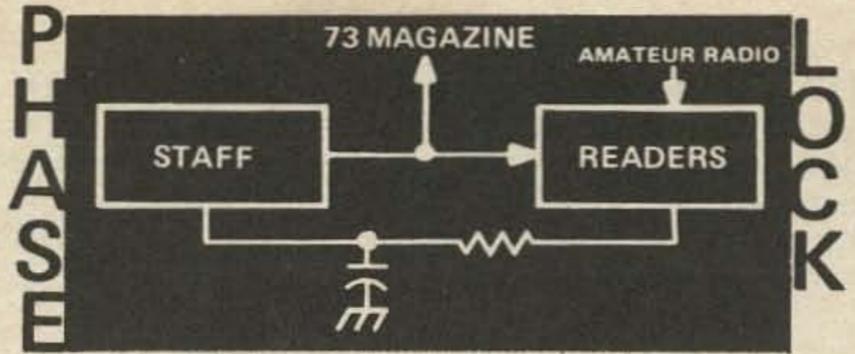Dept. B 925 Sherwood Drive
 Lake Bluff, Ill. 60044



In this issue, do you think there is a need for more

	Yes	No
Simple construction projects	<input type="checkbox"/>	<input type="checkbox"/>
Complex construction projects	<input type="checkbox"/>	<input type="checkbox"/>
General interest articles	<input type="checkbox"/>	<input type="checkbox"/>
Humor articles	<input type="checkbox"/>	<input type="checkbox"/>
Specialized columns	<input type="checkbox"/>	<input type="checkbox"/>
Operating news	<input type="checkbox"/>	<input type="checkbox"/>

Please use the following space for comments on the articles and newspapers in this issue. If you have a specific idea of what you feel would improve 73, please send it to us. If you have two ideas, the space below will probably not be sufficient. Instead of attaching a separate sheet (which would be bulky and awkward), you can vastly simplify the process by buying another copy. This second copy should be kept in a safety deposit box as insurance against fires, floods and thefts by nonsubscribers.

Do you receive 73 from subscription
 newsstand

Fill out this form immediately and mail it with the Reader Service coupon on the reverse side (or vice versa).

READER SERVICE

Please either tear out this list of advertisers and send it in to 73 with as many boxes checked off as you would like to see brochures, data sheets or catalogs. . . or else make a copy and send that in. Include your zip code, please. Send money directly to advertisers.

ADVERTISER INDEX

- | | |
|---|---|
| <input type="checkbox"/> ADVA Elec 19 | <input type="checkbox"/> Janel 54 |
| <input type="checkbox"/> Amateur Wholesale 97 | <input type="checkbox"/> K A Elec 99 |
| <input type="checkbox"/> Andy Elec 54 82 | <input type="checkbox"/> Keeps-It-Kit 60 |
| <input type="checkbox"/> ANTECH 79 | <input type="checkbox"/> K Enterprises 40 |
| <input type="checkbox"/> Arnold's Engraving 60 | <input type="checkbox"/> Meshna 108, 109 |
| * <input type="checkbox"/> ATV Research 82 | <input type="checkbox"/> MFJ 64 |
| <input type="checkbox"/> Babylon 102 | <input type="checkbox"/> Nasem 57 |
| <input type="checkbox"/> Columbia 82 | <input type="checkbox"/> Newtronics CII |
| <input type="checkbox"/> Comm Spec 60 | <input type="checkbox"/> Nurmi 24 |
| <input type="checkbox"/> Comm Unlimited 98, 104 | <input type="checkbox"/> Palomar 53 |
| <input type="checkbox"/> Continental Spec 44 | <input type="checkbox"/> Poly Paks 110 |
| <input type="checkbox"/> Cornell 52 | <input type="checkbox"/> Radio Amateur Callbook 111 |
| <input type="checkbox"/> ECM 40 | <input type="checkbox"/> RGS 107 |
| <input type="checkbox"/> Elec Dist 76 | <input type="checkbox"/> Rohn 25 |
| <input type="checkbox"/> Emergency Beacon 18 | <input type="checkbox"/> Scelbi 52 |
| <input type="checkbox"/> Erickson 65 | <input type="checkbox"/> Selectronics 103 |
| <input type="checkbox"/> Fair 36 | <input type="checkbox"/> Sentry 11 |
| <input type="checkbox"/> Freck 56 | <input type="checkbox"/> Slep 36 |
| <input type="checkbox"/> Gam | <input type="checkbox"/> Solid State 106 |
| <input type="checkbox"/> Gateway 28 | <input type="checkbox"/> Space Elec 54, 71 |
| <input type="checkbox"/> GENAVE 41 | <input type="checkbox"/> Stahler 36 |
| <input type="checkbox"/> Godbout 68 | <input type="checkbox"/> Tech Doc 22 |
| <input type="checkbox"/> Greene 64 | <input type="checkbox"/> Tri Tek 56 |
| <input type="checkbox"/> Hal 43, 58 | <input type="checkbox"/> Trumbull 52 |
| <input type="checkbox"/> Ham Radio Center 48 | <input type="checkbox"/> VHF Eng 101 |
| <input type="checkbox"/> Henry 21, 50 | <input type="checkbox"/> WEIRNU 34 |
| <input type="checkbox"/> HY-GAIN 100, 105 | <input type="checkbox"/> Wilson 5 |
| <input type="checkbox"/> ICOM 29 | <input type="checkbox"/> Wolf 64 |
| <input type="checkbox"/> Inter Telecomm 32 | <input type="checkbox"/> World QSL 64 |
| <input type="checkbox"/> Jan 53 | <input type="checkbox"/> Yaesu CIV |

73 STUFF
 QSLs CII
 Hotline 74
 Books 86
 Subs 89

NEWSSTAND SUBSCRIPTION

*Reader service inquiries not solicited. Correspond directly to company.

JULY 1974

Reader's Service
 73 Inc., Peterborough NH 03458
 Please Print or Type

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

Coupon expires in 60 days

PROPAGATION CHART

J.H. Nelson

Good (open) Fair (□) Poor (O)

July 1974						
Sun	Mon	Tue	Wed	Thu	Fri	Sat
	1	2	3	4	5	6
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30	31			

EASTERN UNITED STATES TO:

	GMT: 00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	7A	14	7	7	7	7	7	7	7	7	7	7
ARGENTINA	14	14	14	7	7	7	14	14	14	14	14	14
AUSTRALIA	14	14	14B	7B	7	7	7	7	7	7	14	14
CANAL ZONE	14	14	7A	7	7	7	7	14	14	14	14	14
ENGLAND	7A	7	7	7	7	7	7A	14	14	14	14	14
HAWAII	14	14	7A	7	7	7	7	7	7A	14	14	14
INDIA	7	7	7B	7B	7B	7B	7	7	7A	14	14	14
JAPAN	14	14	7	7	7	7	7	7	7	7	7	14
MEXICO	14	14	7	7	7	7	7	7	7	14	14	14
PHILIPPINES	14	14	7B	7B	7B	7B	7B	7	7	7	7A	7A
PUERTO RICO	14	7	7	7	7	7	7	7	14	14	14	14
SOUTH AFRICA	7B	7	7	7	7B	14	14	14	14	14	7B	7B
U. S. S. R.	7	7	7	7	7	7	14	14	14	14	14	14
WEST COAST	14	14	14	7	7	7	7	14	14	14	14	14

CENTRAL UNITED STATES TO:

ALASKA	14	14	14	7	7	7	7	7	7	7	7	14
ARGENTINA	14	14	14	7A	7	7	7	14	14	14	14	14
AUSTRALIA	14	14	14	14	7	7	7	7	7	7	14	14
CANAL ZONE	14	14	14	7	7	7	7	14	14	14	14	14
ENGLAND	7	7	7	7	7	7	7	7	7	14	14	14
HAWAII	14	14	14	7	7	7	7	7	7A	14	14	14
INDIA	14	7	7B	7B	7B	7B	7	7	7	7A	7A	7A
JAPAN	14	14	14	7	7	7	7	7	7	7	7	14
MEXICO	14	7	7	7	7	3A	7	7	7	7	14	14
PHILIPPINES	14	14	14	7B	7B	7B	7B	7	7	7	7A	7A
PUERTO RICO	14	14	7	7	7	7	7	14	14	14	14	14
SOUTH AFRICA	7B	7	7	7	7B	7B	14	14	14	14	7B	7B
U. S. S. R.	7	7	7	7	7	7	7	7	7	7A	14	14

WESTERN UNITED STATES TO:

ALASKA	7A	7A	7A	7	7	7	7	7	7	7	7	7A
ARGENTINA	14	14	14	7A	7	7	7	14	14	14	14	14
AUSTRALIA	14	14A	14	14	7A	7	7	7	7	7	14	14
CANAL ZONE	14	14	14	7	7	7	7	14	14	14	14	14
ENGLAND	7A	7	7	7	7	7	7	7	7	7A	7A	14
HAWAII	14	14	14A	14	14	7	7	7	7	14	14	14
INDIA	14	14	14	7B	7B	7B	7	7	7	7	7	7A
JAPAN	14	14	14	14	7	7	7	7	7	7	14	14
MEXICO	14	14	14	7	7	7	7	7	14	14	14	14
PHILIPPINES	14	14	14	14	7	7	7	7	7	14	14	14
PUERTO RICO	14	14	7A	7	7	7	7	14	14	14	14	14
SOUTH AFRICA	7B	7B	7	7	7B	7B	7B	7B	14	14	7B	7B
U. S. S. R.	7	7	7	7	7	7	7	7	7	7A	7A	7
EAST COAST	14	14	14	7	7	7	7	14	14	14	14	14

A = Next higher frequency may be useful also.
 B = Difficult circuit this period.

ADVANCED
AMATEUR
TECHNOLOGY from



YAESU

YOUR ASSURANCE OF PERFORMANCE
AND QUALITY

JOIN THE ACTION ON 2M FM

THE WORLD'S LEADER IN AMATEUR COMMUNICATIONS
NOW OFFERS YOU "TOTAL SPECTRUM COVERAGE"
FROM 160 THROUGH 2 METERS



SIGMASIZER 200R

200 CHANNEL

SYNTHESIZED 2M FM TRANSCEIVER

*NO CRYSTALS TO BUY. GET TOTAL REPEATER
AND SIMPLEX OPERATION OVER THE ENTIRE
FM BAND

*FEATURES

- Complete 146-148 MHz coverage
- 200 channels in 10 KHz increments
- Selectable ± 600 KHz repeater offset
- Built-in repeater tone burst
- Selectable repeater or simplex operation
- Priority channel provision
- Automatic final protection
- Plus many more exciting features

Amateur Net \$449

Available soon from your dealer



FT-2 AUTO

AUTO-SCAN WITH PRIORITY CHANNEL
2M FM TRANSCEIVER

*AUTOMATIC SCANNING ALLOWS YOU TO
CONTINUOUSLY MONITOR ALL OF YOUR
FAVORITE CHANNELS

*FEATURES

- Automatic scan of all 8 channels
- Hi/Low power: 10 Watts or 1 Watt
- Selectable scan of priority channel
- Individual channel lockout
- Automatic channel lock with mike
- Built-in AC & DC power supplies
- Built-in repeater tone burst
- Complete with three channels,
cables, and microphone

Amateur Net \$379

COMING SOON!

NEW FT-224 23 CHANNEL 2M FM TRANSCEIVER
WITH PRIORITY CHANNEL FEATURE

Watch for price announcement and further information on this new, low cost FM Radio

Prices and specifications subject to change without notice

Full dealer warranty with factory service available for continued after warranty service backup

For further information on these, the complete Yaesu line, and a current dealer list, write:



YAESU MUSEN USA INC.

7625 E. Rosecrans Ave., Unit #29, Paramount, CA. 90723
(213) 633-4007