Chapter 18

RF Power Amplifiers

This chapter describes the design and construction of power RF amplifiers for use in an Amateur Radio station. Dick Ehrhorn, WØID (ex-W4ETO), contributed materially to this section.

An amplifier may be required to develop as much as 1500 W of RF output power, the legal maximum in the United States.

YOU CAN BE KILLED by coming in contact with the high voltages inside a

commercial or homebrew RF amplifier. Please don't take foolish chances. Remember that you CANNOT GO WRONG by treating each amplifier as potentially lethal! For a more thorough treatment of this all-important subject, please review the applicable sections of the *Safety* chapter in this *Handbook*.

Every component in an RF power amplifier must be carefully selected to endure high electrical stress levels without failing. Large amounts of heat are produced in the amplifier and must be dissipated safely. Generation of spurious signals must be minimized, not only for legal reasons, but also to preserve good neighborhood relationships. Every one of these challenges must be overcome to produce a loud, clean signal from a safe and reliable amplifier.

Types of Power Amplifiers

Power amplifiers are categorized by their power level, intended frequencies of operation, device type, class of operation and circuit configuration. Within each of these categories there are almost always two or more options available. Choosing the most appropriate set of options from all those available is the fundamental concept of design.

SOLID STATE VERSUS VACUUM TUBES

With the exception of high-power amplifiers, nearly all items of amateur equipment manufactured commercially today use solid-state (semiconductor) devices exclusively. Semiconductor diodes, transistors and integrated circuits (ICs) offer several advantages in designing and fabricating equipment:

- Compact design—Even with their heat sinks, solid-state devices are smaller than functionally equivalent tubes, allowing smaller packages.
- No-tune-up operation—By their nature,

transistors and ICs lend themselves to low impedance, broadband operation. Fixed-tuned filters made with readily available components can be used to suppress harmonics and other spurious signals. Bandswitching of such filters is easily accomplished when necessary; it often is done using solid-state switches. Tube amplifiers, on the other hand, usually must be retuned on each band, and even for significant frequency movement within a band.

- Long life—Transistors and other semiconductor devices have extremely long lives if properly used and cooled. When employed in properly designed equipment, they should last for the entire useful life of the equipment—commonly 100,000 hours or more. Vacuum tubes wear out as their filaments (and sometimes other parts) deteriorate with time in normal operation; the useful life of a typical vacuum tube may be on the order of 10,000 to 20,000 hours.
- Manufacturing ease-Most solid-state

devices are ideally suited for printedcircuit-board fabrication. The low voltages and low impedances that typify transistor and IC circuitry work very well on printed circuits (some circuits use the circuit board traces themselves as circuit elements); the high impedances found with vacuum tubes do not. The IC or transistor's physical size and shape also lends itself well to printed circuits and the devices usually can be soldered right to the board.

These advantages in fabrication mean reduced manufacturing costs. Based on all these facts, it might seem that there would be no place for vacuum tubes in a solidstate world. Transistors and ICs do have significant limitations, however, especially in a practical sense. Individual RF power transistors available today cannot develop more than approximately 150 W output; this figure has not changed much in the past two decades.

Individual present-day transistors cannot generally handle the combination of current and voltage needed, nor can they safely dispose of the amount of heat dissipated, for RF amplification to higher power levels. So pairs of transistors, or even pairs of pairs, are usually employed in practical power amplifier designs, even at the 100-W level. Beyond the 300-W output level, somewhat exotic (at least for most radio amateurs) techniques of power combination from multiple amplifiers ordinarily must be used. Although this is commonly done in commercial equipment, it is an expensive proposition.

It also is far easier to ensure safe cooling of vacuum tubes, which operate satisfactorily at surface temperatures as high as 150-200°C and may be cooled by simply blowing sufficient ambient air past or through their relative large cooling surfaces. The very small cooling surfaces of power transistors should be held to 75-100°C to avoid drastically shortening their life expectancy. Thus, assuming worstcase 50°C ambient air temperature, the large cooling surface of a vacuum tube can be allowed to rise 100-150°C above ambient, while the small surface of a transistor must not be allowed to rise more than about 50°C. Moreover, power tubes are considerably more likely than transistors to survive, without significant damage, the rare instance of severe overheating.

Furthermore, RF power transistors are much less tolerant of electrical abuse than



Fig 18.1—Amplifying device output current for various classes of operation. All assume a sinusoidal drive signal.

are most vacuum tubes. An overvoltage spike lasting only microseconds can—and is likely to—destroy transistors costing \$75 to \$150 each. A comparable spike is unlikely to have any effect on a tube. So the important message is this: designing with expensive RF power transistors demands using extreme caution to ensure that adequate thermal and electrical protection is provided. It is an area best left to knowledgeable designers.

Even if one ignores the challenge of the RF portions of a high-power transistor amplifier, there is the dc power supply to consider. A solid-state amplifier capable of delivering 1 kW of RF output might require regulated (and transient-free) 50 V at more than 40 A. Developing that much current is a challenging and expensive task. These limitations considered, solid-state amplifiers have significant practical advantages up to a couple of hundred watts output. Beyond that point, and certainly at the kilowatt level, the vacuum tube still reigns for amateur constructors because of its cost-effectiveness and ease of equipment design.

CLASSES OF OPERATION

The class of operation of an amplifier stage is defined by its conduction angle, the angular portion of each RF drive cycle, in degrees, during which plate current (or collector or drain current in the case of transistors) flows. This, in turn, determines the amplifier's gain, efficiency, linearity and input and output impedances.

- Class A: The conduction angle is 360°. DC bias and RF drive level are set so that the device is not driven to output current cutoff at any point in the driving-voltage cycle, so some device output current flows throughout the complete 360° of the cycle (see Fig 18.1A). Output voltage is generated by the variation of output current flowing through the load resistance. Maximum linearity and gain are achieved in a Class A amplifier, but the efficiency of the stage is low. Maximum theoretical efficiency is 50%, but 25 to 30% is more common in practice.
- Class AB: The conduction angle is greater than 180° but less than 360° (see Fig 18.1B). In other words, dc bias and drive level are adjusted so device output current flows during appreciably more than half the drive cycle, but less than the whole drive cycle. Efficiency is much better than Class A, typically reaching 50-60% at peak output power. Class AB linearity and gain are not as good as that achieved in Class A, but are very acceptable for even the most rigorous high-power SSB applications

in Amateur Radio.

Class AB vacuum tube amplifiers are further defined as class AB1 or AB2. In class AB1, the grid is not driven positive so no grid current flows. Virtually no drive power is required, and gain is quite high, typically 15-20 dB. The load on the driving stage is relatively constant throughout the RF cycle. Efficiency typically exceeds 50% at maximum output.

In Class AB2, the grid is driven positive on peaks and some grid current flows. Efficiency commonly reaches 60%, at the expense of greater demands placed on the driving stage and slightly reduced linearity. Gain commonly reaches 15 dB.

- Class B: Conduction angle = 180°. Bias and RF drive are set so that the device is just cut off with no signal applied (see Fig 18.1C), and device output current flows during one half of the drive cycle. Efficiency commonly reaches as high as 65%, with fully acceptable linearity.
- Class C: The conduction angle is much less than 180°-typically 90°. DC bias is adjusted so that the device is cut off when no drive signal is applied. Output current flows only during positive crests in the drive cycle (see Fig 18.1D), so it consists of pulses at the drive frequency. Efficiency is relatively highup to 80%-but linearity is extremely poor. Thus Class C amplifiers are not suitable for amplification of amplitudemodulated signals such as SSB or AM, but are quite satisfactory for use in onoff keyed stages or with frequency or phase modulation. Gain is lower than for the previous classes of operation, typically 10-13 dB.
- Classes D through H use various switched mode techniques and are not commonly found in amateur service. Their prime virtue is high efficiency, and they are used in a wide range of specialized audio and RF applications to reduce power-supply requirements and dissipated heat. These classes of RF amplifiers require fairly sophisticated design and adjustment techniques, particularly at high-power levels. The additional complexity and cost could rarely if ever be justified for amateur service.

Class of operation is independent of device type and circuit configuration (see **Electrical Signals and Components** chapter). The active amplifying device and the circuit itself must be uniquely applied for each operating class, but amplifier linearity and efficiency are determined by the class of operation. Clever amplifier design cannot improve on these fundamental limits. Poor design and implementation, though, can certainly prevent an amplifier from approaching its potential in efficiency and linearity.

MODELING THE ACTIVE DEVICE

It is very useful to have a model for the active devices used in a real-world RF power amplifier. Although the actual active device used in an amplifier might be a vacuum tube, a transistor or an FET, each model has certain common characteristics.

See **Fig 18.2A**, where a vacuum tube is modeled as a current generator in parallel with a dynamic plate resistance Rp and a load resistance RL. In this simplified model, any residual reactances (such as the inductance of connecting leads and the output capacity of the tube) are not specifically shown. The control-grid voltage in a vacuum tube controls the stream of electrons moving between the cathode and the plate. An important measure for a tube is its transconductance, which is the change in plate current caused by a change in gridcathode voltage. The plate current is:

$$i_p = g_m \times e_g$$

where

 $i_p = plate current$

 g_m = transconductance (also called mutual conductance) of tube $\Delta i_p / \Delta e_g$ e_{σ} = grid RF voltage.



Fig 18.2—At A, the current-generator model for a vacuum-tube amplifier operating linearly. Typical values for R_p and R_L for small-signal vacuum tubes are 100 k Ω and 5 k Ω respectively. The plate current I_p is equal to the product of the tube tranconductance g_m times the grid voltage. At B, the current-generator model for a transistor. Typical values for R_c and R_L are on the same order as those for a small-signal vacuum tube.

The concept of dynamic plate resistance is sometimes misunderstood. It is a measure of how the plate current changes with a change in plate voltage, given a constant grid voltage. The control-grid voltage is by far the major determinant of the plate current in a triode. In a tetrode or pentode vacuum tube, the screen grid "screens" the plate current even further from the effect of changes in the plate voltage. For smallsignal operation (where the plate voltage does not swing below the screen voltage) the plate current in a pentode or tetrode changes remarkably little when the plate voltage is changed. Thus the dynamic plate resistance is very high in a tetrode or pentode that is operating linearly, and only somewhat less for a triode. The plate current delivered into the load resistance R_L creates RF power.

An FET operates much like the vacuumtube model. Obviously, there is no vacuum inside the case of an FET, and the FET electrodes are called gate, drain and source instead of grid, plate and cathode, but the current-generator model is just as viable for an FET as for a vacuum tube. In a transistor, the base current controls the flows of electrons (or holes) in the collector circuit. See Fig 18.2B. A transistor operating in a linear fashion resembles the operation of a tetrode or pentode vacuum tube since the equivalent collector dynamic output resistance is also high. This is so because the collector current is not affected greatly by the collector voltage-it is mainly determined by the base current. The collector current in the current-generator model for a transistor is:

$$i_{c} = \beta \times i_{b} \tag{2}$$

where

(1)

 $i_c = collector current$

 β = current gain of transistor

 $i_b = base current.$

IMPEDANCE TRANSFORMATION— "MATCHING NETWORKS"

Over the years, some confusion in the amateur ranks has resulted from imprecise use of the terms *matching* and *matching network*. The term "matching" was first used in the technical literature in connection with transmission lines. When a matching network such as an antenna tuner is tuned properly, it "matches" (that is, makes equal) a particular load impedance to the fixed characteristic impedance of the transmission line used at the tuner input.

In this chapter, we are concerned with using active devices to generate useful RF power. For a given active device, RF power is generated most efficiently, and with the least distortion for a linear amplifier, when it delivers RF current into an *optimum value of load resistance*. For an amplifier, the output network transforms the load impedance (such as an antenna) into an optimum value of load resistance for the active device. In part to differentiate active power amplifiers from passive transmission lines, we prefer to call such a transforming network an *output network*, rather than a matching network.

Output Networks and Class AB, B and C Amplifiers

In Class AB, B and C amplifiers, we select a load resistance that will keep the tube or transistor from dissipating too much power or, in the case of Class AB or B amplifiers, to achieve the desired linearity. In these classes of amplifiers, the device output current is zero for large parts of the RF cycle. Because of this, the effective source resistance is no longer the simple dynamic plate resistance of a Class A amplifier. In fact, the value of R_p varies with the drive level. This means that, since the load resistance (of an antenna, for example) is constant, the efficiency of the amplifier also varies with the drive level.

It may at first appear contradictory that Class AB and B amplifiers use nonlinear devices but achieve "linear" operation nevertheless. The explanation is that the peak amplitude of device output current faithfully follows that of the drive voltage, even though its waveform does not. In tuned amplifiers, the flywheel effect of the resonant output network restores the missing part of each RF input cycle, as well as its sinusoidal waveform. In broadband transistor amplifiers, balanced push-pull circuitry commonly is used to restore the missing RF cycles, and low-pass filters on the output remove harmonics and thereby restore the sinusoidal RF waveform. The result in both cases is linear amplification of the input signal-by the clever application of nonlinear devices.

The usual practice in RF power amplifier design is to select an optimum load resistance that will provide the highest power output consistent with required linearity, while staying within the amplifying device's ratings. The optimum load resistance is determined by the amplifying device's current transfer characteristics and the amplifier's class of operation. For a transistor amplifier, the optimum load resistance is approximately:

$$R_{\rm L} = \frac{V_{\rm CC}^2}{2P_{\rm O}}$$
(3)

where

 $R_{\rm L}$ = the load resistance

$$V_{CC}$$
 = the collector dc voltage

$$P_O$$
 = the amplifier power output in watts.

Vacuum tubes have complex current transfer characteristics, and each class of operation produces different RMS values of RF current through the load impedance. The optimum load resistance for vacuumtube amplifiers can be approximated by the ratio of the dc plate voltage to the dc plate current at maximum signal, divided by a constant appropriate to each class of operation. The load resistance, in turn, determines the maximum power output and efficiency the amplifier can provide. The optimum tube load resistance is

$$R_{L} = \frac{V_{P}}{K \times I_{P}}$$
(4)

where

- R_L = the appropriate load resistance, in ohms
- V_P = the dc plate potential, in V
- I_P = the dc plate current, in A
- K = a constant that approximates the RMS current to dc current ratio appropriate for each class. For the different classes of operation:

Class A, $K \approx 1.3$ Class AB, $K \approx 1.5 - 1.7$ Class B, $K \approx 1.57 - 1.8$ Class C, $K \approx 2$.

Graphical or computer-based analytical methods may be used to calculate more precisely the optimum plate load resistance for specific tubes and operating conditions, but the above "rules of thumb" generally provide satisfactory results for design.

The ultimate load for an RF power amplifier usually is a transmission line connected to an antenna or the input of another amplifier. It usually isn't practical, or even possible, to modify either of these load impedances to the optimum value needed for high-efficiency operation. An output network is thus used to transform the real load impedance to the optimum load resistance for the amplifying device. Two basic types of output networks are found in RF power amplifiers: tank circuits and transformers.

TANK CIRCUITS

Parallel-resonant circuits and their equivalents have the ability to store energy. Capacitors store electrical energy in the electric field between their plates; inductors store energy in the magnetic field induced by the coil winding. These circuits are referred to as tank circuits, since they act as storage "tanks" for RF energy.

The energy stored in the individual tank circuit components varies with time. Consider for example the tank circuit shown in Fig 18.3. Assuming that R is zero, the tank circuit dissipates no power. Therefore, no power need be supplied by the source; hence no line current I_{LINE} flows. Only circulating current I_{CIRC} flows, and it is exactly the same through both L and C at any instant. Similarly, the voltage across L and C is always exactly the same. At some point the capacitor is fully charged, and the current through both the capacitor and inductor is zero. So the inductor has no magnetic field and therefore no energy stored in its field. All the energy in the tank is stored in the capacitor's electric field.

At this instant, the capacitor starts to discharge through the inductor. The current flowing in the inductor creates a magnetic field, and energy transferred from the capacitor is stored in the inductor's magnetic field. Still assuming there is no loss in the tank circuit, the increase in energy stored in the inductor's magnetic field is exactly equal to the decrease in energy stored in the capacitor's electric field. The total energy stored in the tank circuit stays constant; some is stored in the inductor. some in the capacitor. Current flow into the inductor is a function of both time and of the voltage applied by the capacitor, which decreases with time as it discharges into the inductor. Eventually, the capacitor's charge is totally depleted and all the tank circuit's energy is stored in the magnetic field of the inductor. At this instant, current flow through L and C is maximum and the voltage across the terminals of both L and C is zero.

Since energy no longer is being transferred to the inductor, its magnetic field begins to collapse and becomes a source of



Fig 18.3—There are two currents in a tank circuit: the line current (I_{LINE}) and the circulating current (I_{CIRC}). The circulating current is dependent on tank Q.

current, still flowing in the same direction as when the inductor was being driven by the capacitor. When the inductor becomes a current source, the voltage across its terminals reverses and it begins to recharge the capacitor, with opposite polarity from its previous condition. Eventually, all energy stored in the inductor's magnetic field is depleted as current decreases to zero. The capacitor is fully charged, and all the energy is then stored in the capacitor's electric field. The exchange of energy from capacitor to inductor and back to capacitor is then repeated, but with opposite voltage polarities and direction of current flow from the previous exchange. It can be shown mathematically that the "alternating" current and voltage produced by this process are sinusoidal in waveform, with a frequency of

$$f = \frac{1}{2\pi\sqrt{LC}}$$
(5)

which of course is the resonant frequency of the tank circuit. In the absence of a load or any losses to dissipate tank energy, the tank circuit current would oscillate forever.

In a typical tank circuit such as shown in Fig 18.3, the values for L and C are chosen so that the reactance (X_I) of L is equal to the reactance (X_C) of C at the frequency of the signal generated by the ac voltage source. If R is zero (since X_{I} is equal to X_C), the line current I_{LINE} measured by M1 is close to zero. However, the circulating current in the loop made up of L, R and C is definitely not zero. Examine what would happen if the circuit were suddenly broken at points A and B. The circuit is now made up of L, C and R, all in series. X_L is equal to X_C , so the circuit is resonant. If some voltage is applied between points A and B, the magnitude of circulating current is limited only by resistance R. If R were equal to zero, the circulating current would be infinite!

THE FLYWHEEL EFFECT

A tank circuit can be likened to a flywheel—a mechanical device for storing energy. The energy in a flywheel is stored in the angular momentum of the wheel. As soon as a load of some sort is attached, the wheel starts to slow or even stop. Some of the energy stored in the spinning flywheel is now transferred to the load. In order to keep the flywheel turning at a constant speed, the energy drained by the load must be replenished. Energy has to be added to the flywheel from some external source. If sufficient energy is added to the flywheel, it maintains its constant rotational speed.

In the real world, of course, flywheels

and tank circuits suffer from the same fate; system losses dissipate some of the stored energy without performing any useful work. Air resistance and bearing friction slow the flywheel. In a tank circuit, resistive losses drain energy.

TANK CIRCUIT Q

In order to quantify the ability of a tank circuit to store energy, a quality factor, Q, is defined. Q is the ratio of energy stored in a system during one complete RF cycle to energy lost.

$$Q = 2\pi \frac{W_S}{W_L}$$
(6)

where

$$W_{S}$$
 = is the energy stored

 W_L = the energy lost to heat and the load.

By algebraic substitution and appropriate integration, the Q for a tank circuit can be expressed as

$$Q = \frac{X}{R}$$
(7)

where

X = the reactance of either the inductor or the capacitor

R = the series resistance.

Since both circulating current and Q are proportional to 1/R, circulating current is therefore proportional to Q. The tank circulating current is equal to the line current multiplied by Q. If the line current is 100 mA and the tank Q is 10, then the circulating current through the tank is 1 A. (This implies, according to Ohm's Law, that the voltage potentials across the components in a tank circuit also are proportional to Q.)

When there is no load connected to the tank, the only resistances contributing to R are the losses in the tank circuit. The unloaded Q (Q_{U}) in that case is:

$$Q_{\rm U} = \frac{X}{R_{\rm Loss}} \tag{8}$$

where

X = the reactance of either the inductor or capacitor

R_{Loss} = the effective series loss resistance in the circuit.

A load connected to a tank circuit has exactly the same effect on tank operation as circuit losses. Both consume energy. It just happens that energy consumed by circuit losses becomes heat rather than useful output. When energy is coupled out of the tank circuit into a load, the loaded Q (Q_L) is:

$$Q_{L} = \frac{X}{R_{Loss} + R_{Load}}$$
(9)

where R_{Load} is the load resistance. Energy dissipated in R_{Loss} is wasted as heat. Ideally, all the tank circuit energy should be delivered to R_{Load} . This implies that R_{Loss} should be as small as practical, to yield the highest reasonable value of unloaded Q.

TANK CIRCUIT EFFICIENCY

The efficiency of a tank circuit is the ratio of power delivered to the load resistance (R_{Load}) to the total power dissipated by losses (R_{Load} and R_{Loss}) in the tank circuit. Within the tank circuit, R_{Load} and R_{Loss} are effectively in series, and the circulating current flows through both. The power dissipated by each is therefore proportional to its resistance. The loaded tank efficiency can therefore be defined as

Tank Efficiency =
$$\frac{R_{\text{Load}}}{R_{\text{Load}} + R_{\text{Loss}}} \times 100$$
(10)

where efficiency is stated as a percentage. By algebraic substitution, the loaded tank efficiency can also be expressed as

Tank Efficiency =
$$\left(1 - \frac{Q_L}{Q_U}\right) \times 100$$
 (11)

where

 Q_L = the tank circuit loaded Q Q_U = the unloaded Q of the tank circuit.

It follows then that tank efficiency can

be maximized by keeping Q_L low, which keeps the circulating current low and the I²R losses down. Q_U should be maximized for best efficiency; this means keeping the circuit losses low.

The selectivity provided by a tank circuit helps suppress harmonic currents generated by the amplifier. The amount of harmonic suppression is dependent upon circuit loaded Q_L, so a dilemma exists for the amplifier designer. A low Q_L is desirable for best tank efficiency, but yields poorer harmonic suppression. High QL keeps amplifier harmonic levels lower at the expense of some tank efficiency. At HF, a compromise value of Q_L can usually be chosen such that tank efficiency remains high and harmonic suppression is also reasonable. At higher frequencies, tank Q_L is not always readily controllable, due to unavoidable stray reactances in the circuit. However, unloaded Q_U can always be maximized, regardless of frequency, by keeping circuit losses low.

TANK OUTPUT CIRCUITS

Tank circuit output networks need not

take the form of a capacitor connected in parallel with an inductor. A number of equivalent circuits can be used to match the impedances normally encountered in a power amplifier. Most are operationally more flexible than a parallel-resonant tank. Each has its advantages and disadvantages for specific applications, but the final choice usually is based on practical construction considerations and the component values needed to implement a particular network. Some networks may require unreasonably high or low inductance or capacitance values. In that case, use another network, or a different value of Q_L. Several different networks may be investigated before an acceptable final design is reached.

The impedances of RF components and amplifying devices frequently are given in terms of a parallel combination of a resistance and a reactance, although it is often easier to use a series R-X combination to design networks. Fortunately, there is a series impedance equivalent to every parallel impedance and vice versa. The equivalent circuits, and equations for conversion from one to the other, are given in **Fig 18.4**. In order to use most readily available design equations for computing matching networks, the parallel impedance must first be converted to its equivalent series form.

The Q_L of a parallel impedance can be derived from the series form as well. Substitution of the usual formula for calculating Q_L into the equations from Fig 18.4 gives

$$Q_{L} = \frac{R_{P}}{X_{P}}$$
(12)

where

 $R_{\rm P}$ = the parallel equivalent resistance



Fig 18.4—Parallel and series equivalent circuits and the formulas used for conversion.

 X_{P} = the parallel equivalent reactance. Several impedance-matching networks are shown in the Receivers and Transmitters chapter. A low-pass T network and two low-pass L networks are possible matching networks. Both types of matching networks provide good harmonic suppression. The pi network is also commonly used for amplifier matching. Harmonic suppression of a pi network is a function of the impedance transformation ratio and the QL of the circuit. Secondharmonic attenuation is approximately 35 dB for a load impedance of 2000 Ω in a pi network with a $\ensuremath{Q_{\mathrm{L}}}$ of 10. The third harmonic is typically 10 dB lower and the fourth approximately 7 dB below that. A typical pi network as used in the output circuit of a tube amplifier is shown in Fig 18.5.

You can calculate Pi-network matching-circuit values using the following equations. These equations are from Elmer (W5FD) Wingfield's August 1983 QST article, "New and Improved Formulas for the Design of Pi and Pi-L Networks," and Feedback in January 1984 QST. (See the Bibliography at the end of this chapter.) Table 18.1 shows some data from a computer program Wingfield wrote to calculate these values. This program (PI-CMIN.EXE) and a similar program to calculate Pi-L network values (PI-LCMIN.EXE) are available from ARRLWeb (see page viii), along with several other useful Wingfield programs. The programs are for IBM PC and compatible computers. A more complete set of tables is also available from ARRL as a template package. See the Component Data and References chapter for ordering information.

The computer programs take into account the minimum practical capacitance (C_{min}) you can expect to achieve with your circuit, based on your knowledge of the tube output capacitance, stray circuit capacitance, the minimum capacitance of the variable tuning capacitors and a reasonable amount of capacitance for tuning. (Start with a minimum capacitance of about 35 pF for vacuum variable capacitors and about 45 to 50 pF for air variable capacitors.)

If the following equations lead to a capacitor value less than the minimum capacitance you expect to achieve, use the minimum value to recalculate the other quantities as shown in the Q_1 Based Pi-Network Equations. This will result in a final circuit operating Q value that is larger than the selected value. (Wingfield uses Q_0 to represent this output Q, which is the same as Q_L referred to earlier in this chapter. We will use Q_0 in the equations.)



Fig 18.5—A pi matching network used at the output of a tetrode power amplifier. RFC2 is used for protective purposes in the event C_{BLOCK} fails.

(14)

The program output includes this new calculated Q_0 value.

Use the following equations to calculate specific component values for a Pi-network matching circuit. Select the desired circuit operating Q, Q_0 , to satisfy these relationships, depending on whether the load resistance is higher or lower than the transformed resistance presented to the plate:

$$Q_0^2 > \frac{R_1}{R_2} - 1 \text{ and } Q_0^2 > \frac{R_2}{R_1} - 1$$
 (13)

where:

- R₁ is the input resistance to be matched, in ohms
- R₂ is the load (output) resistance to be matched, in ohms.

Calculate the value of the input Q, Q1:

$$Q_1 = \frac{R_1 Q_0 - \sqrt{R_1 R_2 Q_0^2 - (R_1 - R_2)^2}}{R_1 - R_2}$$

We will work through an example as the equations are presented. Let's select $Q_0 = 12$, $R_1 = 1500 \Omega$ and $R2 = 50 \Omega$.

$$Q_1 = \frac{1500 \times 12 - \sqrt{1500 \times 50 \times 12^2 - (1500 - 50)^2}}{1500 - 50}$$

$$Q_1 = \frac{1.80 \times 10^4 - \sqrt{8.6975 \times 10^6}}{1450} = 10.38$$

Next calculate the value of the output Q, Q_2 :

$$Q_2 = Q_0 - Q_1$$
(15)

$$Q2 = 12 - 10.38 = 1.62$$

Now calculate the reactance of the input capacitor, output capacitor and inductor.

$$X_{C1} = \frac{R_1}{Q_1} \tag{16}$$

$$X_{C1} = \frac{1500}{10.38} = 144.5 \,\Omega$$
$$X_{C2} = \frac{R_2}{Q_2}$$
(17)

$$X_{C2} = \frac{50}{1.62} = 30.86 \,\Omega$$
$$X_{L} = \frac{R_{1} Q_{0}}{Q_{1}^{2} + 1}$$
(18)

$$X_{L} = \frac{1500 \times 12}{10.38^{2} + 1} = \frac{1.80 \times 10^{4}}{108.74} = 165.5\,\Omega$$

Finally, calculate the component values:

$$C1 = \frac{1}{2\pi X_{C1}}$$
(19)

where f is in Hz and X_{C1} is in ohms.

For our example, let's find the component values at 3.75 MHz.

$$C1 = \frac{1}{2\pi 3.75 \times 10^{6} \times 144.5} = 294 \text{ pF}$$
$$C2 = \frac{1}{2\pi \text{ f } X_{\text{C2}}}$$
(20)

$$C2 = \frac{1}{2\pi 3.75 \times 10^{6} \times 30.86} = 1375 \,\mathrm{pF}$$
$$L = \frac{X_{L}}{2\pi f}$$
(21)

$$L = \frac{165.5}{2\pi 3.75 \times 10^6} = 7.02\,\mu\text{H}$$

As an alternate method, after selecting the values for Q_0 , R_1 and R_2 , you can use

Table 18.1

Pi-Network Values for Various Plate Impedances (Sample Output from PI-CMIN.EXE by W5FD) C in pF and L in μH

Pi-Net Values

R2=50 Ω,	$\mathbf{Q}_0 =$	12,	C(min)	= 35 pF
----------	------------------	-----	--------	---------

112-0	·• ••, ••,	, — · ~ , ~					
Band	C1	C2	L		Band	C1	C2
R1=1: 160 80 40 30 20	500 ohm 580 294 154 109 78	1 s 2718 1378 721 511 364	13.9 7.0 3.7 2.7 1.86	Q ₀ =12.0	R1=2 160 80 40 30 20	000 ohi 446 226 118 84 60	ms 2284 1158 606 429 306
17 15 12 10	61 52 44 38	285 243 207 179	1.45 1.24 1.06 0.91	$Q_0 = 12.0$ $Q_0 = 12.0$ $Q_0 = 12.0$ $Q_0 = 12.0$ $Q_0 = 12.0$	17 15 12 10	47 40 35 35	239 204 184 193
R1=16	600 ohn	ns			R1=21	00 ohn	ns
160 80 40 30 20 17 15 12 10	547 278 145 103 73 57 49 42 36	2619 1328 695 492 351 274 234 199 172	14.6 7.4 3.9 2.8 1.96 1.53 1.31 1.11 0.96	$Q_0=12.0$ $Q_0=12.0$ $Q_0=12.0$ $Q_0=12.0$ $Q_0=12.0$	160 80 40 30 20 17 15 12 10	427 216 113 80 57 45 38 35 35	2213 1122 587 416 296 232 198 189 199
R1=17	700 ohm	1S	15 /		R1=22	200 ohn	ns
160 80 40 30 20 17 15 12 10	518 263 137 97 69 54 46 39 35	2527 1281 671 475 338 265 226 192 173	15.4 7.8 4.1 2.9 2.06 1.61 1.38 1.17 0.99	$Q_0=12.0$ $Q_0=12.0$ $Q_0=12.0$ $Q_0=12.0$ $Q_0=12.3$	80 40 30 20 17 15 12 10	409 207 109 77 55 45 37 35 35	2145 1088 569 403 287 232 192 197 205
R1=18	800 ohm	ıs			R1=23	00 ohn	ns
160 80 40 30 20 17 15 12 10	491 249 130 92 66 51 44 37 35	2441 1238 648 459 327 256 218 186 180	16.1 8.2 4.3 3.0 2.16 1.69 1.44 1.23 0.99	$Q_0=12.0$ $Q_0=12.0$ $Q_0=12.0$ $Q_0=12.0$ $Q_0=13.0$	160 80 40 30 20 17 15 12 10	392 199 104 74 53 41 35 35 35	2081 1055 552 391 279 218 186 210 211
R1=1 9	900 ohm	1 5 2360	16.9		R1=2 4	00 ohn	ns 2020
80 40 30 20 17 15 12 10	237 124 88 63 49 42 36 35	1197 626 443 316 247 211 180 186	8.6 4.5 3.2 2.26 1.77 1.51 1.29 0.99	$Q_0=12.0$ $Q_0=12.0$ $Q_0=12.0$ $Q_0=12.0$ $Q_0=13.7$	80 40 30 20 17 15 12 10	191 100 71 51 40 35 35 35	1024 536 379 270 212 192 207 216
					R1=2	500 ohr	ns
					160 80 40 30 20	363 184 96 68 49	994 520 368 262

the following equations:

$$X_{L} = \frac{Q_{0}(R_{1} + R_{2}) + 2\sqrt{R_{1}R_{2}(Q_{0}^{2} + 4) - (R_{1} + R_{2})^{2}}}{Q_{0}^{2} + 4}$$
(22)

$$K_{\rm L} = \frac{1.86 \times 10^4 + 2\sqrt{1.11 \times 10^7 - 2.4025 \times 10^6}}{148} = 165.5\,\Omega$$

$$Q_1 = \frac{Q_0 R_1}{X_L} - 1$$
 (23)

$$Q_1 = \sqrt{\frac{12 \times 1500}{165.5} - 1} = 10.38$$

$$Q_2 = Q_0 - Q_1 \tag{24}$$

or

L 17.6 8.9 4.7 3.3 2.36

1.85

1.58

1.29

0.98

18.4 9.3 4.9 3.5

2.46

1.92

1.64

1.30

0.98

19.1 9.7 5.1 3.6 2.56

2.00

1.71

1.29

0.98

19.8

10.1

5.3

3.7

2.65

2.08

1.77

1.30

0.98

20.5

10.4 5.5

3.9

2.75

2.15

1.78

1.30

0.98

21.3

10.8

5.6

4.0

2.85

2.23

1.78

1.29

0.98

205

198

215

222

38

35

35

35

17

15

12

10

Q₀=12.0

Q₀=12.0

Q₀=12.0

Q₀=12.5

 $Q_0 = 14.4$

Q₀=12.0

Q₀=12.0

Q₀=12.0

Q₀=13.0

 $Q_0 = 15.1$

Q₀=12.0 Q₀=12.0

Q₀=12.0

Q₀=13.7

Q₀=15.8

Q₀=12.0

Q₀=12.0

Q₀=12.0 Q₀=12.0

 $Q_0 = 16.5$

Q₀=12.0

Q₀=12.0

Q₀=12.5

 $Q_0 = 14.8$

Q₀=17.2

Q₀=12.0

Q₀=12.0

Q₀=13.0

Q₀=15.5

Q₀=17.9

$$Q_2 = \sqrt{\frac{Q_0 R_2}{X_L} - 1}$$
(25)

$$Q_2 = \sqrt{\frac{12 \times 50}{165.5} - 1} = 1.62$$

Use equations 16 and 17 to calculate the reactances of capacitors C1 and C2. Equations 19, 20 and 21 give the capacitance and inductance values for the pi network.

The *pi-L network* is a combination of a pi network followed by an L network. The pi network transforms the load resistance to an intermediate impedance level called the image impedance. Typically, the image impedance is chosen to be between 300 and 700 Ω . The L section then transforms from the image impedance down to 50 Ω . The output capacitor of the pi network is combined with the input capacitor for the L network, as shown in **Fig 18.6**. The pi-L configuration attenuates harmonics better than a pi network. Second harmonic level for a pi-L network with a Q_L of 10 is approximately 52 dB below the fundamental. The third harmonic is attenuated 65 dB and the fourth harmonic approximately 75 dB.

The following equations help you calculate pi-L matching-network values. Select an image resistance value (R_m) that the L network will supply as a load for the pi network. This value must be between the desired pi-L network input resistance (R_1) and the output load resistance (R_2) . For example, you can use the value given:

$$\mathbf{R}_{\mathrm{m}} = \sqrt{\mathbf{R}_1 \times \mathbf{R}_2} \tag{26}$$



Fig 18.6—The pi-L network uses a pi network to transform the input impedances (R1) to the image impedance (Z_{IMAGE}). An L network transforms Z_{IMAGE} to R2.

0. -

The computer program, PI-LCMIN. EXE, uses 300 Ω for Rm in its calculations. Changing the image resistance results in a different network solution. Use this equation to compute the L network Q value, Q_L:

$$Q_{\rm L} = \sqrt{\frac{R_{\rm m}}{R_2} - 1} \tag{27}$$

We will work through an example, using $R_1 = 1500 \Omega$, $R_2 = 50 \Omega$ and the desired pi-L network output Q, $Q_0 = 12$.

$$Q_{\rm L} = \sqrt{\frac{300}{50} - 1} = 2.24$$

 $X_{P2} = \frac{300}{2.24} = 134 \,\Omega$

network section ($Q_{0\pi}$).

 $Q_{0p} = Q_0 - Q_L$

Use equations 28 and 29 to calculate the L-network reactances.

$$X_{L2} = Q_L R_2 \tag{28}$$

 $X_{I,2} = 2.24 \times 50 = 112 \ \Omega$ (29) $X_{P2} = \frac{R_m}{Q_I}$ (30)

(31)

$$X_{P1} = \frac{R_m}{Q_2}$$

$$X_{P1} = \frac{300}{2.92} = 102.7\,\Omega$$

$$X_{L1} = \frac{R_1 Q_{0\pi}}{Q_1^2 + 1}$$
(36)

$$Q_{0\pi} = 12 - 2.24 = 9.76$$

Use equations 14 through 18 or 22 through 26 to calculate the pi-network reactances, $X_{C1},\,X_{L1}$ and X_{P1} as shown in Fig 18.6. Be sure to use the value specified for Rm as R2 in these calculations. Also use the value just calculated for $Q_{0\pi}$ as Q_0 . Notice that X_{P1} is X_{C2} in Eq 20.

Next calculate the desired Q of the pi-

$$Q_1 \frac{R_1 Q_{0\pi} - \sqrt{R_1 R_m Q_{0\pi} - (R_1 - R_m)^2}}{R_1 R_m Q_{0\pi} - (R_1 - R_m)^2}$$

$$R_1 - R_m$$
 (32)

$$\frac{1500 \times 9.76 - \sqrt{1500 \times 300 \times 9.76^2 - (1500 - 300)^2}}{1500 - 300}$$

$$\begin{array}{l} Q_1 = \\ \frac{1.464 \times 10^4 - \sqrt{4.287 \times 10^7 - 1.44 \times 10^6}}{1200} = 6.84 \end{array}$$

$$Q_2 = Q_{0\pi} - Q_1$$
 (33)

$$Q_2 = 9.76 - 6.84 = 2.92$$

$$X_{C1} = \frac{R_1}{Q_1} \tag{34}$$

)
$$X_{C1} = \frac{1500}{6.84} = 219.3 \Omega$$

$$\mathbf{x}_{\mathbf{P}1} = \frac{\mathbf{x}_{\mathbf{m}}}{\mathbf{Q}_2} \tag{35}$$

$$X_{P1} = \frac{300}{2.92} = 102.7\,\Omega$$

$$\frac{m}{2}$$
 (35) $\frac{tran}{can}$

$$_{\rm P1} = \frac{300}{2.92} = 102.7\,\Omega$$

$$=\frac{R_{\rm m}}{Q_2} \tag{35}$$

$$X_{P1} = \frac{300}{2.92} = 102.7\,\Omega$$

$$X_{L1} = \frac{R_1 Q_{0\pi}}{Q_1^2 + 1} \tag{3}$$

$$X_{L1} = \frac{1500 \times 9.76}{6.84^2 + 1} = 306.3 \,\Omega$$

Combine the two parallel capacitors, X_{P1} and X_{P2} to find the Pi-L network X_{C2} value.

$$X_{C2} = \frac{X_{P1} X_{P2}}{X_{P1} + X_{P2}}$$
(37)
$$X_{C2} = \frac{102.7 \times 134}{102.7 + 134} = 58.3 \Omega$$

Finally, calculate the capacitance and inductance values using equations 22 through 24. Table 18.2 shows some data from Wingfield's program, PI-LCMIN. For the sample calculation shown here, we choose a frequency of 3.75 MHz.

$$C_{1} = \frac{1}{2\pi f X_{C1}} = \frac{1}{2\pi 3.75 \times 10^{6} \times 219.3} = 193.5 \text{ pF}$$

$$C_{2} = \frac{1}{2\pi f X_{C2}} = \frac{1}{2\pi 3.75 \times 10^{6} \times 58.3} = 730 \text{ pF}$$

$$L_{1} = \frac{X_{L1}}{2\pi f} = \frac{306.3}{2\pi 3.75 \times 10^{6}} = 13.0 \text{ \muH}$$

$$L_{2} = \frac{X_{L2}}{2\pi f} = \frac{112}{2\pi 3.75 \times 10^{6}} = 4.75 \text{ \muH}$$

The values for L and C in Tables 18.1 and 18.2 are based on purely resistive load impedances and assume ideal capacitors and inductors. Any other circuit reactances will modify these values.

Stray circuit reactances, including tube capacitances and capacitor stray inductances, should be included as part of the matching network. It is not uncommon for such reactances to render the use of certain matching circuits impractical, because they require either unacceptable loaded Q values or unrealistic component values. If all matching network alternatives are investigated and found unworkable, some mise solution must be found.

e 30 MHz, transistor and tube reactances tend to dominate circuit impedances. At the lower impedances found in sistor circuits, the standard networks be applied so long as suitable components are used. Above 50 MHz, capacitors often exhibit values far different from their marked values because of stray internal reactances and lead inductance, and this requires compensation. Tuned circuits are frequently fabricated in the form of strip lines or other transmission lines in order to circumvent the problem of building "pure" inductances and capacitances. The choice of components is often more significant than the type of network used.

The high impedances encountered in VHF tube-amplifier plate circuits are not easily matched with typical networks. Tube output capacitance is usually so large that most matching networks are unsuit-

18.8 Chapter 18

Table Pi-L (Sam C in	e 18.2 Network ple Outj pE and I	Values out from	for Vario PI-LCM	ous Plat IN.EXE	e Impedan by W5FD)	es					
Pi-L	Network	Values									
Rm =	= 300 Q.	Q = 12	B2 = 50	0							
C(Mi	n) = 35 r	∝₀ - ·_,)F									
Band	C1	C2	11	12		Banc	I C1	C2	11	12	
B1=1	500 ohms		L /	22		B1=2	100 ohms	02	L /	LL	
160	382	, 1443	25.7	9.38		160	288	1341	32.5	9.38	
80	194	732	13.0	4.76		80	146	680	16.5	4.76	
40	102	383	6.83	2.49		40	76	356	8.63	2.49	
30	72	270	4.82	1.76	0 10 0	30	54	251	6.09	1.76	0 10 0
20 17	51 40	193	3.44 2.69	0.98	$Q_0 = 12.0$	20 17	39	154	4.35	0.98	$Q_0 = 12.0$ $Q_0 = 13.6$
15	35	131	2.25	0.84	$Q_0 = 12.0$ $Q_0 = 12.2$	15	35	146	2.17	0.84	$Q_0 = 15.0$ $Q_0 = 15.6$
12	35	123	1.64	0.71	Q ₀ =14.0	12	35	138	1.58	0.71	Q ₀ =18.0
10	35	118	1.24	0.62	Q ₀ =15.9	10	35	132	1.19	0.62	Q ₀ =20.5
R1=1	600 ohms	3				R1=2	200 ohms				
160	362	1423	26.9	9.38		160	277	1327	33.6	9.38	
40	96	378	7.13	2.49		80 40	73	352	8.92	2 49	
30	68	267	5.04	1.76		30	52	249	6.30	1.76	
20	48	190	3.60	1.26	Q ₀ =12.0	20	37	178	4.50	1.26	Q ₀ =12.0
17	38	149	2.81	0.98	Q ₀ =12.0	17	35	156	2.95	0.98	Q ₀ =14.1
15	35	134	2.23	0.84	$Q_0 = 12.8$ $Q_0 = 14.7$	15	35	148 140	2.16	0.84	$Q_0 = 16.2$ $Q_0 = 18.7$
10	35	120	1.23	0.62	$Q_0 = 14.7$ $Q_0 = 16.7$	10	35	134	1.18	0.62	$Q_0 = 10.7$ $Q_0 = 21.3$
R1=1	700 ohms	6				R1=2	300 ohms				
160	344	1404	28.0	9.38		160	266	1315	34.7	9.38	
80	175	712	14.2	4.76		80	135	667	17.6	4.76	
40	92	373	7.44	2.49		40	71	349	9.21	2.49	
20	46	203 188	3.75	1.76	Q ₂ =12.0	20	50 36	240 176	0.50 4.65	1.70	0-120
17	36	147	2.94	0.98	$Q_0 = 12.0$ $Q_0 = 12.0$	17	35	158	2.93	0.98	$Q_0 = 12.0$ $Q_0 = 14.6$
15	35	136	2.22	0.84	Q ₀ =13.4	15	35	150	2.15	0.84	Q ₀ =16.7
12	35	129	1.62	0.71	Q ₀ =15.4	12	35	142	1.57	0.71	Q ₀ =19.3
10	35	123	1.22	0.62	Q ₀ =17.5	10	35	137	1.17	0.62	Q ₀ =22.0
H1=1 160	228	1387	29.2	0 38		H1=2 160	257	1302	/35.8	0 38	
80	166	703	14.8	4.76		80	130	660	18.2	4.76	
40	87	368	7.74	2.49		40	68	346	9.50	2.49	
30	61	260	5.47	1.76		30	48	244	6.71	1.76	
20	44	186	3.90	1.26	Q ₀ =12.0	20	35	176	4.71	1.26	Q ₀ =12.2
15	35	147	2 21	0.98	$Q_0 = 12.2$	17	35	152	2.92	0.98	$Q_0 = 15.0$ $Q_0 = 17.3$
12	35	131	1.61	0.71	$Q_0 = 16.0$	12	35	145	1.56	0.71	$Q_0 = 17.0$ $Q_0 = 20.0$
10	35	125	1.21	0.62	Q ₀ =18.2	10	35	139	1.17	0.62	Q ₀ =22.8
R1=1	900 ohms	3				R1=2	500 ohms				
160	313	1371	30.3	9.38		160	248	1291	36.9	9.38	
80 40	83	695 364	15.4	4.70		80 40	66	004 343	18.7	4.76 2.49	
30	59	257	5.68	1.76		30	46	242	6.91	1.76	
20	42	184	4.06	1.26	Q ₀ =12.0	20	35	178	4.70	1.26	Q ₀ =12.6
17	35	149	2.99	0.98	Q ₀ =12.7	17	35	163	2.91	0.98	Q ₀ =15.5
15	35	141	2.20	0.84	$Q_0 = 14.5$	15	35	154	2.13	0.84	$Q_0 = 17.8$
10	35	128	1.20	0.62	$Q_0 = 10.7$ $Q_0 = 19.0$	12	35	147	1.55	0.71	$Q_0 = 20.0$ $Q_0 = 23.5$
R1=2	000 ohms	120	1.20	0.02	u ₀ =10.0	10	00	141	1.10	0.02	Q0-20.0
160	300	1356	31.4	9.38							
80	152	687	15.9	4.76							
40	80	360	8.34	2.49							
30 20	56 40	254 181	5.89 1 20	1.76	0,-12.0						
17	35	152	2.97	0.98	$Q_0 = 12.0$ $Q_0 = 13.2$						
15	35	143	2.18	0.84	Q ₀ =15.1						
12	35	136	1.59	0.71	$Q_0 = 17.4$						
10	35	130	1.19	0.62	Q ₀ =19.7						

able. The usual practice is to resonate the tube output capacitance with a low-loss inductance connected in series or parallel. The result can be a very high-Q tank circuit. Component losses must be kept to an absolute minimum in order to achieve reasonable tank efficiency. Output impedance transformation is usually performed by a link inductively coupled to the tank circuit or by a parallel transformation of the output resistance using a series capacitor.

TRANSFORMERS

Broadband transformers are often used in matching to the input impedance or optimum load impedance in a power amplifier. Multioctave power amplifier performance can be achieved by appropriate application of these transformers. The input and output transformers are two of the most critical components in a broadband amplifier. Amplifier efficiency, gain flatness, input SWR, and even linearity all are affected by transformer design and application. There are two basic RF transformer types, as described elsewhere in this *Handbook*: the conventional transformer and the transmission-line transformer.

The conventional transformer is wound much the same way as a power transformer. Primary and secondary windings are wound around a high-permeability core, usually made from a ferrite or powdered-iron material. Coupling between the secondary and primary is made as tight as possible to minimize leakage inductance. At low frequencies, the coupling between windings is predominantly magnetic. As the frequency rises, core permeability decreases and leakage inductance increases; transformer losses increase as well.

Typical examples of conventional transformers are shown in Fig 18.7. In Fig 18.7A, the primary windings consist of brass or copper tubes inserted into ferrite sleeves. The tubes are shorted together at one end by a piece of copper-clad circuit board material. The secondary winding is threaded through the tubes. Since the lowimpedance winding is only a single turn, the transformation ratio is limited to the squares of integers; for example, 1, 4, 9, 16, and so on. The lowest effective transformer frequency is determined by the inductance of the one-turn winding. It should have a reactance, at the lowest frequency of intended operation, at least four times greater than the impedance it is connected to.

The coupling coefficient between the two windings is a function of the primary tube diameter and its length, and the diameters and insulation thickness of the wire used in the high-impedance winding. High impedance ratios, greater than 36:1, should use large-diameter secondary windings. Miniature coaxial cable (using only the braid as the conductor) works well. Another use for coaxial cable braid is illustrated in Fig 18.7B. Instead of using tubing for the primary winding, the secondary winding is threaded through copper braid. Performance of the two units is almost identical.

The cores used must be large enough so the core material will not saturate at the power level applied to the transformer. Core saturation can cause permanent changes to the core permeability, as well as overheating. Transformer nonlinearity also develops at core saturation. Harmonics and other distortion products are produced, clearly an undesirable situation. Multiple cores can be used to increase the power capabilities of the transformer.

Transmission-line transformers are similar to conventional transformers, but can be used over wider frequency ranges. In a conventional transformer, high-frequency performance deterioration is caused primarily by leakage inductance,





Fig 18.7—The two methods of constructing the transformers outlined in the text. At A, the one-turn loop is made from brass tubing; at B, a piece of coaxial cable braid is used for the loop. which rises with frequency. In a transmission-line transformer, the windings are arranged so there is tight capacitive coupling between the two. A high coupling coefficient is maintained up to considerably higher frequencies than with conventional transformers.

OUTPUT FILTERING

Amplifier output filtering is sometimes necessary to meet spurious signal requirements. Broadband amplifiers, by definition, provide little if any inherent suppression of harmonic energy. Even amplifiers using output tank circuits often require further attenuation of undesired harmonics. High-level signals from one transmitter, particularly at multiple transmitter sites, can be intercepted by an antenna connected to another transmitter, conducted down the feed line and mixed in a power amplifier, causing spurious outputs. For example, an HF transceiver signal radiated from a triband beam may be picked up by a VHF FM antenna on the same mast. The signal saturates the low-power FM transceiver output stage, even with power off, and is reradiated by the VHF antenna. Proper use of filters can reduce such spurious energy considerably.

The filter used will depend on the application and the level of attenuation needed. Band-pass filters attenuate spurious signals above and below the passband for which they are designed. Low-pass filters attenuate only signals above the cutoff frequency, while high-pass filters reduce energy below the design cutoff frequency.

The **RF and AF Filters** chapter includes detailed information about designing suitable filters. Tables of component values in the **Component Data and References** chapter allow you to select a particular design and scale the values for different frequencies and impedance ranges as needed.

TRANSMITTING DEVICE RATINGS Plate Dissipation

The ultimate factor limiting the powerhandling capability of a tube is often (but not always) its maximum plate dissipation rating. This is the measure of how many watts of heat the tube can safely dissipate, if it is cooled properly, without exceeding critical temperatures. Excessive temperature can damage or destroy internal tube components or vacuum seals, resulting in tube failure. The same tube may have different voltage, current and power ratings depending on the conditions under which it is operated, but its safe temperature ratings must not be exceeded in any case! Important cooling considerations are discussed in more detail in the Amplifier Cooling section of this chapter.

The efficiency of a power amplifier may range from approximately 25% to 75%, depending on its operating class, adjustment, and circuit losses. The efficiency indicates how much of the dc power supplied to the stage is converted to useful RF output power; the rest is dissipated as heat, mostly by the plate. By knowing the platedissipation limit of the tube and the efficiency expected from the class of operation selected, the maximum power input and output levels can be determined. The maximum safe power output is

$$P_{OUT} = \frac{P_D N_P}{100 - N_P}$$
(38)

where

 P_{OUT} = the power output in W P_D = the plate dissipation in W N_P = the efficiency (10% = 10).

The dc input power would simply be

$$P_{\rm IN} = \frac{100 \, P_{\rm D}}{100 - N_{\rm P}} \tag{39}$$

Almost all vacuum-tube power amplifiers in amateur service today operate as linear amplifiers (Class AB or B) with efficiencies of approximately 50% to 65%. That means that a useful power output of approximately 1 to 2.0 times the plate dissipation generally can be achieved. This requires, or course, that the tube is cooled enough to realize its maximum plate dissipation rating and that no other tube rating, such as maximum plate current or grid dissipation, is exceeded.

Type of modulation and duty cycle also influence how much output power can be achieved for a given tube dissipation. Some types of operation are less efficient than others, meaning that the tube must dissipate more heat. Some forms of modulation, such as CW or SSB, are intermittent in nature, causing less average heating than modulation formats such as RTTY in which there is continuous transmission. Power-tube manufacturers use two different rating systems to allow for the variations in service. CCS (Continuous Commercial Service) is the more conservative rating and is used for specifying tubes that are in constant use at full power. The second rating system is based on intermittent, low-duty-cycle operation, and is known as ICAS (Intermittent Commercial and Amateur Service). ICAS ratings are normally used by commercial manufacturers and individual amateurs who wish to obtain maximum power output consistent with reasonable tube life

in CW and SSB service. CCS ratings should be used for FM, RTTY and SSTV applications. (Plate power transformers for amateur service are also rated in CCS and ICAS terms.)

Maximum Ratings

Tube manufacturers publish sets of maximum values for the tubes they produce. No maximum rated value should ever be exceeded. As an example, a tube might have a maximum plate-voltage rating of 2500 V, a maximum plate-current rating of 500 mA, and a maximum plate dissipation rating of 350 W. Although the plate voltage and current ratings might seem to imply a safe power input of 2500 V \times 500 mA = 1250 W, this is true only if the dissipation rating will not be exceeded. If the tube is used in class AB2 with an expected efficiency of 60%, the maximum safe dc power input is

$$P_{IN} = \frac{100P_D}{100 - N_D} = \frac{100 \times 350}{100 - 60} = 875 \text{ W}$$

In this case, any combination of plate voltage and current whose product does not exceed 875 W (and which allows the tube to achieve the expected 60% efficiency) is acceptable. A good compromise might be 2000 V and 437 mA: $2000 \times 0.437 = 874$ W input. If the maximum plate voltage of 2500 is used, then the plate current should be limited to 350 mA (not 500 mA) to stay within the maximum plate dissipation rating of 350 W.

TRANSISTOR POWER DISSIPATION

RF power-amplifier transistors are limited in power-handling capability by the amount of heat the device can safely dissipate. Power dissipation for a transistor is abbreviated P_D . The maximum rating is based on maintaining a case temperature of $25^{\circ}C$ (77°F), which is seldom possible if a conventional air-cooled heat sink is used in an ambient air temperature of 70°F or higher. For higher temperatures, the device must be derated (in terms of milliwatts or watts per degree C) as specified by the manufacturer for that particular device. The efficiency considerations described earlier in reference to plate dissipation apply here also. A rule of thumb for selecting a transistor suitable for a given RF power output level is to choose one that has a maximum dissipation (with the heat sink actually to be used) of twice the desired output power.

Maximum Transistor Ratings

Transistor data sheets specify the maximum operating voltage for several conditions. Of particular interest is the V_{CFO}

specification (collector to emitter voltage, with the base open). In RF amplifier service the collector to emitter voltage can rise to twice the dc supply potential. Thus, if a 12-V supply is used, the transistor should have a V_{CEO} of 24 V or greater to preclude damage.

The maximum collector current is also specified by the manufacturer. This specification is actually limited by the currentcarrying capabilities of the internal bonding wires. Of course, the collector current must stay below the level that generates heat higher than the allowable device power dissipation. Many transistors are also rated for the load mismatch they can safely withstand. A typical specification might be for a transistor to tolerate a 30:1 SWR at all phase angles.

Transistor manufacturers publish data sheets that describe all the appropriate device ratings. Typical operating results are also given in these data sheets. In addition, many manufacturers publish application notes illustrating the use of their devices in practical circuits. Construction details are usually given. Perhaps owing to the popularity of Amateur Radio among electrical engineers, many of the notes describe applications especially suited to the Amateur Service. Specifications for some of the more popular RF power transistors are found in the **Component Data and References** chapter.

PASSIVE COMPONENT RATINGS Output Tank Capacitor Ratings

The tank capacitor in a high-power amplifier should be chosen with sufficient spacing between plates to preclude highvoltage breakdown. The peak RF voltage present across a properly loaded tank circuit, without modulation, may be taken conservatively as being equal to the dc plate or collector voltage. If the dc supply voltage also appears across the tank capacitor, this must be added to the peak RF voltage, making the total peak voltage twice the dc supply voltage. At the higher voltages, it is usually desirable to design the tank circuit so that the dc supply voltages do not appear across the tank capacitor, thereby allowing the use of a smaller capacitor with less plate spacing. Capacitor manufacturers usually rate their products in terms of the peak voltage between plates. Typical plate spacings are given in Table 18.3.

Output tank capacitors should be mounted as close to the tube as temperature considerations will permit, to make possible the shortest path with the lowest possible inductive reactance from plate to cathode. Especially at the higher frequen-

Table 18.3

Typical Tank-Capacitor Plate Spacings

Spacing	Peak	Spacing	Peak	Spacing	Peak
Inches	Voltage	Inches	Voltage	Inches	Voltage
0.015	1000	0.07	3000	0.175	7000
0.02	1200	0.08	3500	0.25	9000
0.03	1500	0.125	4500	0.35	11000
0.05	2000	0.15	6000	0.5	13000

Table 18.4

Copper Conductor Sizes for Transmitting Coils for Tube Transmitters

Power	Band	Minimum					
Output	(MHz)	Conductor					
(Watts)		Size					
1500	1.8-3.5	10					
	7-14	8 or ¹ / ₈ "					
	18-28	6 or ³ / ₁₆ "					
500	1.8-3.5	12					
	7-14	10					
	18-28	8 or ¹ / ₈ "					
150	1.8-3.5	16					
	7-14	12					
	18-28	10					
*Whole numbers are AWG; fractions of inches are tubing ODs.							

cies, where minimum circuit capacitance becomes important, the capacitor should be mounted with its stator plates well spaced from the chassis or other shielding. In circuits in which the rotor must be insulated from ground, the capacitor should be mounted on ceramic insulators of a size commensurate with the plate voltage involved and-most important of all, from the viewpoint of safety to the operator-a well-insulated coupling should be used between the capacitor shaft and the knob. The section of the shaft attached to the control knob should be well grounded. This can be done conveniently by means of a metal shaft bushing at the panel.

Tank Coils

Tank coils should be mounted at least half their diameter away from shielding or other large metal surfaces, such as blower housings, to prevent a marked loss in Q. Except perhaps at 24 and 28 MHz, it is not essential that the coil be mounted extremely close to the tank capacitor. Leads up to 6 or 8 inches are permissible. It is more important to keep the tank capacitor, as well as other components, out of the immediate field of the coil.

The principal practical considerations in designing a tank coil usually are to select a conductor size and coil shape that will fit into available space and handle the required power without excessive heating. Excessive power loss as such is not necessarily the worst hazard in using too-small a conductor: it is not uncommon for the heat generated to actually unsolder joints in the tank circuit and lead to physical damage or failure. For this reason it's extremely important, especially at power levels above a few hundred watts, to ensure that all electrical joints in the tank circuit are secured mechanically as well as soldered. Table 18.4 shows recommended conductor sizes for amplifier tank coils, assuming loaded tank circuit Qs of 15 or less on the 24 and 30 MHz bands and 8 to 12 on the lower frequency bands. In the case of input circuits for screen-grid tubes where driving power is quite small, loss is relatively unimportant and almost any physically convenient wire size and coil shape is adequate.

The conductor sizes in Table 18.4 are based on experience in continuous-duty amateur CW, SSB, and RTTY service and assume that the coils are located in a reasonably well ventilated enclosure. If the tank area is not well ventilated and/or if significant tube heat is transferred to the coils, it is good practice to increase AWG wire sizes by two (for example, change from #12 to #10) and tubing sizes by ¹/₁₆ inch.

Larger conductors than required for current handling are often used to maximize unloaded Q, particularly at higher frequencies. Where skin depth effects increase losses, the greater surface area of large diameter conductors can be beneficial. Small-diameter copper tubing, up to ³/s-inch outer diameter, can be used successfully for tank coils up through the lower VHF range. Copper tubing in sizes suitable for constructing high-power coils is generally available in 50-ft rolls from plumbing and refrigeration equipment suppliers. Silver-plating the tubing further reduces losses. This is especially true as the tubing ages and oxidizes. Silver oxide is a much better conductor than copper oxides, so silver-plated tank coils maintain their low-loss characteristics even after years of use.

At VHF and above, tank circuit inductances do not necessarily resemble the familiar coil. The inductances required to resonate tank circuits of reasonable Q at these higher frequencies are small enough that only strip lines or sections of transmission line are practical. Since these are constructed from sheet metal or largediameter tubing, current-handling capabilities normally are not a relevant factor.

RF Chokes

The characteristics of any RF choke vary with frequency. At low frequencies the choke presents a nearly pure inductance. At some higher frequency it takes on high impedance characteristics resembling those of a parallel-resonant circuit. At a still higher frequency it goes through a series-resonant condition, where the impedance is lowest-generally much too low to perform satisfactorily as a shuntfeed plate choke. As frequency increases further, the pattern of alternating parallel and series resonances repeats. Between resonances, the choke will show widely varying amounts of inductive or capacitive reactance.

In series-feed circuits, these characteristics are of relatively small importance because the RF voltage across the choke is negligible. In a shunt-feed circuit such as is used in most high-power amplifiers, however, the choke is directly in parallel with the tank circuit, and is subject to the full tank RF voltage. If the choke does not present a sufficiently high impedance, enough power will be absorbed by the choke to burn it out. To avoid this, the choke must have a sufficiently high reactance to be effective at the lowest frequency (at least equal to the plate load resistance), and yet have no series resonances near any of the higher frequency bands. A resonant-choke failure in a highpower amplifier can be very dramatic and damaging!

Thus any choke intended for shunt-feed use should be carefully investigated with a dip meter. The choke must be shorted endto-end with a direct, heavy braid or strap. Because nearby metallic objects affect the resonances, it should be mounted in its intended position, but disconnected from the rest of the circuit. A dip meter coupled an inch or two away from one end of the choke nearly always will show a deep, sharp dip at the lowest series-resonant frequency and shallower dips at higher series resonances.

Any choke to be used in an amplifier for the 1.8 to 28 MHz bands requires careful (or at least lucky!) design to perform well on all amateur bands within that range. Most simply put, the challenge is to achieve sufficient inductance that the choke doesn't "cancel" a large part of tuning capacitance on 1.8 MHz. At the same time, try to position all its series resonances where they can do no harm. In general, close wind enough #20 to #24 magnet wire to provide about 135 µH inductance on a 3/4 to 1-inch diameter cylindrical form of ceramic, Teflon, or fiberglass. This gives a reactance of 1500 Ω at 1.8 MHz and yet yields a first series resonance in the vicinity of 25 MHz. Before the advent of the 24.9-MHz band this worked fine. But trying to "squeeze" the resonance into the narrow gaps between the 21, 24, and/or 28-MHz bands is quite risky unless sophisticated instrumentation is available. If the number of turns on the choke is selected to place its first series resonance at 23.2 MHz, midway between 21.45 and 24.89 MHz, the choke impedance will typically be high enough for satisfactory operation on the 21, 24 and 28 MHz bands. The choke's first series resonance should be measured very carefully as described above using a dip meter and calibrated receiver or RF impedance bridge, with the choke mounted in place on the chassis.

Investigations with a vector impedance meter have shown that "trick" designs, such as using several shorter windings spaced along the form, show little if any improvement in choke resonance characteristics. Some commercial amplifiers circumvent the problem by bandswitching the RF choke. Using a larger diameter (1 to 1.5 inch) form does move the first series resonance somewhat higher for a given value of basic inductance. Beyond that, it is probably easiest for an all-band amplifier to add or subtract enough turns to move the first resonance to about 35 MHz and settle for a little less than optimum reactance on 1.8 MHz.

Blocking Capacitors

A series capacitor is usually used at the input of the amplifier output circuit. Its purpose is to block dc from appearing on matching circuit components or the antenna. As mentioned in the section on tank capacitors, output-circuit voltage requirements are considerably reduced when only RF voltage is present.

To provide a margin of safety, the voltage rating for a blocking capacitor should be at least 25% to 50% greater than the dc voltage applied. A large safety margin is desirable, since blocking capacitor failure can bring catastrophic results.

To avoid affecting the amplifier's tuning and matching characteristics, the blocking capacitor should have a low impedance at all operating frequencies. Its reactance at the lowest operating frequency should be not more than about 5% of the plate load resistance.

The capacitor also must be capable of handling, without overheating or significantly changing value, the substantial RF current that flows through it. This current usually is greatest at the highest frequency of operation, where tube output capacitance constitutes a significant part of the total tank capacitance. A significant portion of circulating tank current therefore flows through the blocking capacitor. As a conservative and very rough rule of thumb, the maximum RF current in the blocking capacitor (at 28 MHz) is

$$I_{\text{CBlock}} \approx I_{\text{p}} + 0.15 \times C_{\text{OUT}} \times V_{\text{dc}}$$
 (40)

where

I_{CBlock} = maximum RMS current through blocking capacitor, in A C_{OUT} = output capacitance of the output

tubes, in pF

 V_{dc} = dc plate voltage, in kV

 $I_p = dc$ plate current at full output, in A.

Transmitting capacitors are rated by their manufacturers in terms of their RF current-carrying capacity at various frequencies. Below a couple hundred watts at the high frequencies, ordinary disc ceramic capacitors of suitable voltage rating work well in high-impedance tube amplifier output circuits. Some larger disk capacitors rated at 5 to 8 kV also work well for higher power levels at HF; for example, two inexpensive Centralab type DD-602 discs (0.002 µF, 6 kV) in parallel have proved to be a reliable blocking capacitor for 1.5-kW amplifiers operating at plate voltages to about 2.5 kV. At very high power and voltage levels and at VHF, ceramic "doorknob" transmitting capacitors are needed for their low losses and high current handling capabilities. Socalled "TV doorknobs" may break down at high RF current levels and should be avoided.

The very high values of Q_L found in many VHF and UHF tube-type amplifier tank circuits often require custom fabrication of the blocking capacitor. This can usually be accommodated through the use of a Teflon "sandwich" capacitor. Here, the blocking capacitor is formed from two parallel plates separated by a thin layer of Teflon. This capacitor often is part of the tank circuit itself, forming a very low-loss blocking capacitor. Teflon is rated for a minimum breakdown voltage of 2000 V per mil of thickness, so voltage breakdown should not be a factor in any practically realized circuit. The capacitance formed from such a Teflon sandwich can be calculated from the information presented elsewhere in this Handbook (use a dielectric constant of 2.1 for Teflon). In order to prevent any potential irregularities caused by dielectric thickness variations (including air gaps), Dow-Corning DC-4 silicone grease should be evenly applied to both sides of the Teflon dielectric. This grease has properties similar to Teflon, and will fill in any surface irregularities that might cause problems.

The very low impedances found in transistorized amplifiers present special problems. In order to achieve the desired low blocking-capacitor impedance, largevalue capacitors are required. Special ceramic chips and mica capacitors are available that meet the requirements for high capacitance, large current carrying capability and low associated inductance. These capacitors are more costly than standard disk-ceramic or silver-mica units, but their level of performance easily justifies their price. Most of these specialpurpose capacitors are either leadless or come with wide straps instead of normal wire leads. Disc-ceramic and other wirelead capacitors are generally not suitable for transistor power-amplifier service.

SOURCES OF OPERATING VOLTAGES

Tube Filament or Heater Voltage

The heater voltage for the indirectly heated cathode tubes found in low-power classifications may vary 10% above or below rating without seriously reducing the life of the tube. A power vacuum tube can use either a directly heated filament or an indirectly heated cathode. The filament voltage for either type should be held within 5% of rated voltage. Because of internal tube heating at UHF and higher, the manufacturers' filament voltage rating often is reduced at these higher frequencies. The derated filament voltages should be followed carefully to maximize tube life. Series dropping resistors may be required in the filament circuit to attain the correct voltage. The voltage should be measured at the filament pins of the tube socket while the amplifier is running. The filament choke and interconnecting wiring all have voltage drops associated with them. The high current drawn by a power-tube heater circuit causes substantial voltage drops to occur across even small resistances. Also. make sure that the plate power drawn from the power line does not cause the filament voltage to drop below the proper value when plate power is applied.

Thoriated filaments lose emission when the tube is overloaded appreciably. If the overload has not been too prolonged, emission sometimes may be restored by operating the filament at rated voltage, with all other voltages removed, for a period of 30 to 60 minutes. Alternatively, you might try operating the tube at 20% above rated filament voltage for five to ten minutes.

VACUUM-TUBE PLATE VOLTAGE

DC plate voltage for the operation of RF amplifiers is most often obtained from a transformer-rectifier-filter system (see the **Power Supplies** chapter) designed to deliver the required plate voltage at the required current. It is not unusual for a power tube to arc over internally (generally from the plate to the screen or control grid) once or twice, especially soon after it is first placed into service. The flashover by itself is not normally dangerous to the tube, provided that instantaneous maximum plate current to the tube is held to a safe value and the high-voltage plate supply is shut off very quickly.

A good protective measure against this is the inclusion of a high-wattage power resistor in series with the plate high-voltage circuit. The value of the resistor, in ohms, should be approximately 10 to 15 times the no-load plate voltage in kV. This will limit peak fault current to 67 to 100 A. The series resistor should be rated for 25 or 50-W power dissipation; vitreous enamel coated wire-wound resistors of the common Ohmite or Clarostat types have been found to be capable of handling repeated momentary fault-current surges without damage. Aluminum-cased resistors such as some made by Dale are not recommended for this application. Each resistor also must be large enough to safely handle the maximum value of normal plate current; the wattage rating required may be calculated from $P = I^2 R$. If the total filter capacitance exceeds 25 μ F, it is a good idea to use 50-W resistors in any case. Even at high plate-current levels, the addition of the resistors does little to affect the dynamic regulation of the plate supply.

Since tube (or other high-voltage circuit) arcs are not necessarily self-extinguishing, a fast-acting plate overcurrent relay or primary circuit breaker also is recommended to quickly shut off ac power to the HV supply when an arc begins. Using this protective system, a mild HV flashover may go undetected, while a more severe one will remove ac power from the HV supply. (The cooling blower should remain energized however, since the tube may be hot when the HV is removed due to an arc.) If effective protection is not provided, however, a "normal" flashover, even in a new tube, is likely to damage or destroy the tube, and also frequently destroys the rectifiers in the power supply as well as the plate RF choke. A power tube that flashes over more than about 3 to 5 times in a period of several months likely is defective and will have to be replaced before long.

Grid Bias

The grid bias for a linear amplifier should be highly filtered and well regulated. Any ripple or other voltage change in the bias circuit modulates the amplifier. This causes hum and/or distortion to appear on the signal. Since most linear amplifiers draw only small amounts of grid current, these bias-supply requirements are not difficult to achieve.

Fixed bias for class AB1 tetrode and pentode amplifiers is usually obtained from a variable-voltage regulated supply. Voltage adjustment allows setting bias level to give the desired resting plate current. Fig 18.8A shows a simple Zenerdiode-regulated bias supply. The dropping resistor is chosen to allow approximately 10 mA of Zener current. Bias is then reasonably well regulated for all drive conditions up to 2 or 3 mA of grid current. The potentiometer allows bias to be adjusted between Zener and approximately 10 V higher. This range is usually adequate to allow for variations in the characteristics of different tubes. Under standby conditions, when it is desirable to cut off the tube entirely, the Zener ground return is interrupted so the full bias supply voltage is applied to the grid.

In Fig 18.8B and C, bias is obtained from the voltage drop across a Zener diode in the cathode (or filament centertap) lead. Operating bias is obtained by the voltage drop across D1 as a result of plate (and screen) current flow. The diode voltage drop effectively raises the cathode potential relative to the grid. The grid is therefore negative with respect to the cathode by the Zener voltage of the diode. The Zener-diode wattage rating should be twice the product of the maximum cathode current times the rated zener voltage. Therefore, a tube requiring 15 V of bias with a maximum cathode current of 100 mA would dissipate 1.5 W in the Zener diode. To allow a suitable safety factor, the diode rating should be 3 W or more. The circuit of Fig 18.8C illustrates how D1 would be used with a cathode driven (grounded grid) amplifier as

opposed to the grid driven example at B.

In all cases, the Zener diode should be bypassed by a 0.01- μ F capacitor of suitable voltage. Current flow through any type of diode generates shot noise. If not bypassed, this noise would modulate the amplified signal, causing distortion in the amplifier output.

Screen Voltage For Tubes

Power tetrode screen current varies widely with both excitation and loading. The current may be either positive or negative, depending on tube characteristics and amplifier operating conditions. In a linear amplifier, the screen voltage should be well regulated for all values of screen current. The power output from a tetrode is very sensitive to screen voltage, and any dynamic change in the screen potential can cause distorted output. Zener diodes are commonly used for screen regulation.

Fig 18.9 shows a typical example of a regulated screen supply for a power tetrode amplifier. The voltage from a fixed dc supply is dropped to the Zener stack voltage by the current-limiting resistor. A screen bleeder resistor is connected in parallel with the zener stack to allow for the negative screen current developed under certain tube operating conditions. Bleeder current is chosen to be roughly 10 to 20 mA greater than the expected maximum negative screen current, so that screen voltage is regulated for all values of current between maximum negative screen current and maximum positive screen current. For external-anode tubes in the 4CX250 family, a typical screen bleeder current value would be 20 mA. For the 4CX1000 family, a screen-bleeder current of 70 mA is required.

Screen voltage should never be applied to a tetrode unless plate voltage and load also are applied; otherwise the screen will act like an anode and will draw excessive current. Supplying the screen through a series-dropping resistor from the plate supply affords a measure of protection, since the screen voltage only appears when there is plate voltage. Alternatively, a fuse can be placed between the regulator and the bleeder resistor. The fuse should not be installed between the bleeder resistor and the tube, because the tube should never be operated without a load on the screen. Without a load, the screen potential tends to rise to the anode voltage. Any screen bypass capacitors or other associated circuits are likely be damaged by this high voltage.

In Fig 18.9, a varistor is connected from screen to ground. If, because of some circuit failure, the screen voltage should rise substantially above its nominal level, the



Fig 18.8—Various techniques for providing operating bias with tube amplifiers.



Fig 18.9—A Zener-regulated screen supply for use with a tetrode. Protection is provided by a fuse and a varistor.

varistor will conduct and clamp the screen voltage to a low level. If necessary to protect the varistor or screen dropping resistors, a fuse or overcurrent relay may be used to shut off the screen supply so that power is interrupted before any damage occurs. The varistor voltage should be approximately 30% to 50% higher than normal screen voltage.

Transistor Biasing

Solid-state power amplifiers generally operate in Class C or AB. When some bias is desired during Class C operation (**Fig 18.10A**), a resistance of the appropriate value can be placed in the emitter return as shown. Most transistors will operate in Class C without adding bias externally, but in some instances the amplifier efficiency can be improved by means of emitter bias. Reverse bias supplied to the base of the Class-C transistor should be avoided because it will lead to internal breakdown of the device during peak drive periods. The damage is frequently a cumulative phenomenon, leading to gradual destruction of the transistor junction.

A simple method for Class AB biasing is shown in Fig 18.10B. D1 is a silicon diode that acts as a bias clamp at approximately 0.7 V. This forward bias establishes linear-amplification conditions. That value of bias is not always optimum for a specified transistor in terms of IMD. Variable bias of the type illustrated in Fig 18.10C permits the designer sufficient flexibility to position the operating point for best linearity. The diode clamp or the reference sensor for another type of regulator is usually thermally bonded to the power transistor or its heat sink. The bias level then tracks the thermal characteristics of the output transistor. Since a transistor's current transfer characteristics are a function of temperature, thermal tracking of the bias is necessary to maintain device linearity and, in the case of bipolar devices, to prevent thermal runaway and the subsequent destruction of the transistor.

AMPLIFIER COOLING Tube Cooling

Vacuum tubes must be operated within the temperature range specified by the manufacturer if long tube life is to be achieved. Tubes having glass envelopes and rated at up to 25-W plate dissipation may be used without forced-air cooling if the design allows a reasonable amount of convection cooling. If a perforated metal enclosure is used, and a ring of ¹/₄ to ³/₈inch-diameter holes is placed around the tube socket, normal convective airflow can be relied on to remove excess heat at room temperatures.

For tubes with greater plate dissipation ratings, and even for very small tubes operated close to maximum rated dissipation, forced-air cooling with a fan or blower is needed. Most manufacturers rate tube-cooling requirements for continuous-duty operation. Their literature will indicate the required volume of airflow, in cubic feet per minute (CFM), at some particular backpressure. Often this data is given for several different values of plate dissipation, ambient air temperature and even altitude above sea level.

One extremely important consideration is often overlooked by power-amplifier designers and users alike: a tube's plate dissipation rating is only its maximum potential capability. The power that it can actually dissipate safely depends directly on the cooling provided. The actual power capability of virtually all tubes used in high-power amplifiers for amateur service depends on the volume of air forced through the tube's cooling structure.

This requirement usually is given in terms of cubic feet of air per minute, (CFM), delivered into a "back pressure" representing the resistance of the tube cooler to air flow, stated in inches of water. Both the CFM of airflow required and the pressure needed to force it through the cooling system are determined by ambient air temperature and altitude (air density), as well as by the amount of heat to be dissipated. The cooling fan or blower must be capable of delivering the specified airflow into the corresponding backpressure. As a result of basic air flow and heat transfer principles, the volume of airflow required through the tube cooler increases considerably faster than the plate dissipation, and backpressure increases even faster than airflow. In addition, blower air output decreases with increasing backpressure until, at the blower's so-called



Fig 18.10—Biasing methods for use with transistor amplifiers.

Table 18.5

Specifications of Some Popular Tubes, Sockets and Chimneys

Tuba	CEM	Pook Propouro	Saakat	Chimnou		
Tube	CFIN	(inches)	SUCKEL	Chinney		
3-500Z	13	0.13 [´]	SK-400, SK-410	SK-416		
3CX800A7	19	0.50	SK-1900	SK-1906		
3CX1200A7	31	0.45	SK-410	SK-436		
3CX1200Z7	42	0.30	SK-410	_		
3CX1500/8877	35	0.41	SK-2200, SK-2210	SK-2216		
4-400A/8438	14	0.25	SK-400, SK-410	SK-406		
4-1000A/8166	20	0.60	SK-500, SK-510	SK-506		
4CX250R/7850	6.4	0.59	SK602A, SK-610, SK-610A			
			SK-611, SK-612, SK-620,			
			SK-620A, SK-621, SK-630			
4CX400/8874	8.6	0.37	SK1900	SK606		
4CX400A	8	0.20	SK2A	_		
4CX800A	20	0.50	SK1A	_		
4CX1000A/8168	25	0.20	SK-800B, SK-810B,	SK-806		
			SK-890B			
4CX1500B/8660	34	0.60	SK-800B, SK-1900	SK-806		
4CX1600B	36	0.40	SK3A	CH-1600B		
These values are for sea-level elevation. For locations well above sea level (5000 ft/ 1500 m, for example), add an additional 20% to the figure listed.						

"cutoff pressure," actual air delivery is zero. Larger and/or faster-rotating blowers are required to deliver larger volumes of air at higher backpressure.

Values of CFM and backpressure required to realize maximum rated plate dissipation for some of the more popular tubes, sockets and chimneys (with 25°C ambient air and at sea level) are given in **Table 18.5**. Backpressure is specified in inches of water and can be measured easily in an operational air system as indicated in **Figs 18.11** and **18.12**. The pressure differential between the air passage and atmospheric pressure is measured with a device called a *manometer*. A manometer is nothing more than a piece of clear tubing, open at both ends and fashioned in the shape of a "U." The manometer is temporarily connected to the chassis and is removed after the measurements are completed. As shown in the diagrams, a small amount of water is placed in the tube. At Fig 18.12A the blower is "off" and the water seeks its own level, because the air pressure (ordinary atmospheric pressure) is the same at both ends of the manometer tube. At B, the blower is "on" (socket, tube and chimney in place) and the pressure difference, in terms of inches of water, is measured. For most applications a standard ruler used for measurement will yield sufficiently accurate results.

 Table 18.6 gives the performance speci fications for a few of the many Dayton blowers, which are available through Grainger catalog outlets in all 50 states. Other blowers having wheel diameters, widths and rotational speeds similar to any in Table 18.6 likely will have similar flow and backpressure characteristics. If in doubt about specifications, consult the manufacturer. Tube temperature under actual operating conditions is the ultimate criterion for cooling adequacy and may be determined using special crayons or lacquers that melt and change appearance at specific temperatures. The setup of Fig 18.12, however, nearly always gives sufficiently accurate information.

As an example, consider the cooling design of a linear amplifier to use one 3CX800A7 tube, to operate near sea level with the air temperature not above 25°C. The tube, running 1150-W dc input, easily delivers 750-W continuous output, resulting in 400-W plate dissipation ($P_{DIS} = P_{IN} - P_{OUT}$). According to the manufacturer's data, adequate tube cooling at 400 W P_{D} requires at least 6 CFM of air at 0.09 inches of water back pressure. In Table 18.6, a Dayton no. 2C782 will do the job with a good margin of safety.

If the same single tube were to be operated at 2.3 kW dc input to deliver 1.5 kW output (substantially exceeding its maximum electrical ratings!), P_{IN} would be about 2300 W and $P_D \approx 800$ W. The minimum cooling air required would be about 19 CFM at 0.5 inches of water pressure doubling P_{DIS} , more than tripling the CFM of air flow required and increasing back pressure requirements on the blower by a factor of 5.5!

However, two 3CX800A7 tubes are needed to deliver 1.5 kW of continuous maximum legal output power in any case. Each tube will operate under the same conditions as in the single-tube example above, dissipating 400 W. The total cooling air requirement for the two tubes is therefore 12 CFM at about 0.09 inches of water, only two-thirds as much air volume and one-fifth the back pressure required by a single tube. While this may seem surprising, the reason lies in the previously mentioned fact that both the airflow required by a tube and the resultant back pressure increase much more rapidly than P_D of the tube. Blower air delivery capability, conversely, decreases as back-pres-



Fig 18.11—Air is forced into the chassis by the blower and exits through the tube socket. The manometer is used to measure system back pressure, which is an important factor in determining the proper size blower.



Fig 18.12—At A the blower is "off" and the water will seek its own level in the manometer. At B the blower is "on" and the amount of back pressure in terms of inches of water can be measured as indicated.

Table 18.6											
Blower Performance Specifications											
Wheel	Wheel	RPM	Free Air	CFN	1 for B	ack Pre	ssure	(inches)	Cutoff	Stock	
Dia	Width		CFM	0.1	0.2	0.3	0.4	0.5		No.	
2"	1"	3160	15	13	4	_	—		0.22	2C782	
3"	1 ¹⁵ / ₃₂ "	3340	54	48	43	36	25	17	0.67	4C012	
3"	1 ⁷ /8"	3030	60	57	54	49	39	23	0.60	4C440	
3"	1 ⁷ /8"	2880	76	70	63	56	45	8	0.55	4C004	
3 ¹³ / ₁₆ "	1 ⁷ /8"	2870	100	98	95	90	85	80	0.80	4C443	
3 ¹³ / ₁₆ "	2 ¹ / ₂ "	3160	148	141	135	129	121	114	1.04	4C005	

sure is increased. Thus a Dayton 2C782 blower can cool two 3CX800A7 tubes dissipating 800 W total, but a much larger (and probably noisier) no. 4C440 would be required to handle the same power with a single tube.

In summary, three very important considerations to remember are these:

- A tube's actual safe plate dissipation capability is totally dependent on the amount of cooling air forced through its cooling system. Any air-cooled power tube's maximum plate dissipation rating is meaningless unless the specified amount of cooling air is supplied.
- Two tubes will always safely dissipate a given power with a significantly smaller (and quieter) blower than is required to dissipate the same power with a single tube of the same type. A corollary is that a given blower can virtually always dissipate more power when cooling two tubes than when cooling a single tube of the same type.
- Blowers vary greatly in their ability to deliver air against backpressure so

blower selection should not be taken lightly.

A common method for directing the flow of air around a tube involves the use of a pressurized chassis. This system is shown in Fig 18.11. A blower attached to the chassis forces air around the tube base, often through holes in its socket. A chimney is used to guide air leaving the base area around the tube envelope or anode cooler, preventing it from dispersing and concentrating the flow for maximum cooling.

A less conventional approach that offers a significant advantage in certain situations is shown in **Fig 18.13**. Here the anode compartment is pressurized by the blower. A special chimney is installed between the anode heat exchanger and an exhaust hole in the compartment cover. When the blower pressurizes the anode compartment, there are two parallel paths for airflow: through the anode and its chimney, and through the air system socket. Dissipation, and hence cooling air required, generally is much greater for the anode than for the tube base. Because high-volume anode airflow need not be forced through restrictive air channels in the base area, backpressure may be very significantly reduced with certain tubes and sockets. Only airflow actually needed is bled through the base area. Blower backpressure requirements may sometimes be reduced by nearly half through this approach.

Table 18.5 also contains the part numbers for air-system sockets and chimneys available for use with the tubes that are listed. The builder should investigate which of the sockets listed for the 4CX250R, 4CX300A, 4CX1000A and 4CX1600A best fit the circuit needs. Some of the sockets have certain tube elements grounded internally through the socket. Others have elements bypassed to ground through capacitors that are integral parts of the sockets.

Depending on your design philosophy and tube sources, some compromises in the cooling system may be appropriate. For example, if glass tubes are available inexpensively as broadcast pulls, a shorter life span may be acceptable. In such a case, an increase of convenience and a reduction in cost, noise, and complexity can be had by using a pair of "muffin" fans. One fan may be used for the filament seals and one for the anode seal, dispensing with a blower and air-system socket and chimney. The airflow with this scheme is not as uniform as with the use of a chimney. The tube envelope mounted in a cross flow has flow stagnation points and low heat transfer in certain regions of the envelope. These points become hotter than the rest of the envelope. The use of multiple fans to dis-



Fig 18.13—Anode compartment pressurization may be more efficient than grid compartment pressurization. Hot air exits upwards through the tube anode and through the chimney. Cool air also goes down through the tube socket to cool tube's pins and the socket itself.

turb the cross airflow can significantly reduce this problem. Many amateurs have used this cooling method successfully in low-duty-cycle CW and SSB operation but it is not recommended for AM, SSTV or RTTY service. The true test of the effectiveness of a forced air-cooling system is the amount of heat carried away from the tube by the air stream. The power dissipated can be calculated from the airflow temperatures. The dissipated power is

$$P_{\mathbf{D}} = Q_{\mathbf{A}} \left[\frac{T_2}{T_1} - 1 \right] \tag{41}$$

where

- P_D = the dissipated power, in W
- Q_A = the air flow, in CFM (cubic feet per minute)
- T₁ = the inlet air temperature, kelvin (normally quite close to room temperature)
- T_2 = the amplifier exhaust temperature, kelvin.

The exhaust temperature can be measured with a cooking thermometer at the air outlet. The thermometer should not be placed inside the anode compartment because of the high voltage present.

Transistor Cooling

Transistors used in power amplifiers dissipate significant amounts of power, and the heat so generated must be effectively removed to maintain acceptable device temperatures. Some bipolar power transistors have the collector connected directly to the case of the device, as the collector creates most of the heat generated when the transistor is in operation. Others have the emitter connected to the case. However, if operated close to maximum rated dissipation, even the larger

case designs cannot normally conduct heat away fast enough to keep the operating temperature of the device within the safe area-the maximum temperature that a device can stand without damage. Safe area is usually specified in a device data sheet, often in graphical form. Germanium power transistors theoretically may be operated at internal temperatures up to 100°C, while silicon devices may be run at up to 200°C. However, to assure long device lifetimes much lower case temperatures-not greater than 50° to 75°C for germanium and 75° to 100°C for silicon-are highly desirable. Leakage currents in germanium devices can be very high at elevated temperatures; thus, silicon transistors are preferred for most power applications.

A properly chosen heat sink often is essential to help keep the transistor junction temperature in the safe area. For lowpower applications a simple clip-on heat sink will suffice, while for 100 W or higher input power a massive cast-aluminum finned radiator usually is necessary. The appropriate size heat sink can be calculated based on the thermal resistance between the transistor case and ambient air temperature. The first step is to calculate the total power dissipated by the transistor:

$$P_{\rm D} = P_{\rm DC} + P_{\rm RFin} - P_{\rm RFout} \tag{42}$$

where

- P_D = the total power dissipated by the transistor in W
- P_{DC} = the dc power into the transistor, in W
- P_{RFin} = the RF (drive) power into the transistor in W
- P_{RFout} = the RF output power from the transistor in W.

The value of P_D is then used to obtain the θ_{CA} value from

$$\theta_{CA} = (T_C - T_A)/P_D \tag{43}$$

where

- θ_{CA} = the thermal resistance of the device case to ambient
- T_C = the device case temperature in °C T_A = the ambient temperature (room
- temperature) in °C.

A suitable heat sink, capable of transferring all of the heat generated by the transistor to the ambient air, can then be chosen from the manufacturer's specifications for θ_{CA} . A well-designed heat-sink system minimizes thermal path lengths and maximizes their cross-sectional areas. The contact area between the transistor and heat sink should have very low thermal resistance. The heat sink's mounting surface must be flat and the transistor firmly attached to the heat sink so intimate contact-without gaps or air voids-is made between the two. The use of silicone-based heat sink compounds can provide considerable improvement in thermal transfer. The thermal resistance of such grease is considerably lower than that of air, but not nearly as good as that of copper or aluminum. The quantity of grease should be kept to an absolute minimum. Only enough should be used to fill in any small air gaps between the transistor and heat sink mating surfaces. The maximum temperature rise in the transistor junction may easily be calculated by using the equation

$$T_{J} = (\theta_{JC} + \theta_{CA}) P_{D} + TA$$
(44)

where

- T_J = the transistor junction temperature in °C
- θ_{JC} = the manufacturer's published thermal resistance of the transistor

 θ_{CA} = the thermal resistance of the device case to ambient

- P_D = the power dissipated by the transistor
- T_A = the ambient temperature in °C.

The value of T_J should be kept well below the manufacturer's recommended maximum to prevent premature transistor failure. Measured values of the ambient temperature and the device case temperature can be used in the preceding formulas to calculate junction temperature. The **Real-World Component Characteristics** chapter contains a more detailed discussion of transistor cooling.

Most of the problems facing an amplifier designer are not theoretical, but have to do with real-world component limitations. The **Real World Component Characteristics** chapter discusses the differences between ideal and real components.

A simplified equivalent schematic of an amplifying device is shown in Fig 18.14A. The input is represented by a series (parasitic) inductance feeding a resistance in parallel with a capacitance. The output consists of a current generator in parallel with a resistance and capacitance, followed by a series inductance. This is a reasonably accurate description of both transistors and vacuum tubes, regardless of circuit configuration (as demonstrated in Figs 18.17B and C). Both input and output impedances have a resistive component in parallel with a reactive component. Each also has a series inductive reactance, which represents connecting leads within the device. These inductances, unlike the other components of input and output impedance, often are not characterized in manufacturers' device specifications.

The amplifier input and output-matching networks must transform the complex impedances of the amplifying device to the source and load impedances (often $50-\Omega$ transmission lines). Impedances associated with other parts of the amplifier circuit, such as a dc-supply choke, must also be considered in designing the matching networks. The matching networks and other circuit components are influenced by each other's presence, and these mutual effects must be given due consideration.

Perhaps the best way to clarify the considerations that enter into designing various types of RF power amplifiers is through example. The following examples illustrate common problems associated with power-amplifier design. They are not intended as detailed construction plans, but only demonstrate typical approaches useful in designing similar projects.

DESIGN EXAMPLE 1: A HIGH-POWER VACUUM-TUBE HF AMPLIFIER

Most popular HF transceivers produce approximately 100-W output. The EIMAC 8877 can deliver 1500-W output for approximately 60 W of drive when used in a grounded grid circuit. Grounded-grid operation is usually the easiest tube amplifier circuit to implement. Its input impedance is relatively low, often close to 50 Ω . Input/output shielding provided by the grid and negative feedback inherent in the grounded-grid circuit configuration reduce the likelihood of amplifier instability and provide excellent linearity without critical adjustments. Fewer supply voltages are needed in this configuration compared to others: Often just high-voltage dc for the plate and low-voltage ac for the filament.

The first step in the amplifier design process is to verify that the tube is actually capable of producing the desired results while remaining within manufacturer's ratings. The plate dissipation expected during normal operation of the amplifier is computed first. Since the amplifier will be used for SSB, a class of operation producing linear amplification must be used. Class AB2 provides a very good compromise between linearity and good efficiency, with effective efficiency typically exceeding 60%. Given that efficiency, an input power of 2500 W is needed to produce the desired 1500-W output. Operated under these conditions, the tube will dissipate about 1000 W-well within the manufacturer's specifications, provided



Fig 18.14—The electrical equivalents for power amplifiers. At A, the input is represented by a series stray inductance, then a resistor in parallel with a capacitor. The output is a current source in parallel with a resistor and capacitor, followed by a series stray inductance. These effects are applied to tubes and transistors in B and C.

adequate cooling airflow is supplied.

The grid in modern high-mu triodes is a relatively delicate structure, closely spaced to the cathode and carefully aligned to achieve high gain and excellent linearity. To avoid shortening tube life or even destruction of the tube, the specified maximum grid dissipation must not be exceeded for more than a few milliseconds under any conditions. For a given power output, the use of higher plate voltages tends to result in lower grid dissipation. It is important to use a plate voltage that is high enough to result in safe grid current levels at maximum output. In addition to maximum ratings, manufacturers' data sheets often provide one or more sets of "typical operation" parameters. This makes it even easier for the builder to achieve optimum results.

The 8877, operating at 3500 V, can produce 2075 W of RF output with excellent linearity and 64 W of drive. Operating at 2700 V it can deliver 1085 W with 40 W of drive. To some extent, the ease and cost of constructing a high-power amplifier, as well as its ultimate reliability, are enhanced by using the lowest plate voltage that will yield completely satisfactory performance. Interpolating between the two sets of typical operating conditions suggests that the 8877 can comfortably deliver 1.5 kW output with a 3100-V plate supply and 50 to 55 W of drive. Achieving 2500-W input power at this plate voltage requires 800 mA of plate current—well within the 8877's maximum rating of 1.0 A.

The next step in the design process is to calculate the optimum plate load resistance at this plate voltage and current for Class AB2 operation and design an appropriate output-matching network. From the earlier equations, R_L is calculated to be 2200 Ω .

Several different output networks might be used to transform the nominal 50- Ω resistance of the actual load to the 2200- Ω load resistance required by the 8877, but experience shows that pi and pi-L networks are most practical. Each can provide reasonable harmonic attenuation, is relatively easy to build mechanically and uses readily available components. The pi-L gives significantly greater harmonic attenuation than the pi and usually is the better choice-at least in areas where there is any potential for TVI or crossband interference. In a multiband amplifier, the extra cost of using a pi-L network is the "L" inductor and its associated bandswitch section.

To simplify and avoid confusion with terminology previously used in the pi and pi-L network design tables, in the remainder of this chapter Q_{IN} is the loaded Q of the amplifier's input matching tank, Q_{OUT} is the loaded Q of the output pi-L tank, Q_{PI} is the loaded Q of the output pi section only, and Q_L is the loaded Q of the output L section only.

The input impedance of a grounded-grid 8877 is typically on the order of 50 to 55 Ω , shunted by input capacitance of about 38 pF. While this average impedance is close enough to 50 Ω to provide negligible input SWR, the instantaneous value varies greatly over the drive cyclethat is, it is nonlinear. This nonlinear impedance is reflected back as a nonlinear load impedance at the exciter output, resulting in increased intermodulation distortion, reduced output power, and often meaningless exciter SWR meter indications. In addition, the tube's parallel input capacitance, as well as parasitic circuit reactances, often are significant enough at 28 MHz to create significant SWR. A tank circuit at the amplifier input can solve both of these problems by tuning out the stray reactances and stabilizing (linearizing) the tube input impedance through its flywheel effect. The input tank should have a loaded Q (called Q_{Lin} in this discussion) of at least two for good results. Increasing Q_{Lin} to as much as five results in a further

small improvement in linearity and distortion, but at the cost of a narrower operating bandwidth. Even a Q_{Lin} of 1.0 to 1.5 yields significant improvement over an untuned input. A pi network commonly is used for input matching at HF.

Fig 18.15 illustrates these input and output networks applied in the amplifier circuit. The schematic shows the major components in the amplifier RF section, but with band-switching and cathode dcreturn circuits omitted for clarity. C1 and C2 and L1 form the input pi network. C3 is a blocking capacitor to isolate the exciter from the cathode dc potential. Note that when the tube's average input resistance is close to 50 Ω , as in the case of the 8877, a simple parallel-resonant tank often can successfully perform the tuning and flywheel functions, since no impedance transformation is necessary. In this case it is important to minimize stray lead inductance between the tank and tube to avoid undesired impedance transformation.

The filament or "heater" in indirectly heated tubes such as the 8877 must be very close to the cathode to heat the cathode efficiently. A capacitance of several picofarads exists between the two. Particularly at very high frequencies, where these few picofarads represent a relatively low reactance, RF drive intended for the cathode can be capacitively coupled to the lossy filament and dissipated as heat. To avoid this, above about 50 MHz, the filament must be kept at a high RF impedance above ground. The high impedance (represented by choke RFC1 in Fig 18.15) minimizes RF current flow in the filament circuit so that RF dissipated in the filament becomes negligible. The choke's low-frequency resistance should be kept to a minimum to lessen voltage drops in the high-current filament circuit.

The choke most commonly used in this application is a pair of heavy-gauge insulated wires, bifilar-wound over a ferrite rod. The ferrite core raises the inductive reactance throughout the HF region so that a minimum of wire is needed, keeping filament-circuit voltage drops low. The bifilar winding technique assures that both filament terminals are at the same RF potential.

Below 30 MHz, the use of such a choke seldom is necessary or beneficial, but actually can introduce another potential problem. Common values of cathode-to-heater capacitance and heater-choke inductance often are series resonant in the 1.8 to 29.7 MHz HF range. A capacitance of 5 pF and an inductance of 50 μ H, for example, resonate at 10.0 MHz; the actual components are just as likely to resonate near 7 or 14 MHz. At resonance, the cir-

cuit constitutes a relatively low impedance shunt from cathode to ground, which affects input impedance and sucks out drive signal. An unintended resonance like this near any operating frequency usually increases input SWR and decreases gain on that one particular band. While aggravating, the problem rarely completely disables or damages the amplifier, and so is seldom pursued or identified.

Fortunately, the entire problem is easily avoided-below 30 MHz the heater choke can be deleted. At VHF-UHF, or wherever a heater isolation choke is used for any reason, the resonance can be moved below the lowest operating frequency by connecting a sufficiently large capacitance (about 1000 pF) between the tube cathode and one side of the heater. It is good practice also to connect a similar capacitor between the heater terminals. It also would be good practice in designing other VHF/UHF amplifiers, such as those using 3CX800A7 tubes, unless the builder can ensure that the actual series resonance is well outside of the operating frequency range.

Plate voltage is supplied to the tube through RFC2. C5 is the plate blocking capacitor. The output pi-L network consists of tuning capacitor C6, loading capacitor C7, pi coil L2, and output L coil L3. RFC3 is a high-inductance RF choke placed at the output for safety purposes. Its value, usually 100 µH to 2 mH, is high enough so that it appears as an open circuit across the output connector for RF. However, should the plate blocking capacitor fail and allow high voltage onto the output matching network, RFC3 would short the dc to ground and blow the power-supply fuse or breaker. This prevents dangerous high voltage from appearing on the feed line or antenna. It also prevents electrostatic charge-from the antenna or from blocking capacitor leakage-from building up on the tank capacitors and causing periodic dc discharge arcs to ground. If such a dc discharge occurs while the amplifier is transmitting, it can trigger a potentially damaging RF arc.

Our next step is designing the input matching network. As stated earlier, tube input impedance varies moderately with plate voltage and load resistance as well as bias, but is approximately 50 to 55 Ω paralleled by C_{IN} of 38 pF, including stray capacitance. A simple parallel-resonant tank of Q_{IN} = 2 to 3 can provide an input SWR not exceeding 1.5:1, provided all



Fig 18.15—A simplified schematic of a grounded-grid amplifier using a pi network input and pi-L network output.

wiring from RF input connector to tank to cathode is heavy and short. On each band a Q_{IN} between 2 to 3 requires an $X_{Ctot} = X_{Lin}$ between 25 and 17 Ω .

A more nearly perfect match, with greater tolerance for layout and wiring variations, may be achieved by using the pi input tank as shown in Fig 18.15. Design of this input-matching circuit is straightforward. Component values are computed using a Q_{IN} between 2 or 3. Higher Q_{IN} values reduce the network's bandwidth, perhaps even requiring a frontpanel tuning control for the wider amateur bands. The purpose of this input network is to present the desired input impedance to the exciter, not to add selectivity. As with a parallel tank, the value of the capacitor at the tube end of the pi network should be reduced by 38 pF; stray capacity plus tube C_{IN} is effectively in parallel with the input pi network's output.

The output pi-L network must transform the nominal 50- Ω amplifier load to a pure resistance of 2200 Ω . We previously calculated that the 8877 tube's plate must see $2200 \,\Omega$ for optimum performance. In practice, real antenna loads are seldom purely resistive or exactly 50 Ω ; they often exhibit SWRs of 2:1 or greater on some frequencies. It's desirable that the amplifier output network be able to transform any complex load impedance corresponding to an SWR up to about 2:1 into a resistance of 2200 Ω . The network also must compensate for tube C_{OUT} and other stray plate-circuit reactances, such as those of interconnecting leads and the plate RF choke. These reactances, shown in Fig 18.16, must be taken into account when designing the matching networks. Because the values of most stray reactances are not accurately known, the most satisfactory approach is to estimate them, and then allow sufficient flexibility in the matching network to accommodate modest errors.

Fig 18.16 shows the principal reactances in the amplifier circuit. COUT is the actual tube output capacitance of 10 pF plus the stray capacitance between its anode and the enclosure metalwork. This stray C varies with layout; we will approximate it as 5 pF, so C_{OUT} is roughly 15 pF. L_{OUT} is the stray inductance of leads from the tube plate to the tuning capacitor (internal to the tube as well as external circuit wiring.) External-anode tubes like the 8877 have essentially no internal plate leads, so L_{OUT} is almost entirely external. It seldom exceeds about 0.3 mH and is not very significant below 30 MHz. L_{CHOKE} is the reactance presented by the plate choke, which usually is significant only below 7 MHz. C_{STRAY}

represents the combined stray capacitances to ground of the tuning capacitor stator and of interconnecting RF plate circuit leads. In a well-constructed, carefully thought out power amplifier, C_{STRAY} can be estimated to be approximately 10 pF. Remaining components C_{TUNE} , C_{LOAD} , and the two tuning inductors, form the pi-L network proper.

The tables presented earlier in this chapter greatly simplify the task of selecting output circuit values. Both the pi and pi-L design tables are calculated for a QOUT value of 12. A pi network loaded Q much lower than 10 does not provide adequate harmonic suppression; a value much higher than 15 increases matching network losses caused by high circulating currents. For pi networks, a Q_{OUT} of 12 is a good compromise between harmonic suppression and circuit losses. In practice, it often is most realistic and practical with both pi and pi-L output networks to accept somewhat higher Q_{OUT} values on the highest HF frequencies-perhaps as large as 18 or even 20 at 28 MHz. When using a pi-L on the 1.8 and 3.5 MHz bands, it often is desirable to choose a moderately lower Q_{OUT}, perhaps 8 to 10, to permit using a more reasonably-sized plate tuning capacitor.

Nominal pi-L network component values for 2200- Ω plate impedance can be taken directly from Table 18.2. These values can then be adjusted to allow for circuit reactances outside the pi-L proper. First, low-frequency component values should be examined. At 3.5 MHz, total tuning capacitance C1 value from Table 18.2 is 140 pF. From Fig 18.16 we know that three other stray reactances are directly in parallel with C_{TUNE} (assuming that L_{OUT} is negligible at the operating frequency, as it should be). The tube's internal and external plate capacitance to ground, C_{OUT}, is about 15 pF. Strays in the RF circuit, C_{STRAY}, are roughly 10 pF.

Plate chokes with self-resonance characteristics suitable for use in amateur HF amplifiers typically have inductances of about 90 μ H. At 3.5 MHz this is an inductive reactance of +1979 Ω . This appears in parallel with the tuning capacitance, effectively canceling an equal value of capacitive reactance. At 3.5 MHz, an X_C of 1979 Ω corresponds to 23 pF of capacitance—the amount by which tuning capacitor C_{TUNE} must be increased at 3.5 MHz to compensate for the effect of the plate choke.

X_{CHOKE}, is also in parallel with C_{TUNE}.

The pi-L network requires an effective capacitance of 140 pF at its input at 3.5 MHz. Subtracting the 25 pF provided by C_{OUT} and C_{STRAY} and adding the 23 pF canceled by X_{CHOKE}, the actual value of C_{TUNE} must be 140 - 25 + 23 = 138 pF. It is good practice to provide at least 10% extra capacitance range to allow matching loads having SWRs up to 2:1. So, if 3.5 MHz is the lower frequency limit of the amplifier, a variable tuning capacitor with a maximum value of at least 150 to 160 pF should be used.

Component values for the high end of the amplifier frequency range also must be examined, for this is where the most losses will occur. At 29.7 MHz, the values in Table 18.2 are chosen to accommodate a minimum pi-L input capacitance of 35 pF, yielding $Q_{OUT} = 21.3$. Since C_{OUT} and CSTRAY contribute 25 pF, CTUNE must have a minimum value no greater than 10 pF. A problem exists, because this value is not readily achievable with a 150 to 160-pF air variable capacitor suitable for operation with a 3100 V plate supply. Such a capacitor typically has a minimum capacitance of 25 to 30 pF. Usually, little or nothing can be done to reduce the tube's C_{OUT} or the circuit C_{STRAY}, and in fact the estimates of these may even be a little low. If 1.8 MHz capability is desired, the maximum tuning capacitance will be at least 200 to 250 pF, making the minimum-

The impedance of the plate choke,



Fig 18.16—The effective reactances for the amplifier in Fig 18.15.

capacitance problem at 29.7 MHz even more severe.

There are three potential solutions to this dilemma. We could accept the actual minimum value of pi-L input capacitance, around 50 to 55 pF, realizing that this will raise the pi-L network's loaded Q to about 32. This results in very large values of circulating tank current. To avoid damage to tank components—particularly the bandswitch and pi inductor—from heat due to I²R losses, it will be necessary to either use oversize components or reduce power on the highest-frequency bands. Neither option is appealing.

A second potential solution is to reduce the minimum capacitance provided by C_{TUNE}. We could use a vacuum variable capacitor with a 300-pF maximum and a 5-pF minimum capacity. These are rated at 5 to 15 kV, and are readily available. This reduces the minimum effective circuit capacitance to 30 pF, allowing use of the pi-L table values for $Q_{OUT} = 12$ on all bands from 1.8 through 29.7 MHz. While brand-new vacuum variables are quite expensive, suitable models are widely available in the surplus and used markets for prices not much higher than the cost of a new air variable. A most important caveat in purchasing a vacuum capacitor is to ensure that its vacuum seal is intact and that it is not damaged in any way. The best way to accomplish this is to "hi-pot" test the capacitor throughout its range, using a dc or peak ac test voltage of 1.5 to 2 times the amplifier plate supply voltage. For all-band amplifiers using plate voltages in excess of about 2500 V, the initial expense and effort of securing and using a vacuum-variable input tuning capacitor often is well repaid in efficient and reliable operation of the amplifier.

A third possibility is the use of an additional inductance connected in series between the tube and the tuning capacitor. In conjunction with C_{OUT} of the tube, the added inductor acts as an L network to transform the impedance at the input of the pi-L network up to the 2200- Ω load resistance needed by the tube. This is shown in **Fig 18.17A**. Since the impedance at the input of the main pi-L matching network is reduced, the loaded Q_{OUT} for the total capacitance actually in the circuit is lower. With lower Q_{OUT} , the circulating RF currents are lower, and thus tank losses are lower.

 C_{OUT} in Fig 18.17 is the output capacitance of the tube, including stray C from the anode to metal enclosure. X_L is the additional series inductance to be added. As determined previously, the impedance seen by the tube anode must be a 2200 Ω resistance for best linearity and efficiency, and we have estimated C+ of the tube as 15 pF. If the network consisting of C_{OUT} and X_L is terminated at A by 2200 Ω , we can calculate the equivalent impedance at point B, the input to the pi-L network, for various values of series X_L . The pi-L network must then transform the nominal 50- Ω load at the transmitter output to this equivalent impedance.

We work backwards from the plate of the tube towards the $\mathrm{C}_{\mathrm{TUNE}}$ capacitor. First, calculate the series-equivalent impedance of the parallel combination of the desired 2200- Ω plate load and the tube X_{OUT} $(15 \text{ pF at } 29.7 \text{ MHz} = -j 357 \Omega)$. The seriesequivalent impedance of this parallel combination is $56.5 - i 348 \Omega$, as shown in Fig 18.17B. Now suppose we use a 0.5 μ H inductor, having an impedance of $+ j 93 \Omega$ at 29.7 MHz, as the series inductance X_I. The resulting series-equivalent impedance is $56.5 - j \ 348 + j \ 93$, or $56.5 - j \ 255 \ \Omega$. Converting back to the parallel equivalent gives the network of Fig 18.17C: 1205 Ω resistance in parallel with -j 267 Ω , or 20 pF at 29.7 MHz. The pi-L tuning network must now transform the 50- Ω load to a resistive load of 1205 Ω at B, and absorb the shunt capacity of 20 pF.

Using the pi-L network formulas in this chapter for R1 = 1205 Ω and Q_{OUT} = 15 at 29.7 MHz yields a required total capacitive reactance of $1205/15 = 80.3 \Omega$, which is 66.7 pF at 29.7 MHz. Note that for the same loaded Q_{OUT} for a 2200- Ω load line without the series inductor, the capacitive reactance is $2200/15 = 146.7 \ \Omega$, which is 36.5 pF. When the 20 pF of transformed input capacity is subtracted from the 66.7 pF total needed, the amount of capacity is 46.7 pF. If the minimum capacity in $C_{\ensuremath{\text{TUNE}}}$ is 25 pF and the stray capacity is 10 pF, then there is a margin of 46.7 - 35 =10.7 pF beyond the minimum capacity for handling SWRs greater than 1:1 at the load.

The series inductor should be a high-Q coil wound from copper tubing to keep losses low. This inductor has a decreasing, yet significant effect, on progressively lower frequencies. A similar calculation to the above should be made on each band to determine the transformed equivalent plate impedance, before referring to Table 18.2. The impedance-transformation effect of the additional inductor decreases rapidly with decreasing frequency. Below 21 MHz, it usually may be ignored and pi-L network values taken directly from the pi-L tables for R1 = 2200 Ω .

The nominal 90- μ H plate choke remains in parallel with C_{TUNE}. It is rarely possible to calculate the impedance of a real HF plate choke at frequencies higher than about 5 MHz because of self-resonances. However, as mentioned previously, the choke's reactance should be sufficiently high that the tables are useful if the choke's first series-resonance is at 23.2 MHz.

This amplifier is made operational on multiple bands by changing the values of inductance at L2 and L3 for different bands. The usual practice is to use inductors for the lowest operating frequency, and short out part of each inductor with a switch, as necessary, to provide the inductance needed for each individual band. Wiring to the switch and the switch itself add stray inductance and capacitance to the circuit. To minimize these effects at the higher frequencies, the unswitched 10-m L2 should be placed closest to the high-impedance end of the network at C6.



Fig 18.17—The effect of adding a small series inductance in vacuum tube output circuit. At A, a 0.5- μ H coil L_{SERIES} is connected between anode and the output pi network, and this represents a reactance of + j 93 Ω at 29.7 MHz. The 15-pF output capacity (C_{OUT}) of the tube has a reactance of -j 357 Ω at 29.7 MHz. At B, the equivalent series network for the parallel 2200-Ω desired load resistance and the – j 357 Ω C_{OUT} is 56.5 Ω in series with - j 348 Ω. At Č, this seriesequivalent is combined with the series + j 93 Ω X_{SERIES} and converted back to the parallel equivalent, netting an equivalent parallel network of 1205 Ω shunted by a 20-pF capacitor. The pi tuning network must transform the load impedance (usually 50 Ω) into the equivalent parallel combination and absorb the 20-pF parallel component. The series inductor has less effect as the operating frequency is lowered from 29.7 MHz.

Stray capacitance associated with the switch then is effectively in parallel with C7, where the impedance level is around 300 Ω . The effects of stray capacitance are relatively insignificant at this low impedance level. This configuration also minimizes the peak RF voltage that the switch insulation must withstand.

Pi and L coil tap positions that yield desired values of inductance may be determined with fairly good accuracy by using a dip meter and a small mica capacitor of 5% tolerance. The pi and L coils and bandswitch should be mounted in the amplifier and their common point connected only to the bandswitch rotors. Starting at the highest-frequency switch position, lightly tack solder a short length of copper braid or strap to the pi or L switch stator terminal for that band. Using the shortest leads possible, tack a 50 to 100 pF, 5% dipped mica capacitor between the braid and a trial tap position on the appropriate coil. Lightly couple the dip meter and find the resonant frequency. The inductance then may be calculated from the equation

$$L = \frac{1,000,000}{(2\pi f)^2 C}$$
(45)

where

 $L = inductance in \mu H$

C = capacitor value in pF

f = resonant frequency in MHz.

As each tap is located, it should be securely wired with strap or braid and the process repeated for successively lower bands.

The impedance match in both the input and output networks can be checked without applying dc voltage, once the amplifier is built. In operation, the tube input and output resistances are the result of current flow through the tube. Without filament power applied, these resistances are effectively infinite but CIN and COUT are still present because they are passive physical properties of the tube. The tube input resistance can be simulated by an ordinary 5% 1/4-W to 2-W composition or film resistor (don't use wirewound, though; they are more inductive than resistive at RF). A resistor value within 10% of the tube input resistance, connected in parallel with the tube input, presents approximately the same termination resistance to the matching network as the tube does in operation.

With the input termination resistor temporarily soldered in place using very short leads, input matching network performance can be determined by means of a noise bridge or an SWR meter that does not put out more RF power than the temporary termination resistor is capable of dissipating. Any good self- or dipper-powered bridge or analyzer should be satisfactory. Connect the bridge to the amplifier input and adjust the matching network, as necessary, for lowest SWR. Be sure to remove the terminating resistor before powering up the amplifier!

The output matching network can be evaluated in exactly the same fashion, even though the plate load resistance is not an actual resistance in the tube like the input resistance. According to the reciprocity principle, if the impedance presented at the output of the plate matching network is 50- Ω resistive when the network input is terminated with R_L, then the tube plate will "see" a resistive load equal to R_{I} at the input when the output is terminated in a 50- Ω resistance (and vice versa). In this case, a suitable $2200-\Omega$ resistor should be connected as directly as possible from the tube plate to chassis. If the distance is more than a couple of inches, braid should be used to minimize stray inductance. The bridge is connected to the amplifier output. If coil taps have been already been established as described previously, it is a simple matter to evaluate the output network by adjusting the tune and load capacitors, band by band, to show a perfect 50- Ω match on the SWR bridge.

When these tests are complete, the amplifier is ready to be tested for parasitic oscillations in preparation for full-power operation. Refer to Amplifier Stabilization, later in this chapter.

DESIGN EXAMPLE 2: A MEDIUM-POWER 144-MHZ AMPLIFIER

For decades the 4CX250 family of power tetrodes has been used successfully up through 500 MHz. They are relatively inexpensive, produce high gain and lend themselves to relatively simple amplifier designs. In amateur service at VHF, the 4CX250 is an attractive choice for an amplifier. Most VHF exciters used now by amateurs are solid state and often develop 10 W or less output. The drive requirement for the 4CX250 in grounded cathode, Class AB operation ranges between 2 and 8 W for full power output, depending on frequency. At 144 MHz, manufacturer's specifications suggest an available output power of over 300 W. This is clearly a substantial improvement over 10 W, so a 4CX250B will be used in this amplifier.

The first design step is the same as in the previous example: Verify that the proposed tube will perform as desired while staying within the manufacturer's ratings. Again assuming a basic amplifier efficiency of 60% for Class AB operation, 300 W of output requires a plate input power of 500 W. Tube dissipation is rated at 250 W, so plate dissipation is not a problem, as the tube will only be dissipating 200 W in this amplifier. If the recommended maximum plate potential of 2000 V is used, the plate current for 500-W input will be 250 mA, which is within the manufacturer's ratings. The plate load resistance can now be calculated. Using the same formula as before, the value is determined to be 5333 Ω .

The next step is to investigate the output circuit. The manufacturer's specification for C_{OUT} is 4.7 pF. The inevitable circuit strays along with the tuning capacitor add to the circuit capacitance. A carefully built amplifier might only have 7 pF of stray capacitance, and a specially made tuning capacitor can be fabricated to have a midrange value of 3 pF. The total circuit capacitance adds up to about 15 pF. At 144 MHz this represents a capacitive reactance of only 74 Ω . The Q_L of a tank circuit with this reactance with a plate load resistance of 5333 Ω is 5333/74 = 72. A pi output matching network would be totally impractical, because the L required would be extremely small and circuit losses would be prohibitive. The simplest solution is to connect an inductor in parallel with the circuit capacitance to form a parallel-resonant tank circuit.

To keep tank circuit losses low with such a high Q_L , an inductor with very high unloaded Q must be used. The lowest-loss inductors are formed from transmission-line sections. These can take the form of either coaxial lines or strip lines. Both have their advantages and disadvantages, but the strip line is so much easier to fabricate that it is almost exclusively used in VHF tank circuits today.

The reactance of a terminated transmission line section is a function of both its characteristic impedance and its length (see the **Transmission Lines** chapter). The reactance of a line terminated in a short circuit is

$$X_{IN} = Z_0 \tan \ell \tag{46}$$

where

 X_{IN} = is the circuit reactance

 Z_0 = the line's characteristic impedance ℓ = the transmission line length in degrees.

For lines shorter than a quarter wavelength (90°) the circuit reactance is inductive. In order to resonate with the tank-circuit capacitive reactance, the transmission-line reactance must be the same value, but inductive. Examination of the formula for transmission-line circuit reactance suggests that a wide range of

lengths can yield the same inductive reactance, so long as the line Z_0 is appropriately scaled. Based on circuit Q considerations, the best bandwidth for a tank circuit results when the ratio of Z_0 to X_{IN} is between one and two. This implies that transmission line lengths between 26.5° and 45° give the best bandwidth. Between these two limits, and with some adjustment of Z_0 , practical transmission lines can be designed. A transmission-line length of 35° is 8 inches long at 144 MHz, a workable dimension mechanically. Substitution of this value into the transmission-line equation gives a Z_0 of 105 Ω .

The width of the strip line and its placement relative to the ground planes determine the line impedance. Other stray capacitances such as mounting standoffs also affect the impedance. Accurate calculation of the line impedance for most physical configurations requires extensive application of Maxwell's equations and is beyond the scope of this book. The specialized case in which the strip line is parallel to and located halfway between two ground planes has been documented in Reference Data for Radio Engineers (see Bibliography). According to charts presented in that book, a 105- Ω strip line impedance is obtained by placing a line with a width of approximately 0.4 times the ground plane separation halfway between the ground planes. Assuming the use of a standard 3-inch-deep chassis for the plate compartment, this yields a stripline width of 1.2 inches. A strip line 1.2 inches wide located 1.5 inches above the chassis floor and grounded at one end has an inductive reactance of 74 Ω at 144 MHz.

The resulting amplifier schematic diagram is shown in **Fig 18.18**. L2 is the stripline inductance just described. C3 is the tuning capacitor, made from two parallel brass plates whose spacing is adjustable. One plate is connected directly to the strip line while the other is connected to ground through a wide, low-inductance strap. C2 is the plate blocking capacitor. This can be either a ceramic doorknob capacitor such as the Centralab 850 series or a homemade "Teflon sandwich." Both are equally effective at 144 MHz.

Impedance matching from the plate resistance down to 50 Ω can be either through an inductive link or through capacitive reactance matching. Mechanically, the capacitive approach is simpler to implement. **Fig 18.19** shows the development of reactance matching through a series capacitor (C4 in Fig 18.19). By using the parallel equivalent of the capacitor in series with the 50- Ω load, the load resistance can be transformed to the 5333- Ω plate resistance. Substitution of the known values into the parallel-toseries equivalence formulas reveals that a 2.15 pF capacitor at C4 matches the 50- Ω load to the plate resistance. The resulting parallel equivalent for the load is 5333 Ω in parallel with 2.13 pF. The 2.13-pF capacitor is effectively in parallel with the tank circuit.

A new plate line length must now be calculated to allow for the additional capacitance. The equivalent circuit diagram containing all the various reactances is shown in **Fig 18.20**. The total circuit capacitance is now just over 17 pF, which is a reactance of 64 Ω . Keeping the stripline width and thus its impedance constant at 105 Ω dictates a new resonant line length of 31°. This calculates to be 7.14 inches for 144 MHz.

The alternative coupling scheme is through the use of an inductive link. The link can be either tuned or untuned. The length of the link can be estimated based on the amplifier output impedance, in this case, 50 Ω . For an untuned link, the inductive reactance of the link itself should be approximately equal to the output impedance, 50 Ω . For a tuned link, the length depends on the link loaded Q, Q_L. The link Q_L should generally be greater than two, but usually less than five. For a Q_L of three this implies a capacitive reactance of 150 Ω , which at 144 MHz is just over 7 pF. The self-inductance of the link should of course be such that its impedance at 144 MHz is 150 Ω (0.166 mH). Adjustment of the link placement determines the transformation ratio of the circuit line. Some fine adjustment of this parameter can be made through adjustment of the link series tuning capacitor. Placement of the link relative to the plate inductor is an empirical process.

The input circuit is shown in Figs 18.21 and 18.23. C_{IN} is specified to be 18.5 pF for the 4CX250. This is only -j 60 Ω at 2 m, so the pi network again is unsuitable. Since a surplus of drive is available with a 10-W exciter, circuit losses at the amplifier input are not as important as at the output. An old-fashioned "split-stator" tuned input can be used. L1 in Fig 18.18 is series tuned by C_{IN} and C1. The two capacitors are effectively in series (through the ground return). A 20-pF variable at C1 set to 18.5 pF gives an effective circuit capacitance of 9.25 pF. This will resonate at 144 MHz with an inductance of 0.13 µH at L1. L1 can be wound on a toroid core for mechanical convenience. The 50- Ω input impedance is then matched by link coupling to the toroid. The grid impedance is primarily determined by the value for R1, the grid bias feed resistor.

DESIGN EXAMPLE 3: A BROADBAND HF SOLID-STATE AMPLIFIER

Linear power-amplifier design using transistors at HF is a fundamentally simple process, although a good understanding of application techniques is important to insure that the devices are effectively protected against damage or destruction due to parasitic self-oscillations, power transients, load mismatch and/or overdrive.



Fig 18.19—Series reactance matching as applied to the amplifier in Fig 18.18.



Fig 18.18—Simplified schematic for a VHF power amplifier using a power tetrode. The output circuit is a parallel-tuned tank circuit with series capacitive-reactance output matching.



Fig 18.20—The reactances and resistances for the amplifier in Fig 18.18.



Fig 18.21—A simplified schematic of a broadband HF transistorized power amplifier. T1 and T2 are 4:1 broadband transformers to match the low input impedance of the transistor.

An appropriate transistor meeting the desired performance specifications is selected on the basis of dissipation and power output. Transistor manufacturers greatly simplify the design by specifying each type of power transistor according to its frequency range and power output. The amplifier designer need only provide suitable impedance matching to the device input and output, along with appropriate dc bias currents to the transistor.

The Motorola MRF464 is an RF power transistor capable of 80 W PEP output with low distortion. Its usable frequency range extends through 30 MHz. At a collector potential of 28 V, a collector efficiency of 40% is possible. Fig 18.21 shows the schematic diagram of a 2 to 30-MHz broadband linear amplifier using the MRF464. The input impedance of the transistor is specified by the manufacturer to be 1.4 -j 0.30 Ω at 30 MHz and increases to 9.0 -j 5.40 Ω at 2 MHz. Transformers T1 and T2 match the 50- Ω amplifier input impedance to the median value of the transistor input impedance. They are both 4:1 stepdown ratio transmission-line transformers. A single 16:1 transformer could be used in place of T1 and T2, but 16:1 transformers are more difficult to fabricate for broadband service.

The specified transistor load impedance is approximately 6 Ω (in parallel with a corresponding output capacitance) across the frequency range. T3 is a ferrite-loaded conventional transformer with a step-up ratio of approximately 8:1. This matches the transistor output to 50 Ω .

The amplifier has a falling gain characteristic with rising frequency. To flatten out gain across the frequency range, negative feedback could be applied. However, most power transistors have highly reactive input impedances and large phase errors would occur in the feedback loop. Instability could potentially occur.

A better solution is to use an input correction network. This network is used as a frequency-selective attenuator for amplifier drive. At 30 MHz, where transistor gain is least, the input power loss is designed to be minimal (less than 2 dB). The loss increases at lower frequencies to compensate for the increased transistor gain. The MRF464 has approximately 12 dB more gain at 1.8 MHz than at 30 MHz; the compensation network is designed to have 12 dB loss at 1.8 MHz. A properly designed compensation network will result in an overall gain flatness of approximately 1 dB.

AMPLIFIER STABILIZATION Stable Operating Conditions

Purity of emissions and the useful life (or even survival) of the active devices in a tube or transistor circuit depend heavily on stability during operation. Oscillations can occur at the operating frequency or far from it, because of undesired positive feedback in the amplifier. Unchecked, these oscillations pollute the RF spectrum and can lead to tube or transistor over-dissipation and subsequent failure. Each type of oscillation has its own cause and its own cure.

In a linear amplifier, the input and output circuits operate on the same frequency. Unless the coupling between these two circuits is kept to a small enough value, sufficient energy from the output may be coupled in phase back to the input to cause the amplifier to oscillate. Care should be used in arranging components and wiring of the two circuits so that there will be negligible opportunity for coupling external to the tube or transistor itself. A high degree of shielding between input and output circuits usually is required. All RF leads should be kept as short as possible and particular attention should be paid to the RF return paths from input and output tank circuits to emitter or cathode.

In general, the best arrangement using a tube is one in which the input and output circuits are on opposite sides of the chassis. Individual shielded compartments for the input and output circuitry add to the isolation. Transistor circuits are somewhat more forgiving, since all the impedances are relatively low. However, the high currents found on most amplifier circuit boards can easily couple into unintended circuits. Proper layout, the use of double-sided circuit board (with one side used as a ground plane and low-inductance ground return), and heavy doses of bypassing on the dc supply lines often are sufficient to prevent many solid-state amplifiers from oscillating.

VHF and UHF Parasitic Oscillations

RF power amplifier circuits contain parasitic reactances that have the potential to cause so-called parasitic oscillations at frequencies far above the normal operating frequency. Nearly all vacuum-tube amplifiers designed for operation in the 1.8 to 29.7-MHz frequency range exhibit tendencies to oscillate somewhere in the VHF-UHF range—generally between about 75 and 250 MHz depending on the type and size of tube. A typical parasitic resonant circuit is highlighted by bold lines in **Fig 18.22**. Stray inductance between the tube plate and the output tuning capacitor forms a high-Q resonant circuit with the tube's C_{OUT} . C_{OUT} normally is much smaller (higher X_C) than any of the other circuit capacitances shown. The tube's C_{IN} and the tuning capacitor C_{TUNE} essentially act as bypass capacitors, while the various chokes and tank inductances shown have high reactances at VHF. Thus the values of these components have little influence on the parasitic resonant frequency.

Oscillation is possible because the VHF resonant circuit is an inherently high-Q parallel-resonant tank that is not coupled to the external load. The load resistance at the plate is very high, and thus the voltage gain at the parasitic frequency can be quite high, leading to oscillation. The parasitic frequency, f_r , is approximately:

$$f_r = \frac{1000}{2\pi\sqrt{L_P C_{OUT}}}$$
(47)

where

 f_r = parasitic resonant frequency in MHz L_p = total stray inductance between tube plate and ground via the plate tuning capacitor (including tube internal plate lead) in μ H

 C_{OUT} = tube output capacitance in pF.

In a well-designed HF amplifier, L_P might be in the area of 0.2 μ H and C_{OUT} for an 8877 is about 10 pF. Using these figures, the equation above yields a potential parasitic resonant frequency of

$$f_r = \frac{1000}{2\pi\sqrt{0.2 \times 10}} = 112.5 \text{ MHz}$$

For a smaller tube, such as the 3CX800A7 with C_{OUT} of 6 pF, $f_r = 145$ MHz. Circuit details affect f_r somewhat, but these results do in fact correspond closely to actual parasitic oscillations experienced with these tube types. VHF-UHF parasitic oscillations can be prevented (*not* just minimized!) by reducing the loaded Q of the parasitic resonant circuit so that gain at its resonant frequency is insufficient to support oscillation. This is possible with any common tube, and it is especially easy with modern external-anode tubes like the 8877, 3CX800A7, and 4CX800A.

Z1 of Fig 18.22B is a parasitic suppressor. Its purpose is to add loss to the parasitic circuit and reduce its Q enough to prevent oscillation. This must be accomplished without significantly affecting normal operation. L_z should be just large enough to constitute a significant part of the total parasitic tank inductance (origi-

nally represented by L_P), and located right at the tube plate terminal(s). If L_z is made quite lossy, it will reduce the Q of the parasitic circuit as desired.

The inductance and construction of L_z depend substantially on the type of tube used. Popular glass tubes like the 3-500Z and 4-1000A have internal plate leads made of wire. This significantly increases L_P when compared to external-anode tubes. Consequently, $\boldsymbol{L}_{\boldsymbol{z}}$ for these large glass tubes usually must be larger in order to constitute an adequate portion of the total value of L_P. Typically a coil of 3 to 5 turns of #10 wire, 0.25 to 0.5 inches in diameter and about 0.5 to 1 inches long is sufficient. For the 8877 and similar tubes it usually is convenient to form a "horseshoe" in the strap used to make the plate connection. A "U" about 1 inch wide and 0.75 to 1 inch deep usually is sufficient. In either case, L_z carries the full operatingfrequency plate current; at the higher frequencies this often includes a substantial amount of circulating tank current, and Lz must be husky enough to handle it without overheating even at 29 MHz.

Regardless of the form of L_z , loss may

be introduced as required by shunting L_z with one or more suitable noninductive resistors. In high-power amplifiers, two composition or metal film resistors, each 100 Ω , 2 W, connected in parallel across L_z usually are adequate. For amplifiers up to perhaps 500 W a single 47-Ω, 2-W resistor may suffice. The resistance and power capability required to prevent VHF/ UHF parasitic oscillations, while not overheating as a result of normal plate circuit current flow, depend on circuit parameters. Operating-frequency voltage drop across Lz is greatest at higher frequencies, so it is important to use the minimum necessary value of L_z in order to minimize power dissipation in R_{z} .

The parasitic suppressors described above very often will work without modification, but in some cases it will be necessary to experiment with both L_z and R_z to find a suitable combination. Some designers use nichrome or other resistance wire for L_z .

In exceptionally difficult cases, particularly when using glass tetrodes or pentodes, additional parasitic suppression may be attained by connecting a low value



Fig 18.22—At A, typical VHF/UHF parasitic resonance in plate circuit. The HF tuning inductor in the pi network looks like an RF choke at VHF/UHF. The tube's output capacity and series stray inductance combine with the pi-network tuning capacity and stray circuit capacity to create a VHF/UHF pi network, presenting a very high impedance to the plate, increasing its gain at VHF/UHF. At B, Z1 lowers the Q and therefore gain at parasitic frequency.

resistor (about 10 to 15 Ω) in series with the tube input, near the tube socket. This is illustrated by R1 of Fig 18.22B. If the tube has a relatively low input impedance, as is typical of grounded-grid amplifiers and some grounded-cathode tubes with large C_{IN}, R1 may dissipate a significant portion of the total drive power.

Testing Tube Amplifiers for VHF-UHF Parasitic Oscillations

Every high-power amplifier should be tested before being placed in service, to insure that it is free of parasitic oscillations. For this test, nothing is connected to either the RF input or output terminals, and the bandswitch is first set to the lowest-frequency range. If the input is tuned and can be bandswitched separately, it should be set to the highest-frequency band. The amplifier control system should provide monitoring for both grid current and plate current, as well as a relay, circuit breaker or fast-acting fuse to quickly shut off high voltage in the event of excessive plate current. To further protect the tube grid, it is a good idea to temporarily insert in series with the grid current return line a resistor of approximately 1000 Ω to prevent grid current from soaring in the event a vigorous parasitic oscillation breaks out during initial testing.

Apply filament and bias voltages to the amplifier, leaving plate voltage off and/or cutoff bias applied until any specified tube warm-up time has elapsed. Then apply the lowest available plate voltage and switch the amplifier to transmit. Some idling plate current should flow. If it does not, it may be necessary to increase plate voltage to normal or to reduce bias so that at least 100 mA or so does flow. Grid current should be zero. Vary the plate tuning capacitor slowly from maximum capacitance to minimum, watching closely for any grid current or change in plate current, either of which would indicate a parasitic oscillation. If a tunable input network is used, its capacitor (the one closest to the tube if a pi circuit) should be varied from one extreme to the other in small increments, tuning the output plate capacitor at each step to search for signs of oscillation. If at any time either the grid or plate current increases to a large value, shut off plate voltage immediately to avoid damage! If moderate grid current or changes in plate current are observed, the frequency of oscillation can be determined by loosely coupling an RF absorption meter or a spectrum analyzer to the plate area. It will then be necessary to experiment with parasitic suppression measures until no signs of oscillation can be detected under any conditions. This process should be

repeated using each bandswitch position.

When no sign of oscillation can be found, increase the plate voltage to its normal operating value and calculate plate dissipation (idling plate current times plate voltage). If dissipation is at least half of, but not more than, its maximum safe value, repeat the previous tests. If plate dissipation is much less than half of maximum safe value, it is desirable (but not absolutely essential) to reduce bias until it is. If no sign of oscillation is detected, the temporary grid resistor should be removed and the amplifier is ready for normal operation.

Parasitic Oscillations in Solid-State Amplifiers

In low-power solid-state amplifiers, parasitic oscillations can be prevented by using a small amount of resistance in series with the base or collector lead, as shown in **Fig 18.23A**. The value of R1 or R2 typically should be between 10 and 22 Ω . The use of both resistors is seldom necessary, but an empirical determination must be made. R1 or R2 should be located as close to the transistor as practical.

At power levels in excess of approximately 0.5 W, the technique of parasitic suppression shown in Fig 18.23B is effective. The voltage drop across a resistor would be prohibitive at the higher power levels, so one or more ferrite beads placed over connecting leads can be substituted (Z1 and Z2). A bead permeability of 125 presents a high impedance at VHF and above without affecting HF performance. The beads need not be used at both circuit locations. Generally, the terminal carrying the least current is the best place for these suppression devices. This suggests that the resistor or ferrite beads should be connected in the base lead of the transistor.

C3 of Fig 18.24 can be added to some power amplifiers to dampen VHF/UHF parasitic oscillations. The capacitor should be low in reactance at VHF and UHF, but must present a high reactance at the operating frequency. The exact value selected will depend upon the collector impedance. A reasonable estimate is to use an X_C of 10 times the collector impedance at the operating frequency. Silver-mica or ceramic chip capacitors are suggested for this application. An additional advantage is the resultant bypassing action for VHF and UHF harmonic energy in the collector circuit. C3 should be placed as close to the collector terminal as possible, using short leads.

The effects of C3 in a broadband amplifier are relatively insignificant at the operating frequency. However, when a narrow-band collector network is used, the added capacitance of C3 must be absorbed into the network design in the same manner as the C_{OUT} of the transistor.

Low-Frequency Parasitic Oscillations

Bipolar transistors exhibit a rising gain characteristic as the operating frequency is lowered. To preclude low-frequency instabilities because of the high gain, shunt and degenerative feedback are often used. In the regions where low-frequency self-oscillations are most likely to occur, the feedback increases by nature of the feedback network, reducing the amplifier gain. In the circuit of Fig 18.24, C1 and R3 provide negative feedback, which increases progressively as the frequency is lowered. The network has a small effect at the desired operating frequency but has a pronounced effect at the lower frequencies. The values for C1 and R3 are usually chosen experimentally. C1 will usually be between 220 pF and 0.0015 µF for HFband amplifiers while R3 may be a value from 51 to 5600 Ω .

R2 of Fig 18.24 develops emitter degeneration at low frequencies. The bypass capacitor, C2, is chosen for adequate RF bypassing at the intended operating frequency. The impedance of C2 rises progressively as the frequency is lowered, thereby increasing the degenerative feedback caused by R2. This lowers the amplifier gain. R2 in a power stage is seldom greater than 10 Ω , and may be as low as 1 Ω . It is important to consider that under some operating and layout conditions R2 can cause instability. This form of feedback should be used only in those circuits in which unconditional stability can be achieved.

R1 of Fig 18.24 is useful in swamping the input of an amplifier. This reduces the chance for low-frequency self oscillations, but has an effect on amplifier performance in the desired operating range. Values from 3 to 27 Ω are typical. When connected in shunt with the normally low base impedance of a power amplifier, the resistors lower the effective device input impedance slightly. R1 should be located as close to the transistor base terminal as possible, and the connecting leads must be kept short to minimize stray reactances. The use of two resistors in parallel reduces the amount of inductive reactance introduced compared to a single resistor.

Although the same concepts can be applied to tube-type amplifiers, the possibility of self-oscillations at frequencies lower than VHF is significantly lower than in solid-state amplifiers. Tube amplifiers will usually operate stably as long as the input-to-output isolation is greater than the stage gain. Proper shielding and dc-power-lead bypassing essentially



Fig 18.23—Suppression methods for VHF and UHF parasitics in solid-state amplifiers.



Fig 18.24—Illustration of shunt feedback in a transistor amplifier. C1 and R3 make up the feedback network.

eliminate feedback paths, except for those through the tube itself.

On rare occasions tube-type amplifiers will oscillate at frequencies in the range of about 50 to 500 kHz. This is most likely with high-gain tetrodes using shunt feed of dc voltages to both grid and plate through RF chokes. If the resonant frequency of the grid RF choke and its associated coupling capacitor occurs close to that of the plate choke and its blocking capacitor, conditions may support a tunedplate tuned-grid oscillation. For example, using typical values of 1 mH and 1000 pF, the expected parasitic frequency would be around 160 kHz.

Make sure that there is no low-impedance, low-frequency return path to ground through inductors in the input matching networks in series with the low impedances reflected by a transceiver output transformer. Usually, oscillation can be prevented by changing choke or capacitor values to insure that the input resonant frequency is much lower than that of the output.

Amplifier Neutralization

Depending on stage gain and inter-electrode capacitances, sufficient positive feedback may occur to cause oscillation at the operating frequency. This should not occur in well-designed grounded-grid amplifiers, nor with tetrode or pentodes operating at gains up to about 15 dB as is current practice at HF where 50 to 100 W of drive is almost always available. If triodes are griddriven, however, and under certain other circumstances, neutralization may be necessary because of output energy capacitively coupled back to the input as shown in **Fig 18.25**. Neutralization involves coupling a small amount of output energy back to the amplifier input out-of-phase, to cancel the unwanted in-phase (positive) feedback. A typical circuit is given in **Fig 18.26**. L2 provides a 180° phase reversal because it is center tapped. C1 is connected between the plate and the lower half of the grid tank. C1 is then adjusted so that the energy coupled from the tube output through the neutralization circuit is equal in amplitude and exactly 180° out-of-phase with the energy coupled from the output back through the tube. The two signals then cancel and oscillation is impossible.

The easiest way to adjust a neutralization circuit is to connect a low-level RF source to the amplifier output tuned to the amplifier operating frequency. A sensitive RF detector like a receiver is then connected to the amplifier input. The amplifier must be turned off for this test. The amplifier tuning and loading controls, as well as any input network adjustments are then peaked for maximum indication on the RF detector connected at the input. C1 is then adjusted for minimum response on the detector. This null indicates that the neutralization circuit is canceling energy coupled from the amplifier output to its input through tube, transistor or circuit capacitances.

Screen-Grid Tube Stabilization

The plate-to-grid capacitance in a screen-grid tube is reduced to a fraction of a picofarad by the interposed grounded screen. Nevertheless, the power gain of these tubes may be so great in some circuits that only a very small amount of feedback is necessary to start oscillation. To assure a stable tetrode amplifier, it is usually necessary to load the grid circuit, or to use a neutralizing circuit.

Grid Loading

The need for a neutralizing circuit may often be avoided by loading the grid circuit to reduce stage gain, provided that the driving stage has some power capacity to spare. Loading by tapping the grid down on the grid tank coil, or by placing a "swamping" resistor from grid to cathode, is effective to stabilize an amplifier. Either measure reduces the gain of the amplifier, lessening the possibility of oscillation. If a swamping resistor is connected between grid and cathode with very short leads, it may help reduce any tendency toward VHF-UHF parasitic oscillations as well. In a class AB1 amplifier, which draws no grid current, a swamping resistor can be used to replace the bias supply choke if parallel feed is used.

Often, reducing stage gain to the value required by available drive power is suffi-



Fig 18.25—The equivalent feedback path due to the internal capacitance of the tube grid-plate structure in a power amplifier. Also see Fig 18.27.



Fig 18.26—Example of neutralization of a single-ended RF amplifier.



Fig 18.27—A neutralization circuit uses C1 to cancel the effect of the tube internal capacitance.

cient to assure stability. If this is not practical or effective, the bridge neutralizing system for screen-grid tubes shown in **Fig 18.27** may be used. C1 is the neutralizing capacitor. The value of C1 should be chosen so that at some adjustment of C1,

$$\frac{C1}{C3} = \frac{C_{gp}}{C_{IN}}$$
(48)

where

 C_{gp} = tube grid-plate capacitance C_{IN} = tube input capacitance.

The grid-to-cathode capacitance must include all strays directly across the tube capacitance, including the capacitance of the tuning capacitor.

3CX1500D7 RF Linear Amplifier

The following describes a 10-to-160meter RF linear amplifier that uses the new compact Eimac 3CX1500D7 metal ceramic triode. It was designed and constructed by Jerry Pittenger, K8RA.

The amplifier features instant-on operation and provides a solid 1500 W RF output with less than 100 W drive. Specifications for this rugged tube include 1500-W anode dissipation, 50-W grid dissipation and plate voltages up to 6000 V. A matching 4000-V power supply is included. The amplifier can be easily duplicated and provides full output in key-down service with no time constraints in any mode. **Fig 18.28** shows the RF deck and power supply cabinets.

DESIGNOVERVIEW

The Eimac 3CX1500D7 was designed as a compact, but heavy-duty, alternative to the popular lineup of a pair of 3-500Z tubes. It





Fig 18.28—At A, front panel view of RF Deck and Power Supply for 3CX1500D7 amplifier. At B, rear view of RF Deck and Power Supply.



	Та
Fig 18.29—At A. schematic of RF Deck. At	Pi.
B. schematic of control unit.	
B1—Dayton 4C763 squirrel-cage blower.	Fre
Cabinet—Buckeye Shapeform DSC-1054-16	(IVI
(10×17×16-inch H×W×D),	1.
www.buckeyeshapeform.com	3
Chimney (Teflon)—A. Howell, KB8JCY,	
PO Box 5842, Youngstown, OH 44504.	14.
Cp—0.01 µF, 1 kV bypass disc ceramic.	21
C101—400 pF, 10 kV Jennings vacuum	21.
variable, UCSL-400.	28
C102—1000 pF, 5 KV Jennings Vacuum	
Variable, UCSL-1000. C102 C104 $250 \text{ pE} = 5 \text{ kV}$ coromic	Та
doorknob	Co
C105—two parallel 0 001 µF 7 5 kV disc	L1
ceramic (Ukrainian mfg).	
C106, C107—0.001 µF, 7.5 kV disc	
ceramic.	L2
C108, C109–0.01 µF, 3 kV transmitting	
mica (1 kV disc ceramics can be used).	
C401—12 pF piston trimmer.	L3
C403, C403—150 pF silver mica.	
D101, D107, D205-D209—1N5393 (1 kV,	LS
1.5 A). D102 D106 D201 D204 _ 1N5408 (1 kV 2 A)	
D102-D100, D201-D204—1193406 (1KV, 3 A). K1—4PDT_24 Vdc KHP style (gold	
contacts)	
K2—SPST vacuum relay, Kilovac H8/S4	
K3—4PDT, 24 V dc KHP style (gold	
contacts).	
L1-L5—See Table 1.	
L201, L202—Line chokes, 7 µH.	
L401—24 t #22 enamel wire, center tapped	
on T50-6 core.	
LDG Tuner—Modified AT-100Pro	has
Autotuner, www.idgelectronics.com.	pla
523 1 mA movement	10
PC101—2 t $\frac{3}{4}$ -inch diameter x 2-inch long	Th
$^{1}/_{2}$ -inch brass strap with two 150 Ω . 2 W	
non-inductive carbon resistors in	SN
parallel.	thr
Q101—2N3055 TO-220 case on heat sink.	fie
Q102—2N3053 TO-18 case.	sig
R103—25 k Ω , 25 W wire-wound.	cir
R104—10 Ω, 5 W.	Fig
$H108 - 150 \Omega$, 10 W wire-wound.	
R 2 - 00 K 2, 2 W. P 02 - 100 K 0, 5 W trim path	nli
RFC101_90H 3 A Plate Choke Deter W	pn 1
Dahl p/n CKBF000100, pwdahl.com/	nai
cai-bin/store/commerce.cai.	coi
RFC102—14 t #18 enamel wire wound on	an
100 O 2 W resistor	То

RFC103—Bifilar 30 A filament choke, Peter W. Dahl p/n CKRF000080, pwdahl.com/ cgi-bin/store/commerce.cgi.

- RFC104—1 mH, 300 mA RF choke. S1-S4—Alco 164TL2 momentary DPDT,
- www.alliedelec.com/. S5—2P3P rotary switch.
- SW1—RadioSwitch model 86, double-pole 12-position (30° indexing) with 6-finger wiper on each deck, p/n R86R1130001, www.multi-tech-industries.com.
- T2—5 V, 30 A transformer, Peter W. Dahl El-150 x 1.5 core, primary 115/230 V ac, www.pwdahl.com.
- TH1—Thermistor, Thermometrics CL-200 (Mouser 527-CL200).
- Tube socket—Eimac SK-410.
- ZD101-10 V, 1 W zener 1N4740A.

Fable 18.7

Pi-L	Component V	Values					
Frequ (MHz)	ency C1 (pF)	у C1 C2 L1 (pF) pF µH		L2 μΗ	Q		
1.85 3.70	0 211 0 105	1262 631	44.3 22.2	9.6 4.8	12 12		
7.15	0 65 0 33	364 184	9.7 4.9	2.5 1.26	14 14		
18.100 21.200 24.900	0 45 0 33 0 36	208 159 161	2.23 2.21 1.48	0.98 0.84 0.71	23 20 25		
28.25	0 29	133	1.43	0.63	23		
Tank	Circuit Coils						
Coil	Band	Indu	ctance	Construc	tion		
L1	10/12-15/17 m	1 2.3 µ	ιH	7 ¹ / ₂ t, ¹ / ₄ -i 10/12-m 15/17-m	in. coppe tap @ 3 tap @ 7	er tube, 2-in. ID silver-plated ^{1/2} t ^{1/2} t	
L2	20-40 m	7.4 µ	ιH	19 t, ³ / ₁₆ -i 20 tap@ 40 tap @	in. copp 8 t 19 t	er tube, 2-in. ID silver plated	
L3 L4 L5	80 m 160 m L-Coil	12.4 22.0 9.6	μΗ μΗ μΗ	40 tap @ 19 t 17 t on 3×T225-2 cores, #10 Teflon silver wire 23 t on 3×T300-2 cores, #10 Teflon silver wire 19 t on 2×T225-2 cores, #12 tinned wire w/Teflon sleeve 10/12-m tap @ 2 t 15/17-m tap @ 4 t 20-m tap @ 5 t 40-m tap @ 7 t 80-m tap @ 12 t 160-m tap @ 19 t			

has a 5-V/30-A filament and a maximum plate dissipation of 1500W, compared to the 1000-W dissipation for a pair of 3-500Zs. The 3CX1500D7 uses the popular Eimac SK510 socket and requires forced air through the anode for cooling. The amplifier uses a conventional grounded-grid design with an adjustable grid-trip protection circuit. See the RF Deck schematic in **Fig 18.29**.

Output impedance matching is accomplished using a pi-L tank circuit for good harmonic suppression. The 10 to 40-meter coils are hand wound from copper tubing, and they are silver plated for efficiency. Toroids are used for the 80- and 160-meter coils for compactness. The amplifier incorporates a heavy-duty shorting-type bandswitch. Vacuum variable capacitors are used for pi-L tuning and loading.

A unique feature of this amplifier is the use of a commercial computer-controlled input network module from LDG Electronics (**www.ldgelectronics.com**). This greatly simplifies the amplifier design by eliminating the need for complex ganged switches and sometimes frustrating setup adjustments. The computer-controlled input network is reasonably priced and basically plug-and-play.

An adjustable ALC circuit is also included to control excess drive power. The amplifier

metering circuits allow simultaneous monitoring of plate current, grid current, and a choice of RF output, plate voltage or filament voltage.

The blower was sized to allow full 1500watt plate dissipation (65 cfm at 0.45 inches H_2O hydrostatic backpressure). The design provides for blower mounting on the rear of the RF deck or optionally in a remote location to reduce ambient blower noise in the shack.

The power supply is built in a separate cabinet with casters and is connected to the RF deck using a 6-conductor control cable, with a separate high voltage (HV) cable. The power transformer has multiple primary taps (220/230/240 V ac) and multiple secondary taps (2300/2700/3100 V ac). No-load HV ranges can be selected from 3200 to 4600 V dc using different primary-secondary combinations. The amplifier is designed to run at 4000 V dc under load to maintain a reasonable plate resistance and component size. A step-start circuit is included to protect against current surge at turn on that can damage the diode bank. The power supply schematic is shown in Fig 18.30 and a photo of the inside of the power supply is shown in Fig 18.31.

Both +12-V and +24-V regulated power supplies are included in the power supply. The +12 V is required for the computer-con-



Fig 18.30—Schematic for Power Supply for 3CX1500D7 amplifier.

B1—Pilot lamp Alco 164-TZ, 12 V. Cabinet—Buckeye Shapeform DSC-1204-16 (12×18×16-inch H×W×D), www.buckeyeshapeform.com. C301—53 μF, 5 kV oil-filled, Peter W. Dahl p/n CDCF007100, pwdahl.com/cgi-bin/ store/commerce.cgi. Fan—12 Vdc brushless, 2¹/₄ inch (Mouser 432-31432).

R303, R304—100 kΩ, 200 W wirewound, Peter W. Dahl p/n RP002000, pwdahl.com/cgi-bin/store/ commerce.cgi. SRY1-SRY4—Potter & Brumfield solidstate relay, SSR-240D25R. T1—Peter W. Dahl Co, 220/230/240 pri :

2300/2700/3100 sec, 1.5 A, CCS, **pwdahl.com**.

trolled input network and +24 V is needed for the output vacuum relay. The input and output relays are time sequenced to avoid amplifier drive without a 50- Ω load. Relay actuation from the exciter uses a low-voltage/low-current circuit to accommodate the amplifier switching constraints imposed by many new solid-state radios.

Much thought was put into the physical appearance of the amplifier. The goal was to obtain a unit that looks commercial and that would look good sitting on the operating table. To accomplish the desired look, commercial cabinets were used. Not only does this help obtain a professional look but it eliminates a large amount of the metal work required in construction. Careful attention was taken making custom meter scales and cabinet labeling. The results are evident in the pictures provided.

GENERAL CONSTRUCTION NOTES

The amplifier was constructed using basic shop tools and does not require access to a sophisticated metal shop or electronics test bench. Basic tools included a band saw, a jig saw capable of cutting thin aluminum sheet, a drill press and common hand tools. Some skill in using tools is needed to obtain good results and insure safety, but most people can accomplish this project with careful planning and diligence.

Metal work can be a laborious activity. Building cabinets is an art within itself. This part of the project can be greatly simplified by using commercial cabinets. However, commercial cabinets are expensive (~\$250 each) and could be a place where some dollars could be saved.

The amplifier is built in modules. This breaks the project into logical steps and facilitates testing the circuits along the way. For example, modules include the HV power supply, LV power supply, input network, control circuits, tank circuit and wattmeter.



Fig 18.31—Inside view of Power Supply, showing rectifier stack, control relays and HV filter capacitor with bleeder resistors. The heavy-duty Peter W. Dahl transformer is at the upper left in this photo.

Each module can be tested prior to being integrated into the amplifier.

The project also made extensive use of computer tools in the design stage. The basic layout of all major components was done using the *Visio* diagramming software package. The printed-circuit boards were designed using a free layout program called *ExpressPCB* (www.expresspcb. com). Masks were developed and the ironon transfer technique was used to transfer the traces to copper-clad board. The boards were then etched with excellent results. The layout underneath the RF Deck is shown in **Fig 18.32A** and the top side of the RF Deck is shown in Fig 18.32B.

Meter scales were made using an excellent piece of software called *Meter*, available by download from James Tonne, at **tonnesoftware.com**. Also, K8RA wrote an *Excel* spreadsheet to calculate the pi-L tank parameters. (A copy of the spreadsheet is on the CD-ROM that accompanies this book, as are the pc board templates.)

Although using computer tools simplifies the design step, all design work can be done without the use of a computer. Be creative and use the tools and resources at hand! There are many different ways to construct this design. The key secret is diligence and not compromising until it is done right. Note that the tank coils in this amplifier were wound at least three times, the inside side panels were cut twice and many printed circuit boards ended in the trash before acceptable boards were fabricated.

CABINET METAL WORK

By purchasing commercial cabinets, metal work required was minimized but not eliminated. The power supply components are very heavy. The transformer weighs about 70 pounds by itself. Therefore the base plate of the power supply cabinet needed to be reinforced. The original base plate for the cabinet was not used. Oneeighth-inch plate was purchased from a local aluminum scrap company. Two pieces were sandwiched to provide a ¹/₄-inch plate. Of course ¹/₄-inch material could have been used but it was not available at the time of purchase.

The plate can be cut on a metal band saw using a guide or on a radial arm saw. Metal blades are readily available from Sears for both saws. If using a radial arm saw, multiple passes are required, lowering the blade slightly with each pass. Be sure to wear eye protection because the metal chips fly. The edges were then cleaned and straightened using a 4-inch belt grinder. If a belt sander is not available, a large file will work.

The two metal plates were held together with the mounting bolts on the four casters. The power supply base plate exactly matches the original base plate and fastened to the cabinet using the original tapped screw holes. All the heavy components are mounted on the base plate. The power supply must always be handled by lifting the base plate, since the cabinet does not have the structural integrity to bear the weight by itself.

The RF deck needed both a chassis plate and a front sub-panel. See Fig 18.32B. The sub-panel is used to mount the load and tune capacitors, the bandswitch and also provides RF shielding for the meters. Side plates were needed because of the cabinet configuration. The side plates, chassis plate and subpanel all use ¹/₁₆-inch aluminum plate. After the side plates are cut and mounted to the cabinet sides, the chassis plate and front subpanel are mounted using ¹/₂-inch aluminum angle to join the edges.

Cutting holes can often be a challenge. If a drill bit is the correct size, drilling a hole is easy, of course. But large-size round holes and square holes can be a challenge. This was especially true in this project since the front and rear panels are ¹/₈-inch aluminum plate.

The large meter holes can be cut using a hole saw on a drill press. For odd sizes, a "fly cutter" can be used. Fly cutters are available from Sears but a special warning is in order. These devices work well but are extremely dangerous. Make sure the cutting bit and the placement into the drill chuck are secure.

Large square holes are required for the turn counters. Mark the square hole to be cut. Drill a hole in each corner. The hole must be at least the size of the saw blade if a jigsaw is used to finish the hole. Note that the jigsaw must have a removable straight blade. If a metal-cutting jigsaw is not available, a series of small holes can be drilled in a straight line on all four sides and the edges smoothed with a file. Almost any hole can be custom cut by making a hole the approximate size and finishing it to the exact dimension with a file. It is slow and laborious but it works. When using a file on panels, be very careful that the file does not slip out of the hole and put an undesired scratch in the panel!

Once panel holes are cut, carefully label the panels before mounting the components. Dry transfers are used on both the power supply and the RF deck. Dry transfers of all sizes and fonts are available at graphics art stores and hobby shops. The author has found that hobby shops carry an excellent selection of dry transfers in the model railroad section.

RF DECK CONTROL CIRCUITS

The control circuits in the amplifier are



(A)



Fig 18.32—At A, under the chassis of the RF Deck. The autotuner used as the input network for this amplifier is at the upper right. At B, view of the Pi-L output network in the RF Deck.

not complex due to the simplicity of the grounded-grid design and the instant-on capability of the 3CX1500D7 tube. 120 V ac is routed from the HV power supply to the RF Deck in the 6-conductor control cable. When the on/off switch (S1) is

pressed, 120 V ac is sent to the primary of the low voltage transformer (T2) and the filament transformer (T3). The surge current to the filament of the tube is suppressed by the thermistor (TH1) in one leg of the filament transformer primary. These are excellent current limiting devices that have a resistance of approximately 25Ω cold but decrease to less then 1Ω as they heat. Keep the thermistor in open air away from other components since they are designed to run hot.

The low voltage supply provides regulated +12 V dc and +28 V dc. The voltages are regulated using simple three-terminal regulators. Pilot lights are included in each push button switch, S1-S4, and a power indicator on the HV power supply. When the low-voltage power supply first comes on, +12 V dc is directed through the control cable back to the HV supply. High voltage is applied immediately to the instant-on tube. Therefore the amplifier is turned on and ready to go instantly—You don't have to listen to your friends working that rare one for three or four tense minutes while you wait for your amplifier to time in!

The amplifier is switched in and out of the circuit using a 4PDT KHP style relay (K1) for the input and a SPDT vacuum relay (K2) for the output. It is important to select the timing constants for the input relay (C201 and R201) so the input relay closes a few milliseconds after the vacuum relay. This avoids hot switching the output, which could fuse the vacuum-relay contacts. This is a balancing act since the brief time the input relay is open will present an open circuit to the exciter. Many modern radios now have exciter-timing circuits that close the amplifier relay circuit a few milliseconds before RF is transmitted.

It is recommended that timing components for the input relay be located in a place where they can be easily changed. Another approach is to build a breadboard circuit that feeds the relay coils in parallel but places the contacts in series. Feed a low voltage through the contacts of the two relays and monitor the timing with a dual-trace oscilloscope. This technique allows precise timing of contact closure as the two relays work together. Note that different relays will need different timing-circuit component values. A set of contacts on input relay, K1, is used to short across bias resistor, R103. The resistor biases the tube to cutoff in standby.

Approximately +10-V bias is provided to the center tap of the filament transformer to limit the idle current of the tube to approximately 125 mA. The bias is developed using the three components D101, R101 and Q101. These components could be replaced with a single 10-V/50-W zener diode. However, 50-W zeners are expensive and they are difficult to obtain. Using the circuit shown, the bias is provided by a common NPN transistor (Q101) and a one-watt zener (D101) you can obtain from RadioShack.

TUBE PROTECTION CIRCUIT

The main protection for the tube is a platecurrent surge resistor and a grid-trip circuit. The current surge resistor (R308, 50- Ω /50-W) is in series with the B+ line and acts as a fuse should excessive current be drawn from the HV power supply. Ohm's law says that up to 1-A plate current can be drawn through the resistor and still stay within the 50-W rating of R308. However, let's assume a problem occurs and 5 A flows through the resistor. Resistor R3 must now dissipate 1250 W. The resistor will quickly fail and will shut down the HV to the 3CX1500D7 tube.

Q102 is a grid-trip circuit that snaps the amplifier offline if the grid current exceeds 400 mA. The grid current is drawn through the 10- Ω resistor (R104) connected between the B-line and chassis ground. The current creates a voltage across R104 that is fed to the grid-trip adjustment potentiometer, R106. Q102 is turned on when the base voltage reaches 0.6 V and actuates the gridtrip relay K3. K3 contacts break the +28 V dc input and output relay lines (K3B), locks the relay closed (K3C) and extinguishes the pilot bulb (K3A) of the GRID-TRIP RESET normally closed push-button switch (S3) located on the front panel. Pushing the GRID TRIP RESET switch (S3) breaks the current path for the grid-trip relay K3 and resets the relay. The reason the grid trip was actuated should be determined prior to attempting to use the amplifier again. Usually, this is caused by improper setting of the load capacitor or transmitting into the wrong antenna.

INPUT NETWORK

As mentioned before, this amplifier uses a unique concept for the input-matching network, getting rid of a switched network mechanically ganged to the main bandswitch. Not only can such a switching arrangement be awkward mechanically, but obtaining a reasonable network Q and a low SWR over an entire band can be difficult.

Thus the author decided to use a commercial automatic tuner integrated into the RF deck (see Fig 18.32A). The tuner is made by LDG and is based on their popular AT-100 Pro Autotuner, but was supplied without the front panel or rear panel connections and switches. This application is simple but elegant. The unit automatically initiates a retune if the input SWR exceeds approximately 1.5:1. The tuning cycle takes three to five seconds to execute. But retuning does not happen often because the tuner has over 4000 memories and remembers the settings for different frequency ranges. As the amplifier is used on each band, the tuner *learns* and stores settings into the memory. When switching bands, it only takes milliseconds to retrieve the data from memory and actuate the correct tuner relays.

Integration of the tuning network requires connections for RF input and output, +12 V and ground. RF input goes to the center of T1 and ground goes to J2 (clearly marked on the board). RF output goes to J3 and ground goes to J6. The + 12-V dc connection is the larger of the three holes at J10 (next to L10). The other two holes are grounds for dc connections.

A momentary contact switch (S4) is mounted on the front panel to provide manual control of the tuner. A normally open contact on S4 is connected to the input pin J9 (next to L12) and ground. (The pin is marked as the ring for the connector that is not installed.) The correct hole is on the C56 side. If the switch is pushed for less than $1/_2$ second, the tuner alternates between bypass and in-line modes. If S4 is pressed between 0.5 to 2.5 seconds, it does a memory tune from the stored data tables. If S4 is pressed for more than 2.5 seconds with RF applied, it skips the memory access, retunes and stores the new settings into the memory table. The manual retune function is seldom, if ever, used.

The tuner works perfectly and it really simplified the input-network design and construction. The SWR never exceeds 1.5:1 (typically it is 1.2:1). LDG provides the unit as a commercial product to amplifier builders.

PI-LNETWORK

A pi-L network is used to insure good harmonic attenuation. The pi-L circuit is actually a pi-network, followed by an Lnetwork that provides additional harmonic attenuation. The L-section transforms the load of 50 Ω up to an intermediate resistance of 300 Ω . The pi section then transforms 300 Ω up to the desired plate load resistance of 3100 Ω . The plate load is calculated using the following formula:

$$R_{\rm L} = \frac{E_{\rm P}}{1.7 \times I_{\rm P}} = \frac{4000}{1.7 \times 0.750} = 3137\,\Omega$$

A nominal Q of 12 is used for the network. But as with most RF amplifiers, the capacitance needed for the higher-frequency bands is less than is physically possible using variable capacitors. For Q = 12, the tune capacitance (C101) for 10 meters is 14 pF. Using a vacuum variable capacitor for C1 helps because the minimum achievable capacitance (12 pF) is substantially less than with an air variable. But the tune capacitance is the sum of variable C101, 7.1 pF for the output capacitance of the 3CX1500D7 tube and any stray capacitance resulting from the physical layout of the amplifier.

The minimum obtainable capacitance is thus on the order of 30 pF, which yields a higher value of loaded Q than optimum. The solution is two fold. First, connect the platetune capacitor (C101) one turn into the 10meter coil. This actually forms an L-pi-L circuit. Second, accept a higher value of loaded Q so that the variable capacitor can still be tuned. Table 18.7 shows the loaded Q finally used for each band setting. The disadvantages of higher loaded Os are high circulating currents in the tank circuit and the need to retune during excursions across the higher-frequency bands. This amplifier works fine on all bands, delivering a solid 1500 W output even on 10 meters.

Another pi-L tank circuit design constraint in this amplifier is the bandswitch. Many amplifiers use a single-pole, 12-position, nonshorting switch. Although this type of switch is easier to find, it can be problematic because high voltages are generated that could result in arcing in the bandswitch—usually from the wiper to the high frequency taps. You should use a switch with a multiplefinger wiper (see Fig 18.29) that shorts out lower-frequency coil taps not being used. For example, when the amplifier is used on 20 meters, the 40-, 80- and 160-meter taps are shorted to the wiper.

However, shorting switches only allow for six connections with 30° indexing. The common shorting wiper consumes 180° of switch deck on 160 meters. This results in having to design the 10/12-meter and 15/ 17-meter bands to use single taps for each frequency pair. Again, this is accomplished by adjusting the loaded Q for each band so that shared bands so they require nearly the same inductance. From Table 18.7, the same band switch position is shared on the 10/12meter bands (1.4 µH) and the 15/18-meter bands (2.2 µH).

In actual construction of the tank circuit, it is very useful to have access to both a capacitance meter and an inductance meter. The author used an Elenco LCM-1950 meter that measures both capacitance and inductance and is available for under \$100 (www.elenco.com). With the tune and load capacitors mounted and connected to calibrated knobs or turns counters, make a table of capacitance verses knob settings. This is useful to estimate the initial setting for each band during setup and test. Also, measure the inductance of each coil turn to determine initial coil taps for each band. On this amplifier, only the 10-meter tap had to be adjusted from the predetermined settings.

As mentioned above, the pi-L tank circuit was designed for 3100- Ω plate-load resistance. Such a high plate resistance demands higher inductance values to obtain reasonable tank circuit Os. Table 18.7 shows that 160 meters requires 42 µH. If air-wound coils were used exclusively, the coils would require many turns and would take up a lot of cabinet space. To maintain a reasonable physical coil size, therefore, toroidal coils were used for 80 (L3) and 160 (L4) meters in addition to the output coil (L5) (see Fig 18.32B). You should use substantial core material for high-power operation to avoid core heating. Core sizes were increased by using multiple cores taped together. Each ferrite core is wrapped with three layers of high temperature fiberglass tape, available from RF Parts (www.rfparts.com). Teflon-insulated #10 wire was wound to obtain the desired inductance in L3 and L4. Both coils are mounted on ceramic standoffs and held in place with Teflon blocks.

The output coil is wound on a pair of T225-2 cores using #12 tinned wire covered with a Teflon sleeve. Taps onto the coil are made by carefully trimming a small ¹/₈-inch space from the Teflon sleeve on the inner edge of the core facing the bandswitch. Taps are then made from the back section of the 2-pole bandswitch using #12 tinned wire. The proper placement of each tap is determined by first winding #12 insulated wire around the core. A small slit is carved into each turn and the inductance was measured. The copper wire is removed and the final Teflon-covered #12 tinned wire is wound onto the core. Using the output L-coil (L102) design values in Table 18.7, permanent taps were made.

Note that the taps for the output coil are not extremely critical. Select the closest turn to the value needed. The output coil is mounted on the back of the bandswitch on one of the switch wafer screws using a threaded 1-inch diameter Teflon rod. The Teflon rod holds the position of the coil. The weight is carried by the wire taps from the coil to the bandswitch contacts. Table 18.7 also gives the inductance and construction instructions for each coil.

L1 and L2 (10-40 meters) are silver plated. They were wound using a 2-inch aluminum pipe as a form. Clean the copper tubing with #0000 steel wool prior to winding. Wind the copper tubing close spaced on the pipe. Leave plenty of pigtail on each end of the coil. The ends can be trimmed to fit the mounting positions precisely. After winding the desired number of turns, plug the ends by closing the tube ends with a hammer, spread the coil windings and rinse the coil in acetone to remove any oil. Allow a few minutes to dry. The coil is now ready to plate.

Go to any photo shop and beg/buy a gallon of used photographic fixer solution. Note that used fixer solution has silver remnant. The more the solution has been used, the more the silver content. The coils can be silver plated by dipping the clean coil into the solution. Do not leave the coil in the solution too long or it will turn black. A thin but bright silver coat will be deposited on the copper tube. This is called *flash plat*ing. After dipping the coil into the solution, immediately rinse in a bath of clean water and blow dry under pressure with an air compressor, heat gun or hair dryer. If a thicker silver coat is desired, electroplating is necessary, a subject beyond the scope of this article.

A #10 lug is crimped and soldered onto the end of each coil and used to mount the coil. The L2 coil is mounted using a Teflon block that is held in place to the front subpanel with small screws. The block is carefully drilled with ³/₁₆ inch holes the desired spacing of the coil about ³/₄-inch from one edge. The block is sawed down through the holes creating two matching blocks. At each end of the block a hole is drilled and tapped (6-32 tap). The silver plated coil is sandwiched between the two blocks for secure support. The tapped screws serve as the connecting points for the ends of the coil.

METERING

The amplifier uses three separate meters to simultaneously monitor plate current, grid current and a choice of plate voltage, power output or filament voltage. Each meter is identical with a 1-mA full-scale movement. As mentioned previously, the custom scales for each movement were designed using the Meter software from Tonne Software. This allows up to three scales on each meter. Scales can be designed as either linear or log and the number of major and minor tick marks can be specified. Each scale can be labeled using different font size and color. The author printed the scales using a color inkjet printer onto glossy photo paper. The scales were carefully cut to match the meter faceplate and glued into place using a thin coat of adhesive.

Plate current is measured by M1 in series in the B– line using a current divider (R114 and R115) as shown in Fig 18.30. Adjust R114 to obtain full scale with 1-A of plate current. The meter was calibrated prior to installation using a low-voltage power supply with adjustable current limiting in series with an accurate digital meter.

M2 monitors grid current by measuring the voltage drop created by grid current flow through the 10- Ω resistor, R104. Connecting a voltage source (ie, small variable power supply) across R104 and measuring the actual current flow with an external meter provides a way to set the calibration pot, R105.

M3 is a multimeter that reads HV, RF power or filament voltage. The metering circuit is selected using a 2P3T rotary switch (S5). The HV metering circuit is in the HV power supply and fed to the RF deck through the control cable. The filament-voltage detect circuit is shown on the control circuit diagram (Fig 18.29: D207, D201 and R202). Adjust R202 for the proper reading on Meter M3. The 3.1-V zener (D201) expands the meter scale for more precise reading.

The RF wattmeter circuit is also shown in Fig 18.29. Only forward power is measured and potentiometer R403 is used for calibration. The wattmeter is not a precise instrument but gives a relative output reading. It is adequate for peaking power output when tuning. The meter provides good accuracy through 40 meters and then begins to read lower on the higherfrequency bands. This is due to the simplicity of the circuit and the toroid used. Quite honestly, don't expect much accuracy from this wattmeter.

HV POWER SUPPLY

The matching HV Power Supply (Fig 18.30) provides approximately 4000 V under load. It uses a full-wave bridge rectifier and is filtered using a single 53 μ F/5000-V oil filled capacitor (C301). Whenever the HV supply is plugged into the 240-V line, live 120 V ac is routed to the RF deck through the control cable. The 120-V ac line is obtained from L1 and neutral of the 240-V ac line. The neutral line is isolated from ground for safety.

Actuating the on/off switch S1 on the front panel of the RF deck provides ac power to the low-voltage power supply. In turn, +12 V is returned to the power supply through the control cable and routed to a pair of solid state power relays (K1, K2). Also, +12 V is routed to a timer relay that provides a two-second delay in applying +12 V to the second pair of solidstate relays (K3, K4). During the two-second delay, each leg of the 240-V ac primary voltage is routed through a 25- Ω resistor (R301, R302) to reduce the current surge when charging the filter capacitor, C301.

HV is metered at the bottom of the two series 100,000- Ω bleeder resistors (R303, R304). A current divider is created using a small potentiometer (R306) in parallel with a 25- Ω /5-W resistor (R305). The current divider is in series with the bleeder resistors and tied to the B–line. R306 is set to allow 1 mA of current to flow to the HV meter located on the front panel of the RF deck with 5000 V HV dc. The potentiometer R306 and the paralleled fixed resistor R305 need handle only a small amount of power, since the voltage and current flow is quite small at this point in the circuit.

The HV cable between the RF Deck and power supply is made from a length of automotive-ignition cable that has a #20 wire and 60,000-V insulation. Be sure to get a solid-wire center conductor and not the resistive carbon material. Also use high-quality HV connectors that are intended for such an application. Millen HV connectors (50001) were used in this amplifier. Coax boots intended for coaxial cable are used on each connector for added insulation and physical strength. The mounting holes for the Millen connectors are oversized and plastic screws were used for safety.

TUNING AND OPERATION

The amplifier is very easy to tune after the initial settings of the tune (C101) and load (C102) controls are determined. The correct settings are determined with a plate current of 700 mA with a corresponding grid current of 200 mA. The turn counters provide excellent resetability once the proper settings have been found initially. Required drive power is about 75 W for 1500 W output.

Thanks to CPI Eimac Division, LDG Electronics, Peter W Dahl Co, and MTI Inc (Radio Switch) for their support in this project.

A 6-Meter Kilowatt Amplifier Using the Svetlana 4CX1600B

The Svetlana 4CX1600B tube has attracted a lot of attention because of its potent capabilities and relatively low cost. Because of its high gain and its large anode dissipation capabilities, the tube has relatively large input and output capacitances—85 pF at the input and 12 pF at the output. Stray capacitance of about 10 pF must be added in as well. On bands lower than 50 MHz, these capacitances can be dealt with satisfactorily with a broadband $50-\Omega$ input resistor and conventional out-



Fig 18.33—Photo of the front panel of W1QWJ's 6-meter 4CX1600B amplifier.



Fig 18.34—Schematic for the RF deck for the 6-meter 4CX1600B amplifier. Capacitors are disc ceramic unless noted. Addresses for parts suppliers can be found using *TISFind* and other search engines.

- C2, C7—4.6-75 pF, 500-V air-variable trimmer capacitor, APC style.
- C6—Screen bypass capacitor, built into SK-3A socket.
- C13—1-45 pF, 5 kV, Jennings CHV1-45-5S vacuum-variable capacitor.
- C14—50 pF, 7.5 kV, NPO ceramic
- doorknob capacitor. C15—4-102 pF, 1100V, HFA-100A type
- air-variable capacitor. C16, 17, 18, 19, 20, 21—1000 pF, 1 kV
- feedthrough capacitors.

put tuning circuitry.

See the article by George Daughters, K6GT, "The Sunnyvale/Saint Petersburg Kilowatt-Plus" in 2005 for details on suitable control and power-supply circuitry. This 6-meter amplifier uses the same basic design as K6GT's, except for modified input and output circuits in the RF deck. See **Fig 18.33**, a photograph of the front panel of the 6-meter amplifier.

On the 50-MHz band the tube's high input capacitance must be tuned out. Author Dick Stevens, W1QWJ, used a T network so that the input impedance looks like a nonreactive 50 Ω to the transceiver. To keep the output tuning network's loaded

- L1—11 turns, #16, ³/₈-inch diameter, 1-
- inch long. L2—9 turns #16, ³/₈-inch diameter,
- close-wound. L3—8 turns #16, ³/₈-inch diameter, ⁷/₈-inch long.
- L4—1/4-inch copper tubing, 41/2 turns, 11/ 4 inches diameter,
- 4¹/₂ inches long.
- L5—5 turns #14, 1/2 inch diameter, 13/8 inches long.

Q low enough for efficient power generation, he used a 1.5 to 46 pF Jennings CHV1-45-5S vacuum-variable capacitor, in a Pi-L configuration to keep harmonics low. You should use a quarter-wave shorted coaxial stub in parallel with the output RF connector to make absolutely sure that the second harmonic is reduced well below the FCC specification limits.

To guarantee stability, the author had to make sure the screen grid was kept as close as possible to RF ground. This allows the screen to do its job "screening"—this minimizes the capacitance between the control grid and the anode. He used the Svetlana SK-3A socket, which includes a

- M1—0-1.3 A meter, with homemade shunt resistor, R3, across 0-10 mA movement meter.
- PC—Parasitic suppressor, 2 turns #14, 1/2 inch diameter, shunted by two 100- Ω , 2-W carbon composition resistors in parallel.
- RFC1—10 μH, grid-bias choke.
- RFC2—Plate choke, 40 turns #20, 1/2inch diameter, close-wound.
- RFC3—Safety choke, 20 turns #20, 3/8 inch diameter.

built-in screen bypass capacitor, and augmented that with a 50-MHz series-tuned circuit to ground. In addition, to prevent VHF parasitics, he used a parasitic suppressor in the anode circuit.

Unlike the K6GT HF amplifier, this 6-meter amplifier uses no cathode degeneration. W1QWJ wanted maximum stable power gain, with less drive power needed on 6 m. He left the SK-3A socket in stock form, with the cathode directly grounded. This amplifier requires about 25 W of drive power to produce full output.

Fig 18.34 is a schematic of the RF deck built by W1QWJ. The control and power supply circuitry are basically the same as



Fig 18.35—Partial schematic of K6GT HV power supply, showing modification with 250- Ω , 25-W power resistor to ground on B– line, allowing for metering of the plate current in the amplifier.

that used in Fig 18.29 and Fig 18.30 in the K6GT HF amplifier, except that plate current is monitored with a meter in series with the B– lead, since the cathode in this amplifier is grounded directly. The K6GT power supply is modified by inserting a 250- Ω , 25-W power resistor to ground in place of the direct ground connection. See **Fig 18.35**. In Fig 18.34, C1 blocks gridbias dc voltage from appearing at the transceiver, while L1, L2 and C2 make up the T-network that tunes out the input

capacitance of V1. R1 is a non-reactive 50- Ω 50-W resistor.

C6 is the built-in screen bypass capacitor in the SK-3A socket, while L3 and C7 make up the series-tuned screen bypass circuit. RFC3 is a safety choke, in case blocking capacitor C12 should break down and short, which would otherwise place high voltage at the output connector.

CONSTRUCTION

Like the K6GT amplifier, this W1QWJ

amplifier is constructed in two parts: an RF deck and a power supply. Two aluminum chassis boxes bolted together and mounted to a front panel are used to make the RF deck. **Fig 18.36** shows the 4CX1600B tube and the 6-meter output tank circuit.

Fig 18.37 shows the underside of the RF deck, with the input circuitry shown in more detail in Fig 18.38. The $50-\Omega$, 50-W noninductive power resistor is shown at the bottom of Fig 18.38. Note



Fig 18.36 (left)—Close-up photo of the anode tank circuit for 6-meter kW amplifier. The air-cooling chimney has been removed in this photo.

that the tuning adjustment for the input circuit is accessed from the rear of the RF deck.

AMPLIFIER ADJUSTMENT

The tune-up adjustments can be done without power applied to the amplifier and with the top and bottom covers removed. You can use readily available test instruments: an MFJ-259 SWR Analyzer and a VTVM with RF probe.

 Activate the antenna changeover relay, either mechanically or by applying control voltage to it. Connect a 2700-Ω, ¹/₂-W carbon composition resistor from



Fig 18.37—Underneath the 6-meter kW amplifier RF deck, showing on the left the tube socket and input circuitry.

anode to ground using short leads. Connect the SWR analyzer, tuned to 50 MHz, to the output connector. Adjust plate tuning and loading controls for a 1:1 SWR. You are using the Pi-L network in reverse this way.

- Now, connect the MFJ-259 to the input connector and adjust the input T-network for a 1:1 SWR. Some spreading of the turns of the inductor may be required.
- 3. Disconnect the Pi-L output network from the tube's anode, leaving the $2700-\Omega$ carbon composition resistor from the anode still connected. Connect the RF probe of the VTVM to the anode and run your exciter at low power into the amplifier's input connector. Tune the screen series-tuned bypass circuit for a distinct dip on the VTVM. The dip will be sharp and the VTVM reading should go to zero.
- 4. Now, disconnect the 2700- Ω carbon



Fig 18.38—Close-up photo of the input circuitry for the 6-meter kW amplifier. Input tuning capacitor C2 is adjusted from the rear panel during operation, if necessary. The series-tuning capacitor C7 used to thoroughly ground the screen for RF is shown at the lower right. It is adjusted through a normally plugged hole in the rear panel during initial adjustment only.

resistor from the anode and replace the covers. Connect the power supply and control circuitry. When you apply power to the amplifier, you should find that only a slight tweaking of the output controls will be needed for final adjustment.

A 144-MHz Amplifier Using the 3CX1200Z7

This 2-meter, 1-kW amplifier uses the Eimac 3CX1200Z7 triode. The original article by Russ Miller, N7ART, appeared in December 1994 *QST*. The tube requires a warm up of about 10 seconds after applying filament voltage—no more waiting for three agonizingly long minutes until an amplifier can go on-line!

The 3CX1200Z7 is different from the earlier 3CX1200A7 by virtue of its external grid ring, redesigned anode assembly and a 6.3-V ac filament. One advantage to the 3CX1200Z7 is the wide range of plate voltages that can be used, from 2000 to 5500 V. This amplifier looks much like the easily duplicated W6PO design. The RF deck is a compact unit, designed for table-top use (See **Fig 18.39** and schematic



in Fig 18.40.).

Table 18.8 gives some data on the3CX1200Z7 and Table 18.9 lists CWoperating performance for this amplifier.

Input Circuit

The author didn't use a tube socket. Instead, he bolted the tube directly to the top plate of the subchassis, using the four holes (drilled to clear a #6 screw) in the grid flange. Connections to the heater pins are via drilled and slotted brass rods. The

Fig 18.39—This table-top 2-meter power amplifier uses a quick-warm-up tube, a real plus when the band suddenly opens for DX and you want to join in.



- C1-C4-100 pF, 5 kV, Centralab 850.
- C5-1000 pF, 5 kV.
- C6—Anode-tuning capacitor; see text and Fig 18.46 for details.
- C7-Output-loading capacitor; see text and Fig 18.47 for details.
- C8-C10, C13-1000-pF silver mica, 500 V.
- C11—30-pF air variable.
- C12-0.01 µF, 1 kV.
- D1-1000 PIV, 3-A diode, 1N5408 or equiv.
- D2-8.2-V, 50-W Zener diode, ECG 5249A.

- J1-Chassis-mount BNC connector. J2—Type-N connector fitted to output
- coupling assembly (see Fig 18.47). L1, L2—Plate lines; see text and Fig
- 18.45 for details. L3—5 t #14 enameled wire, 1/2-inch diameter, close wound.
- L4-3 t #14, 5/8-inch diameter, 1/4-inch spacing.
- RFC1-7 t #14, 5/8-inch diameter, 13/8 inch long.
- RFC2, RFC3-10 t #12, 5/8-inch diameter, 2 inches long.

- Fig 18.40—Schematic diagram of the 2-meter amplifier RF deck. For supplier addresses, use TISFind or other search engines.
 - T1—Filament transformer. Primary: 120 V; secondary: 6.3 V, 25 A, center tapped. Available from Avatar Magnetics; part number AV-539.
 - M1-Grid milliammeter, 200 mA dc full scale.
 - M2—Cathode ammeter, 2 A dc full scale.
 - MOT1-140 free-air cfm, 120-V ac blower, Dayton 4C442 or equivalent.
 - Sources for some of the hard to get parts include Fair Radio Sales and Surplus Sales of Nebraska.

Table 18.8 3CX1200Z7 Specifications

Maximum Ratings Plate voltage: 5500 V Plate current: 800 mA Plate dissipation: 1200 W Grid dissipation: 50 W

Table 18.9 CW Operating Data

Plate voltage: 3200 V Plate current (operating): 750 mA Plate current (idling): 150 mA Grid current: 165 mA DC Power input: 2400 W RF Power output: 1200 W Plate dissipation: 1200 W Efficiency: 50% Drive power: 85 W Input reflected power: 1 W



Fig 18.41—This view of the cathode-circuit compartment shows the input tuned circuit and filament chokes.



input circuit is contained within a $3^{1/2} \times 6 \times 7^{1/4}$ -inch (HWD) subchassis (Fig 18.40).

Control Circuit

The control circuit (**Fig 18.42**) is a necessity. It provides grid overcurrent protection, keying control and filament surge control. To protect the tube filament from stressful surge current, a timer circuit places a resistor in series with the primary of the filament transformer. After four seconds, the timer shorts the resistor, allowing full filament voltage to be applied. C2 and R4 establish the time delay.

Another timer inhibits keying for a total of 10 seconds, to give the internal tube temperatures a chance to stabilize. C1 and R3 determine the time constant of this timer. After 10 seconds, the amplifier can be keyed by grounding the keying line. When the amplifier is not keyed, it draws







Fig 18.44—Anode collet details.



Fig 18.42—(Schematic diagram of the amplifier-control circuits. C3-0.47-µF, 25-V tantalum capacitor. D1-D5-1N4001 or equiv. D6-1N4007 or equiv. DS1—Yellow LED. DS2—Green LED. DS3—Red LED. K1—Keying-inhibit relay, DPDT, 12-V dc coil, 1-A contact rating (RadioShack 275-249 or equiv). K2—Amplifier keying relay, SPDT, 12-V dc coil, 2-A contact rating (RadioShack 275-248 or equiv). K3-Filament delay relay, SPST, 12-V dc coil, 2-A contact rating (RadioShack 275-248 or equiv). K4-Grid-overcurrent relay, DPDT, 12-V dc coil, 1-A contact rating (RadioShack 275-249 or equiv). Q1, Q2, Q5—2N2222A or equiv. Q3-MPF102 or equiv. Q4-2N3819 or equiv. S1-Normally closed, momentary pushbutton switch (RadioShack 275-1549 or equiv). T1—Power transformer, 120-V primary, 18-V, 1-A secondary. U1-+12 V regulator, 7812 or equiv.



no plate current. When keyed, idle current is approximately 150 mA, and the amplifier only requires RF drive to produce output. A safety factor is built in: The keying circuit requires +12 V from the highvoltage supply. This feature ensures that high voltage is present before the amplifier is driven.

The grid overcurrent circuit should be

Fig 18.45—Plate line details.



Fig 18.46—Plate tuning capacitor details.



Fig 18.47—Details of the output coupling assembly.

set to trip if grid current reaches 200 mA. When it trips, the relay latches and the NORMAL LED extinguishes. Restoration requires the operator to press the RESET switch.

Plate Circuit

Fig 18.43 shows an interior view of the plate compartment. A $4 \times 2^{1/4}$ -inch tuning capacitor plate and a 2×2 -inch output coupling plate are centered on the anode collet. See Fig 18.44. Sufficient clearance in the collet hole for the 3CX1200Z7 anode must be left for the fingerstock. The hole diameter will be approximately $3^{5/8}$ inches. Fig 18.45 is a drawing of the plate line, Fig 18.46 is a drawing of the plate tuning capacitor assembly, and Fig 18.47 shows the output coupling assembly.

Cooling

The amplifier requires an air exhaust through the top cover, as the plate compartment is pressurized. Fashion a chimney from a $3^{1/2}$ -inch waste-water coupling (black PVC) and a piece of $1/3^2$ -inch-thick Teflon sheet. The PVC should extend down from the underside of the amplifier cover plate by $1^{1/8}$ inches, with the Teflon sheet extending down 3/4 inch from the bottom of the PVC.

The base of the 3CX1200Z7 is cooled using bleed air from the plate compartment. This is directed at the tube base, through a ⁷/s-inch tube set into the subchassis wall at a 45° angle. The recommended blower will supply more than enough air for any temperature zone. A smaller blower is not recommended, as it is doubtful that the base area will be cooled adequately. The 3CX1200Z7 filament draws 25 A at 6.3 V! It alone generates a great deal of heat around the tube base seals and pins, so good air flow is critical.

Construction

The amplifier is built into a $12 \times 12 \times 10$ -inch enclosure. A 12×10 -inch partition is installed 7¹/₄ inches from the rear panel. The area between the partition and the front panel contains the filament transformer, control board, meters, switches, Zener diode and miscellaneous small parts. Wiring between the front-panel area and the rear panel is through a ¹/₂-inch brass tube, located near the shorted end of the right-hand plate line.

High voltage is routed from an MHV jack on the rear panel, through a piece of soliddielectric RG-59 (not foam dielectric!), just under the shorted end of the left-hand plate line. The cable then passes through the partition to a high-voltage standoff insulator



Fig 18.48—Schematic diagram of output harmonic filter. C1, C2—27-pF Centralab 850 series ceramic transmitting capacitor.

J1, J2—Female chassis-mount N connector (UG-58 or equiv).

L1, L3—2 t #14 wire, 0.3125 inch ID, 0.375 inch long. L2—3 t #14 wire, 0.3125 inch ID, 0.4375 inch long.

made from nylon. This insulator is fastened to the partition near the high-voltage feedthrough capacitor. A 10- Ω , 25-W resistor is connected between the insulator and the feedthrough capacitor.

The plate lines are connected to the dcblocking capacitors on the plate collet with $1^{3}/_{4} \times 2$ -inch phosphor-bronze strips. The bottom of the plate lines are attached to the sides of the subchassis, with the edge of the L-shaped mounting bracket flush with the bottom of the subchassis.

When preparing the subchassis top plate for the 3CX1200Z7, cut a $2^{11}/_{16}$ -inch hole in the center of the plate. This hole size allows clearance between the tube envelope and the top plate, without putting stress on the envelope in the vicinity of the grid flange seal.

Exercise care in placing the movable tuning plate and the movable output coupling disc, to ensure they cannot touch their fixed counterparts on the plate collet.

Operation

When the amplifier is first turned on, it cannot be keyed until:

- 10 seconds has elapsed.
- High voltage is available, as confirmed by presence of +12 V to the keying circuit.

Table 18.10 Power Supply Specifications High voltage: 3200 V Continuous current: 1.2 A

Intermittent current: 2 A

Step/Start delay: 2 secs

Connect the amplifier to a dummy load through an accurate power meter capable of indicating 1500 W full scale. Key the amplifier and check the idling plate current. With 3200-V plate voltage, it should be in the vicinity of 150 mA. Now, apply a small amount of drive and adjust the input tuning for maximum grid current. Adjust the output tuning until you see an indication of RF output. Increase drive and adjust the output coupling and tuning for the desired output. Do not overcouple the output; once desired output is reached, do not increase loading. Insert the hold-down screw to secure the output coupling capacitor from moving. One setting is adequate for tuning across the 2-meter band if the SWR on the transmission line is reasonably low.

When you shut down the amplifier, leave the blower running for at least three minutes after you turn off the filament voltage. The 3CX1200Z7 is an excellent tube. The author tried it with excessive drive, platecurrent saturation, excessive plate dissipation—all the abuse it's likely to encounter in amateur applications. There were no problems, but that doesn't mean you should repeat these torture tests!

A Companion Power Supply

A well-designed and constructed highvoltage power supply is necessary to ensure linearity in SSB operation. Specifications of the power supply for this amplifier are given in **Table 18.10**. A schematic and parts list for a rugged power supply usable with this project—are in the **Power Supplies** chapter. Although bi-level, it is otherwise similar to the author's design described in the December 1994 issue of *QST*.

Conclusion

This amplifier is a reliable and costeffective way to generate a big 2-meter signal—almost as quickly as a solid-state amplifier. To ensure that the output of the amplifier meets current spectral purity requirements, a high-power output filter, as shown in **Fig 18.48**, should be used. The author reports that he can run full output while his wife watches TV in a nearby room.