

Contents

- 9.1 How Oscillators Work
 - 9.1.1 Maintained Resonance
 - 9.1.2 Amplification
 - 9.1.3 Start-Up
- 9.2 Phase Noise
 - 9.2.1 Effects of Phase Noise
 - 9.2.2 Reciprocal Mixing
 - 9.2.3 A Phase Noise Demonstration
 - 9.2.4 Measuring Receiver Phase Noise
 - 9.2.5 Measuring Oscillator and Transmitter Phase Noise
 - 9.2.6 Low-Cost Phase Noise Testing
- 9.3 Oscillator Circuits and Construction
 - 9.3.1 LC Oscillator Circuits
 - 9.3.2 RC Oscillators
 - 9.3.3 Three High-Performance HF VFOs
 - 9.3.4 VFO Components and Construction
 - 9.3.5 Temperature Compensation
 - 9.3.6 Shielding and Isolation
- 9.4 Designing an Oscillator
- 9.5 Quartz Crystals in Oscillators
 - 9.5.1 Quartz and the Piezoelectric Effect
 - 9.5.2 Frequency Accuracy
 - 9.5.3 The Equivalent Circuit of a Crystal
 - 9.5.4 Crystal Oscillator Circuits
 - 9.5.5 VXOs
 - 9.5.6 Logic-Gate Crystal Oscillators
- 9.6 Oscillators at UHF and Above
 - 9.6.1 UHF Oscillators
 - 9.6.2 Microwave Oscillators
 - 9.6.3 Klystrons, Magnetrons and Traveling Wave Tubes
- 9.7 Frequency Synthesizers
 - 9.7.1 Phase-Locked Loops (PLL)
 - 9.7.2 A PLL Design Example
 - 9.7.3 PLL Measurements
 - 9.7.4 Common Problems in PLL Design
 - 9.7.5 Synthesizer ICs
 - 9.7.6 Improving VCO Noise Performance
 - 9.7.7 Microprocessor Control of Synthesizers
 - 9.7.8 The Role of DDS in Recent Hybrid Architectures
 - 9.7.9 Multi-Phase Division
- 9.8 Present and Future Trends in Oscillator Application
- 9.9 Glossary of Oscillator and Synthesizer Terms
- 9.10 References and Bibliography

Oscillators and Synthesizers

Just say in public that oscillators are one of the most important, fundamental building blocks in radio technology and you will immediately be interrupted by someone pointing out that tuned-RF (TRF) receivers can be built without any form of oscillator at all. This is certainly true, but it shows how some things can be taken for granted. What use is any receiver without signals to receive? All intentionally transmitted signals trace back to some sort of signal generator — an oscillator or frequency synthesizer. In contrast with the TRF receivers just mentioned, a modern, all-mode, feature-laden MF/HF transceiver may contain in excess of a dozen RF oscillators and synthesizers, while a simple QRP CW transmitter may consist of nothing more than a single oscillator.

This chapter, which includes material contributed by David Stockton, GM4ZNX, Frederick J. Telewski, WA7TZY, and Jerry DeHaven, WA0ACF, explores the design, application and performance characteristics of various types of oscillators and frequency synthesizers. Ulrich Rohde, N1UL, contributed two appendices on phase noise and oscillator design which may be found on the *Handbook* CD-ROM.

In the 1980s, the main area of progress in the performance of radio equipment was the recognition of receiver intermodulation as a major limit to our ability to communicate, with the consequent development of receiver front ends with improved ability to handle large signals. So successful was this campaign that other areas of transceiver performance now required similar attention. One indication of this is any equipment review receiver dynamic range measurement qualified by a phrase like “limited by oscillator phase noise.” A plot of a receiver’s effective selectivity can provide another indication of work to be done: An IF filter’s high-attenuation region may appear to be wider than the filter’s published specifications would suggest — almost as if the filter characteristic has grown sidebands! In fact, in a way, it has: This is the result of local-oscillator (LO) or synthesizer *phase noise* spoiling the receiver’s overall performance.

The sheer number of different oscillator circuits can be intimidating, but their great diversity is an illusion that evaporates once their underlying pattern is seen. Almost all RF oscillators share one fundamental principle of operation: an amplifier and a filter operate in a loop (Fig 9.1). There are plenty of filter types to choose from:

- LC
- Quartz crystal and other piezoelectric materials
- Transmission line (stripline, microstrip, open-wire, coax, and so on)
- Microwave cavities, YIG spheres, dielectric resonators
- Surface-acoustic-wave (SAW) devices

Should any new forms of filter be invented, it’s a safe guess that they will also be applicable to oscillators. There is an equally large range of amplifiers to choose from:

- Vacuum tubes of all types
- Bipolar junction transistors
- Field effect transistors (JFET, MOSFET, GaAsFET, in all their varieties)
- Gunn diodes, tunnel diodes and other negative-resistance generators

It seems superfluous to state that anything that can amplify can be used in an oscillator, because of the well-known propensity of all prototype amplifiers to oscillate! The choice of amplifier is widened further by the option of using single- or multiple-stage amplifiers and discrete devices versus integrated circuits. Multiply all of these options with those of filter choice and the resulting set of combinations is very large, but a long way from complete. Then there are choices of how to couple the amplifier into the filter and the filter into the amplifier. And then there are choices to make in the filter section: Should it be tuned by variable capacitor, variable inductor or some form of sliding cavity or line?

Despite the number of combinations that are possible, a manageably small number of types will cover all but very special requirements. Look at an oscillator circuit and “read” it: What form of filter — *resonator* — does it use? What form of amplifier? How have the amplifier’s input and output been coupled into the filter? How is the filter tuned? These are simple, easily answered questions that put oscillator types into appropriate categories and make them understandable. The questions themselves may make more sense if we understand the mechanics of oscillation, in which *resonance* plays a major role.

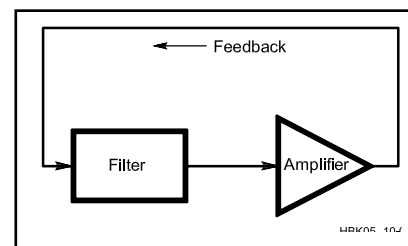


Fig 9.1 — Reduced to essentials, an oscillator consists of a filter and an amplifier operating in a feedback loop.

9.1 How Oscillators Work

9.1.1 Maintained Resonance

The pendulum, a good example of a resonator, has been known for millennia and understood for centuries. It is closely analogous to an electronic resonator, as shown in Fig 9.2. The weighted end of the pendulum can store energy in two different forms: The *kinetic energy* of its motion and the *potential energy* of it being raised above its rest position. As it reaches its highest point at the extreme of a swing, its velocity is zero for an instant as it reverses direction. This means that it has, at that instant, no kinetic energy, but because it is also raised above its rest position, it has some extra potential energy.

At the center of its swing, the pendulum is at its lowest point with respect to gravity and so has lost the extra potential energy. At the same time, however, it is moving at its highest speed and so has its greatest kinetic energy. Something interesting is happening: The pendulum's stored energy is continuously moving between potential and kinetic forms. Looking at the pendulum at intermediate positions shows that this movement of energy is smooth. Newton provided the keys to understanding this. It took his theory of gravity and laws of motion to explain the behavior of a simple weight swinging on the end of a length of string and calculus to perform a quantitative mathematical analysis. Experiments had shown the period of a pendulum to be very stable and predictable. Apart from side effects of air drag and friction, the length of the period should not be affected by the mass of the weight, or by the amplitude of the swing.

A pendulum can be used for timing events, but its usefulness is spoiled by the action of drag or friction, which eventually stops it. This problem was overcome by the invention of the *escapement*, a part of a clock mechanism that senses the position of the pendulum and applies a small push in the right direction and at the right time to maintain the amplitude of its swing or oscillation. The result is a mechanical oscillator: The pendulum acts as the filter, the escapement acts as the amplifier and a weight system or wound-up spring powers the escapement.

Electrical oscillators are closely analogous to the pendulum, both in operation and in development. The voltage and current in the tuned circuit — often called *tank circuit* because of its ability to store energy — both vary sinusoidally with time and are 90° out of phase. There are instants when the current is zero, so the energy stored in the inductor must be zero, but at the same time the voltage across the capacitor is at its peak, with all of the circuit's energy stored in the electric field between the capacitor's plates. There

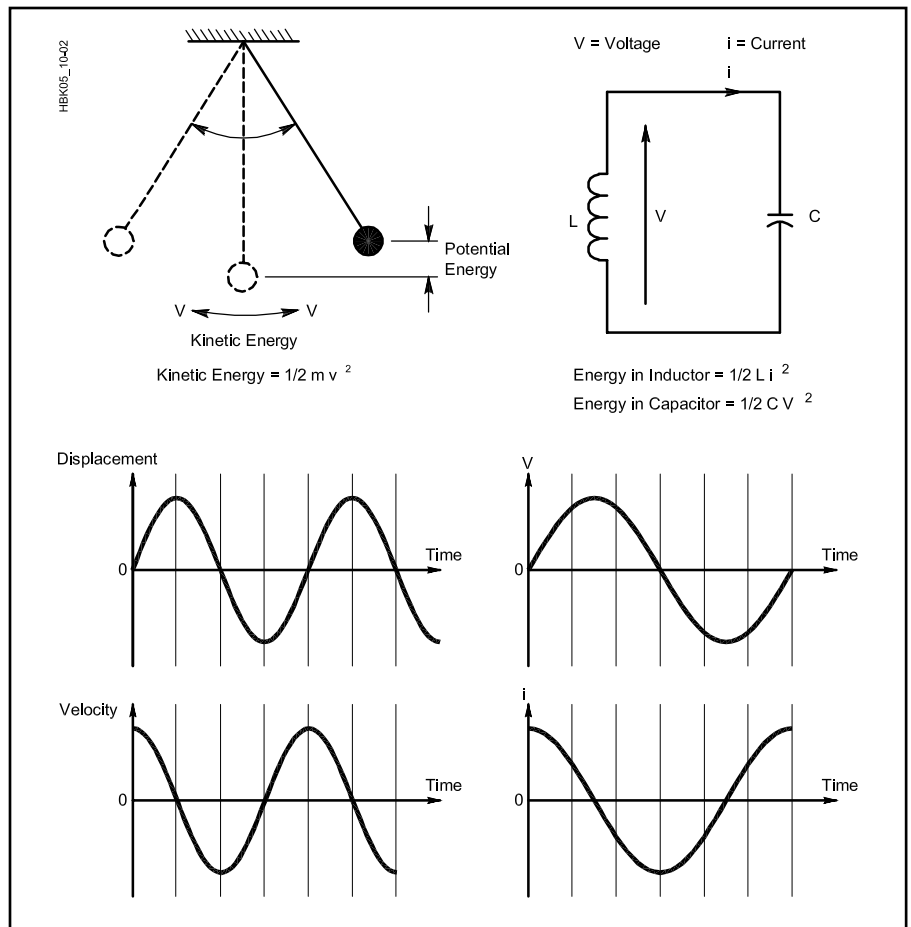


Fig 9.2 — A resonator lies at the heart of every oscillatory mechanical and electrical system. A mechanical resonator (here, a pendulum) and an electrical resonator (here, a tuned circuit consisting of L and C in parallel) share the same mechanism: the regular movement of energy between two forms — potential and kinetic in the pendulum, electric and magnetic in the tuned circuit. Both of these resonators share another trait: Any oscillations induced in them eventually die out because of losses — in the pendulum, due to drag and friction; in the tuned circuit, due to the resistance, radiation and inductance. Note that the curves corresponding to the pendulum's displacement vs velocity and the tuned circuit's voltage vs current, differ by one-quarter of a cycle, or 90°.

are also instants when the voltage is zero and the current is at a peak, with no energy in the capacitor. Then, all of the circuit's energy is stored in the inductor's magnetic field.

Just like the pendulum, the energy stored in the electrical system is swinging smoothly between two forms; electric field and magnetic field. Also like the pendulum, the tank circuit has losses. Its conductors have resistance, and the capacitor dielectric and inductor core are imperfect. Leakage of electric and magnetic fields also occurs, inducing currents in neighboring objects and just plain radiating energy off into space as radio waves. The amplitudes of the oscillating voltage and current decrease steadily as a result. Early intentional radio transmissions, such as those of Heinrich Hertz's experiments, involved abruptly dumping energy into a tuned circuit

and letting it oscillate, or *ring*, as shown in Fig 9.3. This was done by applying a spark to the resonator. Hertz's resonator was a gapped ring, a good choice for radiating as much of the energy as possible. Although this looks very different from the LC tank of Fig 9.2, it has inductance *distributed* around its length and capacitance distributed across it and across its gap, as opposed to the *lumped* L and C values in Fig 9.2. The gapped ring therefore works just the same as the LC tank in terms of oscillating voltages and currents. Like the pendulum and the LC tank, its period, and therefore the frequency at which it oscillates, is independent of the magnitude of its excitation.

Making a longer-lasting signal with the Fig 9.3 arrangement merely involves repeating the sparks. The problem is that a truly

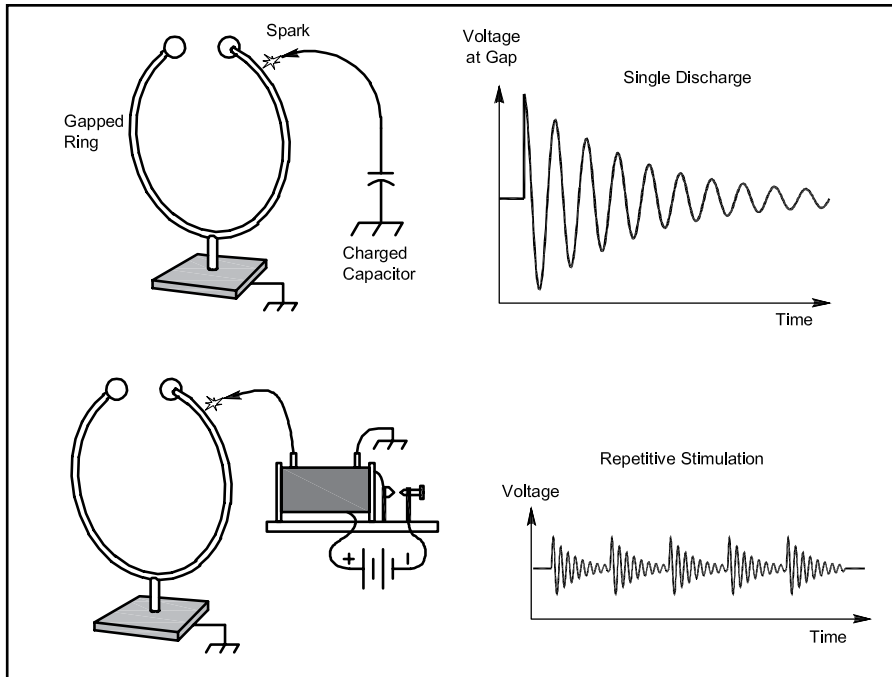


Fig 9.3 — Stimulating a resonance, 1880s style. Shock-exciting a gapped ring with high voltage from a charged capacitor causes the ring to oscillate at its resonant frequency. The result is a damped wave, each successive alternation of which is weaker than its predecessor because of resonator losses. Repetitively stimulating the ring produces trains of damped waves, but oscillation is not continuous.

continuous signal cannot be made this way. The sparks cannot be applied often enough or always timed precisely enough to guarantee that another spark re-excites the circuit at precisely the right instant. This arrangement amounts to a crude spark transmitter, variations of which served as the primary means of transmission for the first generation of radio amateurs. The use of damped waves is now entirely forbidden by international treaty because of their great impurity. Damped waves look a lot like car-ignition waveforms and sound like car-ignition interference when received.

What we need is a *continuous wave (CW)* oscillation — a smooth, sinusoidal signal of constant amplitude, without phase jumps, a “pure tone.” To get it, we must add to our resonator an equivalent of the clock’s escapement — a means of synchronizing the application of energy and a fast enough system to apply just enough energy every cycle to keep each cycle at the same amplitude.

9.1.2 Amplification

A sample of the tank’s oscillation can be extracted, amplified and reinserted. The gain can be set to exactly compensate the tank losses and perfectly maintain the oscillation. The amplifier usually only needs to give low gain, so active devices can be used in oscillators not far below their unity-gain frequency. The amplifier’s output must be lightly coupled

into the tank — the aim is just to replace lost energy, not forcibly drive the tank. Similarly, the amplifier’s input should not heavily load the tank. It is a good idea to think of *coupling* networks rather than *matching* networks in this application, because a matched impedance extracts the maximum available energy from a source, and this would certainly spoil an oscillator.

Fig 9.4A shows the block diagram of an oscillator. Certain conditions must be met for oscillation. The criteria that separate oscillator loops from stable loops are often attributed to Barkhausen by those aiming to produce an oscillator and to Nyquist by those aiming for amplifier stability, although they boil down to the same set of constraints for the circuit. Fig 9.4B shows the loop broken and a test signal inserted. (The loop can be broken anywhere; the amplifier input just happens to be the easiest place to do it.)

The *Barkhausen criterion* for oscillation says that at a frequency at which the phase shift around the loop is exactly zero, the net gain around the loop must equal or exceed unity (that is, one). (Later, when we design phase-locked loops, we must revisit this concept in order to check that those loops *cannot* oscillate.) Fig 9.4C shows what happens to the amplitude of an oscillator if the *loop gain* (total gain of all devices around the loop) is made a little higher or lower than one. (In many treatments of the Barkhausen criterion, the feedback block is shown as a filter. The

resonator and coupling networks shown here perform the same function.)

The loop gain has to be precisely one if we want stable amplitude. Any inaccuracy will cause the amplitude to grow to clipping or shrink to zero, making the oscillator useless. Better accuracy will only slow, not stop this process. Perfect precision is clearly impossible, yet there are enough working oscillators in existence to prove that we are missing something important. In an amplifier, nonlinearity is a nuisance, leading to signal distortion and intermodulation, yet nonlinearity is what makes stable oscillation possible. All of the vacuum tubes and transistors used in oscillators tend to reduce their gain at higher signal levels. With such components, only a tiny change in gain can shift the loop’s operation between amplitude growth and shrinkage. Oscillation stabilizes at that level at which the gain of the active device sets the loop gain at exactly one.

Another gain-stabilization technique involves biasing the device so that once some level is reached, the device starts to turn off over part of each cycle. At higher levels, it cuts off over more of each cycle. This effect reduces the effective gain quite strongly, stabilizing the amplitude. This badly distorts the signal (true in most common oscillator circuits) in the amplifying device, but provided the amplifier is lightly coupled to a high-Q resonant tank, the signal in the tank should not be badly distorted.



Textbooks give plenty of coverage to the frequency-determining mechanisms of oscillators, but the amplitude-determining mechanism is rarely covered. It is often not even mentioned. There is a good treatment in Clarke and Hess, *Communications Circuits: Analysis and Design*.

9.1.3 Start-Up

Perfect components don’t exist, but if we could build an oscillator from them, we would naturally expect perfect performance. We would nonetheless be disappointed. We could assemble from our perfect components an oscillator that exactly met the criterion for oscillation, having slightly excessive gain that falls to the correct amount at the target operating level and so is capable of sustained, stable oscillation. But being capable of something is not the same as doing it, for there is another stable condition. If the amplifier in the loop shown in Fig 9.4A has no input signal, and is perfect, it will give no output! No signal returns to the amplifier’s input via the resonator, and the result is a sustained and stable *lack* of oscillation. Something is needed to start the oscillator.

This fits the pendulum-clock analogy: A wound-up clock is stable with its pendulum at rest, yet after a push the system will sustain

Fig 9.4 — The bare-bones oscillator block diagram of Fig 9.1 did not include two practical essentials: Networks to couple power in and out of the resonator (A). Breaking the loop, inserting a test signal and measuring the loop's overall gain (B) allows us to determine whether the system can oscillate, sustain oscillation or clip (C).

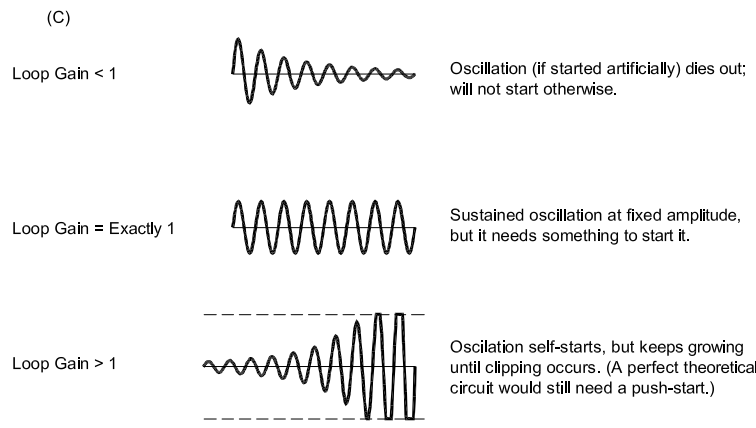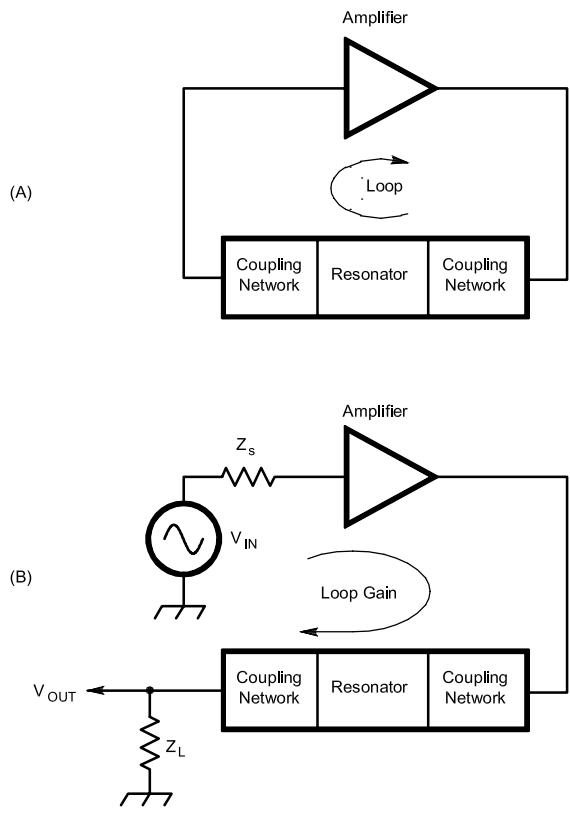

oscillation. The mechanism that drives the pendulum is similar to a Class C amplifier: It does not act unless it is driven by a signal that exceeds its threshold. An electrical oscillator based on a Class C amplifier can sometimes be kicked into action by the turn-on transient of its power supply. The risk is that this may not always happen and should some external influence stop the oscillator, it will not restart until someone notices the problem and cycles the power. This can be very inconvenient!

A real-life oscillator whose amplifier does not lose gain at low signal levels can self-start due to noise. Fig 9.5 shows an oscillator block diagram with the amplifier's noise shown, for our convenience, as a second input that adds with the true input. The amplifier amplifies the noise. The resonator filters the output noise, and this signal returns to the amplifier input. The importance of having slightly excessive gain until the oscillator reaches operating amplitude is now obvious. If the loop gain is slightly above one, the recirculated noise must, within the resonator's bandwidth, be larger than its original level at the input. More noise is continually summed in as a noise-like signal continuously passes around the loop, undergoing amplification and filtering as it does. The level increases, causing the gain to reduce. Eventually, it stabilizes at whatever level is necessary to make the net loop gain equal to one.

So far, so good — the oscillator is running at its proper level, but something seems very wrong. It is not making a proper sine wave; it is recirculating and filtering a noise signal. It can also be thought of as a “Q multiplier” — a controlled (high) gain amplifier, filtering a noise input and amplifying it to a set level. Narrow-band filtered noise approaches a true sine wave as the filter is narrowed to zero width. What this means is that we cannot make a true sine-wave signal — all we can do is make narrow-band filtered noise as an approximation. A high-quality, “low-noise oscillator is merely one that does tighter filtering. Even a kick-started Class-C-amplifier oscillator has noise continuously adding to its circulating signal, and so behaves similarly.

A small-signal gain greater than one is absolutely critical for reliable starting, but having too much gain can make the final operating level unstable. Some oscillators are designed around limiting amplifiers to make their operation predictable. AGC systems have also been used, with an RF detector and dc amplifier used to servo-control the amplifier gain. It is notoriously difficult to design reliable crystal oscillators that can be published or mass-produced without

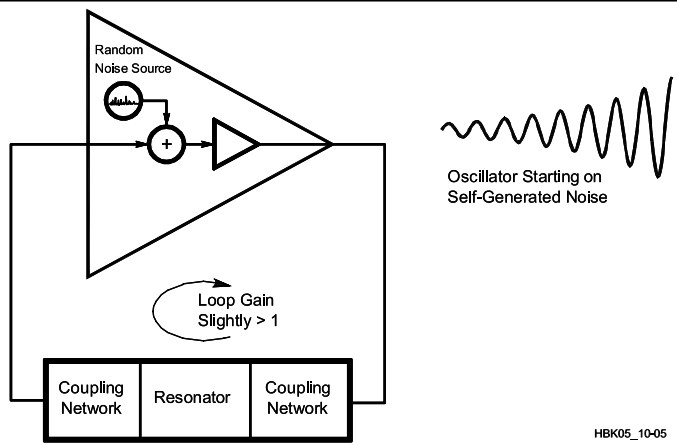


Fig 9.5 — An oscillator with noise. Real-world amplifiers, no matter how quiet, generate some internal noise; this allows real-world oscillators to self-start.

having occasional individuals refuse to start without some form of shock.

Mathematicians have been intrigued by “chaotic systems” where tiny changes in initial

conditions can yield large changes in outcome. The most obvious example is meteorology, but much of the necessary math was developed in the study of oscillator start-up, because it is


a case of chaotic activity in a simple system. The equations that describe oscillator start-up are similar to those used to generate many of the popular, chaotic fractal images.

9.2 Phase Noise

Viewing an oscillator as a filtered-noise generator is relatively modern. The older approach was to think of an oscillator making a true sine wave with an added, unwanted noise signal. These are just different ways of visualizing the same thing: They are equally valid views, which are used interchangeably, depending which best makes some point clear. Thinking in terms of the signal-plus-noise version, the noise surrounds the carrier, looking like sidebands and so can also be considered to be equivalent to random-noise FM and AM on the ideal sine-wave signal. This gives us a third viewpoint. These noise sidebands are called *phase noise*. If we consider the addition of a noise voltage to a sinusoidal voltage, we must take into account the phase relationship. A *phasor diagram* is the clearest way of illustrating this. **Fig 9.6A** represents a clean sine wave as a rotating vector whose length is equal to the peak amplitude and whose frequency is equal to the number of revolutions per second of its rotation. Moving things are difficult to depict on paper, so phasor diagrams are usually drawn to show the dominant signal as stationary, with other components drawn relative to this. (Tutorials on complex numbers, vectors, and phasor notation are available at www.intmath.com. In addition, performing an Internet search for “phasor tutorial” will turn up several excellent Web pages on the subject.)

Noise contains components at many frequencies, so its phase with respect to the dominant, theoretically pure signal — the “carrier” — is random. Its amplitude is also random. Noise can only be described in statistical terms because its voltage is constantly and randomly changing, yet it does have an average amplitude that can be expressed as an RMS value. Fig 9.6B shows noise added to the carrier phasor, with the noise represented as a region in which the sum phasor wanders randomly. The phase of the noise is uniformly random — no direction is more likely than any other — but the instantaneous magnitude

Fig 9.6 — At A, a phasor diagram of a clean (ideal) oscillator. Noise creates a region of uncertainty in the vector’s length and position (B). AM noise varies the vector’s length; PM noise varies the vector’s relative angular position (C) Limiting a signal that contains both AM and PM noise strips off the AM and leaves the PM (D).

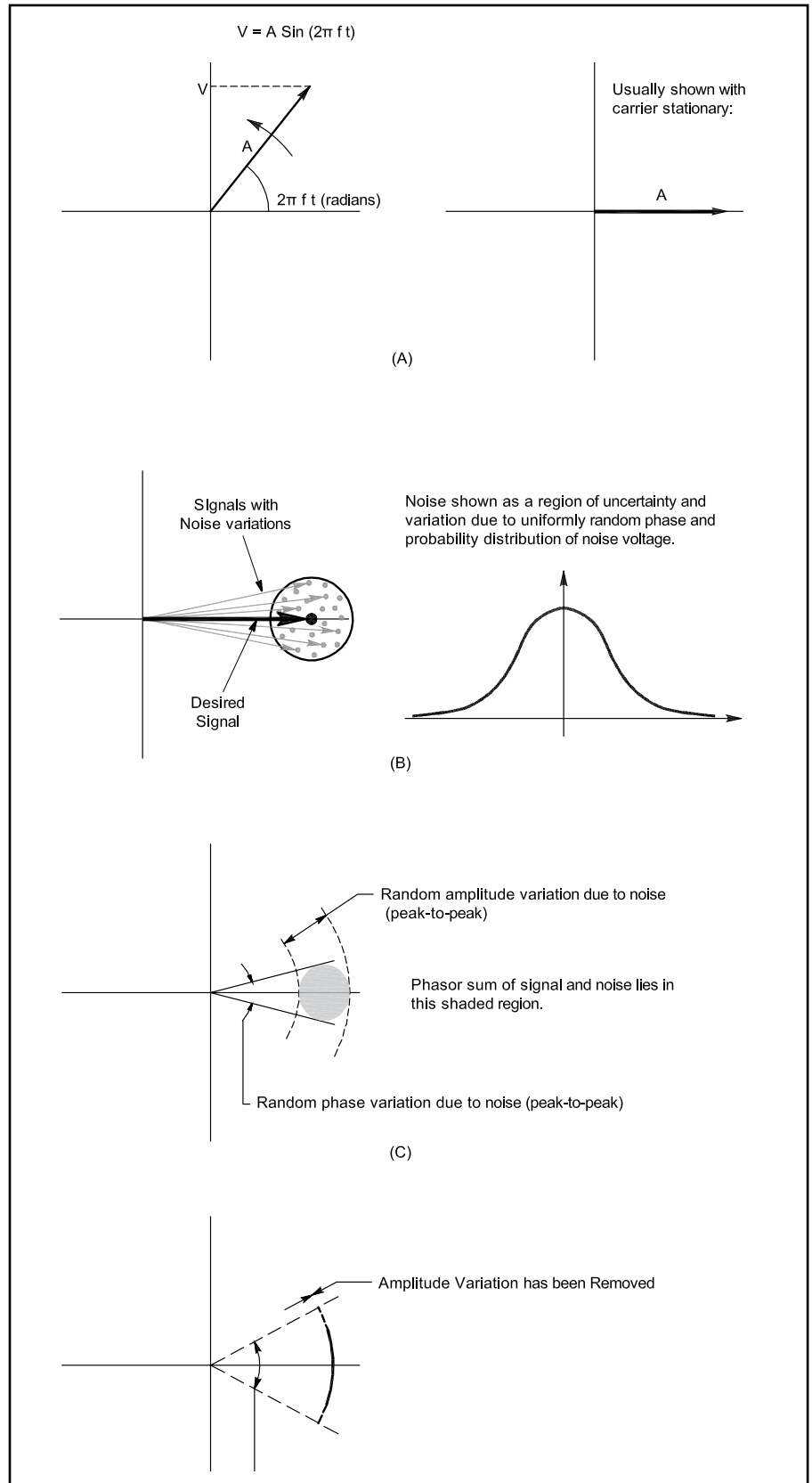

of the noise obeys a probability distribution like that shown, with values farther from the normal carrier frequency being progressively rarer. Fig 9.6C shows how the extremities of the noise region can be considered as extremes of phase and amplitude variation from the normal values of the carrier.

Phase modulation and frequency modulation are closely related. Phase is the integral of frequency, so phase modulation resembles frequency modulation in which deviation decreases with increasing modulating frequency. Thus, there is no need to talk of “frequency noise” because phase noise already covers it.

Fig 9.6C clearly shows AM noise as the random variation of the length of the sum phasor, yet “amplitude noise” is rarely discussed. The oscillator’s amplitude control mechanism acts to reduce the AM noise by a small amount, but the main reason is that the output is often fed into some form of limiter that strips off AM components just as the limiting IF amplifier in an FM receiver removes any AM on incoming signals. The limiter can be obvious, like a circuit to convert the signal to logic levels, or it can be implicit in some other function. A diode ring mixer may be driven by a sine-wave LO of moderate power, yet this signal drives the diodes fully on and fully off, approximating square-wave switching. This is a form of limiter, and it reduces the effect of any AM on the LO. Fig 9.6D shows the result of passing a signal with noise through a limiting amplifier. For these reasons, AM noise sidebands are rarely a problem in oscillators, and so are normally ignored. There is one subtle problem to be aware of, however. If a sine wave drives some form of switching circuit or limiter, and the threshold is offset from the signal’s mean voltage, any level changes will affect the exact switching times and cause *phase jitter*. In this way, AM sidebands are translated into PM sidebands and pass through the limiter. This is usually called *AM-to-PM conversion* and is a classic problem of limiters.

A thorough analysis of oscillator phase noise is beyond the scope of this section. However, a detailed, state-of-the-art treatment by Dr Ulrich Rohde, N1UL, of free-running oscillators using nonlinear harmonic-balance techniques is presented as a supplement on the CD-ROM accompanying this book.

9.2.1 Effects of Phase Noise

You would be excused for thinking that phase noise is a recent discovery, but all oscillators have always produced it. Other changes have elevated an unnoticed characteristic up to the status of a serious impairment. Increased crowding and power levels on the ham bands, allied with greater expectations of receiver performance as a result of other

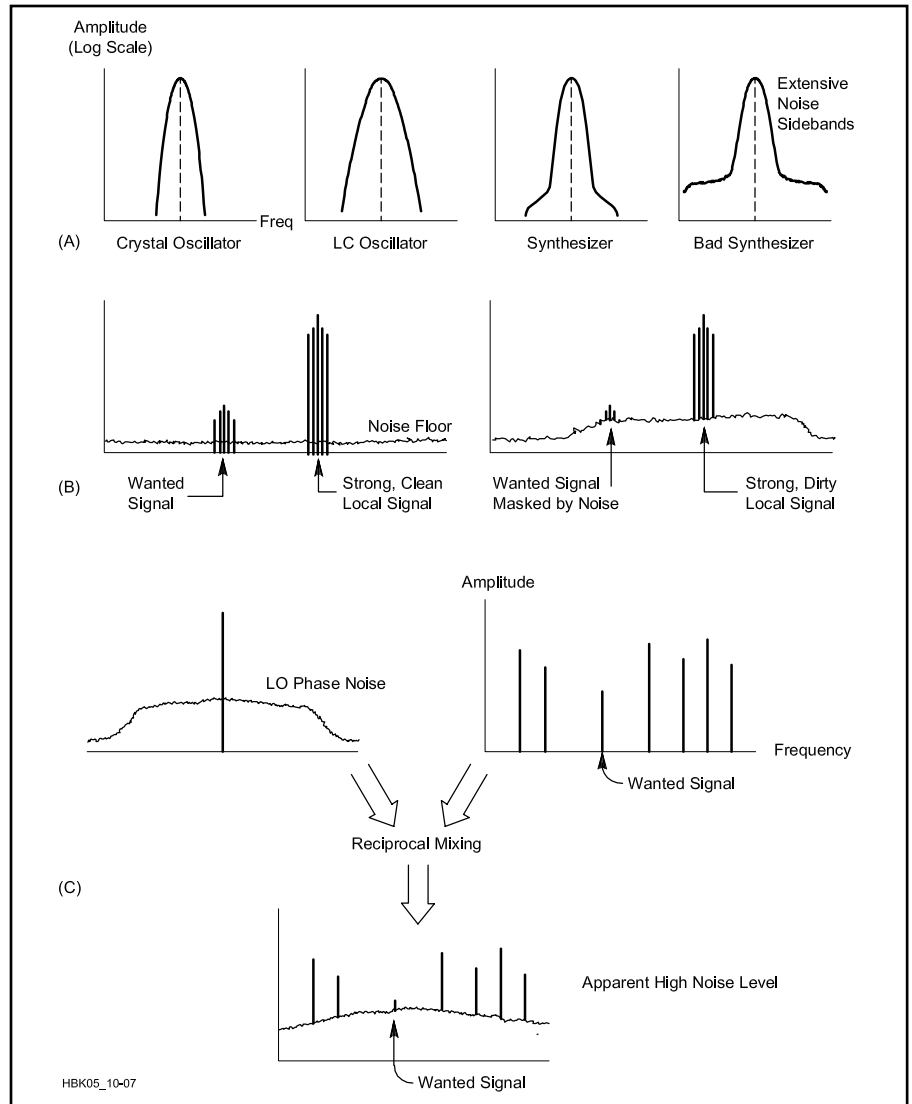


Fig 9.7 — The effects of phase noise. At A, the relative phase-noise spectra of several different signal-generation approaches. At B, how transmitted phase noise degrades the weak-signal performance even of nearby receivers with phase-quiet oscillators, raising the effective noise floor. What is perhaps most insidious about phase noise in Amateur Radio communication is that its presence in a receiver LO can allow strong, clean transmitted signals to degrade the receiver’s noise floor just as if the transmitted signals were dirty. This effect, reciprocal mixing, is shown at C.

improvements, have made phase noise more noticeable, but the biggest factor has been the replacement of analog VFOs in radios by frequency synthesizers. It is a major task to develop a synthesizer that tunes in steps fine enough for SSB and CW while competing with the phase-noise performance of a reasonable-quality LC VFO. Many synthesizers have fallen far short of that target. Phase noise is worse in higher-frequency oscillators and the trend toward general-coverage, up-converting structures has required that local oscillators operate at higher and higher frequencies. Fig 9.7A shows sketches of the relative phase-noise performance of some oscillators. The very high Q of the quartz crystal in a crystal oscillator gives it the potential for

much lower phase noise than LC oscillators. A medium-quality synthesizer has close-in phase noise performance approaching that of a crystal oscillator, while further from the carrier frequency, it degrades to the performance of a modest-quality LC oscillator. There may be a small bump in the noise spectrum at the boundary of these two zones. A bad synthesizer can have extensive noise sidebands extending over many tens (hundreds in extreme cases) of kilohertz at high levels.

Phase noise on a transmitter’s local oscillators passes through its stages, is amplified and fed to the antenna along with the intentional signal. The intentional signal is thereby surrounded by a band of noise. This radiated noise exists in the same proportion to the

transmitter power as the phase noise was to the oscillator power if it passes through no narrow-band filtering capable of limiting its bandwidth. This radiated noise makes for a noisier band. In bad cases, reception of nearby stations can be blocked over many tens of kilohertz above and below the frequency of the offending station. Fig 9.7B illustrates the difference between clean and dirty transmitters.

9.2.2 Reciprocal Mixing

The effects of receiver-LO phase noise are more complicated, but at least it doesn't affect other stations' reception. The process is called *reciprocal mixing*. This is an effect that occurs in all mixers, yet despite its name, reciprocal mixing is an LO, not a mixer, problem. Imagine that the outputs of two supposedly unmodulated signal generators are mixed together and the mixer output is fed into an FM receiver. The receiver produces sounds, indicating that the resultant signal is modulated nonetheless. Which signal generator is responsible? This is a trick question, of course. A moment spent thinking about how a change in the frequency of either input signal affects the output signal will show that FM or PM on either input reaches the output. The best answer to the trick question is therefore "either or both."

The modulation on the mixer output is the combined modulations of the inputs. This means that modulating a receiver's local oscillator is indistinguishable from using a clean LO and having the same modulation present on *all* incoming signals. (This is also true for AM provided that a fully linear multiplier is used as the mixer, but mixers are commonly driven into switching, which strips any AM off the LO signal. This is the chief reason why the phase component of oscillator noise is more important than any AM component.)

The word "indistinguishable" is important in the preceding paragraph. It does not mean that the incoming signals are themselves modulated, but that the signals in the receiver IF and the noise in the IF, sound exactly as if they were. What really happens is that the noise components of the LO are extra LO signals that are offset from the carrier frequency. Each of them mixes with other signals that are appropriately offset from the LO carrier into the receiver's IF. Noise is the sum of an infinite number of infinitesimal components spread over a range of frequencies, so the signals it mixes into the IF are spread into an infinite number of small replicas, all at different frequencies. This amounts to scrambling these other signals into noise. It is tedious to look at the effects of receiver LO phase noise this way. The concept of reciprocal mixing gives us an easier, alternative view that is much more digestible and produces identical results.

A poor oscillator can have significant noise

sidebands extending out many tens of kilohertz on either side of its carrier. This is the same, as far as the signals in the receiver IF are concerned, as if the LO were clean and every signal entering the mixer had these noise sidebands. Not only will the wanted signal (and its noise sidebands) be received, but the noise sidebands added by the LO to signals near, but outside, the receiver's IF passband will overlap it. If the band is busy, each of many signals present will add its set of noise sidebands — and the effect is cumulative. This produces the appearance of a high background-noise level on the band. Many hams tend to accept this, blaming "conditions."

Hams now widely understand reception problems due to intermodulation, and almost everyone knows to apply RF attenuation until the signal gets no clearer. Intermodulation is a nonlinear effect, and the levels of the intermod products fall by greater amounts than the reduction in the intermodulating signals. The net result is less signal, but with the intermodulation products dropped still further. This improvement reaches a limit when more attenuation pushes the desired signal too close to the receiver's noise floor.

Reciprocal mixing is a linear process, and the mixer applies the same amount of noise "deviation" to incoming signals as that present on the LO. Therefore the ratio of noise-sideband power to signal power is the same for each signal, and the same as that on the LO. Switching in RF attenuation reduces the power of signals entering the mixer, but the reciprocal mixing process still adds the noise sidebands at the same *relative* power to each. Therefore, no reception improvement results. Other than building a quieter oscillator, the only way of improving things is to use narrow preselection to band-limit the receiver's input response and reduce the number of incoming signals subject to reciprocal mixing. This reduces the number of times the phase noise sidebands get added into the IF signal. Commercial *tracking preselectors* — selective front-end circuits that tune in step with a radio's band changes and tuning, are expensive, but one that is manually tuned would make a modest-sized home-brew project and could also help reduce intermodulation effects. When using a good receiver with a linear front end and a clean LO, amateurs accustomed to receivers with poor phase-noise performance report the impression is of a seemingly emptier band with gaps between signals — and then they begin to find readable signals in some of the gaps.

Fig 9.7C shows how a noisy oscillator affects transmission and reception. The effects on reception are worst in Europe, on 40 meters, at night. Visitors from North America, and especially Asia, are usually shocked by the levels of background noise. In ITU Region

1, the long-time Amateur Radio 40 meter allocation has been 7.0 to 7.1 MHz; above this, ultra-high-power broadcasters operate. (As of 2009, Region 1 and 2 broadcasters have begun to vacate the 7.1-7.2 MHz allocation, greatly reducing noise levels in these areas.) The front-end filters in commercial ham gear are usually fixed band-pass designs that cover the wider 40-meter allocations in the other regions. This allows huge signals to reach the mixer and mix large levels of LO phase noise into the IF. Operating co-located radios, on the same band, in a multioperator contest station, requires linear front ends, preselection and state-of-the-art phase-noise performance. Outside of amateur circles, only maritime vessel operation is more demanding, with kilowatt transmitters and receivers sharing antennas on the same mast.

9.2.3 A Phase Noise Demonstration

Healthy curiosity demands some form of demonstration so the scale of a problem can be judged "by ear" before measurements are attempted. We need to be able to measure the noise of an oscillator alone (to aid in the development of quieter ones) and we also need to be able to measure the phase noise of the oscillators in a receiver (a transmitter can be treated as an oscillator). Conveniently, a receiver contains most of the functions needed to demonstrate its own phase noise.

No mixer has perfect port-to-port isolation, and some of its local-oscillator signal leaks through into the IF. If we tune a general-coverage receiver, with its antenna disconnected, to exactly 0 Hz, the local oscillator is exactly at the IF center frequency, and the receiver acts as if it is tuned to a very strong unmodulated carrier. A typical mixer might give only 40 dB of LO isolation and have an LO drive power of at least 10 mW. If we tune away from 0 Hz, the LO carrier tunes away from the IF center and out of the passband. The apparent signal level falls. Although this moves the LO carrier out of the IF passband, some of its noise sidebands will not be, and the receiver will respond to this energy as an incoming noise signal. To the receiver operator, this sounds like a rising noise floor as the receiver is tuned toward 0 Hz. To get good noise floor at very low frequencies, some professional/military receivers, like the Racal RA1772, use very carefully balanced mixers to get as much port-to-port isolation as possible, and they also may switch a crystal notch filter into the first mixer's LO feed.

This demonstration cannot be done if the receiver tunes amateur bands only. As it is, most general-coverage radios inhibit tuning in the LF or VLF region. It could be suggested by a cynic that how low manufacturers allow you to tune is an indication of how far they

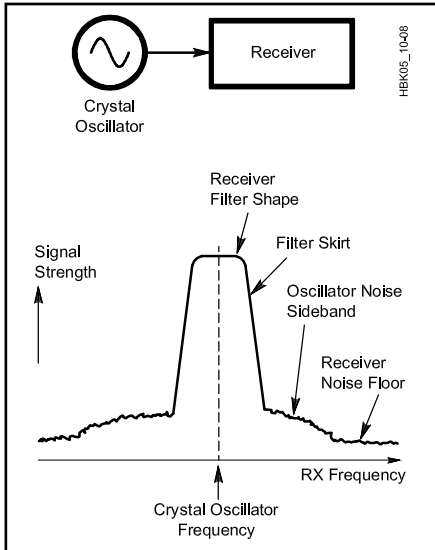


Fig 9.8 — Tuning in a strong, clean crystal-oscillator signal can allow you to hear your receiver's relative phase-noise level. Listening with a narrow CW filter switched in allows you to get better results closer to the carrier.

think their phase-noise sidebands could extend!

The majority of amateur transceivers with general-coverage receivers are programmed not to tune below 30 to 100 kHz, so means other than the “0 Hz” approach are needed to detect LO noise in these radios. Because reciprocal mixing adds the LO’s sidebands to clean incoming signals, in the same proportion to the incoming carrier as they exist with respect to the LO carrier, all we need do is to apply a strong, clean signal wherever we want within the receiver’s tuning range. This signal’s generator must have lower phase noise than the radio being evaluated. A general-purpose signal generator is unlikely to be good enough; a crystal oscillator is needed.

It’s appropriate to set the level into the receiver to about that of a strong broadcast carrier, say $S9 + 40$ dB. Set the receiver’s mode to SSB or CW and tune around the test signal, looking for an increasing noise floor (higher hiss level) as you tune closer towards the signal, as shown in Fig 9.8. Switching in a narrow CW filter allows you to hear noise closer to the carrier than is possible with an SSB filter. This is also the technique used to measure a receiver’s effective selectivity, and some equipment reviewers kindly publish their plots in this format. *QST* reviews, done by the ARRL Lab, often include the results of specific phase-noise measurements.

9.2.4 Measuring Receiver Phase Noise

There are several different ways of measuring phase noise, offering different tradeoffs

between convenience, cost and effort. Some methods suit oscillators in isolation, others suit them in-situ (in their radios).

If you’re unfamiliar with noise measurements, the units involved may seem strange. One reason for this is that a noise signal’s power is spread over a frequency range, like an infinite number of infinitesimal sinusoidal components. This can be thought of as similar to painting a house. The area that a gallon of paint can cover depends on how thinly it’s spread. If someone asks how much paint was used on some part of a wall, the answer would have to be in terms of paint volume per square foot. The wall can be considered to be an infinite number of points, each with an infinitesimal amount of paint applied to it. The question of what volume of paint has been applied at some specific point is unanswerable. With noise, we must work in terms of *power density*, of watts per hertz. We therefore express phase-noise level as a ratio of the carrier power to the noise’s power density. Because of the large ratios involved, expression in decibels is convenient. It has been a convention to use *dBc* to mean “decibels with respect to the carrier.”

For phase noise, we need to work in terms of a standard bandwidth, and 1 Hz is the obvious candidate. Even if the noise is measured in a different bandwidth, its equivalent power in 1 Hz can be easily calculated. A phase-noise level of -120 dBc in a 1-Hz bandwidth (often written as “ -120 dBc/Hz”) translates into each hertz of the noise having a power of 10^{-12} of the carrier power. In a bandwidth of 3 kHz, this would be 3000 times larger.

The most convenient way to measure phase noise is to buy and use a commercial phase noise test system. Such a system usually contains a state-of-the-art, low-noise frequency synthesizer and a low-frequency spectrum analyzer, as well as some special hardware. Often, a second, DSP-based spectrum analyzer is included to speed up and extend measurements very close to the carrier by using the Fast Fourier Transform (FFT). The whole system is then controlled by a computer with proprietary software. With a good system like this costing about \$100,000, this is not a practical method for amateurs, although a

few fortunate individuals have access to them at work. These systems are also overkill for our needs, because we are not particularly interested in determining phase-noise levels very close to and very far from the carrier.

It’s possible to make respectable receiver-oscillator phase-noise measurements with less than \$100 of parts and a multimeter. Although it’s time-consuming, the technique is much more in keeping with the amateur spirit than using a \$100k system! An ordinary multimeter will produce acceptable results; a meter capable of indicating “true RMS” ac voltages is preferable because it can give correct readings on sine waves *and* noise. Fig 9.9 shows the setup. Measurements can only be made around the frequency of the crystal oscillator, so if more than one band is to be tested, crystals must be changed, or else a set of appropriate oscillators is needed. The oscillator should produce about $+10$ dBm (10 mW) and be *very* well shielded. (To this end, it’s advisable to build the oscillator into a die-cast box and power it from internal batteries. A noticeable shielding improvement results even from avoiding the use of an external power switch; a reed-relay element inside the box can be positioned to connect the battery when a small permanent magnet is placed against a marked place outside the box.)

Likewise, great care must be taken with attenuator shielding. A total attenuation of around 140 dB is needed, and with so much attenuation in line, signal leakage can easily exceed the test signal that reaches the receiver. It’s not necessary to be able to switch-select all 140 dB of the attenuation, nor is this desirable, as switches can leak. All of the attenuators’ enclosure seams must be soldered. A pair of boxes with 30 dB of fixed attenuation each is needed to complete the set. With 140 dB of attenuation, coax cable leakage is also a problem. The only countermeasure against this is to minimize all cable lengths and to interconnect test-system modules with BNC plug-to-plug adapters (UG-491A) where possible.

Ideally, the receiver could simply be tuned across the signal from the oscillator and the response measured using its signal-strength (S) meter. Unfortunately, receiver S meters are notoriously imprecise, so an equivalent

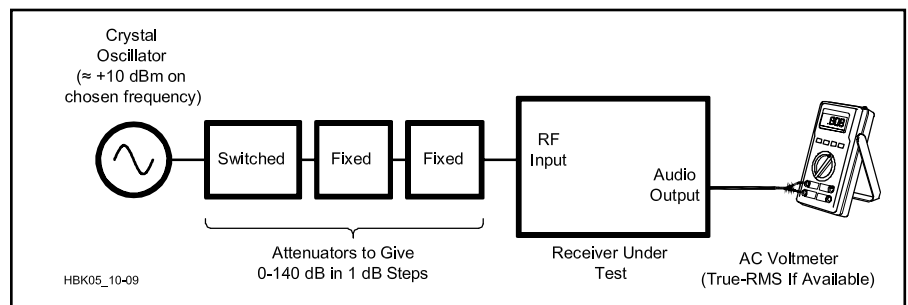


Fig 9.9 — Setup for measuring receiver-oscillator phase noise.

method is needed that does not rely on the receiver's AGC system.

The trick is not to measure the response to a fixed level signal, but to measure the changes in applied signal power needed to give a fixed response. Here is a step-by-step procedure based on that described by John Grebenkemper, KI6WX, in March and April 1988 *QST*:

1. Connect the equipment as shown in Fig 9.9, but with the crystal oscillator off. Set the step attenuator to maximum attenuation. Set the receiver for SSB or CW reception with its narrowest available IF filter selected. Switch out any internal preamplifiers or RF attenuators. Select AGC off, maximum AF and RF gain. It may be necessary to reduce the AF gain to ensure the audio amplifier is at least 10 dB below its clipping point. The ac voltmeter or an oscilloscope on the AF output can be used to monitor this.

2. To measure noise, it is important to know the bandwidth being measured. A true-RMS ac voltmeter measures the power in the noise reaching it. To calculate the noise density, we need to divide by the receiver's *noise bandwidth*. The receiver's -6-dB IF bandwidth can be used as an approximation, but purists will want to plot the top 20 dB of the receiver's bandwidth on linear scales and integrate the area under it to find the width of a rectangle of equal area and equal height. This accounts properly for the noise in the skirt regions of the overall selectivity. (The very rectangular shape of common receiver filters tends to minimize the error of just taking the approximation.)

Switch on the test oscillator and set the attenuators to give an AF output above the noise floor and below the clipping level with the receiver peaked on the signal. Tune the receiver off to each side to find the frequencies at which the AF voltage is half that at the peak. The difference between these is the receiver's -6-dB bandwidth. High accuracy is not needed: 25% error in the receiver bandwidth will only cause a 1-dB error in the final result. The receiver's published selectivity specifications will be close enough. The benefit of integration is greater if the receiver has a very rounded, low-ringing or low-order filter.

3. Retune the receiver to the peak. Switch the oscillator off and note the noise-floor voltage. Turn the oscillator back on and adjust the attenuator to give an AF output voltage 1.41 times (3 dB) larger than the noise floor voltage. This means that the noise power and the test signal power at the AF output are equal — a value that's often called the *MDS* (*minimum discernible signal*) of a receiver. Choosing a test-oscillator level at which to do this test involves compromise. Higher levels give more accurate results where the phase noise is high, but limit the lowest level of

phase noise that can be measured because better receiver oscillators require a greater input signal to produce enough noise to get the chosen AF-output level. At some point, either we've taken all the attenuation out and our measurement range is limited by the test oscillator's available power, or we overload the receiver's front end, spoiling the results.

Record the receiver frequency at the peak, (f_0), the attenuator setting (A_0) and the audio output voltage (V_0). These are the carrier measurements against which all the noise measurements will be compared.

4. Now you must choose the offset frequencies — the separations from the carrier — at which you wish to make measurements. The receiver's skirt selectivity will limit how close to the carrier noise measurements can be made. (Any measurements made too close in are valid measurements of the receiver selectivity, but because the signal measured under these conditions is sinusoidal and not noise like, the corrections for noise density and noise bandwidth are not appropriate.) It is difficult to decide where the filter skirt ends and the noise begins, and what corrections to apply in the region of doubt and uncertainty. A good practical approach is to listen to the audio and tune away from the carrier until you can't distinguish a tone in the noise. The ear is superb at spotting sine tones buried in noise, so this criterion, although subjective,

errs on the conservative side.

Tune the receiver to a frequency offset from f_0 by your first chosen offset and adjust the attenuators to get an audio output voltage as close as possible to V_0 . Record the total attenuation, A_1 and the audio output voltage, V_1 . The SSB phase noise (qualified as SSB because we're measuring the phase noise on only one side of the carrier, whereas some other methods cannot segregate between upper and lower noise sidebands and measure their sum, giving DSB phase noise) is now easy to calculate:

$$L(f) = A_1 - A_0 - 10 \log(BW_{\text{noise}}) \quad (1)$$

where

$L(f)$ = SSB phase noise in dBc/Hz
 BW_{noise} = receiver noise bandwidth, Hz
 A_0 = Attenuator setting in step three
 A_1 = Attenuator setting in step four

This equation begins with the difference between the attenuation necessary to reduce the peak carrier signal to the MDS level (A_0 in step three) and the attenuation necessary to reduce the phase noise to the MDS level (A_1 in step four). Subtracting the bandwidth correction term results in the noise power per Hz of bandwidth with respect to the peak carrier signal. Note that this equation does not depend on the absolute power level of the

Table 9.1
SSB Phase Noise of ICOM IC-745 Receiver Section

Oscillator output power = -3 dBm (0.5 mW)
Receiver bandwidth (Δf) = 1.8 kHz
Audio noise voltage = -0.070 V
Audio reference voltage (V_0) = 0.105 V
Reference attenuation (A_0) = 121 dB

Offset Frequency	Attenuation (A_1) (dB)	Audio V_1 (volts)	Audio V_2 (volts)	Ratio V_2/V_1	SSB Phase Noise (kHz) (dBc/Hz)
4	35	0.102	0.122	1.20	-119
5	32	0.104	0.120	1.15	-122*
6	30	0.104	0.118	1.13	-124*
8	27	0.100	0.116	1.16	-127*
10	25	0.106	0.122	1.15	-129*
15	21	0.100	0.116	1.16	-133*
20	17	0.102	0.120	1.18	-137
25	14	0.102	0.122	1.20	-140
30	13	0.102	0.122	1.20	-141
40	10	0.104	0.124	1.19	-144
50	8	0.102	0.122	1.20	-146
60	6	0.104	0.124	1.19	-148
80	4	0.102	0.126	1.24	-150
100	3	0.102	0.126	1.24	-151
150	3	0.102	0.124	1.22	-151
200	0	0.104			-154
250	0	0.100			-154
300	0	0.98			-154
400	0	0.96			-154
500	0	0.96			-154
600	0	0.97			-154
800	0	0.96			-154
1000	0	0.96			-154

*Asterisks indicate measurements possibly affected by receiver overload (see text).

carrier signal as long as it remains constant during the test.

5. It's important to check for overload. Decrease the attenuation by 3 dB, and record the new audio output voltage, V_2 . If all is well, the output voltage should increase by 22% (1.8 dB); if the receiver is operating non-linearly, the increase will be less. (An 18% increase is still acceptable for the overall accuracy we want.) Record V_2/V_1 as a check: a ratio of 1.22:1 is ideal, and anything less than 1.18:1 indicates a bad measurement.

If too many measurements are bad, you may be overdriving the receiver's AF amplifier, so try reducing the AF gain and starting again back at Step 3. If this doesn't help, reducing the RF gain and starting again at Step 3 should help if the compression is occurring late in the IF stages.

6. Repeat Steps 4 and 5 at all the other offsets you wish to measure. If measurements are made at increments of about half the receiver's bandwidth, any discrete (non-noise) spurs will be found. A noticeable tone in

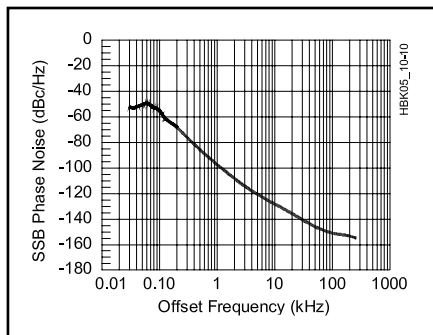


Fig 9.10 — The SSB phase noise of an ICOM IC-745 transceiver (serial number 01528) as measured by KI6WX.

the audio can indicate the presence of one of these. If it is well clear of the noise, the measurement is valid, but the noise bandwidth correction should be ignored, giving a result in dBc.

Table 9.1 shows the results for an ICOM IC-745 as measured by KI6WX, and **Fig 9.10** shows this data in graphic form. His oscilla-

tor power was only -3 dBm, which limited measurements to offsets less than 200 kHz. More power might have allowed noise measurements to lower levels, although receiver overload places a limit on this. This is not important, because the real area of interest has been thoroughly covered. When attempting phase-noise measurements at large offsets, remember that any front-end selectivity, before the first mixer, will limit the maximum offset at which LO phase-noise measurement is possible.

9.2.5 Measuring Oscillator and Transmitter Phase Noise

Measuring the composite phase noise of a receiver's LO requires a clean test oscillator. Measuring the phase noise of an incoming signal, whether from a single oscillator or an entire transmitter, requires the use of a clean receiver, with lower phase noise than the source under test. The sidebar, "Transmitter Phase-Noise Measurement in the ARRL

Transmitter Phase-Noise Measurement in the ARRL Lab

Here is a brief description of the technique used in the ARRL Lab to measure transmitter phase noise. The system consists of a phase noise test set with low-noise variable crystal oscillators for reference signals. The test set zero-beats the oscillator to the transmitter signal using phase detectors on both signals. As shown in **Fig 9.A1**, we use an attenuator after the transmitter to bring the signal down to a suitable level for the phase noise test set. The crystal oscillator output is low level, so it does not require attenuation.

The phase noise test set is an automated system run by a PC that steps through the test, setting parameters in the spectrum analyzers and reading the data back from them,

in addition to performing system calibration measurements at the start of the test. The computer screen displays the transmitted phase-noise spectrum, which can be printed or saved to a file on the hard drive. To test the baseline phase noise of the system, two identical crystal oscillators are tested against each other. It is quite important to be sure that the phase noise of the reference source is lower than that of the signal under test.

A sample phase-noise plot for an amateur transceiver is shown in **Fig 9.A2**. It was produced with the test setup shown in **Fig 9.A1**. These plots do not necessarily reflect the phase-noise characteristics of all units of a particular model.

The reference level (the top horizontal line on the scale in

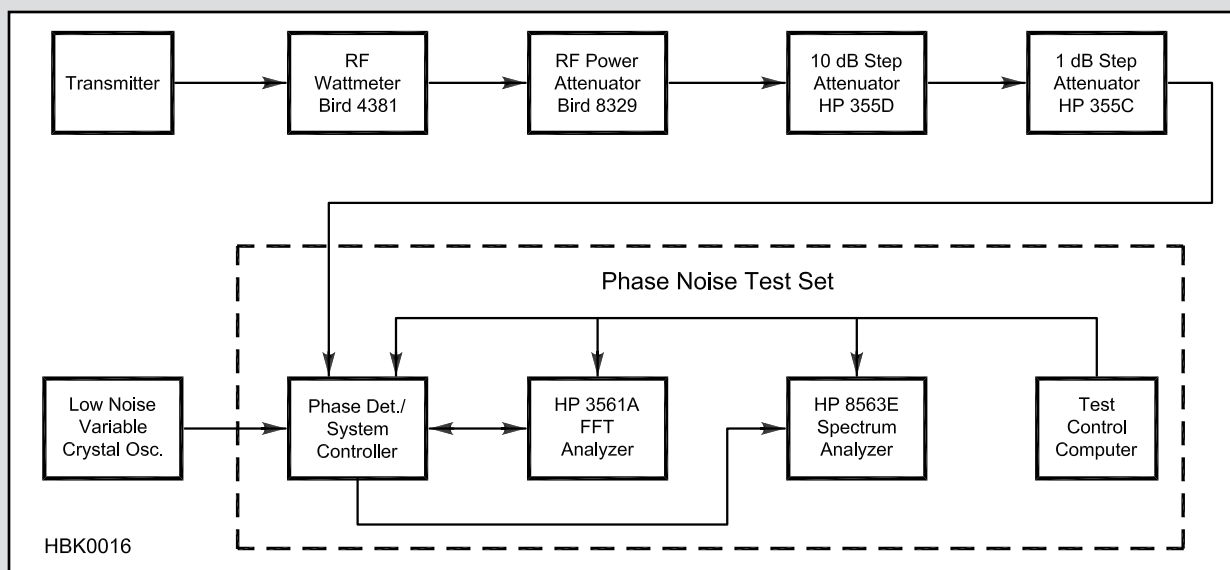


Fig 9.A1 — ARRL Lab phase-noise measurement setup.

Lab,” details the method used to measure composite noise (phase noise and amplitude noise, the practical effects of which are indistinguishable on the air) for *QST* Product Reviews. Although targeted at measuring high power signals from entire transmitters, this approach can be used to measure lower-level signals simply by changing the amount of input attenuation used.

At first, this method — using a low-frequency spectrum analyzer and a low-phase-noise signal source — looks unnecessarily elaborate. A growing number of radio amateurs have acquired good-quality spectrum analyzers for their shacks since older model Tektronix and Hewlett-Packard instruments have started to appear on the surplus market at affordable prices. The obvious question is, “Why not just use one of these to view the signal and read phase-noise levels directly off the screen?” Reciprocal mixing is the problem.

Very few spectrum analyzers have clean enough local oscillators not to completely swamp the noise being measured. Phase-

noise measurements involve the measurement of low-level components very close to a large carrier, and that carrier will mix the noise sidebands of the *analyzer’s* LO into its IF. Some way of notching out the carrier is needed, so that the analyzer need only handle the noise sidebands. A crystal filter could be designed to do the job, but this would be expensive, and one would be needed for every different oscillator frequency to be tested. The alternative is to build a direct-conversion receiver using a clean LO like the Hewlett-Packard HP8640B signal generator and spectrum-analyze its “audio” output with an audio analyzer. This scheme mixes the carrier to dc; the LF analyzer is then ac-coupled, and this removes the carrier. The analyzer can be made very sensitive without overload or reciprocal mixing being a problem.

The remaining problem is then keeping the LO — the HP8640B in this example — at exactly the carrier frequency. 8640s are based on a shortened-UHF-cavity oscillator and can drift a little. The oscillator under

test will also drift. The task is therefore to make the 8640B track the oscillator under test. For once we get something for free: The HP8640B’s FM input is dc coupled, and we can use this as an electronic fine-tuning input. As a further bonus, the 8640B’s FM deviation control acts as a sensitivity control for this input. We also get a phase detector for free, as the mixer output’s dc component depends on the phase relationship between the 8640B and the signal under test (remember to use the dc coupled port of a diode ring mixer as the output). Taken together, the system includes everything needed to create a crude phase-locked loop that will automatically track the input signal over a small frequency range. **Fig 9.11** shows the arrangement.

The oscilloscope is not essential for operation, but it is needed to adjust the system. With the loop unlocked (8640B FM input disconnected), tune the 8640 off the signal frequency to give a beat at the mixer output. Adjust the mixer drive levels to get an undistorted sine wave on the scope. This ensures that the mixer

the plot) represents 0 dBc/Hz. Because each vertical division represents 20 dB, the plot shows the noise level between 0 dBc/Hz (the top horizontal line) and -160 dBc/Hz (the bottom horizontal line). The horizontal scale is logarithmic, with one decade per division (the first division shows noise from 100 Hz to 1000 Hz offset, whereas the last division shows noise from 100 kHz through 1 MHz offset).

What Do the Phase-Noise Plots Mean?

Although they are useful for comparing different radios, plots can also be used to calculate the amount of interference you may receive from a nearby transmitter with known phase-noise characteristics. An approximation is given by

$$A_{\text{QRM}} = \text{NL} + 10 \times \log(\text{BW})$$

where

A_{QRM} = Interfering signal level, dBc

NL = noise level on the receive frequency, dBc

BW = receiver IF bandwidth, in Hz

For instance, if the noise level is -90 dBc/Hz and you are using a 2.5-kHz SSB filter, the approximate interfering signal will be -56 dBc. In other words, if the transmitted signal is 20 dB over S9, and each S unit is 6 dB, the interfering signal will be as strong as an S3 signal.

The measurements made in the ARRL Lab apply only to transmitted signals. It is reasonable to assume that the phase-noise characteristics of most transceivers are similar on transmit and receive because the same oscillators are generally used in local-oscillator (LO) chain.

In some cases, the receiver may have better phase noise characteristics than the transmitter. Why the possible difference? The most obvious reason is that circuits often perform less than optimally in strong RF fields, as anyone who has experienced RFI problems can tell you. A less obvious reason results from the way that many high-dynamic-range receivers work. To get good dynamic range, a sharp crystal filter called a *roofing filter* is often placed immediately after the first mixer in the receive line. This filter removes all but a small slice of spectrum for further signal processing. If the desired filtered signal is a product of mixing an incoming signal with a noisy oscillator, signals far away from the desired one can end up in this slice. Once this slice of spectrum is obtained, however, unwanted signals cannot be reintroduced, no matter how noisy the oscillators used in further signal processing. As a result, some oscillators in receivers don’t affect phase noise.

The difference between this situation and that in transmitters is that crystal filters are seldom used for reduction of phase noise in transmitting because of the high cost involved. Equipment designers have enough trouble getting smooth, click-free break-in operation in transceivers without having to worry about switching crystal filters in and out of circuits at 40-WPM keying speeds! — Zack Lau, W1VT, and Michael Tracy, KC1SX

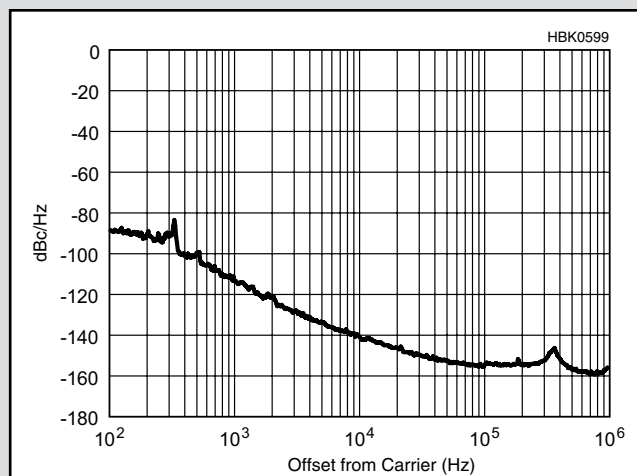


Fig 9.A2 — Sample phase noise plot for an amateur HF transceiver as published in Product Review in *QST*. This is the Elecraft K3.

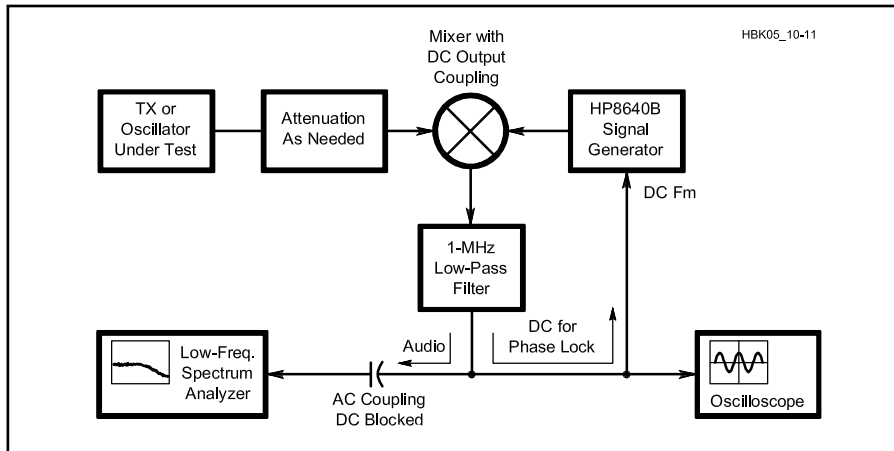


Fig 9.11 — Arrangement for measuring phase noise by directly converting the signal under test to audio. The spectrum analyzer views the signal’s noise sidebands as audio; the signal’s carrier, converted to dc, provides a feedback signal to phase-lock the Hewlett-Packard HP8640B signal generator to the signal under test.

is not being overdriven. While the loop is off-tuned, adjust the beat to a frequency within the range of the LF spectrum analyzer and use it to measure its level, “ A_c ” in dBm. This represents the carrier level and is used as the reference for the noise measurements. Connect the FM input of the signal generator, and switch on the generator’s dc FM facility. Try a deviation range of 10 kHz to start with. When you tune the signal generator toward the input frequency, the scope will show the falling beat frequency until the loop jumps into lock. Then it will display a noisy dc level. Fine tune to get a mean level of 0 V. (This is a very-low-bandwidth, very-low-gain loop. Stability is not a problem; careful loop design is not needed. We actually want as slow a loop as possible; otherwise, the loop would track and cancel the slow components of the incoming signal’s phase noise, preventing their measurement.)

When you first take phase-noise plots, it’s a good idea to duplicate them at the generator’s next lower FM-deviation range and check for any differences in the noise level in the areas of interest. Reduce the FM deviation range

until you find no further improvement. Insufficient FM deviation range makes the loop’s lock range narrow, reducing the amount of drift it can compensate. (It’s sometimes necessary to keep gently trimming the generator’s fine tune control.)

Set up the LF analyzer to show the noise. A sensitive range and 100-Hz resolution bandwidth are appropriate. Measure the noise level, “ A_n ” in dBm. We must now calculate the noise density that this represents. Spectrum-analyzer filters are normally *Gaussian*-shaped and bandwidth-specified at their -3 -dB points. To avoid using integration to find their true-noise power bandwidth, we can reasonably assume a value of $1.2 \times BW$. A spectrum analyzer logarithmically compresses its IF signal ahead of the detectors and averaging filter. This affects the statistical distribution of noise voltage and causes the analyzer to read low by 2.5 dB. To produce the same scale as the ARRL Lab photographs prior to May 2006 *QST*, the analyzer reference level must be set to -60 dBc/Hz, which can be calculated as:

$$A_{\text{ref}} = A_c - 10 \log (1.2 \times BW) + 62.5 \text{ dBm} \quad (2)$$

where

$$A_{\text{ref}} = \text{analyzer reference level, dBm}$$

$$A_c = \text{carrier amplitude, dBm}$$

This produces a scale of -60 dBc/Hz at the top of the screen, falling to -140 dBc/Hz at the bottom. The frequency scale is 0 to 20 kHz with a resolution bandwidth (BW in the above equation) of 100 Hz. This method combines the power of *both* sidebands and so measures DSB phase noise. To calculate the equivalent SSB phase noise, subtract 3 dB for noncoherent noise (the general “hash” of phase noise) and subtract 6 dB for coherent, discrete components (that is, single-frequency spurs). This can be done by setting the reference level 3 to 6 dB higher.

9.2.6 Low-Cost Phase Noise Testing

All that expensive equipment may seem far beyond the means of the average Amateur Radio experimenter. With careful shopping and a little more effort, alternative equipment can be put together for pocket money. (All of the things needed — parts for a VXO, a surplus spectrum analyzer and so on — have been seen on sale cheap enough to total less than \$100.) The HP8640B is good and versatile, but for use at one oscillator frequency, you can build a VXO for a few dollars. It will only cover one oscillator frequency, but a VXO can provide even better phase-noise performance than the 8640B. There is free software available so that you can use your PC soundcard as an LF spectrum analyzer, though you may want to add a simple preamp and some switched attenuators.

In the reference at the end of this chapter, Pontius has also demonstrated that signal-source phase-noise measurements can be accurately obtained without the aid of expensive equipment.

9.3 Oscillator Circuits and Construction

9.3.1 LC Oscillator Circuits

The LC oscillators used in radio equipment are usually designed to be *variable frequency oscillators* (VFOs). Tuning is achieved by either varying part of the capacitance of the resonator or, less commonly, by using a movable magnetic core to vary the inductance. Since the early days of radio, there has been a huge quest for the ideal, low-drift VFO. Amateurs and professionals have spent immense effort on this pursuit. A brief search of the literature reveals a large number of designs, many accompanied by claims of high stability. The quest for stability has been solved by

the development of low-cost frequency synthesizers, which can give crystal-controlled stability. Synthesizers have other problems though, and the VFO still has much to offer in terms of signal cleanliness, cost and power consumption, making it attractive for home construction. No one VFO circuit has any overwhelming advantage over any other — component quality, mechanical design and the care taken in assembly are much more important.

Fig 9.12 shows three popular oscillator circuits stripped of any unessential frills so they can be more easily compared. The

original Colpitts circuit (Fig 9.12A) is now often referred to as the *parallel-tuned Colpitts* because its series-tuned derivative (Fig 9.12B) has become common. All three of these circuits use an amplifier with a voltage gain less than unity, but large current gain. The N-channel JFET source follower shown appears to be the most popular choice nowadays. In the parallel-tuned Colpitts, C3 and C4 are large values, perhaps 10 times larger than typical values for C1 and C2. This means that only a small fraction of the total tank voltage is applied to the FET, and the FET can be considered to be only lightly coupled into the

tank. The FET is driven by the sum of the voltages across C3 and C4, while it drives the voltage across C4 alone. This means that the tank operates as a resonant, voltage-step-up transformer compensating for the less-than-

unity-voltage-gain amplifier. The resonant circuit consists of L, C1, C2, C3 and C4. The resonant frequency can be calculated by using the standard formulas for capacitors in series and parallel to find the resultant capacitance

effectively connected across the inductor, L, and then use the standard formula for LC resonance:

$$f = \frac{1}{2\pi\sqrt{LC}} \quad (3)$$

where

- f = frequency in hertz
- L = inductance in henries
- C = capacitance in farads.

For a wide tuning range, C2 must be kept small to reduce the effect of C3 and C4 swamping the variable capacitor C1. (For more information on component selection, the chapters on oscillators in *Experimental Methods for RF Design* and *Introduction to Radio Frequency Design* listed in the References provide excellent material.)

The series-tuned Colpitts circuit works in much the same way. The difference is that the variable capacitor, C1, is positioned so that it is well-protected from being swamped by the large values of C3 and C4. In fact, *small* values of C3, C4 would act to limit the tuning range. Fixed capacitance, C2, is often added across C1 to allow the tuning range to be reduced to that required, without interfering with C3 and C4, which set the amplifier coupling. The series-tuned Colpitts has a reputation for better stability than the parallel-tuned original. Note how C3 and C4 swamp the capacitances of the amplifier in both versions.

A parallel-tuned Colpitts oscillator is the subject of the detailed paper "A Design Example for an Oscillator for Best Phase Noise and Good Output Power" by Dr Ulrich Rohde, NIUL, available on the CD-ROM accompanying this book. The paper shows the design process by which both noise and power can be optimized in a simple oscillator.

The Hartley of Fig 9.12C is similar to the parallel-tuned Colpitts, but the amplifier source is connected to a tap on the tank inductance instead of the tank capacitance. A typical tap placement is 10 to 20% of the total turns up from the "cold" end of the inductor. (It's usual to refer to the lowest-signal-voltage end of an inductor as "cold" and the other, with the highest signal voltage as "hot".) C2 limits the tuning range as required; C3 is reduced to the minimum value that allows reliable starting. This is necessary because the Hartley's lack of the Colpitts' capacitive divider would otherwise couple the FET's capacitances to the tank more strongly than in the Colpitts, potentially affecting the circuit's frequency stability.

In all three circuits, there is a 1 kΩ resistor in series with the source bias choke. This resistor does a number of desirable things. It spoils the Q of the inevitable low-frequency resonance of the choke with the tank tap circuit. It reduces tuning drift due to choke impedance

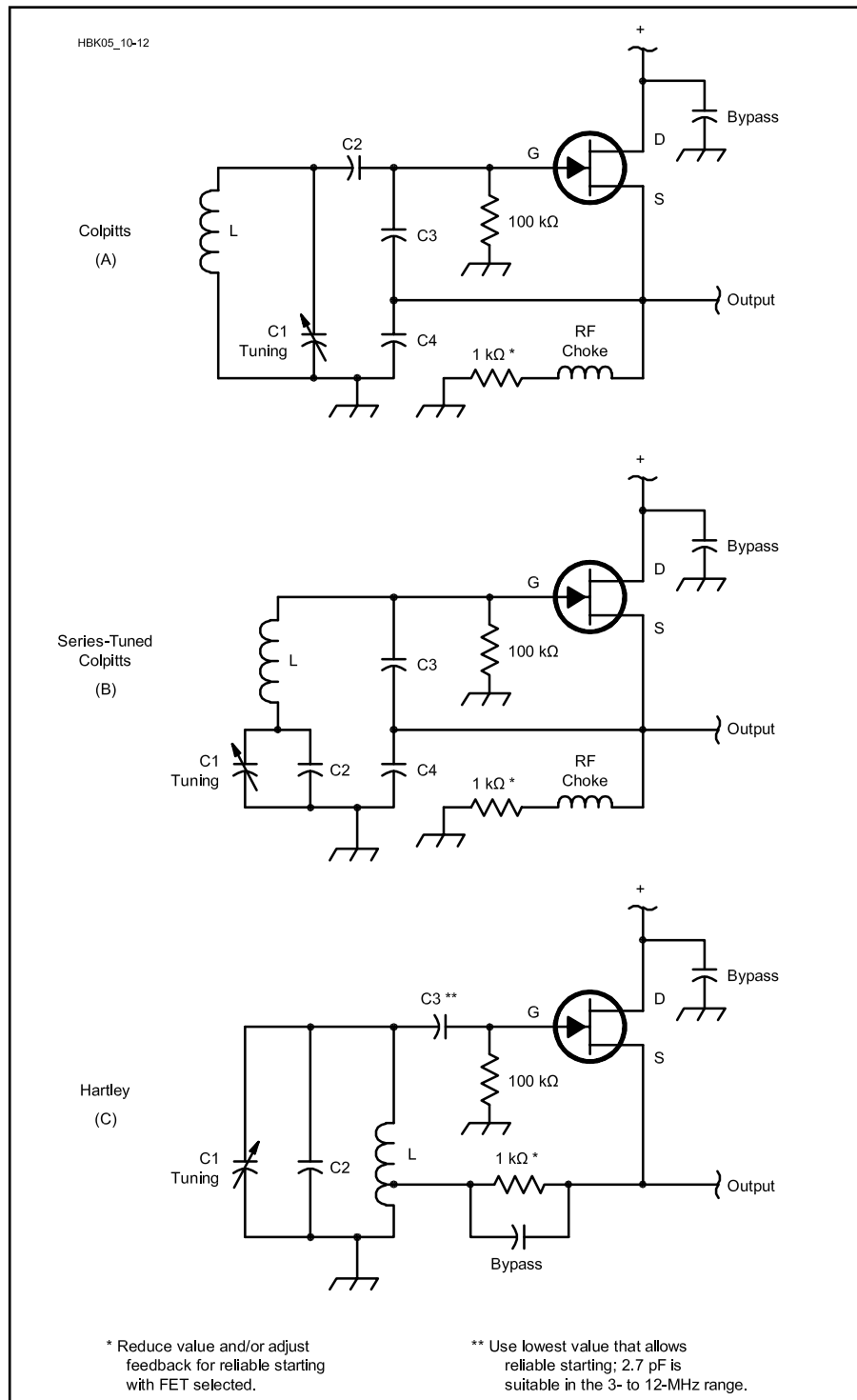


Fig 9.12 — The Colpitts (A), series-tuned Colpitts (B) and Hartley (C) oscillator circuits. Rules of thumb: C3 and C4 at A and B should be equal and valued such that their $X_c = 45 \Omega$ at the operating frequency; for C2 at A, $X_c = 100 \Omega$. For best stability, use C0G or NP0 units for all capacitors associated with the FETs' gates and sources. Depending on the FET chosen, the 1-kΩ source-bias-resistor value shown may require adjustment for reliable starting.

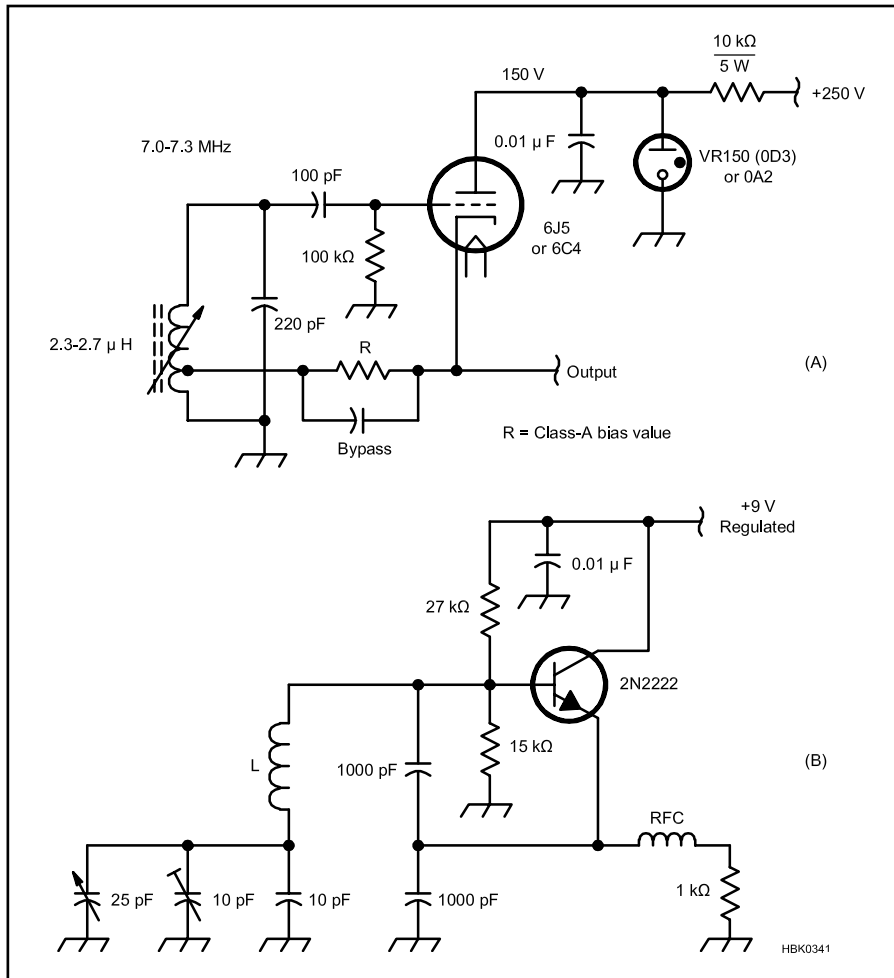


Fig 9.13 — Two more oscillator examples: at A, a triode-tube Hartley; at B, a bipolar junction transistor in a series-tuned Colpitts.

and winding capacitance variations. It also protects against spurious oscillation due to internal choke resonances. Less obviously, it acts to stabilize the loop gain of the built-in AGC action of this oscillator. Stable operating conditions act to reduce frequency drift.

Some variations of these circuits may be found with added resistors providing a dc bias to stabilize the system quiescent current. More elaborate still are variations characterized by a constant-current source providing bias. This can be driven from a separate AGC detector system to give very tight level control. The gate-to-ground clamping diode (1N914 or similar) long used by radio amateurs as a means of avoiding gate-source conduction has been shown by Ulrich Rohde, N1UL, to degrade oscillator phase-noise performance, and its use is virtually unknown in professional circles.

Fig 9.13 shows some more VFOs to illustrate the use of different devices. The triode Hartley shown includes *permeability tuning*, which has no sliding contact like that to a capacitor's rotor and can be made reasonably linear by artfully spacing the coil turns. The

slow-motion drive can be done with a screw thread. The disadvantage is that special care is needed to avoid backlash and eccentric rotation of the core. If a non-rotating core is used, the slides have to be carefully designed to prevent motion in unwanted directions. The Collins Radio Company made extensive use of tube-based permeability tuners, and a semiconductor version can still be found in a number of Ten-Tec radios.

Vacuum tubes cannot run as cool as competitive semiconductor circuits, so care is needed to keep the tank circuit away from the tube heat. In many amateur and commercial vacuum-tube oscillators, oscillation drives the tube into grid current at the positive peaks, causing rectification and producing a negative grid bias. The oscillator thus runs in Class C, in which the conduction angle reduces as the signal amplitude increases until the amplitude stabilizes. As in the FET circuits of Fig 9.12, better stability and phase-noise performance can be achieved in a vacuum-tube oscillator by moving it out of true Class C — that is, by including a bypassed cathode-bias resistor (the resistance appropriate for Class A operation

is a good starting value). A small number of people still build vacuum-tube radios partly to be different, partly for fun, but the semiconductor long ago achieved dominance in VFOs.

The voltage regulator (VR) tube shown in Fig 9.13A has a potential drawback: It is a gas-discharge device with a high striking voltage at which it starts to conduct and a lower extinguishing voltage, at which it stops conducting. Between these extremes lies a region in which decreasing voltage translates to increasing current, which implies negative resistance. When the regulator strikes, it discharges any capacitance connected across it to the extinguishing voltage. The capacitance then charges through the source resistor until the tube strikes again, and the process repeats. This *relaxation oscillation* demonstrates how negative resistance can cause oscillation. The oscillator translates the resultant sawtooth modulation of its power supply into frequency and amplitude variation. Because of VR tubes' ability to support relaxation oscillation, a traditional rule of thumb is to keep the capacitance directly connected across a VR tube to 0.1 μF or less. A value much lower than this can provide sufficient bypassing, as shown in Fig 9.13A because the dropping resistor acts as a decoupler, increasing the bypass's effectiveness.

There is a related effect called *squegging*, which can be loosely defined as oscillation on more than one frequency at a time, but which may also manifest itself as RF oscillation interrupted at an AF rate, as in a super-regenerative detector. One form of squegging occurs when an oscillator is fed from a power supply with a high source impedance. The power supply charges up the decoupling capacitor until oscillation starts. The oscillator draws current and pulls down the capacitor voltage, starving itself of power until oscillation stops. The oscillator stops drawing current, and the decoupling capacitor then recharges until oscillation restarts. The process, the low-frequency cycling of which is a form of relaxation oscillation, repeats indefinitely. The oscillator output can clearly be seen to be pulse modulated if an oscilloscope is used to view it at a suitable time-base setting. This fault is a well-known consequence of poor design in battery-powered radios. As dry cells become exhausted, their internal resistance rises quickly and circuits they power can begin to misbehave. In audio stages, such misbehavior may manifest itself in the "putt-putt" sound of the slow relaxation oscillation called *motorboating*.

Compared to the frequently used JFET, bipolar transistors, Fig 9.13B, are relatively uncommon in oscillators because their low input and output impedances are more difficult to couple into a high-Q tank without excessively loading it. Bipolar devices do tend to give better sample-to-sample ampli-

tude uniformity for a given oscillator circuit, however, as JFETs of a given type tend to vary more in their characteristics.

9.3.2 RC Oscillators

Plenty of RC oscillators are capable of operating to several megahertz. Some of these are really constant-current-into-capacitor circuits, which are easier to make in silicon. Like the phase-shift oscillator above, the timing circuit Q is less than one, giving very poor noise performance that's unsuitable even to the least demanding radio application. One example is the oscillator section of the CD4046 phase-locked-loop IC. This oscillator has poor stability over temperature, large batch-to-batch variation and a wide variation in its voltage-to-frequency relationship. It is not recommended that this sort of oscillator be used at RF in radio systems. (The '4046 phase detector section is very useful, however, as we'll see later.) These oscillators are best suited to audio applications.

9.3.3 Three High-Performance HF VFOs

THE N1UL MODIFIED VACKAR VFO

The oscillator circuit of **Fig 9.14A** was contributed by Dr Ulrich Rohde, N1UL. It is a modified Vackar design (see the sidebar) in which a small coupling capacitor (8 pF) and voltage divider capacitor (18 pF) isolate the resonator circuit (10 μ H and 50 pF tuning capacitor) from the oscillator transistor.

The oscillator transistor is followed by a buffer stage to isolate the oscillator from the load. Because the coupling between the transistor base and the resonator is fixed and light, stability of the oscillator is high across a wide tuning range from 5.5 to 6.6 MHz. Either the inductor or capacitor may be varied to tune the oscillator, but a variable capacitor is recommended as more practical and gives better performance.

Because of the oscillator transistor's large capacitors from base to ground (220 pF) and collector to ground (680 pF), the various parameters of the oscillator transistor have little practical influence on circuit performance. The widely available 2N3904 will perform well for both the oscillator and buffer transistors.

Practical resonator coil and the tuning capacitors will have a positive temperature coefficient. The 8 pF and the 18 pF capacitors should have an N150 temperature coefficient. After 1 hour, the observed drift for this circuit was less than 10 Hz / hour.

THE K7HFD LOW-NOISE DIFFERENTIAL OSCILLATOR

The other high performance oscillator example, shown in **Fig 9.15**, was designed for

The Vackar Oscillator

The original Vackar oscillator is named for Jirí Vackár, who invented the circuit in the late 1940s. The circuit's description — a refinement of the Clapp oscillator — can be found in older editions of the Radio Society of Great Britain's *Radio Communication Handbook*, with some further comments on the oscillator in RSGB's *Amateur Radio Techniques*. The circuit is also described in the Nov 1955 *QST* "Technical Correspondence" column by W9IK. The Vackar circuit optimized the Clapp oscillator for frequency stability: the oscillator transistor is isolated from the resonator, tuning does not affect the feedback coupling, and the transistor's collector output impedance is kept low so that gain is the minimum necessary to sustain oscillation.

low-noise performance by Linley Gumm, K7HFD, and appears on page 126 of ARRL's *Solid State Design for the Radio Amateur*. Despite its publication in that homebrewer's bible (out of print, but available through libraries and loans), this circuit seems to have been overlooked by many builders. It uses no unusual components and looks

simple, yet it is a subtle and sophisticated circuit. It represents the antithesis of G3PDM's VFO: In the pursuit of low noise sidebands, a number of design choices have been made that will degrade the stability of frequency over temperature.

The effects of oscillator noise have already been covered, and Fig 9.7 shows the effect of

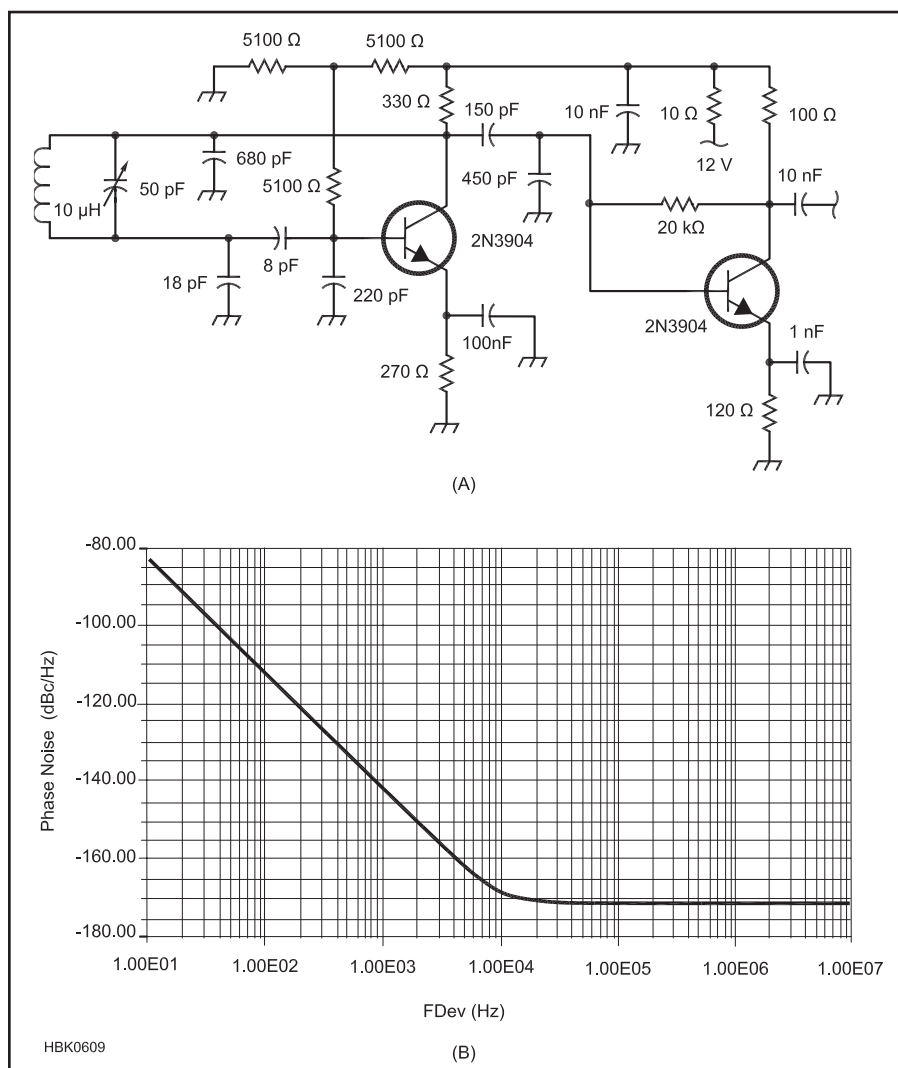


Fig 9.14A — At A, N1UL's Modified Vackar VFO is tuned from 5.5 to 6.6 MHz using the 50 pF capacitor. Tuning may be restricted to narrower ranges by placing a fixed capacitor in parallel with a smaller variable capacitor. The resonant frequency of the oscillator is determined by the 10 μ H inductor and 50 pF tuning capacitor. B shows the excellent phase noise performance of the modified Vackar VFO in this *Harmonica* simulation. At 1 kHz from the carrier, noise is -144 dBc.

VFO Construction

These suggestions by G3PDM can be applied to any analog VFO circuit. Following these guidelines minimizes the effects of temperature change and mechanical vibration (microphonics) on the VFO.

- Use silvered-mica or other highly-stable capacitors for all fixed-value capacitors in the oscillator circuit. Power-supply decoupling capacitors may be any convenient type, such as ceramic or film.
- Tuning capacitors should be a high-quality component with double ball-bearings and silver-plated surfaces and contacts.
- The resonant circuit inductor should be wound on a ceramic form and solidly mounted.
- All oscillator components should be clean and attached to a solid support to minimize thermal changes and mechanical vibration.
- The enclosure should be solid and isolated from mechanical vibration.
- The power supply should be well-regulated, liberally decoupled and free of noise.
- Keep component leads short and if point-to-point wiring is employed, use heavy wire (#16 to #18 AWG).
- Single-point grounding of the oscillator components is recommended to avoid stray inductance and to minimize noise introduced from other sources. If a PCB is used, include a ground-plane.

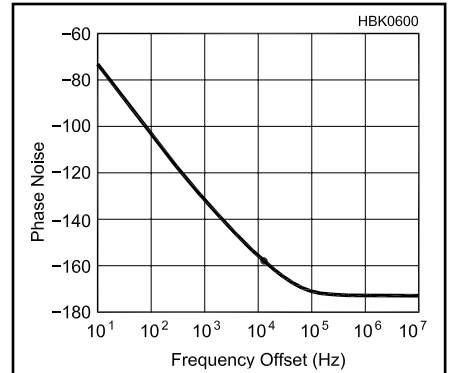


Fig 9.15 B — Modeling of the differential oscillator by Dr Ulrich Rohde, N1UL, shows its excellent phase-noise performance.

the effect on the tank Q. The input transistor base is driven into conduction only on one peak of the tank waveform. The output transformer has the inverse of the current pulse applied to it, so the output is not a low distortion sine wave, although the output harmonics will not be as extensive as simple theory would suggest because the circuit's high output impedance allows stray capacitances to attenuate high-frequency components. The low-frequency transformers used also act to reduce the harmonic power.

With an output of +17 dBm, this is a power oscillator, running with a large dc input power, so appreciable heating results that can cause temperature-induced drift. The circuit's high-power operation is a deliberate ploy to create a high signal-to-noise ratio by having as high a signal power as possible. This also reduces the problem of the oscillator's broadband noise output. The limitation on the signal level in the tank is the transistors' base-emitter-junction breakdown voltage. The circuit runs with a few volts peak-to-peak across the one-turn tap, so the full tank is running at over 50 V_{p-p}.

The single easiest way to damage a bipolar transistor is to reverse bias the base-emitter junction until it avalanches. Most devices are only rated to withstand 5 V applied this way, the current needed to do damage is small, and very little power is needed. If the avalanche current is limited to less than that needed to perform immediate destruction of the transistor, it is likely that there will be some degradation of the device, a reduction in its bandwidth and gain along with an increase in its noise. These changes are irreversible and cumulative. Small, fast signal diodes have breakdown voltages of over 30 V and less capacitance than the transistor bases, so one possible experiment would be to try the effect of adding a diode in series with the base of each transistor and running the circuit at even higher levels.

The amplitude must be controlled by the

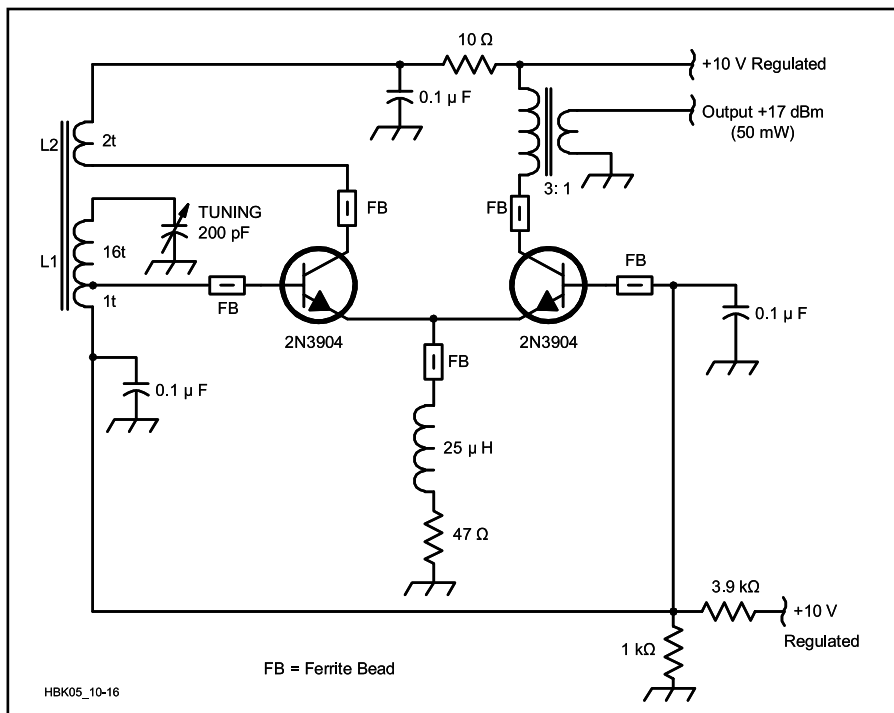


Fig 9.15 A — This low-noise oscillator design by K7HFD operates at an unusually high power level to achieve a high C/N (carrier-to-noise) ratio. Need other frequencies? See the caption of Fig 9.14 for a frequency-scaling technique.

limiting on the signal from a noisy oscillator. Because AM noise sidebands can get translated into PM noise sidebands by imperfect limiting, there is an advantage to stripping off the AM as early as possible, in the oscillator itself. An ALC system in the oscillator will counteract and cancel only the AM components within its bandwidth, but an oscillator based on a limiter will do this over a broad bandwidth. K7HFD's oscillator uses a differential pair of bipolar transistors as a limiting amplifier. The dc bias voltage at the bases and the resistor in the common emitter path to

ground establishes a controlled dc bias current. The ac voltage between the bases switches this current between the two collectors. This applies a rectangular pulse of current into link winding L2, which drives the tank. The output impedance of the collector is high in both the current on and current off states. Allied with the small number of turns of the link winding, this presents a very high impedance to the tank circuit, which minimizes the damping of the tank Q. The input impedance of the limiter is also quite high and is applied across only a one-turn tap of L1, which similarly minimizes

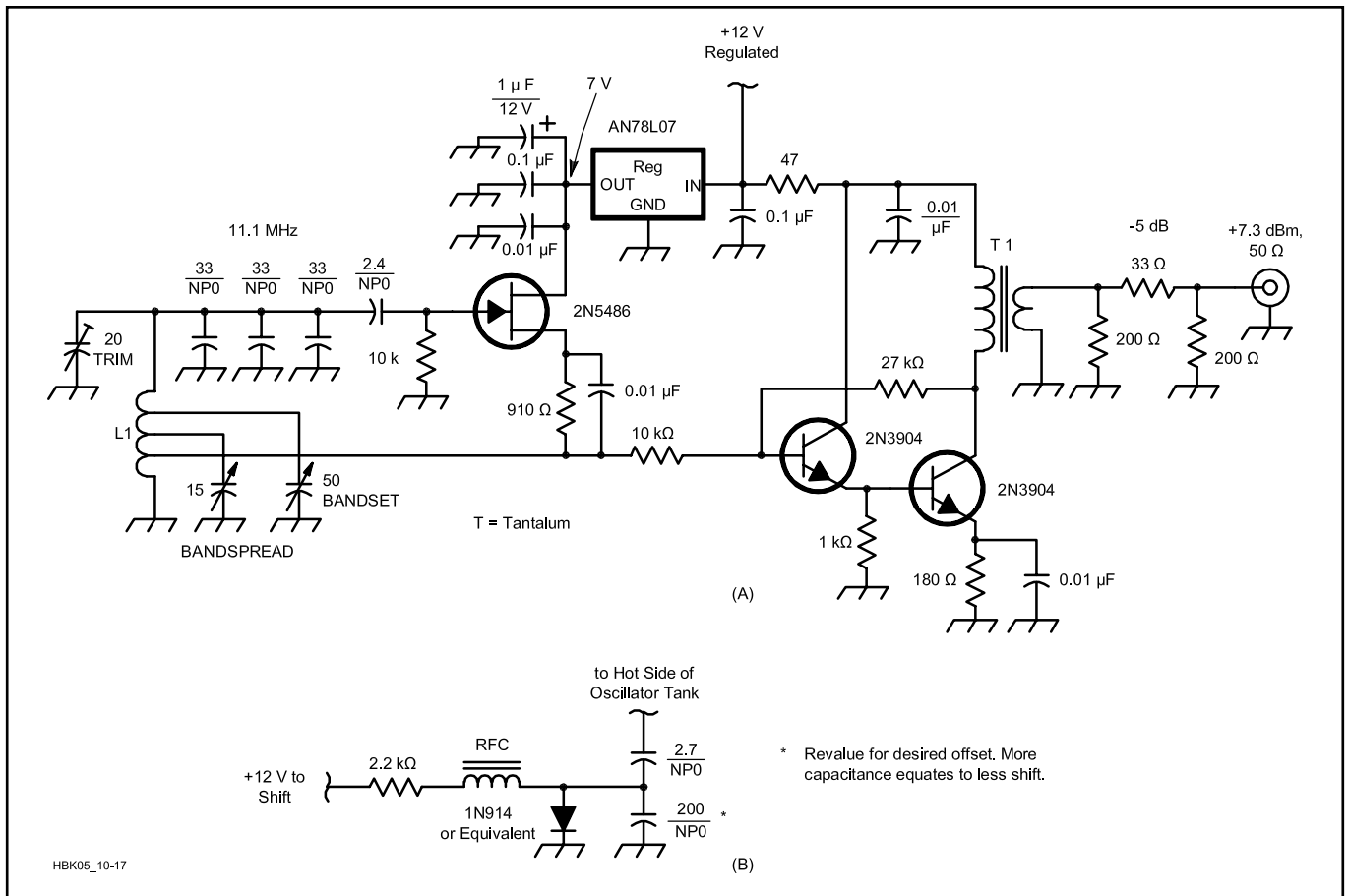


Fig 9.16 — Incorporating ideas from N1UL, KA7EXM, W7ZOI and W7EL, the oscillator at **A** achieves excellent stability and output at 11.1 MHz without the use of a gate-clamping diode, as well as end-running the shrinking availability of reduction drives through the use of bandset and bandspread capacitors. L1 consists of 10 turns of B & W #3041 Miniductor (#22 tinned wire, 1/8 inch in diameter, 24 turns per inch). The source tap is 2½ turns above ground; the tuning-capacitor taps are positioned as necessary for bandset and bandspread ranges required. T1's primary consists of 15 turns of #28 enameled wire on an FT-37-72 ferrite core; its secondary, 3 turns over the primary. **B** shows a system for adding fixed TR offset that can be applied to any LC oscillator. The RF choke consists of 20 turns of #26 enameled wire on an FT-37-43 core. Need other frequencies? See the caption of Fig 9.14 for a frequency-scaling technique.

drive current limit. The voltage on L2 must never allow the collector of the transistor driving it to go into saturation, if this happens, the transistor presents a very low impedance to L2 and badly loads the tank, wrecking the Q and the noise performance. The circuit can be checked to verify the margin from saturation by probing the hot end of L2 and the emitter with an oscilloscope. Another, less obvious, test is to vary the power-supply voltage and monitor the output power. While the circuit is under current control, there is very little change in output power, but if the supply is low enough to allow saturation, the output power will change significantly.

The use of the 2N3904 is interesting, as it is not normally associated with RF oscillators. It is a cheap, plain, general-purpose type more often used at dc or audio frequencies. There is evidence that suggests some transistors that have good noise performance *at RF* have worse noise performance at low frequencies, and that the low-frequency noise they create can modulate an oscillator, creating noise sidebands.

Experiments with low-noise audio transistors may be worthwhile, but many such devices have high junction capacitances. In the description of this circuit in *Solid State Design for the Radio Amateur*, the results of a phase-noise test made using a spectrum analyzer with a crystal filter as a preselector are given. Ten kilohertz out from the carrier, in a 3-kHz measurement bandwidth, the noise was more than 120 dB below the carrier level. This translates into better than $-120 - 10 \log(3000)$, which equals -154.8 dBc/Hz, SSB. At this offset, -140 dBc is usually considered to be excellent. This is state-of-the-art performance by today's standards — in a 1977 publication.

A JFET HARTLEY VFO

Fig 9.16 shows an 11.1-MHz version of a VFO and buffer closely patterned after that used in 7-MHz transceiver designs published by Roger Hayward, KA7EXM, and Wes Hayward, W7ZOI ("The Ugly Weekender") and Roy Lewallen, W7EL ("The Optimized QRP Transceiver"). In it, a 2N5486 JFET

Hartley oscillator drives the two-2N3904 buffer attributed to Lewallen. This version diverges from the originals in that its JFET uses source bias (the bypassed 910-Ω resistor) instead of a gate-clamping diode and is powered from a low-current 7-V regulator IC instead of a Zener diode and dropping resistor. The 5-dB pad sets the buffer's output to a level appropriate for "Level 7" (+7-dBm-LO) diode ring mixers.

The circuit shown was originally built with a gate-clamping diode, no source bias and a 3-dB output pad. Adjusting the oscillator bias as shown increased its output by 2 dB without degrading its frequency stability (200 to 300-Hz drift at power up, stability within ± 20 Hz thereafter at a constant room temperature).

In recognition that precision mechanical tuning components are hard to obtain, the resonator uses "Bandset" and "Bandspread" variable capacitors. Terms from the early days of radio, *bandset* is for coarse-tuning and *bandspread* is for fine-tuning.

9.3.4 VFO Components and Construction

TUNING CAPACITORS AND REDUCTION DRIVES

As most commercially made radios now use frequency synthesizers, it has become increasingly difficult to find certain key components needed to construct a good VFO. Slow-motion drives and variable capacitors are available from *QST* advertiser National RF (www.nationalrf.com), Dan's Small Parts and Kits (www.danssmallpartsandkits.net), and Antique Electronic Supply (www.tubesandmore.com). An alternate approach is also available: Scavenge suitable parts from old equipment; use tuning diodes instead of variable capacitors — an approach that, if uncorrected through phase locking, generally degrades stability and phase-noise performance; or use two tuning capacitors, one with a capacitance range $\frac{1}{2}$ to $\frac{1}{10}$ that of the other, in a bandset/bandspread approach.

Assembling a variable capacitor to a chassis and its reduction drive to a front panel can result in *backlash* — an annoying tuning effect in which rotating the capacitor shaft deforms the chassis and/or panel rather than tuning the capacitor. One way of minimizing this is to use the reduction drive to support the capacitor, and use the capacitor to support the oscillator circuit board.

FIXED CAPACITORS

Traditionally, silver-mica fixed capacitors have been used extensively in oscillators, but their temperature coefficient is not as low as can be achieved by other types, and some silver micas have been known to behave erratically. Polystyrene film has become a proven alternative. One warning is worth noting: Polystyrene capacitors exhibit a permanent change in value should they ever be exposed to temperatures much over 70 °C; they do not return to their old value on cooling. Particularly suitable for oscillator construction are the low-temperature-coefficient ceramic capacitors, often described as *NPO* or *COG* types. These names are actually temperature-coefficient codes. Some ceramic capacitors are available with deliberate, controlled temperature coefficients so that they can be used to compensate for other causes of frequency drift with temperature. For example, the code N750 denotes a part with a temperature coefficient of -750 parts per million per degree Celsius. These parts are now somewhat difficult to obtain, so other methods are needed. (Values for temperature coefficients and other attributes of capacitors are presented in the **Component Data and References** chapter.)

In a Colpitts circuit, the two large-value capacitors that form the voltage divider for the active device still need careful selection.

It would be tempting to use any available capacitor of the right value, because the effect of these components on the tank frequency is reduced by the proportions of the capacitance values in the circuit. This reduction is not as great as the difference between the temperature stability of an NPO ceramic part and some of the low-cost, decoupling-quality X7R-dielectric ceramic capacitors. It's worth using low-temperature coefficient parts even in the seemingly less-critical parts of a VFO circuit — even as decouplers. Chasing the cause of temperature drift is more challenging than fun. Buy critical components like high-stability capacitors from trustworthy sources.

INDUCTORS

Ceramic coil forms can give excellent results, as can self-supporting air-wound coils (Miniductor). If you use a magnetic core, make it powdered iron, never ferrite, and support it stably. Stable VFOs have been made using toroidal cores, but again, ferrite must be avoided. Micrometals mix #6 has a low temperature coefficient and works well in conjunction with NPO ceramic capacitors. Coil forms in other materials have to be assessed on an individual basis.

A material's temperature stability will not be apparent until you try it in an oscillator, but you can apply a quick test to identify those nonmetallic materials that are lossy enough to spoil a coil's *Q*. Put a sample of the coil-form material into a microwave oven along with a glass of water and cook it about 10 seconds on low power. *Do not include any metal fittings or ferromagnetic cores.* Good materials will be completely unaffected; poor ones will heat and may even melt, smoke, or burst into flame. (This operation is a fire hazard if you try more than a tiny sample of an unknown material. Observe your experiment continuously and do not leave it unattended.)

W7ZOI suggests annealing toroidal VFO coils after winding. W7EL reports achieving success with this method by boiling his coils in water and letting them cool in air.

VOLTAGE REGULATORS

VFO circuits are often run from locally regulated power supplies, usually from resistor/Zener diode combinations. Zener diodes have some idiosyncrasies that could spoil the oscillator. They are noisy, so decoupling is needed down to audio frequencies to filter this out. Zener diodes are often run at much less than their specified optimum bias current. Although this saves power, it results in a lower output voltage than intended, and the diode's impedance is much greater, increasing its sensitivity to variations in input voltage, output current and temperature. Some common Zener types may be designed to run at as much as 20 mA; check the data sheet for

your diode family to find the optimum current.

True Zener diodes are low-voltage devices; above a couple of volts, so-called Zener diodes are actually avalanche types. The temperature coefficient of these diodes depends on their breakdown voltage and crosses through zero for diodes rated at about 5 V. If you intend to use nothing fancier than a common-variety Zener, designing the oscillator to run from 5 V and using a 5.1-V Zener, will give you a free advantage in voltage-versus-temperature stability. There are some diodes available with especially low temperature coefficients, usually referred to as *reference* or *temperature-compensated diodes*. These usually consist of a series pair of diodes designed to cancel each other's temperature drift. Running at 7.5 mA, the 1N829A provides 6.2 V $\pm 5\%$ and a temperature coefficient of just ± 5 parts per million (ppm) maximum per degree Celsius. A change in bias current of 10% will shift the voltage less than 7.5 mV, but this increases rapidly for greater current variation. The 1N821A is a lower-grade version, at ± 100 ppm/°C. The LM399 is a complex IC that behaves like a superb Zener at 6.95 V, ± 0.3 ppm/°C. There are also precision, low-power, three-terminal regulators designed to be used as voltage references, some of which can provide enough current to run a VFO. There are comprehensive tables of all these devices between pages 334 and 337 of Horowitz and Hill, *The Art of Electronics*, 2nd ed.

OSCILLATOR DEVICES

The 2N3819 FET, a classic from the 1960s, has proven to work well in VFOs, but, like the MPF102 also long-popular with ham builders, it's manufactured to wide tolerances. Considering an oscillator's importance in receiver stability, you should not hesitate to spend a bit more on a better device. The 2N5484, 2N5485 and 2N5486 are worth considering; together, their transconductance ranges span that of the MPF102, but each is a better-controlled subset of that range. The 2N5245 is a more recent device with better-than-average noise performance that runs at low currents like the 2N3819. The 2N4416/A, also available as the plastic-cased PN4416, is a low-noise device, designed for VHF/UHF amplifier use, which has been featured in a number of good oscillators up to the VHF region. Its low internal capacitance contributes to low frequency drift. The J310 (plastic; the metal-cased U310 is similar) is another popular JFET in oscillators.

The 2N5179 (plastic, PN5179 or MPS5179) is a bipolar transistor capable of good performance in oscillators up to the top of the VHF region. Care is needed because its absolute-maximum collector-emitter voltage is only 12 V, and its collector current must not exceed 50 mA. Although these characteristics may seem to convey fragility, the 2N5179 is suf-

efficient for circuits powered by stabilized 6-V power supplies.

VHF-UHF devices are not really necessary in LC VFOs because such circuits are rarely used above 10 MHz. Absolute frequency stability is progressively harder to achieve with increasing frequency, so free-running oscillators are rarely used to generate VHF-UHF signals for radio communication. Instead, VHF-UHF radios usually use voltage-tuned, phase-locked oscillators in some form of synthesizer. Bipolar devices like the BFR90 and MRF901, with f_T s in the 5-GHz region and mounted in stripline packages, are needed at UHF.

Integrated circuits have not been mentioned until now because few specific RF-oscillator ICs exist. Some consumer ICs — the NE602, for example — include the active device(s) necessary for RF oscillators, but often this is no more than a single transistor fabricated on the chip. This works just as a single discrete device would, although using such on-chip devices may result in poor isolation from the rest of the circuits on the chip. There is one specialized LC-oscillator IC: the Motorola MC1648. This device has been made since the early 1970s and is a surviving member of MECL III, a long-obsolete family of emitter-coupled-logic devices. It is still used in military and commercial equipment. It is difficult to obtain, expensive, power hungry, and offers relatively low performance. Its circuitry is complex for an oscillator, with a multi-transistor limiting-amplifier cell controlled

by an on-chip ALC system. The MC1648's first problem is that the ECL families use only about a 0.8 V swing between logic levels, and this same limitation applies to the signal in the oscillator tuned circuit. It is possible to improve this situation by using a tapped or transformer-coupled tank circuit to give improved Q, but risks the occurrence of the device's second problem.

Periodically, semiconductor manufacturers modernize their plants and scrap old assembly lines used to make old products. Any surviving devices then must undergo some redesign to allow their production by the new processes. One common result of this is that devices are shrunk, when possible, to fit more onto a wafer. All this increases the f_T of the transistors in the device, and such evolution has rendered today's MC1648s capable of operation at much higher frequencies than the specified 200-MHz limit. This allows higher-frequency use, but great care is needed in the layout of circuits using it to prevent spurious oscillation. A number of old designs using this part have needed reengineering because the newer parts generate spurious oscillations that the old ones didn't, using PC-board traces as parasitic tuned circuits.

The moral is that a UHF-capable device requires UHF-cognizant design and layout even if the device will be used at far lower frequencies. Fig 9.17 shows the MC1648 in a simple circuit and with a tapped resonator. These more complex circuits have a greater

risk of presenting a stray resonance within the device's operating range, risking oscillation at an unwanted frequency. This device is *not* a prime choice for an HF VFO because the physical size of the variable capacitor and the inevitable lead lengths, combined with the need to tap-couple to get sufficient Q for good noise performance, makes spurious oscillation difficult to avoid. The MC1648 is really intended for tuning-diode control in phase-locked loops operating at VHF. This difficulty is inherent in wideband devices, especially oscillator circuits connected to their tank by a single "hot" terminal, where there is simply no isolation between the amplifier's input and output paths. Any resonance in the associated circuitry can control the frequency of oscillation.

The popular SA/NE602 mixer IC has a built-in oscillator and can be found in many published circuits. This device has separate input and output pins to the tank and has proved to be quite tame. It may not have been "improved" yet (so far, it has progressed from the SA/NE602 to the SA/NE602A, the A version affording somewhat higher dynamic range than the original SA/NE602). It might be a good idea for anyone laying out a board using one to take a little extra care to keep PCB traces short in the oscillator section to build in some safety margin so that the board can be used reliably in the future. Experienced (read: "bitten") professional designers know that their designs are going to be built for possibly more than 10 years and have learned to make allowances for the progressive improvement of semiconductor manufacture.

9.3.5 Temperature Compensation

The general principle for creating a high-stability VFO is to use components with minimal temperature coefficients in circuits that are as insensitive as possible to changes in components' secondary characteristics. Even after careful minimization of the causes of temperature sensitivity, further improvement can still be desirable. The traditional method was to split one of the capacitors in the tank so that it could be apportioned between low-temperature-coefficient parts and parts with deliberate temperature dependency. Only a limited number of different, controlled temperature coefficients are available, so the proportioning between low coefficient and controlled coefficient parts was varied to "dilute" the temperature sensitivity of a part more sensitive than needed. This was a tedious process, involving much trial and error, an undertaking made more complicated by the difficulty of arranging means of heating and cooling the unit being compensated. (Hayward described such a means in December 1993 *QST*.) As commercial and military equipment have been based on frequency syn-

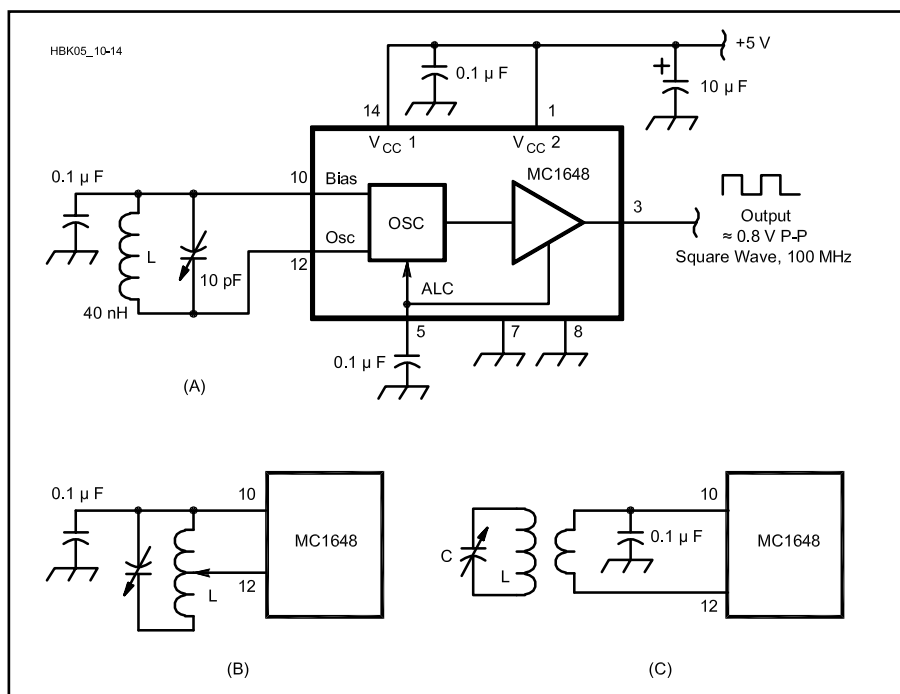


Fig 9.17 — One of the few ICs ever designed solely for oscillator service, the ECL Motorola MC1648 (A) requires careful design to avoid VHF parasitics when operating at HF. Keeping its tank Q high is another challenge; B and C show means of coupling the IC's low-impedance oscillator terminals to the tank by tapping up on the tank coil (B) or with a link (C).

thesizers for some time, supplies of capacitors with controlled temperature sensitivity are drying up. An alternative approach is needed.

A temperature-compensated crystal oscillator (TCXO) is an improved-stability version of a crystal oscillator that is used widely in industry. Instead of using controlled-temperature coefficient capacitors, most TCXOs use a network of thermistors and normal resistors to control the bias of a tuning diode. (See this chapter's Phase-Locked Loop section for information on the use of varactor diodes for oscillator tuning.) Manufacturers measure the temperature vs frequency characteristic of sample oscillators, and use a computer program to calculate the optimum normal resistor values for production. This can reliably achieve at least a tenfold improvement in stability. We are not interested in mass manufacture, but the idea of a thermistor tuning a varactor is worth stealing. The parts involved are likely to be available for a long time.

Browsing through component suppliers' catalogs shows ready availability of 4.5- to 5-k Ω -bead thermistors intended for temperature-compensation purposes, at less than a dollar each. **Fig 9.18** shows a circuit based on this form of temperature compensation. Commonly available thermistors have negative temperature coefficients, so as temperature rises, the voltage at the counterclockwise (CCW) end of R8 increases, while that at the clockwise (CW) end drops. Somewhere near the center, there is no change. Increasing the voltage on the tuning diode decreases its capacitance, so settings toward R8's CCW end simulate a negative-temperature-coefficient capacitor; toward its clockwise end, a positive-temperature-coefficient part. Choose

R1 to pass 8.5 mA from whatever supply voltage is available to the 6.2-V reference diode, D1. The 1N821A/1N829A-family diode used has a very low temperature coefficient and needs 7.5 mA bias for best performance; the bridge takes 1 mA. R7 and R8 should be good-quality multi-turn trimmers. D2 and C1 need to be chosen to suit the oscillator circuit. Choose the least capacitance that provides enough compensation range. This reduces the noise added to the oscillator. (It is possible, though tedious, to solve for the differential varactor voltage with respect to R2 and R5, via differential calculus and circuit theory. The equations in Hayward's 1993 article can then be modified to accommodate the additional capacitors formed by D2 and C1.) Use a single ground point near D2 to reduce the influence of ground currents from other circuits. Use good-quality metal-film components for the circuit's fixed resistors.

The novelty of this circuit is that it was designed to have an easy and direct adjustment process. The circuit requires two adjustments, one at each of two different temperatures, and achieving them requires a stable frequency counter that can be kept far enough from the radio so that the radio, not the counter, is subjected to the temperature extremes. (Using a receiver to listen to the oscillator under test can speed the adjustments.) After connecting the counter to the oscillator to be corrected, run the radio containing the oscillator and compensator in a room-temperature, draft-free environment until the oscillator's frequency reaches its stable operating temperature rise over ambient. Lock its tuning, if possible. Adjust R7 to balance the bridge. This causes a drop of 0 V across R8, a condition you can

reach by winding R8 back and forth across its range while slowly adjusting R7. When the bridge is balanced and 0 V appears across R8, adjusting R8 causes no frequency shift. When you've found this R7 setting, leave it there, set R8 to the exact center of its range and record the oscillator frequency.

Run the radio in a hot environment and allow its frequency to stabilize. Adjust R8 to restore the frequency to the recorded value. The sensitivity of the oscillator to temperature should now be significantly reduced between the temperatures at which you performed the adjustments. You will also have somewhat improved the oscillator's stability outside this range.

For best results with any temperature-compensation scheme, it's important to group all the oscillator and compensator components in the same box, avoiding differences in airflow over components. A good oscillator should not dissipate much power, so it's feasible, even advisable, to mount all of the oscillator components in an unventilated box. In the real world, temperatures change, and if the components being compensated and the components doing the compensating have different thermal time constants, a change in temperature can cause a temporary change in frequency until the slower components have caught up. One cure for this is to build the oscillator in a thick-walled metal box that's slow to heat or cool, and so dominates and reduces the possible rate of change of temperature of the circuits inside. This is sometimes called a *cold oven*.

9.3.6 Shielding and Isolation

Oscillators contain inductors running at moderate power levels and so can radiate strong enough signals to cause interference with other parts of a radio, or with other radios. Oscillators are also sensitive to radiated signals. Effective shielding is therefore important. A VFO used to drive a power amplifier and antenna (to form a simple CW transmitter) can prove surprisingly difficult to shield well enough. Any leakage of the power amplifier's high-level signal back into the oscillator can affect its frequency, resulting in a poor transmitted note. If the radio gear is in the station antenna's near field, sufficient shielding may be even more difficult. The following rules of thumb continue to serve ham builders well:

- Use a complete metal box, with as few holes as possible drilled in it, with good contact around surface(s) where its lid(s) fit(s) on.
- Use feedthrough capacitors on power and control lines that pass in and out of the VFO enclosure, and on the transmitter or transceiver enclosure as well.
- Use *buffer amplifier* circuitry that amplifies the signal by the desired amount and provide sufficient attenuation of signal energy flowing in the reverse direction. This is known as *reverse isolation* and is a frequently

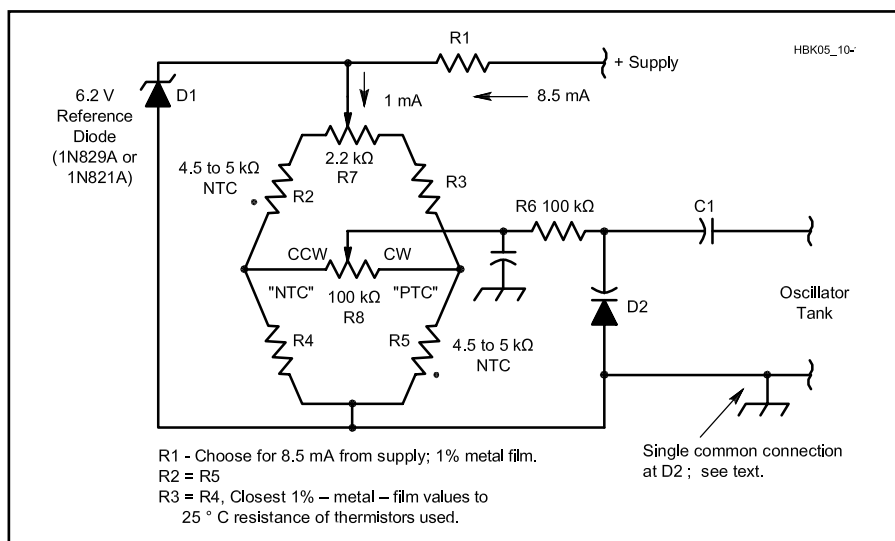


Fig 9.18 — Oscillator temperature compensation is difficult because of the scarcity of negative-temperature-coefficient capacitors. This circuit, by GM4ZNX, uses a bridge containing two identical thermistors to steer a tuning diode for drift correction. The 6.2-V Zener diode used (a 1N821A or 1N829A) is a temperature-compensated part; just any 6.2-V Zener will not do.

overlooked loophole in shielding. Figs 9.15 and 9.16 include buffer circuitry of proven performance. As another (and higher-cost) option, consider using a high-speed buffer-amplifier IC (such as the LM6321N by National Semiconductor, a part that combines the high input impedance of an op amp with

the ability to drive 50-Ω loads directly up into the VHF range).

- Use a mixing-based frequency-generation scheme instead of one that operates straight through or by means of multiplication. Such a system's oscillator stages can operate on frequencies with no direct frequency

relationship to its output frequency.

- Use the time-tested technique of running your VFO at a *subharmonic* of the output signal desired — say, 3.5 MHz in a 7-MHz transmitter — and *multiply* its output frequency in a suitably nonlinear stage for further amplification at the desired frequency.

9.4 Designing an Oscillator

We've covered a lot of ground about how oscillators work, their limitations and a number of interesting circuits, so the inevitable question arises of how to design one. Let's make the embarrassing confession right here at the beginning: Very few oscillators you see in published circuits or commercial equipment were designed by the equipment's designer. Almost all have been "Borrowed," "Re-used" or just plain stolen. While recycling in general is important for the environment, it means in this case that very few professional or amateur designers have ever designed an oscillator from scratch. We all have collections of circuits we've "harvested," and we adjust a few values or change a device type to produce something to suit a new project. Oscillators aren't designed, they evolve. They seem to have a life of their own. The Clarke & Hess book listed in the references contains one of the few published classical design processes.

Modern RF design is heavily reliant on simulation. Universities have shifted emphasis from hardware labs to computer simulations. Simulators work well on amplifiers, filters, modulators, mixers and so on, but not as well on oscillators. This leaves even graduate-level RF engineers rather light on the subject of oscillators.

Such a void is a back-door opportunity to oscillator analysis. Simulation has not been used much by amateurs because it is computationally intensive. Most recent PCs have plenty of power for this task, however. You may not be aware of how powerful your machine is, because things like operating systems and word processor software have become progressively inefficient. Set your computer loose on a math-intensive task like circuit simulation and see what a beast has been hiding behind the flashy graphics and zillions of type fonts.

The simulator needs to be able to handle oscillators, and it needs to be affordable on an amateur budget. High-end RF CAD packages usually contain tools for handling oscillators, but they aren't easy to use and many are afterthought additions that don't mesh with the rest of the package. Oscillators are diabolical things to simulate. Even if you can afford to shovel money at the problem, it still takes a bit of creativity to use a full "bells and whistles" simulator on an oscillator and for the results to make sense. (For detailed information on

simulation, see the chapter on **Computer-Aided Circuit Design.**)

An oscillator is a simple loop with signal flowing round and round in it. We can view the signal flow as being many components adding together at some point at some time. We can think of these components as being different vintages. This component came from thermal noise X microseconds ago and has been round the loop Y times, and that component... you can see the pattern. This is hard to analyze because all components get summed, not separated. So instead of thinking of our oscillator as a single stage with everything distributed in time, let's distribute it in space as well.

The GM4ZNX "Swiss-Roll" technique is to think of a rolled-up jelly cake and unroll the oscillator circuit as illustrated in Fig 9.19. We break the loop open, which leaves us with a tuned amplifier circuit with an input and an output terminal. In a closed oscillator loop, the output terminal would drive the input terminal. In the unrolled circuit, the output terminal drives the input of a second stage and so on.

Instead of infinitely looping signals in a

single stage, we now have a single signal flow down an infinite string of stages. This doesn't sound any better, but we only need to handle a couple of hundred stages. Think about that... we are going to simulate a 200-stage tuned amplifier! But all the stages are identical, so we only have to draw one stage and have the others built as hierarchical repeats. On a 2005 model laptop, a simulation takes several minutes, which is fine.

Affordable RF analysis programs are normally limited to linear simulations and can't handle the oscillator's amplitude control mechanism. We also need a simulator that can handle random noise at the same time so the choice of tools becomes very limited. One example of a suitable simulation package, based on *SPICE*, is available free from the Linear Technologies Web site, www.linear.com. (The program is called *SWCADIII* or *LTSPICE*.) It is optimized for the analysis of switch-mode power supply (SMPS) circuits. This is very good for our purposes. In an SMPS things ring at high frequencies, and slow things settle. *LTSPICE* has some trickery which allows it to easily handle RF speed

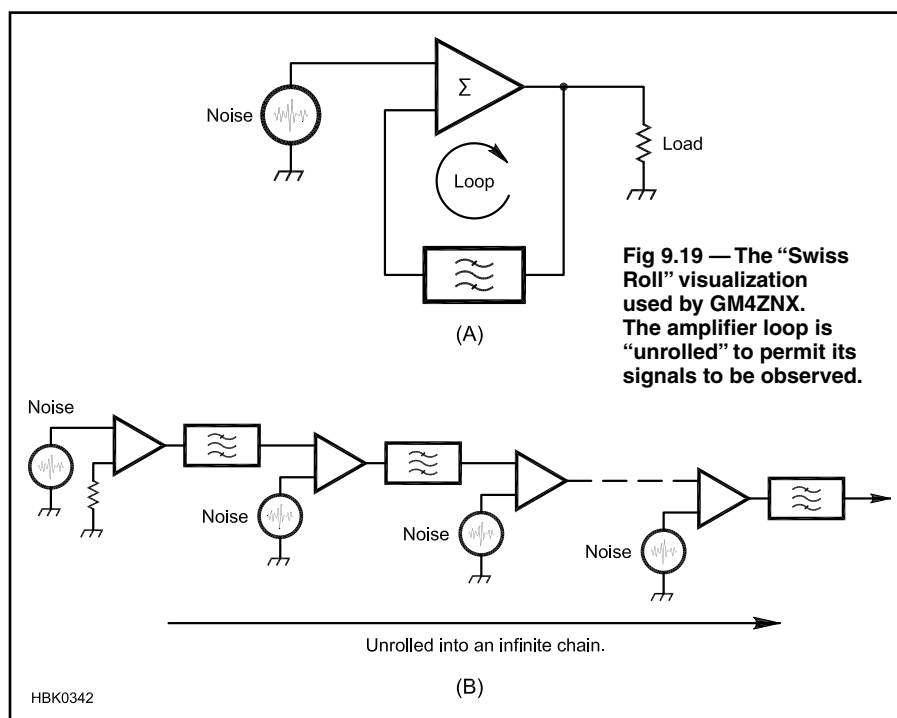


Fig 9.19 — The "Swiss Roll" visualization used by GM4ZNX. The amplifier loop is "unrolled" to permit its signals to be observed.

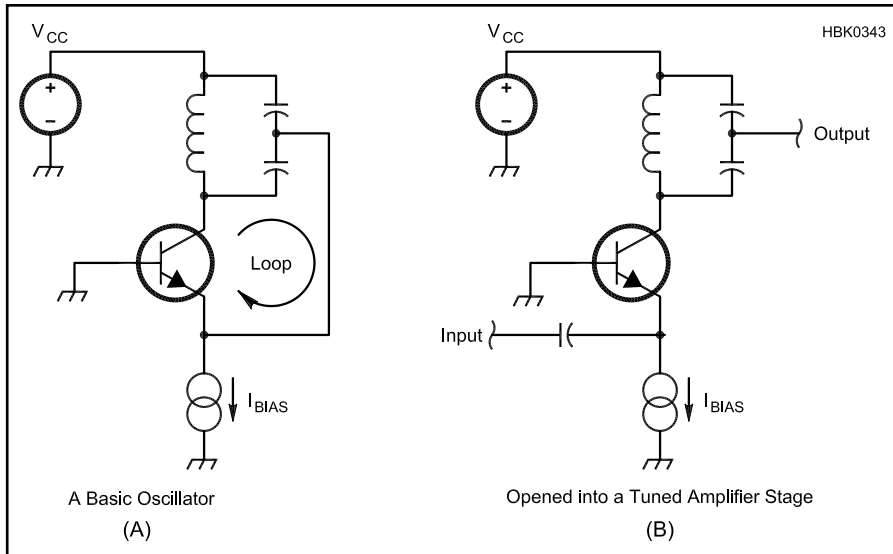


Fig 9.20 — The basic oscillator circuit (A) is built on a tuned amplifier circuit (B).

events, while running a simulation efficiently over a long enough period for control loops to settle. This is what makes it efficient for oscillators. Our oscillator circuits are run at such large signal levels that as the oscillator reaches its long term output, it will affect bias conditions, which are slow-damped by decoupling components. (Again, refer to the **Computer-Aided Circuit Design** chapter for more information on circuit simulation.)

LTSPICE can handle noise, and it can also handle hierarchical schematics. We draw our basic oscillator circuit once, and create a symbol for it. We can then use that symbol in a higher level schematic. For our worked example of an oscillator analysis, a single-stage schematic and symbol were created, then a higher level, a 10-pack of those symbols was created. The top level was made of 20 10-packs. Files for these designs are in the *Handbook's* companion CD, but to be able to set them up in *LTSPICE* you will need to read *LTSPICE's* help files on hierarchical designs. Hierarchical schematics save the need to draw our oscillator stage 200 times. It also allows editing a parameter on one schematic to change all 200 stages at once. Without this feature, things would be tedious.

Fig 9.20 shows a basic oscillator circuit. The transistor is a bipolar type, operated in common-base mode. The resonator is an LC tank with a capacitive tap. The common-base amplifier gives less than unity current gain, low input impedance and high output impedance. There has to be an impedance transformation to make the loop have enough gain to oscillate, and the capacitive tap is it. Instead of having bias resistor networks, the stage has a voltage source to set the collector bias voltage, and a current source to set the quiescent emitter current. You can just type in your bias values without having to calculate resistor

values. One drawback of *LTSPICE* is that it has few RF parts in its libraries, but a search on the Internet will find user groups and guidance on editing models for other *SPICE* variants to work with *LTSPICE*. The 2N4142 in the supplied library is used in this example. A 5 V collector bias and 0.2 mA emitter bias have been chosen as starting points.

In designing this circuit, we must create a stage gain greater than unity, and allow the operating level to rise until that gain is compressed to exactly unity. With a bipolar transistor at RF, we do not want it to go into saturation. Instead, we want it to go into cut-off before that can happen. Set the emitter current for the level you want, and then make sure there is enough collector bias voltage that the instantaneous collector voltage is always a few volts more positive than the emitter. The L/C ratio of the tank, and the capacitive tap ratio are surprisingly tolerant, the circuit will oscillate with these parameters varied over an appreciable range. If your goal is low drift, then you should go for high capacitance in the tank, to dilute the effect of strays. If your goal is low phase noise, then you should try to create as high a tank Q as possible.

Because oscillators of this type use nonlinear device operation to control amplitude, do not try to get low levels of harmonics on their output — the harmonic creation mechanism is fundamental to the oscillator. Try an oscillator with a detector and feedback loop to control its level instead. The square-law characteristic of JFETs is an excellent level-stabilizing mechanism and accounts for their popularity in oscillators. However, their wide range of I_{DSS} for any given type, can be troublesome. MMIC amplifiers with internal feedback are probably the worst choice of device, but some types can be used in special circumstances.

In the simulation circuit provided here you

will find some odd things. The random number source is of uniform density, so several of them are added together to approximate Gaussian noise. The collector load resistor which represents the output of the oscillator is split into two parts, a resistor to ground on the output is needed to define the dc potential of a node between the capacitors of adjacent stages (or else *SPICE* complains) and it also loads the tank via the tap.

When you have got all the schematics in the right directories for *LTSPICE* to use them, and run the simulation, you will have an immense database of all waveforms at all nodes. You can now probe around the top level schematic. The first transistor in the chain acts as an emitter-follower so you can see its noise voltage coming out of its input if you probe there. The way the random number generators work is tied to the simulation time clock and you will see the first random number generator turn on at about 2 μ s into the simulation, followed progressively by the others. This is just an oddity of the realization, but it does illustrate the summation of differently-seeded generators to approximate Gaussian distribution of noise.

Probing along, 10 stages at a time, you will see bigger and bigger noise waveforms until you start to notice the effect of the cumulative selectivity, as it starts to look like a noisy sine wave. Further along you will see the level begin to stabilize. If you zoom out to a larger time-scale, you will see that the sine wave seems to have low frequency random noise AM applied to it. As you probe further along you will see this “AM” compressed until it isn't seen, by the level control action of the oscillator and progressively narrowing bandwidth. Long before you get to the end of the 200 stages, you will have the appearance of a stable sine wave. Remember that the taps earlier in the structure represent the signal in a closed loop oscillator at times close to when it started-up. In a running oscillator, compression eventually reduces the gain of all amplification passes of all signal components. Fourier transform conversion can be used to convert these time-pictures into spectrum displays, if you want to explore further.

Among the accompanying files there is also a simulator that takes a single stage and plots its compression characteristic. It could be improved by adding earlier and later stages to make the source and load impedances more representative. The example oscillator can also have a model of a quartz crystal added in series with its output, to simulate a crystal oscillator. Explore! And have fun.

How can a lower phase noise oscillator be designed? Firstly if you use a lower noise transistor, it will take more stages of gain and filtering to bring it up to the stable output level. The greater repetition of filtering before noise reaches a significant level narrows the

bandwidth of the output signal. Secondly, if you can engineer a higher-Q tank circuit, each pass through the tank has a greater narrowing effect.

The simulation files for this section are included on the CD-ROM that accompanies this book:

SwissRollDemoBasicStage.asc —
(The oscillator stage. Editing this changes

every stage)

SwissRollDemoBasicStage.asc —
(The symbol file for use in higher level schematics)

SwissRollDemo10Pack.asc —
(10 basic stages as a building block)

SwissRollDemo10Pack.asc —
(The symbol for a 10 pack)

SwissRollDemoTopLevel.asc —

(This is the real simulation, uses the above as components)

SwissRollDemoCompression.asc —
(Crude simulation showing stage gain compression)

SwissRollDemoStageBandwidth.asc —
(Crude simulation showing filter Q of one stage)

9.5 Quartz Crystals in Oscillators

Because crystals afford Q values and frequency stabilities that are orders of magnitude better than those achievable with LC circuits, fixed-frequency oscillators usually use quartz crystal resonators. Master references for frequency counters and synthesizers are always based on crystal oscillators.

So glowing is the executive summary of the crystal's reputation for stability that newcomers to radio experimentation naturally believe that the presence of a crystal in an oscillator will force oscillation at the frequency stamped on the can. This impression is usually revised after the first few experiences to the contrary! There is no sure-fire crystal oscillator circuit (although some are better than others); reading and experience soon provide a learner with plenty of anecdotes to the effect that:

- Some circuits have a reputation of being temperamental, even to the point of not always starting.
- Crystals sometimes mysteriously oscillate on unexpected frequencies.

Even crystal manufacturers have these problems, so don't be discouraged from building crystal oscillators. The occasional uncooperative oscillator is a nuisance, not a disaster, and it just needs a little individual attention. Knowing how a crystal behaves is the key to a cure.

Dr Ulrich Rohde, NIUL, has generously contributed a pair of detailed papers that discuss the crystal oscillator along with several HF and VHF designs. Both papers, "Quartz Crystal Oscillator Design" and "A Novel Grounded Base Oscillator Design for VHF/UHF Frequencies" are included on the CD-ROM accompanying this book.

9.5.1 Quartz and the Piezoelectric Effect

Quartz is a crystalline material with a regular atomic structure that can be distorted by the simple application of force. Remove the force, and the distorted structure springs back to its original form with very little energy loss. This property allows *acoustic waves* — sound — to propagate rapidly through quartz with very little attenuation, because the velocity of an acoustic wave depends on

the elasticity and density (mass/volume) of the medium through which the wave travels.

If you heat a material, it expands. Heating may cause other characteristics of a material to change — such as elasticity, which affects the speed of sound in the material. In quartz, however, expansion and change in the speed of sound are very small and tend to cancel, which means that the transit time for sound to pass through a piece of quartz is very stable.

The third property of this wonder material is that it is *piezoelectric*. Apply an electric field to a piece of quartz and the crystal lattice distorts just as if a force had been applied. The electric field applies a force to electrical charges locked in the lattice structure. These charges are captive and cannot move around in the lattice as they can in a semiconductor, for quartz is an insulator. A capacitor's dielectric stores energy by creating physical distortion on an atomic or molecular scale. In a piezoelectric crystal's lattice, the distortion affects the entire structure. In some piezoelectric materials, this effect is sufficiently pronounced that special shapes can be made that bend *visibly* when a field is applied.

Consider a rod made of quartz. Any sound wave propagating along it eventually hits an end, where there is a large and abrupt change in acoustic impedance. Just as when an RF wave hits the end of an unterminated transmission line, a strong reflection occurs. The rod's other end similarly reflects the wave. At some frequency, the phase shift of a round trip will be such that waves from successive round trips exactly coincide in phase and reinforce each other, dramatically increasing the wave's amplitude. This is *resonance*.

The passage of waves in opposite directions forms a standing wave with antinodes at the rod ends. Here we encounter a seeming ambiguity: not just one, but a family of different frequencies, causes standing waves — a family fitting the pattern of $1/2$, $2/3$, $5/2$, $7/2$ and so on, wavelengths into the length of the rod. And this is the case: A quartz rod can resonate at any and all of these frequencies.

The lowest of these frequencies, where the crystal is $1/2$ -wavelength long, is called the *fundamental mode*. The others are named the third, fifth, seventh and so on, *overtone*s. There is a small phase-shift error during reflection

at the ends, which causes the frequencies of the overtone modes to differ slightly from odd integer multiples of the fundamental. Thus, a crystal's third overtone is very close to, but not exactly, three times, its fundamental frequency. Many people are confused by overtones and harmonics. Harmonics are additional signals at exact integer multiples of the fundamental frequency. Overtone is not signals at all; they are additional resonances that can be exploited if a circuit is configured to excite them.

The crystals we use most often resonate in the 1- to 30-MHz region and are of the *AT-cut, thickness shear* type, although these last two characteristics are rarely mentioned. A 15-MHz-fundamental crystal of this type is about 0.15 mm thick. Because of the widespread use of reprocessed war-surplus, pressure-mounted FT-243 crystals, you may think of crystals as small rectangles on the order of a half-inch in size. The crystals we

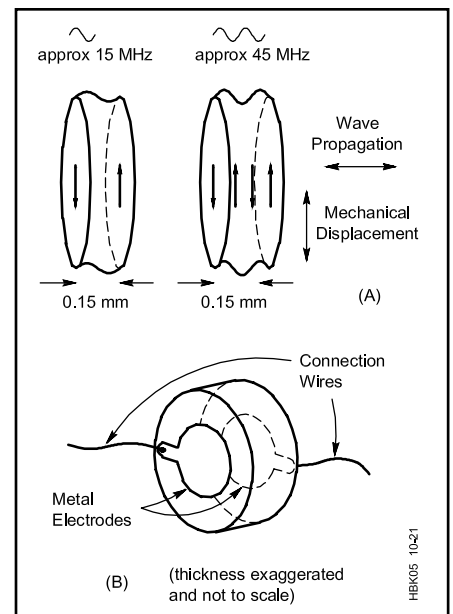


Fig 9.21 — Thickness-shear vibration at a crystal's fundamental and third overtone (A); B shows how the modern crystals commonly used by radio amateurs consist of etched quartz discs with electrodes deposited directly on the crystal surface.

commonly use today are discs, etched and/or doped to their final dimensions, with metal electrodes deposited directly on the quartz. A crystal's diameter does not directly affect its frequency; diameters of 8 to 15 mm are typical. (Quartz crystals are also discussed in the **RF and AF Filters** chapter.)

AT-cut is one of a number of possible standard designations for the orientation at which a crystal disc is sawed from the original quartz crystal. The crystal lattice atomic structure is asymmetric, and the orientation of this with respect to the faces of the disc influences the crystal's performance. *Thickness shear* is one of a number of possible orientations of the crystal's mechanical vibration with respect to the disc. In this case, the crystal vibrates perpendicularly to its thickness. This is not easy to visualize, and diagrams don't help much, but **Fig 9.21** is an attempt at illustrating this. Place a moist bathroom sponge between the palms of your hands, move one hand up and down, and you'll see thickness shear in action.

There is a limit to how thin a disc can be made, given requirements of accuracy and price. Traditionally, fundamental-mode crystals have been made up to 20 MHz, although 30 MHz is now common at a moderately raised price. Using techniques pioneered in the semiconductor industry, crystals have been made with a central region etched down to a thin membrane, surrounded by a thick ring for robustness. This approach can push fundamental resonances to over 100 MHz, but these are more lab curiosities than parts for everyday use. The easy solution for higher frequencies is to use a nice, manufacturably-thick crystal on an overtone mode. All crystals have all modes, so if you order a 28.060-MHz, third-overtone unit for a little QRP transmitter, you'll get a crystal with a fundamental resonance somewhere near 9.353333 MHz, but its manufacturer will have adjusted the thickness to plant the third overtone exactly on the ordered frequency. An accomplished manufacturer can do tricks with the flatness of the disc faces to make the wanted overtone mode a little more active and the other modes a little less active. (As some builders discover, however, this does not *guarantee* that the wanted mode is the most active!)

Quartz's piezoelectric property provides a simple way of driving the crystal electrically. Early crystals were placed between a pair of electrodes in a case. This gave amateurs the opportunity to buy surplus crystals, open them and grind them a little to reduce their thickness, thus moving them to higher frequencies. The frequency could be reduced very slightly by loading the face with extra mass, such as by blackening it with a soft pencil. Modern crystals have metal electrodes deposited directly onto their surfaces (**Fig 9.21B**), and such tricks no longer work.

The piezoelectric effect works both ways.

Deformation of the crystal produces voltage across its electrodes, so the mechanical energy in the resonating crystal can also be extracted electrically by the same electrodes. Seen electrically, at the electrodes, the mechanical resonances look like electrical resonances. Their Q is very high. A Q of 10,000 would characterize a *poor* crystal nowadays; 100,000 is often reached by high-quality parts. For comparison, a Q of over 200 for an LC tank is considered good.

9.5.2 Frequency Accuracy

A crystal's frequency accuracy is as outstanding as its Q. Several factors determine a crystal's frequency accuracy. First, the manufacturer makes parts with certain tolerances: ± 200 ppm for a low-quality crystal for use as in a microprocessor clock oscillator, ± 10 ppm for a good-quality part for professional radio use. Anything much better than this starts to get expensive! A crystal's resonant frequency is influenced by the impedance presented to its terminals, and manufacturers assume that once a crystal is brought within several parts per million of the nominal frequency, its user will perform fine adjustments electrically.

Second, a crystal ages after manufacture. Aging could give increasing or decreasing frequency; whichever, a given crystal usually keeps aging in the same direction. Aging is rapid at first and then slows down. Aging is influenced by the care in polishing the surface of the crystal (time and money) and by its holder style. The cheapest holder is a soldered-together, two-part metal can with glass bead insulation for the connection pins. Soldering debris lands on the crystal and affects its frequency. Alternatively, a two-part metal can be made with flanges that are pressed together until they fuse, a process called *cold-welding*. This is much cleaner and improves aging rates roughly fivefold compared to soldered cans. An all-glass case can be made in two parts and fused together by heating in a vacuum. The vacuum raises the Q, and the cleanliness results in aging that's roughly 10 times slower than that achievable with a soldered can. The

best crystal holders borrow from vacuum-tube assembly processes and have a *getter*, a highly reactive chemical substance that traps remaining gas molecules, but such crystals are used only for special purposes.

Third, temperature influences a crystal. A reasonable, professional quality part might be specified to shift not more than ± 10 ppm over 0 to 70 °C. An AT-cut crystal has an S-shaped frequency-versus-temperature characteristic, which can be varied by slightly changing the crystal cut's orientation. **Fig 9.22** shows the general shape and the effect of changing the cut angle by only a few seconds of arc. Notice how all the curves converge at 25 °C. This is because this temperature is normally chosen as the reference for specifying a crystal. The temperature stability specification sets how accurate the manufacturer must make the cut. Better stability may be needed for a crystal used as a receiver frequency standard, frequency counter clock and so on. A crystal's temperature characteristic shows a little hysteresis. In other words, there's a bit of offset to the curve depending on whether temperature is increasing or decreasing. This is usually of no consequence except in the highest-precision circuits.

It is the temperature of the quartz that is important, and as the usual holders for crystals all give effective thermal insulation, only a couple of milliwatts dissipation by the crystal itself can be tolerated before self-heating becomes troublesome. Because such heating occurs in the quartz itself and does not come from the surrounding environment, it defeats the effects of temperature compensators and ovens.

The techniques shown earlier for VFO for temperature compensation can also be applied to crystal oscillators. An after-compensation drift of 1 ppm is routine and 0.5 ppm is good. The result is a *temperature-compensated crystal oscillator (TCXO)*. Recently, oscillators have appeared with built-in digital thermometers, microprocessors and ROM look-up tables customized on a unit-by-unit basis to control a tuning diode via a digital-to-analog converter (DAC) for temperature compensation. These *digitally temperature-compensated oscillators (DTCXOs)* can reach 0.1 ppm over the temperature range. With automated production and adjustment, they promise to become the cheapest way to achieve this level of stability.

Oscillators have long been placed in temperature-controlled *ovens*, which are typically held at 80 °C. Stability of several parts per billion can be achieved over temperature, but this is a limited benefit as aging can easily dominate the accuracy. These are usually called *oven-controlled crystal oscillators (OCXOs)*.

Fourth, the crystal is influenced by the impedance presented to it by the circuit in which it is used. This means that care is needed to make the rest of an oscillator circuit stable, in


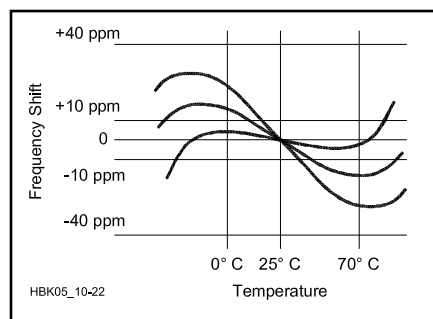


Fig 9.22 — Slight changes in a crystal cut's orientation shift its frequency-versus-temperature curve.

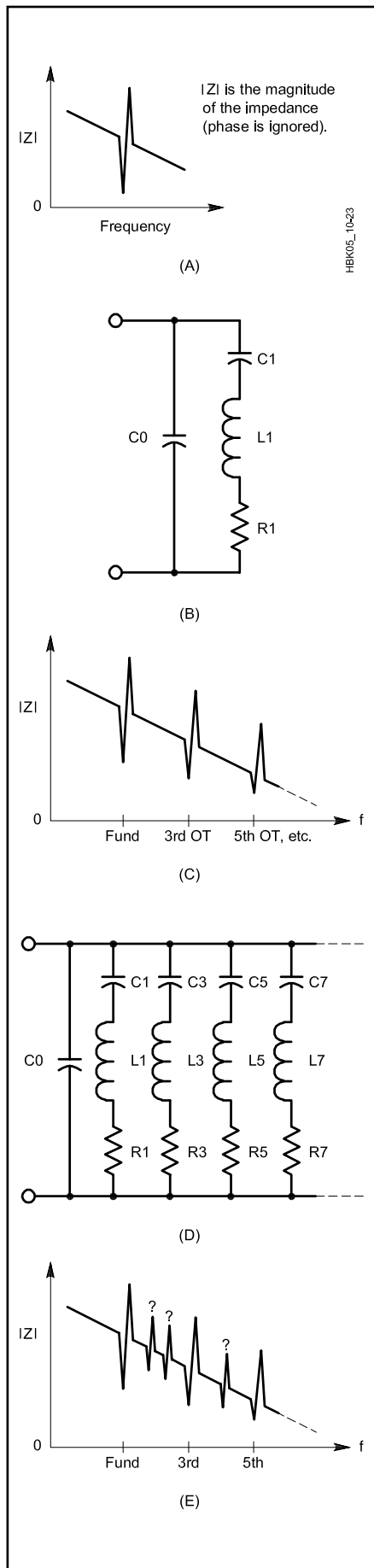

HBR05_10-23

Table 9.2
Typical Equivalent Circuit Values for a Variety of Crystals

Crystal Type	Series L	Series C (pF)	Series R (Ω)	Shunt C (pF)
1-MHz fundamental	3.5 H	0.007	340	3.0
10-MHz fundamental	9.8 mH	0.026	7	6.3
30-MHz third overtone	14.9 mH	0.0018	27	6.2
100-MHz fifth overtone	4.28 mH	0.0006	45	7.0

terms of impedance and phase shift.

Gravity can slightly affect crystal resonance. Turning an oscillator upside down usually produces a small frequency shift, usually much less than 1 ppm; turning the oscillator back over reverses this. This effect is quantified for the highest-quality reference oscillators.

9.5.3 The Equivalent Circuit of a Crystal

Because a crystal is a passive, two-terminal device, its electrical appearance is that of an impedance that varies with frequency. **Fig 9.23A** shows a very simplified sketch of the magnitude (phase is ignored) of the impedance of a quartz crystal. The general trend of dropping impedance with increasing frequency implies capacitance across the crystal. The sharp fall to a low value resembles a series-tuned tank, and the sharp peak resembles a parallel-tuned tank. These are referred to as series and parallel resonances. **Fig 9.23B** shows a simple circuit that will produce this impedance characteristic. The impedance looks purely resistive at the exact centers of both resonances, and the region between them has impedance increasing with frequency, which looks inductive.

C1 (sometimes called *motional capacitance*, C_m , to distinguish it from the lumped capacitance it approximates) and L1 (*motional inductance*, L_m) create the series resonance, and as C0 and R1 are both fairly small, the impedance at the bottom of the dip is very close to R1. At parallel resonance, L1 is resonating with C1 and C0 in series, hence the higher frequency. The impedance of the parallel tank is immense, the terminals are connected to a capacitive tap, which causes them to see only a small fraction of this, which is still a very large impedance. The overtones should not be neglected, so **Figs 9.23C** and **9.23D** include them. Each overtone has series and parallel resonances and so appears as a series tank in the equivalent circuit. C0 again provides the shifted parallel resonance.

Fig 9.23 — Exploring a crystal's impedance (A) and equivalent circuit (B) through simplified diagrams. C and D extend the investigation to include overtones; E, to spurious responses not easily predictable by theory or controllable through manufacture. A crystal may oscillate on any of its resonances under the right conditions.

This is still simplified, because real-life crystals have a number of spurious, unwanted modes that add yet more resonances, as shown in **Fig 9.23E**. These are not well controlled and may vary a lot even between crystals made to the same specification. Crystal manufacturers work hard to suppress these spurs and have evolved a number of recipes for shaping crystals to minimize them. Just where they switch from one design to another varies from manufacturer to manufacturer.

Always remember that the equivalent circuit is just a representation of crystal behavior and does not represent circuit components actually present. Its only use is as an aid in designing and analyzing circuits using crystals. **Table 9.2** lists typical equivalent-circuit values for a variety of crystals. It is impossible to build a circuit with 0.026 to 0.0006-pF capacitors; such values would simply be swamped by strays. Similarly, the inductor must have a Q that is orders of magnitude better than is practically achievable, and impossibly low stray C in its winding.

The values given in **Table 9.2** are nothing more than rough guides. A crystal's frequency is tightly specified, but this still allows inductance to be traded for capacitance. A good manufacturer could hold these characteristics within a $\pm 25\%$ band or could vary them over a 5:1 range by special design. Similarly marked parts from different sources vary widely in motional inductance and capacitance.

Quartz is not the only material that behaves in this way, but it is the best. Resonators can be made out of lithium tantalate and a group of similar materials that have lower Q, allowing them to be *pulled* over a larger frequency range in VCXOs. Much more common, however, are ceramic resonators based on the technology of the well-known ceramic IF filters. These have much lower Q than quartz and much poorer frequency precision. They serve mainly as clock resonators for cheap microprocessor systems in which every last cent must be saved. A ceramic resonator could be used as the basis of a wide range, cheap VXO, but its frequency stability would not be as good as a good LC VFO.

9.5.4 Crystal Oscillator Circuits

(See also the papers "Quartz Crystal Oscillator Design" and "A Novel Grounded Base

Oscillator Design for VHF/UHF Frequencies” by Rohde, included on the CD-ROM accompanying this book.)

Crystal oscillator circuits are usually categorized as series- or parallel-mode types,

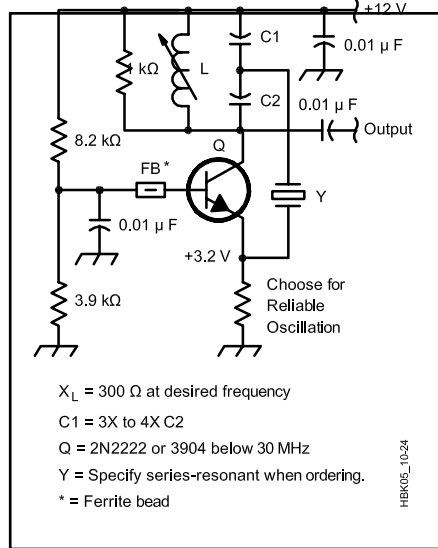


Fig 9.24 — A basic series-mode crystal oscillator. A 2N5179 can be used in this circuit if a lower supply voltage is used' see text.

depending on whether the crystal's low- or high-impedance resonance comes into play at the operating frequency. The series mode is now the most common; parallel-mode operation was more often used with vacuum tubes. **Fig 9.24** shows a basic series-mode oscillator. Some people would say that it is an overtone circuit, used to run a crystal on one of its overtones, but this is not necessarily true. The tank (L-C1-C2) tunes the collector of the common-base amplifier. C1 is larger than C2, so the tank is tapped in a way that transforms to a lower impedance, decreasing signal voltage, but increasing current. The current is fed back into the emitter via the crystal. The common-base stage provides a current gain of less than unity, so the transformer in the form of the tapped tank is essential to give loop gain. There are *two* tuned circuits, the obvious collector tank and the series-mode one “in” the crystal. The tank kills the amplifier's gain away from its tuned frequency, and the crystal will only pass current at the series resonant frequencies of its many modes. The tank resonance is much broader than any of the crystal's modes, so it can be thought of as the crystal setting the frequency, but the tank selecting which of the crystal's modes is active. The tank could be tuned to the crystal's

fundamental, or one of its overtones.

Fundamental oscillators can be built without a tank quite successfully, but there is always the occasional one that starts up on an overtone or spurious mode. Some simple oscillators have been known to change modes while running (an effect triggered by changes in temperature or loading) or to not always start in the same mode! A series-mode oscillator should present a low impedance to the crystal at the operating frequency. In Fig 9.24, the tapped collector tank presents a transformed fraction of the 1-kΩ collector load resistor to one end of the crystal, and the emitter presents a low impedance to the other. To build a practical oscillator from this circuit, choose an inductor with a reactance of about 300 Ω at the wanted frequency and calculate C1 in series with C2 to resonate with it. Choose C1 to be 3 to 4 times larger than C2. The amplifier's quiescent (“idling”) current sets the gain and hence the operating level. This is not easily calculable, but can be found by experiment. Too little quiescent current and the oscillator will not start reliably; too much and the transistor can drive itself into saturation. If an oscilloscope is available, it can be used to check the collector waveform; otherwise, some form of RF voltmeter can be used to allow the collector voltage to be set to 2 to 3 V RMS. 3.3 kΩ would be a suitable starting point for the emitter bias resistor. The transistor type is not critical; 2N2222A or 2N3904 would be fine up to 30 MHz; a 2N5179 would allow operation as an overtone oscillator to over 100 MHz (because of the low collector voltage rating of the 2N5179, a supply voltage lower than 12 V is required). The ferrite bead on the base gives some protection against parasitic oscillation at UHF.

If the crystal is shorted, this circuit should still oscillate. This gives an easy way of adjusting the tank; it is even better to temporarily replace the crystal with a small-value (tens of ohms) resistor to simulate its *equivalent series resistance* (ESR), and adjust L until the circuit oscillates close to the wanted frequency. Then restore the crystal and set the quiescent current. If a lot of these oscillators were built, it would sometimes be necessary to adjust the current individually due to the different equivalent series resistance of individual crystals. One variant of this circuit has the emitter connected directly to the C1/C2 junction, while the crystal is a decoupler for the transistor base (the existing capacitor and ferrite bead not being used). This works, but with a greater risk of parasitic oscillation.

We commonly want to trim a crystal oscillator's frequency. While off-tuning the tank a little will pull the frequency slightly, too much detuning spoils the mode control and can stop oscillation (or worse, make the circuit unreliable). The answer to this is to add

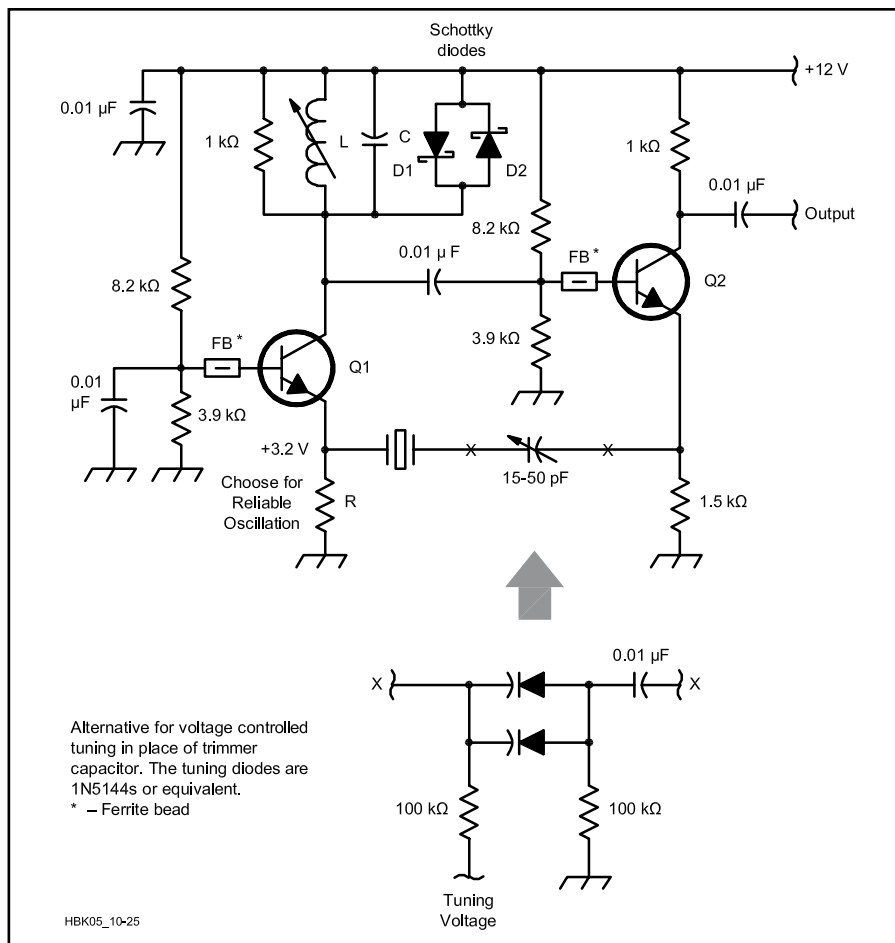


Fig 9.25 — A Butler crystal oscillator.

a trimmer capacitor, which will act as part of the equivalent series tuned circuit, in series with the crystal. This will shift the frequency in one way only, so the crystal frequency must be re-specified to allow the frequency to be varying around the required value. It is common to specify a crystal's frequency with a standard load (30 pF is commonly specified), so that the manufacturer grinds the crystal such that the series resonance of the specified mode is accurate when measured with a capacitor of this value in series. A 15- to 50-pF trimmer can be used in series with

the crystal to give fine frequency adjustment. Too little capacitance can stop oscillation or prevent reliable starting. The Q of crystals is so high that marginal oscillators can take several seconds to start!

This circuit can be improved by reducing the crystal's driving impedance with an emitter follower as in Fig 9.25. This is the Butler oscillator. Again the tank controls the mode to either force the wanted overtone or protect the fundamental mode. The tank need not be tapped because Q2 provides current gain, although the circuit is sometimes

seen with C split, driving Q2 from a tap. The position between the emitters offers a good, low-impedance environment to keep the crystal's in-circuit Q high. R, in the emitter of Q1, is again selected to give reliable oscillation. The circuit has been shown with a capacitive load for the crystal, to suit a unit specified for a 30-pF load. An alternative circuit to give electrical fine tuning is also shown. The diodes across the tank act as limiters to stabilize the operating amplitude and limit the power dissipated in the crystal by clipping the drive voltage to Q2. The tank

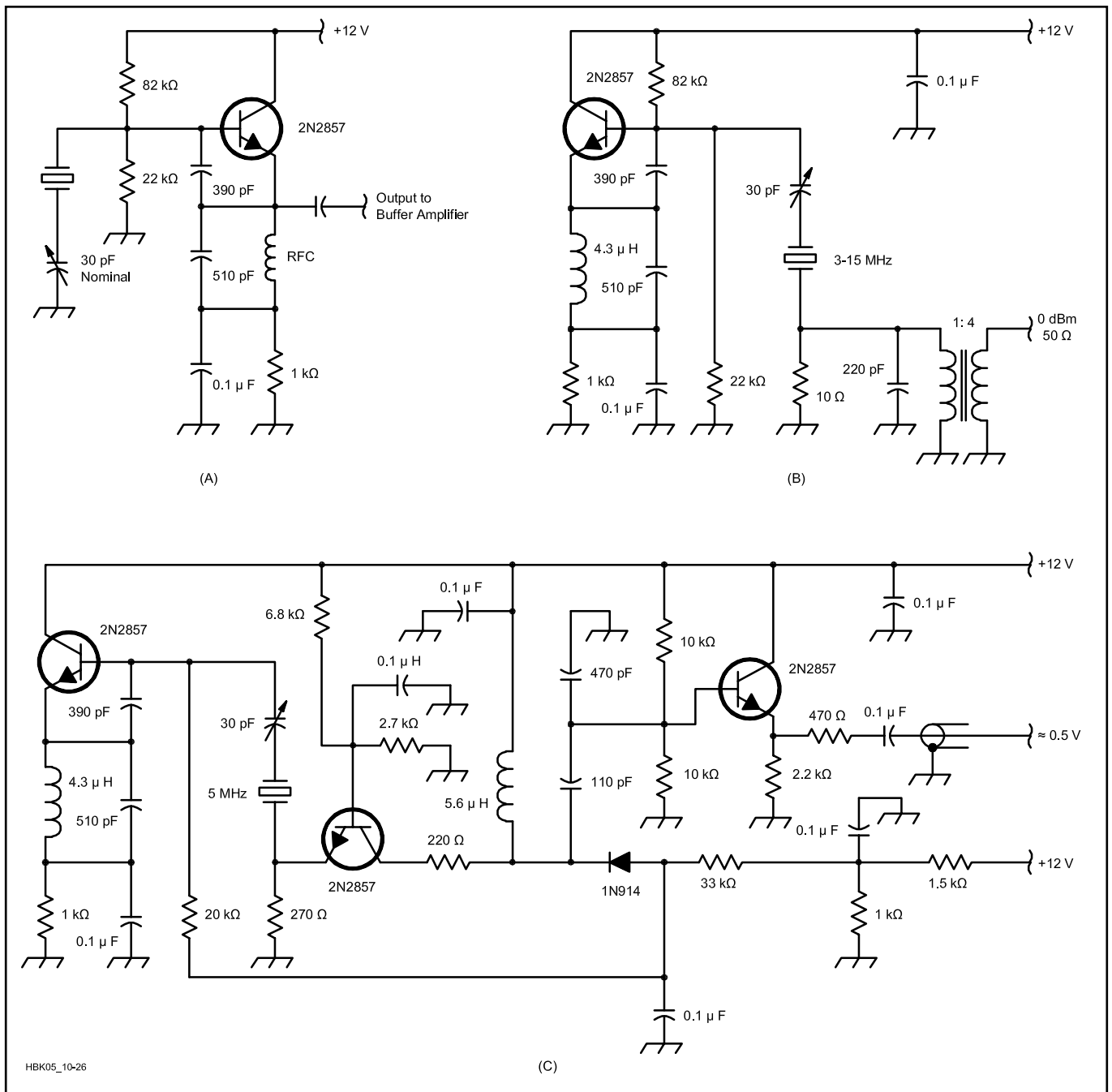


Fig 9.26 — The crystal in the series-tuned Colpitts oscillator at A operates in its series-resonant mode. B shows N1UL's low-noise version, which uses the crystal as a filter and features high harmonic suppression (from Rohde, *Microwave and Wireless Synthesizers Theory and Design*; see references). The circuit at C builds on the B version by adding a common-base output amplifier and ALC loop.

should be adjusted to peak at the operating frequency, not used to trim the frequency. The capacitance in series with the crystal is the proper frequency trimmer.

The Butler circuit works well, and has been used in critical applications to 140 MHz (seventh-overtone crystal, 2N5179 transistor). Although the component count is high, the extra parts are cheap ones. Increasing the capacitance in series with the crystal reduces the oscillation frequency but has a progressively diminishing effect. Decreasing the capacitance pulls the frequency higher, to a point at which oscillation stops; before this point is reached, start-up will become unreliable. The possible amount of adjustment, called *pulling range*, depends on the crystal; it can range from less than 10 to several hundred parts per million. Overtone crystals have much less pulling range than fundamental crystals on the same frequency; the reduction in pulling is roughly proportional to the square of the overtone number.

LOW-NOISE CRYSTAL OSCILLATORS

Fig 9.26A shows a crystal operating in its series mode in a series-tuned Colpitts circuit. Because it does not include an LC tank to prevent operation on unwanted modes, this circuit is intended for fundamental mode operation only and relies on that mode being the most active. If the crystal is ordered for 30-pF loading, the frequency trimming capacitor can be adjusted to compensate for the loading of the capacitive divider of the Colpitts circuit. An unloaded crystal without a trimmer would operate slightly off the exact series resonant frequency in order to create an inductive impedance to resonate with the divider capacitors. Ulrich Rohde, N1UL, in Fig 4-47 of his book *Digital PLL Frequency Synthesizers — Theory and Design*, published an elegant alternative method of extracting an output signal from this type of circuit, shown in Fig 9.26B. This taps off a signal from the current in the crystal itself. This can be thought of as using the crystal as a band-pass filter for the oscillator output. The RF choke in the emitter keeps the emitter bias resistor from loading the tank and degrading the Q. In this case (3-MHz operation), it has been chosen to resonate close to 3 MHz with the parallel capacitor (510 pF) as a means of forcing operation on the wanted mode. The 10- Ω resistor and the transformed load impedance will reduce the in-circuit Q of the crystal, so a further development substituted a common base amplifier for the resistor and transformer. This is shown in Fig 9.26C. The common-base amplifier is run at a large quiescent current to give a very low input impedance. Its collector is tuned to give an output with low harmonic content and an emitter follower is used to buffer this from the load. This oscillator sports a simple ALC

system, in which the amplified and rectified signal is used to reduce the bias voltage on the oscillator transistor's base. This circuit is described as achieving a phase noise level of -168 dBc/Hz a few kilohertz out from the carrier. This may seem far beyond what may ever be needed, but frequency multiplication to high frequencies, whether by classic multipliers or by frequency synthesizers, multiplies the deviation of any FM/PM sidebands as well as the carrier frequency. This means that phase noise worsens by 20 dB for each tenfold multiplication of frequency. A clean crystal oscillator and a multiplier chain is still the best way of generating clean microwave signals for use with narrow-band modulation schemes.

It has already been mentioned that overtone crystals are much harder to pull than fundamental ones. This is another way of saying that overtone crystals are less influenced by their surrounding circuit, which is helpful in a frequency-standard oscillator like this one. Even though 5 MHz is in the main range of fundamental-mode crystals and this circuit will work well with them, an overtone crystal has been used. To further help stability, the power dissipated in the crystal is kept to about 50 μ W. The common-base stage is effectively driven from a higher impedance than its own input impedance, under which conditions it gives a very low noise figure.


9.5.5 VXOs

Some crystal oscillators have frequency trimmers. If the trimmer is replaced by a variable capacitor as a front-panel control, we have a *variable crystal oscillator (VXO)*: a crystal-based VFO with a narrow tuning range, but good stability and noise performance. VXOs are often used in small, simple QRP transmitters to tune a few kilohertz

around common calling frequencies. Artful constructors, using optimized circuits and components, have achieved 1000-ppm tuning ranges. Poor-quality “soft” crystals are more pull-able than high-Q ones. Overtone crystals are not suited to VXOs. For frequencies beyond the usual limit for fundamental mode crystals, use a fundamental unit and frequency multipliers.

ICOM and Mizuho made some 2 meter SSB transceivers based on multiplied VXO local oscillators. This system is simple and can yield better performance than many expensive synthesized radios. SSB filters are available at 9 or 10.7 MHz, to yield sufficient image rejection with a single conversion. Choice of VXO frequency depends on whether the LO is to be above or below signal frequency and how much multiplication can be tolerated. Below 8 MHz multiplier filtering is difficult. Above 15 MHz, the tuning range per crystal narrows. A 50-200 kHz range per crystal should work with a modern front-end design feeding a good 9-MHz IF, for a contest quality 2 meter SSB receiver.

The circuit in **Fig 9.27** is a JFET VXO from Wes Hayward, W7ZOI, and Doug DeMaw, W1FB, optimized for wide-range pulling. Published in *Solid State Design for the Radio Amateur*, many have been built and its ability to pull crystals as far as possible has been proven. Ulrich Rohde, N1UL, has shown that the diode arrangement as used here to make signal-dependent negative bias for the gate confers a phase-noise disadvantage, but oscillators like this that pull crystals as far as possible need any available means to stabilize their amplitude and aid start-up. In this case, the noise penalty is worth paying. This circuit can achieve a 2000-ppm tuning range with amenable crystals. If you have some overtone crystals in your junk box whose fundamental

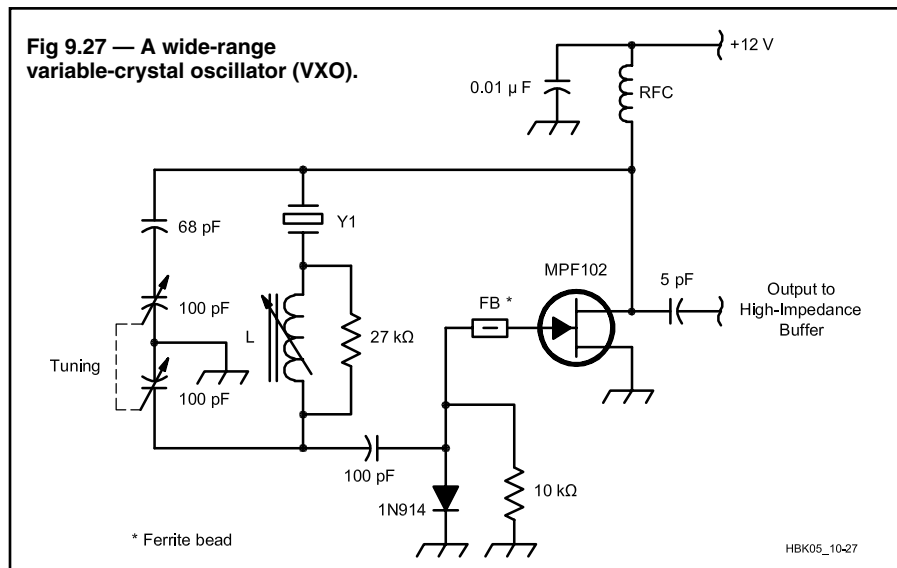

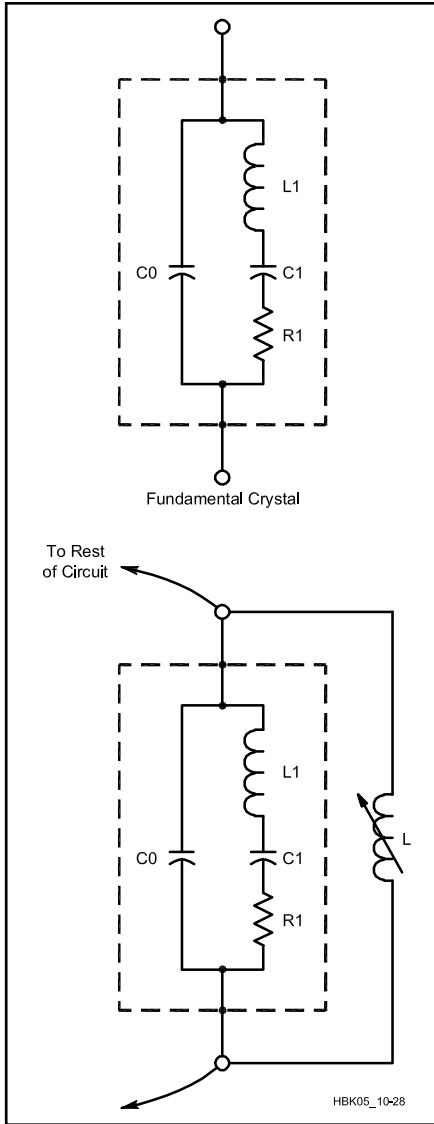


Fig 9.28 — Using an inductor to “tune out” C0 can increase a crystal oscillator’s pulling range.

frequency is close to the wanted value, they are worth trying.

This sort of circuit doesn’t necessarily stop pulling at the extremes of the possible tuning range, sometimes the range is set by the onset of undesirable behavior such as jumping mode or simply stopping oscillating. L was a 16- μ H slug-tuned inductor for 10-MHz operation. It is important to minimize the stray and inter-winding capacitance of L since this dilutes the range of impedance presented to the crystal.

One trick that can be used to aid the pulling range of oscillators is to tune out the C0 of the equivalent circuit with an added inductor. **Fig 9.28** shows how. L is chosen to resonate with C0 for the individual crystal, turning it into a high-impedance parallel-tuned circuit. The Q of this circuit is orders of magnitude less than the Q of the true series resonance of

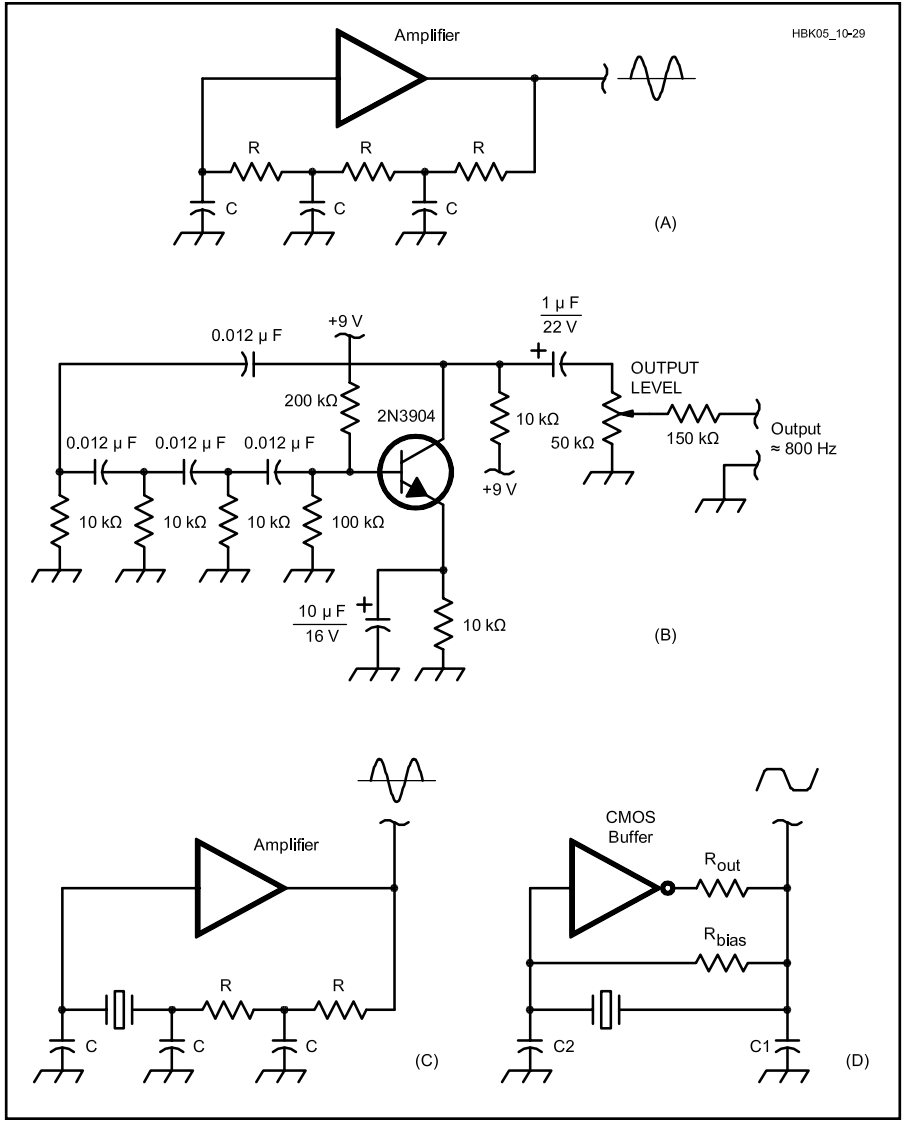


Fig 9.29 — In a phase-shift oscillator (A) based on logic gates, a chain of RC networks — three or more — provide the feedback and phase shift necessary for oscillation, at the cost of low Q and considerable loop loss. Many commercial Amateur Radio transceivers have used a phase-lead oscillator similar to that shown at B as a sidetone generator. Replacing one of the resistors in A with a crystal produces a Pierce oscillator (C), a cut-down version of which (D) has become the most common clock oscillator configuration in digital systems.

the crystal, so its tuning is much broader. The value of C0 is usually just a few picofarads, so L has to be a fairly large value considering the frequency at which it is resonated. This means that L has to have low stray capacitance or else it will self-resonate at a lower frequency. The tolerance on C0 and the variations of the stray C of the inductor means that individual adjustment is needed. This technique can also work wonders in crystal ladder filters.

9.5.6 Logic-Gate Crystal Oscillators

A 180° phase-shift network and an inverting amplifier can be used to make an oscillator. A single stage RC low-pass network

cannot introduce more than 90° of phase shift and only approaches that as the signal becomes infinitely attenuated. Two stages can only approach 180° and then have immense attenuation. It takes three stages to give 180° and not destroy the loop gain. **Fig 9.29A** shows the basic form of the *phase-shift* oscillator; **Fig 9.29B** is an example the phase-shift oscillator commonly used in commercial Amateur Radio transceivers as an audio sidetone oscillator.

The frequency-determining network of an RC oscillator has a Q of less than one, which is a massive disadvantage compared to an LC or crystal resonator. The *Pierce* crystal oscillator is a converted phase-shift oscillator, with the crystal taking the place of one series

resistor, in Fig 9.29C. At the exact series resonance, the crystal looks resistive, so by suitable choice of the capacitor values, the circuit can be made to oscillate.

The crystal has a far steeper phase/frequency relationship than the rest of the network, so the crystal is the dominant controller of the frequency. The Pierce circuit is rarely seen in this full form. Instead, a cut-down version has become the most common circuit for crystal-clock oscillators for digital systems.

Fig 9.29D shows this minimalist Pierce, using a logic inverter as the amplifier. R_{bias} provides dc negative feedback to bias the gate into

its linear region. At first sight it appears that this arrangement should not oscillate, but the crystal is a resonator (not a simple resistor) and oscillation occurs at a frequency offset from the series resonance, where the crystal appears inductive, which makes up the missing phase shift. This is one circuit that *cannot* oscillate exactly on the crystal's series resonance.

This circuit is included in many microprocessors and other digital ICs that need a clock. It is also the usual circuit inside the miniature clock oscillator cans. It is not a very reliable circuit, as operation is dependent on the crystal's equivalent series resistance

and the output impedance of the logic gate, occasionally the logic device or the crystal needs to be changed to start oscillation, sometimes playing with the capacitor values is necessary. It is doubtful whether these circuits are ever designed — values (the two capacitors) seem to be arrived at by experiment. Once going, the circuit is reliable, but its drift and noise are moderate, not good — acceptable for a clock oscillator. The commercial packaged oscillators are the same, but the manufacturers have handled the production foibles on a batch-by-batch basis.

9.6 Oscillators at UHF and Above

9.6.1 UHF Oscillators

A traditional way to make signals at higher frequencies is to make a signal at a lower frequency (where oscillators are easier) and multiply it up to the wanted range. Multipliers are still one of the easiest ways of making a clean UHF/microwave signal. The design of a multiplier depends on whether the multiplication factor is an odd or even number. For odd multiplication, a Class-C biased amplifier can be used to create a series of harmonics; a filter selects the one wanted. For even multiplication factors, a full-wave-rectifier arrangement of distorting devices can be used to create a series of harmonics with strong even-order components, with a filter selecting the wanted component. At higher frequencies, diode-based passive circuits are commonly used. Oscillators using some of the LC circuits already described can be used in the VHF range. At UHF different approaches become necessary.

Fig 9.30 shows a pair of oscillators based on a resonant length of line. The first one is a return to basics: a resonator, an amplifier and a pair of coupling loops. The amplifier can be a single bipolar or FET device or one of the monolithic microwave integrated circuit (MMIC) amplifiers. The second circuit is really a Hartley, and one was made as a test oscillator for the 70 cm band from a 10-cm length of wire suspended 10 mm over an unetched PC board as a ground plane, bent down and soldered at one end, with a trimmer at the other end. The FET was a BF981 dual-gate device used as a source follower.

No free-running oscillator will be stable enough on these bands except for use with wideband FM or video modulation and AFC at the receiver. Oscillators in this range are almost invariably tuned with tuning diodes controlled by phase-locked-loop synthesizers, which are themselves controlled by a crystal oscillator.

There is one extremely common UHF oscillator that is rarely applied intentionally. The answer to this riddle is a configuration

that is sometimes deliberately built as a useful wide-tuning oscillator covering say, 500 MHz to 1 GHz — and is also the modus operandi of a very common form of spurious VHF/UHF oscillation in circuitry intended to process lower-frequency signals! This oscillator has no generally accepted name. It relies on the creation of a small negative resistance in series with a series resonant LC tank. Fig 9.31A shows the circuit in its simplest form.

This circuit is well-suited to construction with printed-circuit inductors. Common FR4 glass-epoxy board is lossy at these frequencies; better performance can be achieved by using the much more expensive glass-Teflon board. If you can get surplus pieces of this type of material, it has many uses at UHF and microwave, but it is difficult to use, as the adhesion between the copper and the substrate can be poor. A high-UHF transistor with a 5-GHz f_T like the BFR90 is suitable; the base inductor can be 30 mm of 1-mm

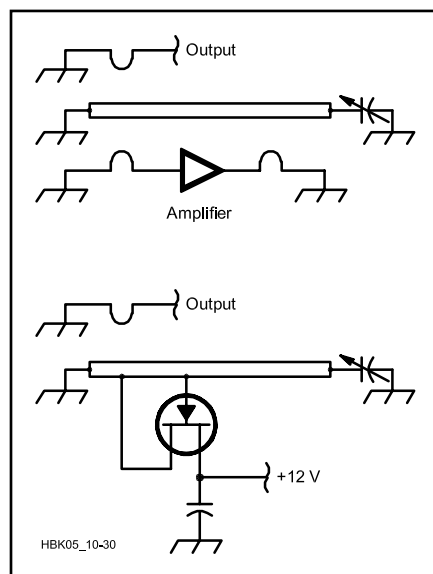


Fig 9.30 — Oscillators that use transmission-line segments as resonators. Such oscillators are more common than many of us may think, as Fig 9.31 reveals.

trace folded into a hairpin shape (inductance, less than 10 nH).

Analyzing this circuit using a comprehensive model of the UHF transistor reveals that the emitter presents an impedance that is small, resistive and negative to the outside world. If this is large enough to more than cancel the effective series resistance of the

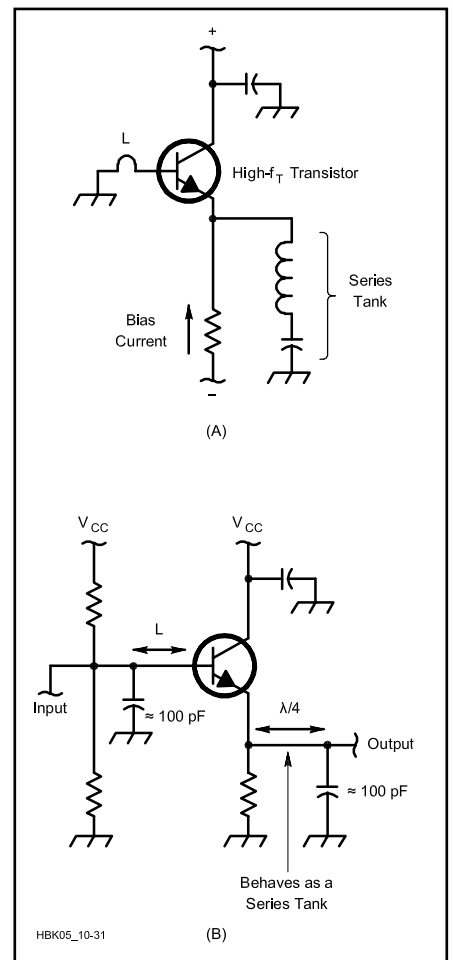


Fig 9.31 — High device gain at UHF and resonances in circuit board traces can result in spurious oscillations even in non-RF equipment.

emitter tank, oscillation will occur.

Fig 9.31B shows a very basic emitter-follower circuit with some capacitance to ground on both the input and output. If the capacitor shunting the input is a distance away from the transistor, the trace can look like an inductor — and small capacitors at audio and low RF can look like very good decouplers at hundreds of MHz. The length to the capacitor shunting the output will behave as a series resonator at a frequency where it is a quarter-wavelength long. This circuit is the same as in Fig 9.31A; it, too, can oscillate. (Parasitic effects are discussed in the **RF Techniques** chapter.)

The semiconductor manufacturers have steadily improved their small-signal transistors to give better gain and bandwidth so that any transistor circuit where all three electrodes find themselves decoupled to ground at UHF may oscillate at several hundred megahertz. The upshot of this is that there is no longer any branch of electronics where RF design and layout techniques can be safely ignored. A circuit must not just be designed to do what it *should* do, it must also be designed so that it cannot do what it *should not* do.

There are three ways of taming such a circuit; adding a small resistor, of perhaps 50 to 100 Ω in the collector lead, close to the transistor, or adding a similar resistor in the base lead, or by fitting a ferrite bead over the base lead under the transistor. The resistors can disturb dc conditions, depending on the circuit and its operating currents. Ferrite beads have the advantage that they can be easily added to existing equipment and have no effect at dc and low frequencies. Beware of some electrically conductive ferrite materials that can short transistor leads. If an HF oscillator uses beads to prevent any risk of spurs (Fig 9.15), the beads should be anchored with a spot of adhesive to prevent movement that can cause small frequency shifts. Ferrite beads of Fair-Rite #43 material are especially suitable for this purpose; they are specified in terms of impedance, not inductance. Ferrites at frequencies above their normal usable range become very lossy and can make a lead look not inductive, but like a few tens of ohms, resistive.

9.6.2 Microwave Oscillators

SOLID-STATE OSCILLATORS

Low-noise microwave signals are still best made by multiplying a very-low-noise HF crystal oscillator, but there are a number of oscillators that work directly at microwave frequencies. Such oscillators can be based on resonant lengths of stripline or microstrip, and are simply scaled-down versions of UHF oscillators, using microwave transistors and printed striplines on a low-loss substrate, like alumina. Techniques for printing metal traces

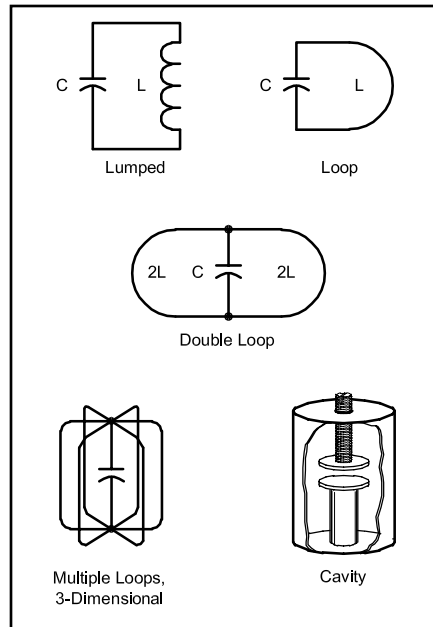


Fig 9.32 — Evolution of the cavity resonator.

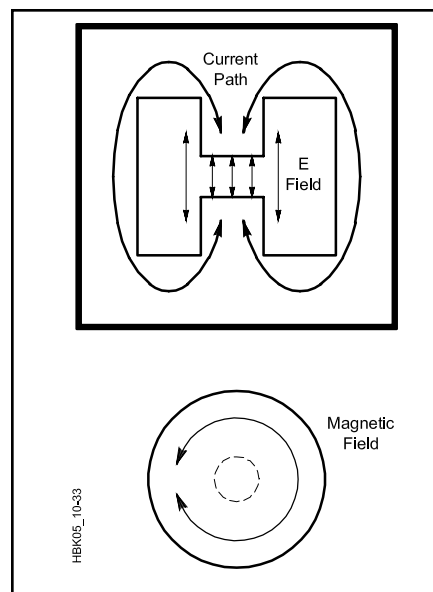


Fig 9.33 — Currents and fields in a cavity.

on substrates to form filters, couplers, matching networks and so on, have been intensively developed over the past two decades. Much of the professional microwave community has moved away from waveguide and now uses low-loss coaxial cable with a solid-copper shield — semi-rigid cable — to connect circuits made flat on ceramic or Teflon based substrates. Semiconductors are often bonded on as unpackaged chips, with their bond-wire connections made directly to the traces on the substrate. At lower microwave frequencies, they may be used in standard surface-mount packages. From an Amateur Radio

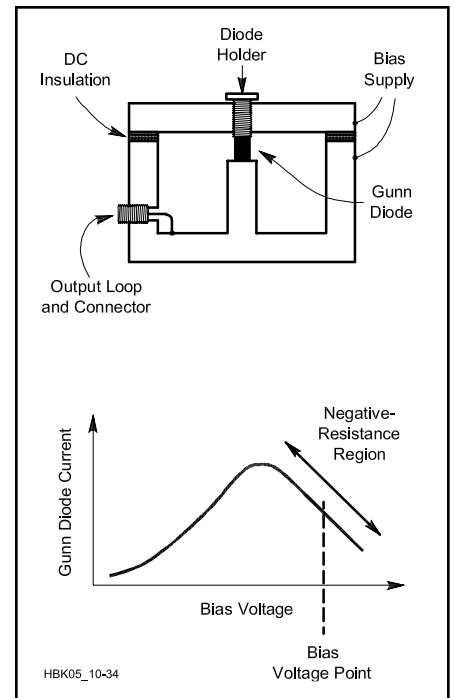


Fig 9.34 — A Gunn diode oscillator uses negative resistance and a cavity resonator to produce radio energy.

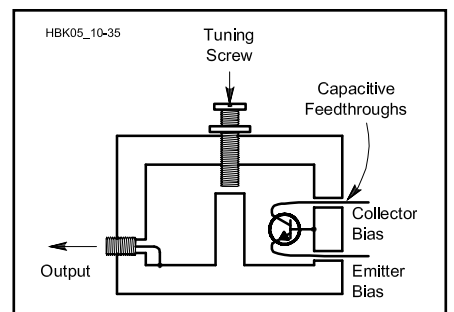


Fig 9.35 — A transistor can also directly excite a cavity resonator.

viewpoint, many of the processes involved are not feasible without access to specialized furnaces and materials. Using ordinary PC-board techniques with surface-mount components allows the construction of circuits up to 4 GHz or so. Above this, structures get smaller and accuracy becomes critical; also PC-board materials quickly become very lossy.

Older than stripline techniques and far more amenable to home construction, cavity-based oscillators can give the highest possible performance. The dielectric constant of the substrate causes stripline structures to be much smaller than they would be in free air, and the lowest-loss substrates tend to have very high dielectric constants. Air is a very low-loss dielectric with a dielectric constant of 1, so it gives high Q and does not force excessive miniaturization. **Fig 9.32** shows

a series of structures used by G. R. Jessop, G6JP, to illustrate the evolution of a cavity from a tank made of lumped components. All cavities have a number of different modes of resonance, the orientation of the currents and fields are shown in **Fig 9.33**. The cavity can take different shapes, but that shown has proven to suppress unwanted modes well. The gap need not be central and is often right at the top. A screw can be fitted through the top, protruding into the gap, to adjust the frequency.

To make an oscillator out of a cavity, an amplifier is needed. Gunn and tunnel diodes have regions in their characteristics where their current *falls* with increasing bias voltage. This is negative resistance. If such a device is mounted in a loop in a cavity and bias applied, the negative resistance can more than cancel the effective loss resistance of the cavity, causing oscillation. These diodes are capable of operating at extremely high frequencies and were discovered long before transistors were developed that had any gain at microwave frequencies.

A *Gunn-diode* cavity oscillator is the basis of many of the Doppler-radar modules used to detect traffic or intruders. **Fig 9.34** shows a common configuration. The coupling loop and coax output connector could be replaced with a simple aperture to couple into waveguide or a mixer cavity. **Fig 9.35** shows a transistor cavity oscillator version using a modern microwave transistor. FET or bipolar devices can be used. The two coupling loops are completed by the capacitance of the feedthroughs.

DIELECTRIC-RESONATOR OSCILLATORS (DRO)

The *dielectric-resonator oscillator (DRO)* may soon become the most common microwave oscillator of all, as it is used in the downconverter of satellite TV receivers. The dielectric resonator itself is a ceramic cylinder, like a miniature hockey puck, several millimeters in diameter. The ceramic has a very high dielectric constant, so the surface (where ceramic meets air in an abrupt mismatch) reflects electromagnetic waves and makes the ceramic body act as a resonant cavity. It is mounted on a substrate and coupled to the active device of the oscillator by a stripline that runs past it. At 10 GHz, a FET made of gallium arsenide (GaAsFET), rather than silicon, is normally used. The dielectric resonator elements are made at frequencies appropriate to mass applications like satellite TV. The set-up charge to manufacture small quantities at special frequencies is likely to be prohibitive for the foreseeable future. The challenge with these devices is to devise new ways of using oscillators on industry standard frequencies. Their chief attraction is their low cost in large quantities and compatibility with

microwave stripline (microstrip) techniques. Frequency stability and Q are competitive with good cavities, but are inferior to that achievable with a crystal oscillator and chain of frequency multipliers. Satellite TV downconverters need free running oscillators with less than 1 MHz of drift at 10 GHz.

YIG OSCILLATORS

The *yttrium-iron garnet (YIG)* oscillator was developed for a wide tuning range as a solid-state replacement for the *backward wave oscillator (BWO)*, a type of vacuum tube oscillator, and many of them can be tuned over more than an octave. They are complete, packaged units that appear to be a heavy block of metal with low-frequency connections for power supplies and tuning, and an SMA connector for the RF output. The manufacturer's label usually states the tuning range and often the power supply voltages. This is very helpful because, with new units priced in the kilo-dollar range, it is important to be able to identify surplus units. The majority of YIGs are in the 2- to 18-GHz region, although units down to 500 MHz and up to 40 GHz are occasionally found. In this part of the spectrum there is no octave-tunable device that can equal their cleanliness and stability. A 3-GHz unit drifting less than 1 kHz per second gives an idea of typical stability. This seems very poor — until we realize that this is 0.33 ppm per second. Nevertheless, any YIG application involving narrow-band modulation will usually require some form of frequency stabilizer.

Good quality, but elderly, RF spectrum analyzers have found their way into the workshops of a number of dedicated constructors. A 0- to 1500-MHz analyzer usually uses a 2- to 3.5-GHz YIG as its first local oscillator, and its tuning circuits are designed around it. A reasonable understanding of YIG oscillators will help in troubleshooting and repair.

YIG spheres are resonant at a frequency controlled not only by their physical dimensions, but also by any applied magnetic field. A YIG sphere is carefully oriented within a coupling loop connected to a negative-resistance device and the whole assembly is placed between the poles of an electromagnet. Negative-resistance diodes have been used, but transistor circuits are now common. The support for the YIG sphere often contains a thermostatically controlled heater to reduce temperature sensitivity.

The first problem with a magnetically tuned oscillator is that magnetic fields, especially at low frequencies, are extremely difficult to shield; the tuning will be influenced by any local fields. Varying fields will cause frequency modulation. The magnetic core must be carefully designed to be all-enclosing in an attempt at self-shielding and then one or more nested mu-metal cans are fitted around everything. It is still important to site the unit

away from obvious sources of magnetic noise, like power transformers. Cooling fans are less obvious sources of fluctuating magnetic fields, since some are 20 dB worse than a well designed 200-W 50/60-Hz transformer.

The second problem is that the oscillator's internal tuning coils need significant current from the power supply to create strong fields. This can be eased by adding a permanent magnet as a fixed "bias" field, but the bias will shift as the magnet ages. The only solution is to have a coil with many turns, hence high inductance, which will require a high supply voltage to permit rapid tuning, thus increasing the power consumption. The usual compromise is to have dual coils: One with many turns allows slow tuning over a wide range; a second with much fewer turns allows fast tuning or FM over a limited range. The main coil can have a sensitivity in the 20 MHz/mA range; and the "FM" coil, perhaps 500 kHz/mA.

The frequency/current relationship can have excellent linearity. **Fig 9.36** shows the construction of a YIG oscillator.

9.6.3 Klystrons, Magnetrons and Traveling Wave Tubes

There are a number of thermionic (vacuum-tube) devices that are used as oscillators or amplifiers at microwave frequencies. Standard vacuum tubes (see the **RF Amplifiers** chapter for an introduction to vacuum tubes) work well for frequencies up to hundreds of megahertz. At frequencies higher than this, the amount of time that it takes for the electrons to move between the cathode and the plate becomes a limiting factor. There are several special tubes designed to work at microwave frequencies, usually providing more power than can be obtained from solid-state devices.

The *klystron* tube uses the principle of velocity modulation of the electrons to avoid transit time limitations. The beam of electrons travels down a metal drift tube that has interaction gaps along its sides. RF voltages are applied to the gaps and the electric fields that they generate accelerate or decelerate the passing electrons. The relative positions of the electrons shift due to their changing velocities causing the electron density of the beam to vary. The modulation of the electron density is used to perform amplification or oscillation. Klystron tubes tend to be relatively large, with lengths ranging from 10 cm to 2 m and weights ranging from as little as 150 g to over 100 kg. Unfortunately, klystrons have relatively narrow bandwidths, and are not re-tunable by amateurs for operation on different frequencies.

The *magnetron* tube is an efficient oscillator for microwave frequencies. Magnetrons are most commonly found in microwave ovens and high-powered radar equipment. The anode

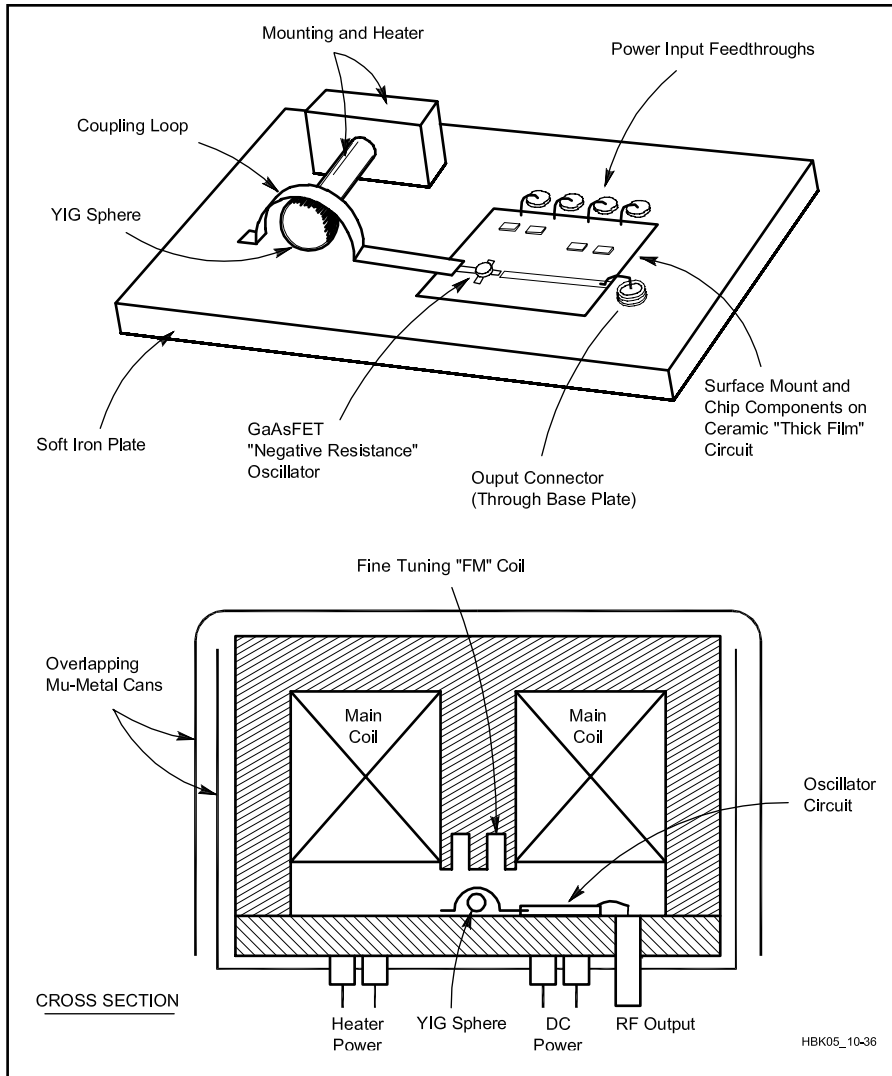


Fig 9.36 — A yttrium-iron-garnet (YIG) sphere serves as the resonator in the sweep oscillators used in many spectrum analyzers.

9.7 Frequency Synthesizers

Like many of our modern technologies, the origins of frequency synthesis can be traced back to WW II. The driving force was the desire for stable, rapidly switchable and accurate frequency control technology to meet the demands of narrow-band, frequency-agile HF communications systems without resorting to large banks of switched crystals. Early synthesizers were cumbersome and expensive, and therefore their use was limited to the most sophisticated communications systems. With the help of the same technologies that have taken computers from “room-sized” to the palms of our hands, the role of frequency synthesis has gone far beyond its original purpose and has become one of the most enabling technologies in modern communications equipment.

Just about every communications device manufactured today, be it a handheld transceiver, cell phone, pager, AM/FM entertain-

ment radio, scanner, television, HF communications equipment, or test equipment contains a synthesizer. Synthesis is the technology that allows an easy interface with both computers and microprocessors. It provides amateurs with many desirable features, such as the feel of an analog knob with 10-Hz frequency increments, accuracy and stability determined by a single precision crystal oscillator, frequency memories, and continuously variable splits. Now reduced in size to only a few small integrated circuits, frequency synthesizers have also replaced the cumbersome chains of frequency multipliers and filters in VHF, UHF and microwave equipment, giving rise to many of the highly portable communications devices we use today. Frequency synthesis has also had a major impact in lowering the cost of modern equipment, as well as reducing manufacturing complexity.

of a magnetron is made up of a number of coupled resonant cavities that surround the cathode. The magnetic field causes the electrons to rotate around the cathode and the energy that they give off as they approach the anode adds to the RF electric field. The RF power is obtained from the anode through a vacuum window. Magnetrons are self-oscillating with the frequency determined by the construction of their anodes; however, they can be tuned by coupling either inductance or capacitance to the resonant anode. The range of frequencies depends on how fast the tuning must be accomplished. The tube may be tuned slowly over a range of approximately 10% of the center frequency. If faster tuning is necessary, such as is required for frequency modulation, the range decreases to about 5%.

A third type of tube capable of operating in the microwave range is the *traveling wave tube* (TWT). For wide-band amplifiers in the microwave range this is the tube of choice. Either permanent magnets or electromagnets are used to focus the beam of electrons that emerges from an electron gun similar to one for a CRT display tube. The electron beam passes through a helical slow-wave structure, in which electrons are accelerated or decelerated, providing density modulation due to the applied RF signal, similar to that in the klystron. The modulated electron beam induces voltages in the helix that provides an amplified tube output whose gain is proportional to the length of the slow-wave structure. After the RF energy is extracted from the electron beam by the helix, the electrons are collected and recycled to the cathode. Traveling wave tubes can often be operated outside their designed frequencies by carefully optimizing the beam voltage.

An Introduction to Phase-Locked Loops

By Jerry DeHaven, WA0ACF

Phase locked loops (PLLs) are used in many applications from tone decoders to stabilizing the pictures in your television set, to demodulating your local FM station or 2-m repeater. They are used for recovering weak signals from deep space satellites and digging out noisy instrumentation signals. Perhaps the most common usage for PLLs in Amateur Radio is to combine the variability of an LC oscillator with the long term stability and accuracy of a crystal oscillator in PLL frequency synthesizers. Strictly speaking a PLL is not necessarily a frequency synthesizer and a frequency synthesizer is not necessarily a PLL, although the terms are used interchangeably.

PLL Block Diagram

The block diagram in Fig 9.A3 shows a basic *control loop*. An example of a control loop is the furnace or air conditioning system in your house or the cruise control in your car. You input a desired output and the control loop causes the system output to change to and remain at that desired output (called a *setpoint*) until you change the setpoint. Control loops are characterized by an input, an output and a feedback mechanism as shown in the simple control loop diagram in Fig 9.A3. The setpoint in this general feedback loop is called the *reference*.

In the case of a heating system in your house, the reference would be the temperature that you set at the thermostat. The feedback element would be the temperature sensor inside the thermostat. The thermostat performs the comparison function as well. The generator would be the furnace which is turned on or off depending on the output of the comparison stage. In general terms, you can see that the reference input is controlling the output of the generator.

Like other control loops, the design of a PLL is based on feedback, comparison and correction as shown in Fig 9.A3. In this section we will focus on the concepts of using a phase locked loop to generate (synthesize) one or more frequencies based on a single reference frequency.

In a typical PLL frequency synthesizer there are six basic functional blocks as shown in Fig 9.A4. The PLL frequency synthesizer block diagram is only slightly more complicated than the simple control loop diagram, so the similarity should be evident. After a brief description of the function of each block we will describe the operational behavior of a PLL frequency synthesizer.

In Fig 9.A4, the general control loop is implemented with a bit more detail.

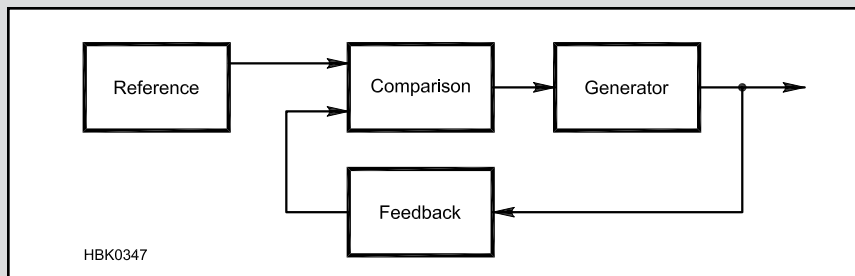


Fig 9.A3 — Simple control loop. The Comparison block creates a control signal for the Generator by comparing the output of the Reference and Feedback blocks.

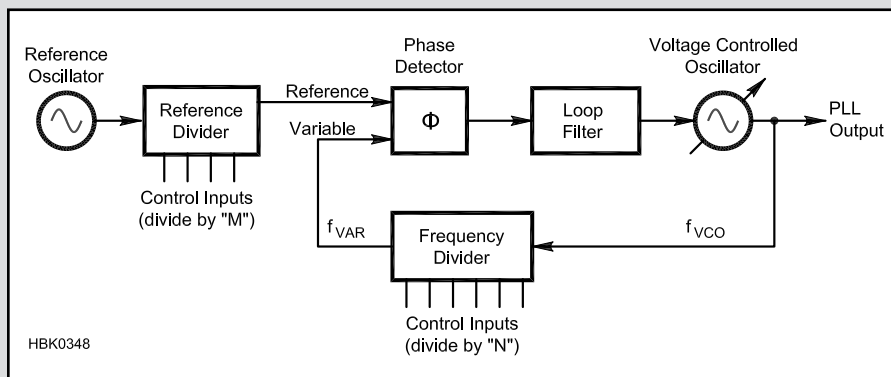


Fig 9.A4 — PLL frequency synthesizer block diagram. The PLL is locked when the frequency PLL Output / N is the same as the Reference Oscillator / M.

The Reference block is composed of the Reference Oscillator and the Reference Divider. The Comparison block consists of the Phase Detector and Loop Filter. The Generator is replaced by the Voltage-Controlled Oscillator (or VCO) and the Feedback block is replaced by the Frequency Divider. The two signals being compared are both frequencies; the reference frequency and variable frequency signals. The output of the Loop Filter is made up of dc and low frequency ac components that act to change the VCO frequency. The output of the PLL is an integer multiple of the reference frequency (the output of the Reference Divider). It is probably not obvious why, but read on to find out!

The Reference Oscillator — The reference oscillator is usually a crystal oscillator with special attention paid to thermal stability and low mechanical and electronic noise. The main function of the reference oscillator is to generate a stable frequency for the PLL. Let us make a distinction between the reference oscillator frequency and the reference frequency. The output of the reference oscillator is at the crystal frequency, say 5.000 MHz. The choice of the actual crystal frequency depends on the PLL design, the availability

of another oscillator in the radio, the avoidance of spurious responses in the receiver, and so on.

The *reference frequency* is the output of the reference (crystal) oscillator divided by the integer M to a relatively low frequency, say 10 kHz. In this case, 10 kHz is the reference frequency. The reference frequency equals the step size between the PLL output frequencies. In this simple example the crystal frequency can be any frequency that is an integer multiple of 10 kHz and within the operating range of the Reference Divider.

The Phase Detector — There are many types of phase detectors but for now let us just consider a basic mixer, or a multiplier. The phase detector has two inputs and one output. In its simplest form, the output of the phase detector is a dc voltage proportional to the phase difference between the two inputs. In practice, a phase detector can be built using a diode double-balanced mixer or an active multiplier.

The output of the mixer consists of products at many frequencies both from multiplication and from nonlinearities. In this application, the desired output is the low frequency and dc terms so all of the RF products are terminated

in a load and the low frequency and dc output is passed to the PLL loop filter.

When the PLL is locked — meaning that the output frequency is the desired multiple of the reference frequency — the phase detector output is a steady dc voltage somewhere between ground and the PLL power supply voltage. When the PLL is commanded to change to another frequency, the phase detector output will be a complex, time-varying signal that gradually settles in on its final value.

The Loop Filter —The loop filter is a low-pass filter that filters the output of the phase detector. The loop filter can be a simple resistor-capacitor (RC) low-pass filter or an active circuit built with bipolar transistors or operational amplifiers. The cutoff frequency of the low pass filter is on the order of 100 Hz to 10 kHz. Although the frequencies involved are dc and low audio frequencies the design of the loop filter is critical for good reference suppression and low noise performance of the PLL frequency synthesizer.

The output of the loop filter is a dc voltage that “steers” the following stage, the Voltage Controlled Oscillator. The dc value can vary over a substantial portion of the PLL power supply. For example, if the loop filter runs off a 9-V power supply you may expect to see the output voltage range from about 2 V to 7 V depending on the VCO frequency range.

The Voltage Controlled Oscillator (VCO)—The VCO is probably the most critical stage in the PLL frequency synthesizer. This stage is the subject of many conflicting design goals. The VCO must be electrically tunable over the desired frequency range with low noise and very good mechanical stability. Ideally, the output frequency of the VCO will be directly proportional to the input control voltage. A key characteristic is the *VCO constant* or *tuning gain*, usually expressed in MHz per volt (MHz/V). The VCO has one input, the dc voltage from the loop filter, and usually two outputs; one for the PLL output, the other driving the feedback stage — the frequency divider.

The Frequency Divider — The VCO frequency divider that acts as the feedback block is a programmable frequency divider or counter. The division ratio N is set either by thumbwheel switches, diode arrays or a microprocessor. The input to the divider is the VCO output frequency. The output of the divider is the VCO output frequency divided by N .

When the PLL is unlocked, such as when the PLL is first turned on, or commanded to change to another frequency, the frequency divider’s output frequency will vary in a nonlinear manner until the PLL locks. Under locked conditions, the divider’s output fre-

quency (VCO Output / N) is the same as the reference frequency (Reference Oscillator / M).

The function of the frequency divider as the feedback element is easier to understand with an example. Let’s assume that the desired PLL output frequency is 14.000 MHz to 14.300 MHz and it should change in steps of 10 kHz (0.010 MHz). A step size of 10 kHz means that the reference frequency must be 10 kHz. There are 31 output frequencies available — one at a time, not simultaneously. (Don’t forget to count 14.000 MHz.) Let us arbitrarily choose the reference oscillator as a 5.000 MHz crystal oscillator. To generate the 10 kHz reference frequency, the reference divider must divide by $M = 500 = 5.000 \text{ MHz} / 0.010 \text{ MHz}$. (Use the same units, don’t divide MHz by kHz.)

To generate a matching 10 kHz signal from the VCO output frequency, the Frequency Divider (the feedback stage), must be programmable to divide by $N = 1400$ to $1430 = 14.000$ to $14.300 \text{ MHz} / 0.010 \text{ MHz}$. The reference divisor ($M = 500$) is fixed, but the Frequency Divider stage needs to be programmable to divide by $N = 1400$ to 1430 in steps of 1. In this way, the output frequency of the PLL is compared and locked to the stable, crystal-generated value of the reference frequency.

PLL Start-up Operation

Let’s visualize the PLL start-up from power on to steady state, visualizing in sequence what each part of the PLL is doing. Some portions of the loop will act quickly, in microseconds; other parts will react more slowly, in tens or hundreds of milliseconds.

The reference oscillator and its dividers will probably start oscillating and stabilize within tens of microseconds. The reference oscillator divider provides the reference frequency to one input of the phase detector.

The VCO will take a bit longer to come up to operation because of extensive power supply filtering with high-value capacitors. The VCO and the programmable dividers will probably reach full output within a few hundred microseconds although the VCO will not yet be oscillating at the correct frequency.

At this point the phase detector has two inputs but they are at different frequencies. The mixer action of the phase detector produces a beat note at its output. The beat note, which could be tens or hundreds of kHz, is low-pass filtered by the PLL loop filter. That low-pass filter action averages the beat note and applies a complicated time-varying ac/dc voltage to the VCO input.

Now the VCO can begin responding to the control voltage applied to its input. An important design consider-

ation is that the filtered VCO control signal must steer the VCO in the correct direction. If the polarity of the control signal is incorrect, it will steer the VCO away from the right frequency and the loop will never lock. Assuming correct design, the control voltage will begin steering the VCO in such a direction that the VCO divider frequency will now get closer to the reference frequency.

With the phase detector inputs a little bit closer in frequency, the beat note will be lower in frequency and the low pass filtered average of the phase detector output will change to a new level. That new control voltage will continue to steer the VCO in the right direction even closer to the “right” frequency. With each successive imaginary trip around the loop you can visualize that eventually a certain value of VCO control voltage will be reached at which the VCO output frequency, when divided by the frequency divider, will produce zero frequency difference at the inputs to the phase detector. In this state, the loop is *locked*. Once running, the range over which a PLL can detect and lock on to a signal is its *capture range*.

PLL Steady-state Operation

When the divided-down VCO frequency matches the reference frequency, the PLL will be in its steady-state condition. Since the comparison stage is a phase detector, not just a frequency mixer, the control signal from the loop filter to the VCO will act in such a way that maintains a constant relationship between the *phase* of the reference frequency and the frequency divider output. For example, the loop might stabilize with a 90° difference between the inputs to the phase detector. As long as the phase difference is constant, the reference frequency and the output of the frequency divider (and by extension, the VCO output) must also be the same.

As the divisor of the frequency divider is changed, the loop’s control action will keep the divided-down VCO output phase locked to the reference frequency, but with a phase difference that gets closer to 0 or 180° , depending on which direction the input frequency changes. The range over which the phase difference at the phase detector’s input varies between 0° and 180° is the widest range over which the PLL can keep the input and VCO signals locked together. This is called the loop’s *lock range*.

If the divisor of the frequency divider is changed even further, the output of the loop filter will actually start to move in the opposite direction and the loop will no longer be able to keep the VCO output locked to the reference frequency and the loop is said to be *out of lock* or *lost lock*.

Loop Bandwidth

Whether you picture a control loop such as the thermostat in your house, the speed control in your car or a PLL frequency synthesizer, they all have “bandwidth,” that is, they can only respond at a certain speed. Your house will take several minutes to heat up or cool down, your car will need a few seconds to respond to a hill if you are using the speed control. Likewise, the PLL will need a finite time to stabilize, several milliseconds or more depending on the design.

This brings up the concept of *loop bandwidth*. The basic idea is that disturbances outside the loop have a low-pass characteristic up to the loop bandwidth, and that disturbances inside the loop have a high-pass characteristic up to the loop bandwidth. The loop bandwidth is determined by the phase detector gain, the loop filter gain and cutoff frequency, the VCO gain and the divider ratio. Loop bandwidth and the phase response of the PLL determine the stability and transient response of the PLL.

PLLs and Noise

Whether the PLL frequency synthesizer output is being used to control a receiver or a transmitter frequency, the spectral cleanliness of the output is important. Since the loop filter output voltage goes directly to the VCO, any noise or spurious frequencies on the loop filter output will modulate the VCO causing FM sidebands. On your transmitted signal, the sidebands are heard as noise by adjacent stations. On receive, they can mix with other signals, resulting in a higher noise floor in the receiver.

A common path for noise to contaminate the loop filter output is via the power supply. This type of noise tends to be audible in your receiver or transmitter audio. Use a well-regulated supply to minimize 120-Hz power supply ripple. Use a dedicated low-power regulator

separate from the receiver audio stages so you do not couple audio variations from the speaker amplifier into the loop filter output. If you have a computer / sound card interface, be careful not to share power supplies or route digital signals near the loop filter or VCO.

A more complicated spectral concern is the amount of reference frequency feed-through to the VCO. This type of spurious output is above the audio range (typically a few kHz) so it may not be heard but it will be noticed, for example, in degraded receiver adjacent channel rejection. In the example above, Fig 9.A4, the reference frequency is 10 kHz. High amounts of reference feed-through on the VCO control input will result in FM sidebands on the VCO output.

Loop filter design and optimization is a complicated subject with many tradeoffs. This subject is covered in detail in the PLL references, but the basic tradeoff is between loop bandwidth (which affects the speed at which a PLL can change frequency and lock) and reference rejection. Improved phase detectors can be used which will minimize the amount of reference feed-through for the loop filter to deal with. Another cause of high reference sidebands is inadequate buffering between the VCO output and the frequency divider stage.

One indication of PLL design difficulty is the spread of the VCO range expressed either in percent or in octaves. It is fairly difficult to make a VCO that can tune over one octave, a two-to-one frequency spread. Typically, the greater the spread of the VCO tuning range, the worse the noise performance gets. The conflicting design requirements can sometimes be conquered by trading off complexity, cost, size, and power consumption.

A common source of noise in the VCO is microphonics. Very small variations in capacitance can frequency

modulate the VCO and impose audible modulation on the VCO output. Those microphonic products will be heard on your transmit audio or they will be superimposed on your receiver audio output. An air-wound inductor used in a VCO can move slightly relative to a shield can under vibration, for example. A common technique to minimize microphonics is to cover the sensitive parts with wax, Q-Dope, epoxy or a silicone sealer. As with the loop filter use a well-filtered, dedicated regulator for the VCO to minimize modulation by conducted electrical noise.

Types of PLLs

One of the disadvantages of a single loop PLL frequency synthesizer is that the reference frequency determines the step size of the output frequency. For two-way radio and other systems with fixed channel spacing that is generally not a problem. For applications like amateur radio CW and SSB operation, tuning steps smaller than 10 Hz is almost a necessity. Like so many design requirements there are trade-offs with making the reference frequency smaller and smaller. Most evident is that the loop filter bandwidth would have to keep getting lower and lower to preserve spectral cleanliness and loop stability. Because low frequency filters take longer to settle, a single-loop PLL with a 10 Hz loop bandwidth would take an unacceptably long time to settle to the next frequency.

Creative circuit architectures came up involving two or more PLLs operating together to achieve finer tuning increments with only moderate complexity. The main portion of this chapter discusses these multi-loop PLL frequency synthesizers. Once you understand the basics of a single loop PLL you will be able to learn and understand the operation of a multi-loop PLL.

the indirect technique and some of the latter developments. There are entire textbooks devoted to treating these various methods in depth, and as such it is not practical to discuss each one in detail in this handbook. We will focus on the indirect approach, based on phase-locked loops. This approach came to dominate frequency synthesis long ago, and is still dominant today.

9.7.1 Phase-Locked Loops (PLL)

To understand the indirect synthesizer, we need to understand the *phase-locked loop* (PLL). The sidebar “An Introduction to Phase-Locked Loops” provides an overview of this

technology. This section presents a detailed discussion of design and performance topics of the PLL and PLL synthesizers and the circuits used to construct them. The digital logic circuits and terms included in this discussion are covered in the **Digital Basics** chapter.

The principle of the phase-locked loop (PLL) synthesizer is very simple. An oscillator can be built to cover the required frequency range, so what is needed is a system to keep it tuned to the desired frequency. This is done by continuously comparing the phase of the oscillator to a stable reference, such as a crystal oscillator and using the result to steer the tuning. If the oscillator frequency is too high, the phase of its output will start to lead that of the reference by an increas-

ing amount. This is detected and is used to decrease the frequency of the oscillator. Too low a frequency causes an increasing phase lag, which is detected and used to increase the frequency of the oscillator. In this way, the oscillator is locked into a fixed-phase relationship with the reference, which means that their frequencies are held exactly equal.

The oscillator is now under control, but is locked to a fixed frequency. **Fig 9.37** shows the next step. The phase detector does not simply compare the oscillator frequency with the reference oscillator; both signals have now been passed through frequency dividers. Advances in digital integrated circuits have made frequency dividers up to microwave frequencies (over 10 GHz) commonplace.

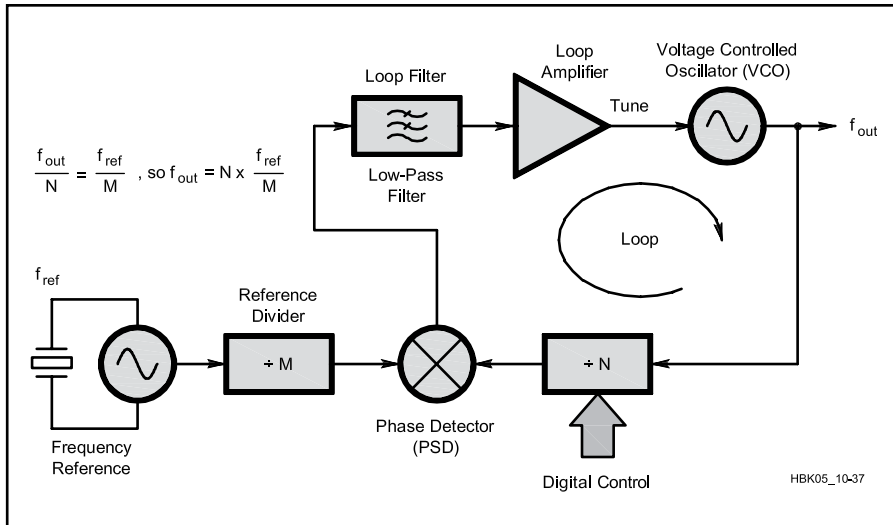


Fig 9.37 — A basic phase-locked-loop (PLL) synthesizer acts to keep the divided-down signal from its voltage-controlled oscillator (VCO) phase-locked to the divided-down signal from its reference oscillator. Fine tuning steps are therefore possible without the complication of direct synthesis.

The divider on the reference path has a fixed division factor, but that in the VCO path is programmable, the factor being entered digitally as a (usually) binary word. The phase detector is now operating at a lower frequency, which is a submultiple of both the reference and output frequencies.

The phase detector, via the loop amplifier, steers the oscillator to keep both its inputs equal in frequency. The reference frequency, F_{ref} , divided by M , is equal to the output frequency divided by N . The output frequency equals the reference frequency $\times N/M$. N is programmable (and an integer), so this synthesizer is capable of tuning in steps of F_{ref}/M .

As an example, to make a 2 meter FM radio covering 144 to 148 MHz with a 10.7-MHz IF, we need a local oscillator covering 154.7 to 158.7 MHz. If the channel spacing is 20 kHz, then F_{ref}/M is 20 kHz, so N is 7735 to 7935. There is a free choice of F_{ref} or M , but division by a round binary number is easiest. Crystals are readily available for 10.24 MHz, and one of these (divided by 512) will give 20 kHz at low cost. ICs are readily available containing most of the circuitry necessary for the reference oscillator (less the crystal), with the programmable divider and the phase detector.

LOOP FREQUENCY RESPONSE

The phase detector in this example compares the relative timing of digital pulses at 20 kHz. Inevitably, the phase detector output will contain strong components at 20 kHz and its harmonics in addition to the desired “steering” signal. The loop filter must reject these unwanted signals; otherwise the loop amplifier will amplify them and apply them to the VCO, generating unwanted FM. No filtering can be perfect and the VCO is very

sensitive, so most synthesizers have measurable sidebands spaced at the phase detector operating frequency (and harmonics) away from the carrier. These are called *reference-frequency sidebands*. (Exactly which is the reference frequency is ambiguous: Do we mean the frequency of the reference oscillator, or the frequency applied to the reference input of the phase detector? You must look carefully at context whenever “reference frequency” is mentioned.)

The loop filter is not usually built as a single block of circuitry, it is often made up of three sub-circuits: Some components directly at the output of the phase detector, a shaped frequency response in the loop amplifier, and more components between the loop amplifier and the VCO.

The PLL is a feedback control loop, although the “signal” around its loop is represented by frequency in some places, by phase in others and by voltage in others. Like any feedback amplifier, there is the risk of instability and oscillations, which can be seen as massive FM on the output and a strong ac signal on the tuning line to the VCO. The loop’s frequency response has to be designed to prevent this by controlling filtering and gain.

The following example illustrates the effect of frequency response on loop action: Imagine that we shift the reference oscillator by 1 Hz. The reference applied to the phase detector would shift $1/M$ Hz, and the loop would respond by shifting the output frequency to produce a matching shift at the other phase detector port, so the output is shifted by N/M Hz.

Imagine now that we apply a very small amount of FM to the reference oscillator. The amount of deviation will be amplified by N/M — but this is only true for low modulating

frequencies. If the modulating frequency is increased, the VCO has to change frequency at a higher rate. As the modulating frequency continues to increase, eventually roll-off of the low-pass loop filter frequency response starts to reduce the gain around the loop, the loop ceases to track the modulation and the deviation at the output falls. This is referred to as the *closed-loop frequency response* or *closed-loop bandwidth*. The design of the loop filtering and the gain around the loop sets the closed-loop performance.

Poorly designed loops can have poor closed-loop responses. For example, the gain can have large peaks above N/M at some reference modulation frequencies, indicating marginal stability and excessively amplifying any noise at those offsets from the carrier.

STEP SIZE TRADEOFFS

In a single-loop synthesizer, there is a trade-off between how small the step size can be versus the performance of the loop. A loop with a very small step size requires the phase detector to operate at a very low frequency, so the loop bandwidth has to be kept very, very low to keep the reference-frequency sidebands low. Also, the reference oscillator usually has much better phase-noise performance than the VCO, and (within the loop bandwidth) the loop acts to oppose the low-frequency components of the VCO phase-noise sidebands. This very useful cleanup activity is lost when loops have to be narrowed in bandwidth to allow narrow steps.

Low-bandwidth loops are slow to respond — they exhibit overly long *settling times* — to the changes in N necessary to change channels. The tradeoffs between step size and loop performance make it difficult to obtain small step sizes from a phase-locked loop.

For a number of reasons, single-loop synthesizers are okay for the 2 meter FM radio discussed earlier: Channel spacing (the step size) in this band is not too small, FM is more tolerant of phase noise than other modes, 2 meter FM is rarely used for weak-signal DXing, and the channelization involved does away with the desirability of simulating fast, smooth, continuous tuning. None of these excuses apply to MF/HF radios, however, and ways to circumvent the problems are needed.

A clue was given earlier, by carefully referring to *single-loop synthesizers*. It’s possible to use *several* PLLs, or for that matter, some of the other mentioned techniques such as DDS, fractional- N , variable- or dual-modulus etc, as components in a larger structure, dividing the frequency of one loop and adding it to the frequency of another that has not been divided. This represents a form of hybrid between the old direct synthesizer and the PLL. A form of PLL containing a mixer in place of the programmable divider can be used to perform the frequency addition.

Let us continue our discussion of phase-locked loop synthesizers by examining the role of each of the component pieces of the system. They are, the VCO, the dividers, prescalers, the phase detector and the loop-compensation amplifier.

VOLTAGE-CONTROLLED OSCILLATORS

Voltage-controlled oscillators are commonly referred to as *VCOs*. (Voltage-tuned oscillator, VTO, more accurately describes the circuitry most commonly used in VCOs, but tradition is tradition! An exception to this is the YIG oscillator, described earlier as sometimes used in UHF and microwave PLLs, which is current-tuned.) In all the oscillators described so far, except for permeability tuning, the frequency is controlled or trimmed by a variable capacitor. These are modified for voltage tuning by using a tuning diode. The oscillator section of this chapter shows the schematic symbol and construction detail of a voltage-controlled or *varactor* (tuning) diode. (see **Fig 9.38**)

The VCO circuit of **Fig 9.39** is representative of a VCO implemented with discrete components. (Most PLL ICs include a VCO with all necessary frequency control elements except the tank circuit inductor.) The circuit is a Colpitts oscillator whose tank capacitance has been replaced by the back-to-back tuning diodes. The control voltage applied through the 10-k Ω resistor is assumed to be decoupled and bypassed by components not shown on the schematic.

When this oscillator is used in a PLL, the PLL adjusts the tuning voltage to completely cancel any drift in the oscillator (provided it does not drift further than it can be tuned) regardless of its cause, so no special care is needed to compensate a PLL VCO for temperature effects. Adjusting the inductor core will not change the frequency; the PLL will adjust the tuning voltage to hold the oscillator on frequency. This adjustment is important, though. It's set so that the tuning voltage neither gets too close to the maximum available, nor too low for acceptable *Q*, as the PLL is tuned across its full range.

In a high-performance, low noise synthesizer, the VCO may be replaced by a bank of switched VCOs, each covering a section of the total range needed, each VCO having better *Q* and lower noise because the lossy diodes constitute only a smaller part of the total tank capacity than they would in a single, full-range oscillator. Another method uses tuning diodes for only part of the tuning range and switches in other capacitors (or inductor taps) to extend the range. The performance of wide-range VCOs can be improved by using a large number of varactors in parallel in a high-C, low-L tank.

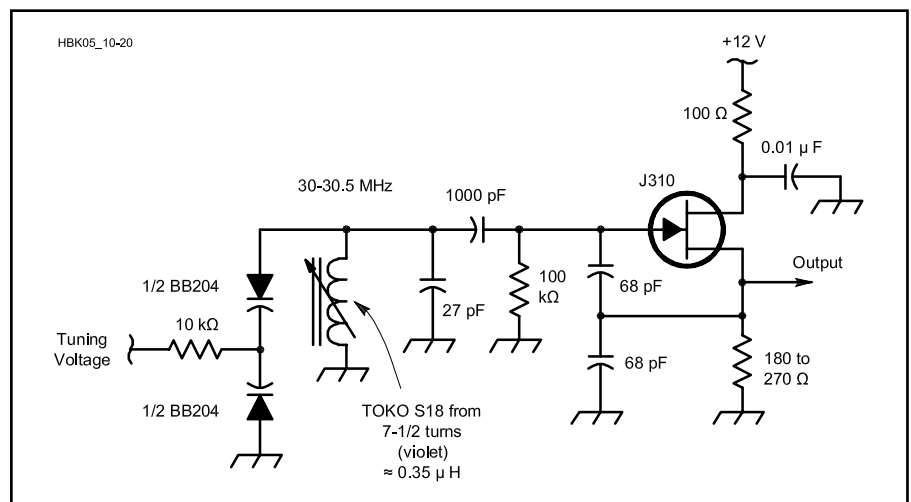
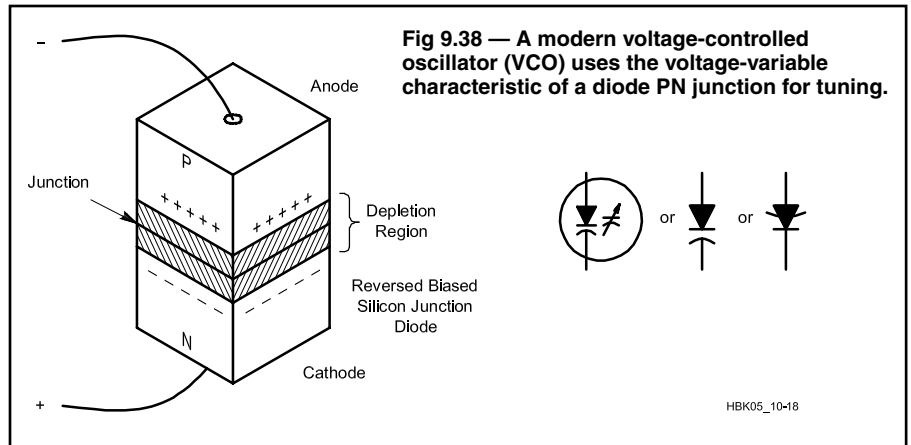


Fig 9.39 — A practical VCO. The tuning diodes are halves of a BB204 dual, common-cathode tuning diode (capacitance per section at 3 V, 39 pF) or equivalent. The ECG617, NTE617 and MV104 are suitable dual-diode substitutes, or use pairs of 1N5451s (39 pF at 4 V) or MV2109s (33 pF at 4 V).

PROGRAMMABLE DIVIDERS

Designing your own programmable divider is now a thing of the past, as complete systems have been made as single ICs for over 10 years. The only remaining reason to do so is when an ultra-low-noise synthesizer is being designed.

It may seem strange to think of a digital counter as a source of random noise, but digital circuits have propagation delays caused by analog effects, such as the charging of stray capacitances. Thermal noise in the components of a digital circuit or signal artifacts coupled from nearby circuitry or the power supply, when added to the signal voltage will slightly change the times at which thresholds are crossed. As a result, the output of a digital circuit will have picked up some timing *jitter*, which is noise in time instead of in amplitude. Jitter in one or both of the signals applied to a phase detector can be viewed as low-level

random phase modulation. Within the loop bandwidth, the phase detector steers the VCO so as to oppose and cancel it, so phase jitter or noise is applied to the VCO in order to cancel out the jitter added by the divider. This makes the VCO noisier.

The maximum frequency of operation of the programmable divider shown as part of **Fig 9.40** is limited by the minimum time needed to reliably detect that the division cycle has completed and then reload the counter. (A programmable divider is a type of counter circuit that outputs one pulse for every pre-programmed number of input pulses. See the **Digital Basics** chapter for more information on counters.) Timing limits are determined by the speed of available logic. Noise performance of the high-speed CMOS logic normally used in programmable dividers is good. For ultra-low-noise dividers, high-speed ECL devices are sometimes used.

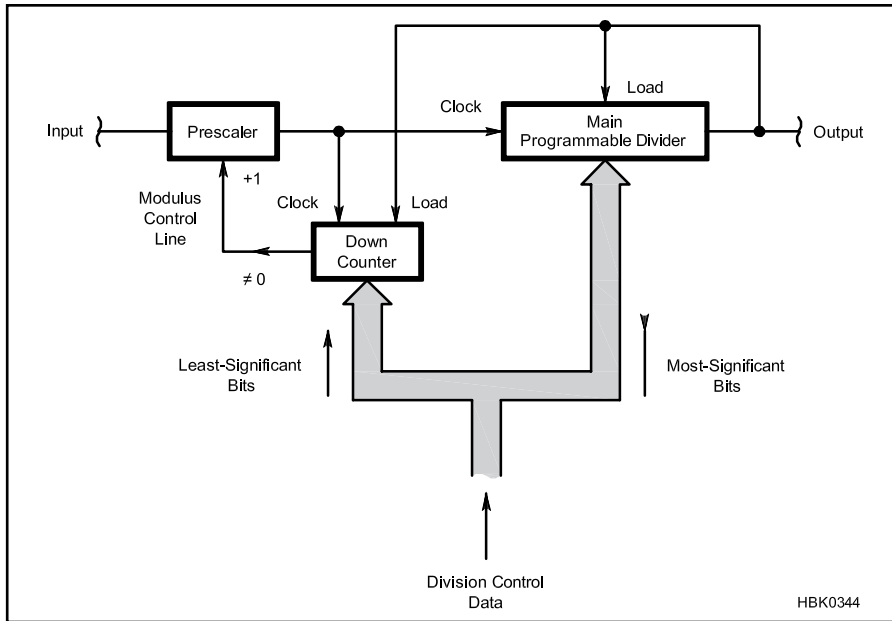


Fig 9.40 — The function of a dual-modulus prescaler. The counter is reloaded with N when the count reaches 0 or 1, depending on the sequencer action.

The synchronous reset cycle forces the entire divider to be made of equally fast logic. Just adding a fast *prescaler* — a fixed-ratio divider ahead of the programmable one — will increase the maximum frequency that can be used, but it also scales up the loop step size. Equal division has to be added to the reference input of the phase detector to restore the step size, reducing the phase detector’s operating frequency. The loop bandwidth has to be reduced to restore the filtering needed to suppress reference frequency sidebands. This makes the loop much slower to change frequency and degrades the noise performance.

VARIABLE OR DUAL-MODULUS PRESCALERS

A plain programmable divider for use at VHF would need to be built from ECL devices. It would be expensive, hot and power-hungry. The idea of a fast front end ahead of a CMOS programmable divider would be perfect if these problems could be circumvented. Consider a fast divide-by-10 prescaler ahead of a programmable divider where division by 947 is required. If the main divider is set to divide by 94, the overall division ratio is 940. The prescaler goes through its cycle 94 times and the main divider goes through its cycle once, for every output pulse. If the prescaler is changed to divide by 11 for 7 of its cycles for every cycle of the entire divider system, the overall division ratio is now $[(7 \times 11) + (87 \times 10)] = 947$. At the cost of a more elaborate prescaler and the addition of a slower programmable counter to control it, this prescaler does not multiply the step size and avoids all the problems of fixed prescaling.

Fig 9.40 shows the general block diagram of a dual-modulus prescaled divider. The down counter controls the modulus of the prescaler. The numerical example, just given, used decimal arithmetic for ease of understanding, although binary is used by the logic itself.

Each cycle of the system begins with the last output pulse having loaded the frequency control word, shown as “Division Control Data” in Fig 9.40, into both the main divider and the prescaler controller. If the division control data’s least significant bits loaded into the prescaler controller are not zero, the prescaler is set to divide by 1 greater than its normal ratio. Each cycle of the prescaler clocks the down counter. Eventually, it reaches zero, and two things happen: The counter is designed to hold (stop counting) at zero (and it will remain held until it is next reloaded) and the prescaler is switched back to its normal ratio until the next reload. One way of visualizing this is to think of the prescaler as just being a divider of its normal ratio, but with the ability to “steal” a number of input pulses controlled by the data loaded into its companion down counter. Note that a dual-modulus prescaler system has a *minimum* division ratio, needed to ensure there are enough cycles of the prescaler to allow enough input pulses to be stolen.

Because the technique is widely used, dual-modulus prescaler ICs are widely used and widely available. Devices for use to a few hundred megahertz are cheap, and devices in the 2.5-GHz region are commonly available. Common prescaler IC division ratio pairs are: 8-9, 10-11, 16-17, 32-33, 64-65 and

so on. Many ICs containing programmable dividers are available in versions with and without built-in prescaler controllers.

PHASE DETECTORS

A *phase detector* (PSD) produces an output voltage that depends on the phase relationship between its two input signals. If two signals, *in phase on exactly the same frequency*, are mixed together in a conventional diode-ring mixer with a dc-coupled output port, one of the products is direct current (0 Hertz). If the phase relationship between the signals changes, the mixer’s dc output voltage changes. With both signals in phase, the output is at its most positive; with the signals 180° out of phase, the output is at its most negative. When the phase difference is 90° (the signals are said to be *in quadrature*), the output is 0 V.

Applying sinusoidal signals to a phase detector causes the detector’s output voltage to vary sinusoidally with phase angle, as in Fig 9.41A. This nonlinearity is not a problem, as the loop is usually arranged to run with phase differences close to 90°. What might seem to be a more serious complication is that the detector’s phase-voltage characteristic repeats every 180°, not 360°. Two possible input phase differences can therefore produce a given output voltage. This turns out not to be a problem, because the two identical voltage points lie on opposing slopes on the detector’s output-voltage curve. One direction of slope gives positive feedback (making the loop unstable and driving the VCO away from what otherwise would be the lock angle) over to the other slope, to the true and stable lock condition.

MD108, SBL-1 and other diode mixers can be used as phase detectors, as can active mixers like the MC1496. Mixer manufacturers make some parts (such as the Mini-Circuits Labs RPD-1) that are specially optimized for phase-detector service. All these devices can make excellent, low-noise phase detectors but are not commonly used in ham equipment. A high-speed sample-and-hold circuit, based on a Schottky-diode bridge, can form a very low-noise phase detector and is sometimes used in specialized instruments. This is just a variant on the basic mixer; it produces a similar result, as shown in Fig 9.41B.

The most commonly used simple phase detector is just a single exclusive-OR (XOR) logic gate. This circuit gives a logic 1 output only when *one* of its inputs is at logic 1; if both inputs are the same, the output is a logic 0. If inputs A and B in Fig 9.41C are almost in phase, the output will be low most of the time, and its average filtered value will be close to the logic 0 level. If A and B are almost in opposite phase, the output will be high most of the time, and its average voltage will be close to logic 1. This circuit is very similar to the mixer. In fact, the internal circuit of ECL XOR gates is the same transistor circuit found

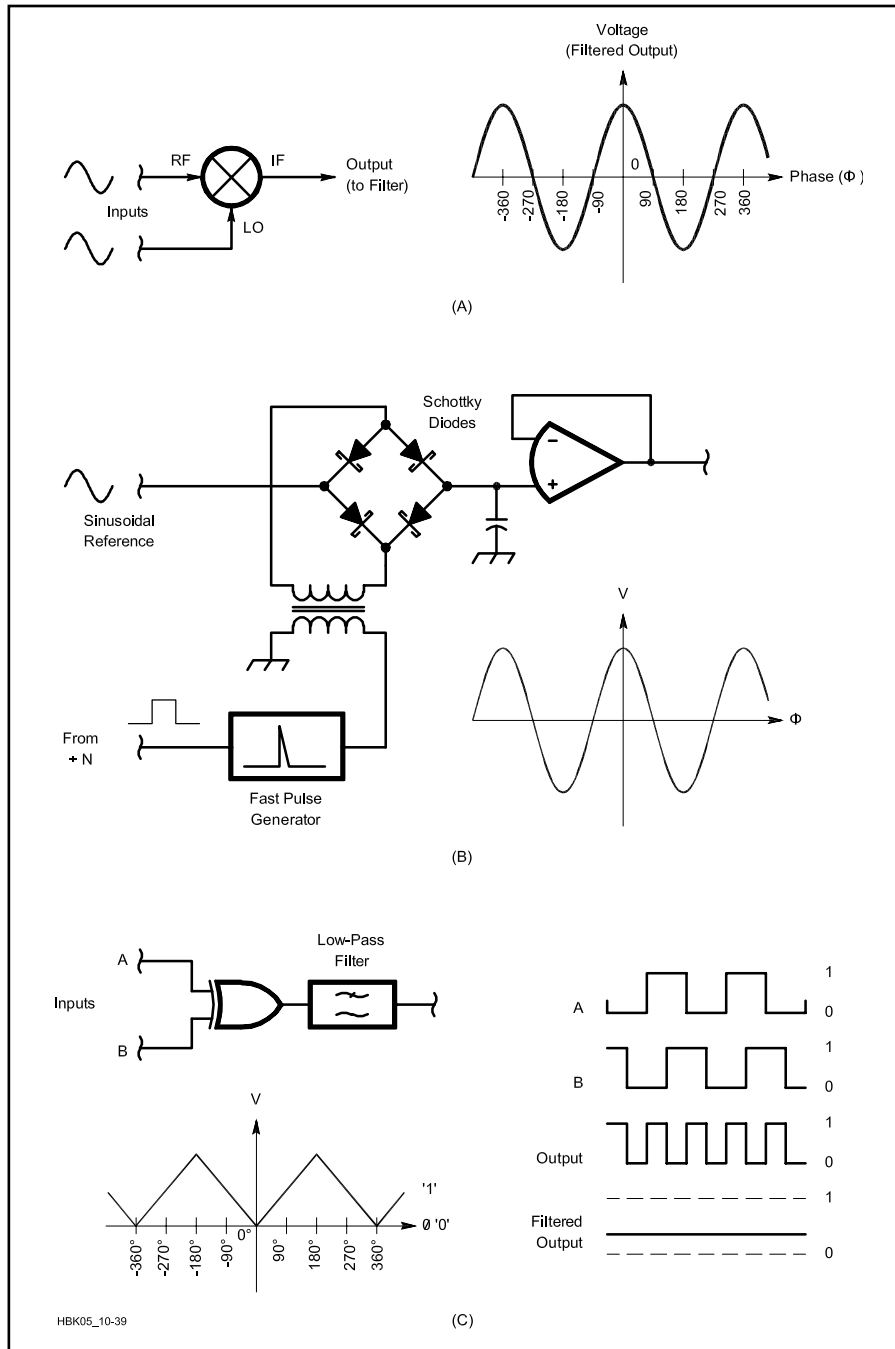


Fig 9.41 — Simple phase detectors: a mixer (A), a sampler (B) and an exclusive-OR gate (C).

in the MC1496 and similar mixers, with some added level shifting. Like the other simple phase detectors, it produces a cyclic output, but because of the square-wave input signals, produces a triangular output signal. To achieve this circuit's full output-voltage range, it's important that the reference and VCO signals applied operate at a 50% duty cycle.

PHASE-FREQUENCY DETECTORS

All the simple phase detectors described so far are really specialized mixers. If the loop is out of lock and the VCO is far off

frequency, such phase detectors give a high-frequency output midway between zero and maximum. This provides no information to steer the VCO towards lock, so the loop remains unlocked. Various solutions to this problem, such as crude relaxation oscillators that start up to sweep the VCO tuning until lock is acquired, or laboriously adjusted "pretune" systems in which a DAC, driven from the divider control data, is used to coarse tune the VCO to within locking range, have been used in the past. Many of these solutions have been superseded, although pretune systems

are still used in synthesizers that must change frequency very rapidly.

The *phase-frequency detector* is the usual solution to lock-acquisition problems. It behaves like a simple phase detector over an extended phase range, but its output remains at maximum or minimum and does not repetitively cycle with larger and larger phase errors. Because its output voltage stays high or low, depending on which input is higher in frequency, this PSD can steer a loop towards lock from anywhere in its tuning range.

Fig 9.42 shows the internal logic of the phase-frequency detector in the CD4046 PLL chip. (The CD4046 also contains an XOR PSD). When the phase of one input leads that of the other, one of the output MOSFETs is pulsed on with a duty cycle proportional to the phase difference. Which MOSFET receives drive depends on which input is leading. If both inputs are in phase, the output will include small pulses due to noise, but their effects on the average output voltage will cancel. If one signal is at a higher frequency than the other, its phase will lead by an increasing amount, and the detector's output will be held close to either V_{DD} or ground, depending on which input signal is higher in frequency. To get a usable voltage output, the MOSFET outputs can be terminated in a high-value resistor to $V_{DD}/2$, but the CD4046's output stage was really designed to drive current pulses into a capacitive load, with pulses of one polarity charging the capacitor and pulses of the other discharging it. The capacitor then integrates the pulses. Simple phase detectors are normally used to lock their inputs in quadrature (90° difference), but phase-frequency detectors are used to lock their input signals in phase (0° difference).

Traditional textbooks and logic-design courses give extensive coverage to avoiding *race conditions*, timing hazards caused by near-simultaneous signals racing through parallel circuit paths to control a single output. Avoiding such situations is important in many circuits because the outcome is strongly dependent on slight differences in gate speed. The phase-frequency detector is the one circuit whose entire function depends on its built-in ability to *make* both its inputs race. Consequently, it's not easy to home-brew a phase-frequency detector from ordinary logic parts. Fortunately, they are available in IC form, usually combined with other functions. The MC4044 is an old stand-alone TTL phase-frequency detector; the MC12040 is an ECL derivative, and the much faster and compatible MCH 12140 can be used to over 600 MHz. The Hittite HMC403S8G can be used to 1.3 GHz. CMOS versions can be found in the CD4046 PLL chip and in almost all current divider-PLL synthesizer chips.

The race-condition hazard does cause one problem in phase-frequency detectors:

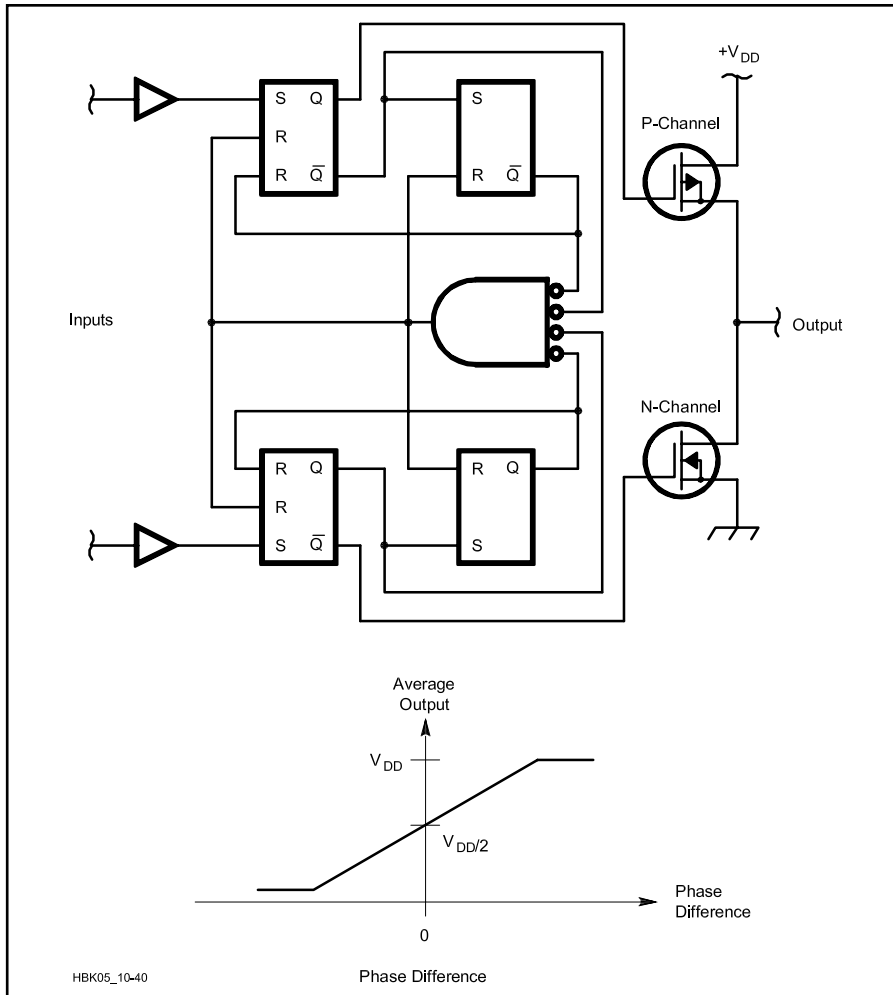


Fig 9.42 — Input signals very far off frequency can confuse a simple phase-detector; a phase-frequency detector solves this problem.

A device's delays and noise, rather than its input signals, control its phase-voltage characteristic in the zero-phase-difference region. This degrades the loop's noise performance and makes its phase-to-voltage coefficient uncertain and variable in a small region, a "dead zone" — unfortunately, in the detector's normal operating range! It's therefore normal to bias operation slightly away from *exact* phase equality to avoid this problem. Fortunately, the newer, faster phase detectors like the MCH 12140 and HMC403S8G tend to minimize this "dead zone" problem.

THE LOOP COMPENSATION AMPLIFIER

Phase-locked loops have acquired a troublesome reputation for a variety of reasons. In the past, a number of commercially made radios have included poorly designed synthesizers that produced excessive noise sidebands, or wouldn't lock reliably. Some un-producible designs have been published for home construction that could not be made to work. Many experimenters have toiled over

an unstable loop, desperately trying anything to get it to lock stably. So the PLL has earned a shady reputation.

Luckily, the proliferation of synthesis techniques and PLLs in contemporary equipment have led to a number of excellent integrated circuits, as well as fine application notes to support them.

The *first* task is to take action to ensure that all previously discussed components of the loop are functioning properly and stably before attempting to close the loop. This means that the oscillators, dividers and amplifiers must all be unconditionally stable. Any instability or "squegging" in these components must be dealt with prior to attempting to close the loop.

The *second* task is to produce a closed-loop characteristic that best suits the application. Herein is where the greatest difficulty frequently lies. The selection of the closed-loop bandwidth and phase margin or peaking is usually one of great compromise and thought. The process frequently begins with an educated approximation that is then

evaluated and modified. There are many factors to consider, including the degree of reference frequency suppression, switching speed, noise, microphonics and modulation, if any. Once the optimum loop characteristic is established, the next problem is to maintain it with respect to variations of the division resulting from the synthesis, and also gain variations associated with the nonlinear tuning curve of the VCO. While not always required in amateur applications, loops in sophisticated synthesizers frequently employ programmable multiplying DACs to maintain constant loop bandwidths and phase margin. In an example later in this chapter, we will actually describe the process for establishing the loop bandwidth for a simple synthesizer.

The *third* task is to design a loop compensation amplifier (loop filter) that will ensure stable operation when the loop is closed. The design of this compensation network or filter requires knowledge of the VCO gain and linearity, the phase-detector gain, and the effective division ratio and its variation in the loop. The foregoing requirements imply the necessity for measurement and calculation to have any reasonable hope of producing a successful outcome.

Note carefully that we are designing a *loop*. Trial and error, intuitive component choice, or "reusing" a loop amplifier design from a different synthesizer may lead to a low probability of success. All oscillators are loops, and any loop will oscillate when certain conditions are met. Look again at the RC phase-shift oscillator from which the "Pierce" crystal oscillator is derived (Fig 9.29A). Our PLL is a loop, containing an amplifier and a number of RC sections. It has all the parts needed to make an oscillator. If a loop is unstable and oscillates, there will be an oscillatory voltage superimposed on the VCO tuning voltage. This will produce massive unwanted FM on the output of the PLL, which is absolutely undesirable.

Before you turn to a less demanding chapter, consider this: It's one of nature's jokes that easy procedures often hide behind a terror-inducing facade. The math you need to design a good PLL may look weird when you see it for the first time and seem to involve some obviously impossible concepts, but it ends in a very simple procedure that allows you to calculate the response and stability of a loop. Professional designers must handle these things daily, and because they like differential equations no more than anyone else does, they use a graphical method based on the work of the mathematician, Laplace, to generate PLL designs. (We'll leave proofs in the textbooks, where they belong! Incidentally, if you can get the math required for PLL design under control, as a free gift you will also be ready to do modern filter synthesis and design beam antennas, since the math

they require is essentially the same.)

The easy solutions to PLL problems can only be performed during the design phase. We must deliberately design loops with sufficient stability safety margins so that all foreseeable variations in component tolerances, from part-to-part, over temperature and across the tuning range, cannot take the loop anywhere near the threshold of oscillation. More than this, it is important to have adequate stability margin because loops with lesser margins will exhibit amplified phase-noise sidebands, and that is another PLL problem that can be designed out.

At the beginning of this chapter (following the text cite of Fig 9.4A), the criterion for stability/oscillation of a loop was mentioned: Barkhausen's for oscillation or Nyquist's for stability. This time Harry Nyquist is our hero.

A PLL is a negative feedback system, with the feedback opposing the input, this opposition or inversion around the loop amounts to a 180° phase shift. This is the frequency-independent phase shift round the loop, but there are also frequency-dependent shifts that will add in. These will inevitably give an increasing, lagging phase with increasing frequency. Eventually an extra 180° phase shift will have occurred, giving a total of 360° around the loop at some frequency. We are in trouble if the gain around the loop has not dropped below unity (0 dB) by this frequency.

Note that we are not concerned only with the loop operating frequency. Consider a 30-MHz low-pass filter passing a 21-MHz signal. Just because there is no signal at 30 MHz, our filter is no less a 30-MHz circuit. Here we use the concept of frequency to describe "what would happen if a signal was applied at that frequency."

The next sections use the graphical concepts of poles and zeros to calculate the gain and phase response around a loop. The graphical concepts are quite useful in that they provide insight into the effect of various component choices on the loop performance. (Poles and zeroes are discussed in the **Analog Basics** chapter.)

Poles and Zeroes in the Loop Amplifier

The loop-amplifier circuit used in the example loop has a blocking capacitor in its feedback path. This means there is no dc feedback. At higher frequencies the reactance of this capacitor falls, increasing the feedback and so reducing the gain. This low-pass filter is an *integrator*. The gain is immense at 0 Hz (dc) and rolls off at 6 dB per octave, pointing to a pole at 0 Hz. This is true whatever the value of the series resistance feeding the signal into the amplifier inverting input and whatever the value of the feedback capacitor. The values of these components scale

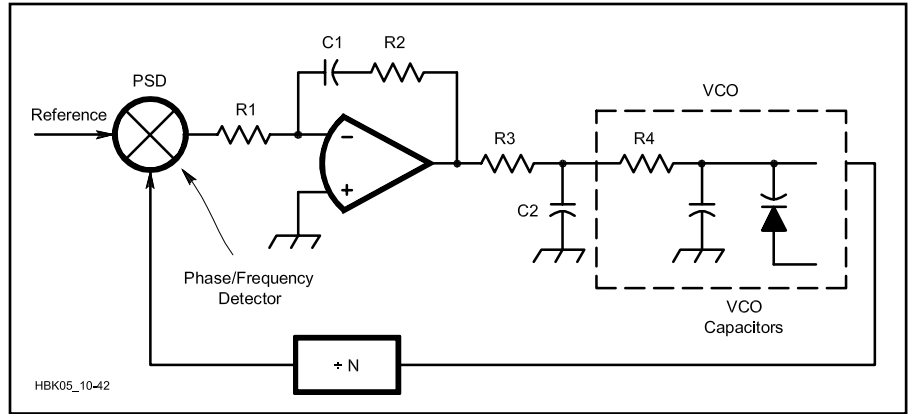


Fig 9.43 — A common loop-amplifier/filter arrangement.

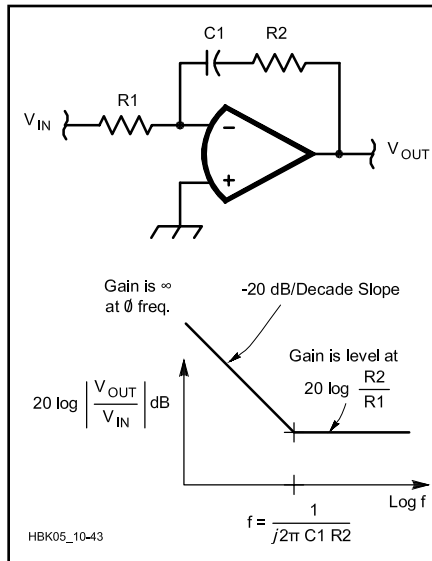


Fig 9.44 — Loop-amplifier detail.

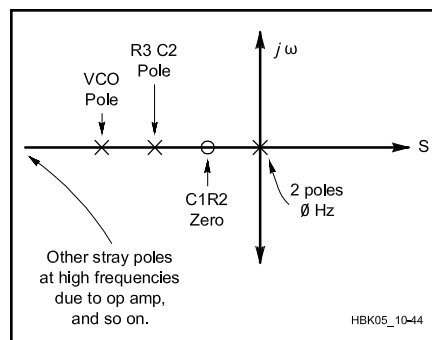


Fig 9.45 — The loop's resulting pole-zero "constellation."

the frequency response of the gain rather than shape it. The roll-off of the integrator gain is fixed at -6 dB per octave, but these components allow us to move it to achieve some wanted gain at some wanted frequency.

At high frequencies, the feedback capacitor in an ordinary integrator will have very

low reactance, giving the circuit very low gain. In our loop amplifier, there is a resistor in series with the capacitor. This limits how low the gain can go, in other words the integrator's downward (with increasing frequency) slope is leveled off. This resistor and capacitor create a zero, and its +6 dB per octave slope cancels the -6 dB per octave slope created by the pole at 0 Hz.

RECIPE FOR A PLL POLE-ZERO DIAGRAM

We can choose a well-tried loop-amplifier circuit and calculate values for its components to make it suit our loop. Fig 9.43 shows a common synthesizer loop arrangement. The op amp operates as an integrator, with R2 added to level off its falling gain. An integrator converts a dc voltage at its input to a ramping voltage at its output. Greater input voltages yield faster ramps. Reversing the input polarity reverses the direction of the ramp.

The system's phase-frequency detector (connected to work in the right sense) steers the integrator to ramp in the direction that tunes the VCO toward lock. As the VCO approaches lock, the phase detector reduces the drive to the integrator, and the ramping output slows and settles on the right voltage to give the exact, locked output frequency. Once lock is achieved, the phase detector outputs short pulses that "nudge" the integrator to keep the divided VCO frequency exactly locked in phase with the reference. Now we'll take a look around the entire loop and find the poles and zeroes of the circuits.

The integrator produces a -20 dB per decade roll off from 0 Hz, so it has a pole at 0 Hz. It also includes R2 to cancel this slope, which is the same as adding a rising slope that exactly offsets the falling one. This implies a zero at $f = 1/(2\pi C1R2)$ Hz, as Fig 9.44 shows. R3 and C2 make another pole at $f = 1/(2\pi C2R3)$ Hz. A VCO usually includes a series resistor that conveys the control voltage to the tuning diode, which also is loaded by various capacitors. This

creates another pole.

The VCO generates frequency, while the phase detector responds to phase. Phase is the integral of frequency, so together they act as another integrator and add another pole at 0 Hz.

What about the frequency divider? The frequency divider's effect on loop response is that of a simple attenuator. Imagine a signal generator that is switched between 10 and 11 MHz on alternate Tuesdays. Imagine that we divide its output by 10. The output of the divider will change between 1 and 1.1 MHz, still on alternate Tuesdays. The divider divides the deviation of the frequency (or phase) modulated signal, but it cannot affect the modulating frequency.

A possible test signal passing around the example loop is in the form of frequency modulation as it passes through the divider, so it is simply attenuated. A divide-by-N circuit will give $20 \log_{10}(N)$ dB of attenuation (reduction of loop gain). This completes the loop. We can plot all this information as shown in Fig 9.45, and the pattern of poles and zeroes is sometimes referred to as a *pole-zero constellation*.

OPEN-LOOP GAIN AND PHASE

Just putting together the characteristics of the blocks around the loop, without allowing for the loop itself, gives us the system's *open-loop* characteristic, which is all we really need.

What Is Stability? — Here “open-loop response” means the gain around the loop that would be experienced by a signal at some frequency *if* such a signal were inserted. We do not insert such signals in the actual circuit, but the concept of frequency-dependent gain is still valid. We need to ensure that there is insufficient gain, at *all* frequencies, to ensure that the loop cannot create a signal and begin oscillating. More than this, we want a good safety margin to allow for component variations and because loops that are *close* to instability perform poorly.

The loop gain and phase are doing interesting things on our plots at frequencies in the AF part of the spectrum. This does not mean that there is visible operation at those frequencies. Imagine a bad, unstable loop. It will have a little too much loop gain at some frequency, and unavoidable noise will build up until a strong signal is created. The amplitude will increase until nonlinearities limit it. An oscilloscope view of the tuning voltage input to the VCO will show a big signal, often in the hertz to tens of kilohertz region, and often large enough to drive the loop amplifier to the limits of its output swing, close to its supply voltages. As this big signal is applied to the tuning voltage input to the VCO, it will modulate the VCO frequency across a wide range. The output will look

Complex Frequency

We are accustomed to thinking of frequency as a real number — so many cycles per second — but frequency can also be a complex number, s , with both a real part, designated by σ , and an imaginary part, designated by $j\omega$. (ω is also equal to $2\pi f$.) The resulting complex frequency is written as $s = \sigma + j\omega$. Complex frequency is used in Laplace transforms, a mathematical technique used for circuit and signal analysis. (Thorough treatments of the application of complex frequency can be found in college-level textbooks on circuit and signal analysis.)

The graphs in Fig 9.44 and 9.45 plot s on a pair of real and imaginary axes. This is also called the *s-plane*. Each pole and zero has a complex frequency that is plotted on the s -plane just as complex numbers are plotted in Cartesian coordinates. The graph of the poles and zeroes is called a *pole-zero map* or *pole-zero diagram*.

When complex frequency is used, a sinusoidal signal is described by Ae^{st} , where A is the amplitude of the signal and t is time. Because s is complex, $Ae^{st} = Ae^{(\sigma+j\omega)t} = A(e^{\sigma t})(e^{j\omega t})$. The two exponential terms describe independent characteristics of the signal. The second term, $e^{j\omega t}$, is the sine wave with which we are familiar and that has frequency f , where $f = \omega/2\pi$. The first term, $e^{\sigma t}$, represents the rate at which the signal increases or decreases. If σ is negative, the exponential term decreases with time and the signal gets smaller and smaller. If σ is positive, the signal gets larger and larger. If $\sigma = 0$, the exponential term equals 1, a constant, and the signal amplitude stays the same.

Complex frequency is very useful in describing a circuit's stability. If the response to an input signal is at a frequency on the right-hand side of the s -plane for which $\sigma > 0$, the system is *unstable* and the output signal will get larger until it is limited by the circuit's power supply or some other mechanism. If the response is on the left-hand side of the s -plane, the system is *stable* and the response to the input signal will eventually die out. The larger the absolute value of σ , the faster the response changes. If the response is precisely on the $j\omega$ axis where $\sigma = 0$, the response will persist indefinitely.

The practical effects of complex frequency can be experienced in a narrow CW crystal or LC filter. The poles of such a filter are just to the left of the $j\omega$ axis, so the input signal causes the filters to “ring”, or output a damped sine wave along with the desired signal. Similarly, the complex frequency of an oscillator's output at power-up must have $\sigma > 0$ or the oscillation would never start! The output amplitude continues to grow until limiting takes place, reducing gain until $\sigma = 1$ for a steady output.

like that of a sweep generator on a spectrum analyzer. What is wrong? How can we fix this loop? Well, the problem may be excessive loop gain, or improper loop time constants. Rather than work directly with the loop time constants, it is far easier to work with the pole and zero frequencies of the loop response. It's just a different view of the same things.

Now imagine a good, stable loop, with an adequate stability safety margin. There will be some activity around the loop: the PSD (phase detector) will demodulate the phase noise of the VCO and feed the demodulated noise through the loop amplifier in such a way as to cancel the phase noise. This is how a good PLL should give *less* phase noise than the VCO alone would suggest. In a good loop, this noise will be such a small voltage that a 'scope will not show it. In fact, connecting test equipment in an attempt to measure it can usually *add* more noise than is normally there.

Finally, imagine a poor loop that is just barely stable. With an inadequate safety margin, the action will be like that of a Q multiplier or a regenerative receiver close to the point of oscillation: There will be an amplified noise peak at some frequency. This spoils the effect of the phase detector trying to combat the VCO phase noise and gives the opposite effect. The output spectrum will show promi-

nent regions of exaggerated phase noise, as the excess noise frequency modulates the VCO.

Now, let's use the pole-zero diagram as a graphic tool to find the system open-loop gain and phase. As we do so, we need to keep in mind that the frequency we have been discussing in designing a loop response is the frequency of a theoretical test signal passing around the loop. In a real PLL, the loop signal exists *in two forms*: Between the output of the phase detector and the input of the VCO it is a sinusoidal voltage, and elsewhere it is a sinusoidal modulation of the VCO frequency. The VCO translates the signal from voltage to frequency.

With our loop's pole-zero diagram in hand, we can pick a frequency at which we want to know the system's open-loop gain and phase. We plot this value on the graph's vertical $j\omega$ axis and draw lines between it and each of the poles and zeros, as shown in Fig 9.46. Next, we measure the lengths of the lines and the “angles of elevation” of the lines. The loop gain is proportional to the product of the lengths of all the lines to zeros *divided by* the product of all the lengths of the lines to the poles. The phase shift around the loop (lagging phase equates to a positive phase shift) is equal to the sum of the pole angles minus the sum of the zero angles. We can

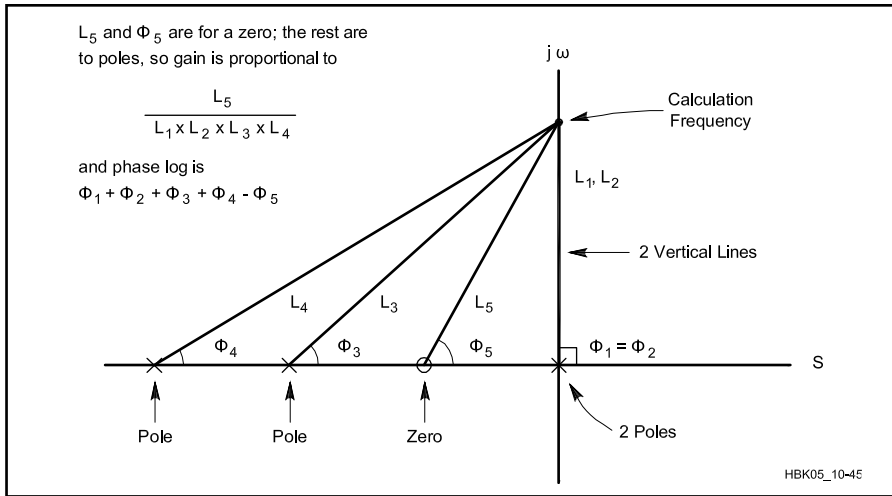


Fig 9.46 — Calculating loop gain and phase characteristics from a pole-zero diagram.

repeat this calculation for a number of different frequencies and draw graphs of the loop gain and phase versus frequency.

All the lines to poles and zeros are hypotenuses of right triangles, so we can use Pythagoras's rule and the tangents of angles to eliminate the need for scale drawings. Much tedious calculation is involved because we need to repeat the whole business for each point on our open-loop response plots. This much tedious calculation is an ideal application for a computer.

The procedure we've followed so far gives only *proportional* changes in loop gain, so we need to calculate the loop gain's *absolute* value at some (chosen to be easy) frequency and then relate everything to this. Let's choose 1 Hz as our reference. (Note that it's usual to express angles in radians, not degrees, in these calculations and that this normally renders frequency in peculiar units of *radians per second*. We can keep frequencies in hertz if we remember to include factors of 2π in the right places. A frequency of 1 Hz = 2π radians/second, because 2π radians = 360° .)

We must then calculate the loop's proportional gain at 1 Hz from the pole-zero diagram, so that the constant of proportion can

be found. For starters, we need a reasonable estimate of the VCO's *voltage-to-frequency gain* — how much it changes frequency per unit change of tuning voltage. As we are primarily interested in stability, we can just take this number as the slope, in Hertz per volt, at the steepest part of voltage-versus-frequency tuning characteristic, which is usually at the low-frequency end of the VCO tuning range. (You can characterize a VCO's voltage-versus-frequency gain by varying the bias on its tuning diode with an adjustable power supply and measuring its tuning characteristic with a voltmeter and frequency counter.)

The loop divide-by-N stage divides our theoretical modulation — the tuning corrections provided through the phase detector, loop amplifier and the VCO tuning diode — by its programmed ratio. The worst case for stability occurs at the divider's lowest N value, where the divider's "attenuation" is least. The divider's voltage-versus-frequency gain is therefore $1/N$, which, in decibels, equates to $-20 \log(N)$.

The change from frequency to phase has a voltage gain of one at the frequency of 1 radian/second, $1/(2\pi)$, which equates to -16 dB, at 1 Hz. The phase detector will have a specified

"gain" in volts per radian. To finish off, we then calculate the gain of the loop amplifier, including its feedback network, at 1 Hz.

There is no need even to draw the pole-zero diagram. Fig 9.47 gives the equations needed to compute the gain and phase of a system with up to four poles and one zero. They can be extended to more singularities and put into a simple computer program. Alternatively, you can type them into your favorite spreadsheet and get printed plots. There are numerous on-line calculators to help, such as those found at www.circuitsage.com/pll.html.

Fig 9.48 shows the sort of gain- and phase-versus-frequency plots obtained from a "recipe" loop design. We want to know where the loop's phase shift equals, or becomes more negative than, -180° . Added to the -180° shift inherent in the loop's feedback (the polarity of which must be negative to ensure that the phase detector drives the VCO toward lock instead of away from it), this will be the point at which the loop itself oscillates — if any loop gain remains at this point. The game is to position the poles and zero, and set the unit frequency gain, so that the loop gain falls to

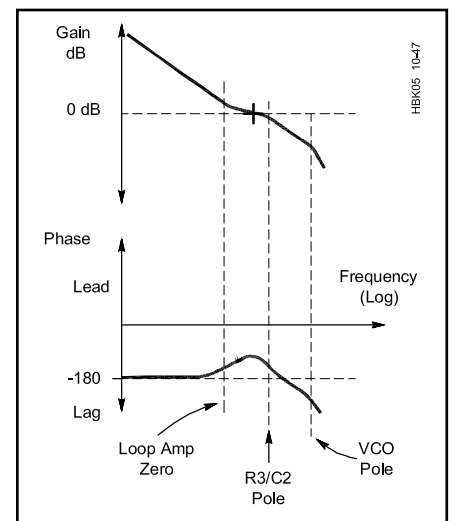


Fig 9.48 — An open-loop gain/phase plot.

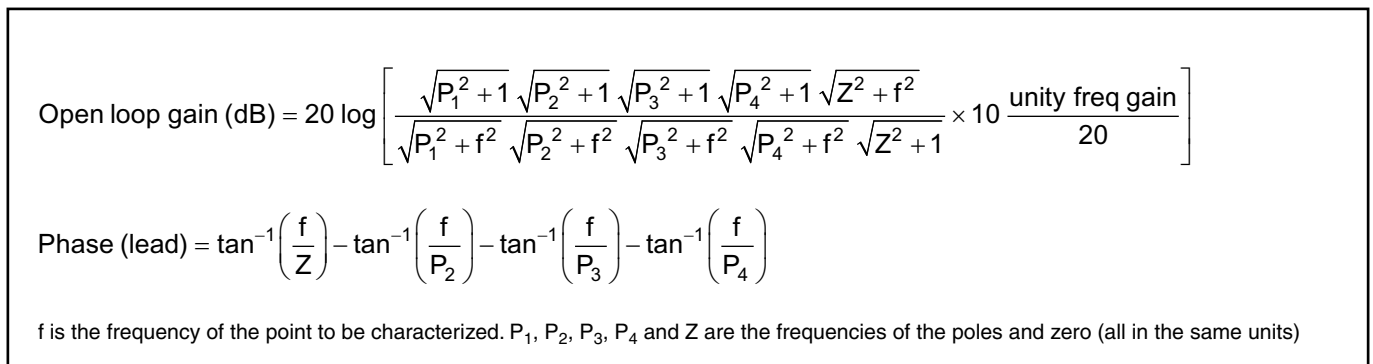


Fig 9.47 — Pole-zero frequency-response equations capable of handling up to four poles and one zero.

below 0 dB before the -180° line is crossed.

At the low-frequency end of the Fig 9.48 plots, the two poles have had their effect, so the gain falls at 40 dB/decade, and the phase remains just infinitesimally on the safe side of -180° . The next influence is the zero, which throttles the gain's fall back to 20 dB/decade and peels the phase line away from the -180° line. The zero would eventually bring the phase back to 90° of lag, but the next pole bends it back before that and returns the gain slope back to a fall of 20 dB/decade. The last pole, that attributable to the VCO, pushes the phase over the -180° line.

It's essential that there not be a pole between the 0-Hz pair and the zero, or else the phase will cross the line early. In this example, the R3-C2 pole and the zero do all the work in setting this critical portion of the loop's response. Their frequency spacing should create a phase bump of 30 to 45° , and their particular frequency positions are constrained as a compromise between sufficient loop bandwidth and sufficient suppression of reference-frequency sidebands. We know the frequency of the loop amplifier zero (that contributed by R1 and C1), so all we need to do now is design the loop amplifier to exhibit a frequency response such that the open-loop gain passes through 0 dB at a frequency close to that of the phase-plot bump.

This loop-design description may have been hard to follow, but a loop amplifier can be designed in under 30 minutes with a little practice. The high output impedance of commonly used CMOS phase detectors favors loop amplifiers based on FET-input op amps and allows the use of high-impedance RC networks (large capacitors can therefore be avoided in their design). LF356 and TL071 op amps have proven successful in loop-amplifier service and have noise characteristics suited to this environment.

To sum up, the recipe gives a proven pole zero pattern (listed in order of increasing frequency):

1. Two poles at 0 Hz (one is the integrator, the other is implicit in all PLLs)
2. A zero controlled by the RC series in the loop amplifier feedback path
3. A simple RC low-pass pole
4. A second RC low-pass pole formed by the resistor driving the capacitive load of the tuning voltage inputs of the VCO

To design a loop: Design the VCO, divider, phase detector and find their coefficients to get the loop gain at unit frequency (1 Hz), then, keeping the poles and zeros in the above order, move them about until you get the same 45° phase bump at a frequency close to your desired bandwidth. Work out how much loop-amplifier unit-frequency gain is needed to shift the gain-frequency-frequency plot so that 0-dB loop gain occurs at the center of the phase bump. Then calculate R and C

values to position the poles and zero and the feedback-RC values to get the required loop amplifier gain at 1 Hz.

Design tips: You can scale the example loop to other frequencies: Just take the reactance values at the zero and pole frequencies and use them to scale the components, you get the nice phase plot bump at a scaled frequency. Even so, you still must do the loop-gain design.

Don't forget to do this for your lowest division factor, as this is usually the least stable condition because there is less attenuation. Also, VCOs are usually most sensitive at the low end of their tuning range.

NOISE IN PHASE-LOCKED LOOPS

Differences in Q usually make the phase-noise sidebands of a loop's reference oscillator much smaller than those of the VCO. Within its loop bandwidth, a PLL acts to correct the phase-noise components of its VCO and impose those of the reference. Dividing the reference oscillator to produce the reference signal applied to the phase detector also divides the deviation of the reference oscillator's phase-noise sidebands, translating to a 20-dB reduction in phase noise per decade of division, a factor of $20 \log(M)$ dB, where M is the reference divisor. Offsetting this, within its loop bandwidth the PLL acts as a *frequency multiplier*, and this multiplies the deviation, again by 20 dB per decade, a factor of $20 \log(N)$ dB, where N is the loop divider's divisor. Overall, the reference sidebands are increased by $20 \log(N/M)$ dB. Noise in the dividers is, in effect, present at the phase detector input, and so is increased by $20 \log(N)$ dB. Similarly, op-amp noise can be calculated into an equivalent phase value at the input to the phase detector, and

this can be increased by $20 \log(N)$ to arrive at the effect it has on the output.

Phase noise can be introduced into a PLL by other means. Any amplifier stages between the VCO and the circuits that follow it (such as the loop divider) will contribute some noise, as will microphonic effects in loop- and reference-filter components (such as those due to the piezoelectric properties of ceramic capacitors and the crystal filters sometimes used for reference-oscillator filtering). Noise on the power supply to the system's active components can modulate the loop. The fundamental and harmonics of the system's ac line supply can be coupled into the VCO directly or by means of ground loops.

Fig 9.49 shows the general shape of the PLL's phase noise output. The dashed curve shows the VCO's noise performance when unlocked; the solid curve shows how much locking the VCO to a cleaner reference improves its noise performance. The two noise "bumps" are a classic characteristic of a phase-locked loop. If the loop is poorly designed and has a low stability margin, the bumps may be exaggerated — a sign of noise amplification due to an overly peaky loop response.

Exaggerated noise bumps can also occur if the loop bandwidth is less than optimum. Increasing the loop bandwidth in such a case would widen the band over which the PLL acts, allowing it to do a better job of purifying the VCO — but this might cause other problems in a loop that's deliberately bandwidth-limited for better suppression of reference-frequency sidebands. Immense loop bandwidth is not desirable, either: Farther away from the carrier, the VCO may be so quiet on its own that widening the loop would make it *worse*.

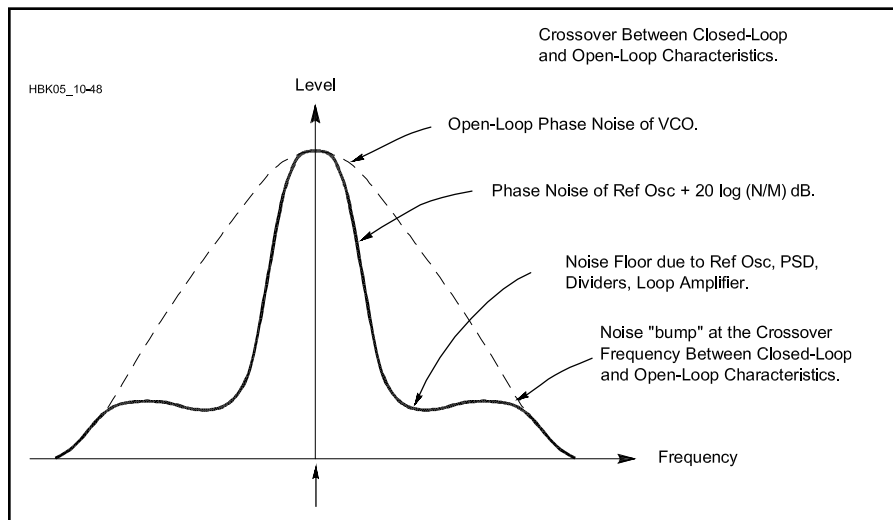


Fig 9.49 — A PLL's open- and closed-loop phase-noise characteristics. The noise bumps at the crossover between open- and closed-loop characteristics are typical of PLLs; the severity of the bumps reflects the quality of the system's design.

9.7.2 A PLL Design Example

In this section, we will explore the application of the design principles previously covered, as well as some of the tradeoffs required in a practical design. We will also cover measurement techniques designed to give the builder confidence that the loop design goals have been met. Finally, we will cover some common troubleshooting problems.

As our design example, a synthesized local oscillator chain for a 10-GHz transverter will be considered. Fig 9.50 is a simplified block diagram of a 10-GHz converter. This example was chosen as it represents a departure from the traditional multi-stage multiply-and-filter approach. It permits realization of the oscillator system with two very simple loops and minimal RF hardware. It is also representative of what is achievable with current hardware, and can fit in a space of 2 to 3 square inches. This example is intended as a vehicle to explore the loop design aspects and is not offered as a “construction project.” The additional detail required would be beyond the scope of this chapter.

In this example, two synthesized frequencies, 10 GHz and 340 MHz, are required. Since 10.368 GHz is one of the popular traffic frequencies, we will mix this with the 10-GHz LO to produce an IF of 368 MHz. The 368-MHz IF signal will be subsequently mixed with a 340-MHz LO to produce a 28-MHz final IF, which can be fed into the 10 meter input of any amateur transceiver. We will focus our attention on the design of the 10-GHz synthesizer only. Once this is done, the same principles may be applied to the 340-MHz section. Our goal is to attempt to design a low-noise LO system (this implies minimum division) with a loop reference oscillator that is an integer multiple of 10 MHz. Using this technique will allow the entire system to be locked at a later time to a 10-MHz standard for precise frequency control.

Ideally, we would like to start with a low-noise 100-MHz crystal reference and a 10-GHz oscillator divided by 100. It is here that we are already confronted with our first practical design tradeoff. We are considering using a line of microwave integrated circuits made by Hittite Microwave. These include a selection of prescalers operating to 12 GHz, a 5-bit counter that will run to 2.2 GHz and a phase/frequency detector that will run up to 1.3 GHz. The 5-bit counter presents the first problem. Our ideal scheme would be to use a divide-by-4 prescaler and enter the 5-bit counter at 2.5 GHz, subsequently dividing by 25 to 100 MHz. The problem is that the 5-bit counter is only rated to 2.2 GHz and not 2.5 GHz. This forces us to use a divide-by-8 prescaler and enter the 5-bit divider at 1.25 GHz. This is well within the range of the

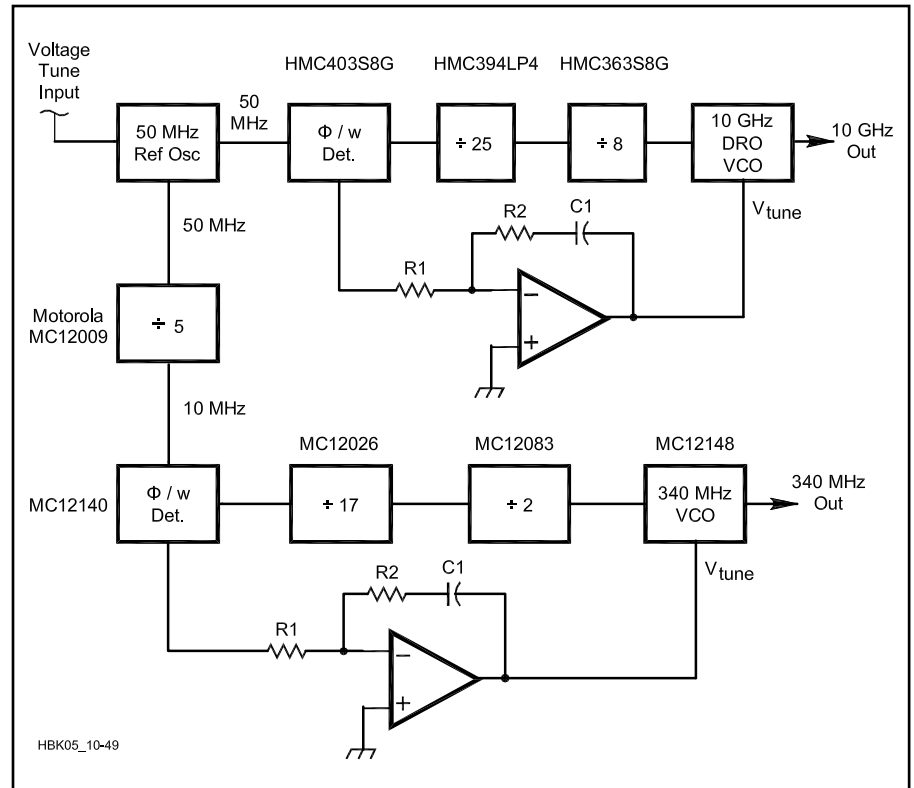


Fig 9.50 — A simplified block diagram of a local oscillator, for a 10-GHz converter.

divider, but we can no longer use an integer division (ie, $1.25 \text{ GHz}/12.5 = 100 \text{ MHz}$) to get to 100 MHz. The next easiest option is to reduce the reference frequency to 50 MHz and to let the 5-bit divider run as a divide-by-25, giving us a total division ratio of 200.

Having already faced our first design tradeoff, a number of additional aspects must be considered to minimize the conflicts in the design:

First, this is a *static* synthesizer — that is, it will not be required to change frequency during operation. As a result, switching time considerations are irrelevant, as are the implications that the switching time would have had on the loop bandwidth. The effects of variable division ratios are also eliminated, as well as any problems associated with non-linear tuning of the VCOs.

Second, the reference frequencies (50 MHz and 10 MHz) are very large with respect to any practically desirable loop bandwidths. This makes the requirement of the loop filter to eliminate reference sidebands quite easy to achieve. In fact, reference sideband suppression will more likely be a function of board layout and shielding effectiveness rather than suppression in the loop filter. This also allows placement of the reference suppression poles far out in the pole zero constellation and well outside the loop bandwidth at about $10 \times \text{BW}_3$ (the 3-dB bandwidth of the loop). This placement of the reference suppression poles

will give us the option of using a “type 2, 2nd-order” loop approximation, which will greatly simplify the calculation process.

Third, based on all of the foregoing tradeoffs, the loop bandwidth can be chosen almost exclusively on the basis of noise performance.

Before we can proceed with the loop calculations we need some additional information: specifically VCO gain, VCO noise performance, divider noise performance, phase detector gain, phase detector noise performance and finally reference noise performance. The phase detector and divider information is available from specification sheets. Now we need to select the 50-MHz reference and the 10-GHz VCO. An excellent choice for a low noise reference is the one described by John Stephensen on page 13 in Nov/Dec 1999 *QEX*. The noise performance of this VCXO is in the order of -160 dBc/Hz at 10-kHz offset at the fundamental frequency. For the 10-GHz VCO, there are many possibilities, including cavity oscillators, YIG oscillators and dielectric resonator oscillators. Always looking for parts that are easily available, useable and economical, salvaging a dielectric resonator from a Ku band LNB (see Jan-Feb 2002 *QEX*, p 3) appears promising. These high-Q oscillators can be fitted with a varactor and tuned over a limited range with good results. The tuning sensitivity of our dielectric resonator VCO is about 10 MHz per volt and

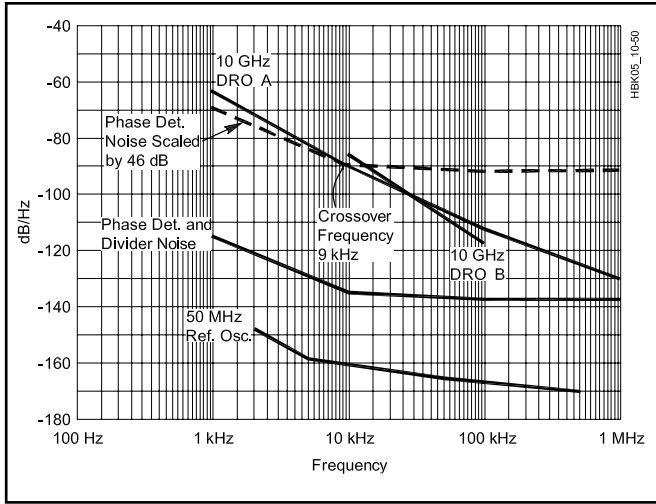


Fig 9.51 — Phase noise plots of the 10-GHz transverter design example.

the phase noise at 10-kHz offset is $-87\text{dBc}/\text{Hz}$. We are now in a position to plot the phase noise of the reference, the dividers, the division effect (46 dB) and the VCO. The phase noise plots are shown in **Fig 9.51**. The noise of the reference is uniformly about 25 dB below the divider and phase detector noise floor. This means that the noise of the phase detector and dividers will be the dominant contribution within the loop bandwidth. The cross-over point is at approximately 9 kHz. At frequencies lower than 9 kHz, the loop will reduce the noise of the VCO (eg, at 1 kHz the reduction will be about 20 dB). At frequencies above 9 kHz, the natural noise roll off of the VCO will dominate. At this point, we can also see the effect of having chosen a reference frequency of 50 MHz. Had we been able to use a 100-MHz reference instead of 50 MHz and reduce the division factor from 200 to 100, we could have put the loop bandwidth at about 30 kHz and picked up an additional 6-dB improvement in close-in noise performance. Nevertheless, even with the 6-dB penalty, this will be quite a respectable 9-GHz LO. It should be apparent that a fair amount of thought and effort was required to be able to determine an applicable bandwidth for this loop.

Now that we have some estimate of the noise performance and the required loop bandwidth, it is time to design the loop. The second consideration cited above enabling the application of the “type-2, 2nd order” approximation is now going to pay off. The math for this loop is really quite simple. There are two main variables, the *natural frequency* of the loop, ω_n , in radians/second, and the *damping factor*, ζ , which is dimensionless.

The closed-loop bandwidth of the loop is a function of ω_n and ζ . **Fig 9.52** shows loop

response as a function of ω_n and ζ . Values of ζ less than 0.5 (“underdamped”) are not desirable, as they tend towards instability and poor phase margin. A value for ζ of 0.707 is referred to as “critically damped” and is favored in applications where settling time is critical (see Gardner). For our application, we will choose a ζ of 1.0. This will give acceptable phase margin and further simplify the math. For a ζ of 1, $\omega_n = (6.28 \times \text{BW}_3) / 2.48$. Substituting the 9-kHz loop bandwidth for BW_3 yields 22790 radians per second for ω_n . Our loop filter will take the basic form shown in Fig 9.44. We can compute values for R1, R2 and C1 as follows.

$$R1 = \frac{K_{PD} \times K_{VCO}}{N \times \omega_n^2 \times C1} \quad (4)$$

where

K_{PD} is the phase detector gain, 1/6.28 V/radian in this case,

K_{VCO} is the VCO gain in radians/Hz, 6.28×10^7 radians/V in this case,

N is the division factor, 200 in this case, and

C1 is the feedback capacitor value in farads.

To proceed, we need to start with an estimate for C1. Practically speaking, since odd values of capacitors are more difficult to obtain, let us try a value for C1 of 0.01 μF .

$$R2 = \frac{2 \times \zeta}{\omega_n^2 \times C1} \quad (5)$$

R1 computes as 9626 Ω and R2 is 8775 Ω . Since we will be using a phase/frequency detector with differential outputs, we will have to modify the circuit of Fig 9.44 to become a differential amplifier. We will also add a passive input filter to keep the inputs

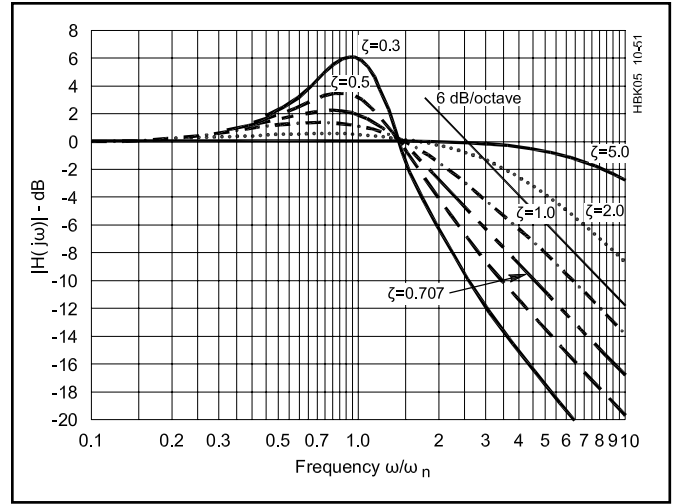


Fig 9.52 — Closed-loop frequency response of a second-order loop as a function of the loop’s natural frequency (ω_n) and damping factor (ζ). (Based on Gardner, *Phase-lock Techniques*. See references.)

of the op amp from being stressed by the very fast and short pulses emanating from the phase/frequency detector. We will also add a passive “hash filter” at the output of the op amp to limit the amount of out of band noise delivered to the VCO tuning port. Both of these filters will be designed for a cutoff frequency of 90 kHz (i.e. 10 times the 9-kHz closed-loop bandwidth, as cited above in the second consideration. Both of these filters will also aid in the rejection of reference frequency sidebands. For the input filter, we simply divide the input resistor in half and add a capacitor to ground. The value of this capacitor is determined as follows:

$$C2 = \frac{4}{62.8 \times \text{BW}_3 \times R1} = 735 \text{ pF} \quad (6)$$

Using 680 or 750 pF will be adequate. The output filter is also quite simple, with one minor stipulation. Op amps can exhibit stability problems when driving a capacitive load through too low a resistance. One very safe way around this is not to use a value for R3 lower than the recommended minimum impedance for full output of the amplifier. For many amplifiers, this value is around 600 Ω . For the output filter, we compute C3 as follows, for R3 = 600 Ω :

$$C3 = \frac{1}{62.8 \times \text{BW}_3 \times R3} = 2950 \text{ pF} \quad (7)$$

Using 3000 pF will be adequate. This completes the computations for the loop compensation amplifier. The complete amplifier is shown in **Fig 9.53**.

9.7.3 PLL Measurements

One of the first things we need to measure

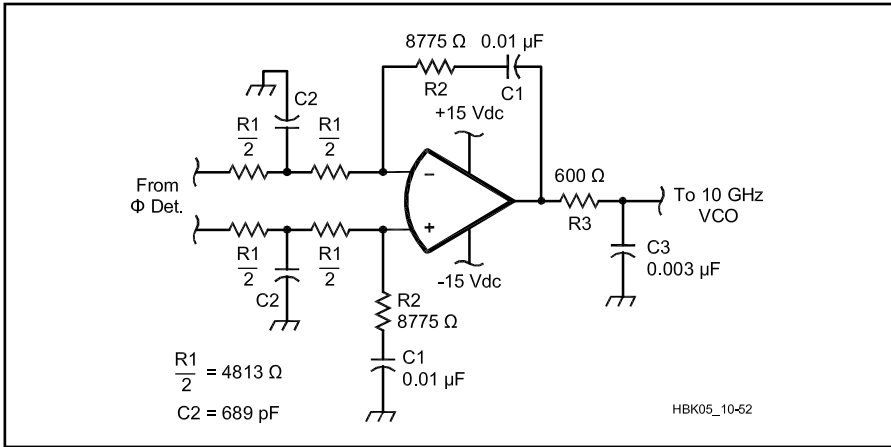


Fig 9.53 — A complete loop-compensation amplifier for the design example 10-GHz transverter.

when designing a PLL is the VCO gain. The tools we will need include a voltmeter, some kind of frequency measuring device like a receiver or frequency counter and a clean source of variable dc voltage. The setup in **Fig 9.54** containing one or more 9-V batteries and a 10-turn, 10-kΩ pot will do nicely. One simply varies the voltage some amount and then records the associated frequency change of the VCO. The gain of the VCO is then the change in f divided by the change in voltage (Hz/V). The phase detector gain constant can usually be found on the specification sheets of the components selected.

Measuring closed-loop bandwidth is slightly more complicated. The way it is commonly done in the laboratory is to replace the reference oscillator with a DCFM-able (ie, a signal generator whose FM port is dc coupled) signal generator and then feed the tracking generator output of a low-frequency spectrum analyzer into the DCFM-able generator while observing the spectrum of the tuning voltage on the spectrum analyzer (see **Fig 9.55**). While this approach is quite straightforward, few amateurs have access to or can afford the test equipment to do this. Today however, thanks to the PC sound card-based spectrum analyzer and tracking generator programs, amateurs can measure the closed-loop response of loops that are less than 20 kHz in bandwidth for significantly less than a king's ransom in test equipment! Here's how:

One approach is to build the reference oscillator with some "built-in test equipment" (BITE) already in the design. This BITE takes the form of some means of DC-FMing the reference oscillator. This is one of the things that makes John Stephenson's oscillator (previously mentioned) attractive. The oscillator includes a varactor input for the purpose of phase locking it to a high-stability low-frequency standard oscillator. This same varactor tuning input takes the place of the

mentioned DCFM-able signal generator.

Now all we need to complete our test setup is some batteries. First, we need to make sure the input of our sound card is ac-coupled (when connected to the VCO tuning port, there will be a dc component present and the sound card may not like this) and that the ac coupling is flat down to at least 10% of the natural frequency of the loop. If the sound card is not ac-coupled, a capacitor will be needed at the input to block the dc on the tuning voltage.

The next step is to determine the tuning sensitivity of the reference oscillator. This is done in the same manner as was done for the VCO described above. Once this has been established, we will set the audio oscillator for an output voltage that will produce between 100 Hz and 1 kHz of deviation. We will also need to establish that the output of

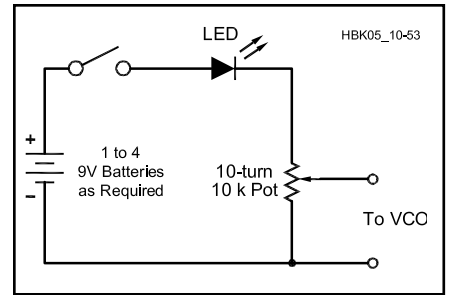


Fig 9.54 — Clean, variable dc voltage source used to measure VCO gain in a PLL design.

the sound card is dc-coupled so that we can place a small battery in series with the audio generator and the tuning port of the reference oscillator. We can provide a dc return on the output by putting a resistive 10-dB attenuator of the appropriate impedance on the output of the sound card and passing the varactor bias through the attenuator to ground. This is required to bias the varactors and also assure that the audio voltage will not drive the varactors into conduction. We can now connect the ac-coupled input of the sound card to the VCO tuning voltage and turn on the loop.

Do not be surprised to see signal components at multiples of the power line frequency, as well as the signal from the audio oscillator. The presence of line frequency components is an indication that the loop is doing its job and removing these components from the spectrum of the VCO. We can now "sweep" the audio oscillator and, by plotting the amplitude of the audio oscillator's response, determine the closed-loop bandwidth of the PLL. In the case of the loop described above, ($\omega_n = 22790$, $\zeta = 1.0$) we should expect to see

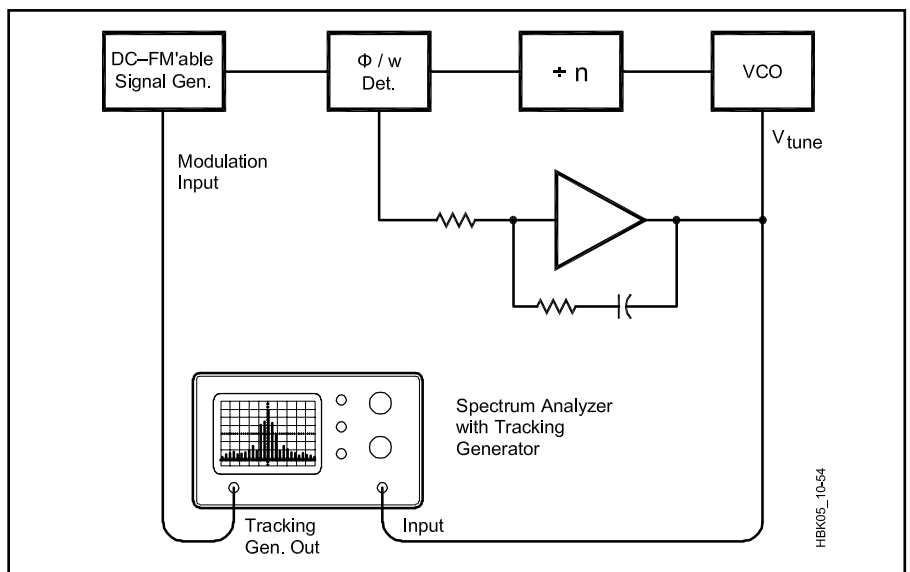


Fig 9.55 — Common laboratory setup for measuring the closed-loop bandwidth of loops.

slightly over 1 dB of peaking at $0.7 \omega_n$ and the 3-dB down point should fall at $2.5 \omega_n$. In any event, if the peaking exceeds 3 dB, the loop phase margin is growing dangerously small and steps should be taken to improve it.

9.7.4 Common Problems in PLL Design

Here are some frequently encountered problems in PLL designs:

- The outputs of the phase detector are inverted. This results in the loop going to one or the other rail. The loop cannot possibly lock in this condition. Solution: Swap the phase detector outputs.

- The loop cannot comply with the tuning voltage requirements of the VCO. If the loop runs out of tuning voltage before the required voltage for a lock is reached, the locked condition is not possible. Solution: Re-center the VCO at a lower tuning voltage or increase the rail voltages on the op amp.

- The loop is very noisy and the tuning voltage is very low. The tuning voltage on the varactor diodes should not drop below the RF voltage swing in the oscillator tank circuit. Solution: Adjust the VCO so that the loop locks with a higher tuning voltage.

9.7.5 Synthesizer ICs

In the earlier section of this chapter on oscillators and synthesizers, we have explored oscillators and how they work along with modern simulation techniques. In the synthesis section, we have covered the basics of the PLL and its components and how to compute a proper loop. The subject of loop measurements and trouble shooting has also been covered. Some of the more common but traditional architectures have also been examined.

The following section is not intended to be project oriented, but rather is designed to expose the reader to additional concepts that are too complex to be fully explored here. The reader, being made aware of these ideas, may wish to examine them in detail using references at the end of this chapter.

In this section, we will explore several areas:

- Using commercially available synthesizer chips
- Improving VCO performance
- The microprocessor in a house keeping function
- The role of DDS in more recent hybrid architectures
- Multi-phase division

There have been many synthesizer chips introduced in recent years for cellular and WiFi applications. One might reasonably ask if any of these devices are well suited to amateur applications. The chips conform to a fairly strict applications profile. They are

designed for minimum power consumption at battery potentials of 3 to 5 V. Applications using these chips strive for a minimum of external components and a maximum of on-chip components. The communication environment is typically one of sending a few tens of megabits for distances of less than 3 miles (5 km). Some are even designated as “low noise” with respect to other chips of their ilk, but not really with respect to most amateur radio requirements.

What this means is that these devices are not the type of synthesizer that one would directly use in amateur applications. For many reasons, the phase noise while adequate for their intended application, is not good enough for many HF, VHF and UHF applications without additional measures being taken. Despite all this, they do have some interesting properties and capabilities that can be exploited with additional components. Some properties that can be exploited are programmable charge pump current, a rich set of division options for creating multiple-loop synthesizers and typically low power consumption.

One of the easiest ways to improve the overall performance is to follow one of these chips with additional division. Consider the following example. One of these chips could be used as a 500 to 550 MHz synthesizer, followed with two cascaded decade dividers for a total division of 100. This division would reduce the phase noise profile by 40 dB making a reasonable quiet synthesizer for the 5 to 5.5 MHz range. The step size would also be reduced by a factor of 100 making the spacing required in the 500 to 550 MHz range equal to 1 kHz for a step size of 10 Hz at 5 MHz. This would make a good local oscillator for a simple traditional radio that covers 80 and 20 meters using both mixer products against a 9 MHz SSB generator.

There are also other techniques that can prove helpful. Decoupling the VCO from the chip will permit one to avoid much of the “on chip” noise that VCOs are susceptible to at the expense of some more complexity. If the VCO is implemented externally, there is an opportunity to design it with increased operating Q and thereby improving the overall phase noise performance. An external VCO also opens other opportunities.

As mentioned earlier, these chips are designed for operation at 3 to 5 V V_{CC} , typically using an internal charge pump to generate the operating voltage. This limits the tuning voltage swing to V_{CC} . One must be able to fit the entire tuning range voltage and the ac voltage excursion in the VCO tank circuit within the V_{CC} range. This problem could be overcome with the addition of voltage gain in an external operational amplifier, running at a higher voltage. This would allow the signal-to-noise ratio of the oscillator to be improved

by increasing the tank voltage swing and still having adequate voltage range to perform the tuning function. These are just a few examples of how the performance of these devices could be improved for amateur applications.

9.7.6 Improving VCO Noise Performance

It is tempting to regard VCO design as a matter of coming up with a suitable oscillator topology with a variable capacitor, simply replacing the variable capacitor with a suitable varactor diode and applying a tuning voltage to the diode. Unfortunately, things are more complex. There is the matter of applying the tuning voltage to the diode without significantly disturbing the oscillator performance. There is also an issue of not introducing parasitic oscillation with the varactor circuit.

Next, as mentioned earlier, one would not like the tuning voltage to drop below the voltage swing in the oscillator tank. If this is allowed to occur, the tuning diodes will go into conduction and the oscillator noise will get worse. A good first approach is to use varactor diodes back to back as shown in Fig 9.39. This will allow the tank voltage swing to be developed across two diodes instead of one, as well as allow for a more balanced loading of the oscillator’s tank. The semiconductor industry has realized this and there are a number of varactors available prepackaged in this configuration today.

IMPROVING THE OPERATING Q OF THE VCO

Many times the Q of passive capacitors available for use in an oscillator tank will exceed the Q of available varactors. One way of reducing the influence of the varactor is to use only the amount of varactor capacity required to tune the oscillator over its desired range. The balance of the capacity is supplied to the tank in the form of a higher Q fixed capacitor. This has the advantage of not requiring the varactor to supply all the capacity needed to make the circuit function, and will often allow for the use of a lower capacity varactor.

Lower capacity varactors typically exhibit higher Q values than their larger capacity counterparts. This concept can be extended by splitting the oscillator tuning range, say 70 MHz to 98 MHz (for a typical lower-side up-converter receiver design popular for the last three decades), into multiple bands. For this example let us consider four oscillators, each with 7 MHz of tuning range. The varactor Q effects can further be swamped by high-Q fixed capacitors. This can be further improved through the use of a “segment-tuned VCO” discussed below. A secondary but important benefit of this is to reduce the effective tuning gain (MHz/volt) of the oscillators, making them less susceptible to other

noise voltage sources in the synthesizer loop. These noise sources can come from a variety of places including, but not limited to, varactor leakage current, varactor tuning drive impedance and output noise of the driving operational amplifier or charge pump.

Segment-tuned VCOs provide the designer with additional benefits, but with them come additional challenges. By segmented we mean that circuit elements, which could be both inductance and capacitance, are selected for each range that the VCO is expected to tune. Fig 9.56 shows the frequency range-switching section of a typical VCO in which several diode switches are used to alter the total tank circuit inductance in small steps. Thus, the segments create a type of “coarse tuning” for the VCO and the output of the loop filter performs “fine tuning.” Usually the component values are arranged in some sort of binary tree. In some advanced designs, 64 or even 128 sub-bands are available from the VCO. This represents the ultimate in reducing the undesirable effects of the varactor.

Many times the segmented-VCO concept is applied to an oscillator design that is required to cover several octaves in frequency. For example, this would be the case with a single-IF radio with the IF at about 8 MHz. The VCO would be required to cover 8 MHz to 48 MHz for 100 kHz to 50 MHz coverage of a typical transceiver. While segmentation will allow one to deal with the tuning of a multi-octave oscillator, segmentation also imposes some additional constraints.

Recalling the earlier section in this chapter on oscillators, the condition for oscillation is an oscillator loop gain of 1 at a phase angle of 0 degrees. Over several octaves, the gain of the oscillating device (typically a transistor) will vary, decreasing as operating frequency increases. While conventional limiting in the oscillator circuit will deal with some of this, it is not good practice to let the normal limiting process handle the entire gain variation. This becomes the role of automatic gain control (AGC) in multi-octave oscillator designs. Application of AGC will allow for the maintenance of the oscillation criteria, a uniform output and good starting characteristics.

Finally, a properly designed segmented VCO can improve synthesizer switching speed. The segmentation allows the designer to “pre-steer” the system and reduce the time required for the integrator to slew the VCO to the desired frequency for lock.

9.7.7 Microprocessor Control of Synthesizers

So far we have examined some interesting components that share one interesting trait, in that they require direction in order to work

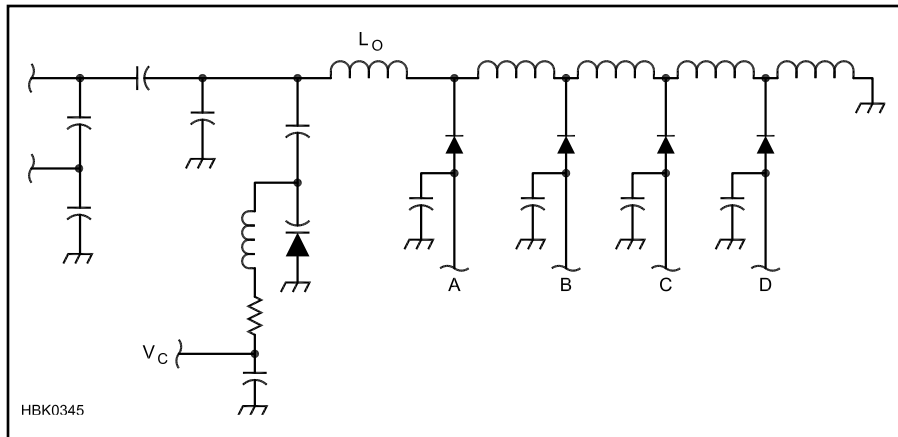


Fig 9.56 — The resonator portion of an inductor-switched segment-tuned VCO. A varactor diode provides tuning over a small range. Diode switches will alter the total inductance, changing the frequency in larger steps. Inductor-switched, capacitor-switched, and combinations are all used in VCO designs. (From Hayward, *Introduction to Radio Frequency Design*, Chapter 7. See references.)

in a system. This direction or “housekeeping” is best often left to a microprocessor and some software. One can differentiate this from DDS or DSP in that the microprocessor does not operate directly on some digital representation of the signal, but rather directs a number of components to perform the task.

The microprocessor may be tasked with selecting the appropriate frequency divisor values, depending on the dial or keyboard input, for the synthesizer. It may also select the appropriate charge pump current (loop gain) as well as pre-steer the system to the proper VCO segment for operation. There are also gain linearizations and offsets that may be supplied with the help of multiplying digital-to-analog converters.

9.7.8 The Role of DDS in Recent Hybrid Architectures

While DSP and DDS (Direct Digital Synthesis) techniques are improving rapidly and are capable of producing a good and economical medium performance transceiver, they are not as yet capable of “competition grade” performance. Present techniques still require some sort of analog/digital hybrid to achieve this. (DSP and DDS are discussed in the **DSP and Software Radio Design** chapter.)

One method of incorporating DDS is to use a hybrid system in which the DDS is allowed to supply the least significant digits and to sum that DDS output into a conventional divide-by-N loop that supplies the most significant digits. This method is employed in a number of commercial signal generators as well as some of the more modern transceivers. Keep in mind that the industry is still looking for cost-to-performance advantages, and that this architecture may be more complex than other methods.

For many years, designers have recognized

that there is a trade off between stability and the best phase noise performance in an oscillator. Stable, frequency-standard-grade oscillators operate their crystals at low drive levels to diminish the effects of aging on the crystal. By necessity, this reduces the signal-to-noise ratio in the oscillator and consequently the phase noise performance. Designers have also come to realize that much of the noise performance can be recaptured by passing the output of the stable low-drive configuration through an additional crystal filter and removing significant amounts of the phase noise sidebands.

Designers have also realized that if one could move the reference in frequency or “rubber reference”, which is normally contradictory to the idea set forth in the last paragraph, they could supply the frequency deviation required to fill in the least significant digits. The big problem is how to achieve this in a mathematically determinable manner. The benefits of as such a system would be great, as it would yield one of the ultimate goals of synthesis, i.e., the true single-loop synthesizer without additional mixing.

This application has recently become fertile ground for DDS techniques. A DDS is clocked from a stable reference oscillator. The output of the DDS is only allowed to deviate enough, through its programming, as is required to fill in the least significant digits of the synthesis. The output of the DDS is then passed through a narrow crystal filter which removes the artifacts of the DDS as well as enhancing the phase noise. The output of the DDS through the filter is then applied to a conventional PLL IC. The PLL IC then directs a highly segmented VCO to achieve the desired output. The beauty of this system is that it is entirely mathematically determinate and may be executed under the direction of a microprocessor as a housekeeper. The performance of such a system

can be competition-grade, while less than a Euro-card size with excellent economy. This technique is used in some of the very latest transceiver designs.

9.7.9 Multi-Phase Division

So far, we have discussed a variety of improvements that can be made to synthesizer components and architectures. One of the limiting factors is the division itself, especially for large divisors. It is relatively common to accept that the signal-to-noise ratio of the divider is as it is and there is not much that can be done about it. *Multi-phase division* (see the patent by Telewski and Drucker in the listed references) can in fact be used to improve the phase noise performance of conventionally available dividers and phase detectors. In its simplest form, the output of the VCO is sent through independent, but identical, dividers and recombined after the phase detector. This is illustrated in the block diagram of Fig 9.57.

The system works in that the noise generated in the individual divider chains is not correlated, and therefore sums as the root of the squares or in quadrature. This yields a 3-dB increase in noise. The signals, on the other hand, sum by linear superposition and effectively increase by 6 dB, giving a

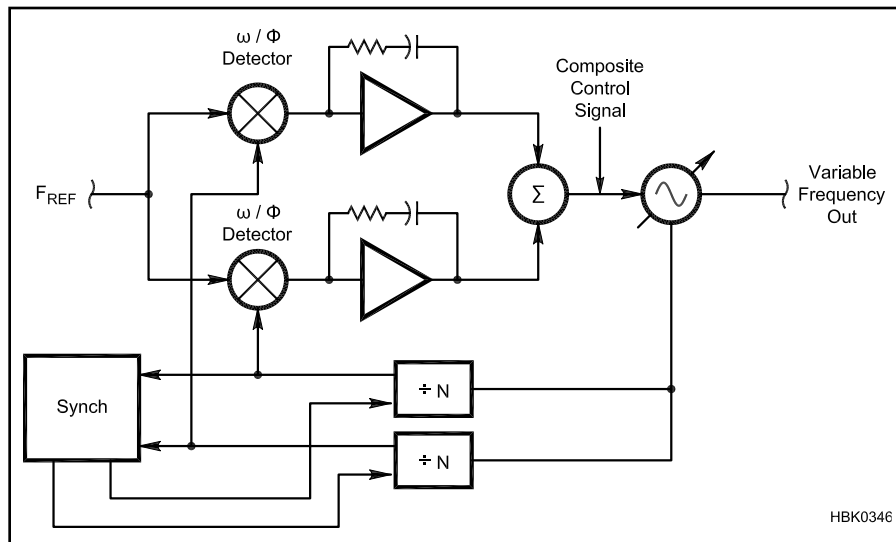


Fig 9.57 — A block diagram of a multi-phase synthesizer.

3-dB advantage in signal-to-noise ratio for each time the divider system is doubled. One might reasonably argue that this is a fair amount of effort for improvement of 3 dB, but remember that multiple dividers

can easily and economically be integrated in one higher-performance chip. It would not be unreasonable to see this technique employed in newer chips, yielding substantially better division performance.

9.8 Present and Future Trends in Oscillator Application

In this chapter a wide variety of oscillator types and frequency-synthesis schemes are discussed. Which techniques are the most important today and which ones will likely become important in the future?

As we follow radio technology from the invention of the vacuum tube, we can see a continuous evolution in the types of oscillators deemed most useful at any given time. Broadly speaking, communications systems started out with LC oscillators, and when the need for greater frequency stability arose, designers moved to crystal oscillators. As the need to vary frequency became apparent, low-drift VFOs were developed to replace the crystals. As higher frequencies began to be exploited, stability again became the dominant problem. Multi-conversion systems that used low-frequency stable VFOs with crystal oscillators were developed to establish the desired high frequency stability. Those designs gave way to highly-stable frequency-synthesis techniques more amenable to digital control for variability and programmability. As more and more of the radio becomes digital and processing power increases, direct digital synthesis (DDS) is

found even in entry-level equipment.

When we look inside today's transceivers, we usually see only two types of oscillators. The first is a temperature-compensated crystal oscillator (TCXO), whose main purpose is to set the frequency calibration of the transceiver. The second type is a DDS VFO interfaced directly to the controlling microprocessor. In the previous generation of equipment, the second type of oscillator was the low phase-noise, voltage-controlled oscillator (VCO) used in synthesizer PLLs.

Yesteryear's mechanically tuned VFOs have fallen by the wayside, with the exception perhaps being their use in low-power, all-analog radios. Even this could change in the near future, as very low power consumption synthesizers are already employed in cell phones and handhelds.

As we look to the future, we can see several emerging trends. Contemporary radios are now employing DSP at the IF. As A-D/D-A technology offers 16 bits of resolution at sample rates exceeding 60 MHz, 1.8 to 30-MHz transceivers are available that are implemented entirely by DSP. Their only remaining analog RF sections are input filtering and gain

compensation, and the output power amplifier and filtering. All of the traditional local oscillator synthesis hardware, IF filters, IF amplifiers, mixers and demodulation are done in a DSP engine that resides between an A-D/D-A converter pair. For the frequency ranges covered by the A-D/D-A pair, the synthesis process is substantially "hidden." This technology is discussed at length in this *Handbook's* chapter on **DSP and Software Radio Design**.

What comes next? On the design horizon in labs around the world are Cognitive Radio and the rapid adoption of digital modes and protocols, even in Amateur Radio. What kinds of oscillators will be required for this architecture and what parameters will be most important?

Cognitive Radio, the ability of the radio to configure itself on-the-fly to adapt to the requirements of its user, will demand oscillators that are highly frequency-agile and that can be adapted to all kinds of currently-unknown digital protocols and modulations. Efforts to share spectrum between competing services — just as amateurs have done manually for a century — will place new demands on spectral purity, as well. The use

of digital modes, particularly for spread-spectrum and high-speed data transmission, will put a premium on frequency accuracy and stability. Both types of oscillators will be integrated into the digital “radio-on-a-chip” architectures being developed in the wireless telephony industry.

The extreme (in today’s terms) requirements for accuracy, stability, and noise may cause even the high-stability TCXO to join other designs of the past. GPS technology can lock terrestrial time-bases to the master rubidium frequency standards carried by each satellite and synchronized to the world-wide network. As this capability is being relentlessly squeezed into consumer-grade devices, Amateur Radio will naturally adopt this

inexpensive source of technology, just as it adopted the components manufactured for broadcast radios 80 years ago.

Having discussed the technology for HF transceivers, what about VHF, UHF and microwave amateur equipment? It is reasonable to assume that the direct DSP approach could be extended up in frequency as the A-D/D-A technologies improve in speed, however, there are some limiting factors regarding phase noise performance. The method of using a transverter and a high-performance DSP-based HF transceiver is likely to remain the practical option for some time to come.

If the transverter’s oscillators are phase-locked to the HF transceiver’s GPS-derived time base, the result would be frequency syn-

thesizers with low phase noise and greater accuracy than the mixer-based up- and down-conversion designs in use today. The low-noise VCO will be an important element in these designs. These UHF and microwave VCOs will continue to take advantage of low-noise, highly-sensitive technology developed for wireless telephony and networking technology and direct satellite broadcast services.

The only thing that stays constant in oscillator and synthesizer design and application is that it changes constantly! As each generation of technology matures, its replacement is already being tested in laboratory prototypes. Amateur Radio will continue to adopt — and even advance — state-of-the art technology in the quest for better performance.

9.9 Glossary of Oscillator and Synthesizer Terms

Buffer — A circuit that amplifies the output of a circuit while isolating it from the load.

Bypass — Create a low ac impedance to ground at a point in the circuit.

Cavity — A hollow structure used as an electrical resonator.

Closed-loop — Operation under the control of a feedback loop (see also **open-loop**).

Coupling — The transfer of energy between circuits or structures.

Damping (factor) — the characteristics of the decay in a system’s response to an input signal. The **damping factor**, ζ , is a numeric value specifying the degree of damping. An **underdamped** system alternately overshoots and undershoots the eventual steady-state output. An **overdamped** system approaches the steady-state output gradually, without overshoot. A **critically-damped** system approaches the steady-state output as quickly as possible without overshoot.

dBc — Decibels with respect to a carrier level.

DC-FM — control of a signal generator’s output frequency by a dc voltage.

Decouple — To provide isolation between circuits, usually by means of filtering.

Direct digital synthesis (DDS) —

Generation of signals by using counters and accumulators to create an output waveform.

Distributed — Circuit elements that are inherent properties of an extended structure, such as a transmission line.

ESR — Equivalent series resistance.

Free-running — Oscillating without any form of external control.

Fundamental — Lowest frequency of natural vibration or oscillation.

Integrator — A low-pass filter whose output is approximately the integral of the input signal.

Intermodulation — Generation of distortion products from two signals interacting in a nonlinear medium, device, or connection.

Isolation — Preventing signal flow between two circuits or systems.

Reverse isolation refers to signal flow against the desired signal path.

Jitter (phase jitter) — Random variations of a signal in time, usually refers to random variations in the transition time of digital signals between states.

Linearization — Creation of a linear amplification or frequency characteristic through corrections supplied by an external system.

Loop gain — The total gain applied to a signal traveling around a feedback control loop.

Lumped (element) — Circuit elements whose electrical functions are concentrated at one point in the form of an electronic component.

Match — Equal values of impedance.

Modulus — The number of states of a digital counter or divider.

Motional capacitance (inductance) — The electrical effect of a crystal’s mechanical properties, modeled as a capacitance (inductance).

Natural frequency (ω_n) — Frequency at which a system oscillates without any external control.

Noise bandwidth — The width of an ideal rectangular filter that would pass the

same noise power from white noise as the filter being compared (also called **equivalent noise bandwidth**).

Open-loop — Operation without controlling feedback.

Oscillation — Repetitive mechanical motion or electrical activity created by the application of positive feedback.

Overtone — Vibration or oscillation at frequencies above the **fundamental**, usually harmonically related to the fundamental.

Permeability tuning — Varying the permeability of the core of an inductor used to control an oscillator’s frequency.

Phase-lock — Maintain two signals in a fixed phase relationship by means of a control system.

Phase noise — Random variations of a signal in time, expressed as variations in phase of a sinusoidal signal.

Phasor — Representation of a sinusoidal signal as an amplitude and phase.

Power density — Amount of power per unit of frequency, usually specified as dBc/Hz or as RMS voltage/ $\sqrt{\text{Hz}}$.

Prescaler — A frequency divider used to reduce the frequency of an input signal for processing by slower circuitry.

Preselector — Filters applied at a receiver’s input to reject out-of-band signals.

Pull — Change the frequency at which a crystal oscillates by changing reactance of the circuit in which it is installed.

Quadrature — A 90° phase difference maintained between two signals.

Reciprocal mixing — Noise in a mixer’s output due to the LO’s noise sidebands mixing with those of the desired signal.

Relaxation oscillation — Oscillation produced by a cycle of gradual accumulation of energy followed by its sudden release.

Resonator — Circuit or structure whose resonance acts as a filter.

Simulation — Calculate a circuit's behavior based on mathematical models of the components.

Spurious (spur) — A signal at an undesired frequency, usually unrelated to the frequency of a desired frequency.

Squegg — Chaotic or random jumps in an oscillator's amplitude and/or frequency.

Static (synthesizer) — A synthesizer designed to output a signal whose frequency does not change or that is not

changed frequently.

Synthesis (frequency) — The generation of variable-frequency signals by means of nonlinear combination and filtering (direct synthesis) or by using phase-lock or phase-control techniques (indirect synthesis).

TCXO — Temperature-compensated crystal oscillator. A **digitally temperature-compensated oscillator (DTCXO)** is controlled by a microcontroller or computer to maintain a constant frequency. **Oven-controlled crystal oscillators (OCXO)** are placed in a heated enclosure to maintain a constant temperature and frequency.

Temperature coefficient (tempco) — The

amount of change in a component's value per degree of change in temperature.

Temperature compensation — Causing a circuit's behavior to change with temperature in such a way as to oppose and cancel the change with temperature of some temperature-sensitive component, such as a crystal.

Varactor (Varicap) — Reverse-biased diode used as a tunable capacitor.

VCO — Voltage-controlled oscillator (also called **voltage-tuned oscillator**).

VFO — Variable-frequency oscillator.

VXO — Variable crystal oscillator, whose frequency is adjustable around that of the crystal.

9.10 References and Bibliography

Clarke and Hess, *Communications Circuits; Analysis and Design* (Addison-Wesley, 1971; ISBN 0-201-01040-2).

Wide coverage of transistor circuit design, including techniques suited to the design of integrated circuits. Its age shows, but it is especially valuable for its good mathematical treatment of oscillator circuits, covering both frequency- and amplitude-determining mechanisms. Look for a copy at a university library or initiate an interlibrary loan.

J. Grebenkemper, "Phase Noise and Its Effects on Amateur Communications," *Part 1, QST*, Mar 1988, pp 14-20; *Part 2, QST*, Apr 1988 pp 22-25. Also see Feedback, *QST*, May 1988, p 44.

W. Hayward and D. DeMaw, *Solid State Design for the Radio Amateur* (Newington, CT: ARRL, 1986). Now out of print, this is dated but a good source of RF design ideas.

W. Hayward, W7ZOI, R. Campbell, KK7B, and B. Larkin, W7PUA, *Experimental Methods in RF Design* (Newington, CT: ARRL, 2003). A good source of RF design ideas, with good explanation of the reasoning behind design decisions.

W. Hayward, W7ZOI, *Introduction to Radio Frequency Design* (Newington, CT: ARRL, 1994). In-depth treatments of circuits and techniques used at RF.

"Spectrum Analysis...Random Noise Measurements," Hewlett-Packard Application Note 150-4. Source of correction factors for noise measurements using spectrum analyzers.

HP notes should be available through local HP dealers.

B. Parzen, A. Ballato, *Design of Crystal and Other Harmonic Oscillators* (Wiley-Interscience, 1983, ISBN 0-471-08819-6). This book shows a thorough treatment of modern crystal oscillators including the optimum design. It is also the only book that looks at the base and collector limiting effect. The second author is affiliated with the US Army Electronics Technology & Devices Laboratory, Fort Monmouth, New Jersey.

U. Rohde, *Microwave and Wireless Synthesizers Theory and Design* (John Wiley and Sons, 1997, ISBN 0-471-52019-5). This book contains the textbook-standard mathematical analyses of frequency synthesizers combined with unusually good insight into what makes a better synthesizer and a lot of practical circuits to entertain serious constructors. A good place to look for low-noise circuits and techniques.

U. Rohde, D. Newkirk, *RF/Microwave Circuit Design for Wireless Applications* (John Wiley and Sons, 2000, ISBN 0-471-29818-2) While giving a deep insight into circuit design for wireless applications, Chapter 5 (RF/Wireless Oscillators) shows a complete treatment of both discrete and integrated circuit based oscillators. Chapter 6 (Wireless Synthesizers) gives more insight in synthesizers and large list of useful references.

U. Rohde, J. Whitaker, *Communications Receivers DSP, Software Radios, and Design*, 3rd ed., (McGraw-Hill,

2001, ISBN 0-07-136121-9). While mostly dedicated to communication receivers, this book has a useful chapter on Frequency Control and Local Oscillators, specifically on Fractional Division Synthesizers.

G. Vendelin, A. Pavio, U. Rohde, *Microwave Circuit Design Using Linear and Nonlinear Techniques*, 2nd ed., (Wiley-Interscience, 2005, ISBN 0-471-414479-4). This is a general handbook on microwave circuit design. It covers (in 200 pages) a large variety of oscillator design problems including microwave applications. It provides a step-by-step design guide for both linear and nonlinear oscillator designs.

U. Rohde, A. Poddar, G. Boeck, *The Design of Modern Microwave Oscillators for Wireless Applications Theory and Optimization* (Wiley-Interscience, 2005, ISBN 0-471-72342-8). This is the latest and most advanced textbook on oscillator design for high frequency/microwave application. It shows in detail how to design and optimize high frequency and microwave VCOs. It also contains a thorough analysis of the phase noise as generated in oscillators. While highly mathematical, the appendix gives numerical solutions that can be easily applied to various designs. It covers both bipolar transistors and FETs.

U. Rohde, "All About Phase Noise in Oscillators," Part 1, *QEX*, Dec 1993 pp 3-6; Part 2, *QEX*, Jan 1994 pp 9-16; Part 3, *QEX*, Feb 1994, pp 15-24.

U. Rohde, "Key Components of Modern

- Receiver Design,” Part 1, *QST*, May 1994, pp 29-32; Part 2, *QST*, June 1994, pp 27-31; Part 3, *QST*, Jul 1994, pp 42-45. Includes discussion of phase-noise reduction techniques in synthesizers and oscillators.
- U. Rohde, “A High-Performance Hybrid Frequency Synthesizer,” *QST*, Mar 1995, pp 30-38.
- E.W. Pappenfus, W. Bruene and E.O. Schoenike, *Single Sideband Circuits and Systems*, (McGraw-Hill, 1964). A book on HF SSB transmitters, receivers and accoutrements by Rockwell-Collins staff. Contains chapters on synthesizers and frequency standards. The frequency synthesizer chapter predates the rise of the DDS and other recent techniques, but good information about the effects of synthesizer performance on communications is spread throughout the book.
- Motorola Applications Note AN-551, “Tuning Diode Design Techniques,” included in Motorola RF devices data books. A concise explanation of varactor diodes, their characteristics and use.
- I. Keyser, “An Easy to Set Up Amateur Band Synthesizer,” *RADCOM* (RSGB), Dec 1993, pp 33-36.
- B. E. Pontius, “Measurement of Signal Source Phase Noise with Low-Cost Equipment,” *QEX*, May-Jun 1998, pp 38-49.
- V. Manassewitsch, *Frequency Synthesizers Theory and Design* (Wiley-Interscience, 1987, ISBN 0 471-01116-9).
- Frederick J Telewski and Eric R Drucker, “Noise Reduction Method and Apparatus for Phase-locked Loops”, U.S. Patent 5,216,387.
- David Stockton, “Polyphase noise-shaping fractional-N frequency synthesizer”, U.S. Patent 6,509,800.
- F. Gardner, *Phaselock Techniques*, (John Wiley and Sons, 1966, ISBN 0-471-29156-0).
- INTERESTING MODERN JOURNAL PUBLICATIONS**
- Oscillator References**
- C.-C. Wei, H.-C. Chiu, and W.-S. Feng, “An Ultra-Wideband CMOS VCO with 3-5 GHz Tuning Range,” *IEEE, International Workshop on Radio-Frequency Integration Technology*, Nov 2005, pp 87-90.
- A. P. S. (Paul) Khanna, “Microwave Oscillators: The State of The Technology”, *Microwave Journal*, Apr 2006, pp. 22-42.
- M-S Yim, K. K. O., “Switched Resonators and Their Applications in a Dual Band Monolithic CMOS LC Tuned VCO,” *IEEE MTT*, Vol. 54, Jan 2006, pp 74-81.
- A. D. Berny, A. M. Niknejad, and R. G. Meyer, “A 1.8 GHz LC VCO with 1.3 GHz Tuning Range and Digital Amplitude Calibration,” *IEEE Journal of SSC*, vol. 40. no. 4, 2005, pp 909-917.
- U.L. Rohde, “A New Efficient Method of Designing Low Noise Microwave Oscillators,” Dr.-Ing. Dissertation, TU- Berlin, Germany, 12 Feb 2004.
- N. Nomura, M. Itagaki, and Y. Aoyagi, “Small packaged VCISO for 10 Gbit Ethernet Application”, *IEEE IUFFCS*, 2004, pp. 418-421.
- A. K. Poddar, “A Novel Approach for Designing Integrated Ultra Low Noise Microwave Wideband Voltage-Controlled Oscillators,” Dr.-Ing. Dissertation, TU- Berlin, Germany, 14 Dec 2004.
- Sheng Sun and Lei Zhu, “Guided-Wave Characteristics of Periodically Nonuniform Coupled Microstrip Lines- Even and Odd Modes,” *IEEE Transaction on MTT*, Vol. 53, No. 4, Apr 2005, pp. 1221-1227.
- A. Ravi, B. R. Carlton, G. Banerjee, K. Soumyanath, “A 1.4V, 2.4/5.2 GHz, 90 nm CMOS system in a Package Transceiver for Next Generation WLAN,” *IEEE Symp. on VLSI Tech.*, 2005.
- A. Chenakin, “Phase Noise Reduction in Microwave Oscillators”, *Microwave Journal*, Oct 2009, pp 124-140.
- Synthesizer References**
- R. E. Best, *Phase-Locked Loops: Design, Simulation, and Applications*, 5th ed., McGraw-Hill, 2003.
- H. Arora, N. Klemmer, J. C. Morizio, and P. D. Wolf, “Enhanced Phase Noise Modeling of Fractional-N Frequency Synthesizer,” *IEEE Trans. Circuits and Systems-I: Regular Papers*, vol 52, Feb 2005, pp 379-395.
- A. Natrajan, A. Komijani, and A. Hajimiri, “A Fully 24-GHz Phased-Array Transmitter in CMOS,” *IEEE Journal of SSC*, vol 40, no 12, Dec 2005, pp 2502-2514.
- C. Lam, B. Razavi, “A 2.6/5.2 GHz Frequency Synthesizer in 0.4um CMOS Technology,” *IEEE JSSC*, vol 35, May 2000, pp 788-79.
- W. Rahajandraibe, L. Zaid, V. C. de Beaupre, and G. Bas, “Frequency Synthesizer and FSK Modulator For IEEE 802.15.4 Based Applications,” 2007 RFIC Symp. Digest, pp 229-232.
- C. Sandner, A. Wiesbauer, “A 3 GHz to 7 GHz Fast-Hopping Frequency Synthesizer For UWB,” *Proc. Int. Workshop on Ultra Wideband Systems* 2004, pp 405-409.
- J. Lee, “A 3-to-8 GHz Fast-Hopping Frequency Synthesizer in 0.18-um CMOS Technology,” *IEEE Journal of SSC*, vol 41, no 3, Mar 2006, pp 566-573.
- R. van de Beek, D. Leenaerts, G. van der Weide, “A Fast-Hopping Single-PLL 3-band UWB Synthesizer in 0.25um SiGe BiCMOS,” *Proc. European Solid-State Circuit Conf.* 2005, pp 173-176.
- R. B. Staszewski and others, “All Digital PLL and Transmitter for Mobile Phones,” *IEEE J. Solid-State Circuits*, vol 40, no 12, Dec 2005, pp 2469-2482.