

## Contents

- |                                                                             |                                                            |
|-----------------------------------------------------------------------------|------------------------------------------------------------|
| 24.1 A 100-W Compact Z-Match Antenna Tuner                                  | 24.8 A Trio of Transceiver/Computer Interfaces             |
| 24.2 A Microprocessor-Controlled SWR Monitor                                | 24.9 A Simple Serial Interface                             |
| 24.3 A 160- and 80-meter Matching Network for Your 43-Foot Vertical         | 24.10 USB Interfaces For Your Ham Gear                     |
| 24.4 Switching the Matching Network for Your 43-Foot Vertical               | 24.11 The Universal Keying Adapter                         |
| 24.5 An External Automatic Antenna Switch for Use With Yaesu or ICOM Radios | 24.12 The TiCK-4 — A Tiny CMOS Keyer                       |
| 24.6 A Low-Cost Remote Antenna Switch                                       | 24.13 Adapting Aviation Headsets to Ham Radios             |
| 24.7 Audible Antenna Bridge                                                 | 24.14 An Audio Intelligibility Enhancer                    |
|                                                                             | 24.15 An Audio Interface Unit for Field Day and Contesting |


# Station Accessories

An Amateur Radio station is much more than the transceiver, amplifier and other major pieces of equipment found in a typical ham shack. In this chapter you will find a number of accessory items to make operation more convenient, or to tie other pieces of equipment together. Projects include antenna matching and switching solutions, transceiver/computer interfaces and other station accessories. Additional station accessory projects may be found on the *Handbook* CD-ROM.

## 24.1 A 100-W Compact Z-Match Antenna Tuner

A Z-Match tuner will match just about anything on all HF bands, and only uses two controls. They are well regarded, but acquiring the necessary air-wound inductors and variable capacitors can be difficult. In addition, air-wound inductors imply large tuners. The antenna tuner described here by Phil Salas, AD5X, is compact enough for portable HF operation, handles 100 W and uses readily available parts. The Z-Match circuit was originally described in "Multiband Tuning Circuits" by R.W. Johnson, W6MUR, in July 1954 *QST* and the article is included in this book's supplemental material.

The idea for this project came from an article by Charles Lofgren, W6JJZ, in the *ARRL Antenna Compendium Vol 5*. In that article, the author suggested using a toroid core-based inductor. This would solve the air-core inductor/size problem. Suitable variable capacitors are available at a good price. The result is the compact unit shown in **Fig 24.1**.

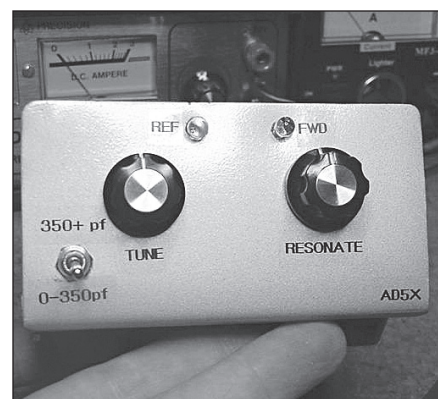

**Fig 24.1** — The Z-Match Tuner handles 100 W and can be used from 80 through 10 meters.

### TUNER CONSTRUCTION

The final circuit shown in **Fig 24.2** is based on W6JJZ's article. The only real change was to go from two switch-selected output links (10 turns and 4 turns) to a single 8-turn output link, and to increase the variable capacitor size to 400-pF. The tuner provides a good match from 80-10 meters!

The tuner is built into a 3 × 5¼ × 5⅞ inch (HWD) aluminum box. Toroid T1 is supported by its leads and some hot glue between the inductor and the frame of C2. Also put a little hot glue between T1 and the side of the case.

The variable capacitors must be insulated from ground, therefore mount both capacitors on a piece of single-sided circuit- or perf-board that is cut just wide enough to fit into the aluminum case. Then mount this capacitor/perf-board assembly in the case with stand-off screws. Capacitor shaft couplings are made from a ¼-NPT brass nipple, available from the plumbing section of most hardware stores. These nipples have a ¼-inch inside diameter. Cut a 1-inch nipple in half to make two couplers. Then drill and tap holes for two #6 screws in each piece. See **Fig 24.3** for capacitor mounting and shaft coupler details. For the insulated shafts, use ¼-inch diameter nylon rods available from many hardware stores.

## OPERATION

Tuning the Z-Match tuner is very easy. First adjust C2 for maximum receiver noise. Then apply some RF power and adjust C1 and C2 for minimum SWR. If you need more capacitance for matching, use S1 to switch in the extra section of C1, or switch in a fixed mica capacitor across C1. Balanced feed lines

terminated in banana plugs can plug right into the center pin of the output SO-239 and the adjacent banana jack. To feed coax, ground one end of the output link with switch S2.

## OPTICAL HF SWR METER FOR THE Z-MATCH TUNER

While you can use any external SWR meter

with the Z-Match tuner — including the SWR meter built into most rigs — the author built an optical SWR meter into the same case for convenience. Refer to **Fig 24.4A**. It works well with high intensity LEDs rather than conventional meters. The SWR meter is built on a small piece of perf-board and mounted to the solder lug on the tuner's input SO-239. A little hot glue between the perf-board and the back of the chassis adds stability (**Fig 24.5**).


This broadband circuit works well at the 100-W power level through at least 30 MHz. With careful lead control, it should work up through 6 meters. The transformer is an FT37-43 ferrite core wound with 10 bifilar turns of #26 enameled wire. The primary is just the single wire passing through the center of the toroid. To calibrate the SWR bridge, connect the output to a resistive 50-Ω load. Apply RF power on any HF band and adjust the 20-pF variable capacitor until the REFL LED goes out.

The FWD LED gives an indication of transmitter forward power. You may want to increase the value of the 4.7 kΩ resistor in the FWD circuit if the green LED is too bright. Or you could eliminate this LED and just use the REFL LED.

## A BAR-GRAPH DISPLAY FOR THE OPTICAL SWR METER

If you can supply dc power to your Z-Match Tuner and SWR meter, you may want to add the bar graph display as shown in **Fig 24.4B** to display SWR reflected power. A version of the tuner with bar graph option is shown in **Fig 24.6**. The nice thing about using the bar graph display is that it seems easier to null the reflected power because the display gives more of an analog meter “feel.” Adjust the Z-Match tuner for minimum brightness of the REFL LED. When this occurs, the SWR should be less than 1.5:1.


This tuner addresses the issues of inductor size and finding reasonably priced multi-section variable capacitors. The result is a wide-band, easily adjustable tuner for either portable or base station operation.

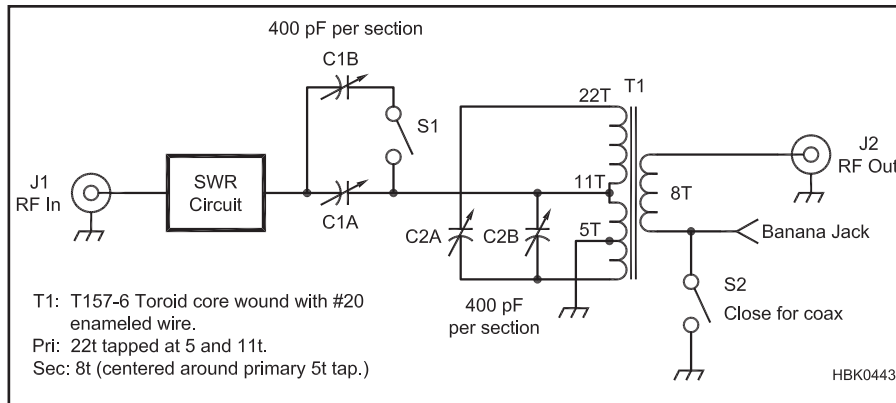

**Fig 24.2 — Schematic of the 100-W Z-Match tuner.**



C1, C2 — 400 pF per section, 2-section variable capacitor (Oren Elliott S2-399, [www.orenelliottproducts.com](http://www.orenelliottproducts.com)). If you substitute another variable capacitor, use one with at least 350 pF per section, rated at 500 V RMS minimum.  
J1, J2 — SO-239 connectors.  
S1, S2 — SPDT mini-toggle switch.

T1 — Primary: 22 turns #20 AWG enam wire tapped at 5 and 11 turns. Secondary: 8 turns, with 4 turns either side of the primary 5 turn tap. Wound on T157-6 toroid (Amidon Associates, [www.amidon-inductive.com](http://www.amidon-inductive.com)).  
Enclosure (Eagle, 40UB103 from [www.mouser.com](http://www.mouser.com)).

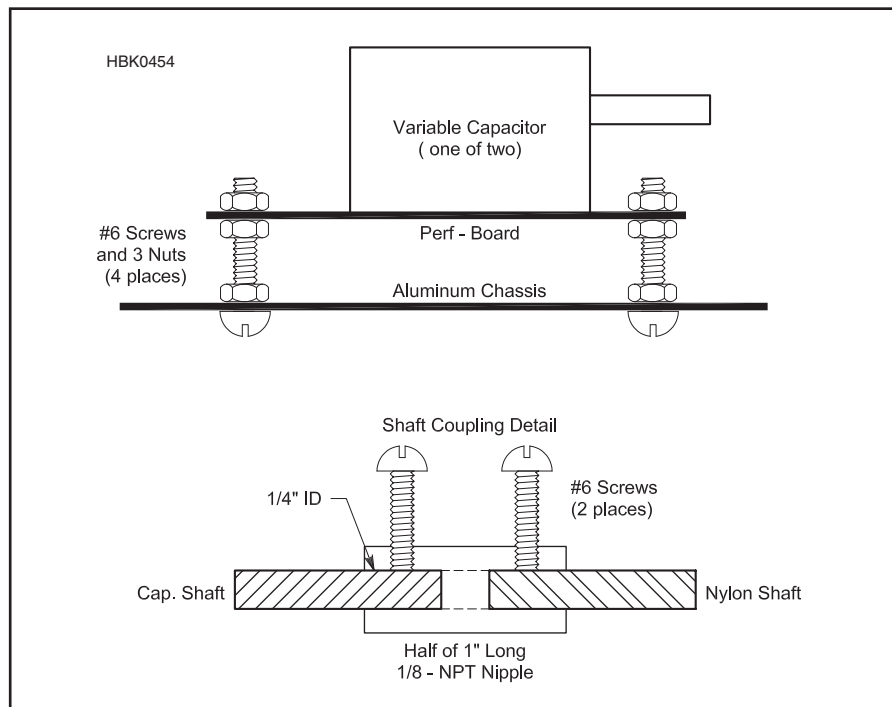

**Fig 24.3 — The variable capacitors are insulated from the chassis by mounting them on perforated board. A 1/8-NPT nipple is made into a shaft coupling to couple the insulating shafts to the main capacitor shafts.**

**Fig 24.4 — Optical SWR meter schematic with the bar graph display modification (see text). The basic LED version is shown in A and the bar graph addition in B.**  
**C3 — 2-20 pF variable capacitor (Mouser 24AA113 4-34 pF variable is suitable).**  
**D1 — Red LED, high-intensity.**  
**D2 — Green LED, high-intensity.**  
**L1 — 10 bifilar turns of #26 enam wire on FT37-43 toroid core (Amidon Associates, [www.amidon-inductive.com](http://www.amidon-inductive.com)).**  
**U1 — Display driver IC, LM3914 (All Electronics, [www.allelectronics.com](http://www.allelectronics.com)).**  
**U2 — 10-LED bar graph display (Mouser 859-LTL-1000HR). Any 10-segment LED bar graph will work, but verify pinout.**

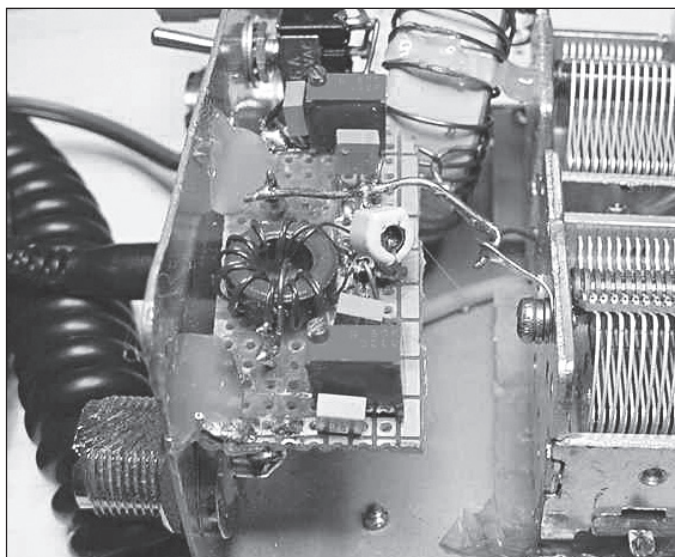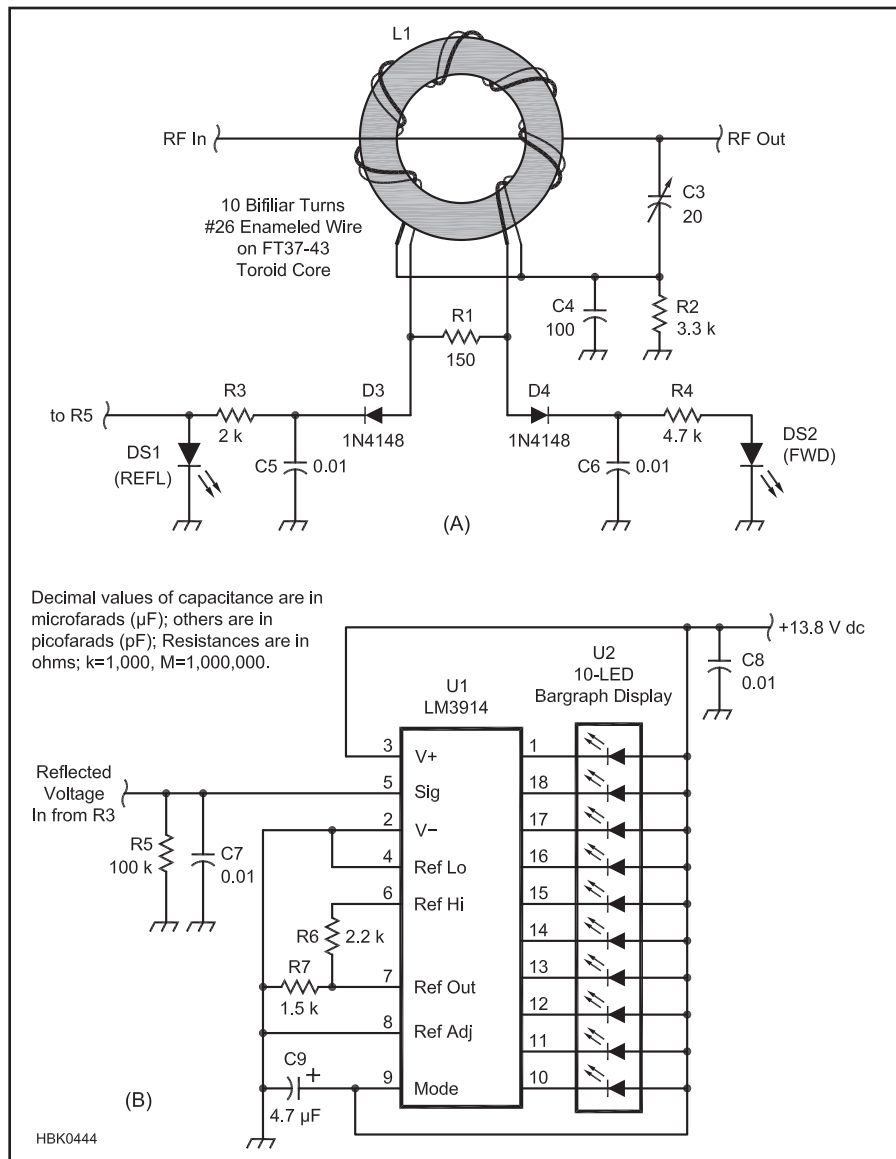

**Fig 24.5 — The SWR meter circuit board is soldered directly to the RF input connector and attached to the back panel with hot glue.**



**Fig 24.6 — The bar graph display of reflected power makes tuning easier and more intuitive.**



## 24.2 A Microprocessor Controlled SWR Monitor


This update of the basic SWR meter, designed by Larry Coyle, K1QW, uses a microprocessor to drive an analog panel meter, exploiting the best features of both analog and digital technology. The instrument also displays forward/reflected/net power and return loss (see the **Transmission Lines** chapter) with peak-hold capability. All display selections are selected by front panel switches. *[More information is available on K1QW's Web site, [www.lcb systems.com](http://www.lcb systems.com), and a complete package of information on this project with supporting files and photos is available on the CD-ROM accompanying this Handbook.]*

### OVERVIEW AND BLOCK DIAGRAM

After a bit of work, the author came up with the SWR/Power/Return Loss monitor shown in block diagram form in **Fig 24.7**. There are three interacting assemblies: SWR sense head, front panel assembly and signal processor board. (The latter two make up the Display and Signal Processor unit.) The SWR sense head is a conventional Stockton dual-transformer bridge with Schottky diode detectors. This component converts the forward and reflected RF amplitudes to dc and connects to the Display and Signal Processor by an ordinary stereo audio cable.

The user interface to the SWR monitor is familiar and intuitive. As you can see in **Fig 24.8A**, a front-panel rotary switch selects the quantity to be measured and an analog meter displays the result.

- Forward power on a linear scale
- Reflected power as a percentage of forward power
- Net power delivered to the load

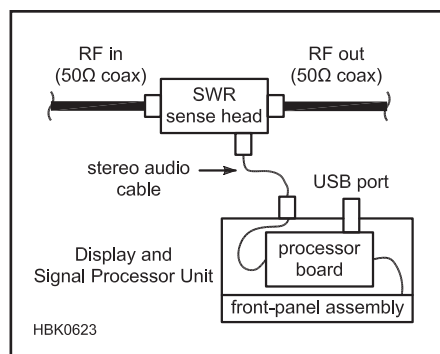

**Fig 24.7** — This block diagram shows how the SWR sense head and the signal processor box are connected by an ordinary two-conductor shielded stereo audio cable. The signal processor box contains the processor board and the front panel assembly.

- SWR on a linear scale
  - Return loss on a linear scale
- Some additional features are:
- Peak-hold front panel switch
  - A front panel switch to multiply the meter sensitivity by 3X
  - Data logging to a computer using the USB port.

• Transmitter Lockout (XLO) at high SWR  
The rear panel, **Fig 24.8B**, shows the power switch and external connections


Transmitter Lockout (XLO) is a protective feature that lights a LED on the front panel and energizes a relay when the SWR exceeds a preset level. This opens a set of relay contacts which are connected to a pair of banana jacks on the rear panel. Once triggered, the relay remains energized for either three or nine seconds, depending on the configuration of the DIP switch located on the signal processor board. The same DIP switch also allows you to

select the SWR level at which the XLO relay triggers — 1.5, 2, 3 or 4:1. By connecting the relay contacts in series with your rig's PTT or keying line, transmitting into high SWR can be prevented.


The two dc signals from the sense head make up the analog input to the signal processor board. The analog output for driving the meter is a pulse width modulated (PWM) signal generated by the microprocessor and smoothed by a simple resistor-capacitor (RC) filter.
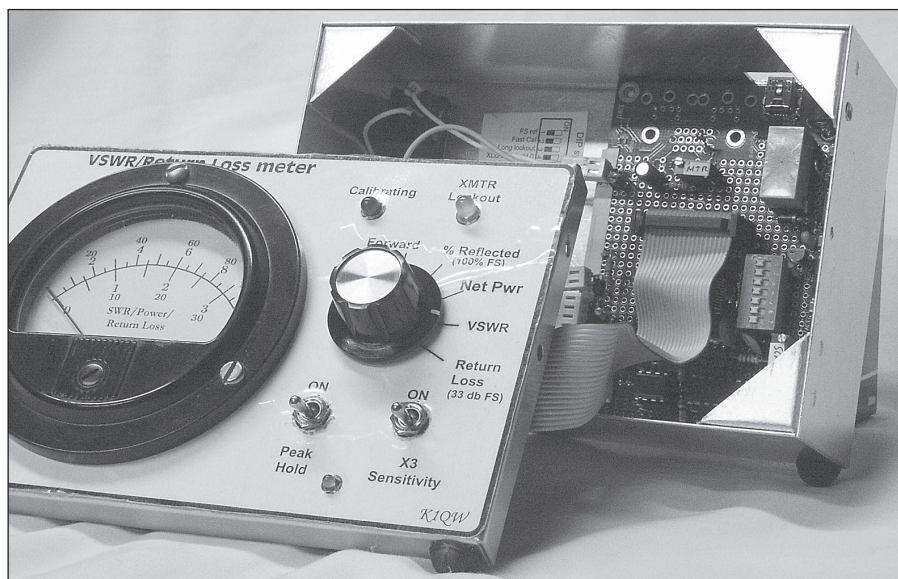
### THE MICROPROCESSOR

The Parallax "Propeller" microprocessor ([www.parallax.com](http://www.parallax.com)) is unique in that it's really eight processors ("cogs") in one package, each one able to run its own separate program during its own time slot, controlled by a central "hub." This may sound challenging, but this actually makes programming the chip



(A)

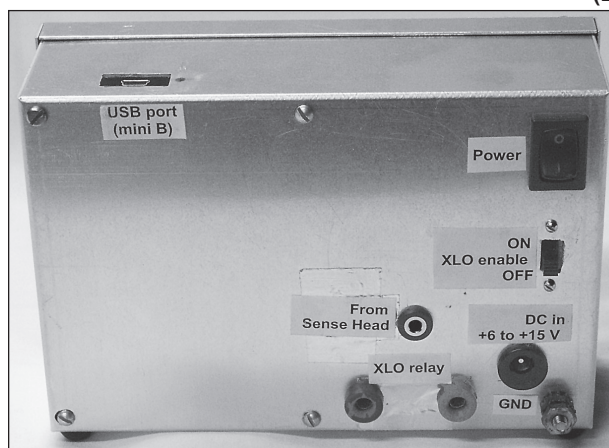

(B)

**Fig 24.8** — (A) Front panel of the display and signal processor unit. The meter face and the front panel lettering were created using Microsoft Visio, printed on heavy paper stock and attached with contact cement. With the front cover moved aside, you can see the ribbon cable carrying signals between the front panel assembly and the processor board. (B) Rear panel of the display and signal processor. The mini-B USB connector is accessible through the opening on the top surface of the enclosure.

much easier. If you need to carry out several tasks at once — and most microprocessor applications do — just assign each job to its own individual cog and work on them separately. The central hub makes sure each cog gets its turn and keeps things synchronized.

The project uses the 3 × 4 inch Propeller USB Development Board from Parallax. It includes the Propeller chip, an Electrically-Erasable Programmable Read-Only Memory (EEPROM) for program storage, a 5 MHz crystal, two voltage regulators and, a USB mini-B connector with all the necessary USB interface circuitry.

The Propeller is programmed in a language called “Spin” which should make anyone who is familiar with the BASIC computer language feel at home. All the tools you need to write software for and to program the Propeller is available for free on the Parallax Web site, including an extensive library of pre-built code routines that you can just drop into your own programs.

Software is loaded onto the development board using the USB port from a host computer with a USB port. When not in use as a programming port, the same USB port is used as a serial data port for passing data between the SWR monitor and a computer running a terminal program such as HyperTerminal.

## MICROPROCESSOR BOARD CIRCUITRY

The development board includes a prototyping area large enough to hold all the parts of the SWR monitor except for front and rear panel components. Since most of the parts come assembled on the development board, construction of the digital board is quite easy. As you can see in **Fig 24.9A**, the electrical schematic, only two integrated circuits and a few analog components are required.

The dc signals representing forward and reflected power from the SWR sense head are received by dual op-amp U2. Each section of U2 is configured as a unity-gain voltage follower with a compensating diode (D1 and D2) to balance out the dc offset introduced by the Schottky rectifier diodes in the sensing head. (The technique of using a diode in the feedback path of an op amp to compensate for the non-linearity of an RF detector diode is described in detail in “A Compensated, Modular RF Voltmeter” in the **Test Equipment and Measurements** chapter of this book.) Each section also has an RC low-pass filter at its input to filter out unwanted RF — always a possibility around a ham shack.

The next stage in the signal path is U3, an analog multiplexer (MUX). This chip acts as a three-position switch under control of the microprocessor. (A fourth channel is unused.) The forward and reflected signals (on pins 14 and 15) are sampled alternately, 20 times per second, as long as the program is running. The

**Table 24.1A**  
**Digital Inputs**

<i>Digital Input</i>	<i>Originates at</i>	<i>What it does</i>
X3SEL	front panel - toggle switch	increases meter sensitivity by 3X
PEAKENBL	front panel - toggle switch	enables peak hold function on the meter
RLOSSEL	front panel - rotary switch	displays return loss on the meter
SWRSEL	front panel - rotary switch	displays SWR on meter
NETSEL	front panel - rotary switch	displays net power on meter
REFSEL	front panel - rotary switch	displays percent reflected power on meter
FWDSEL	front panel - rotary switch	displays forward power on meter
HIREFSEL	proc board - DIP switch	drives meter to full scale for calibration (must be OFF for normal operation)
FASTCAL	proc board - DIP switch	speeds up meter response for calibration (must be OFF for normal operation)
XLOLONG	proc board - DIP switch	enables long xmtr lockout (about 9 seconds)
XLTHRESH0	proc board - DIP switch	XLO threshold bit 0
XLTHRESH1	proc board - DIP switch	XLO threshold bit 1
XLOCKENBL	rear panel switch	enables xmtr lockout function
DIAG	proc board - jumper JP1	displays raw input levels on terminal
W100	proc board - jumper JP2	changes terminal display to 0-100 watt range (required when using 100-watt sense head)

**Table 24.1B**  
**Digital Signals for SWR Threshold Select**

<i>XLTHRESH1</i>	<i>XLTHRESH0</i>	<i>Selects SWR threshold level</i>
OFF	OFF	1.5:1
OFF	ON	2:1
ON	OFF	3:1
ON	ON	4:1

third input to the MUX (pin 12) is grounded, and is also sampled by the microprocessor from time to time. This gives a measure of any dc offsets introduced by the analog-to-digital conversion and is used to correct the forward and reflected readings in software. This automatic zero adjustment takes place every five seconds or so and is indicated by a brief flash from the front-panel “Calibrating” LED that also serves as a “digital heartbeat” to show that the software is running.

The MUX output (pin 13) is passed to a potentiometer voltage divider to allow the scale factor to be set during calibration. From there it goes to the Propeller microprocessor itself where a delta-sigma analog-to-digital conversion takes place. (See the **Analog Basics** chapter for information on analog-to-digital conversion.)

## DIGITAL INPUT/OUTPUT

The microprocessor responds to the user’s inputs by monitoring the state of 13 digital input pins. Most of these pins are controlled by the rotary and toggle switches on the front panel. The panel connects to the processor board by a short ribbon cable as shown in **Fig 24.8A**. See **Fig 24.9B** for a schematic of the separate front panel assembly. The ribbon cable also carries power for the LEDs. On the

processor board there are a multi-section dual in-line package (DIP) switch, S2, and two jumpers, JP1 and JP2, which select among the various operating modes. Lastly, the Xmtr Lockout (XLO) switch is mounted on the rear panel and visible in **Fig 24.8B**. These inputs to the microprocessor and the various modes of operation they control are summarized in **Table 24.1A**. The digital inputs are all active low; ie, the function is enabled when the signal line is at a low logic level. XLTHRESH1 and XLTHRESH0 form a two-bit code to select one of four SWR levels. When this SWR level is exceeded and if XLO is enabled, the transmitter lockout function is triggered.


There are only six digital *outputs*:

- Two address lines for the analog MUX to select among the three input channels
- Two lines to power the Calibrating and XLO LEDs located on the front panel
- One PWM signal to drive the front-panel analog meter
- One line to control the XLO relay.


**Fig 24.8A** shows the built-up processor board inside the 2 × 4 × 6 inch aluminum enclosure connected to the front panel with the ribbon cable. Here you can also see some of the wiring to the rear panel components. The USB connector is at the top edge of the circuit board and is accessible through a rectangular hole nibbled out of the top surface of the aluminum box.

## THE RF SENSE HEAD

The SWR sense head is the business end of the SWR meter where the forward and reflected amplitude components of the RF present on the transmission line are separated and converted to dc. For this project I adopted a straightforward Stockton directional coupler circuit, with Schottky diode detectors and, unlike other designs, it requires no

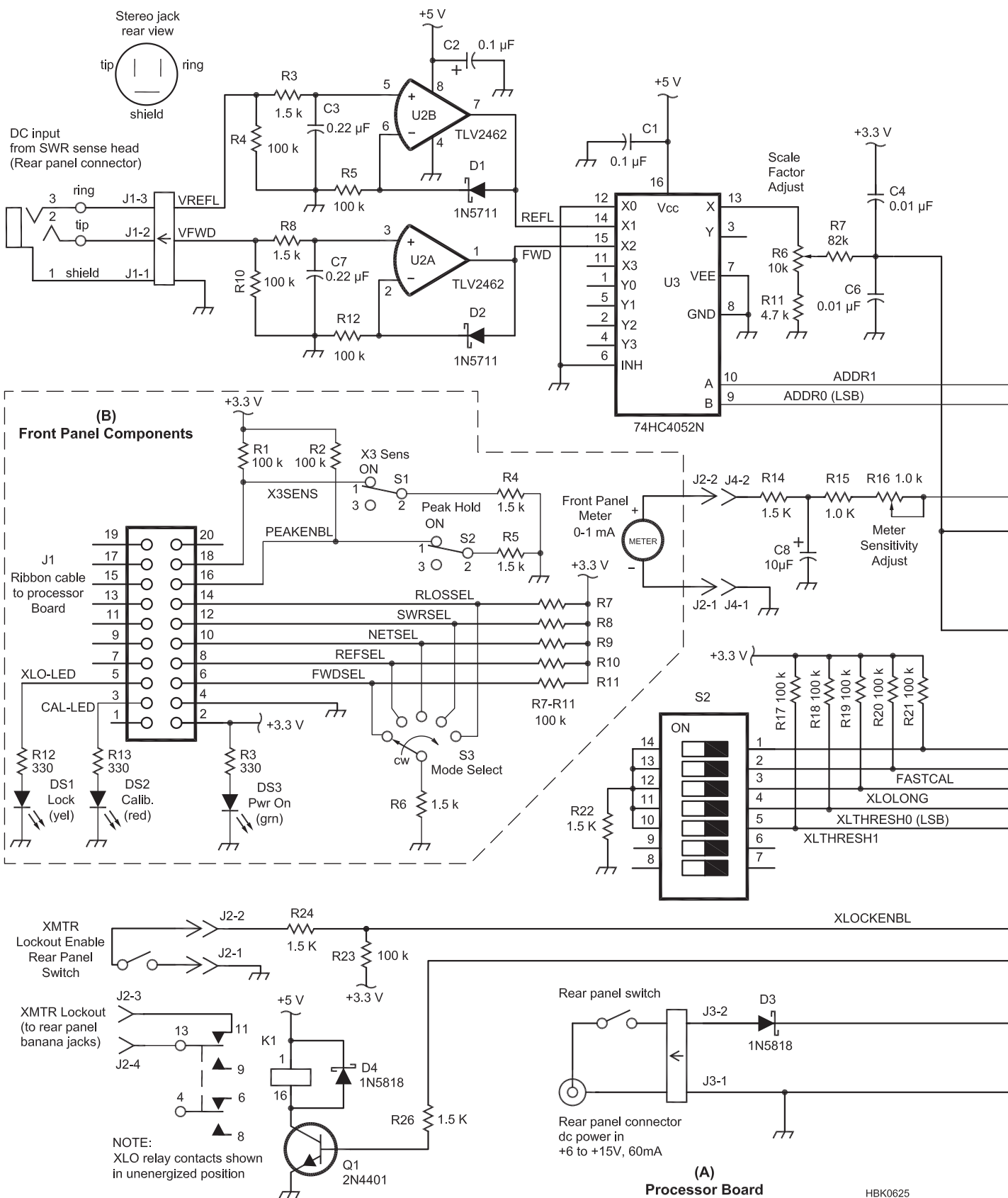

**Fig 24.9 — (A) Processor board schematic. All of the parts shown here, except for the rear panel components, are mounted on the Parallax Propeller Development Board. The parts within the dotted line are already installed at the factory, and are shown here only for completeness. (B) Front panel schematic. Switches and LEDs connect to the processor board via a 20-pin dual-row header, J1, and a ribbon cable. For convenience in wiring, the analog meter connects to the processor board by a separate 2-pin connector. (See Parts List on page 24.8.)**

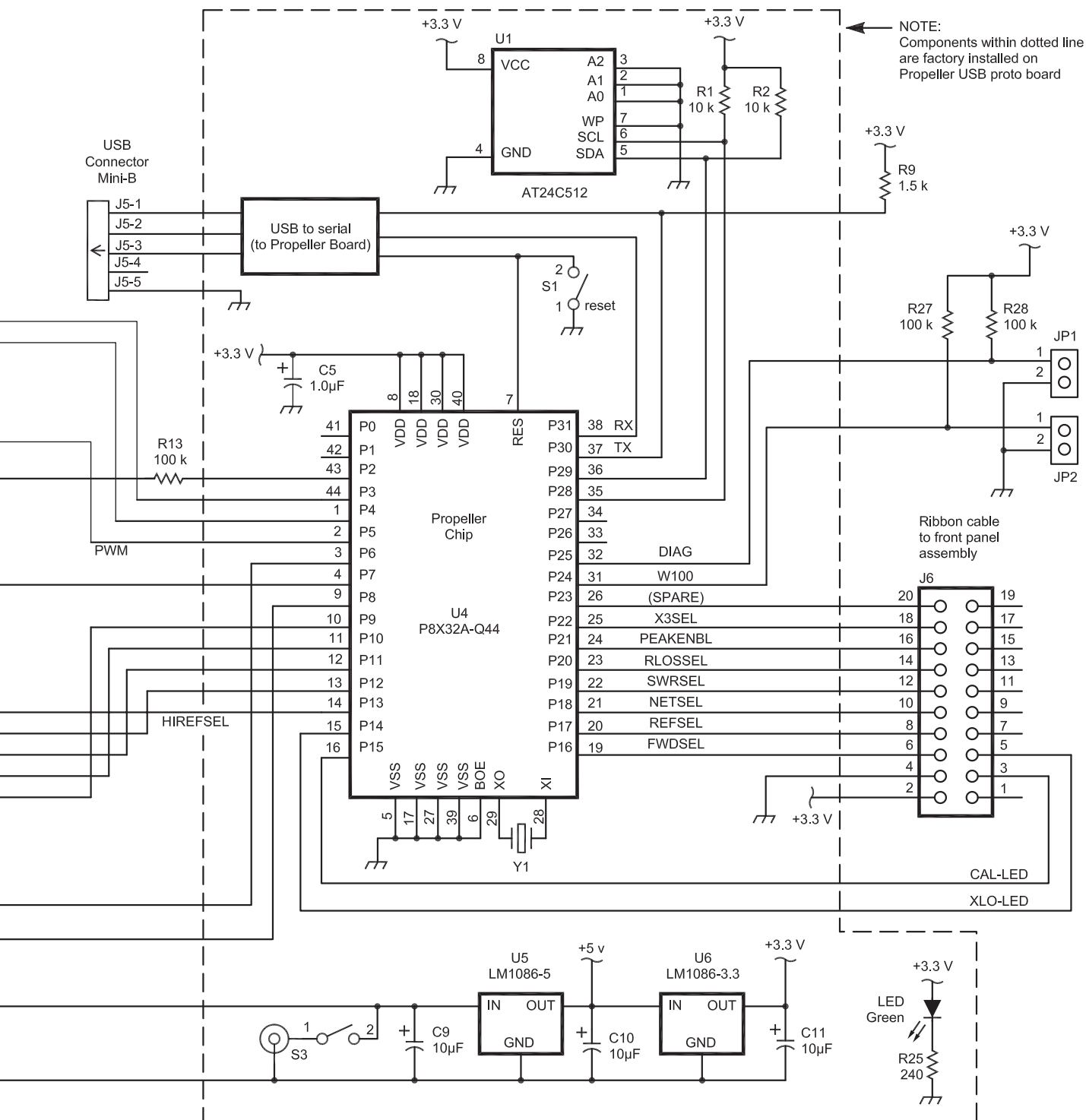

**(A)  
Processor Board Continued**

HBK0625



## Parts List for Figure 29 on previous 2 pages.

### Parts List – Processor Board

C3, C7 — 0.22  $\mu$ F ceramic capacitor  
 C1, C2 — 0.1  $\mu$ F ceramic capacitor  
 C4, C6 — 0.01  $\mu$ F ceramic capacitor  
 C8-C11 — 10  $\mu$ F, 16 V electrolytic capacitor  
 D1, D2 — 1N5711 Schottky diode  
 D3, D4 — 1N5818 Schottky diode  
 J6 — 20-pin dual row header  
 JP1, JP2 — single jumper header  
 K1 — SPDT 5 V relay  
 Q1 — 2N4401 NPN transistor  
 R3, R8, R9, R14, R22, R24, R26 — 1.5  $k\Omega$ ,  $\frac{1}{2}$  W, 5% resistor  
 R4, R5, R10, R12, R13, R17, R18, R19, R20, R21, R23, R27, R28 — 100  $k\Omega$ ,  $\frac{1}{2}$  W, 5% resistor  
 R6 — 10  $k\Omega$  trim pot, 25 turns  
 R7 — 82  $k\Omega$ ,  $\frac{1}{2}$  W, 5% resistor  
 R11 — 4.7  $k\Omega$ ,  $\frac{1}{2}$  W, 5% resistor  
 R15 — 1  $k\Omega$ ,  $\frac{1}{2}$  W, 5% resistor  
 R16 — 1.0  $k\Omega$  trim pot, 25 turns  
 S2 — 7-position DIP switch  
 U2 — TLV2462CP dual op amp  
 U3 — 74HC4052N dual 4-channel MUX  
 Parallax Proto USB Development Board, Part # 32812


### Parts List – Front Panel

DS1 — yellow LED  
 DS2 — red LED  
 DS3 — green LED  
 J1 — 20-pin dual row header  
 R1, R2, R7, R8, R9, R10, R11 — 100  $k\Omega$ ,  $\frac{1}{2}$  W, 5% resistor  
 R4, R5, R6 — 1.5  $k\Omega$ ,  $\frac{1}{2}$  W, 5% resistor  
 R3, R12, R13 — 330  $\Omega$ ,  $\frac{1}{2}$  W, 5% resistor  
 S1, S2 — SPST toggle switch  
 S3 — 5-position rotary switch  
 0-1 mA dc meter


balancing trimmers. The schematic is given in Fig 24.10 and the circuit is described in the article by J. Grebenkemper, KA3BLO, “The Tandem Match — an Accurate Directional Wattmeter,” *QST*, Jan 1987, pp 18-26 (also published in the 2009 and earlier editions of *The ARRL Handbook*).

The accuracy of this circuit can be greatly improved by taking care to match the diodes in the sensing head with the corresponding compensation diodes in the op amp input stages on the signal processor board (D1 and D2 in Fig 24.9A). The easiest way to do this is with the diode test function included on most utility digital multimeters which passes a small dc current through the diode being tested and displays the forward voltage drop. The high-frequency range can be extended by using surface-mount components in the sensing head.

There are two versions of the SWR sensing head. The QRP version has a maximum range of 10 W. The other can handle up to 100 W. The only difference between the two versions is the number of turns on the toroid transformers (see the parts list in Fig 24.10). The high frequency performance of the 100-W head at 50 MHz proved to be poorer than the 10-W unit. I attribute this to the added capacitance

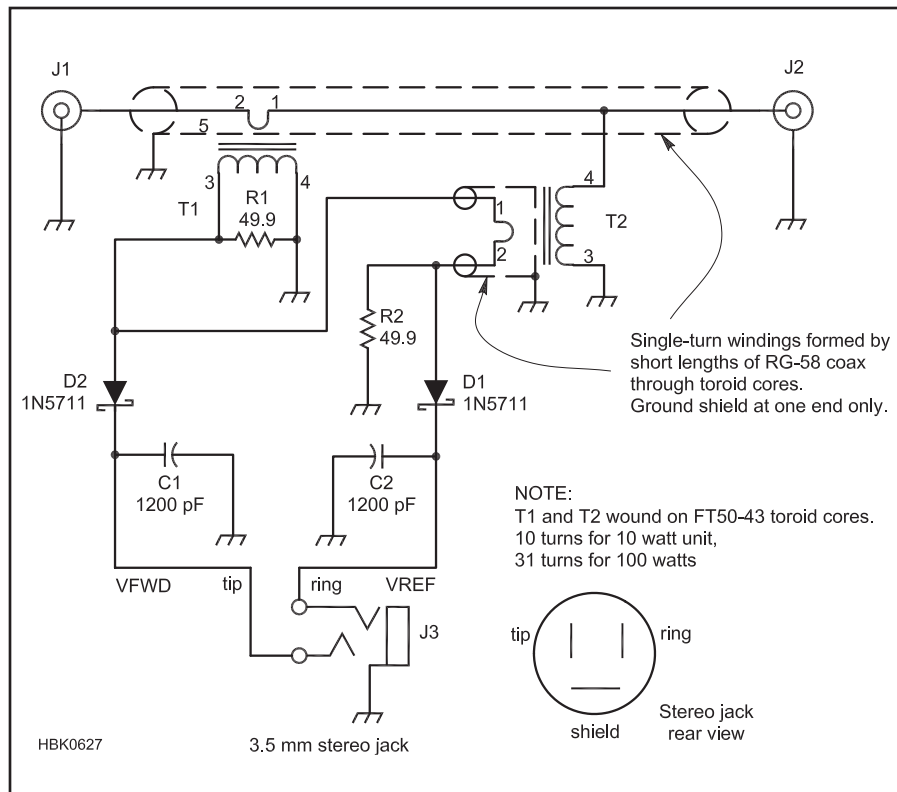

**Fig 24.10 — SWR sense head schematic.** All components except for the transformers are surface mount parts. R1 and R2 are size 1210, rated at  $\frac{1}{2}$  W. Transformers T1 and T2 are wound on FT50-43 ferrite toroid cores. For the 10-W sense head, use 10 turns of 24 AWG wire. For the 100-W head, use 31 turns.

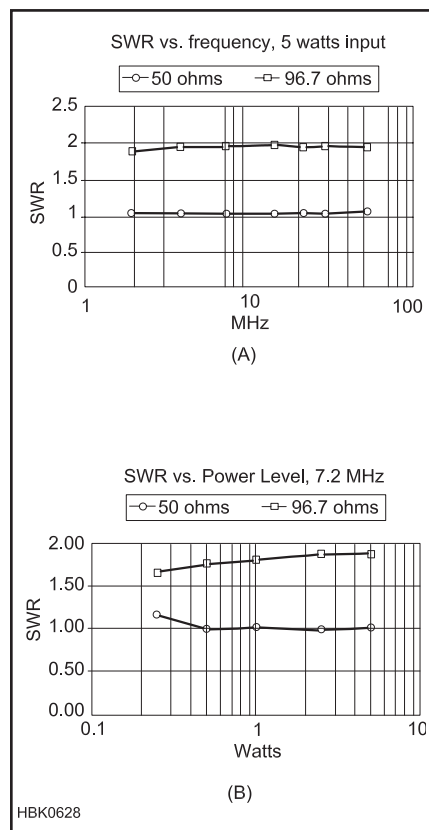

of the transformer windings (the higher power transformers have three times as many turns as the low-power ones).

The overall accuracy of the monitor compares fairly well to commercial devices. Fig 24.11A and 24.11B show performance data I took using dummy loads of 50 and 96.7  $\Omega$ . At five watts input, using the 10-W sensing head, the SWR readings were within 3% over a range of 1.8 to 30 MHz, and within 5% at 50 MHz. Fig 24.11B shows good accuracy down to 500 mW input (great for QRP rigs!) and is even usable down to 250 mW.

### 24.4.6 Software

For those who want to duplicate this project, the Spin language software listing, ready to program into the Parallax USB Development Board, is available in the package of

**Fig 24.11 — (A) SWR plotted against frequency, up to 50 MHz. (B) SWR as a function of input power level at a fixed frequency of 7.2 MHz.** The data shown here were taken using the 10-W sense head, with dummy loads measured at 50 and 96.7  $\Omega$ .



supporting files on the CD-ROM. There are also details of the subroutines handled by each of the Propeller cogs plus additional text and graphic files covering operation and features of the instrument.

As explained above, the organization of the Propeller into several peripheral processors (cogs) makes it easy to follow the program flow. The main program object (MAIN) runs in its own cog and is the first to be executed when power is applied (or whenever the chip is reset). Its first order of business is to set individual microprocessor pins to be inputs or outputs, as required.

Next, MAIN starts up three separate cogs

for (1) analog-to-digital conversion (the ADC3CH cog), (2) generating the pulse width modulated waveform to drive the analog panel meter (the PWM cog) and (3) communicating with the terminal via the USB port (the MONITOR cog). They run continuously, swapping data with the MAIN program by means of variables stored in memory. After these three cogs are started, the MAIN program object enters a loop, endlessly repeating the following steps:

- 1) Read forward and reflected amplitudes and SWR data generated by the ADC3CH object.
- 2) Calculate forward power, percent re-

flected power, net power, SWR and return loss in decibels.

3) Display the quantity selected by the front panel switch on the panel meter using the PWM object.

4) Convert power levels, SWR and return loss information to ASCII strings and send them to the MONITOR object, which writes to the USB port.

This is a shining example of building on the accomplishments of others who have made their work freely available. Without such an extensive library of pre-tested routines on hand, the author probably would never have even started this project.

## 24.3 A 160- and 80-Meter Matching Network for Your 43-Foot Vertical

Many amateurs are using 43-ft vertical antennas for multiband operation. These antennas have higher radiation resistance than shorter verticals, which minimizes ground losses. This is especially important when you have an electrically short antenna — a characteristic of even a 43-ft antenna on 160 and 80 meters.

When fed with a 1:4 unun (unbalanced-to-unbalanced transformer), a 43-ft antenna has a reasonable compromise SWR on 60-10 meters, which means that cable and unun losses are pretty much negligible on these bands. Performance on 160 meters, and to a lesser extent on 80 meters, is not as good unless you provide matching right at the antenna. The high capacitive reactance and low radiation resistance of a 43-ft antenna on 160 and 80 meters make the mismatch so bad that it is almost impossible to match from your shack if you are using low-loss coax. If you can match the antenna system from your shack, you will lose a lot of power in your coax and unun because of the very bad mismatch at the antenna. Phil Salas, AD5X, describes two impedance matching devices for use with 43-ft verticals designed to significantly reduce SWR-related losses and to “help out” inside tuners on 160 and 80 meters.

### THE MATCHING REQUIREMENT

Antenna analyzer measurements of the author’s 43-ft vertical antenna indicate a capacitive reactance of about  $580\ \Omega$  on 160 meters. This value will vary with different kinds of 43-ft verticals, proximity to other objects and other factors unique to each installation but is usually in the 550-650  $\Omega$  range. With this amount of capacitive reactance, approximately  $50\ \mu\text{H}$  of inductance is


needed to resonate the antenna. On 80 meters, approximately  $9\ \mu\text{H}$  is needed. A  $50\ \mu\text{H}$  high-Q inductor is large, but a toroidal inductor will be more compact.

**Fig 24.12** shows the circuit of a compact design that handles 1500 W SSB or CW on 80 and 160 meters. **Table 24.2** lists the necessary parts. The inductor consists of 35 turns of #14 AWG solid copper insulated house wiring wound on a T400A-2 toroid core, with the feed tapped 2 turns from the ground end for 80 meters, and 3 turns from the ground end for 160 meters. Start with 38 turns and then remove turns as necessary to get the network to resonate where you want it in the 160 meter band (more on this later).

The toroid assembly fits in a  $6 \times 6 \times 4$ -inch NEMA enclosure. The assembly is secured with a 2.5-inch long #10 screw and associated hardware along with a  $2 \times 4$  inch piece of unplated fiberglass PC board material (**Fig 24.13**). Before mounting the toroid, prepare it by scraping the insulation off the outside of the wire at turns 2, 3 and 11-13. Because of the high voltages possible with 1500 W (especially on 160 meters), wrap

the toroid with two layers of 3M #27 glass-cloth electrical tape for added insulation between the wire and the toroid core.

To select between 160- and 80-meter operation, the appropriate connections are made with external jumpers across binding

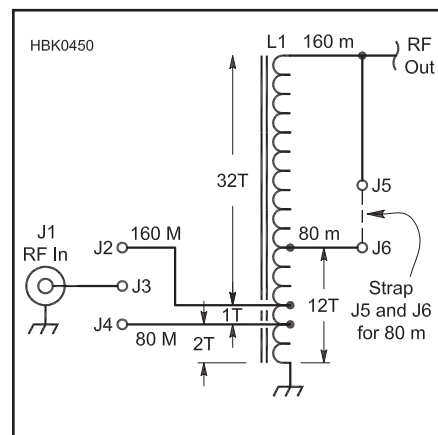

**Fig 24.12 — 160/80-meter impedance matching network for use with a 43-ft vertical. See Table 24.2 for a parts list.**

**Table 24.2**

**Parts List: 160/80-Meter Impedance Matching Assembly**

Qty	Description	Source/Part Number
1	6x6x4 inch NEMA enclosure	Hardware store/home center
1	T400A-2 powdered iron toroid (L1)	Amidon T400A-2
1	SO-239 connector (J1)	Mouser 601-25-7350
4	Black binding post (J2, J4-J6)	Mouser 164-R126B-EX
1	Red binding post (J3)	Mouser 164-R126R-EX
4	Banana plug	Mouser 174-R802-EX
1 roll	3M #27 glass tape (for L1)	Hardware store/home center

Misc: #14 AWG house wiring, stainless steel hardware.

posts as shown in **Fig 24.14**. Stainless steel #8 hardware (screws, washers, lockwashers, nuts) is used for the matching unit ground and RF output. Internal to the matching unit, a 2-inch-wide strip of aluminum duct repair tape makes a good low-impedance ground between the coax connector and the ground screw on the bottom of the case. Finally, use #14 AWG stranded insulated wire for all internal connections.

### TUNING THE MATCHING NETWORK TO RESONANCE

Your particular installation will almost certainly require you to change the resonant frequency of the matching network. This is because there will be variations of the antenna impedance based on your particular installation and desired operating frequency range. The design is such that the overall inductance is too large for 160 meters, so the network should resonate at or below the lower band edge. Therefore, you will need to remove one or more of the upper inductor turns to resonate the network for the desired frequency on 160 meters. To do this, first solder wires from the turn 2 and 3 tap points on the coil to the two outer binding posts by the RF IN connector. The input tap points tend to be fairly non-critical and will probably always be the same for all installations.

Now solder a short wire from the RF IN center pin to the middle binding post. Next, externally jumper the middle binding post to the 160 meter binding post (turn 3). Connect the matching assembly to the base of your

43-ft vertical and use an antenna analyzer to find the minimum SWR point on 160 meters. If the resonant frequency is too low, remove a turn of wire and measure again. You should see a 50 kHz upward move in frequency per turn of wire removed.


When you have reached the desired resonant point on 160 meters, it is time to move to 80 meters. Externally jumper the input tap middle binding post to the 80-meter binding post (turn 2), and use a clip lead to short from the top of the coil to about turn 12. Again, find the frequency where minimum SWR occurs. Move the tap point up or down until you reach the desired resonance point. Solder a wire from this tap point to one of the binding posts. Solder another wire from the top of the coil to another binding post. Now you will be able to externally jumper these binding posts to go from 160 to 80 meters.

**Fig 24.15** shows the author's final results for 160 and 80 meters as measured with an antenna analyzer connected directly to the matching network input at the base of the antenna. With resonance set for the CW end of these bands, the 2:1 SWR bandwidth on 160 meters is about 50 kHz and about 150 kHz on 80 meters. Even a 3:1 SWR on


these bands results in negligible SWR-related cable losses and is easily matched with an in-shack tuner.

### OPERATION

Using the matching unit is simple. Just disconnect your normal unun when you want to operate on 160 or 80 meters and connect this matching unit to the base of the antenna. Select either 160 or 80 meters with the external straps. You can connect both the unun and this matching unit to the antenna at the same time, and just leave off the ground wire from the unit that is not used. The matching unit connected to the base of a 43-ft vertical is shown in **Fig 24.16**.

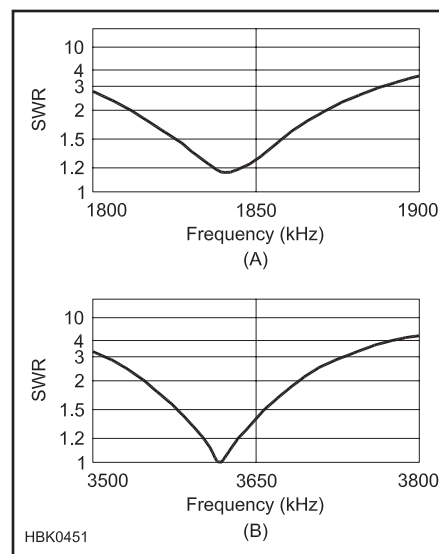

**Fig 24.15** — Measured at the antenna base, the 2:1 SWR bandwidth is about 50 kHz for 160 meters and 150 kHz for 80 meters.

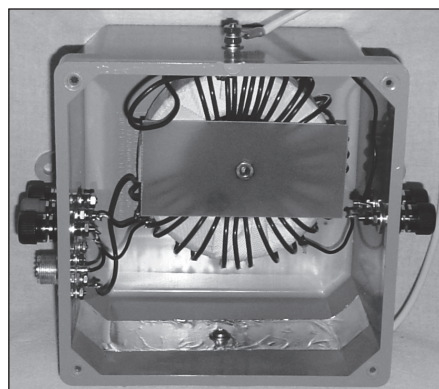

**Fig 24.13** — Mounting details of the toroidal inductor for the 160/80-meters matching unit. The input side of the enclosure is on the left. Coax to the station connects to the RF IN SO-239, and a strap between the center binding post and one of the outer posts selects the input tap for operation on 160 or 80 meters. On the right side, a jumper between the two binding posts shorts a section of the coil for 80-meter operation. The RF OUT connection to the base of the antenna is made with via the #8 machine screw and hardware at the top, and the ground connection is on the bottom.



(A)



(B)

**Fig 24.14** — Binding posts are used for jumpers to select 160 or 80 meter operation.



**Fig 24.16** — The finished matching unit at the base of the author's 43-ft antenna (strapped for 80 meter operation).

## 24.4 Switching the Matching Network for Your 43-Foot Vertical

Another project in this chapter describes a simple 160 and 80 meter impedance matching network for installation at the base of a 43-ft vertical antenna. While that unit is very effective and inexpensive to build, it is also a little inconvenient in that you must connect it when it is needed, and you must also manually enable 160 or 80 meter operation using jumpers. Phil Salas, AD5X, enhances the original design with a more versatile matching assembly that can be controlled remotely for operation on all bands.

## FIRST — A WORD ABOUT RF VOLTAGES

This unit uses relays for selecting the different bands, so a discussion of RF voltages is appropriate. RF voltages at the base of an untuned vertical can be quite high. As the antenna becomes shorter, the capacitive reactance becomes higher and so the resultant voltage drop across the combination of reactance and radiation resistance increases. With the 43-ft vertical, the worst-case situation will occur on 160 meters where the capacitive reactance is approximately  $600\ \Omega$ . The radiation resistance is approximately  $3\ \Omega$ .

With a perfect ground (no ground loss) and 1500 W of power properly matched to the antenna, peak RF voltage works out to about 19,000 V<sub>pk</sub>:

$$I = \sqrt{1500 \text{ W} / 3 \Omega} = 22.4 \text{ A}$$

$$|Z| = \sqrt{3^2 + 600^2} = 600 \, \Omega$$

$$V_{\text{RMS}} = 22.4 \times 600 = 13,440 \text{ V}$$

$$V_{pk} = 13,440 \times 1.414 = 19,004 \text{ V}$$

Very few hams have a ground system that is lossless. With a ground loss of  $10\ \Omega$  (better than most hams have), it works out to about  $9100\text{ V}_{\text{pk}}$ . With the author's 600-W amplifier, assuming a ground loss of  $10\ \Omega$ , it's about  $5800\text{ V}_{\text{pk}}$ .

The author experimented with two different relays from Array Solutions. The RF-10 DPDT relay has 1.7 kV<sub>pk</sub> contact-to-contact and 3.1 kV<sub>pk</sub> contact-to-coil voltage breakdown ratings. This relay proved to be a good solution for up to about 500 W on 160 meters when the two sets of contacts are put in series. The second relay is the RF-3PDT-15 which has 3.1 kV<sub>pk</sub> contact-to-contact and 5.3 kV<sub>pk</sub> contact-to-coil voltage breakdown ratings. This relay has nearly twice the contact breakdown rating of the RF-10, and it's 3PDT so an additional set of contacts can be put in series to increase the breakdown voltage. This relay can be used in a full legal limit application if applied properly in the circuit (more on this later).

Depending on your power level and ground losses, the less expensive and smaller RF-10 may be all you need. Make the calculations to determine which relay is more appropriate for you. If you look for alternative relays, pay attention to the breakdown voltage rating; it's hard to find relays with suitable ratings for this application. The Array Solutions relays have 30 A contacts, but 15 A or more should be sufficient.


## THE ALL-BAND MATCHING SOLUTION

As explained in the companion project describing a simple matching network, when fed with a 1:4 unun (unbalanced-to-unbalanced transformer), a 43-ft antenna has a reasonable compromise SWR on 60-10 meters. The antenna requires approximately 50  $\mu\text{H}$  of inductance to resonate on 160 meters and

9  $\mu\text{H}$  on 80 meters. For convenient all-band operation from the shack, the solution shown in **Fig 24.17** uses two relays to switch in the unun for 60-10 meter operation or the appropriate inductance for 160 and 80 meters. The unit will handle up to 1500 W from 160-10 meters.

Relay control requires inputs of 0 V, +12 V dc or -12 V dc. The matching unit operates as follows:

- With no control voltage applied, the 1:4 unun is connected to the antenna for 60-10 meter operation, and the inductor is disconnected, so the original antenna compromise SWR on these bands is preserved.
- With +12 V applied for 80-meter operation, K1 and K2 close. Contact K1C connects the unun secondary to L1 through K2C at the 200  $\Omega$  point (6 turns from the ground end). Contacts K2A and K2B short out the top part

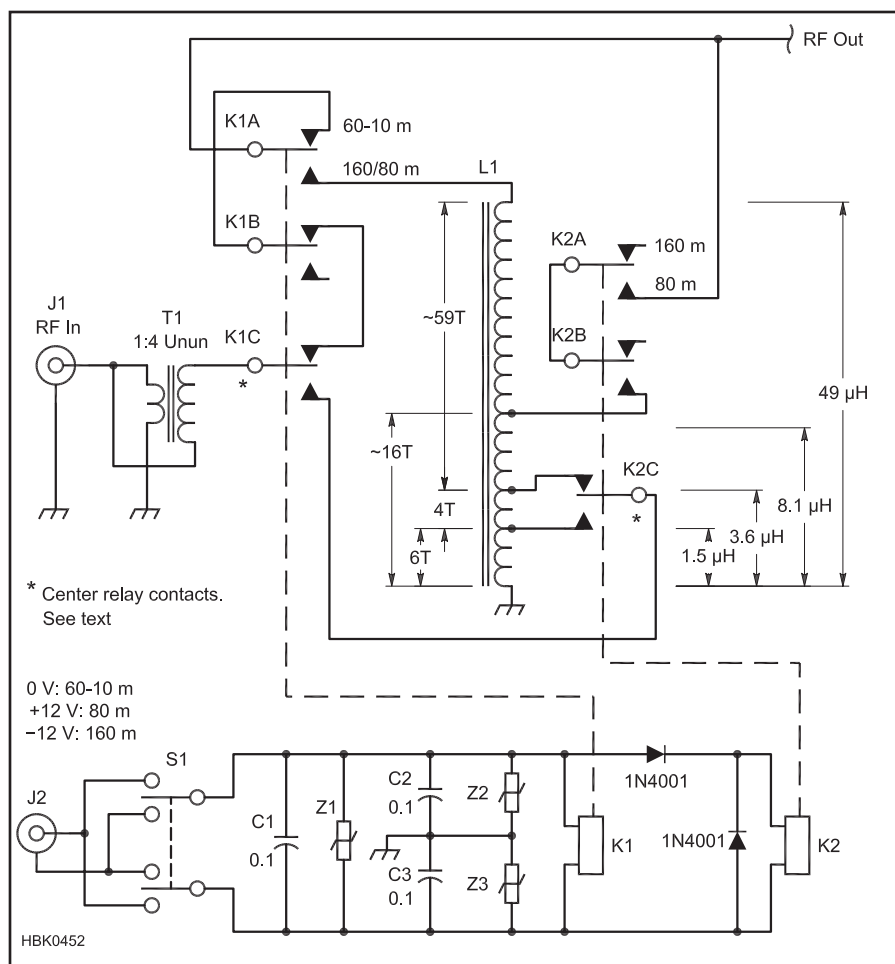

**Fig 24.17 — This switched impedance matching network for use with a 43-ft vertical allows operation on 160-10 meters and is controlled from the station operating position. See Table 24.3 for a parts list.**




of L1 (about 16 turns from the ground end), resonating the antenna on 80 meters.

•When the voltage is reversed ( $-12\text{ V}$ ) for 160-meter operation, K1 stays closed but K2 opens. K2C now connects the unun secondary to L1 at the  $200\ \Omega$  point for 160 meters (10 turns from the ground end). Contacts K2A and K2B open, removing the short and allowing the entire coil to be used to resonate the antenna on 160 meters.

Connecting the unun to L1 at the  $200\ \Omega$  point keeps the unun secondary voltage reasonable, and the feed line and unun losses very low as well.

## CONSTRUCTION

**Fig 24.18** shows the layout. The matching unit is built in  $8 \times 8 \times 4$ -inch NEMA weatherproof box available from most home centers. The author used an MFJ 404-0669 air-wound coil, and this box is too small to fit the entire inductor length needed. The inductor is split into two pieces; the long section consists of 61 turns, and the short section consists of 12 turns. As drawn in the schematic, the longer coil section is at the “bottom” (one end connects to ground), while the shorter coil is at the “top” (one end connects to RF OUT). If you have room for a larger box, a  $12 \times 12$

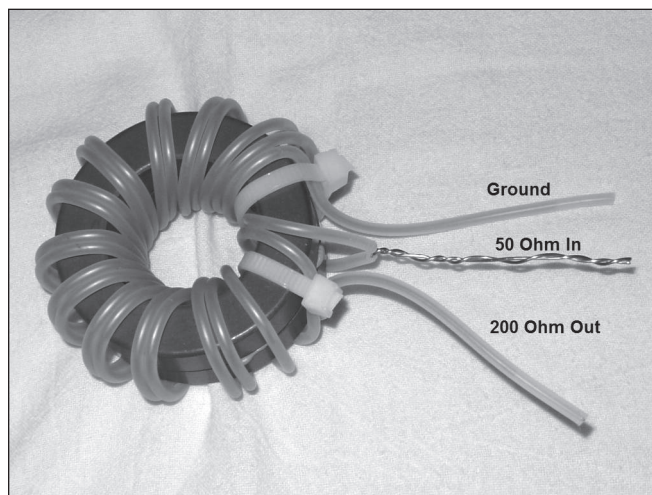

**Fig 24.19 —** Connections for a voltage unun (MFJ 10-10989D shown).

$\times 4$ -inch NEMA box fits the full inductor length without cutting.

Two Array Solutions RF-3PDT-15 relays are mounted to the case next to each other in the upper center. These are enclosed relays with all connections on one side, making for easy assembly. The  $2.1 \times 5.5\text{ mm}$  dc power jack and SO-239 RF IN connector are in the upper left corner. The MOVs and bypass capacitors for the control line are mounted on a terminal strip near the power connector.

The unun is mounted to the side of the enclosure using a machine screw and a piece of PC board material with the copper removed. The antenna is unbalanced, so a current balun or voltage unun (*not* a voltage balun) is typically used. A voltage unun should be wired as shown in **Fig 24.19**.


All internal wiring consists of insulated #14 AWG stranded wire. Attach the wires to the coil tap points using the MFJ coil clips called out in the parts list. (You can solder the

wires directly to the coil, but this is difficult because of the size of the coil wire and the spacing of the turns.) Use #8 stainless steel screws, washers, lock-washers and nuts for coil mounting, and for the ground and RF OUT (antenna feed) terminals. **Table 24.3** lists the parts and part sources.

## Relay Connections


As discussed earlier, the voltage across the full coil can be very high on 160 meters. Connecting the relay contacts in series as shown in the schematic increases the overall breakdown voltage. Also, the tap points on the inductor provide additional voltage-above-ground, which helps with the overall breakdown voltage.

The main concern is with the contact-to-

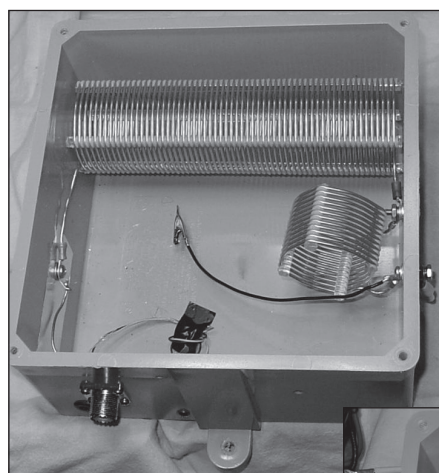


(A)

**Fig 24.18 —** Inside the enclosure. At A, the air-wound inductor has been cut into two pieces (see text) and mounted. The wire from the shorter piece will attach to the RF OUT terminal. At B, the other components have been added. The unun is mounted on the left side of the case. The relays are at the top center, and the MOVs and bypass capacitors are mounted on a terminal strip at the upper left, next to the RF IN and dc control connectors.

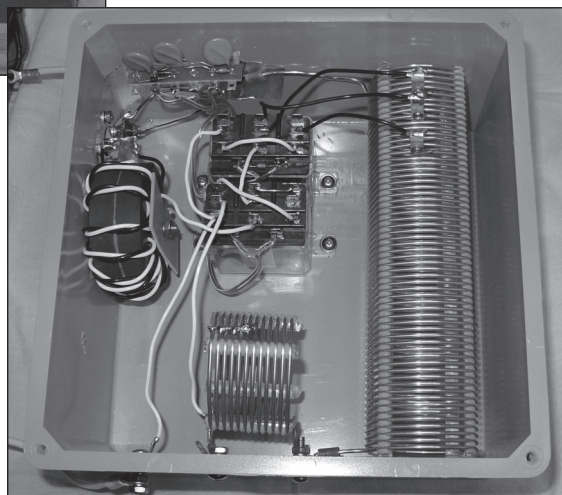

(B)

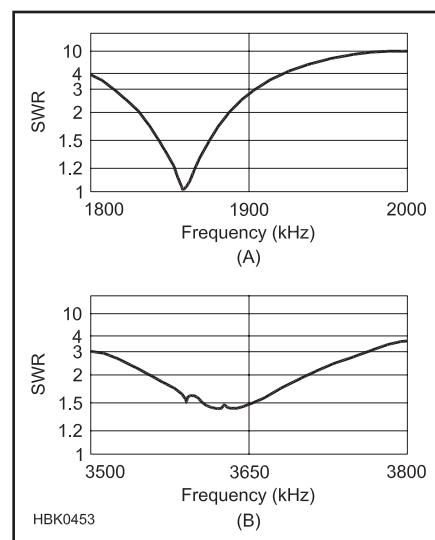

**Fig 24.20 —** Measured at the antenna base, the 2:1 SWR bandwidth is about 50 kHz for 160 meters and 150 kHz for 80 meters.

**Table 24.3****Parts List: Switchable 160-10 Meter Impedance Matching Assembly**

Qty	Description	Source/Part Number
1	8x8x4-inch NEMA box	Hardware store/home center
1	2-inch diam x 12-inch long coil, air wound with #12 AWG wire (79 $\mu$ H, L1)	MFJ 404-0669
2	3PDT power relay (K1, K1)	Array Solutions RF-3PDT-15
4	Coil clips	MFJ 755-4001
1	SO-239 connector (J1)	MFJ-7721
1	1:4 unun, 1.5 kW rating (T1)	MFJ 10-10989D
1	2.1x5.5 mm dc jack (J2)	Mouser 163-1060-EX
3	18 V dc MOV (Z1-Z3)	Mouser 576-V22ZA2P
3	0.1 $\mu$ F capacitor (C1-C3)	Mouser 581-SR215C104KAR
1	6-lug terminal strip	Mouser 158-1006
5	Micro-gator clips	Mouser 548-34
5	Test clips	Mouser 13AC130
1	2x1.38x0.8-inch plastic box (for control switch)	All Electronics 1551-GBK
1	DPDT center-off switch (S1)	All Electronics MTS-12
1	12-V dc, 1-A wall transformer	All Electronics DCTX-1218

Misc: #14 AWG house wiring, stainless steel hardware.

coil breakdown rating of 5.3 kV peak. The outer contacts are connected via insulated internal wires that are well separated from the coil by 0.1-0.2 inch. The problem is with the common wire for the center contacts, which is in contact with the coil. While the coil and common wire are both insulated, there is no air gap separation between them; this close proximity is what determines the relay breakdown voltage rating. Wired as shown in Fig 24.17, the center relay contacts are used for the lowest voltage points.

The switched control voltage input uses

a 12-V, 1-A wall transformer supply. It's a good idea to keep the  $\pm 12$  V control voltages separate and isolated from the regular station power supply to eliminate any possibility of shorting the main power supply when the control voltage polarity is flipped. The switching is easily done with a DPDT center-off switch (S1).

### MATCHING NETWORK RESONANCE

Some initial adjustment is required to tune the resonant frequency of the matching network to account for variations in the antenna impedance based on your particular installation and desired operating frequency range. The overall starting inductance is too large for 160 meters, so the network will resonate at or below the lower band edge. Therefore, you can simply short one or more turns at the upper (RF OUT) end of the inductor to tune the network higher in frequency.

For the initial adjustments, don't connect the wire leads that attach between the relay contacts and the tap points on the coil. Instead, build short jumpers using the

test clips and micro clips (perfect for the coil turn taps) called out in the parts list, and attach these between the relay contacts and coil using the suggested tap points shown on the schematic.

Next, connect the matching assembly to the base of your 43-ft vertical, enable 160 meter operation by applying  $-12$  V dc and jumper turns from the RF OUT end of the inductor with a short clip lead until you find the desired 160 meter resonance point. Next, move the 160 meter relay tap point (from the unun secondary through K2C) until you get minimum SWR. (The starting point is 10 turns from the ground end.) Now permanently short the inductor turns by soldering a piece of #16 AWG buss wire across them. As shown in the photos, the author needed to short six turns (on the short coil).


Next apply  $+12$  V to the relay assembly to enable 80-meter operation. Select the coil shorting point (from K2B — start 16 turns from the ground end) for your desired resonant frequency. Then adjust the tap point (from K2C — start 6 turns from ground) for best SWR. Finally remove the test clips leads, attach the coil clips, and solder wires between the coil clips and relay.

Fig 24.20 shows the results for 160 and 80 meters as measured with an antenna analyzer connected directly to the matching network input at the base of the author's antenna. With resonance set for the CW end of these bands, the 2:1 SWR bandwidth on 160 meters is about 50 kHz and about 150 kHz on 80 meters. Even a 3:1 SWR on these bands results in negligible SWR-related cable losses and is easily matched with an in-shack tuner.

### OPERATION

Operation of this matching unit couldn't be simpler. When no control voltage is applied, the unun is connected and the antenna functions as it always has on 60-10 meters. For 80-meter operation, apply  $+12$  V dc, and for 160-meter operation apply  $-12$  V dc. The matching unit connected to the base of the author's 43-ft vertical is shown in Fig 24.21.

The matching network discussed in this article will permit very effective operation of your 43-ft vertical on all bands from 160-10 meters. Feel free to experiment a little. You might prefer to use the toroid from the basic matching network in the companion project instead of the air-core inductor. And if you are not running more than about 500 W, the less expensive RF-10 relays are all you need.

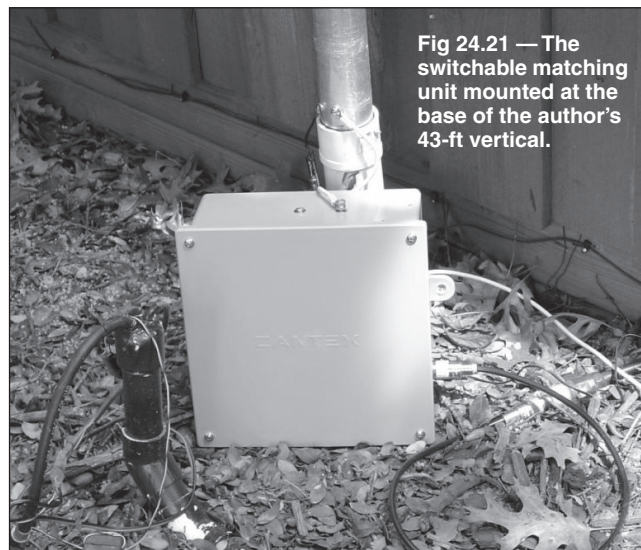

**Fig 24.21 — The switchable matching unit mounted at the base of the author's 43-ft vertical.**



# 24.5 An External Automatic Antenna Switch for Use With Yaesu or ICOM Radios

This antenna-switching-control project involves a combination of ideas from several earlier published articles.<sup>1,2,3</sup> This system was designed to mount the antenna relay box outside the shack, such as on a tower. With this arrangement, only a single antenna feed line needs to be brought into the shack. **Fig 24.22** shows the control unit and relay box, designed and built by Joe Garcia, NJ1Q. Either an ICOM or Yaesu HF radio will automatically select the proper antenna. In addition, a manual switch can override the ICOM automatic selection. That feature also provides a way to use the antenna with other radios. The antenna switch is not a two-radio switch, though. It will only work with one radio at a time.

Many builders may want to use only the ICOM or only the Yaesu portion of the interface circuitry, depending on the brand of radio they own. The project is a “hacker’s dream.” It can be built in a variety of forms, with the only limitations being the builder’s imagination.

## CIRCUIT DESCRIPTION

**Fig 24.23** is a block diagram of the complete system. An ICOM or Yaesu HF radio connects to the appropriate decoder via the accessory connector on the back of the radio. Some other modern rigs have an accessory connector used for automatic bandswitching of amplifiers, tuners and other equipment. For example, Ten-Tec radios apply a 10 to 14-V dc signal to pins on the DB-25 interface connector for the various bands. Other radios use particular voltages on one of the accessory-connector pins to indicate the selected band. Check the owner’s manual of your radio for specific information, or contact the manufacturer’s service department for more details. You may be able to adapt the ideas presented in this project for use with other radios.

A single length of coax and a multiconduc-

tor control cable run from the rig and decoder/control box to the remotely located switch unit. The remote relay box is equipped with SO-239 connectors for the input as well as the output to each antenna. You can use any type of connectors, though.

ICOM radios use an 8-V reference and a voltage divider system to provide a stepped band-data output voltage. **Table 24.4** shows the output voltage at the accessory socket

when the radio is switched to the various bands. Notice that seven voltage steps can be used to select different antennas. The ICOM accessory connector pin assignments needed for this project are:

- Pin 1 +8 V reference
  - Pin 2 Ground
  - Pin 4 Band signal voltage
  - Pin 7 +12 (13.8) V supply
- Yaesu radios provide the band information

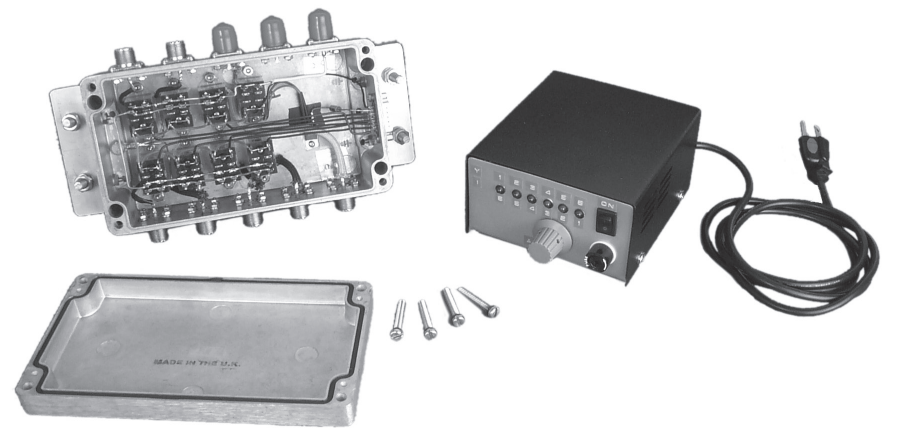


Fig 24.22 — Automatic antenna switch relay box (left) and control box (right).

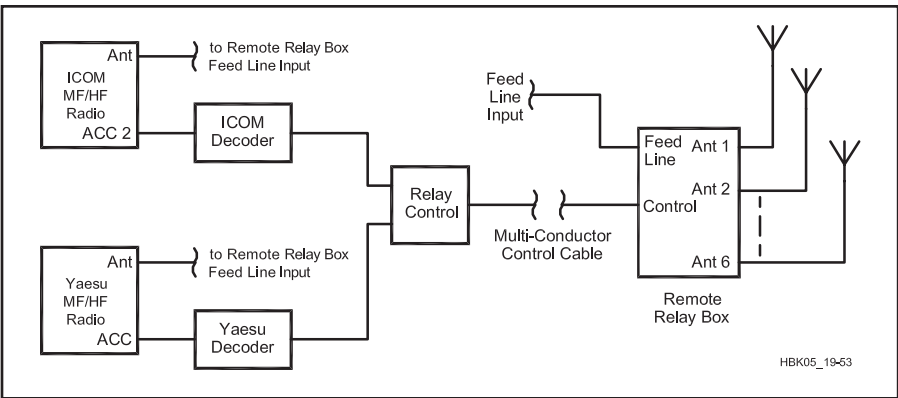


Fig 24.23 — Block diagram of the remotely controlled automatic antenna switch.


**Table 24.4**  
ICOM Accessory Connector Output Voltages By Band

Band (MHz)	Output Voltage
1.8	7 – 8.0
3.5	6 – 6.5
7	5 – 5.5
14	4 – 4.5
18, 21	3 – 3.5
24, 28	2 – 2.5
10	0 – 1.2

**Note:** The voltage step between bands is not constant, but close to 1.0 V, and the 10-MHz band is not in sequence with the others.

**Table 24.5**  
Yaesu Band Data Voltage Output (BCD)

Band	A (1)	B (2)	C (4)	D (8)	(BCD Equiv.)
1.8	5V	0V	0V	0V	1
3.5	0V	5V	0V	0V	2
7.0	5V	5V	0V	0V	3
10.1	0V	0V	5V	0V	4
14	5V	0V	5V	0V	5
18.068	0V	5V	5V	0V	6
21	5V	5V	5V	0V	7
24.89	0V	0V	0V	5V	8
28	5V	0V	0V	5V	9

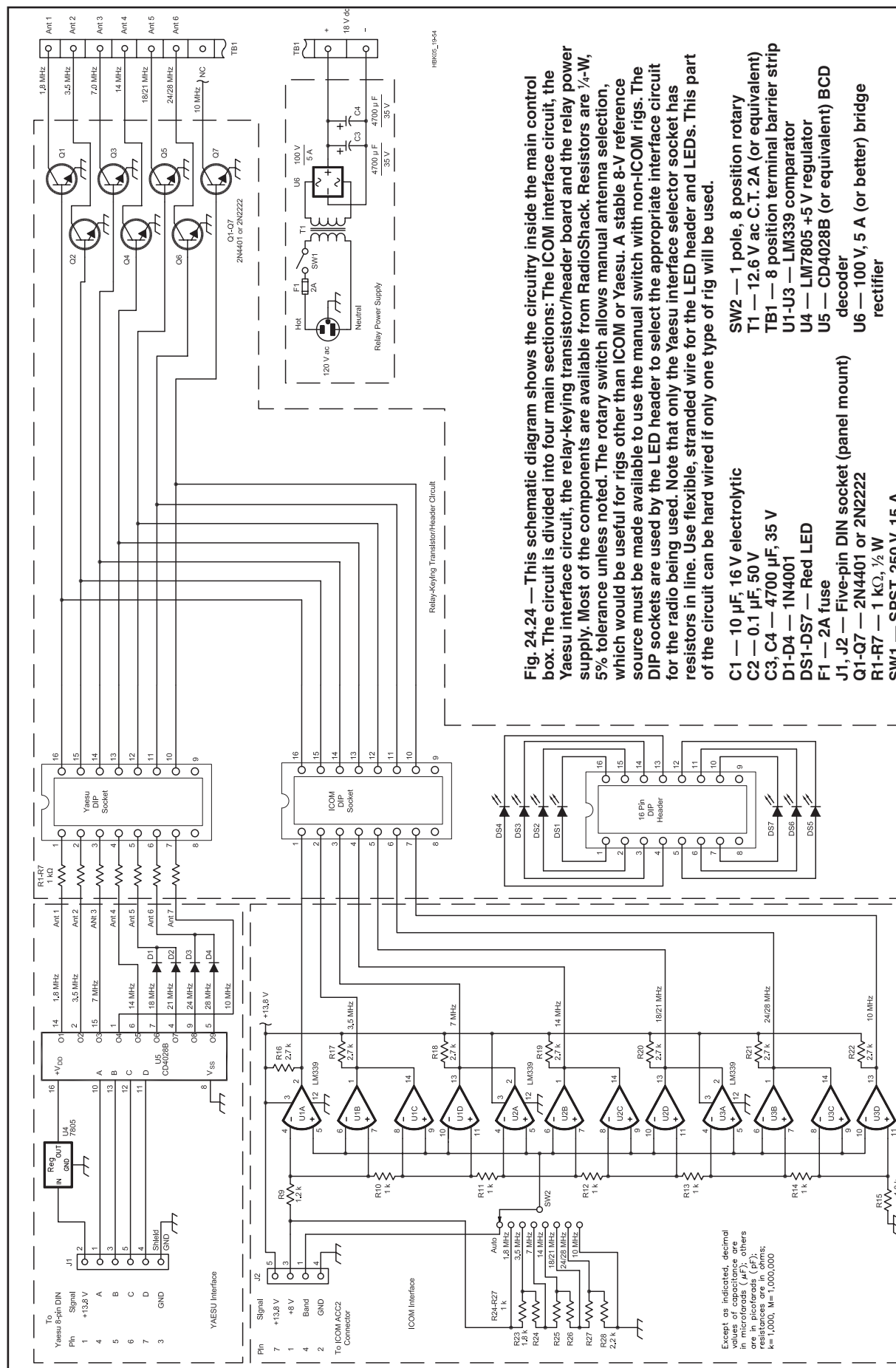

as binary coded decimal (BCD) data on four lines. Nine different BCD values allow you to select a different antenna for each of the MF/HF bands. **Table 24.5** shows the BCD data from Yaesu radios for the various bands. The Yaesu 8-pin DIN accessory connector pin assignments needed for this project are:

Pin 1	+12 (13.8) V supply
Pin 3	Ground
Pin 4	Band Data A
Pin 5	Band Data B
Pin 6	Band Data C
Pin 7	Band Data D

**Fig 24.24** is the schematic diagram for the control box. We will discuss each part of the control circuit later in this description. First, let's turn our attention to the external antenna box.

### EXTERNAL ANTENNA BOX

Only the number of control lines going out to the relay box limits the number of antennas this relay box will switch. The unit shown in the photos has 10 SO-239 connectors, to switch the common feed line to any of nine antennas. Many hams will use an eight-conductor rotator cable (such as Belden 9405) to the relay box. Using eight wires, we can control seven relays (six for antennas and one to ground the feed line for lightning protection) plus the relay coil power supply and ground lead. The photos show eight relays, and the box can be expanded further if desired. There is also a connector for power and control lines. Use of a DB-15 allows for the addition of more relays and control lines later. A DB-9 connector would be suitable for use with the eight-conductor control cable, or you may wish to use a weatherproof connector. **Fig 24.25** shows the relay box schematic diagram.

Since the box will be located outside, use a weatherproof metal box — a Hammond Manufacturing, type 1590Z150, watertight aluminum box is shown. It's about 8.5×4.25×3.125 inches. This is a rather hefty box, meant to be exposed to years of various weather conditions. You can, however, use almost anything.

The coax connectors are mounted so each particular antenna connector is close to the relay, without too much crowding. For added weather protection (and conductivity), apply Penetrox to the connector flange mount, including the threads of the mounting screws. On the power/control line connector, use Coax Seal or other flexible cable sealant.


The aluminum angle stock on either side of the box is for mounting to a tower leg. The U-bolts should be of the proper size to fit the tower leg. They should also be galvanized or made of stainless steel.

### ANTENNA RELAYS

One of the more difficult parts of this project was the modification of the relays (DPDT Omron LY2F-DC12). To improve isolation, the moveable contacts (armature) are wired in parallel and the connecting wire is routed through a hole in the relay case.

Remove the relay from its plastic case. Unsolder and remove the small wires from the armatures. Carefully solder a jumper across


the armature lugs with #20 solid copper. Then solder a piece of very flexible wire (such as braid from RG-58 cable) to either armature lug. Obviously, the location of the wire depends on which side you wish to connect the SO-239. You will also need to make a hole in the plastic case that is large enough to accommodate the armature wire without placing any strain on the free movement of the armature. Slip a length of insulating tubing

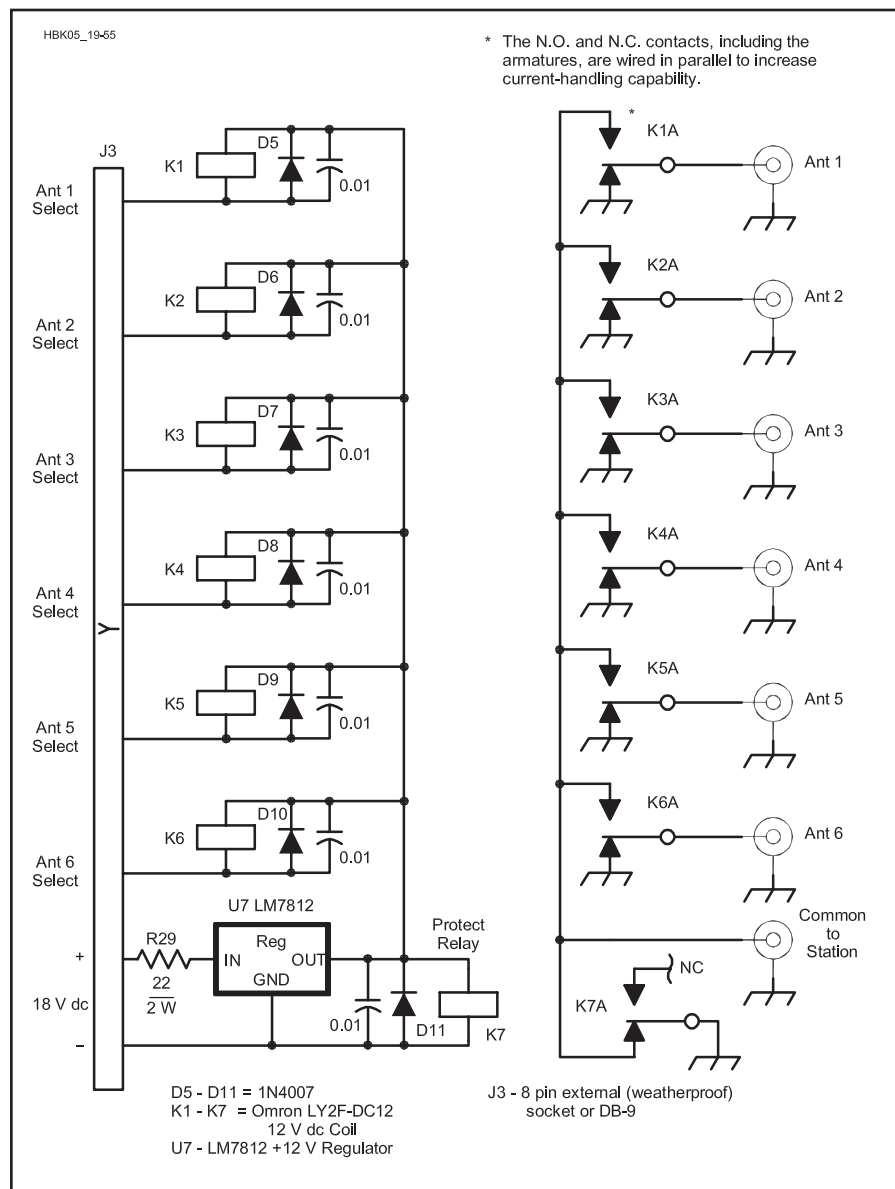


**Fig 24.25— The schematic diagram for the external antenna relay box. All relays are DPDT, 250 V ac, 15 A contacts. R29 is used to limit the regulator current. Mount the regulator using TO-220 mounting hardware, with heatsink compound. With the exception of the normally closed and normally open contacts, all wiring is #22 solid copper wire.**

**D5-D11 — 1N4007.  
J3 — 8 pin external weatherproof connector (or DB-9 with appropriate weather sealant).**

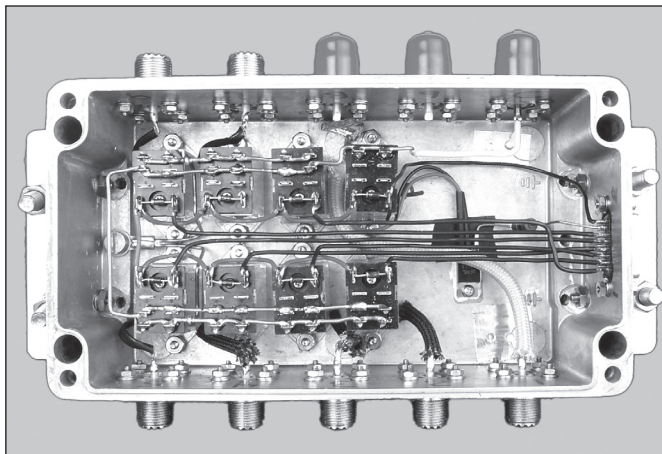**K1-K7 — Omron LY2F-DC12 with 12 V coil.  
U7 — LM7812 +12 V regulator.**



(A)

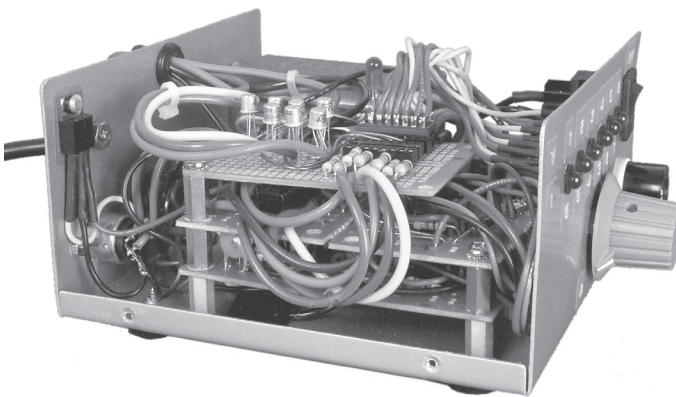

(B)

**Fig 24.26** — At A, the external relay box. The LM7812 regulator is mounted to the bottom of the box. The relay normally open and normally closed contacts are wired in parallel using #12 solid copper. The two extra flange-mount SO-239 connectors at the upper right are for future expansion. At B, inside the control box. Components are mounted on RadioShack Universal Project Board. The bottom board in the enclosure as well as the right half of the middle section hold the ICOM circuit. The Yaesu interface is on the left side of the middle section. The top circuit board holds the DIP sockets and relay-selection transistors. All high voltage leads are insulated. The 7805 5-V regulator is mounted on the back panel using TO-220 mounting hardware, with heatsink compound.

over this wire to prevent it from shorting to the aluminum box.

The normally open and normally closed contacts are also wired in parallel. This can be done on the lugs themselves. For this, use #12 solid copper wire.

Mount the relays in the aluminum box, oriented so they can be wired together without difficulty. (See **Fig 24.26A**.) With the exception of the wire used for the relay coils (#22 solid wire), use #12 solid copper wire for the rest of the connections.

To eliminate the possibility of spikes or “back emf,” a 1N4007 diode is soldered across the coil contacts of each relay. In addition, 0.01- $\mu$ F capacitors across the diodes will reduce the possibility of stray RF causing problems with the relay operation.

Since the cable run from the shack to the tower can be quite long, consideration has to be given to the voltage drop that may occur. The relays require 12 V dc. The prototype used a 12 V dc regulator in the relay box, fed with 18 V dc (at 2 A) from the control box. If the cable run is not that long, however, you could just use a 12-V supply and skip the regulator.

One of the relays is used for lightning protection. When not in use, the relay grounds the line coming in from the shack. When the control box is activated, it applies power to this relay, thus removing the ground on the station feed line. All the antenna lines are grounded through the normally closed relay contacts. They remain grounded until the relay receives power from the control box.

## CONTROL BOX

This is the heart of the system. The 18 V dc

power supply for the relays is located in this box, in addition to the Yaesu and ICOM decoder circuits and the relay-control circuitry. All connections to the relay box are made via an 8-position terminal barrier strip mounted on the back of the control box.

The front of the box has LEDs that indicate the selected antenna. A rotary switch can be used for manual antenna selection. The power switch and fuse are also located on the front panel.

The wiring schemes on the Yaesu and ICOM ACC sockets are so different that the unit shown in the photos has a 5-pin DIN connector for each rig on the control box. Since there is only one set of LEDs, use an 8-pin DIP header to select the appropriate control circuit for each radio. See **Fig 24.26B**. The unit is built with point-to-point wiring on Radio Shack Universal Project Boards.

## ICOM Circuitry

This circuit originally appeared in April 1993 *QST* and is modified slightly for this application. The original circuit allowed for switching between seven antennas (from 160 to 10 meters). The Band Data signal from the ICOM radios goes to a string of LM339 comparators. Resistors R9 through R15 divide the 8-V reference signal from the rig to provide midpoint references between the band signal levels. The LM339 comparators decide which band the radio is on. A single comparator selects the 1.8 or 10 MHz band because those bands are at opposite ends of the range. The other bands each use two comparators. One determines if the band signal is above the band level and the other determines if it is below the band level. If

the signal is between those two levels, the appropriate LED and relay-selection transistor switch is turned on.

The ICOM circuit allows for manual antenna selection. The 8-V reference is normally taken directly from the ICOM ACC socket. If this circuit is to be used with other equipment, then a regulated 8-V source should be provided.

## Yaesu Circuitry

The neat thing about Yaesu band data is that it's in a binary format. This means you can use a simple BCD decoder for band switching. The BCD output ranges from 1 to 9. In essence, you can switch between 9 antennas (or bands). Since the relay box switches just six antennas, steering diodes (D1 through D4 in **Fig 24.24**) allow the use of one antenna connection for multiple bands. One antenna connection is used for 17 and 15 meters, and another connection for 12 and 10 meters because the ICOM band data combines those bands. There is no control line or relay for a 30-meter antenna with this version of the project.

## DIP Sockets and Header

A RadioShack Universal Project Board holds the DIP sockets along with the relay keying transistors. This board is shown as the top layer in **Fig 24.26B**. The Yaesu socket has 1-k $\Omega$  resistors wired in series with each input pinch. The other header connects directly to the ICOM circuitry.

The DIP header is used to switch the keying transistors between the ICOM and Yaesu circuitry. The LEDs are used to indicate antenna number. Use stranded wire (for



its flexibility) when connecting to the LEDs.

## Relay Keying Transistors

Both circuits use the same transistor-keying scheme, so you need only one set of transistors. Each transistor collector connects to the terminal barrier strip. The emitters are grounded, and the bases are wired in parallel to the two 16-pin DIP sockets. The band data turns on one of the transistors, effectively

grounding that relay-control lead. Current flows through the selected relay coil, switching that relay to the normally open position and connecting the station feed line to the proper antenna.

## Power Supply

The power supply is used strictly for the relays. Other power requirements are taken from the rig used. There is room here for varia-

tions on the power supply theme; the parts used in this version were readily available.

## Notes

<sup>1</sup>"An Antenna Switching System for Multi-Two and Single-Multi Contesting," by Tony Brock-Fisher, K1KP, January 1995 *NCJ*.

<sup>2</sup>"A Remotely Controlled Antenna Switch," by Nigel Thompson, April 1993 *QST*.

<sup>3</sup>NA Logging Program Section 11.

# 24.6 A Low-Cost Remote Antenna Switch

Getting multiple antenna feed lines into the shack is a common problem that can be easily solved with a suitable remote antenna switch. The project described here by Bill Smith, KO4NR, provides an easy and inexpensive solution. It originally appeared in April 2005 *QST*.

## RELAY SELECTION

Interesting innovations in printed circuit board (PCB) power relay design have produced a number of compact units that exhibit high dielectric strength and can carry impressive amounts of current.

Although not factory tested for RF use, the American Zettler AZ755 series PCB relays work very well in this application. (See [www.americanzettler.com](http://www.americanzettler.com) for datasheets and information.) The AZ755 is rated for 480 W switched power with a resistive load and a maximum switched current of 20 A. Despite the relay's small physical size, the dielectric strength between the contacts and coil is 5 kV RMS, with an impressive 1 kV RMS between the open contacts. This means that

**Fig 24.27 — Schematic and parts list for the remote antenna switch. Part numbers indicated with an M are available from Mouser Electronics ([www.mouser.com](http://www.mouser.com)). PC boards are available from FAR Circuits ([www.farcircuits.net](http://www.farcircuits.net)).**


**C1-C6 — 0.001  $\mu$ F, 50 V disc ceramic (M 140-50P5-102K-TB).**

**D1-D6 — 1N4001 (M 512-1N4001).**


**J1-J7 — SO-239A chassis mount coaxial connector with silver-plated 4-hole square flange and Teflon insulation (Amphenol 83-798 available as Mouser 523-83-798).**

**K1-K6 — SPDT PC board power relay with 12 V dc coil (American Zettler AZ755-1C-12DE). Available from [www.relaycenter.com](http://www.relaycenter.com). See text.**


**TB1, TB2 — PC board terminal block with 6 contacts (M 651-1729050).**

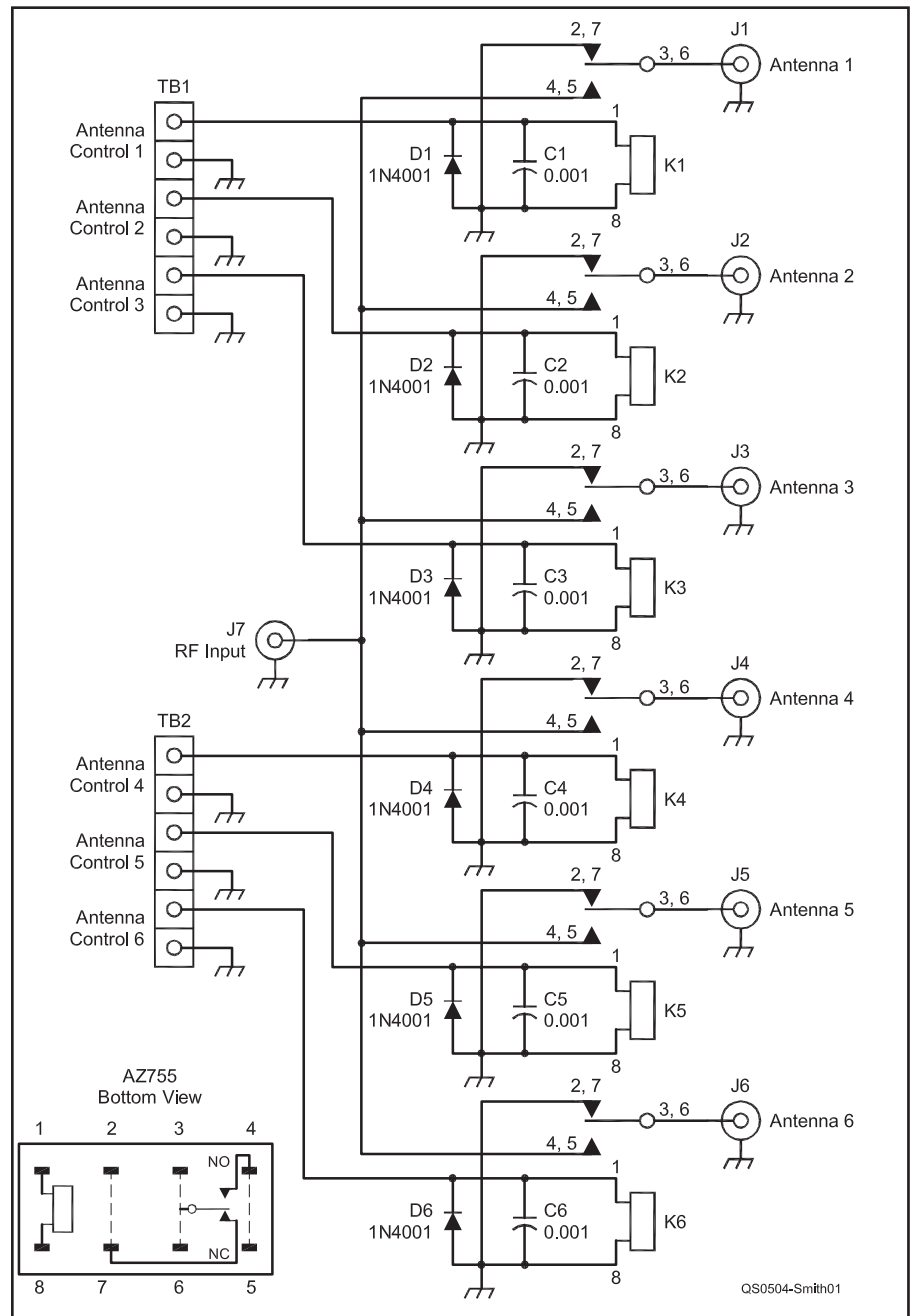



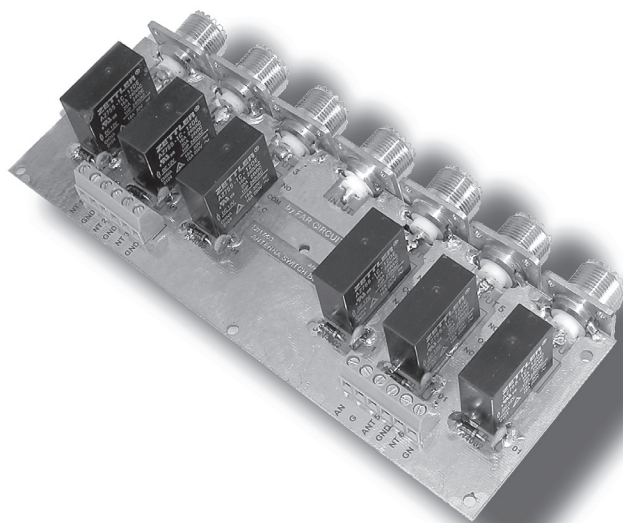

**Fig 24.28** — A completed remote antenna switch. The RF INPUT connector is in the center, with three ANTENNA connectors on each side. The control cable connects to the two terminal blocks.

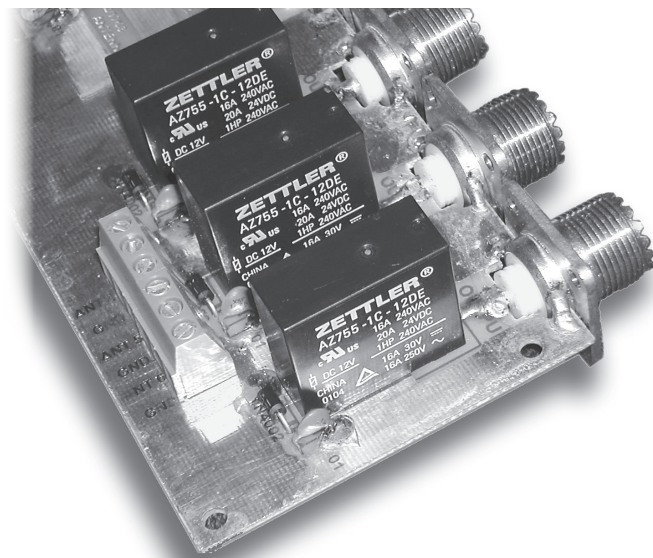

**Fig 24.29** — Connector flanges are soldered to the board's ground plane top and bottom. The ground ends of D1-D6 and C1-C6 are also soldered top and bottom. The relays have two pins each for the contact connections. Solder all pins and install eyelets supplied with the FAR Circuits board to ensure good connections for the relay common and normally closed pins.

the relay is resistant to a flashover that could damage the coil or pit the contacts.

The AZ755 series relays are offered in a wide variety of configurations. This project uses part number AZ755-1C-12DE. This model has a 12 V dc coil, but you can use any of the available coil voltages in the series. The contact style is Form C, which is SPDT. The E suffix indicates that the relay epoxy is sealed for better protection from dirt and moisture. For relays that are not epoxy sealed, drop the E from the part number.

## CIRCUIT DESIGN

**Fig 24.27** shows the circuit, which handles up to six antennas. The common contacts of the relays (K1-K6) are connected to SO-239 connectors (J1-J6) for the antenna feed lines. The normally open (NO) contacts are all connected to the RF INPUT connector, J7. The normally closed (NC) contacts are all connected to ground so that the antennas are grounded when not in use. To select an antenna, apply 12 V dc to the appropriate ANTENNA CONTROL terminal to energize the relay and connect the ANTENNA to the RF INPUT.

C1-C6 help to keep stray RF out. In addition, D1-D6 are installed across the coils to prevent voltage spikes when the power is removed from the coil. The finished board (available from FAR Circuits) with all components mounted is shown in **Fig 24.28**.

## ASSEMBLY NOTES

The design is simple and assembly doesn't require special tools. In addition to the PC


board and parts, you'll need a suitable enclosure to keep the board dry and pests away. The author used a plastic children's lunch box that hangs under his deck.

The most difficult part of the project is drilling the holes in the enclosure for the SO-239 connectors and getting everything to line up. You may find it easier to install the connectors in the enclosure first, and then solder them to the board. (Use the board to mark the center line and location of the connectors on the enclosure.) After the connectors are tacked in place, remove the screws holding the SO-239s to the enclosure and remove the total assembly. This ensures a perfect fit when reassembling.

Make sure the SO-239s are all the same type and brand to ensure a uniform fit. The board was designed around the Amphenol connectors recommended in the parts list. They have silver-plated center pins and flanges, and Teflon insulation. The silver plating makes the connectors easier to solder than nickel-plated connectors, and the Teflon insulation is much less prone to melting than the plastic often found on inexpensive connectors. Other SO-239 connectors may fit with possible modification for a good fit.

Use a *hot* soldering iron when soldering the flange of the SO-239 to the board's ground plane as shown in **Fig 24.29**. Be sure to solder top and bottom.

The PC board is double-sided, and FAR Circuits supplies eyelets with the board to use in the larger holes for the common and normally closed relay pins. They provide

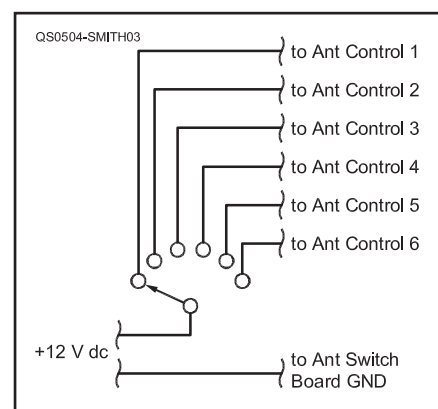

**Fig 24.30** — Antennas are selected with a simple 12-V supply and rotary switch.

for a better connection to the component side of the board. In addition, soldering a short length of #14 bare copper wire into the center pin of each SO-239 will give you a better connection to the circuit trace on the board. Be sure to solder the ground ends of C1-C6 and D1-D6 on both the top and bottom sides of the board.

## POWERING IT UP

The switch is controlled with a 12-V dc power supply and small ceramic rotary switch as shown in **Fig 24.30**. The switch simply sends 12 V to energize one of the relay coils and select the desired antenna. When 12 V is removed, the normally closed relay contacts connect all feed lines to ground. Connect the

PC board's ground plane to a ground rod for lightning protection and as a means of eliminating static.

The control cable can be the 8-conductor variety usually used for rotators. Long runs of wire may require large conductors to prevent unacceptable voltage drops at the relay coils, but the relays will work over a fairly wide range of coil voltages so it's not critical.

### TESTING

Initial testing should be conducted on the bench with an antenna analyzer or a transceiver (internal antenna tuner off) and power/SWR meter connected to the RF INPUT jack.

Connect a 50  $\Omega$  load to one of the antenna jacks on the switch board. Apply a small of RF power. The SWR should be close to 1:1 (similar to readings without the switch in the line).

If everything looks okay, increase the power and check the SWR through the switch on all bands that you plan to use it on. Next, move the wattmeter to the switch output and verify that the power on that side is about the same as the power at the input. There should be little or no measurable loss through the switch. Repeat these tests for all of the switch positions.

If you run an amplifier, test the switch at

high power. The author used the switch at 1-1.3 kW during normal intermittent operation (SSB and CW) with no problems.

Although they are not designed for RF, the relays perform well. The board exhibits low SWR, low insertion loss and good isolation over a wide frequency range. The ARRL Lab tested the completed antenna switch board. Insertion loss measured <0.1 dB for 2-50 MHz (for all ports to common). SWR measured 1.1:1 or less from 2-28 MHz, 1.2:1 or less on 50 MHz. Isolation was >60 dB for 2-28 MHz, except for the two innermost ports, which were 50 dB at 28 MHz. Worst-case isolation on 50 MHz was 45 dB.

## 24.7 Audible Antenna Bridge

The audible antenna bridge (AAB) shown in **Fig 24.31** was designed by Rod Kreuter, WA3ENK. This project would help a visually impaired ham, but sighted hams will also find it very useful. (For example, tuning a mobile screwdriver antenna while you're driving.) The AAB is rugged and easy to use, both in the harsh light of day and in the dark of night. It's also inexpensive to build, and a kit is available.<sup>1</sup>

An absorptive type of SWR meter, the AAB is used to indicate how close the match is between your transmitter and your antenna. Its output is a tone whose pitch is proportional to SWR. It also sends the SWR value in Morse code.

Unlike most SWR meters on the market, this one actually absorbs power from your transmitter while you're tuning, helping to protect your transmitter during tune-up. Many transmitters have SWR foldback capability and will decrease the output power if the antenna match is poor, but some do not.

By absorbing power in the AAB, no matter what you do at the antenna port, the transmitter never sees an SWR greater than 2:1. The trade-off is that 75% of your transmitter power ends up as heat in the bridge, so you need to switch out the AAB after you have tuned your antenna.

### THEORY OF OPERATION

The AAB works on a principle taken right from the *ARRL Antenna Book*. The bridge consists of four impedances, or arms. See **Fig 24.32**. If three of the arms are 50  $\Omega$  resistors and the fourth is an antenna (or an antenna and tuner combination), then the bridge will be balanced when the antenna port is also 50  $\Omega$ . Diodes D1 and D2 sample the forward and reverse voltages, respectively. A periph-



**Fig 24.31** — Front view of the audible antenna bridge.

eral interface controller (PIC) with a 10 bit analog to digital converter (A/D) digitizes these voltages and calculates the SWR.

The SWR is used to control a hardware pulse width modulator that produces the output tone. It's also used by the Morse code routine to send the actual value of SWR, at 15 WPM with 5 WPM spacing.

The power that the AAB can handle during tune-up is a function of the resistors used in the three reference arms of the bridge. The 30 W noninductive resistors, R1-R3, are made by a

number of companies but are not cheap. The bridge resistors must be noninductive. Don't use wire wound resistors!

Antenna tuning should be done with minimal power, and the AAB will work down to about 1 W. The 30 W resistors will handle tune-ups with about 60 W or perhaps 100 W for a short time. If you always remember to turn down your transmitter power, and you tune up quickly, the bridge resistors could be perhaps 5 W for normal rigs and 1 W for QRP rigs.

### BUILDING THE AAB


A PC board is a nice way to build the AAB, but you could easily construct such a simple circuit using ugly construction. Keep the wires short in the RF section. See **Fig 24.33**.

Use a heat sink for the noninductive resistors. Like many power devices, the power rating depends on getting the heat out! These resistors get really hot running at 10 or 20 W. See **Fig 24.34**. Use a big heat sink with heat sink compound, give yourself plenty of room in the cabinet and drill some holes to let the heat escape.

Switch S1 chooses TUNE/OPERATE and S2, the INQUIRE button, is used to report on various conditions, such as the SWR value in Morse code. You can eliminate the TUNE/OPERATE switch, but remember to remove the AAB from your feed line after tuning up.

To use the AAB in a QRP station, you may want to reduce resistors R4 and R5. They are sized so that a 25 W transmitter will not saturate the analog to digital converter (ADC) on the PIC when using fresh batteries (more on this later). A good value for a 5 W transmitter would be about 20 k $\Omega$ . So long as the voltages at pin 12 and pin 13 of U1 are below the battery voltage, the system will work fine.



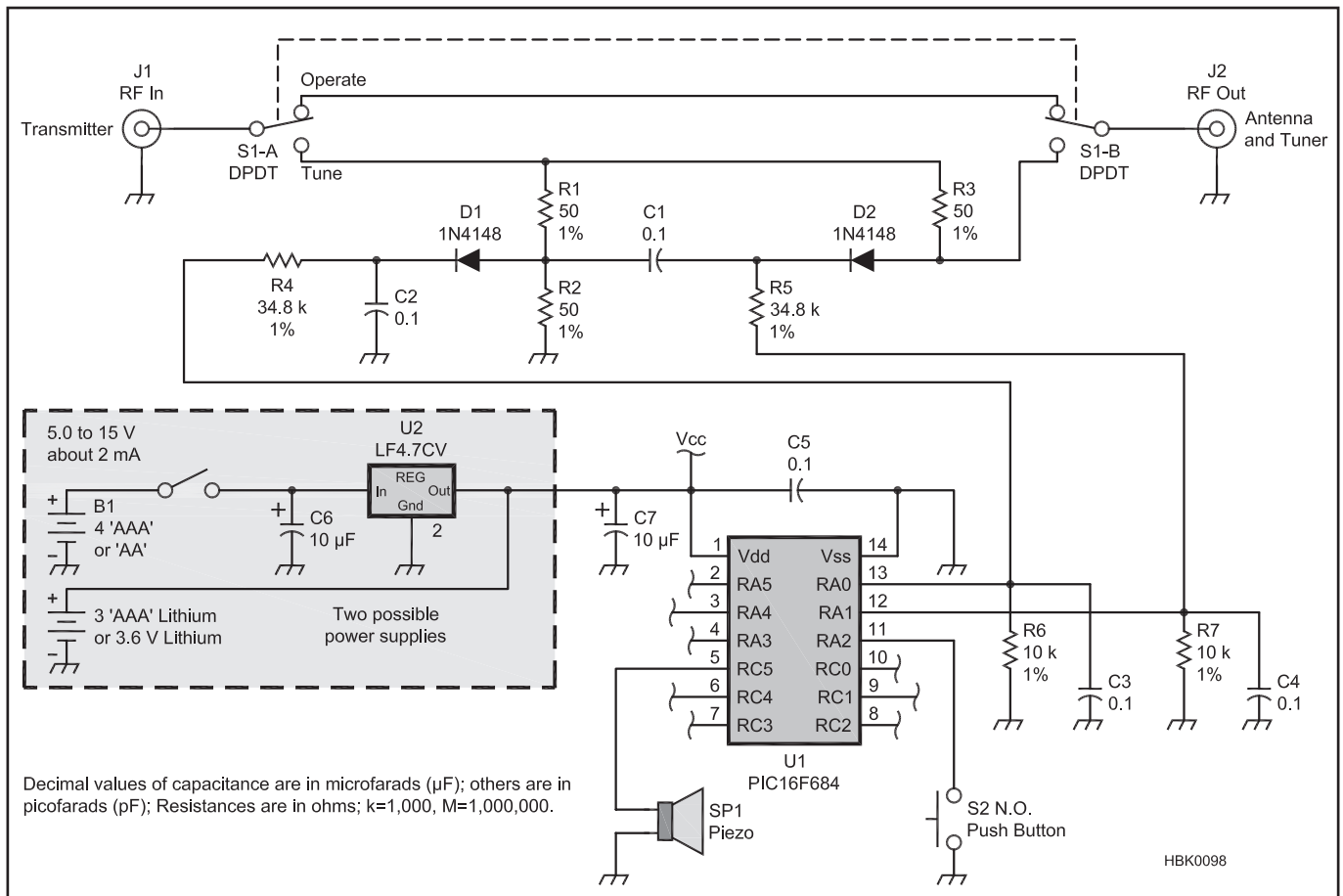


**Fig 24.32 — Schematic and parts list of the AAB.**


C1-C5 — 0.1  $\mu\text{F}$  ceramic.  
 C6, C7 — 10  $\mu\text{F}$ , 25 V electrolytic.  
 D1, D2 — 1N4148.  
 J1, J2 — SO-239 UHF coaxial jack.  
 R1 -R3 — Resistor, 50  $\Omega$ , 1%, 30 W  
 Caddock noninductive  
 (Mouser 684-MP930-50).

R4, R5 — Resistor, 34.8 k $\Omega$ , 1%.  
 R6, R7 — Resistor, 10 k $\Omega$ , 1%.  
 S1 — DPDT (Digi-Key SW333-ND).  
 S2 — Momentary contact  
 (Mouser 612-TL1105LF250Q).  
 SP1 — Piezoelectric buzzer EFB-  
 RD24C411 (Digi-Key P9924-ND).

U1 — PIC16F684 (Digi-Key PIC16F684-  
 1/P-ND). Must be programmed before  
 use. See Note 1.  
 U2 — LF4.7CV regulator  
 (Mouser 511-LF47CV).

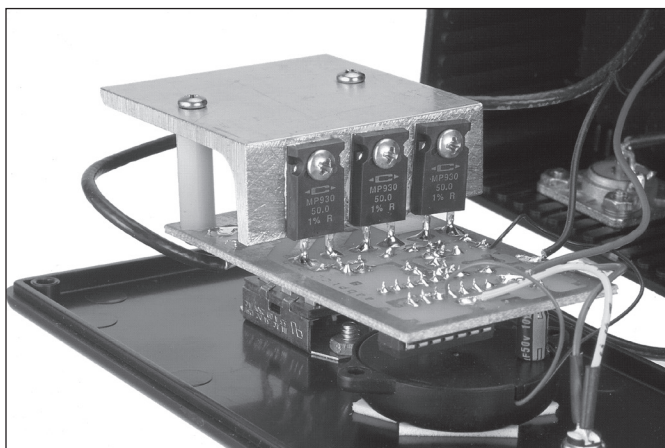

**Fig 24.33 — Close-up view of three Caddock TO-220 style bridge resistors mounted on the heat sink.**

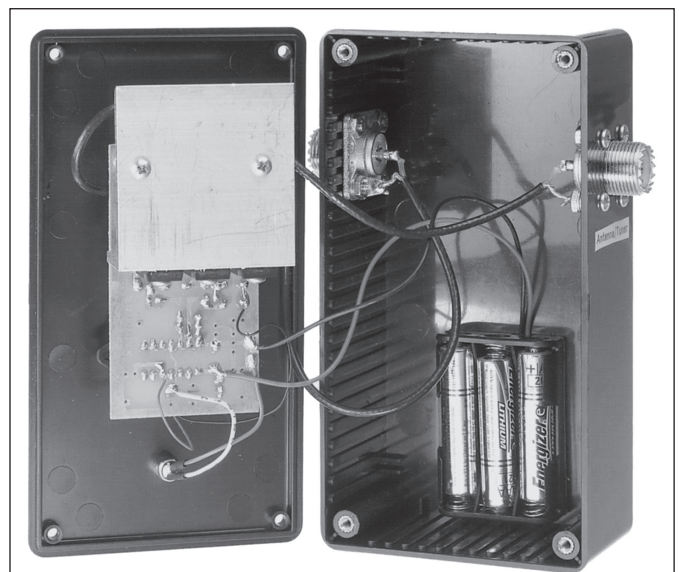

**Fig 24.34 — Interior view of the AAB, showing the battery pack at the bottom of the enclosure.**

## POWERING THE AAB

To save power the AAB uses a sleep mode. If you haven't pushed the INQUIRE button for about 5 minutes, the AAB will go to sleep after sending the letter N for "night night." During sleep the current draw is about 2  $\mu$ A. Pushing the switch while it's sleeping will wake up the AAB and it will send the letter U ("up").

The first four prototypes used four AAA batteries and a low-dropout 4.7 V regulator. This made for a nice stiff supply and very good battery life, with only one problem. Even though the PIC uses less than 2  $\mu$ A during sleep, the regulator uses 500  $\mu$ A. Battery data says that alkaline AA batteries will last 6 months at this level and AAA batteries about half that long. Consider adding an ON/OFF switch if you go this route.

The other option is to use batteries without a regulator. Normally you couldn't get away with this without providing a separate voltage reference for the ADC in the PIC. In this case it doesn't matter as much because SWR is a ratio of two voltages.

What does matter is the battery voltage with respect to the voltage produced by the RF signal. Diodes D1 and D2 rectify the RF and produce a dc voltage proportional to RF power. This voltage is divided by resistors R4, R6 and R5, R7. The voltage at the ADC inputs of the PIC, pins 12 and 13, must be less than the power supply voltage. With a regulated supply this isn't much of a problem and if you're careful it can also work with unregulated batteries.

Microchip recommends that these parts be run on 2.5 to 5.5 V if you need the 10 bit ADC to be accurate. Many battery combinations will provide this, but consider lithium batteries instead of alkaline. The voltage from an alkaline battery begins to fall very early in its life and continues at a downward slope until it is exhausted. A lithium battery, on

the other hand, provides a nearly constant voltage throughout its useful life. A 3.6 V AA size lithium should last a few years, but with the lower output voltage you may want to reduce R4 and R5. The final prototype used three AAA lithium batteries (each about 1.7 V when new), with no regulator or ON/OFF switch, which should last at least two years.

U1's ADC converter will saturate at some level. With new batteries, let's say this level is 25 W when the power supply is 4.5 V. When the power supply has fallen to 3.5 V, the RF level that will saturate the converter will be 15 W. So if you find that the output of your rig, which used to be fine, is now saturating the ADC, it's time to change batteries.

## USING THE AAB

Connect your transmitter to the INPUT and your antenna/tuner to the OUTPUT. Turn your transmit power down to 5 or 10 W and put S1 in the TUNE position. Wake the AAB up by pushing the INQUIRE button. Key your transmitter in a mode with some carrier power. The AAB should start to produce a steady tone. Adjust your tuner or antenna for the lowest tone pitch. Press the INQUIRE button for the numeric SWR value.

When the AAB is operating normally, it produces a tone proportional to SWR. The tone ranges from 250 Hz at an SWR of 1.0:1, rising to 4450 Hz at an SWR of about 15:1. Errors can occur and at times the AAB can't make a measurement. If an error occurs, either a high pitched tone or no tone is produced. Pushing the INQUIRE button will give you more information. Five different conditions can occur:

*Normal operation.* A tone proportional to SWR is produced. Press INQUIRE and a two digit SWR value is sent separated by the letter R (Morse for the decimal point character).

*Error 1.* The forward power is too low for a reliable measurement. No tone is produced. INQUIRE button sends letter L (low).

*Error 2.* Forward power is too high (almost saturating the ADC). A pulsing tone proportional to SWR is produced. However, if the ADC is saturated this value might be meaningless. INQUIRE button sends letter S (saturated).

*Error 3.* SWR is greater than 9.9:1. A tone proportional to SWR is produced. INQUIRE button sends letter H (high).

*Error 4.* The reverse voltage is greater than the forward voltage. Two things can cause this error. You might be near a high power transmitter, or you connected the transmitter to the output port. No tone is produced. INQUIRE button sends letter F (fault).

The PIC used in this design could be used in a more standard SWR meter, such as those with a transformer type sensor. As long as the meter produces a forward and reverse voltage that you can scale to be from 0 to 3 up to 5 V (depending on your power supply choice), it will work just fine. However, the driving impedance of the voltage must be 10 k $\Omega$  or less.

The author thanks the Ham Radio Committee of the National Federation of the Blind for inspiration, and Tom Fowle, WA6IVG, and Bill Gerrey, WA6NPC, of the Smith-Kettlewell Research Institute for testing prototypes.

<sup>1</sup>A kit of parts including a printed circuit board is available from Q-Sat, 319 McBath St, State College, PA 16801. The price is currently \$30, postpaid. PC boards are available for \$7 postpaid and a programmed PIC is available for \$6 postpaid. Source code for an unprogrammed PIC is available on the ARRL Web site. Go to [www.arrl.org/qst-in-depth](http://www.arrl.org/qst-in-depth) and look for Kreuter0607.zip in the 2007 section.

# 24.8 A Trio of Transceiver/Computer Interfaces

Virtually all modern Amateur Radio transceivers (and many general-coverage receivers) have provisions for external computer control. Most hams take advantage of this feature using software specifically developed for control, or primarily intended for some other purpose (such as contest logging), with rig control as a secondary function.

Unfortunately, the serial port on most radios cannot be directly connected to the serial port on most computers. The problem is that most radios use TTL signal levels while most computers use RS-232-D.

The interfaces described here simply convert the TTL levels used by the radio to the RS-232-D levels used by the computer, and

vice versa. Interfaces of this type are often referred to as level shifters. Two basic designs, one having a couple of variations, cover the popular brands of radios. This article, by Wally Blackburn, AA8DX, first appeared in February 1993 *QST*.

## TYPE ONE: ICOM CI-V


The simplest interface is the one used for the ICOM CI-V system. This interface works with newer ICOM and Ten-Tec rigs. **Fig 24.35** shows the two-wire bus system used in these radios.

This arrangement uses a CSMA/CD (carrier-sense multiple access/collision detect) bus. This refers to a bus that a number of

stations share to transmit and receive data. In effect, the bus is a single wire and common ground that interconnect a number of radios and computers.

The single wire is used for transmitting and receiving data. Each device has its own unique digital address. Information is transferred on the bus in the form of packets that include the data and the address of the intended receiving device.

The schematic for the ICOM/Ten-Tec interface is shown in **Fig 24.36**. It is also the Yaesu interface. The only difference is that the transmit data (TxD) and receive data (RxD) are jumpered together for the ICOM/Ten-Tec version.

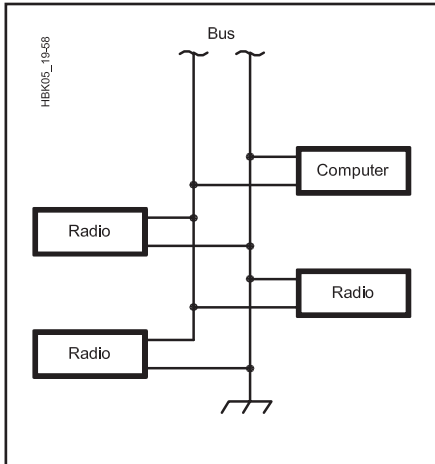

**Fig 24.35 — The basic two-wire bus system that ICOM and newer Ten-Tec radios share among several radios and computers. In its simplest form, the bus would include only one radio and one computer.**

The signal lines are active-high TTL. This means that a logical one is represented by a binary one (+5 V). To shift this to RS-232-D it must be converted to -12 V while a binary zero (0 V) must be converted to +12 V. In the other direction, the opposites are needed: -12 V to +5 V and +12 V to 0 V.

U1 is used as a buffer to meet the interface specifications of the radio's circuitry and provide some isolation. U2 is a 5-V-powered RS-232-D transceiver chip that translates between TTL and RS-232-D levels. This chip uses charge pumps to obtain  $\pm 10$  V from a single +5-V supply. This device is used in all three interfaces.


A DB25 female (DB25F) is typically used at the computer end. Refer to the discussion of RS-232-D earlier in the chapter for 9-pin connector information. The interface connects to the radio via a 1/8-inch phone plug. The sleeve is ground and the tip is the bus connection.

It is worth noting that the ICOM and Ten-Tec radios use identical basic command sets (although the Ten-Tec includes additional commands). Thus, driver software is compatible. The manufacturers are to be commended for working toward standardizing these interfaces somewhat. This allows Ten-Tec radios to be used with all popular software that supports the ICOM CI-V interface. When configuring the software, simply indicate that an ICOM radio (such as the IC-735) is connected.

#### TYPE TWO: YAESU INTERFACE

The interface used for Yaesu rigs is identical to the one described for the ICOM/Ten-Tec, except that RxD and TxD are not jumpered together. Refer to Fig 24.36. This arrangement uses only the RxD and TxD lines; no flow control is used.

The FT-990 and FT-1000/FT-1000D use an emitter follower as the TTL output. If the input

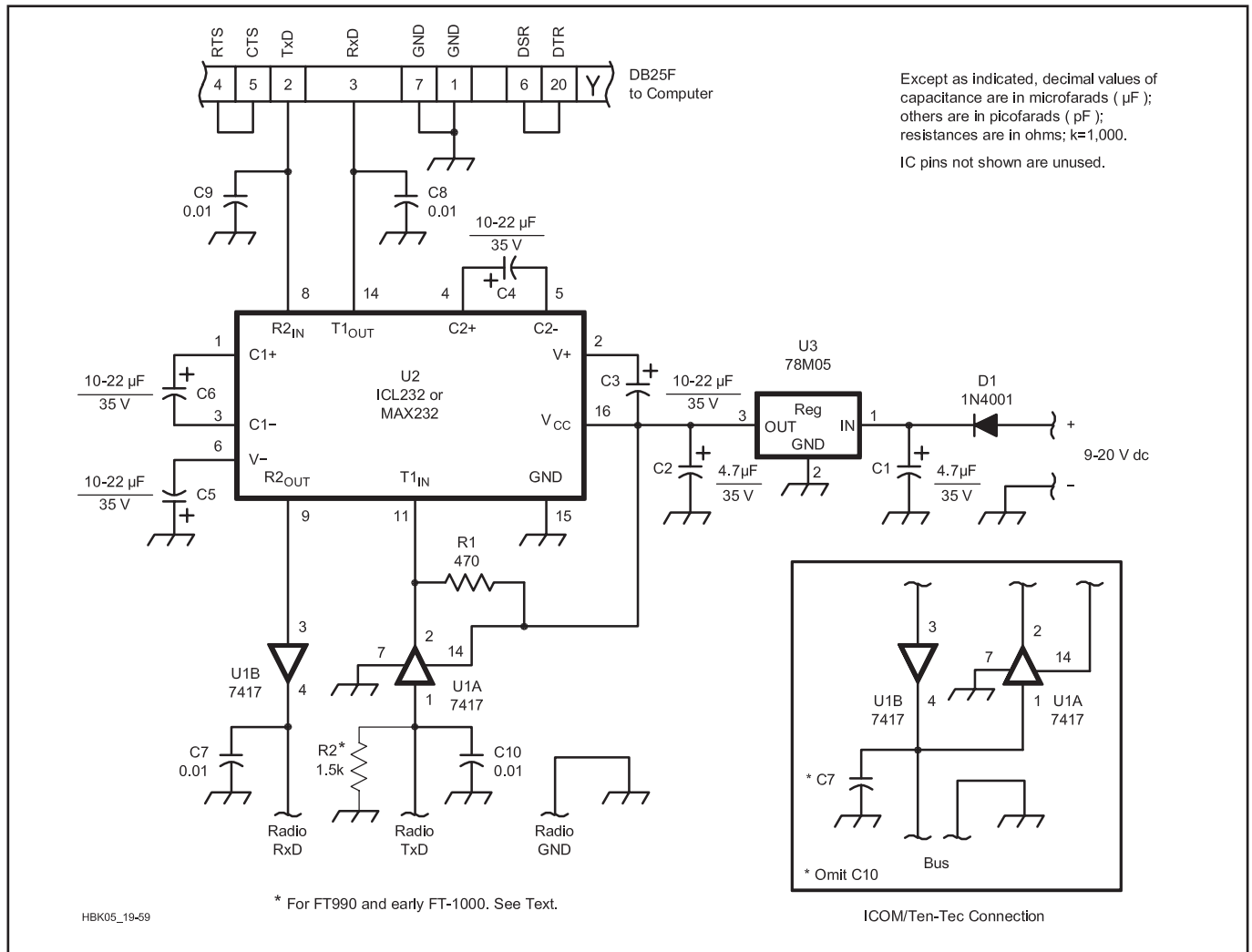

**Fig 24.36 — ICOM/Ten-Tec/Yaesu interface schematic. The insert shows the ICOM/Ten-Tec bus connection, which simply involves tying two pins together and eliminating a bypass capacitor.**

C7-C10 — 0.01- $\mu\text{F}$  ceramic disc.

U1 — 7417 hex buffer/driver.

U2 — Harris ICL232 or Maxim MAX232.



The same computer connector is used, but the radio connector varies with model. Refer to the manual for your particular rig to determine the connector type and pin arrangement.

The interface setup used with Kenwood radios is different in two ways from the previous two: Request-to-Send (RTS) and Clear-to-Send (CTS) handshaking is implemented


The schematic in **Fig 24.37** shows the Kenwood interface circuit. Note the different grounds for the computer and the radio. This, in conjunction with a separate power supply for the interface, provides excellent isolation.

Some of the earlier Kenwood radios require additional parts before their serial connection can be used. The TS-440S and R-5000
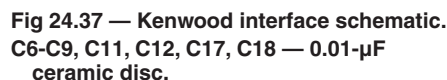
## CONSTRUCTION AND TESTING

It is a good idea to enclose the interface in a metal case and ground it well. Use of a separate power supply is also a good idea. You may be tempted to take 13.8 V from your radio — and it works well in many cases: but you sacrifice some isolation and may have noise problems. Since these interfaces draw only 10 to 20 mA, a wall transformer is an easy option.

The interface can be tested using the data



**U1-U4 — PS2501-1NEC (available from Digi-Key).**  
**U5 — Harris ICL232 or Maxim MAX232.**

**Table 24.6**  
**Kenwood Interface Testing**

Apply	Result
GND to Radio-5	-8 to -12 V at PC-5
+5 V to Radio-5	+8 to +12 V at PC-5
+9 V to PC-4	+5 V at Radio-4
-9 V to PC-4	0 V at Radio-4
GND to Radio-2	-8 to -12 at PC-3
+5 V to Radio-2	+8 to +12 V at PC-3
+9 V to PC-2	+5 V to Radio-3
-9 V to PC-2	0 V at Radio-3

in **Tables 24.6, 24.7 and 24.8**. Remember, all you are doing is shifting voltage levels. You will need a 5-V supply, a 9-V battery and a voltmeter. Simply supply the voltages as described in the corresponding table for your interface and check for the correct voltage on the other side. When an input of -9 V is called for, simply connect the positive terminal of the battery to ground.

During normal operation, the input signals

**Table 24.7**  
**ICOM/Ten-Tec Interface Testing**

Apply	Result
GND to Bus	+8 to +12 V at PC-3
+5 V to Bus	-8 to -12 V at PC-3
-9 V to PC-2	+5 V on Bus
+9 V to PC-2	0 V on Bus

to the radio float to 5 V because of pullup resistors inside the radio. These include RxD on the Yaesu interface, the bus on the ICOM/Ten-Tec version, and RxD and CTS on the Kenwood interface. To simulate this during testing, these lines must be tied to a 5-V supply through 1-k $\Omega$  resistors. Connecting these to the supply without current-limiting resistors will damage the interface circuitry. R5 and R6 in the Kenwood schematic illustrate this. They are not shown (but are still needed) in

**Table 24.8**  
**Yaesu Interface Testing**

Apply	Result
GND to Radio TxD	+8 to +12 V at PC-3
+5 V to Radio TxD	-8 to -12 V at PC-3
+9 V to PC-2	0 V at Radio RxD
-9 V to PC-2	+5 V at Radio RxD

the ICOM/Ten-Tec/Yaesu schematic. Also, be sure to note the separate grounds on the Kenwood interface during testing.

Another subject worth discussing is the radio's communication configuration. The serial ports of both the radio and the computer must be set to the same baud rate, parity, and number of start and stop bits. Check your radio's documentation and configure your software or use the PC-DOS/MS-DOS MODE command as described in the computer manual.

## 24.9 A Simple Serial Interface

A number of possibilities exist for building an RS-232-to-TTL interface level converter to connect a transceiver to a computer serial port. The interface described here by Dale Botkin, NØXAS, is extremely simple, requiring only a few common parts.

Most published serial interface circuits fall into one of the following categories:

- Single chip, MAX232 type. These are relatively expensive, require several capacitors, take up lots of board space and usually require ordering parts.


- Single chip, MAX233 type. This version doesn't need capacitors. Otherwise it shares most of the characteristics of the MAX232 type device, but is even more expensive.

- Transistors. Usually transistor designs use a mix of NPN and PNP devices, four to eight or more resistors, and usually capacitors and diodes. This is just too many parts!

- Other methods. Some designs use series resistors, or TTL logic inverters with resistors. The idea is that the voltages may be out of specification for the chip, but if the current is low enough it won't damage the device. This is not always safe for the TTL/CMOS device. With just a series resistor the serial data doesn't get inverted, so it requires the use of a software USART. It can work, but it's far from ideal.

### A SIMPLER APPROACH

The EIA-232 specification specifies a

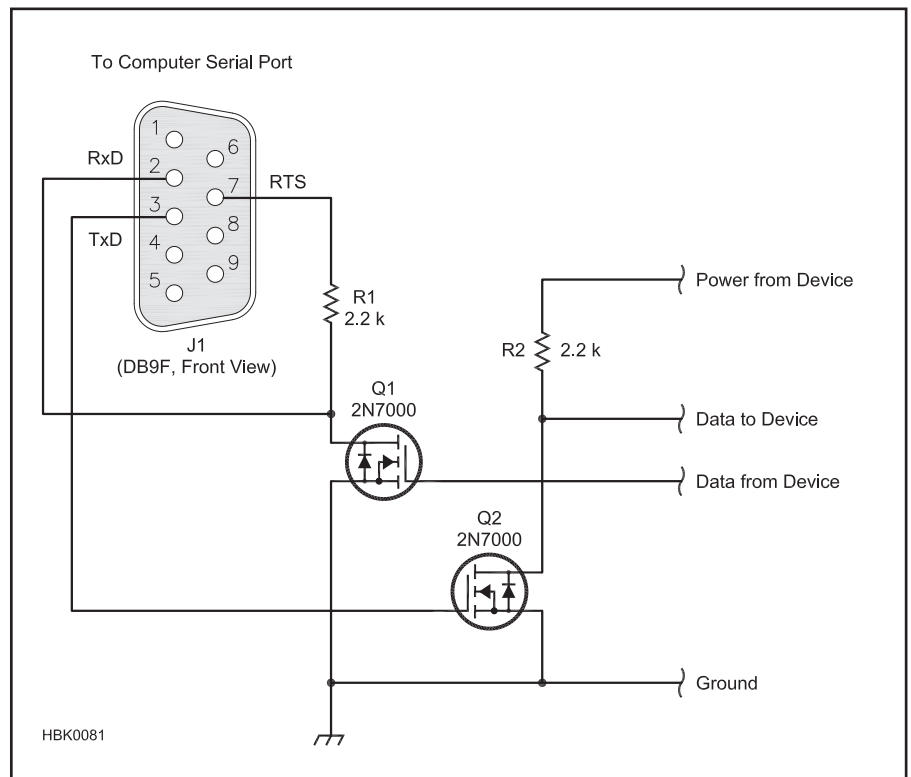

**Fig 24.38 — Schematic for the simple serial interface.**

**J1** — DB9F or connector to fit device serial port. Note that pin assignments for RxD, TxD and RTS are different on DB25 connectors.

**Q1, Q2** — Small signal MOSFET, 2N7000 or equiv.

signal level between  $\pm 3$  V and  $\pm 12$  V for data. The author looked at data sheets for devices ranging from the decades-old 1489 line receiver to the latest single-chip solutions. Not a single device found actually required a negative input voltage! In fact, the equivalent schematic shown for the old parts clearly shows a diode that holds the input to the first inverter stage at or near ground when a negative voltage is applied. The data sheets show that a reasonable TTL-level input will drive these devices perfectly well.

Relieved of the burden of exactly replicating the PC-side serial port voltages, the interface shown in **Fig 24.38** is designed for minimum parts count and low cost — under \$1.

Why use MOSFETs for Q1 and Q2? In switching application such as this, there are several advantages to using small signal

MOSFETs over the usual bipolar choices like the 2N2222 or 2N3904. First, they need no base current limiting resistors — the MOSFET is a voltage operated device, and the gate is isolated from the source and drain. The gate on a 2N7000 is rated for  $\pm 20$  V, so you don't need a clamping diode to prevent negative voltages from reaching the gate. They can also be had just as cheaply as their common bipolar cousins. (If sourcing 2N7000s is a challenge in Europe, the BS170 is basically identical except for the pins being reversed.) Now all that is needed is a drain limiting resistor, since the gate current is as close to zero as we are likely to care about.

Q1 gets its input from the TTL-level device. Q1 and R1 form a simple inverter circuit, with the inverted output going to pin 2 (RxD) of the serial connector. The pull-up voltage for RxD comes from pin 7 (RTS) of the serial

connector, so the voltage will be correct for whatever device is connected — be it a PC or whatever else you have. Q2 and R2 are another inverter, driven by TxD from pin 3 of the serial connector. The pull-up voltage for R2 should be supplied by the low-voltage device — your radio or microcontroller project.

There you go. Two cheap little MOSFETs, two resistors. The 2.2 k $\Omega$ ,  $\frac{1}{4}$  W resistors, seem to work with every serial port tried so far. The author has sold several hundred kits using this exact circuit for the serial interface without issues from any users. It's been tested with laptops, desktops, USB-to serial-converters, a serial LCD display and even a Palm-III with an RS-232 serial cable. It's also been used with very slight modifications in computer interfaces for VX-7R and FT-817 transceivers. It's simple, cheap and works great — what more could you ask?

## 24.10 USB Interfaces For Your Ham Gear

Over the past several years, serial ports have been slowly disappearing from computers. The once-ubiquitous serial port, along with other interfaces that were once a basic part of every computer system, has largely been replaced by Universal Serial Bus (USB) ports. This presents problems to the amateur community because serial ports have been and continue to be the means by which we connect radios to computers for control, programming, backing up stored memory settings, contest logging and other applications. Radios equipped with USB ports are rare indeed, and many of the optional computer interface products sold by ham manufacturers are serial-only. The project described here by Dale Botkin, NØXAS, offers a solution.

### THE UNIVERSAL SERIAL BUS

So what is USB, and how can it be used in the ham shack? The USB standard came about during the early 1990s as a replacement for the often inconvenient and frustrating array of serial, parallel, keyboard, mouse and various other interfaces commonly used in personal computer systems. The idea is to use a single interface that can handle multiple devices sending and receiving different types of data, at different rates, over a common bus. In practice, it works quite well because of the very well defined industry specification for signal levels, data formats, software drivers and so forth.

At least two and sometimes as many as six or more USB ports are now found as standard equipment on nearly all new computer systems. Support for USB ports and generic USB devices is built into most operating systems including *Windows*, *Linux*, *Solaris*, *Mac OS* and *BSD* to name a few. USB use has spread beyond computers, and the standard USB “B”


or the tiny 4-conductor “Mini B” connectors are now found on all manner of electronic devices including cameras, cell phones, PDAs, TVs, CD and DVD recorders, external data storage drives and even digital picture frames. USB is indeed becoming *universal*, as its name implies — everywhere, it seems, except for Amateur Radio gear!

The EIA-232 serial interface specification we have used for decades is just that — an electrical interface specification that defines voltage levels used for signaling. The asynchronous serial format most commonly used with serial ports defines how data is sent over whatever interface is being used. Any two devices using the same protocol and format can talk to each other, whether they are both computers, both peripheral devices (like printers, terminals or TNCs) or any combination. All that is required is the proper cable and the selection of matching parameters (speed, data bits, handshaking) on each end of the connection.

This is not the case with USB devices. USB uses a tiered-star architecture, with well defined roles for the host controller (your computer) and devices. Devices cannot communicate directly with each other, only with a host.

See **Fig 24.39**. At the top of the stack is the *host controller device* (HCD), usually your computer, which controls all communication within the USB network. The computer may have several host controllers, each with one or more ports. The host controller discovers, identifies and talks to up to 127 devices using a complex protocol. No device can communicate directly with another device; all communication is initiated and controlled by the host controller. As a result, you cannot simply connect two USB devices together and expect them to communicate. (Some USB printers will talk directly to digital cameras because the printer also has a host controller built in.)

As you have probably already figured out, moving from serial to USB is not a simple

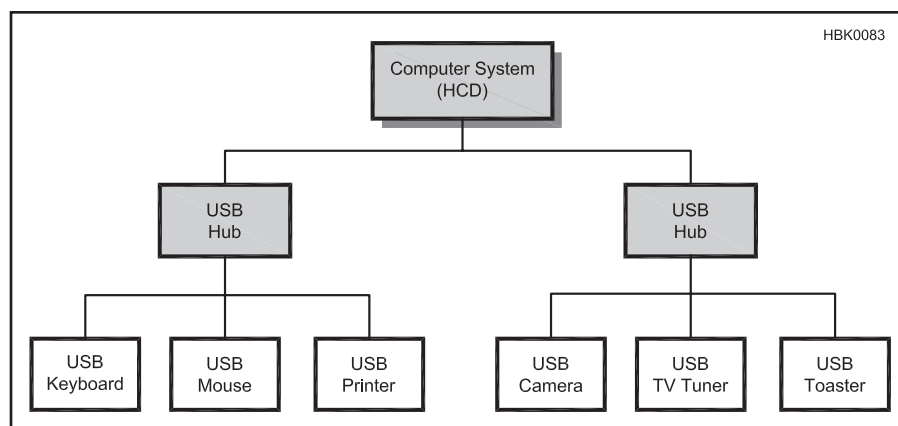

**Fig 24.39 — Typical USB architecture.**



matter of converting voltage levels or even data formats. USB devices all need some embedded “smarts,” usually in the form of either a dedicated USB interface chip or a microcontroller using firmware to talk to the USB host. Where we could once use simple transistor circuits to adapt RS-232 serial to the TTL voltage levels used by many radios, we now must add the complete USB interface into the picture.

The USB specification is freely available and well documented, and there are books dealing with designing the software to use the interface. If you’re starting from scratch it is a very daunting task to even understand exactly how USB works, let alone design and build your own USB-equipped device. If you’re willing and dedicated enough, you can implement your own USB device using a fairly broad range of available microcontrollers. There are also dedicated function chips that implement a complete USB interface — or parts of it — in one or two devices.

Fortunately, several manufacturers have stepped up to make using USB relatively easy for the experimenter. One of the most commonly used solutions is from Future Technology Devices International (FTDI). FTDI manufactures a line of USB interface chips that plug into the Universal Serial Bus on one side and present a serial or parallel interface on the other side. The chips are quite versatile and are commonly used to add USB functionality to a wide range of devices ranging from cell phones to USB-to-serial cables. They are also available in several forms such as plug-in modules with a USB connector and the interface logic, all on a small PC board with pins that can be plugged into a standard IC socket.

## CONSTRUCTION

This project uses an FT232R series chip from FTDI to bridge the USB interface from your computer to a TTL-level serial interface that can be adapted to use with many different ham rigs. The chip has built-in logic to handle the USB interface, respond to queries and commands from the computer, and send and receive serial data. By using special drivers available from FTDI (and built into *Windows* and many other systems), it can appear to your programs as a standard serial COM port.

Once the conversion to serial data is done, all that remains is to adapt the signals to the particular interface used by your equipment. In many cases, this serial data can simply be connected directly to the rig using the appropriate connector. In others it may require some extra circuitry to accommodate various interface schemes used by manufacturers. The most common is an open-collector bus type interface, which is easily accommodated using a few inexpensive parts.

Construction of this project can be handled in a couple of different ways. The FT232R series chips are available from various sup-

pliers at low cost. Unfortunately they are only available in SSOP and QFLP surface mount packages that can be difficult to work with unless you use a custom printed circuit board. (An additional letter is tacked onto the part number to identify the package. For example, the FT232RL uses a 28-pin SSOP package.) There are SSOP-to-through-hole adapter boards available, but they are relatively expensive and still require some fine soldering.

Fortunately FTDI also sells a solution in the form of the TTL-232R (Fig 24.40). It incorporates a USB “A” connector, an FT232RQ chip and the required power conditioning on a tiny PCB encapsulated in plastic, all about the size of a normal USB connector. A 6-ft long cable terminates in a 6-position inline header that provides ground, +5 V, and TTL level TxD, RxD, RTS and CTS signals.

You can connect these signals directly to your own microprocessor projects and have an “instant” USB connection. You can also build a variety of interface cables or boards for use with different radios. This arrangement is ideal for the experimenter and the person who might need several different interfaces for use with several different rigs — like many of us! The cost of the TTL-232R cable is quite reasonable, in fact lower than the cost of having a prototype PCB made to build your own equivalent device. Of course that option is still available to those who need more flexibility.


## USING USB IN THE SHACK

With the USB-to-serial conversion handled so easily, the only remaining task is to adapt the TTL-level serial interface of the FT232R to the interface used by your particular radio. In the case of some rigs, such as the Yaesu FT-817, Kenwood TM-G707A and many others, it’s simply a matter of wiring up the right connector, as shown in Fig 24.41.


For communicating with individual ICOM and Ten-Tec rigs, one simple solution is to simply connect the transmit and receive data signals together and wire up a 1/8-inch stereo plug as shown in Fig 24.42. This will work with a single device connected, but lacks the open-collector drivers needed to be compatible with attaching multiple devices to the CI-V bus.




**Fig 24.40 — The FTDI TTL-232R cable simplifies construction.**

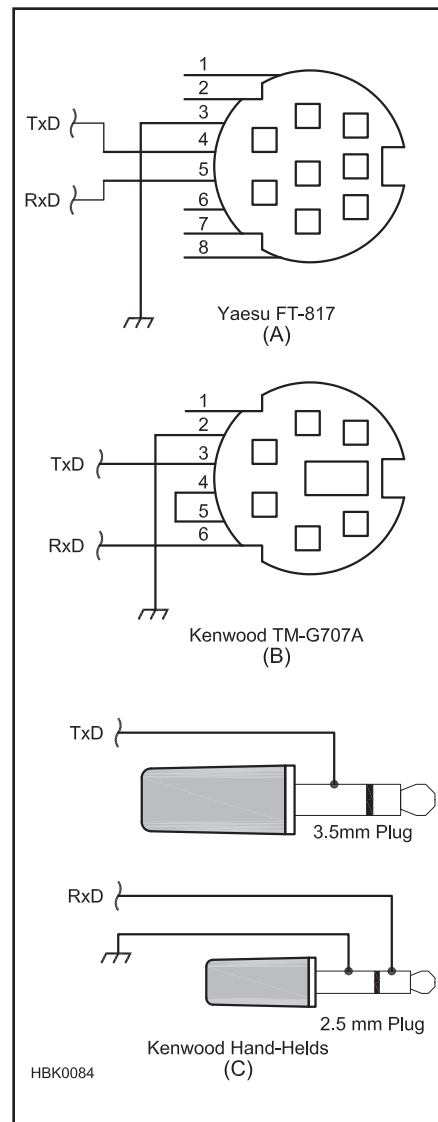

**Fig 24.41 — Using the FTDI USB-to-serial interface with some radios is as simple as wiring up a connector. Connections for the Yaesu FT-817 are shown at A, the Kenwood TM-G707A (PG-4 type) at B, and Kenwood hand-helds (PG-5 type) at C. Ground, RxD and TxD connections are made to the 6-pin connector on the TTL-232R cable.**

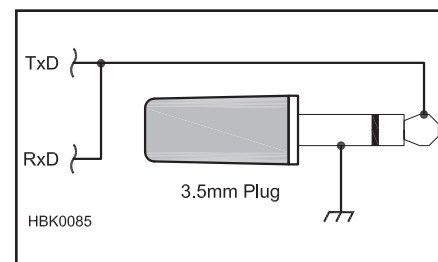

**Fig 24.42 — The transmit and receive data signals can be connected together for use with a single Ten-Tec or ICOM CI-V device.**

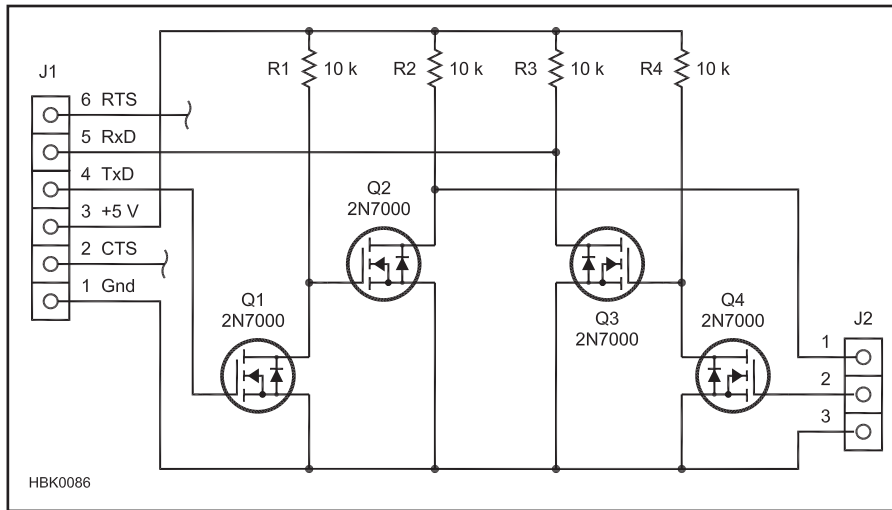


**Fig 24.43 — Schematic of the basic interface buffer board.**

**J1** — 6-pin, 0.1-in pitch header to match TTL-232R cable.

**J2** — 3-pin header to match radio cable.

**Q1-Q4** — Small-signal MOSFET, 2N7000, BS-170 or equiv.

**R1-R4** — 10 k $\Omega$ , 1/4 W.

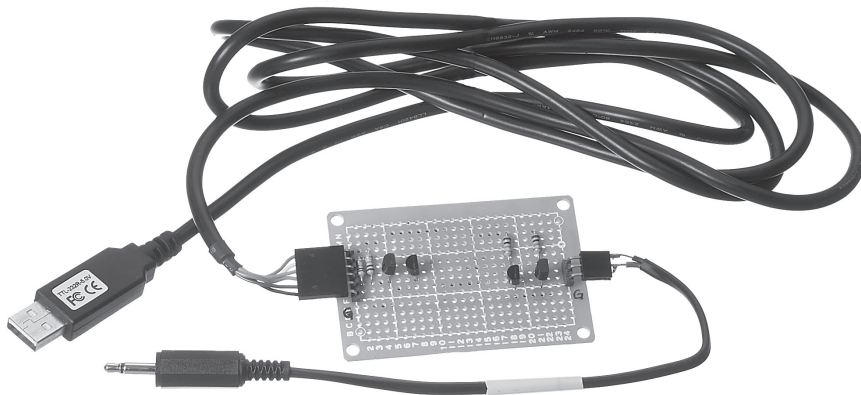

**Fig 24.44 — The completed buffer board. Adapter cables for various radios plug into the header on the right edge of the board.**

### A LITTLE MORE VERSATILITY

Many hand-held transceivers use a single data line for both transmit and receive. This method is very similar to CI-V, but requires an open-collector or open-drain configuration for a single device. Some additional buffering is required to provide an interface to the rig.

**Fig 24.43** shows the design of the general-purpose buffer board for use with various radios. This circuit simply provides a noninverting, open-drain buffer for data in each direction. Adapters for various rigs can be plugged into J2 with no further changes needed. Use of MOSFETs instead of their bipolar counterparts simply reduces the parts count. No additional resistors are needed to limit base current, as you would need when using 2N2222 or similar transistors. Parts can be mounted on a small project board as shown in **Fig 24.44**.


This arrangement turns out to be extremely versatile and will work with CI-V, FT-817,

Yaesu VX-series handhelds and the other rigs the author was able to test as well. All that is required is the proper adapter cable from the base interface board to the rig. Some examples are shown in **Fig 24.45**.

### ADDING PTT

Handling PTT is quite simple, and it can be done either with or without isolation as shown in **Fig 24.46**. For a non-isolated PTT line, we can simply drive the gate of a 2N7000 or similar MOSFET from the FT232RL's RTS output. If you prefer an optically isolated PTT output, all you need to add is one resistor and an optocoupler such as a 4N27 or PS-7142. Note that the TTL-232R provides a 100  $\Omega$  resistor in series with the RTS signal (the same is true for TxD), so a smaller value resistor (R1) can be used for the optocoupler's input than you would normally use.


While connecting the data lines directly to the rig is a suitable solution for many ap-

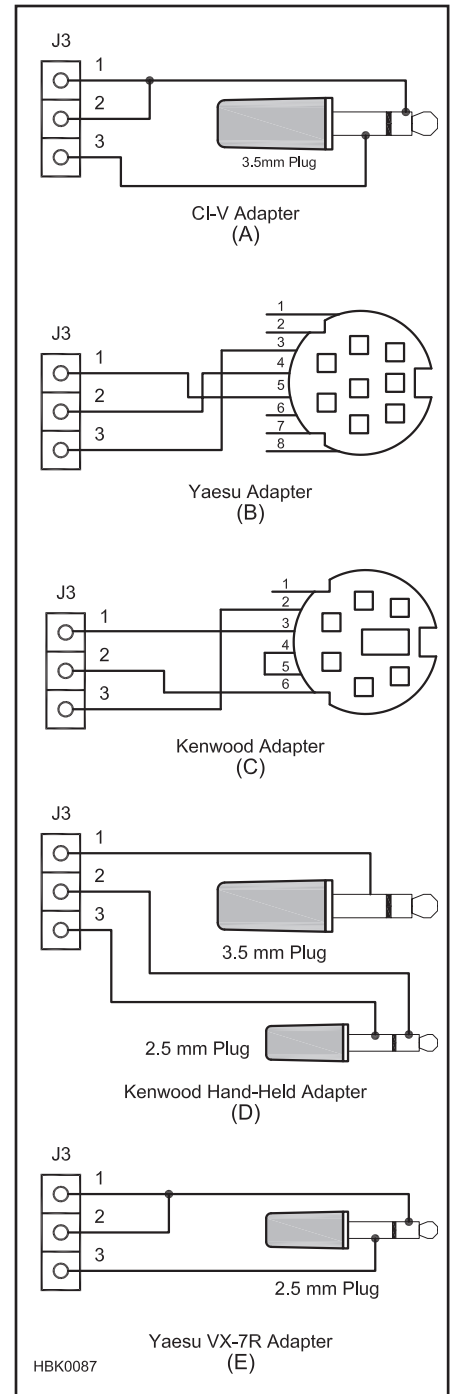

**Fig 24.45 — Adapters for using the buffer board with various radios. J3 matches the adapter used on the buffer board.**


plications, some Kenwood HF rigs require a different approach. They require inverted TTL-level data, and may experience “hash” noise from the computer when not using an isolated interface. **Fig 24.47** shows an optically isolated method of connecting to a Kenwood rig such as the TS-850S. Note that this has not been tested but the design is similar to numerous examples of serial interfaces for the TS-850S and similar radios.

It's probably only a matter of time before

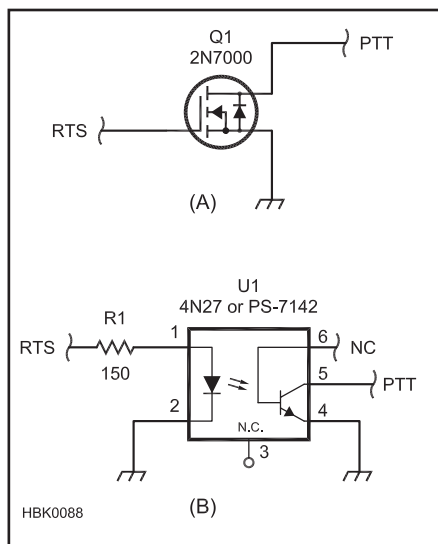

**Fig 24.46 — PTT can be added either without isolation (A) or with an optoisolator (B).**

we start seeing the tiny USB “Mini B” connector appear on new ham gear. It has become inexpensive and easy to add USB to pretty much any product, and as serial ports become more and more rare the manufacturers will eventually face overwhelming consumer demand to switch. In the meantime, you can do a little homebrewing and use your new, serial port free computer to talk to all of your ham gear for very little cost.

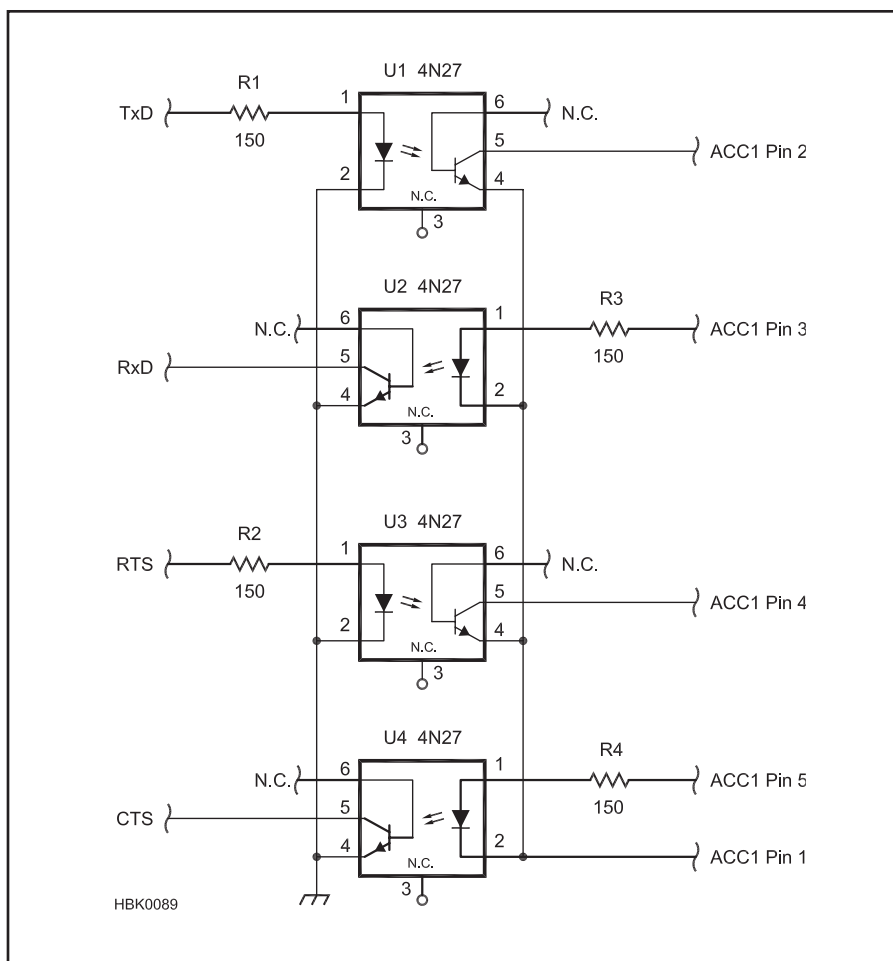


**Fig 24.47 — Isolated Kenwood interface for the TS-850S and similar HF transceivers requiring inverted TTL-level data and isolated lines.**

## 24.11 The Universal Keying Adapter

When Dale Botkin, NØXAS, was about to start restoring his old Heathkit HW-16, he decided it was time to explore what would be needed to key this tube rig using an electronic keyer. He also remembered — not fondly — having been “bitten” a few times when he touched metal parts of the key. There was some substantial voltage on the key, and he wanted to avoid touching it again. The key jack of this rig has a negative voltage, something like –85 V or more. Even the 2N7000 output of a solid-state keyer, rated at 60 V, would be no match for that. The Universal Keying Adapter (UKA) shown in **Fig 24.48** bridges the gap between a modern keyer and a classic tube-type transmitter, and it can also be used to key older tube-type amplifier TR switching lines with solid-state transceivers that can’t handle the voltage or current requirements.

### KEYING SCHEMES

Older gear generally uses one of two keying

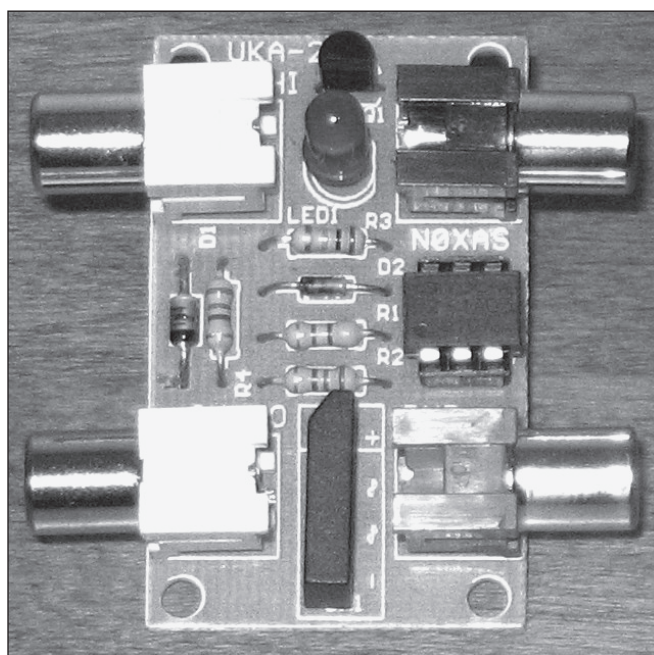

**Fig 24.48 — This version of the Universal Keying Adapter 2 is available as a kit from [www.hamgadgets.com](http://www.hamgadgets.com). Parts count is low, and it can easily be built on a small project board.**



schemes, grid-block or cathode keying. Grid-block keying requires that your key handle fairly high negative bias voltages, often in the 150 V range. Cathode keying is more demanding, with voltages up to +350 V or so. Most modern solid state keyers use a simple transistor output circuit suitable only for low-voltage, positive keying. Obviously, neither grid-block nor cathode keyed transmitters should be connected to such an output! At the very least it's going to damage the keyer.

Most grid-block keying adapters use one or two bipolar transistors and are designed specifically to key grid-block rigs. This is fine as far as it goes, but also requires that you have one setup for solid state rigs, another for grid-blocked rigs, and still another if you have a cathode keyed boat anchor as well. It's not an optimum solution. Of course one could use a relay to key just about anything, but relay contact noise would quickly get really irritating. Relays also eventually wear out, contacts get dirty and the coils can use quite a bit of current, meaning battery powered keyers will suffer from very limited battery life.

## Solid-State Relays

Solid state relays exist, but they can be expensive. The author finally hit upon what seems to be an ideal solution. It's cheap, small, relatively low current, uses low voltage control and is capable of switching fairly high ac or dc voltages. Perfect! Crydom, NEC, Fairchild, Omron and other manufacturers make very similar small, inexpensive MOSFET solid state relays. Suitable model numbers include the NEC PS7142 and PS7342, Fairchild HSR412, Omron G3VM-401B and others. Depending on the part selected they can handle up to a couple hundred milliamps and will switch up to 400 V ac or dc. All of this in a 6-pin DIP form factor, and for just a few bucks!

The MOSFET solid-state relay (SSR) is very similar to an optoisolator, but somewhat more versatile. Ac or dc loads can be switched, and the allowable load voltages are much higher than regular optoisolators. Driving the relay input involves supplying a few mA of current to turn on an LED inside the device. This requires about 1.4 V at a recommended forward current of 10 to 30 mA. The output is a pair of MOSFETs with common sources and a photo gate rather than a hard-wired gate. Turn on the LED and the MOSFETs conduct, turn off the LED and the MOSFETs shut off. Just like a relay, it's simple and elegant.


## KEYING ADAPTER CIRCUITS

For a simple keying adapter arrangement, all that is needed is the MOSFET solid-state relay, one resistor, and a dc power source such as a battery. See Fig 24.49. The keying input from your hand key or electronic keyer completes the input circuit through the cur-

rent limiting resistor and the input side of the SSR, turning the output on. In this example, the value of R1 is determined using Ohm's Law to give between 10 and 30 mA of current at the desired input voltage. For example, for use with two AA alkaline batteries, a range of 100 to 300  $\Omega$  is okay; 150 or 220  $\Omega$  will work reliably with NiCd or NiMH cells as well. If you plan to use a 13.8 V dc power supply, a 1 k $\Omega$  resistor should be fine for R1.

It soon became apparent that other uses existed in addition to just isolating the key or keyer from a transmitter. The addition of a simple transistor inverter allows the use of


computer keying in parallel with input from a straight key, bug or keyer. This is handy, for example, to testers using computers for keying who may need to send some information by hand from time to time. See Fig 24.50. The use of a 2N7000 MOSFET instead of the common NPN transistor makes it easier to accommodate both serial and parallel port use, since the gate will withstand up to 20 V positive or negative and does not need to be current limited. In this example, the value of R1 should be determined as mentioned earlier. R2's purpose is to keep the MOSFET gate from floating, so its value is not critical but

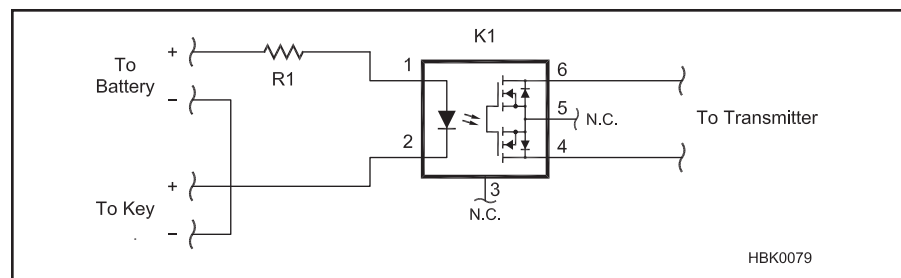

**Fig 24.49** — The original Universal Keying Adapter circuit used a solid-state relay and a battery for power.

**K1** — Optically coupled solid-state relay, Fairchild HSR412 or equivalent.  
**R1** —  $\frac{1}{4}$  W resistor, varies with supply

voltage (see text). Use 150 or 220  $\Omega$  for two AA cells; 1 k $\Omega$  for 13.8 V dc power source.

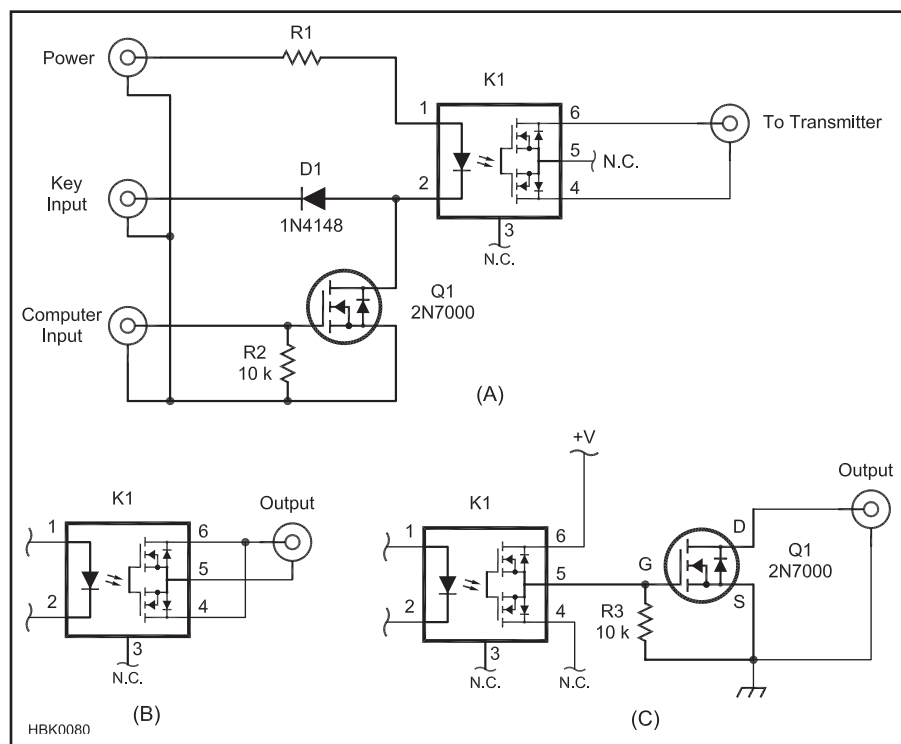

**Fig 24.50** — The Universal Keying Adapter circuit with provisions for using computer keying in parallel with a hand key or keyer. Two methods of increasing the load current capacity are shown at B and C (see text for discussion).

**K1** — Optically coupled solid-state relay, Fairchild HSR412 or equivalent.  
**R1** —  $\frac{1}{4}$  W resistor, varies with supply

voltage (see text). Use 150 or 220  $\Omega$  for two AA cells; 1 k $\Omega$  for 13.8 V dc power source.

10 k $\Omega$  or 100 k $\Omega$  are good values.

The design eventually evolved to include a full-wave bridge rectifier allowing either ac or dc input, a Zener diode for voltage regulation and an LED keying indicator. The result was the Universal Keying Adapter 2, which is also available in kit form (see [www.hamgadgets.com](http://www.hamgadgets.com)). The UKA-2 can accept any dc or ac power source up to about 30 V, and is adaptable to lower power battery operation by substituting or eliminating some of the power supply parts.

### OTHER CONFIGURATIONS

It is worth noting that if only positive or only negative voltages will be used, the output current capacity can be greatly increased and the on-state resistance greatly decreased by connecting the two MOSFET drain outputs in parallel rather than serial. An example of this is shown in Fig 24.50B. For the HSR412, maximum load current increases

from 140 mA for series output to 210 mA for parallel. An added feature of this arrangement is the presence of the intrinsic “body diodes” of the MOSFETs. If you are keying an amp that has an internal keying relay, this can serve to absorb some of the back EMF when the relay releases. Note that this arrangement requires that pin 5 of the IC be at a lower voltage than the other two pins — in other words, ground for positive keying, or  $-V$  for negative keying. Since the output is completely isolated from the input, the polarity of the output connector can be changed without the risk of exposing your other gear to dangerous voltages.

Although the IC solid-state relays are good for a wide range of uses, there are applications that present more of a load than the device is able to safely handle even with the outputs in parallel. For loads of more than the rated device current, an external

MOSFET switch can be used. Again, the resulting output is optically isolated from the input. Resistor R3 shown in Fig 24.50C keeps the gate of the 2N7000 MOSFET low until the input is activated, so its value is not critical. The gate voltage  $+V$  needs only to be within the safe range for the device selected; in most cases 12 V will do fine.

The UKA design works well with both grid-block and cathode keyed rigs, as well as solid state. It's been tested with a TS-930SAT, Heath HW-16, FT-817, Rock-Mites, FT-480R and more. It has also been used with cathode keyed rigs such as the Heath DX-40, and many more examples of this circuit are in use keying various “boat anchor” rigs and amps. It works quite well to key older tube power amplifiers with solid-state transceivers that are not equipped with suitable keying relays or circuits. The input works well with any rig, key, electronic keyer, serial or parallel port tried so far.

## 24.12 The TiCK-4 — A Tiny CMOS Keyer

TiCK stands for “Tiny CMOS Keyer” and this is the fourth version of the chip. It is based on an 8-pin DIP microcontroller from Microchip Corporation, the PIC12CE674. This IC is a perfect candidate for all sorts of Amateur Radio applications because of its small size and high performance capabilities. This project originally used the TiCK-2 chip (based on the PIC12C509) and was described fully in Oct 1997 *QST* by Gary M. Diana, Sr, N2JGU, and Bradley S. Mitchell, WB8YGG. The keyer has the following features:

- Mode A and B iambic keying.
  - Low current requirement to support portable use.
  - Low parts count consistent with a goal for small physical size.
  - Simple rig and user interfaces. The operator shouldn't need a manual and the rig interface should be paddles in, key line out.
  - An audible sidetone for user-feedback functions and to support transceivers without a built-in sidetone.
  - Paddle select, allowing the operator to swap the dot and dash paddles without having to rewire the keyer (or flip the paddles upside down!).
  - Manual keying to permit interfacing a straight key (or external keyer) to the TiCK.
- New for the TiCK-4 version are:
- Two 50-character message memories (up from one).
  - Remembers operating parameters (but not

message memories) when power is removed.

### DESIGN

Fig 24.51 shows the schematic for the keyer. The PIC12CE674 has 3.6 kbytes of program read-only memory (ROM) and 128 bytes of random-access memory (RAM). This means that all the keyer *functions* have to fit within the ROM. The keyer *settings* such as speed, paddle selection, iambic mode and sidetone enable are stored in RAM. Unlike the previous TiCK keyers, this microcontroller also includes EEPROM memory that's used to store these operating parameters. So you can power the chip off, and upon power-up it will remember the last stored values for the settings.

A PIC12CE674 has eight pins. Two pins are needed for the dc input and ground connections. The IC requires a clock signal. Several clock-source options are available. You can use a crystal, RC (resistor and capacitor) circuit, resonator, or the IC's internal oscillator. The authors chose the internal 4-MHz oscillator to reduce the external parts count. Two I/O lines are used for the paddle input. One output feeds the key line, another output is required for the audio feedback (sidetone) and a third I/O line is assigned to a pushbutton.

### USER INTERFACE

Using the two paddles and a pushbutton, you can access all of the TiCK's functions.

Certain user-interface functions need to be more easily accessible than others; a prioritized list of functions (from most to least accessible) is presented in **Table 24.9**.

The TiCK employs a *single button interface* (SBI). This simplifies the TiCK PC board, minimizes the part count and makes for ease of use. Most other electronic keyers have multibutton user interfaces, which, if used infrequently, make it difficult to remember the commands. Here, a single button push takes you through the functions, one at a time, at a comfortable pace (based on the current speed of the keyer). Once the code for the desired function is heard, you simply let up on the button. The TiCK then executes the appropriate function, and/or waits for the appropriate input, either from the paddles or the pushbutton itself, depending on the function in question. Once the function is complete, the TiCK goes back into keyer mode, ready to send code through the key line.


The TiCK-4 IC generates a sidetone signal that can be connected to a piezoelectric element or fed to the audio chain of a transceiver. The latter option is rig-specific, but can be handled by more experienced builders.

### THE TiCK LIKES TO SLEEP


To meet the low-current requirement, the authors took advantage of the PIC12CE674's ability to *sleep*. In sleep mode, the processor shuts down and waits for input from either of





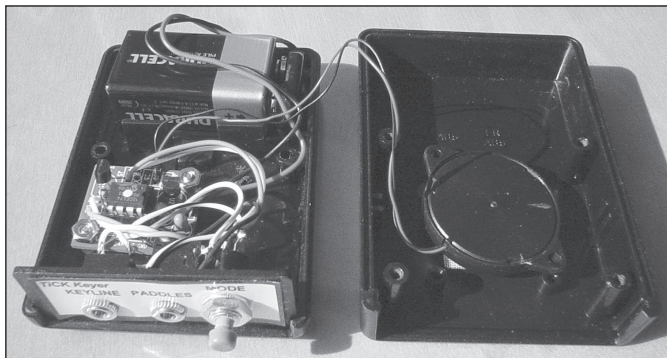

**Fig 24.52** — Here's the completed TiCK-4 keyer complete with battery, mounted in a small case. (Photos courtesy Bill Kelsey, N8ET)

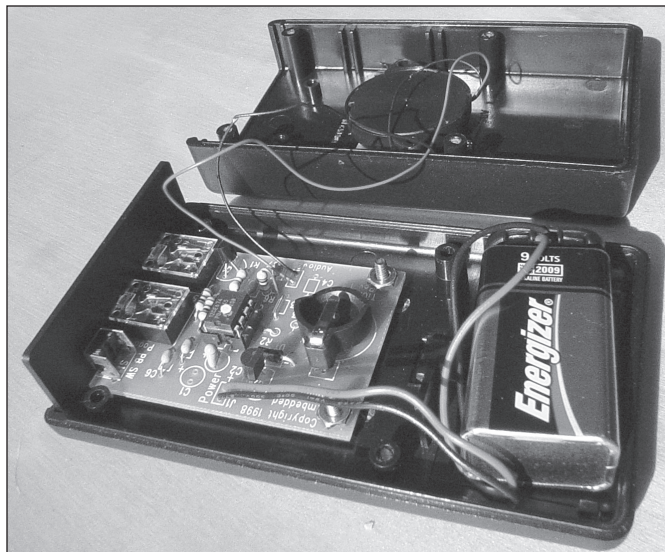

**Fig 24.53** — The enhanced EMB version of the TiCK-4 includes a low-current regulator, battery backup and board-mounted jacks and switches.

the two paddles. While sleeping, the TiCK consumes about 1  $\mu$ A. The TiCK doesn't wait long to go to sleep either: As soon as there is no input from the paddles, it's snoozing! This feature should be especially attractive to amateurs who want to use the TiCK in a portable station.

### ASSEMBLING THE TICK

The TiCK-4's PC board size (1×1.2 inches) supports its use as an embedded and stand-alone keyer. See **Fig 24.52**. The PC board has two dc input ports, one at J2 for 7 to 25 V and another (J4, AUXILIARY) for 2.5 to 5.5 V. The input at J2 is routed to an on-board 5-V regulator (U2), while the AUXILIARY input feeds the TiCK directly. When making the dc connections, observe proper polarity: There is no built-in reverse-voltage protection at either dc input port.

The voltage regulator's bias current is quite high and will drain a 9 V battery quickly, even though the TiCK itself draws very little current. For this reason, the "most QRP way" to go may be to power the chip via the AUXILIARY power input and omit U2, C1 and C2. Another alternative is use of a low quiescent current 5 V regulator, such as the LP2950CZ-5.0, for U2.

When using the AUXILIARY dc input port, or if *both* dc inputs are used, connect a diode between the power source and the AUXILIARY power input pin, attaching the diode anode to the power source and the cathode to the AUXILIARY power input pin. This provides IC

and battery protection and can also be used to deliver battery backup for your keyer settings.

### SIDETONE

A piezo audio transducer can be wired directly to the TiCK-4's audio output. Pads and board space are available for voltage-divider components. This eliminates the need to interface the TiCK with a transceiver's audio chain. Use a piezo *element*, not a piezo *buzzer*. A piezo buzzer contains an internal oscillator and requires only a dc voltage to generate the sound, whereas a piezo element requires an external oscillator signal (available at pin 3 of U1).

If you choose to embed the keyer in a rig and want to hear the keyer's sidetone instead of the rig's sidetone, you may choose to add R2, R3, C4 and C5. Typically R3 should be 1 M $\Omega$  to limit current. R2's value is dictated by the amount of drive required. A value of 27 k $\Omega$  is a good start. C4 and C5 values of 0.1  $\mu$ F work quite well. C4 and C5 soften the square wave and capacitively couple J6-1 to the square-wave output of pin 3. Decreasing the value of R2 decreases the amount of drive voltage, especially below 5 k $\Omega$ . Use a 20 k $\Omega$  to 30 k $\Omega$  trimmer potentiometer at R2 when experimenting.

### IN USE

To avoid RF pickup, keep all leads to and from the TiCK as short as possible. The authors tested the TiCK in a variety of RF environments and found it to be relatively

immune to RF. Make sure your radio gear is well grounded and avoid situations that cause an RF-hot shack.

The TiCK keys low-voltage positive lines, common in today's solid-state rigs. Don't try to directly key a tube rig because you will likely — at a minimum — ruin output transistor Q1.

To use the TiCK as a code-practice oscillator, connect a piezo element to the audio output at pin 3. If more volume is needed, use an audio amplifier, such as RadioShack's 277-1008.

The higher the power-supply voltage (within the specified limits), the greater the piezo element's volume. Use 5 V (as opposed to 3 V) if more volume is desired. Also, try experimenting with the location of the piezo element to determine the proper mounting for maximum volume.

### SEVERAL VERSIONS

The TiCK keyer has been around for more than 10 years. The TiCK-4 is a direct plug-in replacement for the TiCK-1 and TiCK-2, so if you have built a keyer with an earlier version, you can upgrade to the TiCK-4 and gain the two memories and nonvolatile parameter memory features. The TiCK-3 is a surface-mount version with limited availability. An enhanced version, the TiCK-EMB-4, includes RF/static protection, low quiescent current regulator, battery backup and board-mounted jacks and switches. See **Fig 24.53**.

# 24.13 Adapting Aviation Headsets to Ham Radios

Aviation headsets are widely used for commercial and private aircraft. They have a frequency response well-suited for Amateur Radio and are comfortable when worn for long periods, even with glasses. The noise-canceling aviation microphone and the headphone earmuff's 23 dB isolation of acoustic noise are very helpful in noisy environments and contests. Adapting these headphones for amateur use requires impedance matching for the audio circuits and power for the standard electret microphone. Since aviation headsets are designed to a specific standard, other brands and models should have comparable performance.

## ADAPTING THE HEADPHONE CIRCUIT

The headset earphones may be either 300  $\Omega$  stereo or 150  $\Omega$  monaural (some older sets are series connected 600  $\Omega$ ). The plug fits a standard 1/4 inch phone jack (two or three conductor to match). Stereo versions usually have a mono/stereo switch. If the plug is a mono version, a RadioShack 274-360 stereo-to-mono adapter can be used.


Most radios are designed for 8  $\Omega$  headphones. If your radio works with a Heil Pro Set type headset (200  $\Omega$ ) no additional matching is required. To change the 8  $\Omega$  output to higher impedances, a RadioShack audio output transformer (273-1380) will do the job. Connect the low-impedance winding to the radio's headphone jack and the high-impedance winding to the headset earphones.

## ADAPTING THE MICROPHONE

The microphone cannot be used with current radio models without an adapter. This project provides two different circuits — **Fig 24.54** uses a transformer-based circuit and **Fig 24.55** uses a resistive circuit with variable frequency response. **Fig 24.56** shows the relative size of a typical adapter circuit enclosure.

Aviation headsets use an electret circuit that mimics an old-style carbon microphone. The microphone amplifier requires an industry standard dc supply of 4 V at 15 mA of current. (Most headphones will tolerate higher voltages but the microphone circuit can be damaged if excess voltage is applied directly to the headset.) Current radio models can provide the needed bias voltage at the microphone jack (ICOM and Kenwood provide 8 V, Ten-Tec 9 V, Yaesu 5 V, and so on).

Nominal audio output is 400 mV into a 150-500  $\Omega$  load. A PL068 microphone plug is standard and requires a 0.210 inch three conductor jack. The tip contact is PTT (push-to-talk) and the ring contact carries the audio. A typical amateur transceiver specifies the mic input

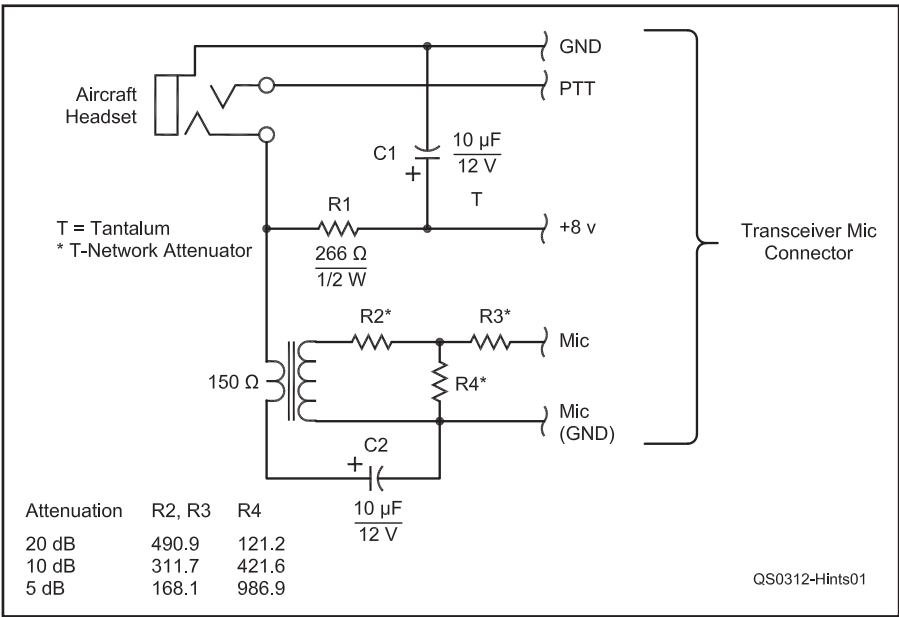

**Fig 24.54 — K5ALQ's transformer-based aviation-headset interface circuit. C1 is optional, but its use is considered best practice. The headset requires a 150  $\Omega$  primary; the secondary must match the load presented by the radio and use appropriate attenuation.**

impedance at 200-10 k $\Omega$ , 600  $\Omega$  nominal.

## TRANSFORMER-BASED ADAPTER

The adapter in Figure 24.54 provides proper bias to the headset microphone, removes dc from the primary of the transformer, matches the impedance of the headset output and provides appropriate attenuation for the necessary match of level and impedance to an amateur transceiver. The value of R1 is selected for a bias voltage of 8 V. To operate properly with 9 V bias from a radio or battery, R1 should be 330  $\Omega$ , 1/2 W. For 5 V bias, R1 should be 68  $\Omega$ .

A Digi-Key 237-1122ND transformer is used with 600  $\Omega$ /150  $\Omega$  primary and secondary windings. Connect the 150  $\Omega$  winding to the headset microphone and the 600  $\Omega$  secondary to the radio. The 600  $\Omega$  T-network 20 dB attenuator values for R2 and R3 are 490.9  $\Omega$  each, and R4 is 121.1  $\Omega$ . Since these are not standard values, use resistors with close tolerances, handpick the resistors, and combine parallel resistors to achieve these values. An alternative is to accept the attenuation yielded by standard-value resistors. Resistor values for other amounts of attenuation are given on the schematic.

## RESISTIVE-ATTENUATOR ADAPTER

A circuit that uses resistive matching is shown in Figure 24.55 (the parts list is in **Table 24.10**). R1 provides the load for the microphone. R1 plus R2 supply the dc voltage from the radio (or battery). For Yaesu radios


**Table 24.10**

### Aviation Headphone Adapter Parts List

C1	100 $\mu$ F, 16 V (not needed for Yaesu)
C2, C3	10 $\mu$ F, 16 V
C4	See Table 24.11
C5	0.001 $\mu$ F, 50 V
J1	0.210 3-conductor jack
R1	470 $\Omega$ , 1/4 W
R2	390 $\Omega$ , 1/4 W (not needed for Yaesu)
R3	1/4 W (see Table 24.11)
R4	620, 1/4 W
R5	1/4 W (see Table 24.11)
P1	Plug to match radio microphone jack
S1	SPDT miniature toggle switch
T1	1000 $\Omega$ center-tapped to 8 $\Omega$ audio transformer (RadioShack 273-1380 if needed, see text)

with 5 V, eliminate R2 and C1 and connect R1 directly to the +5 V pin. C2 isolates the circuit from the microphone voltage and C3 isolates bias, if any, from the radio microphone pin (ie, ICOM radios). C5 reduces the chance of RFI via the bias supply. Aviation microphones are designed to be RFI resistant but a 0.001  $\mu$ F capacitor across the circuit output to ground could be added if necessary.

R4 provides the load for the radio mic input circuit. The divider consisting of R3, R5, C4 and R4 reduces microphone audio output to an appropriate level. C4 creates a selectable "DX" rising frequency response. R5 reduces "normal" response by 2 dB to keep average

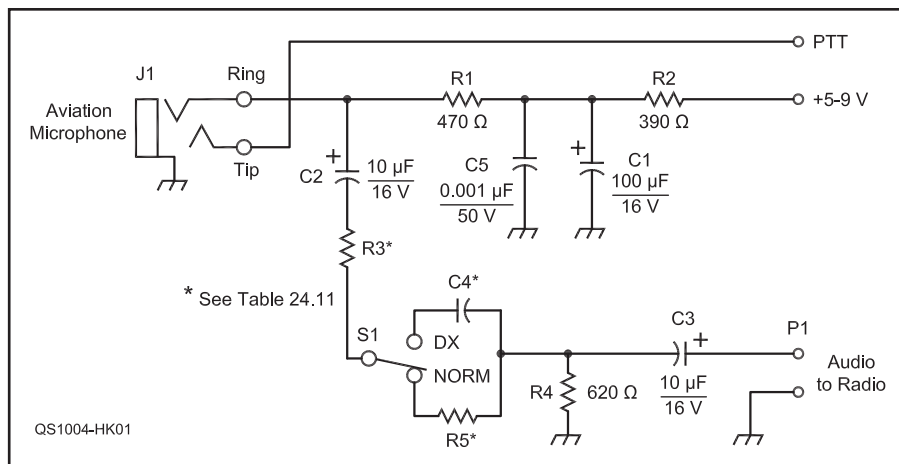

**Table 24.11**

*Aviation Headphone Adapter Microphone Equivalents*

Microphone Equivalent Output	R3	R5	C4
Heil HC-5 (−68 dB)	18 k	3.5 k	0.01 µF
Dynamic microphone (−62 dB)	9.1 k	1.8 k	0.02 µF
Electret (−54 dB)	3.5 k	680	0.05 µF
Older ICOM radios (−46 dB)	1.5 k	300	0.12 µF

output similar to that of the “DX” response.

By selecting different values for R3 (and related R5 and C4) we can adjust the microphone output to match just about any microphone/radio combination. **Table 24.11** lists values to match a popular Heil cartridge, other dynamic and electret microphones (as used by ICOM, Yaesu, Kenwood, etc). Values are also

shown for older ICOM radios such as the IC-745/751/781 and early 706s, which require even higher output. Further adjustments to these values may be required to match radios that require different input levels.

The headset microphone jack is a Switchcraft C12B or S12B. The PTT connection can be ignored if not needed. You will also

need the appropriate plug for your radio's microphone jack. A RadioShack 1×2×3 inch plastic box (270-1801) will accommodate the components. If you also need to include a 9 V battery, a larger 270-1802 box will work.


A spectrum analysis of a SoftComm C-20 headset with this circuit shows the frequency response is flat through 3200 Hz, dropping off rapidly above that frequency. The “DX” frequency response is similar to Heil HC-4 cartridges.

## 24.14 An Audio Intelligibility Enhancer

Here's a simple audio processor (**Fig 24.57**) described by Hal Kennedy, N4GG, that can improve intelligibility, particularly for those with degraded high-frequency hearing. It might just give you an edge in that next DX pileup.

What we understand (intelligibility) of what we hear or detect is strongly affected by the end-to-end frequency response of a given communications circuit. Our equipment typically has a fixed audio bandwidth spanning about 300 Hz to 2700 Hz for SSB operation, but our hearing varies widely from operator to operator and it sometimes varies widely for an individual over the course of his or her life.

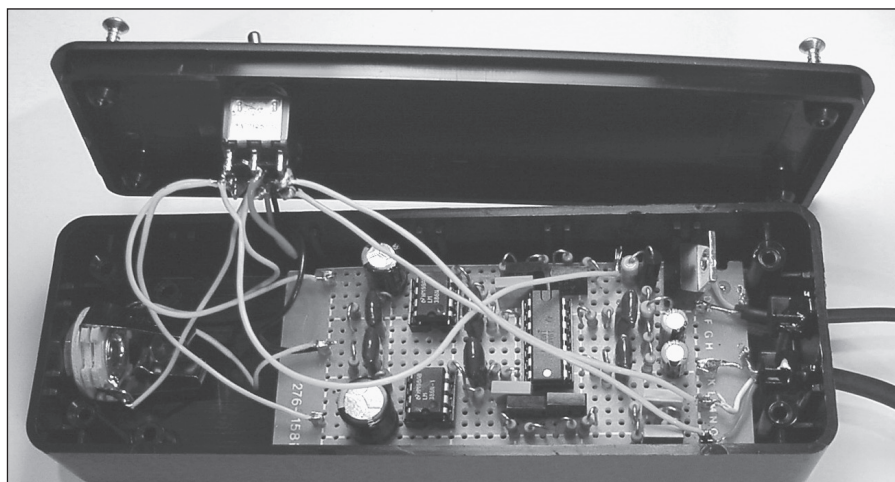Speech intelligibility has been studied extensively since the 1940s. In brief, the “human speech signal” can be thought of as being made up of vowel and consonant sounds. The vowel sounds are low in frequency, with fundamental frequencies typically between





100 Hz and 400 Hz, and harmonics as high as 2 kHz. Consonant sounds occupy higher frequencies — typically from 2 kHz to as high as 9 kHz. (See “Speech Intelligibility Papers” at [www.meyersound.com/support/papers/speech/](http://www.meyersound.com/support/papers/speech/)). In spoken English, vowel sounds contain most of the energy in the speech signal, while consonant sounds are short, noise-like, and convey the majority of intelligibility. When consonants are not heard well, it sounds like the speaker is mumbling. It becomes difficult to distinguish *F* from *S* and *D* from *T*.

Frequently, hearing degradation manifests itself both as a loss of sensitivity over all frequencies and a frequency dependent loss where the sensitivity of our hearing degrades as the frequency increases. Sensitivity loss that is flat over frequency does not affect intelligibility, assuming that levels are high enough to be heard. A simple loss of sensitivity can be addressed by turning up the AF gain! Unfortunately, turning up the gain does not compensate for frequency-dependent loss, and frequency-dependent loss does degrade intelligibility by reducing the ability to hear the consonants in human speech. A quick Web search for “human hearing” will yield a multitude of sites describing the basic concepts.


The author’s audiology test results are shown in **Fig 24.58**. Audiologists refer to this pattern as *age induced hearing loss* — a roll-off of hearing sensitivity as frequency increases. Fortunately, intelligibility can be improved significantly for those with this common condition, by simply adding amplification that increases as a function of frequency.

Hearing deficiencies can be much more complex than the typical high frequency loss associated with aging. One’s hearing can include notches and/or peaking as a function of frequency, as well as significant mismatch between the left and right ears. Most of these can be addressed through use of audio circuits whose gain approximates the inverse function of the hearing problem(s). Analog circuit designs become complex when more than a simple high-pass or single-notch filter is required. Modern high-end hearing aids use DSP circuits that break the audio spectrum into narrow frequency bands, each with programmable gain.

A professional audiology exam and threshold sensitivity test results are recommended as the starting point for determining how much, if any, audio shaping might improve your ham radio activities.

## A VARIETY OF PRACTICAL OPTIONS

The author’s operating interests require stereo operation to make significant use of a transceiver’s dual receiver function when chasing DX, and to operate two radios simultaneously in contests. In each case operation is in stereo, with each ear dedicated to one of

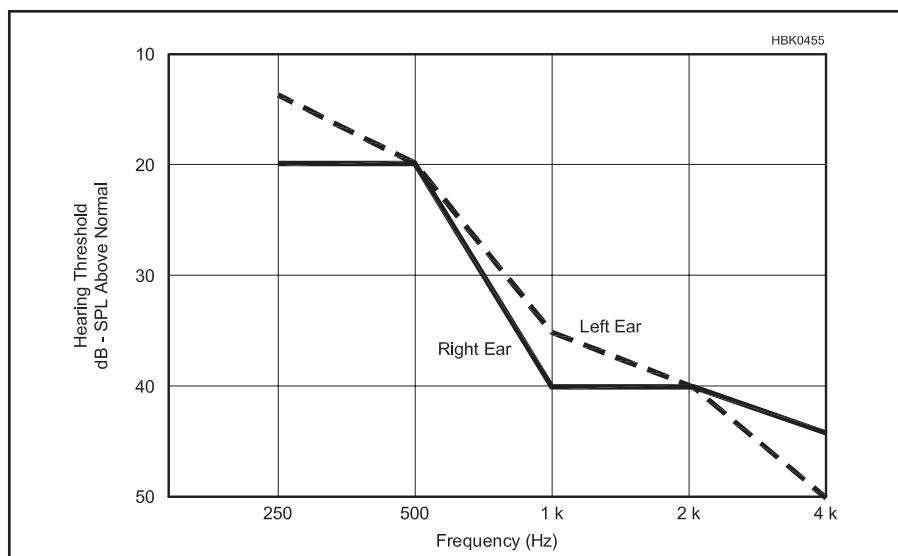


**Fig 24.58 — The author’s audiology exam results. Threshold sensitivity loss as a function of frequency is commonly associated with aging.**

the two receivers. Monaural designs also have a potential drawback, in that the frequency response adjustments apply equally to both ears. In some cases the frequency response of each ear is different.

Stereo equalizers have been around for decades. The most basic are four-band graphic equalizers; they have adjustments to provide up to about 12 dB of gain or attenuation across frequency bands that are centered at four frequencies, each frequency typically one octave

above the next (an octave is a doubling of frequency). Seven, 10, 12 and 15 band equalizers are readily available, allowing for finer tailoring of amplification characteristics as the number of bands go up and the frequency range for each band gets smaller.

Parametric equalizers are also available — these differ from graphic equalizers in that the center frequency and bandwidth of each filter element is adjustable. Prices are very reasonable.

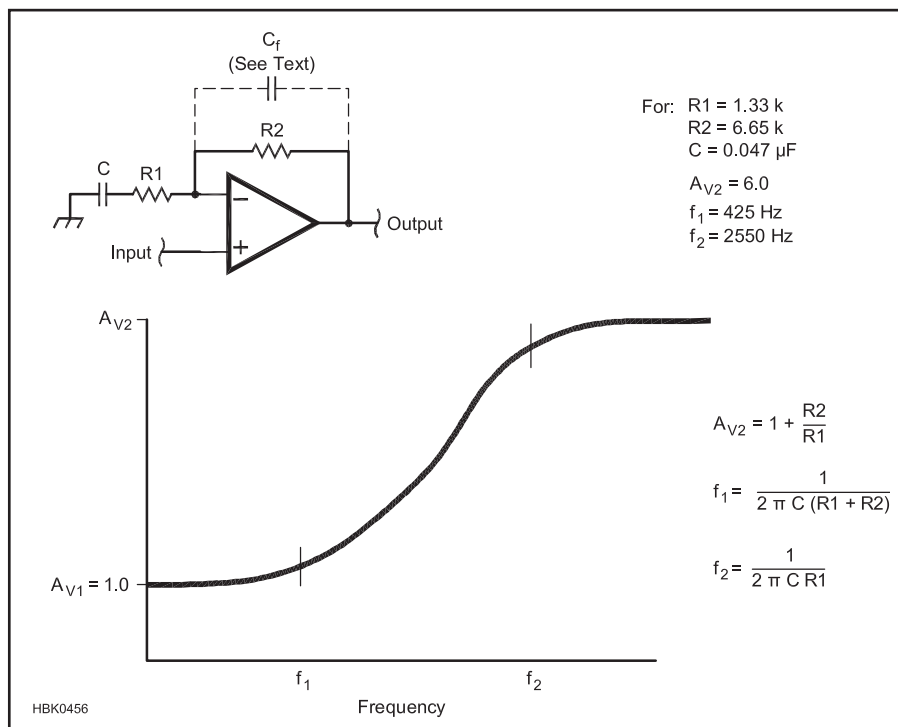

**Fig 24.59 — Schematic and frequency response for a high-pass audio shelving filter.**


An equalizer is a near-perfect solution to compensating for hearing deficiencies, and the ability to readily adjust gain at multiple frequencies allows optimizing via experimentation. Many equalizers are strictly low-level devices and lack sufficient output power to directly drive headphones, requiring an amplifier if the equalizer is to be inserted between rig and headphones.

Some transceivers include adjustable audio DSP circuits for receive as well as transmit audio. It may be possible to adjust the audio response of your transceiver to improve intelligibility without the use of an external device.

### CIRCUIT DESCRIPTION

The heart of this audio intelligibility enhancer (AIE) is what audiophiles refer to as

a *high-pass shelving filter*. Shelving filters are sometimes used in high-end audio systems to compensate for deficiencies in crossover networks or loudspeakers. The basic circuit and its frequency response are shown in **Fig 24.59**. Note that the shape of this response curve is the inverse of the hearing response of Fig 24.58. Referring to Fig 24.59, the circuit provides a gain,  $A_{V1}$ , equal to 1.0 for frequencies some-

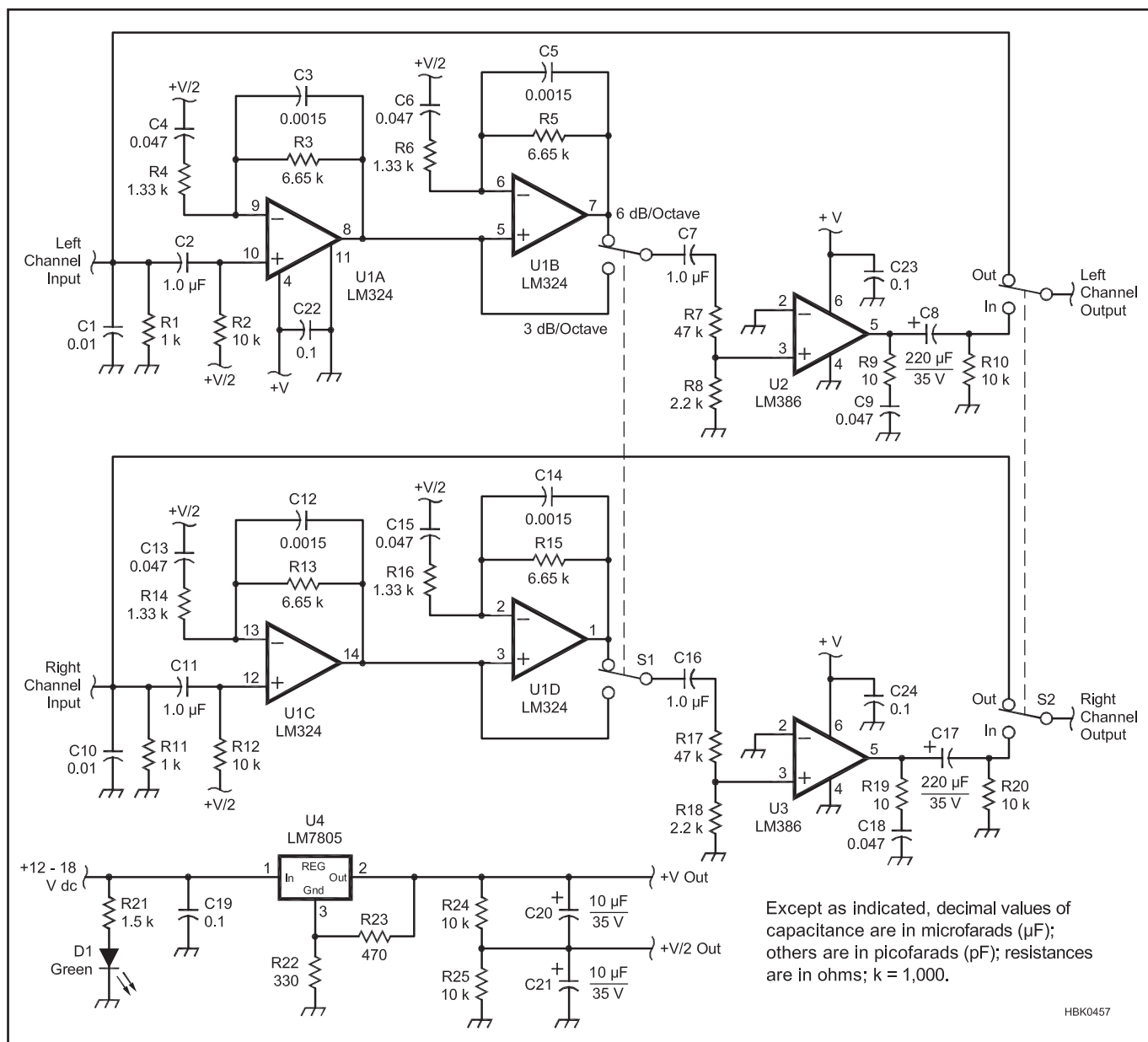

**Fig 24.60** — The audio intelligibility enhancer schematic. Resistors are  $\frac{1}{4}$  W. Parts are available from RadioShack, ([www.radioshack.com](http://www.radioshack.com)) and Mouser Electronics ([www.mouser.com](http://www.mouser.com)) as well as many other suppliers. The part numbers shown in parentheses are RadioShack unless otherwise noted.

C1, C10 — 0.01  $\mu\text{F}$ , 500 V ceramic (272-131).  
C2, C7, C11, C16 — 1.0  $\mu\text{F}$ , 250 V metal film (272-1055).  
C3, C5, C12, C14 — 0.0015  $\mu\text{F}$ , 100 V ceramic (Mouser 80-CK12BX152K).  
C4, C6, C9, C13, C15, C18 — 0.047  $\mu\text{F}$ , 50 V, metal film (272-1068).

C8, C17 — 220  $\mu\text{F}$ , 35 V, electrolytic (272-1029).  
C19, C22, C23, C24 — 0.1  $\mu\text{F}$ , 50 V ceramic (272-109).  
C20, C21 — 10  $\mu\text{F}$ , 35 V, electrolytic (272-1025).  
D1 — LED with holder, green (276-069).  
S1, S2 — Miniature DPDT (275-626).

U1 — LM324 quad operational amplifier (276-1711).  
U2, U3 — LM386 audio amplifier (276-1731).  
U4 — LM7805, +5 V regulator (276-1770).  
Project box, 6x2x1 in (270-1804) (see text).  
Grid-style PC board, 0.1-in centers (276-158) (see text).

what below  $f_1$  and a higher gain,  $A_{V2}$ , that is given by  $A_{V2} = 1 + R2/R1$  for frequencies somewhat above  $f_2$ . Frequency  $f_1$  is given by  $f_1 = 1/[2\pi C(R1+R2)]$ , and frequency  $f_2 = 1/(2\pi CR1)$ . Conveniently available component values of  $R1 = 1.33 \text{ k}\Omega$ ,  $R2 = 6.65 \text{ k}\Omega$ , and  $C = 0.047 \text{ }\mu\text{F}$  yield a high frequency gain,  $A_{V2} = 6.0$ , and cut-on and cut-off frequencies of  $f_1 = 425 \text{ Hz}$ , and  $f_2 = 2550 \text{ Hz}$ . With these values, the circuit gain rises at an average of 3 dB per octave from 300 Hz to 2700 Hz — the frequency range for SSB transmission. For those interested in modifying the design, or using a shelving filter for other purposes, it's important to note that rearranging the equations yields:  $f_2/f_1 = A_{V2}$ . The ratio of the two break frequencies always equals the maximum gain.


Fig 24.59 also shows a feedback capacitor,  $C_f$ , which, while not contributing to the shelving filter function, is included as good design practice. The LM324 op amps used to implement the filters have gain-bandwidth products in excess of 1 MHz. Operating them with gain at frequencies above the useful limits of our hearing (and all the way out to beyond 1 MHz) is an open invitation for RFI problems and unwanted high frequency noise. So, feedback capacitor  $C_f$  provides high frequency gain roll-off above the frequency  $f = 1/(2\pi C_f R2)$  which for the value of  $C_f$  in this design (0.0015  $\mu\text{F}$ ) is 16.8 kHz.

**Fig 24.60** is the complete schematic for the AIE. Two shelving filters, as described above, are used in series in each audio channel. Two filters in series provide sufficient gain change versus frequency to approximately match the author's high frequency hearing loss, which has a slope of about -7.5 dB/octave across the audiologist's measuring points from 250 Hz to 4 kHz. Two filters in series provide +6 dB/octave gain change from 300 Hz to 2700 Hz and 31 dB of total gain ( $A_{V\text{total}} = A_{V2} \times A_{V2} = 6 \times 6 = 36$  or about 31 dB). Some tips for tailoring the circuit to your hearing are included in the next section.

The shelving filters are followed by LM386 audio amplifiers (U2, U3). These provide sufficient output power to drive headphones or small speakers. LM386s have a built-in voltage gain of 20, so they are preceded by 20:1 voltage dividers (R7+R8, R17+R18) to maintain an end-to-end gain of 1 at low frequencies.

Voltage regulator U4 provides regulated and filtered dc voltage to the shelving filters and the output stages. Current draw for the AIE is approximately 35 mA from a +13.6 V dc source, if the LED pilot light (D1) is included. D1 draws 10 mA by itself, however, and R21 and D1 can be deleted if current consumption is a concern. Supply voltage is not critical — anything from 12 to 18 V dc will work.

Capacitors C1 and C10 are used to prevent RFI, by bypassing to ground RF that may enter at the inputs. The original AIE without

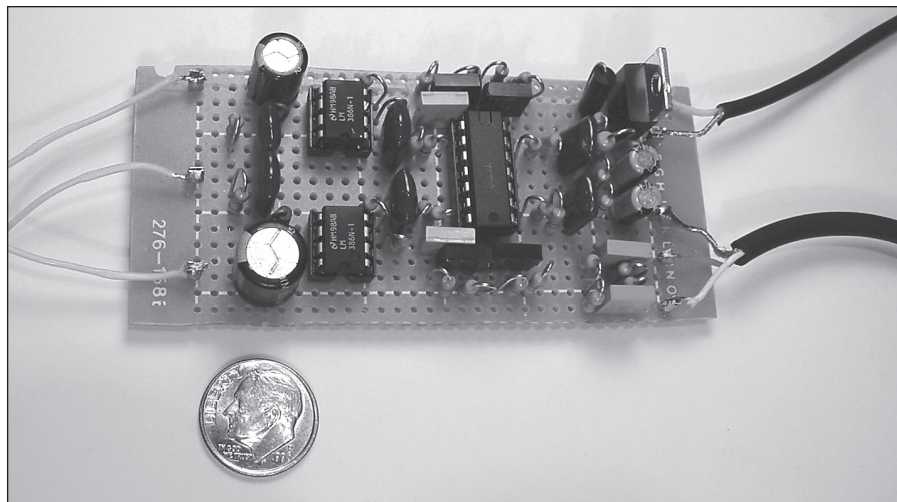

**Fig 24.61** — A close-up of the AIE before mounting in the project box. It all fits neatly within a 6x2x1 inch enclosure if you have the patience to build within tight spaces.

these capacitors suffered interference from loud distorted sounds (unrectified SSB RF) during transmit. C1 and C10 eliminated RFI problems, but they could be insufficient in the presence of large RF fields. If necessary, additional RF filtering can be achieved by adding RF chokes in series with both audio input and output lines.

### TAILORING THE DESIGN TO YOUR HEARING

The AIE design presented here is intended to address high frequency hearing loss, and not other hearing deficiencies. This AIE design does, however, have a reasonable amount of flexibility for tailoring to an individual's hearing.

The design as it is presented in Fig 24.60 includes two shelving filters per channel and switch S1. S1 allows selection of one (3 dB/octave amplification) or two (6 dB/octave amplification) filter stages. If you are the only operator of your station and you know your hearing deficiency is less than about 5 dB/octave, the switch and the second filter in each channel can simply be eliminated. If you are unsure of how much high frequency amplification you might need, or in the case where more than one operator may be sharing a station, the switch and the second stages will prove useful. S1 could also be replaced with two switches — one for each channel — if your high frequency hearing is not similar in both ears.

For gain slopes other than 3 dB/octave or 6 dB/octave, one or both filters in either channel can be modified using the equations given earlier. Taking this further, one or both of the op amps in either channel do not have to be shelving filters — they can be used to implement a variety of other filter functions including notching, peaking, or multi-pole

functions. Op-amp filter design is covered extensively in circuit design handbooks and on the Internet.

In addition to tailoring the gain change versus frequency, the overall gain of each channel can be adjusted to compensate for the sensitivity differences between ears. Overall gain is adjusted by changing the voltage dividers R7+R8 and R17+R18. R8 and R18 can also be replaced with 5-k $\Omega$  potentiometers if adjustable gain is desired.

When considering changing the design, it's important to know that human speech recognition is remarkably tolerant of deviations from an ideal amplitude versus frequency response curve. Also, personal preference comes into play — you may hear more comfortably with less than complete compensation for high frequency hearing loss. Although 6 dB/octave compensation closely matches the author's hearing loss, he usually has the AIE switched to 3 dB/octave compensation. At this setting, intelligibility is improved considerably.

### CONSTRUCTION

With a few exceptions, the layout of the component parts is not critical. The leads on the IC power decoupling capacitors (C22, C23, C24) and all leads to the op amp inputs should be kept as short as possible. Be sure to make the U1 power connections at pins 4 and 11.

The completed AIE is shown in **Figs 24.61** and **24.62**. The prototype is built on a grid style PC board with 0.1 inch centers — these are available from RadioShack — cut to fit snugly in a 6x2x1 inch plastic project box. Parts numbers for the PC board and the project box are included in the parts list. A PC board is available from FAR Circuits ([www.farcircuits.net](http://www.farcircuits.net)).





**Fig 24.62 — The AIE takes up little desk space. It plugs inline between the transceiver and headphones and requires 13.6 V dc. In the author's shack, the unit is powered from a transceiver accessory jack and is always switched on.**

Two cautions are in order. First, building an AIE as small as the prototype requires small tools, a large magnifying glass and patience. Since the circuit design is not particularly sensitive to layout, consider using a larger layout and a larger enclosure. The second caution is with regard to using a plastic enclosure. Susceptibility to RFI and 60 Hz hum pickup will be greatly reduced by using a metal enclosure. If you have lots of RF in your shack you may have no choice but to use a metal enclosure.

Several of the components are not available from RadioShack, but they are readily available from mail order suppliers and can be found in a well-stocked junk box. Several substitutions can be made to yield an "all RadioShack" design. The 1.33-k $\Omega$  resistors can be made from a 1-k $\Omega$  and a 330  $\Omega$  resistor in series; the 6.65-k $\Omega$  resistors can be made from two 3.3-k $\Omega$  resistors in series and the 1.5-k $\Omega$  resistor can be made from a 1-k $\Omega$  and a 470  $\Omega$  resistor in series. The value of the 0.0015  $\mu$ F feedback capacitors

is not critical (C3, C5, C12, C14) — 0.001  $\mu$ F disk ceramics can be substituted (RadioShack 272-126).

### HOW WELL DOES IT WORK?

Intelligibility is absolutely crucial to maintaining high QSO rates and correct logging in contests, and in pulling the weak ones out of the noise when DXing or operating in less-than-ideal conditions. The AIE has provided the author with an immense improvement in both activities. It's just as helpful for reducing listening fatigue during ragchewing or general listening as well.

A real surprise was how much intelligibility improved on CW. This may seem counterintuitive at first, if you view "continuous wave" as comprising a single frequency. From a communications standpoint, however, the CW waveform is not continuous — it is comprised of elements — dots and dashes. The leading and trailing edges of each element are made up of frequencies higher than the carrier frequency, and hearing these helps the listener separate one

element from the next. When the rise and/or fall times of the elements are very fast compared to the carrier frequency, the high frequency content of the waveform becomes sufficiently large to cause key clicks. Very slow rise and/or fall times produce the opposite of clicks — a sound that experienced CW operators describe as "mushy." Mushy code is very difficult to copy, particularly at high speeds, because the ability to decipher when an element has started or stopped has been reduced. Degraded high frequency hearing has the same detrimental effect on CW intelligibility as slowing down the waveform edges — it makes a properly formed CW waveform sound mushy. The AIE restores perception of the waveform edges in CW, just as it does for speech.

How much an AIE or any other approach to compensating for your hearing deficiencies will help you depends, to a large degree, on the state of your hearing. The more you have lost, the more you have to gain back. Audio shaping may also offer some intelligibility improvement if your hearing is within normal limits. Typical receiver bandwidths are narrower than the audio range needed to fully support intelligibility — some of this can be gained back with high frequency amplification.

One cautionary note from Jim Collins, N9FAY, a designer in the hearing aid industry. At low volume levels, a device such as the AIE is helpful in improving intelligibility. At high volume levels, the audio will start to sound "tinny." This happens because as sound levels increase, the corrective frequency curve must flatten. At upper sound levels of comfortable hearing, it becomes almost a flat line with unity gain. In other words, the hearing response is close to normal at high sound levels. If a device like the AIE is used for prolonged periods at high volume levels, it may accelerate hearing loss at upper frequencies. For more discussion, see Technical Correspondence in May 2005 *QST*, p 70.



## 24.15 An Audio Interface Unit for Field Day and Contesting

For Field Day and multioperator contest operation, it's sometimes desirable for a logger or observer to listen to a transceiver in addition to the main operator. The project shown in **Fig 24.63**, by John Raydo, KØIZ, makes two-person operation more efficient. Dual stereo headphone jacks, volume controls and an external speaker jack are provided, as well as jacks for both dynamic and electret microphones and an intercom feature for operator and logger to more easily communicate via headset mics.

There are times when the operator and logger need to talk to each other, for example to resolve a call-sign ambiguity. With this unit the operator can initiate two-way intercom communication by closing an intercom switch. The logger, however, can only initiate one-way intercom to the operator. This is so that the logger can't inadvertently cut off the operator during a contact. To respond, the operator closes his intercom switch. In both instances, radio volume is reduced for "talk-over" during intercom use.

Both the operator and logger need headsets with microphones. The unit has two intercom switches plus jacks for optional foot switches for hands-free operation. Here's how it works:

*Operator communicating with the logger:* The operator presses and holds the OPERATOR TALK switch (S3 on the unit or by using a foot switch connected to J4). This disconnects the operator mic from radio. Both mics are connected via an internal amplifier to both headphones. Radio volume is reduced (adjustable using the RADIO VOL control). Operator and logger can talk to each other.

*Logger communicating with the operator:* The logger presses and holds the LOGGERTALK switch (S4 on the unit or by using a foot switch connected to J5). Logger mic is connected via an internal amplifier to both headphones. Operator mic remains connected to radio and can still transmit on the radio. Radio volume is reduced. The operator can respond to the logger by pressing the OPERATOR TALK switch.

### CIRCUIT DESCRIPTION

The circuit diagram shown in **Fig 24.64** is designed for use with dynamic microphones such as the HC4 and HC5 elements used in various Heil headsets, or for Heil iC type headsets that use an electret element. The electret mic jacks supply the required dc for that type microphone. Mic bias current is limited to less than 1 mA to avoid damage if a dynamic mic is accidentally plugged into the wrong jack. The higher electret output is reduced by resistors R11 and R28.

Both mics have preamplifiers with 34 dB gain set by the ratio of the resistors R4/R3 and R9/R8. The INTERCOM volume controls, R14 and R15, allow operator and logger to individually adjust their intercom volumes. The preamps feed a single 2-W intercom amplifier.

Closing the OPERATOR TALK switch transfers the operator mic from radio to intercom preamp and amplifier via K1 and then to the headphones via K2. Pressing the LOGGERTALK switch will also activate K2 (but not K1). During intercom use, audio from the radio passes through control R20 (RADIO VOL) at reduced volume. S2 (L+R) allows selection of both

left and right sides of the headphones or only the right side, for the intercom. The operator and logger each have individual headphone PHONE VOL controls R24 and R25 (the operator control also incorporates the POWER switch, S1).

### CONSTRUCTION

The unit shown is built in a PacTec plastic box. The front panel has the control switches and volume controls described in the previous section. The back panel (**Fig 24.65**) has ¼-inch stereo jacks for two pair of headphones, two 3.5-mm mono jacks for headset microphones, 3.5-mm stereo and mono jacks for connection to the radio's headphone and mic jacks, one stereo 3.5-mm jack for a speaker, two 3.5-mm mono jacks for foot switches and a jack for a 9-V power supply (a wall wart is okay). A 12-V dc supply can be substituted if K1 and K2 are changed to 12-V units and the LED series resistors R22 and R23 are changed to 1 kΩ.

Other than controls and jacks, most components are mounted on a RadioShack prototype circuit board supported by four ½ inch spacers and shown in the box in **Fig 24.66**. A suggested parts layout is shown in **Fig 24.67**. Point-to-point wiring is used between circuit board pads and is not particularly critical. A PC board for this project has been developed by FAR Circuits ([www.farcircuits.net](http://www.farcircuits.net)).


Connections to both mic jacks and the radio mic jack use shielded cable to reduce hum and risk of interference pickup. Connect the shields on the operator and radio mic cables to a common ground point on the circuit board near U1. Bypass capacitors C8, C9 and C16 and resistor R6 are mounted at their respective jacks. Rub-on lettering, followed by a couple light coats of clear plastic spray, helps give a professional appearance.

Connecting an external speaker in addition to two headphones might be too much of a load for some radios and cause reduced volume and/or distortion. Try an inexpensive amplified computer speaker plugged into the audio interface external speaker jack to reduce the load.

You will need two cables to connect the unit to your radio. A 3.5 mm mono plug-to-plug shielded cable for the mic circuit is compatible with a Heil headset mic. A 3.5 mm stereo plug-to-plug cable (RadioShack 42-2387 plus 274-367 adapter) works for the earphones.



**Fig 24.63** — Front view of the audio interface box. Operator controls are on the left and logger controls are on the right.

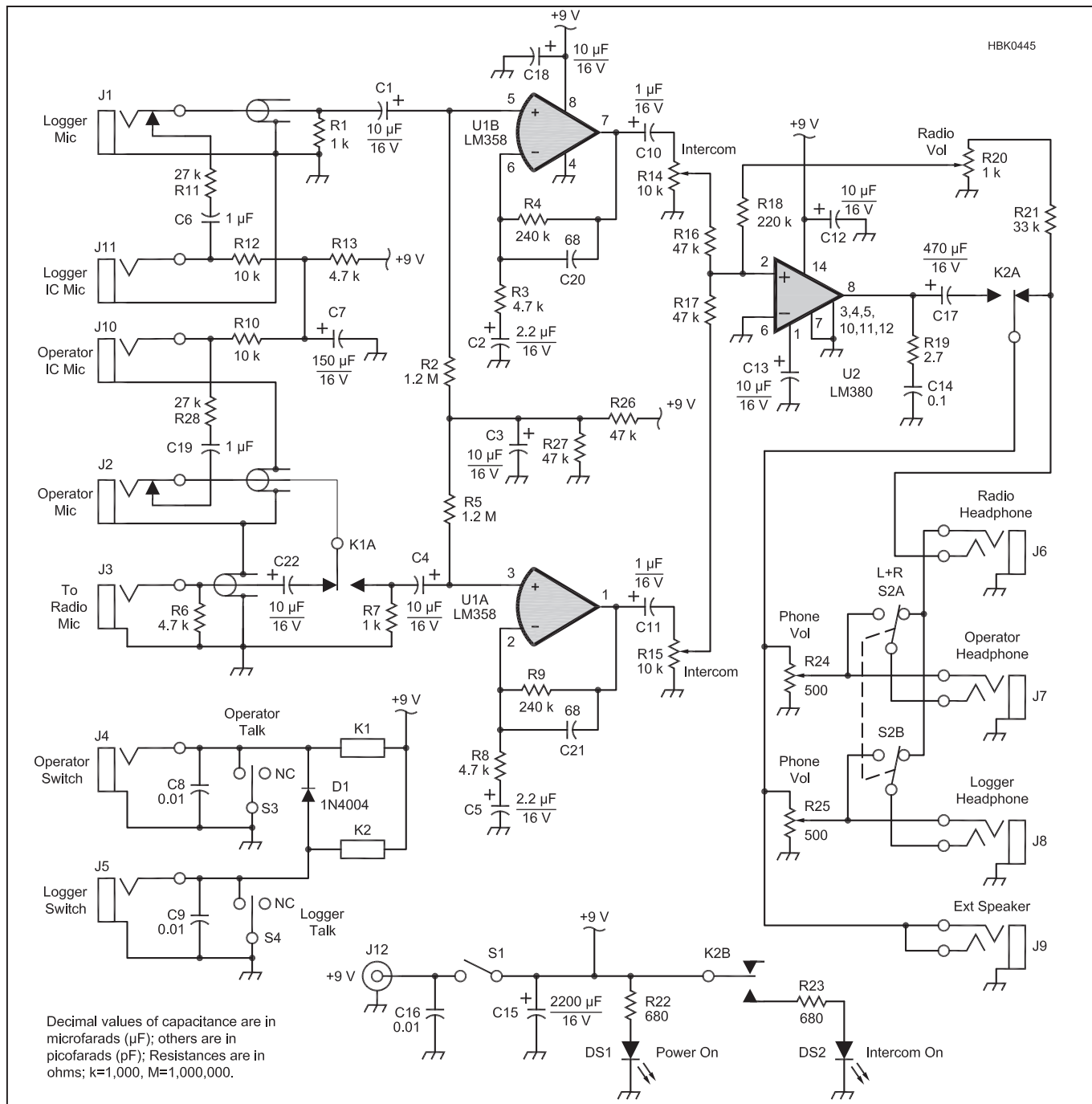

**Fig 24.64 — Schematic diagram and parts list for the audio interface unit. Mouser parts are available at [www.mouser.com](http://www.mouser.com), RadioShack parts at [www.radioshack.com](http://www.radioshack.com). Resistors are  $\frac{1}{4}$  W unless notes ( $\frac{1}{4}$  W are fine too.) A PC board is available from FAR Circuits ([www.farcircuits.net](http://www.farcircuits.net)).**

C1, C3, C4, C12, C13, C18, C22 — 10  $\mu\text{F}$ , 16 V electrolytic.  
 C2, C5 — 2.2  $\mu\text{F}$ , 16 V electrolytic.  
 C6, C10, C11, C19 — 1  $\mu\text{F}$ , 16 V electrolytic.  
 C7 — 150  $\mu\text{F}$ , 16 V electrolytic.  
 C8, C9, C16 — 0.01  $\mu\text{F}$ , 50 V ceramic.  
 C14 — 0.1  $\mu\text{F}$ , 50 V ceramic.  
 C15 — 2200 pF, 16 V electrolytic.  
 C17 — 470  $\mu\text{F}$ , 18 V electrolytic.  
 C20, C21 — 68 pF ceramic.  
 D1 — 1N4004.  
 DS1 — Red LED.  
 DS2 — Yellow LED.  
 J1-J5, J10, J11 — 3.5 mm mono jack, Mouser 16PJ135. Note: This is a

switched jack. The switch contact is not connected on J3-J5, J10 and J11.  
 J6, J9 — 3.5 mm stereo jack, Mouser 161-3402E.  
 J7, J8 — Three conductor  $\frac{1}{4}$  inch jack, Mouser 502-12B.  
 J12 — 2.5 mm jack for dc input, Mouser 502-712A.  
 K1, K2 — DPDT relay, 9 V coil, Mouser 653-G6A-274P40-DC9.  
 R14, R15 — 10-k $\Omega$  potentiometer, Mouser 31JA401-F.  
 R20 — 1-k $\Omega$  potentiometer, Mouser 31JN301-F.  
 R24, S1 — 500- $\Omega$  potentiometer with SPST

switch, Mouser 31VM205-F.  
 R25 — 500- $\Omega$  potentiometer, Mouser 31VA205-F.  
 S2 — DPDT toggle switch, Mouser 10TC260.  
 S3, S4 — SPDT momentary contact switch, center off, with long handle, Mouser 10TA445.  
 U1 — Dual op amp, LM358, Mouser 595-LM358P.  
 U2 — Audio amplifier, LM380 or NTE740A, Mouser 526-NTE740A.  
 Project box, 8 x 4.25 x 2.25 in, Mouser 616-72004-510-000.  
 Circuit board, RadioShack 276-158.



Fig 24.65 — Rear view of the audio interface box. Operator jacks are on the right, logger on the left. Connections to the radio are in the center.

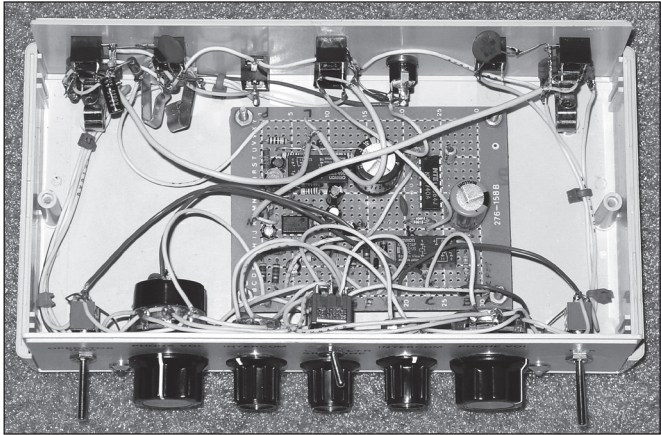


Fig 24.66 — Inside view of the audio interface box. A RadioShack project board is used for most components.

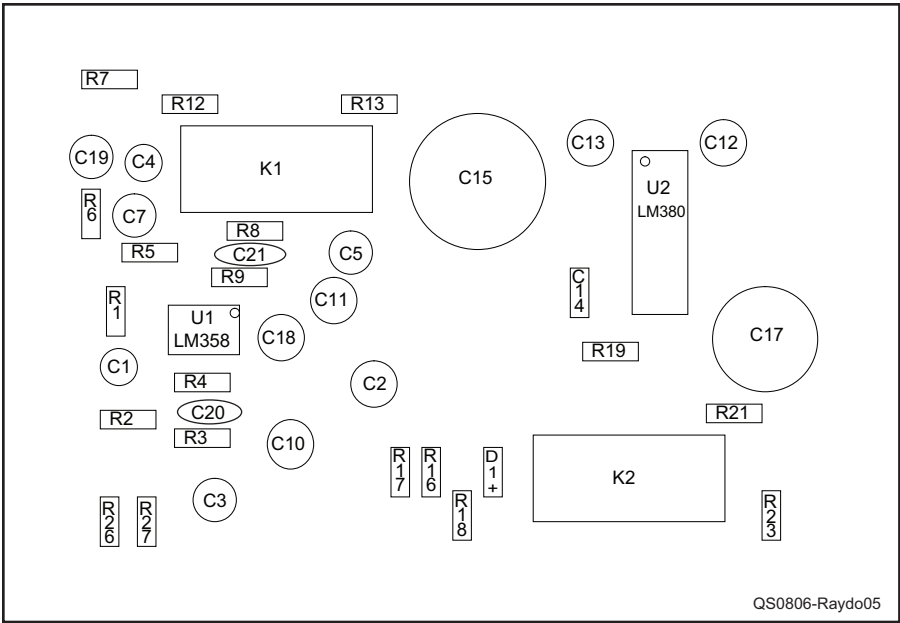


Fig 24.67 — Suggested parts layout for audio interface box.