
A REMOTE POWER CONTROLLER

Some older solid-state transceivers such as the Ten-Tec Triton IV will run from battery power but lack a switch to turn the radio on or off from the front panel. You have to either unplug the power cord or remove the cables from the battery. As designed, the power switch for the Triton IV controls the 120 V ac supply primary circuit in the matching model 262 power supply. The power switch does not, and cannot, handle the more than 20 A at 13.8 V dc the transceiver requires.

Mike Bryce, WB8VGE, developed the remote power controller shown in **Fig 19.75** to solve the problem. It was originally described in September 2007 *QST*. The front power switch on the radio operates normally, but it now controls a large power relay. This relay sends +13.8 V dc to the

radio from any source, be it a battery or an ordinary dc power supply.

What Makes it Tick

The relay, K1, is controlled by power MOSFET Q1. The MOSFET is controlled by turning on the radio's power switch, which sends 13 V to the gate of Q1 through R3, a current limiter. Resistor R2 discharges the gate of Q1 when the power switch is turned off. Resistor R4 keeps the gate low, preventing Q1 from turning on from noise or stray voltage. Resistor R4 serves another purpose too. It allows about 2 mA of current to flow through the radio's power switch. This is enough to clean the contacts of the power switch.

Capacitor C1 charges via K1's coil, causing closure of the relay contacts. Once

K1 has pulled in, however, it doesn't require the same amount of current to keep the contacts closed. Resistor R1 provides just enough current to hold the contacts in after C1 charges. The result is a savings of over half the required holding current. For the Omron relay specified, the nominal coil current is 90 mA. With R1 in series, the current drops to a battery saving 40 mA. While it does not sound like a lot, of savings, over the course of several hours or days this adds up to quite a few ampere-hour savings.

DS1 lights up when the relay pulls in. (If minimum power consumption is your goal you can leave out R5 and the LED.) Diode D1 clamps the EMF produced when K1's coil drops.

Filter capacitors C2, C3 and C4 keep

