

A Compensated, Modular RF Voltmeter

Build this voltmeter—it measures voltages from 100 mV to 300 V, from 30 MHz down to audio, on chassis or in coax, accurate to ± 0.5 dB, with built-in meter or with your DVM. It's portable, simple and inexpensive.

By Sid Cooper, K2QHE

This project was started to replace a reconditioned commercial RF voltmeter that required calibration every six months. It was quite accurate when it was in calibration, but was expensive to recalibrate. The idea then was to build a stable, solid-state RF voltmeter in less than six months so that the commercial one could then calibrate the homebrew unit, but—it has long been known what happens to your best-laid plans.

The requirements for my RF voltmeter (RFVM, [Fig 1](#)) are many:

- Provide accurate, stable measurements
- Measure voltage at frequencies from audio through HF

- Measure voltage levels from QRP to QRO
- Measure voltages inside equipment or in coax
- Operate portably or from ac lines
- Be flexible: work with digital voltmeters already in the shack, or independently
- Be inexpensive

This last goal is an old fashioned idea; most equipment today is not in that category.

Design Approach

To achieve stability, the RFVM uses op amps and any drift in the probe's diode detector is compensated by a matched diode in the RF op amp. This stretches the sensitivity to QRP levels. The dynamic range extends linearly from 0.1 V to 300 V (RMS) by

using a series of compensated voltage multipliers.

The frequency response was flattened by using Schottky diodes, which easily reach from 60 Hz to 30 MHz. Both the basic probe and the multipliers very simply adapt to function as a probe, clip to various measurement points on chassis or to screw onto UHF connectors. The active devices are only two op amps. They draw 800 μ A of resting current and a maximum of 4.0 mA during operation from a 9-V battery, which is disconnected when a 9-V wall unit is plugged into a jack on the back panel. As designed, the RFVM has a small sloping panel cabinet with a microammeter display. A pair of front-panel banana **OUTPUT** jacks can be used with a DVM; this eliminates one op amp, the meter and

a multiposition switch. Since the meter and switch are the most expensive parts (when they are not bought at a hamfest), how low-cost can this RF voltmeter get?

The Probe

The low-voltage probe is a detector circuit that uses a Schottky diode and a high-impedance filter circuit (Fig 2). The diode is matched with the one in the feedback circuit of the CA3160 shown in Fig 20. This match reduces the diode's threshold voltage from about 0.34 V to less than 0.1 V, making the voltage drop comparable to that of a germanium diode. Since I think 0.1 V adequately covers QRP requirements, I made no further tests with germanium diodes to determine how much lower in voltage we could go.¹

Use the low voltage probe and the output of the CA3160 in the meter unit (Fig 20) to find a matched diode pair. Build the CA3160 circuit first for this purpose. Select a diode and place it in the feedback loop of the CA3160, then test each of the remaining diodes in the probe with the three pots set about midrange. Test each diode, first at probe inputs of 100 mV, then at 3.00 V, at 400 Hz. Record the dc output from the CA3160, using the **OUTPUT** terminals. A bag of 20 diodes from Mouser Electronics² contained seven matched pairs, with identical readings at both low and high voltages. My tests used the ac scale (good to 500 Hz) of a Heath 2372 DVM to read the input voltage, and its dc scale to read the output. The number of matched pairs is surprising, but the diodes in the bag may all be from the same production run.

¹Notes appear on page 34.



Fig 1—The RF voltmeter with meter unit, RF probe and voltage multipliers.

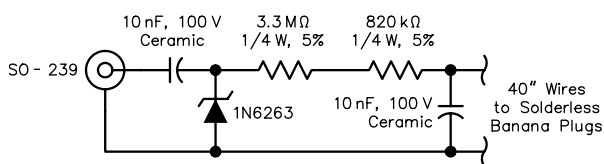


Fig 2—A schematic diagram of the RF probe.

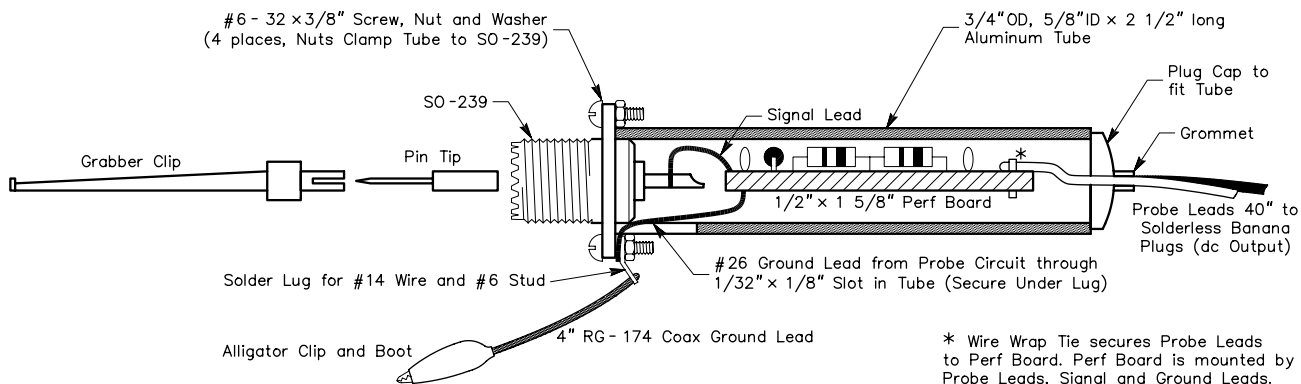


Fig 3—RF probe construction showing the grabber clip (RS 270-334), pin tip (Mouser 534-1600), lug (Mouser 571-34120, for #14-#16 wire and a #6 stud), alligator clip (RS 270-1545), plug cap (Mouser 534-7604), grommet (Mouser 5167-208) and four-inch ground lead made from shield of RG-174.

RF Probe Assembly

After selecting matched diodes, all components of the RF probe are mounted on a piece of perf board that is inserted in an aluminum tube (Fig 3). Since the circuit board is very light, it is supported on each end only by its input and output wires. The input RF wire is soldered to the center pin of the SO-239 connector. The two dc-output wires are held to the board by a small tie wrap, consisting of a piece of the #26 insulated wire, after having been passed through the plug cap and grommet. Cut a slit in the aluminum tube, perpendicular to its end. Make it at least $\frac{1}{8}$ -inch long and $\frac{1}{32}$ -inch wide to allow a bare #26 ground wire to pass through it.

Let's look at how the probe is assembled. The aluminum tube just fits around the back end of the SO-239 connector. When the four #6-32 screws, nuts and washers are installed in the four holes of the SO-239 connector, the flat face of the nut bears down strongly on the aluminum tube and rigidly holds it in place. Most standard SO-239 connector holes easily accept #6-32 screws; if yours do not, enlarge them with a #27 bit. The slit cut in the aluminum tube allows the bare ground wire from the perf board to pass from inside the tube to the outside and around the screw that secures the ground lead of the probe. As can be seen in Fig 3, the threaded part of the SO-239 connector faces away from the aluminum tube.

This probe allows easy voltage measurements in a coaxial cable when the probe SO-239 is secured to a mating T connector. To make a probe reading at any point on a chassis or PC board with this connector, simply insert the larger end of a nicely mating pin tip into the SO-239. The pin tip's diameter is 0.08 inches at the small end and—fittingly—0.14 inches at the mating end. I made this purely fortu-

itous discovery while rummaging through a very ancient junk box. Further, to make measurements with the probe clipped to a part or test point on a PC board or chassis, a clip or grabber can be mated to the pin tip that protrudes from the SO-239. This is shown in Figs 3 and 4. This was another lucky strike. All this may have been known to people in the connector industry, but it appears not to have been known or used elsewhere. Fig 5 shows the grabber connected to the RF probe using the pin tip to join the two.

Probe Measurements

The probe can accept RF signals up to 20 V (RMS) when there is no dc voltage or a combination of dc voltage and peak ac of about 28 V without exceeding the reverse-voltage rating of the diode. I made linearity measurements of the RF probe from 100 mV to 8.0 V at 400 Hz. (The range was limited by my available signal generator.) Fig 6 is a plot of the error at the probe output versus the input amplitude. This was measured using a digital voltmeter with a 10-M Ω input resistance. This input resistance and the 4.1-M Ω resistor in the probe converts the peak voltage of a sine wave signal to the RMS reading of the DVM. The error is -44% at 100 mV, then 10% (0.9 dB) at 1.0 V and finally 2.9% at 8.0 V. The RF probe and DVM are obviously intended for higher voltage readings where the diode voltage drop doesn't affect the accuracy significantly.

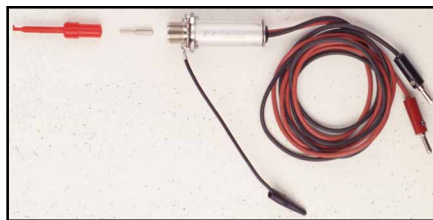


Fig 4—A photo of the grabber clip, pin tip and RF probe.

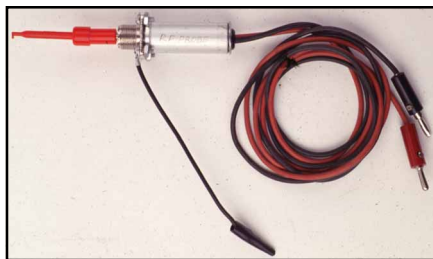


Fig 5—The RF probe with the pin tip and grabber clip in place. The pin tip is not visible, but it provides the physical bridge and electrical connection between the clip and SO-239 of the RF probe.

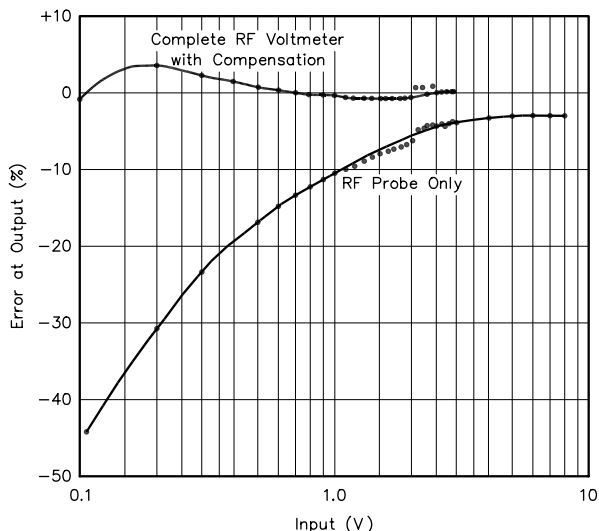


Fig 6—Amplitude linearity of the RF probe alone and in combination with the RF voltmeter.

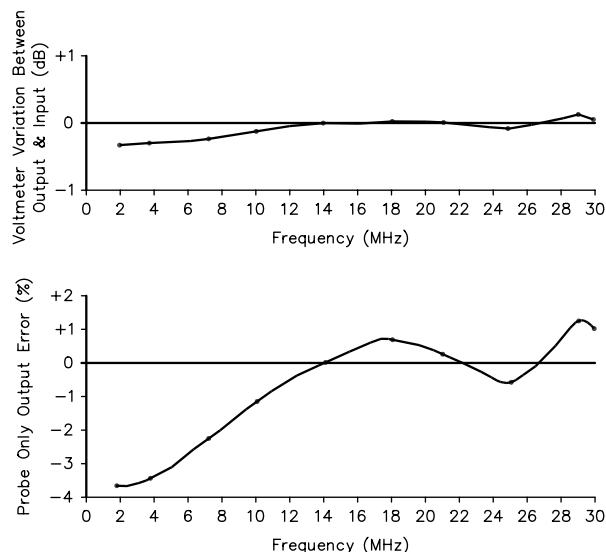


Fig 7—A frequency-response plot for the RF voltmeter. The response of the probe determines the overall system response.

The frequency response of the probe was measured at the midpoint of each ham band from 1.9 to 30 MHz with 650 mV input (see Fig 7). This time, because the input voltage was low and the absolute error would have been high, the probe was connected to the meter unit, which will be described later. The compensating diode loop of the meter unit reduces the error that would otherwise be read by the DVM from 90 mV (14%) to 4 mV (0.6%). The frequency response, however, is controlled by the probe. Use of the meter unit—which operates entirely on the dc signal—does not affect the frequency response, but it does improve the sensitivity of the readings. The measured response shown goes from -3.6% (-0.32 dB) to +1.2% (+0.1 dB).

Multipliers

To extend the voltage range of the RF probe, use a 10× multiplier, which is a compensated divider, shown in Fig 8. The electrical design is straightforward and includes a small trimmer capacitor to adjust for a flat frequency response. These components are very lightweight, so they require no perf board and are easily supported by their leads, which are anchored at the two SO-239 connectors. To make measurements, the input connector can be mated to connectors in a coaxial cable, a pin tip can be inserted for probing PC boards or a grabber can be added for connections to components on a chassis. The multiplier can connect to the RF probe either through a male-to-male UHF fitting or by a piece of coax with a UHF male connector at each end.

The typical way to adjust the trimmer requires a square-wave input and



Fig 10—A view showing the 10× multiplier with grabber, pin tip and a male UHF coupler that connects the multiplier to the RF probe.

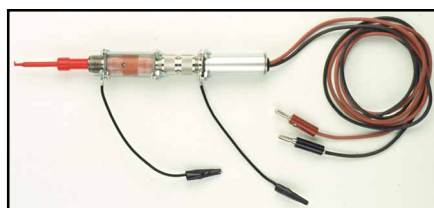


Fig 11—The complete RF probe and 10× multiplier assembly.

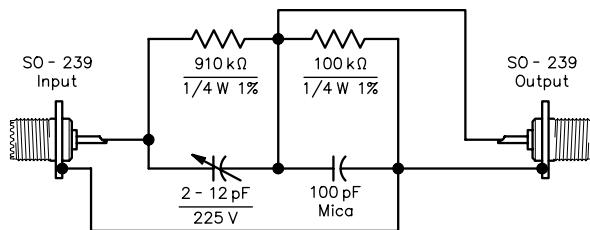


Fig 8—A schematic of the 10× multiplier. The trimmer capacitor is from Ocean State Electronics (see Note 10).

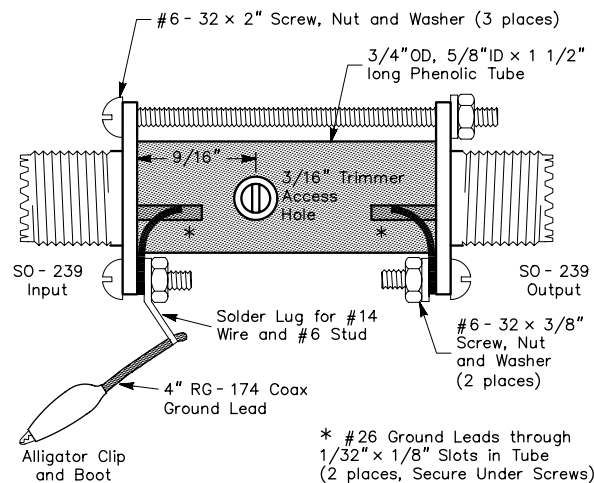


Fig 9—Construction of the 10× multiplier. The phenolic tube is US Plastics #47081, see Note 3. The lug is Mouser 571-34120.

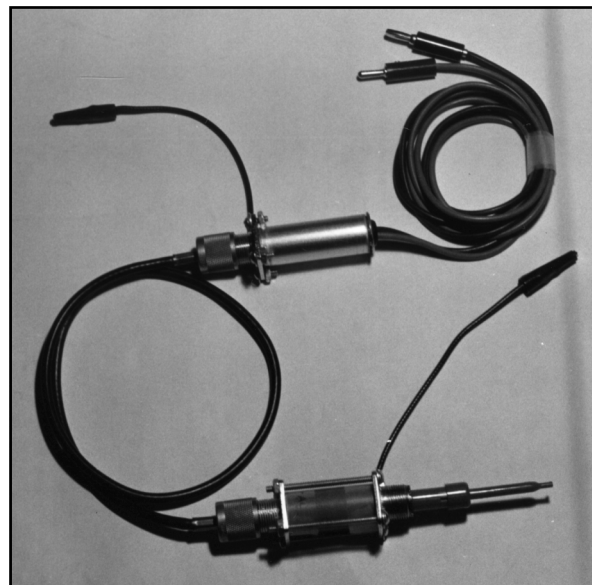


Fig 12—The RF probe and multiplier can be separated by a piece of coax less than 12 inches long if it makes measurements more convenient.

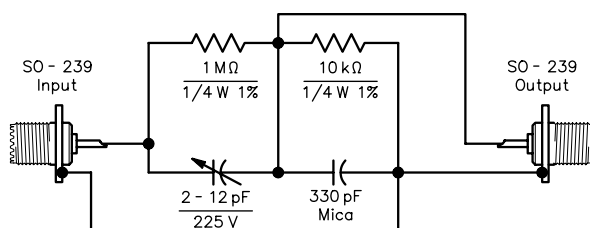


Fig 13—Schematic of the 100× multiplier (maximum allowable input is 150 V RMS). The trimmer capacitor is from Ocean State Electronics (see Note 10).

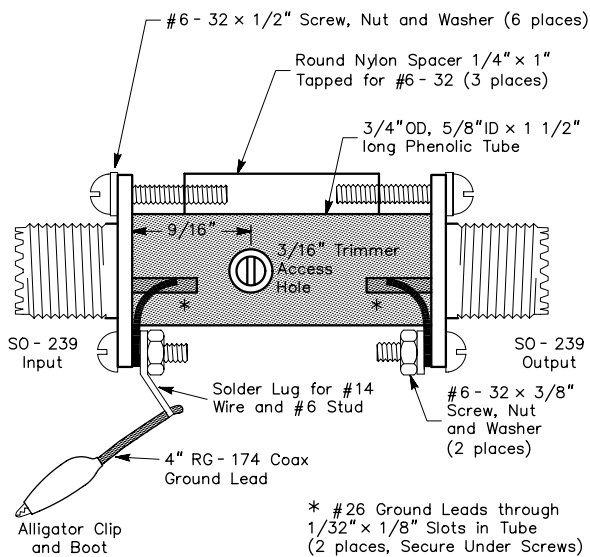


Fig 14—100x multiplier assembly showing the round Nylon spacer (Mouser 561-TSP10), phenolic tube (US Plastics #47081, see Note 3). The lug is Mouser 571-34120.

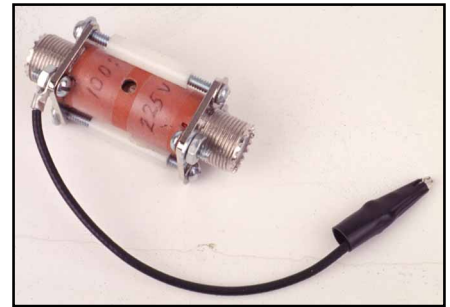


Fig 15—The assembled 100x multiplier.

that in the RF probe with #6-32 screws to hold it all together, but the frequency response began to drop off at 21 MHz. By replacing the aluminum tube with a phenolic tube³ having the same dimensions, the response is adequate to 30 MHz.

Fig 9 shows construction methods. Two slits at the ends of the tube allow the ground wires at the input and output ends to exit and wrap around the screws of each connector. A hole in the phenolic tube allows adjustment of the trimmer capacitor.

Fig 10 shows the exploded view of the pin tip and grabbers at the input end of the multiplier and a UHF male-to-male connector on the output side to mate with the RF probe. The assembled multiplier and probe are shown in Fig 11. The whole assembly is only 3 1/2 inches long and is comfortable in the hand. If more flexibility is desired, the two pieces may be separated by as much as one foot of coax (Fig 12) without doing too much damage to the accuracy of the measurement.

The 100x multiplier follows the same design concepts as the 10x multiplier including the obligatory trimmer capacitor, as in Fig 13. Here too, the 225 V dc rating of the trimmer limits the maximum RF to 150 V RMS. So, this is not useful should it be used only with the probe and your DVM because the 10x multiplier already covers this range. Later, we will see how it is useful with the RF probe and the meter unit.

The 100x unit also uses a phenolic-tube housing with a hole to adjust the trimmer and a slit at each end to bring out the ground wires, which then wrap around screws in the connectors. In order to reach at least 30 MHz, however, the two-inch steel screws between the two SO-239 connectors must be insulated. Using plastic washers at the connector holes could do this job but would have required #4-40x2-inch-long screws. After a long search at the biggest hardware stores and catalogs,

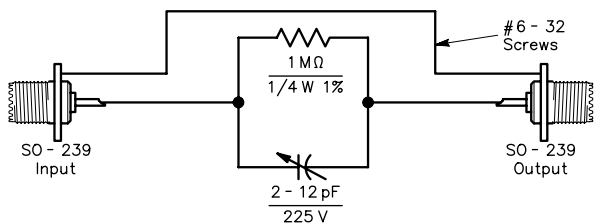


Fig 16—A schematic diagram of the 2x multiplier. Its output connects to the input of the 100x multiplier for 200x measurements up to 300 V RMS. This multiplier is used only with the 100x multiplier.

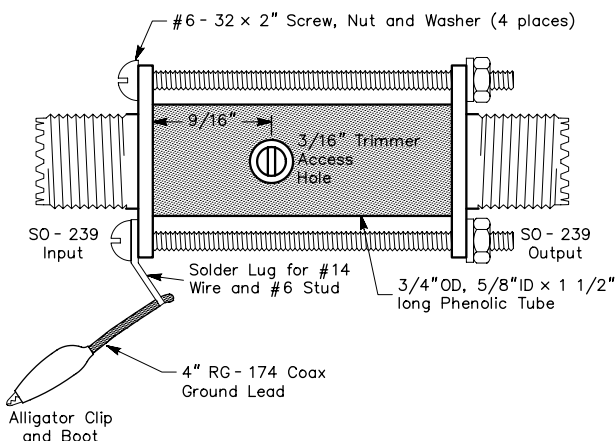


Fig 17—2x multiplier assembly showing the phenolic tube (US Plastics #47081, see Note 3). The lug is 16-14 #6 stud (Mouser 571-34120).

an oscilloscope on the output. The trimmer is then set to produce a flat square-wave output with no overshoots on the leading edges and no droop across the top. An RF signal generator that covers 1.9 MHz to 30 MHz can be used instead, if a square wave generator is not available. Since this is a 10x multiplier, it is reasonable to expect the input to handle up to 200 V

(RMS), but the limit is 150 V because the trimmer capacitor is rated at 225 V dc. You may be able to find small trimmers with higher voltage ratings that will take the multiplier to 200 V and still fit inside the tube housing.

Multiplier construction follows the same methods used for the RF probe but with a few differences. My first model used an aluminum tube like

I found nothing longer than 1½ inches. That's the best way to assemble this multiplier, if you can find the screws. Otherwise, use nylon spacers and shorter screws as shown in Figs 14 and 15. The pin tip and grabber at the input and UHF male-to-male connector or coaxial cable at the output are used as with the 10× multiplier.

The only purpose of the 2× multiplier is to create a 200× multiplier when used with the 100× multiplier in series, so as to extend the voltage range from 150 V to 300 V (1800 W at 50 Ω only under matched conditions⁴). The trimmer in each multiplier now divides in half the input voltage. Fig 16 shows the 2× multiplier with only one RC section since it relies on the RC sections in the 100× multiplier to complete the division (multiplication).

The construction, Fig 17, returns to the tubular format as before, but this time there are no slots to pass the ground wires; the four screws are able to do the job. The two multipliers are shown in series in Fig 18.

The input capacitance for each multiplier is shown in Table 1.

When measurements are made on a load resistance of 50 Ω, the input capacitance of the multipliers has no effect on readings below 30 MHz. When the impedance of the load resistance is larger, consider any error it introduces. To get a sense of the effects of the load resistance, use the equation below. It shows the relationship between the resistance, capacitance and frequency when the measured voltage is 3 dB down from what it would be if it were read by a meter with no input capacity:

$$f = \frac{1}{2\pi R_L C_p} \quad (\text{Eq 1})$$

where

R_L = load resistance

C_p = probe capacitance

For example, at a load of 1 kΩ and a probe capacity of 13.3 pF, the 3 dB down frequency is about 12 MHz, where the error is 30%. If an attenuator were used instead of the multiplier, it would not have this problem because it works with either a fixed 50-Ω load at high frequencies or a 600-Ω at low frequencies. Probes cannot select their frequency or load impedance and are thereby more flexible in use, so measurements must

be made with consideration, but these multipliers would not have a problem at 50 Ω or 600 Ω either.

Table 2 summarizes the voltage ranges using only the multiplier with the RF probe and a DVM that has a 10-MΩ input resistance that's available in the shack.

The multipliers are intended for use at high voltages where safety precautions are a primary consideration to avoid personal injury. *The ARRL Handbook* has an entire chapter devoted to safety, for good reason. In Tektronix' *ABC's of Probes*,⁵ an entire section thoroughly covers the hazards and necessary precautions when making measurements with probes. It is worth the little effort to get a copy of it and also the Pomona Catalog,⁶ which has some good information on probe use.

The multipliers have panel connectors at both ends and the RF probe has one at one end. Their grounds are connected and brought to the meter unit. This unit is grounded only when the ac-powered 9-V power supply that may be used with it, is grounded. When it is battery operated, the meter unit relies on the ground-clip connection to the ground of the equipment under test. This is satisfactory if there is no unknown break in the chain of ground connections that would make the panel connector hot. Furthermore, as insurance, it is well to wrap these connectors with vinyl tape or to cover the multiplier with a plastic boot to prevent contact with either hands or equipment under test. This is not shown in any photographs because it would have

obscured the appearance and construction of the probe and multipliers.

The frequency responses of the multipliers were determined using an RF signal generator set at the midpoint of each ham band from 160 to 10 meters, including 30 MHz. An error of 5.42% (0.46 dB) was measured from 160 to 17 meters, which then decreased to 4.13% (0.35 dB) at 15 meters and then to zero through 30 MHz. The constant error from 160 to 17 meters is probably due to the inherent errors in the test equipment. The oscilloscope has a 60 MHz bandwidth, an input impedance of 1 MΩ and 30 pF, which introduces a load effect on the multiplier outputs. It also has a reading accuracy of ±3%. When the multiplier-components accuracy of 1% is included, it is not surprising to find the overall inaccuracy to be at most 5.42%.⁷ The error of the multiplier itself could be inherently less than this. Before the overall frequency response was measured, the trimmer capacitor was adjusted with the input frequency set mid-frequency at 15 MHz. If your interest in RF probes and multipliers has been raised and you have more questions, see the references in Notes 5 and 6.

The Meter Unit

The meter unit serves several purposes when used with the RF probe. It increases the accuracy of the probe and DVM from -45% to -3.5% at a voltage of 100 mV RF. At higher voltages, it maintains a minimum advantage of 5:1 in reducing the error, when the probe is used with a DVM. This is an increase in both sensitivity and accuracy. The usual non-linearity caused by the diode in the probe is reduced when used with the meter unit. The technique also incidentally provides temperature compensation for diode drift. The meter unit has a ±5% panel meter to display measurements, but it also contains a pair of OUTPUT terminals for a DVM. Add a DVM when more accuracy is desired

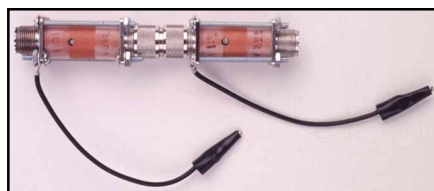


Fig 18—The 2× and 100× multipliers are joined by a male UHF coupler for readings up to 300 V (RMS, 1800 W, see Note 4).

Table 2—Multiplier versus Voltage Range

Probe Configuration	Range (V)	Maximum Voltage
Probe Alone*	1.0-20 V ac	20 V ac
With 10× Multiplier*	10-150 V ac	225 V (ac + dc)
With 100× and 2× Multiplier†	150-200 V ac	450 V (ac + dc)
With 100× and 2× Multiplier††	200-300 V ac	450 V (ac + dc)

*error less than -10% or -0.83 dB

†with error of -45% to -10% or less than 3.2 dB. A trimmer capacitor with a rating of 300 V dc increases the 10× range to 200 V ac and reduces the error from 45% to 10%. The RF probe and meter unit reduces the error to less than -3.5% or less than -0.3 dB.

††with error less than -6% or -0.54 dB

Table 1—Multiplier Range versus Capacitance


Multiplier	10×	100×	200×
Input Cap (pF)	13.3	10.9	13.5

at the low end of the range or when you want a bit more resolution. Finally, since the meter unit is fully portable, low-level field-strength measurements are possible with a whip antenna at the probe input connector. Due to its sensitivity and accuracy, the probe can be adapted for use in many places around the shack.

The non-linear response of the probe diode is compensated (improved) by a circuit in the meter unit. The feedback loop of a CA3160 op amp contains a diode matched to the one in the probe (see [Note 1](#)). Fig 19 and its sequence of equations present a very simple sketch of how matched diodes do this when dc is applied through a diode. The final equation shows that any difference between the op amp input and output is due to a difference in voltage drops across the two diodes. When the diodes are matched, the error disappears. When RF is applied, the average currents through the diodes must be equal to keep the voltage drops

equal. Articles by Kuzdrall ([Note 1](#)) Grebenkemper⁸ and Lewallen⁹ are first-class descriptions of the principles used in this RF voltmeter.

Fig 20 shows three pots for calibrating the meter unit. This should be performed at 400 Hz to avoid any effects due to RF. The 100-kΩ pot is typi-

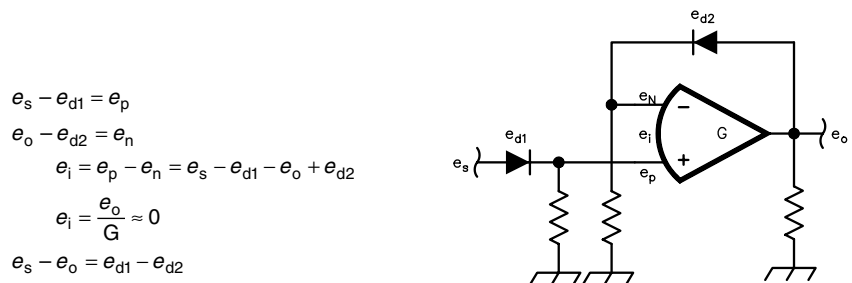

e_s represents the input of the RF probe as a dc signal.

e_o represents the output from the high-gain CA3160 op amp.


e_{d1} is the voltage drop across the diode in the RF probe.

e_{d2} the voltage drop across the diode in the feedback loop.

$G = 320,000$ for the CA3160

The last equation shows that any difference between the signal and output results from unequal diode drops when the diodes are not matched.

Fig 19—Basics of the diode-compensation method to improve measurement accuracy at low input voltages. It also provides a measure of temperature compensation and drift reduction. See [Fig 6](#).

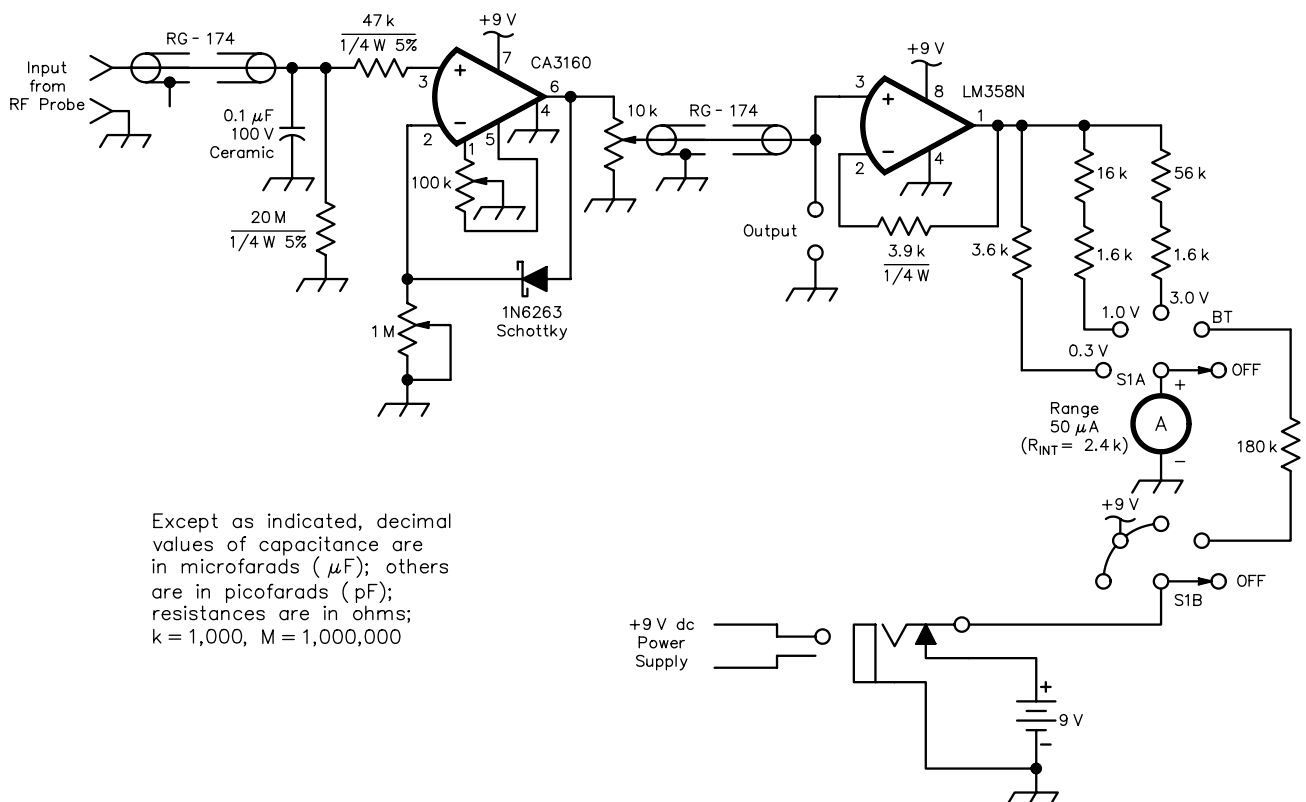

Except as indicated, decimal values of capacitance are in microfarads (μF); others are in picofarads (pF); resistances are in ohms; $k = 1,000$, $M = 1,000,000$

Fig 20—Schematic of the RF voltmeter. The DVM adds resolution to the panel-meter reading. When the panel meter reads full scale with S1 in the B+ position, the battery is at 9V.

S1—2P5T non-shorting rotary switch, one-inch diameter.

A one-lug tie strip is mounted on the negative-terminal screw of the meter to provide a mounting point for the meter resistors.

The following resistors are all carbon-composition or metal-film components ($1/4\text{W}$, $\pm 1\%$): 1.6 k, 3.6 k, 16 k, 56 k.

The three pots are cermet 12-turn components adjustable from the top. The input connector for the RF probe and the output connector for the optional DVM

are double banana connectors.

The resistors, capacitors, ICs diodes and pots are mounted on RadioShack multipurpose PC board #276-150. The meter, two banana plugs and switch are mounted on the front of the case, the phone jack on the back.


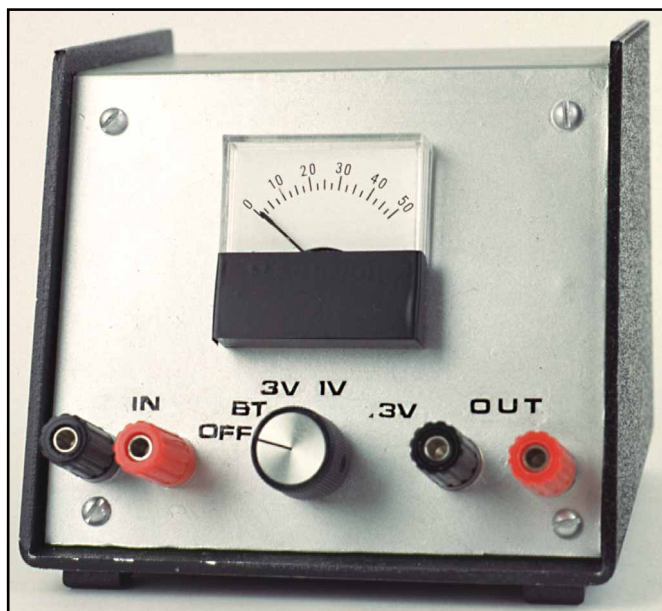


Fig 21(above)—The assembled meter unit.

Fig 22(right)—Inside view of the meter unit. RG-174 connects the INPUT and OUTPUT banana binding posts to the circuit board. The rotary switch, one-lug tie strip and battery are also visible.

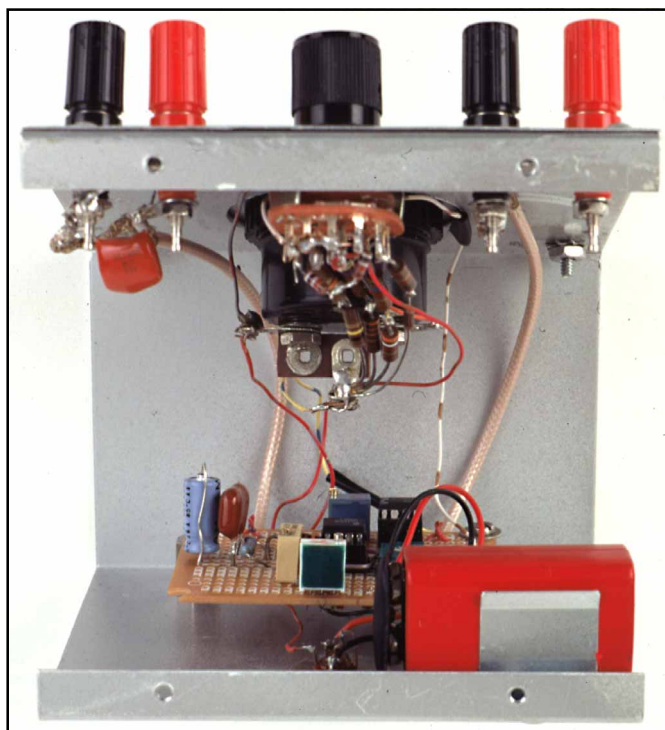

cally used to null the offset of the CA3160, but is used here to initially set the offset to about 0.5 mV to 1.0 mV with no input. Then the 1-M Ω pot sets the output to 100 mV with no input, and the 10 k Ω pot sets the output to 3.0 V when the input is 3.0 V. Finally, the three pots are alternately adjusted until the 100 mV and 3.0 V set points occur together. The 100-k Ω pot is helpful in fine tuning the 100-mV point. A DVM was used at the optional OUTPUT sockets during calibration.

A CA3160 was selected for the input op amp because of its high input impedance of 1.5 T Ω and high gain of 320,000. Although it has diodes that provide protection, I think it could be sensitive to electrostatic discharge, so handle it carefully. Use IC sockets to permit easy replacement of the ICs in case of damage. An LM358N IC follows the CA3160 (see Fig 20), primarily to drive the panel meter. If you use a DVM as the display, you can omit the LM358N circuit, meter and multi-position switch. The only functions lost are the battery-voltage check and power on/off switch. Add a on/off switch to the circuit when the multi-position switch is omitted. The CA3160 op amp circuit easily spans the range from 100 mV to 3.0 V without the need for a range switch.

Construction

A 5 \times 5 \times 4 $\frac{1}{2}$ -inch sloping-front instru-



Fig 23—The meter unit with RF probes and a DVM connected to the OUTPUT jacks.

ment case was used to house the components of the meter unit (see Fig 21). The meter on the front panel has a 2 \times 2-inch face and requires a 1 $\frac{1}{2}$ -inch hole in the panel. Although a 50- μ A meter from the junk box is used here, a 1-mA movement will work as well, provided the series resistors are changed accordingly.

The rotary switch has two poles and five positions for changing the meter range, testing the battery condition and switching the power off. Two sets of double banana binding posts are used, the INPUT pair accepts the dc signal from the RF probe. The OUTPUT pair provides a voltage for a DVM dis-

play, whether the panel meter is used or not. On the rear of the case, a miniature phone jack accepts 9-V power from either a battery or a 9-V dc supply. The ICs and other parts are mounted on a RadioShack multipurpose PC board that has very convenient holes and traces. The board is bolted to the back of the case via stand-off insulators and wired to the front panel components (see Fig 22). The assembly of the meter unit, RF probe and DVM are shown in Fig 23.

Acknowledgement

The original goal of the design was a linear scale with an accuracy of 5%,

from 100 mV to 3 V (RMS) for frequencies from audio through HF. When I discussed it with *QEX* Managing Editor Robert Schetgen, KU7G, he thought the utility of the meter could be much improved if the voltage range were increased. That set off a chain reaction of improvements, beginning with the compensated multipliers for the RF probe input. The early probe design had a pin at its input, however, which does not easily connect to a divider with an SO-239 connector at its output. Part of the answer is a SO-239 panel connector at the probe input for measurements in coaxial terminations. This was a new voltmeter application, but it seemed to defeat the meter's original purpose: troubleshooting on a chassis.

Rummaging through an ancient parts box provided the link: a probe pin tip with a shank that fits perfectly into the female center pin of the SO-239 connectors on the probe and multipliers. This pin tip is still available in catalogs, surprisingly, but as a standard pin tip it also fits into available alligator clips. This single pin is used for probing

or for adding alligator clips or probe adapters to either the RF probe or multipliers. The tip can be removed anytime and the SO-239 used for cable measurements. Bob's outstanding suggestion was taken seriously. The result is an inexpensive, wide-range, RF voltmeter that should not require calibration every six months.

Notes

- ¹J. A. Kuzdrall, "Linearized RF Detector Spans 50-to-1 Range," Analog Applications Issue *Electronic Design*, June 27, 1994.
- ²Mouser Electronics, 2401 Hwy 287 N, Mansfield, TX 76063; tel 800-346-6873, fax 817-483-0931; E-mail sales@mouser.com; www.mouser.com.
- ³United States Plastics Corp., 1390 Neubrecht Road, Lima, OH 45801-3196, tel 419-228-2242, fax 419-228-5034.
- ⁴If the power remains constant, load mismatch multiplies the voltage by the SWR. A 2:1 SWR would produce 600 V, 3:1 900 V and so on.—Ed
- ⁵*ABCs of Probes*, Tektronix Inc., Literature number 60W-6053-7, July 1998. Tektronix, Inc. Export Sales, PO Box 500 M/S 50-255 Beaverton, OR 97707-0001; 503-627-6877. Johnny Parham, "How to Select the Proper Probe," *Electronic Products*, July 1997.

⁶Pomona Test and Measurement Accessories catalog. ITT Pomona Electronics, 1500 E Ninth St, Pomona, CA 91766-3835.

⁷A. Frost, "Are You Measuring Your Circuit or Your Scope Probe?" *EDN*, July 22, 1999. E. Feign, "High-Frequency Probes Drive 50-Ω Measurements," *RF Design*, Oct 1998.

⁸J. Grebenkemper, KI6WX, "The Tandem Match—An Accurate Directional Wattmeter," *QST*, Jan 1987, pp 18-26; and "Tandem Match Corrections," *QST*, Jan 1988, p. 49.

⁹R. Lewallen, W7EL, "A Simplified and Accurate QRP Directional Wattmeter," *QST*, Feb 1990, pp 19-23, 36.

¹⁰Ocean State Electronics, 6 Industrial Dr, PO Box 1458, Westerly, RI 02891; tel 800-866-6626, fax 401-596-3590.

Sid Cooper, K2QHE, received his license 45 years ago, although he claims he was genetically programmed by his brother, Bert, WA0BHE (SK), for electronics long before that. He worked on radar and computer design programs as an electronics engineer and manager, then retired from RCA after 20 years. He is fairly active at the IRAC ham club in Roseland, New Jersey, and is a fairly regular participant on the Northeast Corridor Net on Monday nights. □□

EZNEC 3.0

All New Windows Antenna Software by W7EL

EZNEC 3.0 is an all-new antenna analysis program for Windows 95/98/NT/2000. It incorporates all the features that have made *EZNEC* the standard program for antenna modeling, plus the power and convenience of a full Windows interface.

EZNEC 3.0 can analyze most types of antennas in a realistic operating environment. You describe the antenna to the program, and with the click of a mouse, *EZNEC 3.0* shows you the antenna pattern, front/back ratio, input impedance, SWR, and much more. Use *EZNEC 3.0* to analyze antenna interactions as well as any changes you want to try. *EZNEC 3.0* also includes near field analysis for FCC RF exposure analysis.

See for yourself

The *EZNEC 3.0* demo is the complete program, with on-line manual and all features, just limited in antenna complexity. It's free, and there's no time limit. Download it from the web site below.

Prices - Web site download only: \$89. CD-ROM \$99 (+ \$3 outside U.S./Canada). VISA, MasterCard, and American Express accepted.

Roy Lewallen, W7EL phone 503-646-2885
P.O. Box 6658 fax 503-671-9046
Beaverton, OR 97007 email w7el@eznec.com

<http://eznec.com>

800-522-2253

This Number
May Not Save
Your Life...

But it could make it a lot easier!
Especially when it comes to
ordering non-standard connectors.

RF/MICROWAVE CONNECTORS

- Specials our specialty virtually any SMA, N, TNC, BNC, SMB, or SMC delivered in 2-4 weeks
- Cross reference library to all major manufacturers.
- Large inventory of piece parts for all types of coaxial connectors.
- Experts in supplying "hard to get" RF connectors.
- Connectors supplied to your drawings and specs.
- Our 56 Standard adapters can satisfy virtually any combination of requirements, between SMA, TNC, N, 7mm, BNC and others.
- Extensive inventory of passive RF/Microwave components including attenuators, terminations and dividers.

NEMAL

Cable & Connectors
for the Electronics Industry

NEMAL ELECTRONICS INTERNATIONAL, INC.

12240 N.E. 14TH AVENUE
NORTH MIAMI, FL 33161
TEL: 305-899-0900 • FAX: 305-895-8178
E-MAIL: INFO@NEMAL.COM
URL: WWW.NEMAL.COM



The impressive **IC-756 Pro** covers HF plus 6 meters. The high resolution 5 inch TFT color display provides more operating information than ever, including a spectrum scope. The 32 bit floating point DSP provides crisp, clear reception with 41 built-in filters. The "Pro" is the choice for serious DXers and contesters.



The **IC-746** covers 160-10 meters plus 6 and 2 meters with 100 watts on all bands. Call or visit our website for further details and pricing on this and other ICOM radios.

Universal Radio
6830 Americana Pkwy.
Reynoldsburg, OH 43068
♦ Orders: 800 431-3939
♦ Info: 614 866-4267
www.universal-radio.com