

THE MICRO M+

The Micro M+ is an ideal photovoltaic (PV) controller for use at home or in the field. It's an easy-to-build, one-evening project even a beginner can master. This project was designed by Mike Bryce, WB8VGE. An earlier charge controller called the "Micro M" proved to be a very popular project.¹

Hams really do like to operate their rigs from solar power. Many have found solar power to be very addictive. I had dozens of requests for information on how to increase the current capacity of the original "Micro M" controller. The Micro M would handle up to 2 A of current. I wanted to improve the performance of the Micro M while I was at it. Because the Micro M switched the negative lead of the solar panel on and off, that lead had to be insulated from the system ground. While that's not a problem with portable use, it may cause trouble with a home station where all the grounds should be connected. Here's what I wanted to do:

- Reduce the standby current at night
- Increase current handling capacity to 4 A
- Change the charging scheme to high (positive) side switching
- Improve the charging algorithm
- Keep the size as small as possible, but large enough to easily construct.

I called the end result the Micro M+. You can assemble one in about an hour. Everything mounts on one double-sided PC board. It's small enough to mount inside your rig yet large enough so you won't misplace it! You can stuff four of them in your shirt pocket! And, you need not worry about RFI being generated by the Micro M+. It's completely silent and

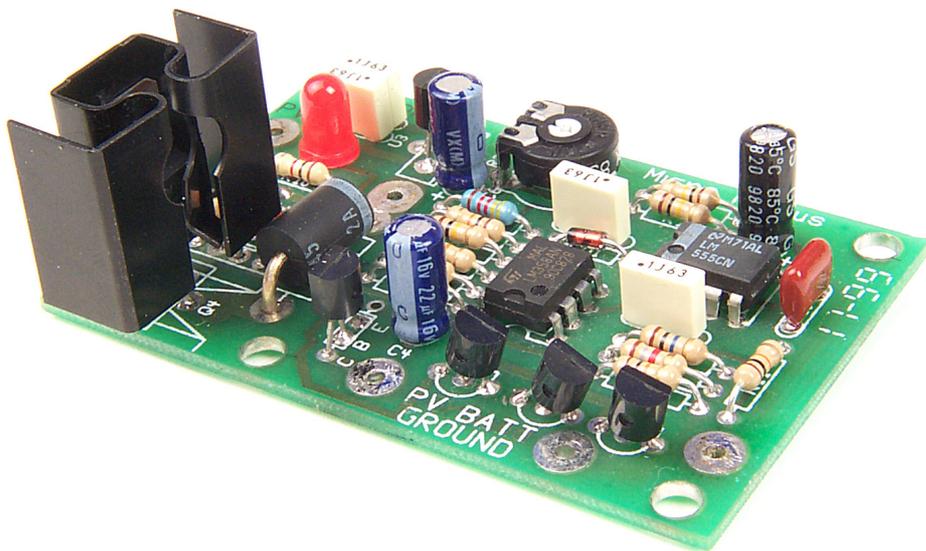


Fig 17.50 — This photo shows the Micro M+ charge controller circuit board. Leads solder to the board and connect to a solar panel and to the battery being charged.

makes absolutely no RFI!

The Micro M+ will handle up to 4 A of current from a solar panel. That's equal to a 75-W solar panel.² I've reduced the standby current to less than one milliamp. I've also introduced a new charging algorithm to the Micro M+. All the current switching is done on the positive side. Now, you can connect the photovoltaic array, battery and load grounds together.

A complete kit of parts is available as well as just the PC board.³ The Micro M+ is easy to build, making it a perfect first time project.

HOW IT WORKS

Fig 17.50 shows the complete Micro

M+. **Fig 17.51** shows the schematic diagram. Let's begin with the current handling part of the Micro M+. Current from the solar panel is controlled by a power MOSFET. Instead of using a common N-channel MOSFET, however, the Micro M+ uses an STMicroelectronics STP80PF55 P-channel MOSFET. This P-channel FET has a current rating of 80 A with an $R_{DS(on)}$ of 0.016 Ω . It comes in a TO-220 case. Current from the solar panel is routed directly to the MOSFET source lead.

N-channel power MOSFETs have very low $R_{DS(on)}$ and even lower prices. To switch current on and off in a high-side application, though, the gate of an N-channel MOSFET must be at least 10 V higher

considered very low. At that time an N channel MOSFET had an RDS_{on} of 0.009 Ω . Suppose you want to control 10 A of current from your solar panel. Using the N-channel MOSFET above we find the MOSFET will dissipate less than a watt of power. On the other hand, the P-channel MOSFET will dissipate 12 W of power! Current generated by our solar panels is way too precious (and expensive) to have 12 W go up as heat from the charge controller.

The second factor was price. The P-channel MOSFET I described above would have easily sold for \$19 each. The N-channel device would have been a few dollars.

More recently, the RDS_{on} of a typical P-channel MOSFET has fallen to 0.028 Ω . The price, while still a bit expensive, has dropped to about \$8 each.

With the P channel MOSFET controlling the current, diode D4 — an SB520 Schottky — prevents battery current from flowing into the solar panel at night. This diode also provides reverse polarity protection to the battery in the event you connect the solar panel backwards. This protects the expensive P channel MOSFET.

Zener diode D2, a 1N4747, protects the gate from damage due to spikes on the solar panel line. Resistor R12 pulls the gate up, ensuring the power MOSFET is off when it is supposed to be.

THE MICRO M+ LIKES TO SLEEP

The Micro M+ never draws current from the battery. The solar panel provides all the power the Micro M+ needs, which means the Micro M+ goes to sleep at night. When the sun rises, the Micro M+ will start up again. As soon as the solar panel is producing enough current and voltage to start charging the battery, the Micro M+ will pass current into the battery.

To reduce the amount of stand-by current, diode D3 passes current from the solar panel to U3, the voltage regulator. U3, an LM78L08 regulator, provides a steady +8 V to the Micro M+ controller. Bypass capacitors, C6, C7 and C8 are used to keep everything happy. As long as there is power being produced by the solar panel, the Micro M+ will be awake. At sun down, the Micro M+ will go to sleep. Sleep current is on the order of less than 1 mA!

BATTERY SENSING

The battery terminal voltage is divided down to a more usable level by resistors, R1, R2 and R3. Resistor R3, a 10 k Ω trimmer, sets the state-of-charge for the Micro M+. A filter consisting of R5 and C1 helps keep the input clean from noise picked up by the wires to and from the solar panel.

Diode D1 protects the op-amp input in case the battery sense line was connected backwards.

An LM358 dual op-amp is used in the Micro M+. One section (U1B) buffers the divided battery voltage before passing it along to the voltage comparator, U1A. Here the battery sense voltage is compared to the reference voltage supplied by U4. U4 is an LM336Z-5.0 precision diode. To prevent U1A from oscillating, a 10-M Ω resistor is used to eliminate any hysteresis.

As long as the voltage of the battery under charge is below the reference point, the output of U1A will be high. This saturates transistors Q1 and Q2. Q2 conducts and lights LED DS1, the CHARGING LED. Q1, also fully saturated, pulls the gate of the P channel MOSFET to ground. This effectively turns on the FET, and current flows from the solar panel into the battery via D4.

As the battery begins to take up the charge, its terminal voltage will increase. When the battery reaches the state-of-charge set point, the output of U1A goes low. With Q1 and Q2 now off, the P channel MOSFET is turned off, stopping all current into the battery. With Q2 off, the CHARGING LED goes dark.

Since we have eliminated any hysteresis in U1A, as soon as the current stops, the output of U1A pops back up high again. Why? Because the battery terminal voltage will fall back down as the charging current is removed. If left like this, the Micro M+ would sit and oscillate at the state-of-charge set point.

To prevent that from happening, the output of U1A is monitored by U2, an LM555 timer chip. As soon as the output of U1A goes low, this low trips U2. The output of U2 goes high, fully saturating transistor Q3. With Q3 turned on, it pulls the base of Q1 and Q2 low. Since both Q1 and Q2 are now deprived of base current, they remain off.

With the values shown for R15 and C2, charging current is stopped for about four seconds after the state-of-charge has been reached.

After the four second delay, Q1 and Q2 are allowed to have base drive from U1A. This lights up the charging LED and allows Q4 to pass current once more to the battery.

As soon as the battery hits the state-of-charge once more, the process is repeated. As the battery becomes fully charged, the “on” time will shorten up while the “off” time will always remain the same four seconds. In effect, a pulse of current will be sent to the battery that will shorten over time. I call this charging algorithm “Pulse Time Modulation.”

As a side benefit of the pulse time modulation, the Micro M+ won't go nuts if you put a large solar panel onto a small battery. The charging algorithm will always keep the off time at four seconds allowing the battery time to rest before being hit by higher current than normal for its capacity.

BUILDING YOUR OWN MICRO M+

There's nothing special about the circuit. The use of a PC board makes the assembly of the Micro M+ quick and easy. It also makes it much easier if you need to troubleshoot the circuit. The entire circuit can be built on a piece of perf board.

The power MOSFET must be protected against static discharges. A dash of common sense and standard MOSFET handling procedures will work best. Don't handle the MOSFET until you need to install it in the circuit. A wrist strap is a good idea to prevent static damage. Once installed in the PC board, the device is quite robust.

A small clip-on heat sink is used for the power MOSFET. If you desire, the MOSFET could be mounted to a metal chassis. If you do this, make sure you electrically insulate the MOSFET tab from the chassis.

If you plan to use the Micro M+ outside, then consider soldering the IC directly onto the board. I've found that cheap solder-plated IC sockets corrode. If you want to use an IC socket, use one with gold plated contacts.

Feel free to substitute part values. There's nothing really critical. I do suggest you stick with 1% resistors for both R1 and R2. This isn't so important for their closer tolerance but for the 50-PPM temperature compensation they have. You can use standard off-the-shelf parts for either or both R1 and R2, but the entire circuit should then be located in an environment with a stable temperature.

ADJUSTMENTS

You'll need a good digital voltmeter and a variable power supply. Set the power supply to 14.3 V. Connect the Micro M+ battery negative lead to the power supply negative lead. Connect the Micro M+ PV positive and battery positive leads to the power supply positive lead. The charging LED should be on. If not, adjust trimmer R3 until it comes on. Check for +8 V at the VCC pins of the LM358 and the LM555. You should also see +5 V from the LM336Z5.0 diode.

Quickly move the trimmer from one end of its travel to the other. At one point the LED will go dark. This is the switch point. To verify that the “off pulse” is working, as soon as the LED goes dark quickly

reverse the direction of the trimmer. The LED should remain off for several seconds and then come back on. If everything seems to be working, it's time to set the state-of-charge trimmer.

Now, slowly adjust the trimmer until the LED goes dark. You might want to try this adjustment more than once as the closer you get the comparator to switch at exactly 14.3 V, the more accurate the Micro M+ will be. Here's a hint I've learned after adjusting hundreds of Micro M+ controllers. Set the power supply to slightly above the cut-off voltage that you want. If you want 14.3 V, then set the supply to 14.5 V. I've found that in the time it takes to react to the LED going dark, you overshoot the cut-off point. Setting the supply higher takes this into account and usually you can get the trimmer set to exactly what you need in one try. That's all you need to do. Disconnect the supply from the Micro M+ and you're ready for the solar panel.

ODDS AND ENDS

The 14.3-V terminal voltage will be correct for just about all sealed and flooded-cell lead-acid batteries. You can change

the state-of-charge set point if you want to recharge NiCds or captive sealed lead-acid batteries.

Keep the current from the solar panel within reason for the size of the battery you're going to be using. If you have a 7-amp hour battery, then don't use a 75-W solar panel. You'll get much better results and smoother operation with a smaller panel.

The tab of the power MOSFET is electrically hot. If you plan on using the Micro M+ without a protective case, make sure you insulate the tab from the heatsink. A misplaced wire touching the heatsink could cause real damage to both the Micro M+ and your equipment. A small plastic box from RadioShack works great.

MORE CURRENT?

Well yes, you can get the Micro M+ to handle more current. You must increase the capacity of the blocking diode and mount the power MOSFET on a larger heat sink. I've used an MBR2025 diode and a large heatsink for the MOSFET and can easily control 12 A of current.

BATTERY CHARGING WITHOUT A SOLAR PANEL?

Yes, it's possible. The trick is to use a power supply for which you can limit the output current. A discharged lead-acid battery will draw all the current it can from the charging source. In a solar panel setup, if the panel produces 3 A, that's all it will do. With an ac-powered supply, the current can be excessive. To use the Micro M+ with an ac-powered supply, set the voltage to 15.5 V. Then limit the current to 2 or 3 A.

No matter if you're camping in the out-back, or storing photons just in case of an emergency, the Micro M+ will provide your battery with the fullest charge. The Micro M+ is simple to use and completely silent. Just like the sun!

Notes

¹The Micro M, September 1996 *QST*, p 41.

²A 75-W module produces 4.4 A at 17 V. The Micro M+ can easily handle the extra 400 ma.

³PC boards, partial kits and full kits are available from Sunlight Energy Systems, www.seslogic.com.