

An RF Step Attenuator

When you can find a good, commercially made RF attenuator, expect to pay the price. Here's where doing it yourself can provide you with what you need—inexpensively.

By Denton Bramwell, K7OWJ
3139 Royalton Hts Rd
St Joseph, MI 49085

If you're doing any serious receiver home brewing, a good RF step attenuator is one of the key pieces of equipment that belongs on your workbench. Good attenuators are hard to find at prices that won't injure your wallet. If you're lucky, you may find a used HP-355 series unit at a flea market, but it won't be cheap! Hams who have them—and know their value—don't surrender them easily!

Hams are accustomed to substituting ingenuity for money. That was my approach. The result: a home brew step attenuator that provides good performance, yet can be built with a few basic tools.¹ This unit is designed for use in 50- Ω line, provides a total attenuation of 71 dB in 1-dB steps, offers respectable accuracy and insertion loss through 225 MHz and can be used at 450 MHz (see Table 1).

Description

Refer to Figure 1. The attenuator consists simply of 10 resistive π attenuator sections such as the one shown here. Each section consists of a DPDT slide switch and three $\frac{1}{4}$ -W, 1%-tolerance metal-film resistors whose values are chosen to obtain the desired amount of attenuation. The completed unit contains single 1, 2, 3 and 5-dB sections, and six 10-dB sections. Table 2 lists the resistor values required for each section.

The enclosure is made of brass sheet stock, readily available at many hardware stores. By selecting the right stock, you can avoid having to bend the metal and perform a minimal amount of cutting.

Construction

I built the enclosure using only a nibbling tool, a drill press, metal shears and a butane-heated soldering iron. To cut the rectangular tubing to length, I used my drill press equipped with a small abrasive cutoff wheel. It's not an elegant solution, but it's inexpensive and works well enough.

Brass is easy to work and solder. For the enclosure, you'll need two precut $2 \times 12 \times 0.025$ -inch sheets and two $1 \times 12 \times$

¹Notes appear on page 34.

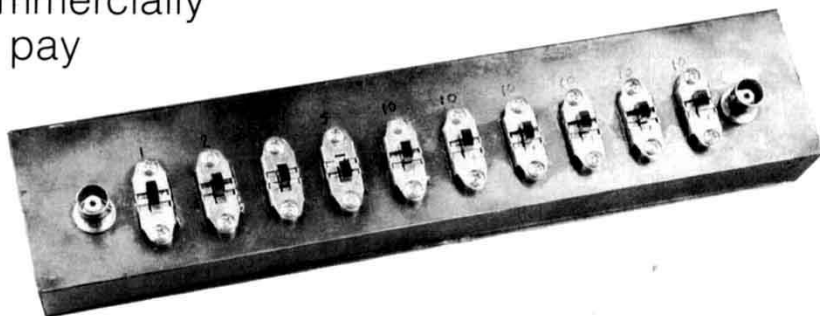


Table 1
Step Attenuator Performance at 148, 225 and 450 MHz
Measurements made in the ARRL Laboratory

Attenuator set for maximum attenuation (71 dB)		Attenuator set for minimum attenuation (0 dB)	
Frequency (MHz)	Attenuation (dB)	Frequency (MHz)	Attenuation (dB)
148	72.33	148	0.4
225	73.17	225	0.4
450	75.83	450	0.84

Note: Laboratory-specified measurement tolerance of ± 1 dB.

0.025-inch sheets. The 2-inch-wide stock is used for the front and back panels; the 1-inch-wide stock is used for the ends and sides. For the innards, you need a piece of $\frac{5}{32} \times \frac{5}{16}$ -inch rectangular tubing, a $\frac{1}{4} \times 0.032$ -inch strip, and a few small pieces of 0.005-inch-thick stock to provide inter-stage shields and form the 50- Ω transmission lines that run from the BNC connectors to the switches at the ends of the step attenuator.

For the front panel, nibble or shear a piece of 2-inch-wide brass to a length of about $9\frac{1}{2}$ inches. Space the switches from each other so that a piece of the rectangular brass tubing lies flat and snugly between them. Drill holes for the #4-40 mounting screws and nibble or punch rectangular holes for the bodies of the slide switches.

Before mounting any parts, solder in place one of the 1-inch-wide chassis side pieces to make the assembly more rigid. Solder the side piece to the edge of the top plate that faces the "through" side of the switches; this makes later assembly easier (see Figure 2).

I installed BNC input and output connectors on the top (front) panel, which may not be the best location. You may be able to achieve a little better lead dress and high-frequency performance if you mount the connectors at the ends of the enclosure.

The DPDT slide switches I used are designed for sub-panel mounting. Their mounting holes are tapped for a #4-40 screw, so I slightly enlarged the holes to allow a #4-40 screw body to slide through. Before mounting the switches, make the "through" switch connection (see Figure 1) by bending the two lugs at one end of each switch to-

Table 2
Closest 1%-Tolerance Resistor Values

Attenuation (dB)	R1 (Ω)	R2 (Ω)
1.00	866.00	5.60
2.00	436.00	11.50
3.00	294.00	17.40
5.00	178.00	30.10
10.00	95.30	71.50

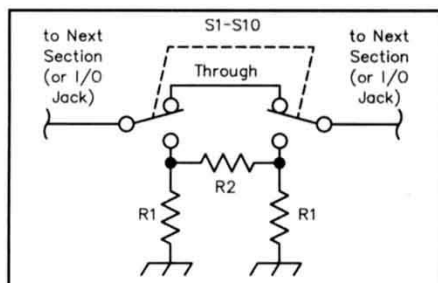


Figure 1—Schematic of one section of the attenuator. All resistors are $\frac{1}{4}$ -W, 1%-tolerance metal-film units. See Table 2. Any attenuation value from 1 to 71 dB, in 1-dB steps, can be selected by using the appropriate combination of switches. Good accuracy is maintained through 225 MHz and even 450 MHz (see Table 1).

S1-S10—DPDT slide switch (Digi-Key SW116-ND, Digi-Key Corp, 701 Brooks Ave S, PO Box 677, Thief River Falls, MN 56701-0677, tel 800-344-4539, 218-681-6674, fax 218-681-3880); equivalent switches can be substituted.

Misc: Brass sheet and rectangular tubing (see text), metal spacers, hardware and input/output connectors.

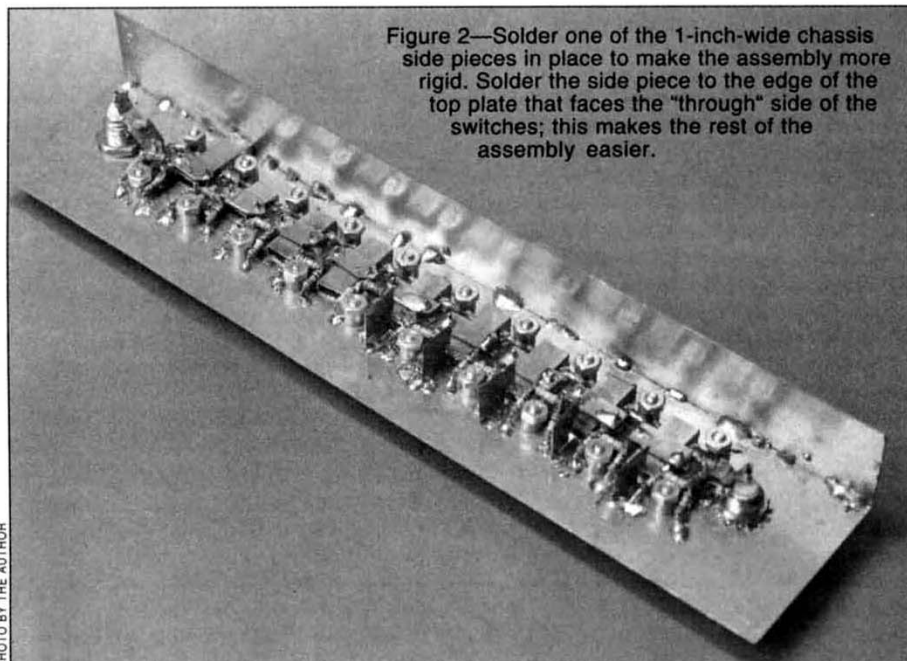


Figure 2—Solder one of the 1-inch-wide chassis side pieces in place to make the assembly more rigid. Solder the side piece to the edge of the top plate that faces the "through" side of the switches; this makes the rest of the assembly easier.

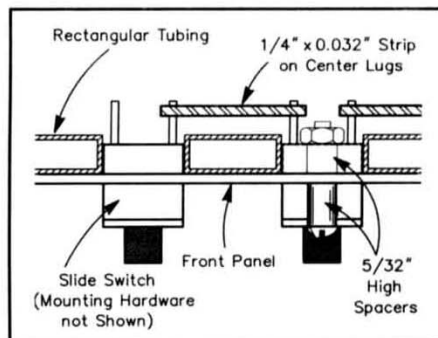


Figure 3—The trick to getting acceptable insertion loss in the "through" position is to make the whole device look as much as possible like 50-Ω coax. The rectangular tubing and the $\frac{1}{4} \times 0.032$ -inch brass strip between the switch sections form a 50-Ω stripline.

ward each other and soldering the lugs together. Or, solder a small strip of brass between the lugs and clip off the lug ends. Mount the switches above the front panel, using $\frac{5}{32}$ -inch-high by $\frac{7}{32}$ -inch-OD spacers. Use the same size spacer on the inside. On the inside, the spacer creates a small post that helps reduce capacitive coupling from one side of the attenuator to the other. The spacers position the switch so that the 50-Ω stripline can be formed later.

The trick to getting acceptable insertion loss in the "through" position is to make the attenuator look as much as possible like 50-Ω coax. That's where the rectangular tubing and the $\frac{1}{4} \times 0.032$ -inch brass strip come into the picture (see Figure 3); they form a 50-Ω stripline.

Cut pieces of the rectangular tubing, about $\frac{1}{4}$ -inch long, and sweat solder them to the front panel between each of the slide switches. Next, cut lengths of the $\frac{1}{4}$ -inch strip long enough to conveniently reach from switch to switch, then cut one more piece. Drill $\frac{1}{16}$ -inch holes near both ends of all but one of the $\frac{1}{4}$ -inch strips. The undrilled piece is used as a temporary spacer, so make sure it is flat and deburred.

Lay the temporary spacer on top of the rectangular tubing between the first two switches, then drop one of the drilled $\frac{1}{4}$ -inch pieces over it, with the center switch lugs through the $\frac{1}{16}$ -inch holes. Before soldering, check the strip to make sure there's sufficient clearance between the $\frac{1}{4}$ -inch strip and the switch lugs; trim the corners if necessary. Use a screwdriver blade to hold the strip flat and solder the lugs to the strip. Remove the temporary spacer. Repeat this procedure for all switch sections. When you're done, you'll have a 50-Ω stripline running the length of the attenuator.

Next, solder in place the three resistors of each section. Use 1%-tolerance resistors and keep their leads as short as possible. If you

must leave a resistor ground lead longer than you like, use a generous blob of solder to make the lead less inductive. Install a $\frac{1}{2}$ -inch-square brass shield between each 10-dB section to ensure that signals don't couple around the sections at higher frequencies.

Use parallel $\frac{1}{4}$ -inch strips of 0.005-inch-thick brass spaced 0.033 inch apart to form 50-Ω feed lines from the BNC connectors to the switch contacts at each end of the stripline (see Figure 4).

Finally, solder in place the remaining enclosure side, cut and solder the end pieces, and solder brass #4-40 nuts to the inside walls of the case to hold the rear (or bottom) panel. (You may find it easier and sturdier to solder the screws to the case walls.—Ed.) Drill and attach the rear panel and round off the sharp corners to prevent scratching or cutting anyone or anything. Add stick-on feet and labels, and your step attenuator is ready for use.

Summary

You'll find the attenuator a useful tool.

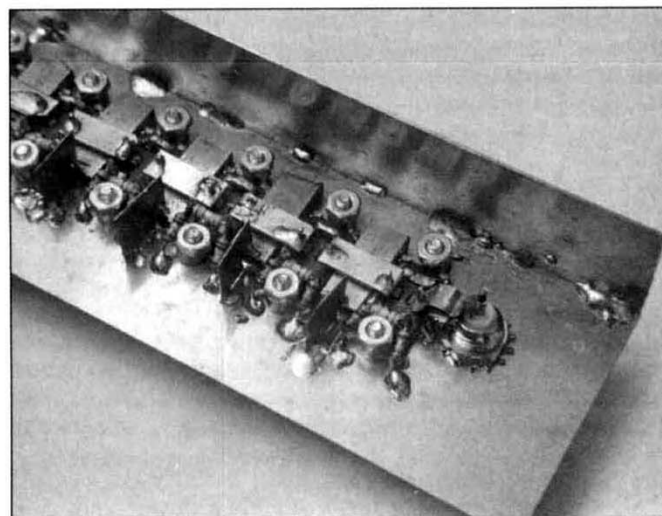


Figure 4—The attenuator before final mechanical assembly. The $\frac{1}{4}$ -inch strips are spaced 0.033 inch apart to form a 50-Ω connection from the BNC connector to the stripline. There are $\frac{1}{2}$ -inch square shields between 10-dB sections. The square shields have a notch in one corner to accommodate the end of the rectangular tubing.

Used with a simple broadband detector,² it provides a convenient way to make absolute power measurements up to 250 mW. For antenna gain, F/B and F/S measurements, the attenuator can be used in line, with the receiver acting as the detector. Calibrated attenuator steps are much more accurate for this purpose than most receivers' S meters. Of course, the attenuator is also useful for performing receiver MDS and two-tone dynamic-range measurements.

Remember: This unit is built with $\frac{1}{4}$ -W resistors, so it can't dissipate a lot of power. Remember, too, that for the attenuation to be accurate, the input to the attenuator must be a 50-Ω source and the output line must be terminated in a 50-Ω load.

Notes

¹See also Bob Shriner, WA0UZO, and Paul K. Pagel, N1FB, "A Step Attenuator You Can Build," *QST*, Sep 1982, pp 11-13. PC-board material cut to size and with switch and jack mounting holes made for the 1982 attenuator enclosure only is available from FAR Circuits, 18N640 Field Ct, Dundee, IL 60118-9269. Price: \$8, plus \$1.50 shipping.

²See the sidebar "Measuring Double-Tuned Circuit Performance" on page 31 in Wes Hayward, W7ZOI, "The Double-Tuned Circuit: An Experimenter's Tutorial," *QST*, Dec 1991, pp 29-34.