

# A PIC-Based Digital Frequency Display



Build this inexpensive, miniature counter for your test bench or as a display for your superhet or direct-conversion HF, VHF, UHF or SHF rig. Adjustable IF offset and prescale compensation make its application to your radio a snap!

**T**he IF offset required for using a frequency counter to display the frequency of superheterodyne receivers and transmitters has always been a problem—that is, until now. The Digital Frequency Display (DFD) is a frequency counter with a difference. The sidebar “DFD Specifications” gives a quick overview of the project.

IF offsets from 0 to 32.7675 MHz (in 500-Hz steps) can be set via two 15-turn trimmer pots. A discrete input determines whether the IF offset adds to or subtracts from the LO count. This discrete input can connect to the band switch of band-imaging receivers to display the correct frequency for both bands. The LO input limit of 30 MHz covers the HF bands. VHF, UHF or SHF operation requires an external prescaler to keep the DFD input lower than 30 MHz. A third, **PRESCALE**, 15-turn pot sets a multiplication factor from 1 to 256. The LO, IF and resultant displayed frequency are all multiplied by the prescale value, to compensate for the division of an external prescaler. This allows the DFD to display up to 8 GHz with an external prescaler.

A fourth input reads an external resistor to select an operating mode for display. The available modes are: blank (no mode), AM, FM, CW, USB, LSB, FSK and FAX. By incorporating appropriate resistors into the mode-switch circuitry, you may be able to control the mode display from the mode switch in your radio.

Counter displays like the DFD are unsuitable for swept-frequency applications such as spectrum analyzers.

## Theory of Operation

The brain of the DFD is a PIC16C71 microcontroller. (See Figure 1.) Like all PICs, this one has an externally incrementable counter and an 8-bit internal prescaler. In the DFD, the PIC prescaler is set to 16. A measurement period of 160 ms provides a frequency resolution of 100 Hz and an update rate of about six times per second.

The 16C71 has four channels of 8-bit A/D conversion. Two channels read the **COARSE** and **FINE** controls to provide a 16-bit number that the software multiplies by 500 Hz to obtain the IF offset. The offset then adds to or subtracts from the measured frequency as determined by the  $\pm$  (RB7)

input. A third A/D channel reads an 8 bit value from the **PRESCALE** pot, which is multiplied by the RF ( $= LO \pm IF$ ) value before displaying the result. The fourth A/D channel reads the mode-programming resistor network. Voltage division across an external **MODE** resistor and R5 determines the mode display. (See Table 1.)

The input section is a CD74HC4046 IC. You may wonder what a CMOS PLL is doing in a frequency counter. Refer to Figure 2, and you'll see. The DFD circuit uses only the two circuits in heavy lines. (Pin 5 is tied high to inhibit oscillation.) Phase comparator 1 (PC1) is an **EXCLUSIVE-OR** gate, and as long as pin 3 is tied high or low (zero frequency),

## DFD Specifications

**LO input:** 0 to 30 MHz, 50 mV P-P (–22 dBm) to 5 V P-P (+18 dBm).  $Z_{in} = 250\text{ k}\Omega$  or less.

**IF Offset:** Two on-board, 15-turn controls (**COARSE** and **FINE**) select offsets from 0 to 32.7675 MHz, in 500 Hz increments (when Prescale = 1).

**ZERO:** This input disables IF-offset calculations for direct frequency measurements. Ground (0 V) to disable offset, high (5 V) to enable offset calculations.

**$\pm$ :** This input determines whether IF offset is added or subtracted from the LO count. This can be connected to the bandswitch of band-imaging receivers.

**PRESCALE:** Set by on-board, 15-turn pot. Compensates display for external prescalers with divide ratios of 1 to 256 (IF Offset, LO frequency and resolutions are multiplied by the Prescale value)

**Display:** 16-character LCD

Frequency: 6 digit, floating point in kHz, MHz or GHz (100-Hz resolution when Prescale = 1). Updates 6 times per second

Mode: blank, AM, FM, CW, USB, LSB, FSK or FAX, as determined by external resistor (see Table1)

**Power requirement:** 8 to 18 V, 30 mA, unregulated



If you have a band-imaging receiver for the 17 and 30-meter bands with an IF of 4.0 MHz and an LO of 14.0 to 14.168 MHz, the readout frequencies will be 18.0 to 18.168 MHz (LO + IF) and 10.0 to 10.168 MHz (LO - IF).

If you have a band-imaging receiver for the 80 and 20-meter bands with an IF of 9.0 MHz and an LO of 5.0 to 5.5 MHz, then the readout frequencies will be 14.0 to 14.5 MHz (LO + IF) and 4.0 to 3.5 MHz (LO - IF). In this latter case the frequency tunes backward. Mathematically, LO - IF returns a negative number, however, the DFD will display the correct frequency because it displays the absolute value of LO - IF.

### Setting Up the DFD

Adjust the contrast control until the background is just barely visible. Start with the pot at the zero voltage setting (wiper at the ground end, fully counterclockwise). Reduce the contrast to the desired level by turning clockwise.

### Superheterodyne Mode (ZERO = +5 V)

When the LO input is shorted, the unit displays the IF offset, which allows it to be easily set. Begin by adjusting the **PRESCALE** pot to the 0-V end (fully ccw). This sets the prescale value to 1. Adjust the **IF Offset** pots until the display shows the desired IF. (If the prescale value is to be greater than 1, adjust the IF offset to IF ÷ prescale.) Finally adjust the **PRESCALE** control to display the actual IF.

For example, if the IF of a UHF device is 100 MHz and the LO input passes through a divide-by-16 prescaler, then, with **PRESCALE** set to 1, adjust for a display of 100 MHz ÷ 16 = 6.2500 MHz then adjust **PRESCALE** to obtain a reading of 100.000 MHz. In this way, both the IF-offset and prescale values will be correctly set. Connect the LO input to a buffered output of your LO and you're up and running.

### Direct Conversion, Bench-Top Counter Mode. (ZERO = 0 V)

The IF-offset controls are disabled and

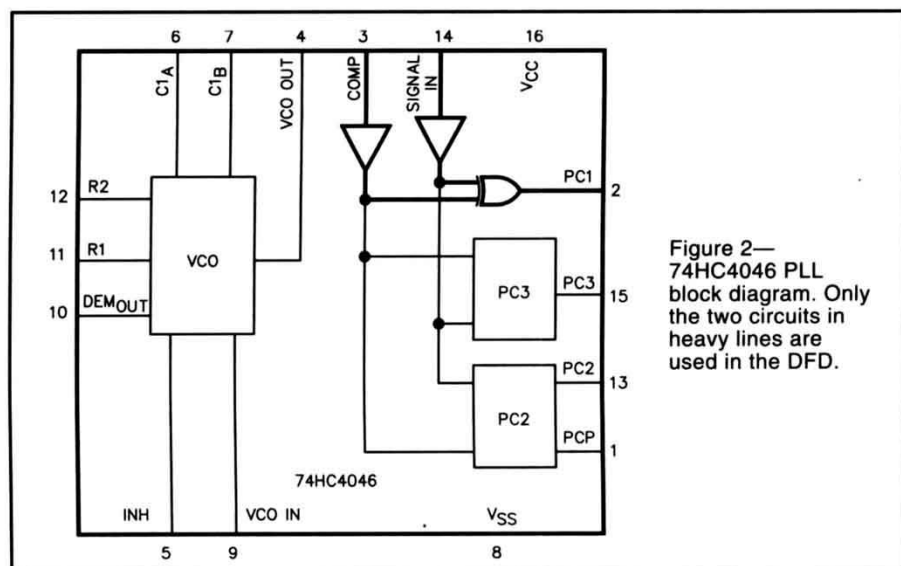


Figure 2—74HC4046 PLL block diagram. Only the two circuits in heavy lines are used in the DFD.

the LO input is displayed directly. The **PRESCALE** control still works to display frequency data from an external prescaler.

To adjust the prescale value start with **PRESCALE** set to 1. Use the superheterodyne mode and set DFD for a 1.00000 MHz IF. Then adjust **PRESCALE** until display shows the prescale value. Then ground **ZERO**.

For example, if your prescaler divides by 16, tie **ZERO** high, adjust **PRESCALE** to 1 (0 V, fully ccw), adjust the IF offset to 1.0000 MHz, adjust **PRESCALE** to display 16.0000 MHz then ground **ZERO**.

### Operating Tips

For maximum long-term stability, set the IF-offset and **PRESCALE** controls halfway between their transition points.

The DFD includes a regulated battery power supply. You may omit this supply if regulated 5-V power is available.

If you're concerned about battery drain, wire a push-button switch into the power lead. That way the DFD will operate (and draw

power) only when you press the button.

### Conclusion

The DFD is a versatile, inexpensive frequency counter and display that can be easily adapted to most any radio. Build one and try it with your existing rig or your next project. Even the simplest radios can now sport an accurate frequency display.

Neil was a professional electronics engineer (BSEE) for over 35 years with the Boeing Company of Seattle, Washington. He retired a couple of years ago, and now designs and manufactures kits and software for electronic hobbyists, engineers and radio amateurs as a retirement hobby. Neil's Amateur Radio license (W0NRC) expired in about 1957. He was one of the first SSB operators in those days. He discovered, however, that his interests were in equipment design, rather than operation. Neil has several ham projects under development now, so he plans to get a new license. You can reach Neil at Almost All Digital Electronics (see Note 1).

QST

## New Products

### WIZARD, AFFORDABLE HF PROPAGATION PREDICTION SOFTWARE FROM KANGAROO TABOR

◆ Featuring a fast 32-bit IonCAP+ prediction engine, Wizard provides ham operators with specialized, intuitive information and predictions about HF radio circuits worldwide. "At a glance" reports include Best Band Summary, an hourly prediction of the band most likely to support a given radio circuit; All Band Summary, a 24-hour

report of anticipated conditions for each ham band; Band Summary Plus, additional band data including accommodations for take-off angle and specific propagation modes; and Dynamic Band Summary, where users can quickly toggle between CW and SSB modes, signal-to-noise ratio, take-off angle, propagation mode and service probability.

Other features include an intelligent Mercator projection map that's dynamically linked to a DXCC database. Requires Windows 3.x or Windows 95 running on a 486-class PC or better. Price: \$29.95 plus \$5 s/h. For more information, contact Kangaroo Tabor Software at Rt 2 Box 106, Farwell, TX 79325; tel 806-225-6989, fax 806-225-4006, e-mail [ku5s@wtrt.net](mailto:ku5s@wtrt.net),

WWW <http://www.wtrt.net/~ku5s>. VISA/MC accepted.

### THE NIGHT PATTERN BOOK FROM THE NATIONAL RADIO CLUB

◆ The fourth and newest edition of the NRC's *Night Pattern Book* is now available. In 208 wide-format pages (punched for standard three-ring binders), the book details maps, indexes and nighttime antenna radiation patterns for radio stations in US and Canada.

Price: \$22.95 (US and Canada); \$21 (Latin America); \$24 (Europe); and \$28 (elsewhere). Please mail prepaid orders to National Radio Club, Publications Center, PO Box 164, Mannsville, NY 13661; tel 315-387-3583.

QST