

QEX²⁸

June
1984
\$1



The ARRL Experimenters' Exchange

Packet Radio Gathers Forces

The bearded experimenters have emerged from their basements! This was the aura at the 1984 Dayton Hamvention as 300 plus crowded into the Packet Radio Forum. In previous gatherings, technical speakers shared the rewards, as well as failures, of their experiments, spoke of protocols, and how this technology might work one day. This time, however, people came to recount the group's accomplishments; to get things going at a faster pace. Packet radio communications is slowly, but successfully, evolving.

About 1700 terminal-node-controller (TNC) boards, (or software equivalents), have been sold. Thirteen hundred of them are considered operational being mostly owned by the Tucson Amateur Packet Radio (TAPR) Group. Other TNCs are available from VADCG, AEA, Ashby, and GLB Electronics. Richcraft Engineering sells packet software for the TRS-80[®] models I and III, as well.

A number of new networks have been sprouting locally since the ARRL Hq. packet repeater has been installed on 145.01 MHz. It recently had a call sign change to W1AW/R and has become more active with these new check-ins. We are in the process of locating a permanent site at a better location. Our goal is to get a solid path to the new packet machine installed atop Mt. Graylock in Massachusetts by the New England Packet Radio Association (NEPRA).

Not long ago, we reported OSCAR 10 teleport experiments by several stations. The same type of relaying is being done to connect HF packeteers to the Washington, DC VHF local net by WB4APR. Lis-

ten weekends in the upper 10 kHz region of the 30-meter band and you should hear some activity.

The bugs in the link-layer protocol seem to have been removed, and KA9Q appears to have solved the last problem -- how to use the poll/final bit. Unless someone screams, AX.25 level-2 author, WB4JFI, will make the changes in the specification. If all goes well, we will have a final spec and several implementations of mature software ready for ARRL Board approval in October.

The next standards hurdle is the network-layer protocol. Proposals will be discussed at the ARRL Digital Committee meeting in September at ARRL Hq. We're hoping for agreement at this meeting.

If you haven't read K1ZZ's editorial in June QST, take a look. It reflects growing acceptance of packet radio as a means of solving some ageless problems.

Second Spread-Spectrum STA

The FCC just granted a second special temporary authority (STA) for experimentation in spread spectrum to the Amateur Radio Research and Development Corp. (AMRAD). This STA covers VHF frequency hopping. Look for more details in QEX.

Are There Columnists Out There?

If you fancy yourself a potential QEX columnist, let us hear from you. Rather than restricting your thinking by our suggesting column subjects, we'd like to hear your proposal. -- W4RI

Correspondence

Log Program for the Apple IIe

I recently purchased an Apple IIe computer with two disk drives and an MX 80 Epson printer. I am a member of the International Ten Tec club and chase certificates. My problem? I've purchased two different programs on keeping logs and neither one is satisfactory for my needs. Is there anyone with knowledge of a program that incorporates up to 8 certificates with recall on each by either their call or 10-X number?

I have heard discussions on ten meters about computers performing services such as this. After conferring with these hams, I learned that they are using other computers and not an Apple. If anyone knows of where I could obtain a program like this, I would be happy to hear from them. -- Joseph Terest, Jr., KAØKCE, 6201 Chowen Ave. South, Edina, MN 55410.

More on the Osborne Computer and RTTY

This is in response to J. Don Corley's, W5KTX, note in the April "Correspondence" column (QEX, no. 26), but may be of interest to other readers as well. Advent Products, 965 N. Main St., Orange, CA, 92667 manufactures a retro-fit switchable baud-rate device for the Osborne. Rates are 50 to 19,200, including 110. In addition to permitting amateur-baud rates, the device allows dumping into a spooler at a high rate, freeing the use of equipment for other tasks. The price is in the \$70 range. Several amateurs in the Seattle area own this device and have them running with no problem. -- Dave Plant, NA7K, 10811 NE 143, Kirkland, WA 98034.

For Want of a Better Article

What a disappointment! I was reading an

article on using my Timex computer for Amateur Radio purposes and all it told me was that it works.

How about some how-to data on interfacing with RTTY, AMTOR, CW, etc? It's out of my field, but of great interest to me. -- Dave Zinder, W7PMD, ARRL Technical Advisor, Southwestern Division, 4121 West Augusta, Phoenix, AZ 85021.

In This Issue

Part 2 of, "The GB3US Mk2: A Microprocessor Repeater Logic System," starts on page 5. The Radio Society of Great Britain kindly granted us permission to reprint this fine article in QEX. It originally appeared in the RSGB journal, RADIO COMMUNICATION, November 1983.

You can now join The Radio Society of Great Britain through ARRL Headquarters. Annual dues are \$23 and you will receive their monthly membership journal, RADCOM. ARRL will also handle renewals.

We welcome correspondence from subscribers and/or readers who happen upon an issue of QEX in their ramblings through Amateur Radio related literature. Whether your comments are positive or negative, we are interested in your response. Only you can tell us what articles you would like to see or what we are doing wrong.

For those gifted in the art of writing, we would be happy to review articles for publication. If you have information you would like to share about Packet Radio, RTTY, or computer programs performing an important Amateur Radio function, send them in. - KALDYZ.

QEX

QEX Subscription Order Card

American Radio Relay League
Newington, Connecticut, U.S.A. 06111

For 12 issues of QEX:

In the U.S.

ARRL Member \$6.00

Non-Member \$12.00

in Canada, Mexico, and

U.S. by First Class Mail

ARRL Member \$8.40

Non-Member \$14.40

Elsewhere by Airmail

ARRL Member \$20.00

Non-Member \$26.00

Elsewhere by Surface Mail

ARRL Member \$9.60

Non-Member \$15.60

Remittance must be in U.S.

funds and checks must be

drawn on a bank in the U.S.

Prices subject to change

without notice.

QEX, The ARRL Experimenter's Exchange is available at the rates shown at left. Maximum term is 12 issues, and because of the uncertainty of postal rates, prices are subject to change without notice.

Renewal New Subscription

ARRL Membership Control # _____

Name _____ Call _____

Address _____

City _____ State or Province _____ Zip or Postal Code _____

Profession: _____ Signature _____

Payment Enclosed

Charge to my

Mastercard

VISA

American Express

Account # _____ Valid from _____

Signature _____ Good thru _____ MC Bank # _____

Date _____

QEX1 683

QEX June 1984

Modifications for the Heathkit ET-3400A Microprocessor Trainer

By Donald G. Varner,* WB3CEH

How would you like to double the memory capacity of your Heathkit ET-3400A with no additional hardware? It can be done and this article deals with such a modification. If you have ever experimented with microprocessors in Amateur Radio, you know that they are becoming increasingly popular. Their tasks vary from controlling various functions within the radio to microprocessor-based repeater controllers.

The origin of this modification begins with Bill Johnson, K3FOW. We were comparing our Heathkit 3400 series microprocessor trainers. Bill mentioned that he had increased the Random Access Memory (RAM) in his 3400 early-version trainer, using two 2114's NMOS (1024 x 4) static RAM chips. We noticed that my trainer, a later version -- the 3400A, uses these same two static RAMS already on board the trainer. These devices have a capacity of 1 k Ω , but the 3400A was only using 0.5 k Ω .

K3FOW's goal was to revise the schematic. My job was to review the X-ray drawing. With this information, it was determined that a minor modification could be employed to use the remaining 0.5 k Ω of RAM in the 3400A without adding any hardware.

The modification centers around 4 IC's: U14, no. 443-764, an MM2114; U15, no. 443-764, an MM2114; U20, no. 443-807, a 74LS42; and U5, no. 443-45, a 7408. (Reference the schematic for actual wiring changes.)

The first step is to get the A9 lines (pins 15) of U14 and U15 off ground and tied together. This is easily accomplished by removing the IC's and their sockets from the board. The tracks for

pins 15 are on the top side of the board and under the sockets, making socket removal necessary.

U15 also has a track on the bottom side of the board. It is connected to the leg of C26 which is at ground potential. This track has to be cut from pin 15 to C26, and the point at C26 reconnected to a convenient ground point.


A continuity check is appropriate here to see if in fact the IC holes for pins 15 are off ground. If they are not, even though the tracks are cut, it is because a shield at ground potential is used in the middle of the board between the top and bottom track surfaces. It might be necessary to drill out these IC holes and insert a sleeve of Teflon tubing over the IC socket legs of pins 15 to ensure that they will not be grounded inadvertently. They can now be wired together, point-to-point, and reconnected to the proper point (see schematic).

The additional changes are straight forward. U5a, pins 2 and 3, tracks should be cut. The connections at these points should be removed and reconnected to the proper points on U20.

By taking your time and using the circuit board X-ray view, feed through holes can be located and used to make the wiring modification solder connections to the appropriate circuit points. The finished modification can be done with hook-up wire on the back side of the board, leaving the trainer's top board unblemished.

It is worth the effort to obtain additional 0.5 k Ω of RAM. This doubles the 3400A's board memory capacity at no extra cost. The memory obtained after modification is addressed from 0200 through 03FF. Good experimenting with the 6808 microprocessor!

*214 Bryant St., Vandergrift, PA 15690

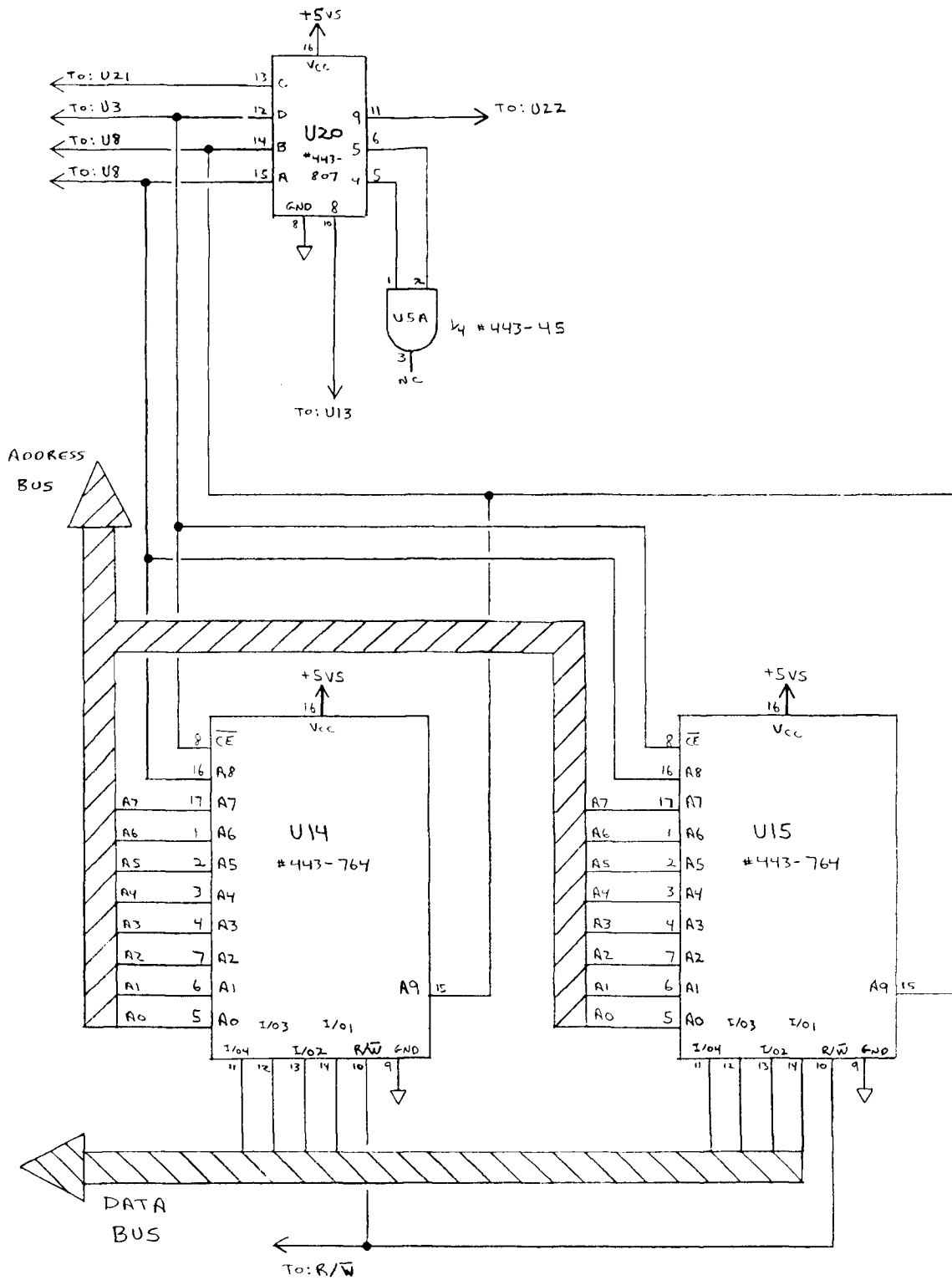

The Heathkit ET-3400A Microprocessor Trainer schematic. Modifications are shown.

THE GB3US Mk2

A microprocessor repeater logic system

PART 2

by A. J. T. Whitaker, G3RKL*

Construction

Fig 4 shows the pcb layout, and Fig 5 the corresponding component positions, the holes for which should be drilled 0.85mm diameter, except those for X1, Z1, RG1, C15 and all the preset resistors, which should be 1mm. The board has been designed so that there are no top soldered connections at any of the ic pins, so holders can be used throughout. If holders are used for ics 7, 11 and 14, RV8, RV9 and RV11 should be mounted on Veropins, otherwise they will not clear the holders without some "adjustment" with a file. Mounting the components is quite straightforward, the recommended order being through-pins (Veropins), diodes, resistors, presets, capacitors, ic holders and the remaining components. The crystal should be mounted on fibre washers, and the lugs on SK1 and SK2 (if used) removed to prevent fouling RV5, RV6 and the board mounting holes. When all the components have been inserted, a thorough check should be made to ensure that every connection, **top** and **bottom**, has been properly soldered, with no bridges; component polarity is correct where appropriate, and that no snagging or unwanted contact is made by the presets when turned through their full travel.

Setting up

The only test instruments required are a multimeter, dual-trace oscilloscope and audio oscillator.

1. If holders are used throughout, without any ics in place, apply +13.5V, check for shorts, and that the +5V and +10V lines are correct.
2. Set RV1, 2, 3, 7, 8 and 10 midway, and the rest of the presets fully counter-clockwise. Insert a 100Ω, 0.5W resistor between pins 21 and 12 in IC2's holder, and, omitting IC2 (the eeprom), carefully insert all the other ics, taking due precautions with the cmos devices. Temporarily short SK1/5 (reset) to earth.
3. Apply +13.5V, check that the current is approximately 65mA and that the +5V and +10V lines are (still) correct.

4. Check that the crystal oscillator is working, and that a 1,750Hz square wave appears on IC10/2, 875Hz on IC10/5 and a short negative pulse of about 200μs on IC1/36 every 9.1ms.
5. Inject a 2V peak-to-peak sine wave into the receiver audio input (SK1/8) at 1,750Hz—the frequency can be checked against IC10/2—and set RV4 to give 1V pp at its wiper. As with the Mk1, this control is set in actual operation to give 1V p-p at this point for the maximum audio signal from the receiver (5kHz deviation for fm).
6. With the scope, testing at IC13/7 (notch filter output), carefully adjust RV1, which should give a small portion of travel over which the 1,750Hz signal is reduced. Set it in the centre of this portion and adjust RV2 and RV3 alternately to give minimum signal. Re-adjust these three presets to give the best null symmetrically about 1,750Hz. IC5/13, the logical audio input, should show a 1,750Hz square wave.
7. With the scope, testing at IC8/5 (pll vco), set RV6 to give a 1,750Hz waveform (again compare with IC10/2) changing R23 if necessary.
8. With the 1,750Hz still applied, advance RV5 to give about 400mV p-p at IC8/3. The 567 should lock, as indicated by IC5/15 going low.
9. Check all the other input lines at IC5 by putting the required logic value(s) on the appropriate input(s) at SK1 and SK2, including the frequency/battery indication.
10. Testing with the scope at the "hot" end of RV9, hold a 100nF capacitor across pins 4 and 5 of IC10, to leak a little 875Hz to the keying filter, and adjust RV8 for a maximum. Holding the 100nF capacitor across pins 2 and 3 of IC10, similarly tune the 1,750Hz filter with RV7.
11. Remove power, the 100Ω resistor in IC2's holder and the shunt across reset. Insert IC2, the eeprom containing the station program and power up.
12. After about 5s, the unit will begin at its initialization point. If it does not, power down and up again (or just reset) until it does. Since it is now under software control, what happens will depend entirely on the program. The GB3US version sends a long bcs (beacon callsign) at this point. Testing with the scope at the transmitter audio output, by simulating the proper receiver audio and squelch inputs, the high level keyed tone amplitudes can be set and matched to the through-audio with RV9, low level with RV11, the Q output (software generated tone) with RV12, and the overall output level to the transmitter with RV10.
13. Finally, re-adjust with the station receiver and transmitter to give the required performance. A few minutes "tweaking" soon gives a feel for the adjustment procedure, which is actually quite straightforward. As with the Mk1, the outside connections may need to be made through a combination of ferrite beads, leadthrough and decoupling capacitors.

Software

A full description of the software is beyond the scope of this article, but a detailed listing, with some explanatory notes, of the original GB3US program is available by writing to the author. The basic subroutine blocks

An extract from the RSGB/Dept of Trade & Industry Specification for 145MHz/433MHz speech repeaters

Except where marked as a recommendation, the specification below is mandatory and forms part of the licence. Groups **must** equal or better the agreed specification.

Control logic

Access: The repeater must not be carrier-accessed directly from "cold", and adequate immunity must be provided against access by speech. Access shall be by a tone of 1,750Hz ± 25Hz at half-system deviation. The acceptance time of the tone shall be between 200 and 400ms.

Re-access: Once the repeater transmitter is switched on, subsequent control of talkthrough must be by carrier unless tone re-access has been permitted in writing by the RSGB.

Timeout: Provision of a restriction on "over" length is optional. If provided, timing is at the discretion of the group. Typical times are 2min on 145MHz units and 5min on 433MHz units.

Close-down: When the repeater is no longer required (no signals on input) it should automatically close down within a recommended period of 5-15s. From this point, access must require a further toneburst. In exceptional cases, the repeater may remain carrier accessed for up to 30s after it has shut down.

Station identification: The callsign as stated on the repeater licence (or as notified to you by RSGB HQ) must be transmitted automatically at not greater than 15min intervals, preferably more frequently, in F3A. A tone frequency of 1,750Hz is recommended, at 500-1,500Hz peak deviation. RSGB recommends that 433MHz repeaters identify every time they are accessed, and at an interval of 5 to 15min, whether they are in use or not (ie "beacon" "callsign"). Procedure on 145MHz units is optional but must be within the guidelines laid down in this paragraph.

*University of Sheffield, Department of Electronic & Electrical Engineering, Mappin Street, Sheffield S1 3JD.

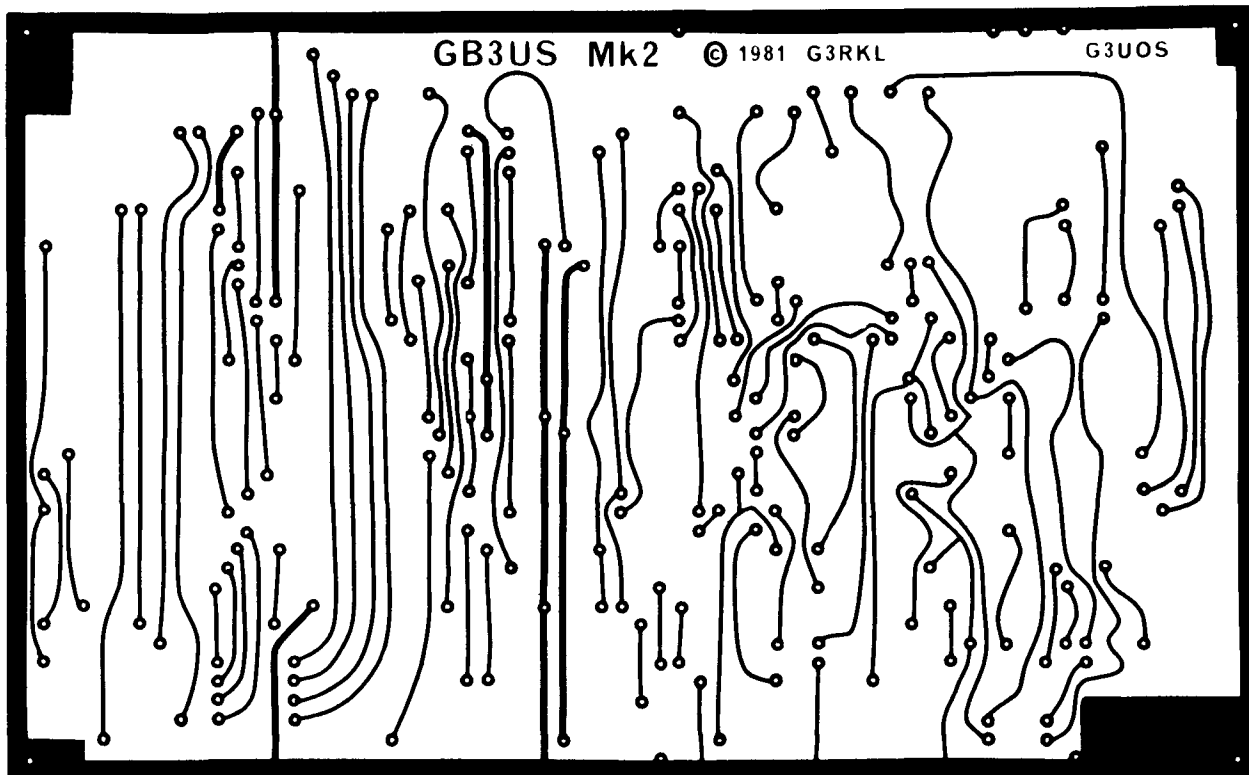


Fig 4(a) Top view of the pcb

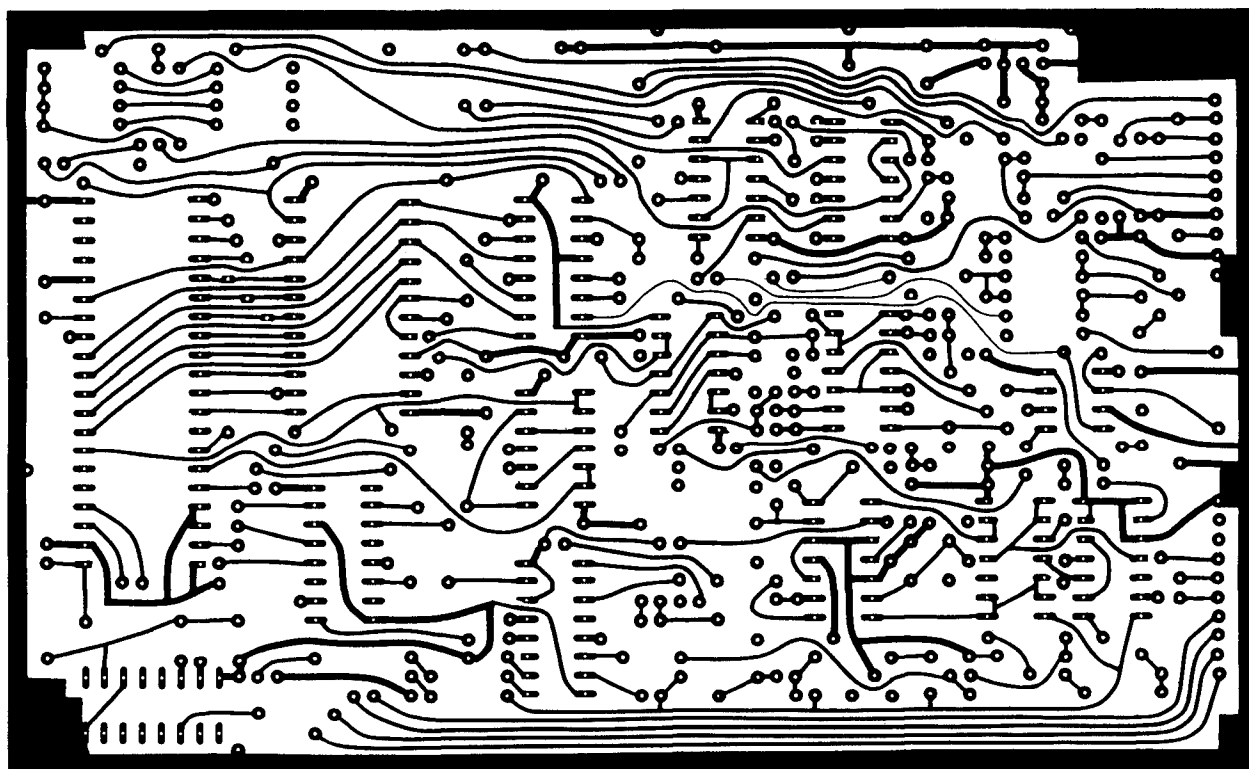


Fig 4(b) Underside view of the pcb

and their interconnection are shown in Fig 6, which give the following operating characteristics:

- (a) Beacon callsign at 875Hz every 5min when not in use, sent as DE GB3US (short bcs), with every fourth one sent as DE GB3US SHEFFIELD (long bcs).
- (b) Valid tone plus 5s of carrier for full initial access, success indicated by a low deviation callsign at 1,750Hz.

(c) 4min talkthrough time. (Present RWG recommended time is 5min for a 432MHz repeater.)

- (d) 1s forbidden gap before reaccess, to allow other stations to break in.
- (e) Carrier reaccess during a 10s reaccess period, indicated by two high-level 1,750Hz pips spaced 5s apart, the first replaceable by a status level H, L or B. Identification callsign sent when the timer is reset, if a period greater than 2min has elapsed since the last one.

The GB3US control program

000	7100	F800	B1F8	08A1	F89A	BCBD	2D9D	3A0C	370	938E	FA18	A395	F6F6	F6F6	3387	F633	8283
010	858E	A2A8	ACAD	AEAF	F801	BFF8	4082	E2C4	380	3092	83F9	0230	92F6	338F	83F9	0130	9283
020	9FFA	EF8F	FEFE	F1FA	2032	389E	FA0C	3238	390	F903	B59F	FA80	3A9F	9EF9	038E	C006	809F
030	F80C	3238	9EF8	0C38	9E52	92F9	4082	F800	3A0	FAEF	BFF8	0380	F8AA	A0D0	E0F8	00B1	F848
040	61F8	40A1	E070	0000	02F8	01AE	FA20	3254	380	A170	0029	89FA	10CE	7A00	893A	C0F8	1FA9
050	9FF9	088F	9D3A	5F8D	3A5F	9FF9	208F	382D	3C0	78F8	5AA3	2383	3AC4	39C0	7A30	C19F	FA40
060	8EFA	0132	6892	F938	B230	7892	FA38	3278	300	3AD6	9EFA	338E	9FFA	78F9	038F	8FFA	7FAF
070	92FF	0862	8EF9	01AE	8EFA	0232	8392	F907	3E0	F866	B6F8	8AA6	3000				
080	6230	9892	FA87	32A6	92FF	0182	8EF9	82AE	400	2888	3A1C	9FFA	78F9	058F	8FFA	7FF9	08AF
090	82FA	003A	9E22	82F8	163A	E4F8	DAE2	82FA	410	F804	B6F8	50A6	F890	ASC0	0680	8EFA	0132
0A0	7F32	E422	38E4	82FA	8032	D182	FA7F	32D1	420	2D9F	FAF8	F903	B8F8	FA7F	F900	AF9F	FA80
0B0	88FA	803A	B8F8	B7A8	288E	FA01	32CE	88FA	430	CA03	9FC0	0680	F833	B7F8	45A7	F880	80F8
0C0	7F32	CA8E	FA02	32E4	30CE	9FF9	108F	F800	440	2CAD	F806	B9F8	66A9	F81F	B8F8	7088	AA9F
0D0	A8F8	00A2	9FFA	18F8	183A	E49E	FA01	C201	450	F940	FADF	BF9E	FA3F	F941	BEC0	0680	
0E0	06C0	0509	F800	B3F8	E8A3	D39F	FA07	B18F	500	8EFA	0132	1A25	853A	1397	3A0D	87CA	03CD
0F0	FA80	A1D1							510	C001	869E	F903	BEC0	0680	2696	F804	3A49
100	9FFA	1032	11F8	02B7	F823	A78F	F980	AF30	520	86F8	4E3A	4995	FA03	FC60	A9F8	0689	F804
110	809F	FA20	3247	9EFA	3032	239E	FF10	8EF8	530	B8F8	6088	AA9F	F940	BF9E	FA3F	F941	8EF8
120	1F30	299E	F930	8EF8	4288	F806	B9F8	66A9	540	9ABC	F800	ACB5	C006	8096	F802	3A53	86F8
130	9EF9	016E	F880	BDF8	2CAD	F880	B8AA	9FF9	550	2832	2896	3A96	863A	968F	FA01	3269	9FFA
140	40FA	5FBF	C006	809F	FA80	3262	8EFA	013A	560	F18F	8FFA	7EAF	C004	369F	FAF7	BF8F	F981
150	62F8	0888	F806	B9F8	64A9	9EF9	416E	F870	570	3065							
160	303C	9FFA	403A	689E	FA30	BE8F	FAFE	AFC0	580	9FFA	10CA	0186	9FFA	403A	179F	FAF9	BF8F
170	0680								590	FA7F	AFC0	0167	F890	A59E	FAFD	3016	
180	923A	B787	3AB7	F833	B7F8	45A7	F880	BDF8	600	8EFA	013A	0885	3211	2530	2797	3A23	873A
190	2CAD	9FFA	403A	A4F8	0689	F866	A9F8	1F88	610	239F	FA40	3A43	9FFA	F8F9	058F	8FF9	80AF
1A0	F870	B8AA	9FF9	43FA	588F	9EFA	3FF9	438E	620	C004	3627	F86E	A59F	FA40	3A43	9FF9	408F
1B0	8FFA	7FAF	C003	E08E	FA01	328F	A530	E185	630	F806	B9F8	49A9	F80C	B8F8	2068	AA9E	FA30
1C0	FA80	3AC7	F887	A525	85FA	7F3A	EE9F	FA40	640	F941	8EF8	0085	C006	80AA	AA55		
1D0	3AD7	9EFA	F030	DA9E	FAFD	BE8F	FA7F	AF30	660	808A	AAEA	5EE5	7A27	E3A8	A8CA	CA92	A2A8
1E0	E99E	F903	BE27	C006	809F	FA7F	BF38	27C0	670	8AE2	B8A2	2E8E	95				
1F0	0680								680	9FFA	403A	8CF8	0080	F820	A000	9832	E288
300	9FFA	403A	989C	3A10	8C3A	109F	F908	BF38	690	3295	2830	8598	F6F6	F6F6	A88A	FA0F	C649
310	2C96	F802	3A18	86F8	2332	4796	FF60	3A24	6A0	BABA	FA03	3AC2	9AFE	BA38	DF9E	FE38	B7FE
320	8FFA	FEAF	963A	4E86	3A4E	9FFA	D8F9	868F	6B0	3BBC	9EF9	0D30	BF9E	F905	308F	9EF9	098E
330	8FFA	7FF9	08AF	F880	BDF8	2CAD	F80C	87F8	6C0	30DF	F801	3AD1	9AFE	BA33	DF8A	F903	AAF8
340	D1A7	9EFA	F030	989F	F980	BFF8	1FA9	269F	6D0	02F8	023A	DF9B	FF01	BB9E	FAF3	BE30	DF1A
350	FA20	CA04	3697	3A5B	87CE	C427	8EFA	013A	6E0	3085	9FFA	BF8F	9EFA	3F8E	3085		
360	6CF8	6EAB	9FFA	F8F9	048F	3093	86FA	7F3A									

- (f) Pulsed pre-timeout warning tone, under the through-audio, during the last 5s of relay.
- (g) Non-reaccessible timeout indicated by a trimtone type tone (the famous 'HH' 'strangled parrot'), with 30s maximum default time.
- (h) Tone reaccessible, high-level callsign (1,750Hz) at the end of timeout or first end-of-reaccess.
- (i) Initial access conditions during second end-of-reaccess callsign, if less than 15s of relay have elapsed inbetween.
- (j) Automatic Mode 2 during a 'jammed' input, indicated by a reversal of the usual keyed tone frequencies. This allows the timer to be reset at any time by a valid tone. Automatic return to Mode 1 when the input clears.
- (k) Software determination of a valid tone virtually eliminates false triggering on speech. Nominal acceptance duration is 200ms minimum to 1,000ms maximum, followed by 500ms of carrier.
- (l) Letter 'C' sent (1,750Hz) to indicate that the input has cleared after timeout and the transmitter has closed down.

The program is written in 1802 machine code, as shown in the listing. By copying this **exactly**, with the appropriate changes to the message store and length parameters, an eprom can be 'blown' for a unit to work to the above specifications. The bes message is stored (start address = 666) as a series of two-bit characters, 00 = interletter gap, 01 = interword gap, 10 = a dot, and 11 = a dash, the dot and dash characters automatically containing the one dot space. Thus the sequence 'DE' will be coded as: interword gap, dash, dot, dot, interletter gap, dot, which equals 01, 11, 10, 10, 00, 10, which in hex is 7A,2-. The message length parameters, as a (two-bit) character count are located as follows: short bes (and all other callsigns) at 120, 19E and 449 (= 1F for the 'US program), and long bes at 128 (= 42 for 'US). The talkthrough timer is set at: high byte 3E1, low byte 3E4 as the number of 9.14285ms interrupts required, eg 4min = 26,250 = 668A. Location 04A should be 01 for a logical squelch (1 for

carrier), and 00 for a relay squelch (0 for carrier). To help groups get started, on receipt of a 2516 the author is willing to program it as above, with the requested bes message.

Program development

All the software for this unit has been developed using the RCA COSMAC evaluation kit (CDP18S020), by electrically substituting the kit's micro and ram for the unit's micro and eprom. This enabled the program to be edited in situ with the kit's monitor, but it is unlikely that many people would be able to use this very effective method. However, it might be possible to interface the unit to any of the popular home computers to give the same result, but probably the easiest way to develop a program is to actually blow an eprom and try it, since most home computers have eprom blowing capabilities. With the low cost of 2516s and of the unit itself, it is quite practical for a group to build at least two units, using the spare(s) for standby and program development.

Conclusion

The GB3US Mk2 logic unit is a completely self-contained board suitable for the control of any single channel phone repeater. It is small, easy to build, cheap, economical on power and very flexible in its method of operation. It is particularly suitable for groups running more than one repeater, as it offers the capability of hardware standardization between stations, but individual mode of operation determined solely by one replaceable eprom chip.

The actual program can be made as simple or as complicated as desired, giving the group complete control over the behaviour of their repeater(s), and it can be changed at any time to incorporate additional facilities or Department of Trade & Industry/Repeater Working Group requirements

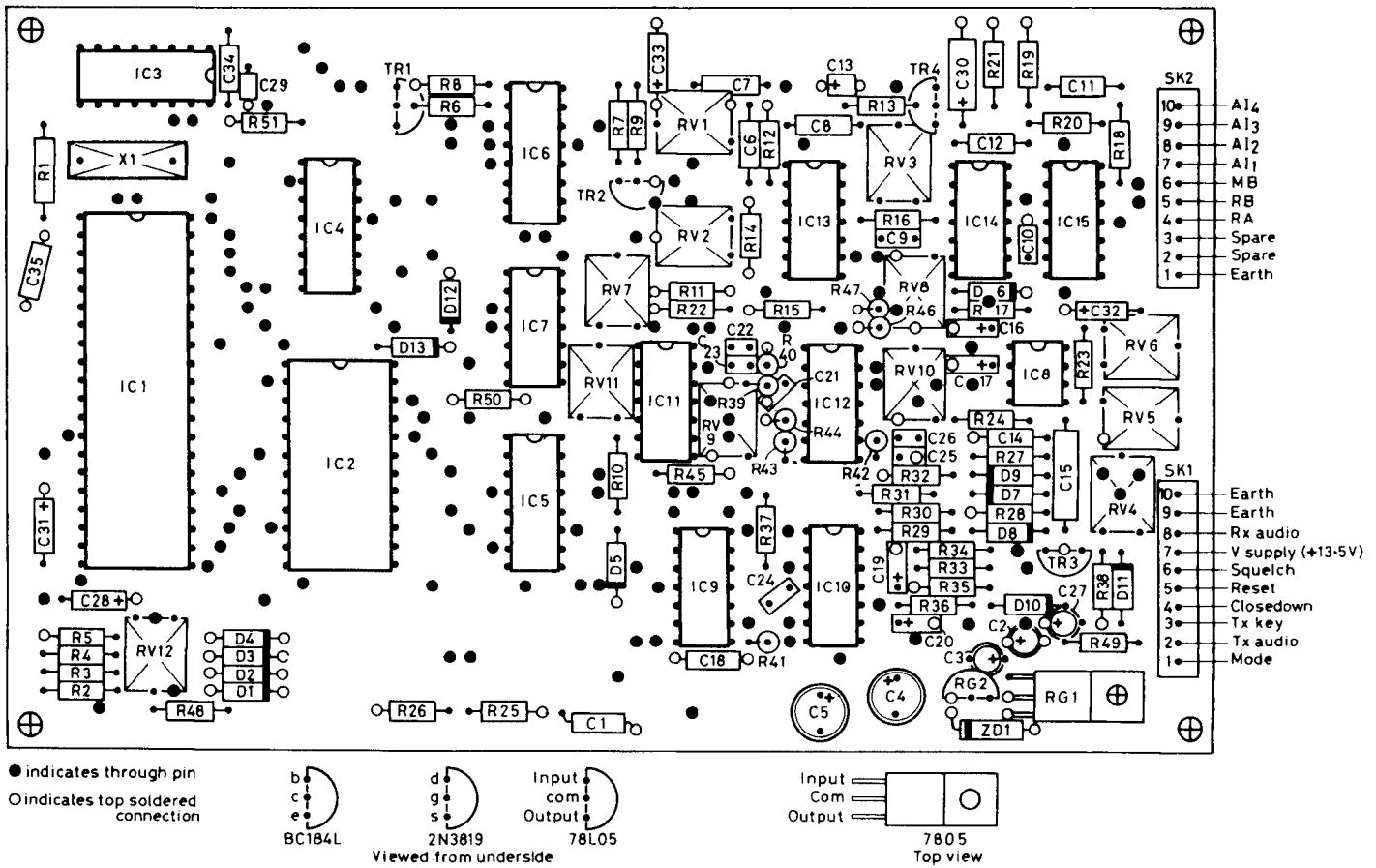


Fig 5. PCB component layout

as necessary. Program development should be possible on any of the popular home computers, providing they have a 2516 eeprom programming board. For the many groups already using GB3US Mk1 logics, the Mk2 is a direct physical and electrical replacement, which will enable them to upgrade their control system to any desired level with a minimum of effort. Two units have been running on GB3US and GB3HH for over a year, and have given very satisfactory and reliable service.

References

- [1] "A basic repeater logic system (the GB3US Mk1)" A. J. T. Whitaker, G3RKL. *Rad Com* Vol 56, No 1, January 1980, pp34-40.
- [2] "Some additions to the GB3US basic repeater logic" A. J. T. Whitaker, G3RKL. *Rad Com* Vol 58, No 1, January 1982, pp30-31.
- [3] *The CDP 1802CD Microprocessor Data Sheet—File Number 1023*. RCA Solid State Division, Somerville, NJ, 08876.

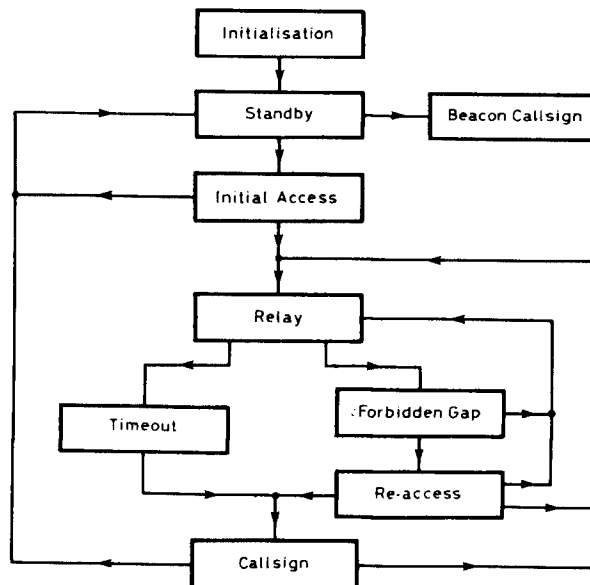


Fig 6. Software block diagram

The Motorola MC3361P

A new addition to the Motorola low power, narrow band FM-IF product line is the MC3361P. It is designed for use in FM dual conversion communications equipment, and is similar in design and application to the MC3357P. It contains an oscillator/mixer, limiting IF, quadrature detector, active filter, and mute function. The difference is that the MC3361P will work at supply voltages as low as 2.0-V dc, with the MC3357P operating only to 4.0-V dc. This is important in portable applications such as the cordless telephone handset, where it permits a battery complement reduction of two cells.

The MC3361P will operate without compromise on two carbon zinc AA (penlight) cells at near end-of-life condition. Also, it has a typical current drain of 4.2 mA. This is low with respect to the capabilities of this type of circuit, so battery life is long.

The performance of this circuit has not been compromised. Typical (-3 dB) limiting sensitivity is 2.0 uV rms, and recovered audio output voltage (at $V_{in} = 5$ mV rms) is 150 mV rms typical. The 100 and up price is \$1.61 and its availability from stock is 6 weeks from the factory or through authorized Motorola distributors.

The Linker 100

The Analogic Corporation of Danvers, Massachusetts, engages in the design and manufacture of high precision measurement, signal translation, and data manipulation equipment. The major business areas of the Company comprise four groups: Advanced Technology, Industrial Technology, Medical Technology, and Test and Measurements. These groups are involved in the dis-

ciplines of data conversion and array processing, industrial controls and calibration instruments, patient monitoring and diagnostic imaging, and automated testing.

The Industrial Technology Group is responsible for the Linker /TM/ 100, a newly-introduced industrial terminal/controller. Recently, networking capability was added to it so communications could be possible with a remote host computer or single intelligent peripherals from a central location via an RS422 or optional 20 mA compatible link, in addition to RS232C. The Linker 100 is user-programmable for performing PID, ramp/soak, cascade, ratio, or custom algorithms. Combining the features of compactness with intelligence, it is also ideal for field service/testing applications.

The Linker 100 is now supplied with a user-memory socket for expansion of the battery-protected RAM by 2k or 8k, or to add an additional 4, 8, 16, or 32k of UV PROM. A 2-line LCD display permits up to 40 ASCII characters per line.

The Linker 100 contains a central on-board computer (a Z8 processor with compact BASIC) that communicates with two internal intelligent peripherals (display and keyboard) and the equipment under control. Independent processors enhance programming flexibility and optimize computing speed. The Z8 is supported by external battery-protected 1.2k of user CMOS RAM and by an 8k utility PROM.

The Linker 100 is available from the Analogic Corporation at a price of \$400 in quantities of 100 units or \$595 for single orders. The 20-mA current loop is \$50 with delivery approximately 6 weeks.



QEX: The ARRL Experimenters' Exchange is published by the

American Radio Relay League
225 Main Street
Newington, CT 06111 USA
telephone 203-666-1541

Larry E. Price, W4RA
President

David Sumner, K1ZZ
General Manager

Paul L. Rinaldo, W4RI
Editor

David W. Borden, K8MMO (Data Communications)
Geoffrey H. Krauss, WA2GFP (VHF+ Technology)
Associate Editors

Maureen Thompson, KA1DYZ
Assistant Editor

Debbie Chapor
QEX Circulation Manager

The purposes of QEX are to:

- 1) provide a medium for the exchange of ideas and information between Amateur Radio experimenters,
- 2) document advanced technical work in the Amateur Radio field, and
- 3) support efforts to advance the state of the Amateur Radio art.

Subscriptions are available to ARRL members and non-members at the rates shown on the QEX Subscription Order Card inside this issue.

All correspondence concerning QEX should be addressed to the American Radio Relay League, 225 Main Street, Newington, CT USA 06111. Envelopes containing manuscripts and correspondence for publication in QEX should be marked: Editor, QEX. QEX subscription orders, changes of address, and reports of missing or damaged copies may be marked: QEX Circulation. Members are asked to include their membership control number or a label from their QST wrapper when applying.

Both theoretical and practical technical articles are welcomed. Manuscripts should be typed and double spaced. Please use the standard ARRL abbreviations found in the latest December issue of QST. Authors should supply their own artwork using black ink on white paper. When essential to the article, photographs may be included. Photos should be glossy, black-and-white positive prints of good definition and contrast, and should be the same size or larger than the size it will be when printed in QEX.

Any opinions expressed in QEX are those of the authors, not necessarily those of the editor or the League. While we attempt to ensure that all articles are technically valid, authors are expected to defend their own material. Products mentioned in QEX are included for your information; not advertising, nor is any endorsement implied. The information is believed to be correct, but readers are cautioned to verify availability of the product before sending money to the vendor. Material may be excerpted from QEX without prior permission provided that the original contributor is credited, and QEX is identified as the source.

QEX: The ARRL
Experimenters' Exchange
American Radio Relay League
225 Main Street
Newington, CT USA 06111

Nonprofit Organization
U.S. Postage
PAID
Hartford, Conn.
Permit No. 2929