

# CQ

JANUARY, 1949

## The Radio Amateurs' Journal

35¢



### THIS MONTH

- Applications of the Grid-Dip Oscillator
- Permanent Rotary — Putting One Up to Stay
- Beginners' Converter for 6, 10-11 Meters

Published by RADIO MAGAZINES, INC. Subscription \$3.00 a year

# PUT YOURSELF ON YOUR CARRIER

*Reproduce the Individuality of Your Voice...*

*Transmit Your Own Personality*

*...with an E-V Microphone*



#### **The CARDAX**

World's favorite premium crystal microphone. The only high level crystal cardioid with dual frequency response.



#### **The "630"**

Super dynamic. Long proved in service. Ideal frequency response. High output. Acoustalloy diaphragm.



#### **The "910"**

Rugged, handsome, crystal microphone. Outstanding performer, at low cost.

With an E-V microphone, you assure *accurate reproduction of your own speaking voice*. The shading and

warmth of your speech arrive at the other end of the QSO undistorted and undiminished.

*Your carrier is modulated with your exact speech . . . the individuality of your voice is clearly retained . . . your personality is on your carrier.*

WRITE FOR HELPFUL BULLETINS

*Authorized Distributors Everywhere*

**ELECTRO-VOICE, INC., BUCHANAN, MICH.**  
Export: 13 East 40th St., N. Y. 16, U.S.A. Cables: Arlab

NO FINER CHOICE THAN

## ***Electro-Voice***

E-V Pat. Pend. Licensed under Brush Patents



In efficient rigs, what can you expect to find at the other end of the mike-cord?



## A KEN-RAD 6SJ7 QUALITY-MADE TUBE!

One goes with the other — your microphone and Type 6SJ7. Hams are alike in endorsing this pentode for audio-amplifier work, and experience has shown them how much Ken-Rad quality means to 6SJ7 performance.

Because of further amplification, the audio signal passed on by your 6SJ7 should be free from spurious effects. Here Ken-Rad superior design does a job by providing a filament that cuts "hum" 'way down. Also, Ken-Rad painstaking manufacture plays its part by building a tube with the least microphonic response.

Result for you...improved transmission; a clean signal to cut through the QRM!

The benefits of Ken-Rad better design, better manufacture, go beyond the 6SJ7. Throughout your rig, wherever superior tube performance will aid, it's the smart thing to *assure* this by plugging in Ken-Rad tubes of the types required.

Ask your distributor or dealer to tell you more about the high standards met in building tubes marked "Ken-Rad." Then check this full-measure worth against Ken-Rad moderate prices. These fine tubes — in performance, in value — are real ham bargains!



**6SJ7**  
SHARP-CUT-OFF  
DETECTOR-AM-  
PLIFIER PENTODE

FOR KEN-RAD QUALITY,  
LOOK BEYOND THE DATA SHEET!



**KEN-RAD** *Radio Tubes*

PRODUCT OF GENERAL ELECTRIC COMPANY

Schenectady 5, New York

YOUR PREFERRED SOURCE FOR AMATEUR TUBES IS YOUR NEARBY KEN-RAD DISTRIBUTOR OR DEALER

# VERY FINEST OPERATION

*is their  
UNANIMOUS  
opinion!*

**W 5 CNK SAYS** . . . . "Since installing the BUD VFO, 3213 contacts made on ten meters. 37 zones, 48 states. Less than 2% incomplete contacts. NOT ONE SINGLE REPORT OF SIGNAL DRIFT."

**W 4 FNQ SAYS** . . . . "the BUD VFO is way ahead in stability . . . have been able to work consistently into Cuba, Bahamas and around the state . . . reports almost invariably T9X."

**W 4 JIH SAYS** . . . . "I have owned and used a BUD VFO-21 since they came on the market with very good results . . . I would like to take this opportunity to congratulate you on the design of BUD equipment. I use your products throughout my rig and like them for the simplicity of design . . . Tnx for building equipment for the hams."

These unsolicited testimonials make us mighty proud of our VFO-21. Why shouldn't it be just as fine for you as for these hams and the many others who have written to us? This is your chance to buy a fine variable frequency oscillator at a low cost. The BUD VFO-21 is available at \$52.50 net including a set of 40 meter coils. Coils for other bands available at \$4.00 per set.



NOW IS THE TIME FOR YOU TO SEE IT AT YOUR DISTRIBUTOR. NOW IS THE TIME FOR YOUR RIG TO GO VFO WITH BUD. THE VFO-21 PROVES ONCE AGAIN THAT THE BEST BUY IS BUD.



The mark *of perfection*

**BUD RADIO INC.**

2120 EAST 55th ST.  
CLEVELAND 3, OHIO

BUD RADIO, INC., 2120 E. 55th St., Cleveland 3, Oh'o. Send copy of NEW BUD CATALOG.

NAME.....

COMPANY.....

ADDRESS.....

CITY.....STATE.....

# CQ

# The Radio Amateurs' Journal

Published monthly by RADIO MAGAZINES, INC., at 342 Madison Ave., New York 17, N.Y. Telephone MUrray Hill 2-1346. Entered as Second Class Matter Oct. 10, 1947 at the Post Office, New York, N.Y. under the Act of March 3, 1879.

## EDITORIAL STAFF

JOHN H. POTTS, Editor

Managing Editor  
LAWRENCE LeKASHMAN, W2IOP

Assistant Editors  
OLIVER P. FERRELL  
LOUISA B. DRESSER, W2OOH

DX Editor  
HERBERT BECKER, W6QD

V. H. F.—U. H. F. Editor  
VINCENT G. DAWSON, WØZJB

Contributing Editors  
ROBERT C. CHEEK, W3LOE  
FRANK C. JONES, W6AJF  
R. LEIGH NORTON, W6CEM

Technical Draftsman  
FRANK Y. HAYAMI, W2TNE

## BUSINESS STAFF

J. H. POTTS, President  
S. R. COWAN, Publisher  
S. L. CAHN, Advertising Director  
H. N. REIZES, Advertising Manager  
D. SALTMAN, Production Manager  
E. E. NEWMAN, W2RPZ, Circulation Mgr.

Branch Office: Los Angeles—J. C. Galloway, 816 W. 5th St., Los Angeles 13, Calif. MUtual 8335.

Subscription Rates: in U.S.A., U.S. Possessions, Canada and Pan American Union—1 year \$3.00, 2 years \$5.00. Elsewhere \$4.00 per year. Single copies 35 cents. (Title Reg. U. S. Pat. Off.) printed in U.S.A. Copyright 1949 by Radio Magazines, Inc.

Foreign Subscription Representatives: Dale International Publications Ltd., 105 Bolsover St., London, W. 1, England; Radio Society of Great Britain, New Ruskin House, Little Russel St., London WC 1 England. Technical Book & Magazine Co., 297 Swanston St., Melbourne CI, Victoria, Australia.

Vol. 5

JANUARY, 1949

No. 1

## In This Issue


**COVER**—An improved model of the Dipper compactly built into one small case. The a-c power supply and the grid meter are self-contained. The line cord is connected by means of a plug so it may be removed for substitution of a battery cable if desired. The "probe" coils are each protected by an insulated sleeve and the range of the instrument is 2 to 300 mc. The coil with the alligator clips, shown next to the Dipper, is an inductance "standard" used for measuring capacitors of from 5  $\mu\mu\text{f}$  to .01  $\mu\text{f}$  as described in "Applications of the Grid-Dip Oscillator." Construction of this model will be described in February CQ. —Photo by Sacco-Newman.

|   |    |
|---|----|
| Letters .....   | 4  |
| Scratchi .....  | 8  |
| Zero Bias (Editorial).....  | 11 |
| A Permanent Rotary<br><i>Lawrence LeKashman, W2IOP</i> .....                        | 13 |
| Frequency Standard from C.F.I. Unit<br><i>A. W. Horst, W9CUX</i> .....              | 18 |
| Beginners' Converter for 6, 10 and 11 Meters<br><i>George H. Floyd, W2RYT</i> ..... | 22 |
| Land of Sunshine—and YLs<br><i>Louisa B. Dresser, W2OOH</i> .....                   | 28 |
| Applications of the Grid-Dip Oscillator<br><i>Wilfred M. Scherer, W2AEF</i> .....   | 30 |
| The Other Fellow's Statinn—W1BB.....  | 35 |
| Inside the Shack and Workshop.....  | 36 |
| Crystal Grinding Simplified<br><i>E. W. Johnson, W2UXA, ex-W9RAB</i> .....          | 37 |
| Monthly DX Predictions—January.....   | 41 |
| DX and Overseas News.....   | 42 |
| W.A.Z. Honor Roll.....  | 44 |
| V.H.F.-U.H.F. ....  | 46 |
| 50-mc Honor Roll.....   | 50 |
| The YL's Frequency.....   | 52 |
| Parts and Products.....   | 54 |
| Advertising Index.....  | 96 |

Designed for



Application

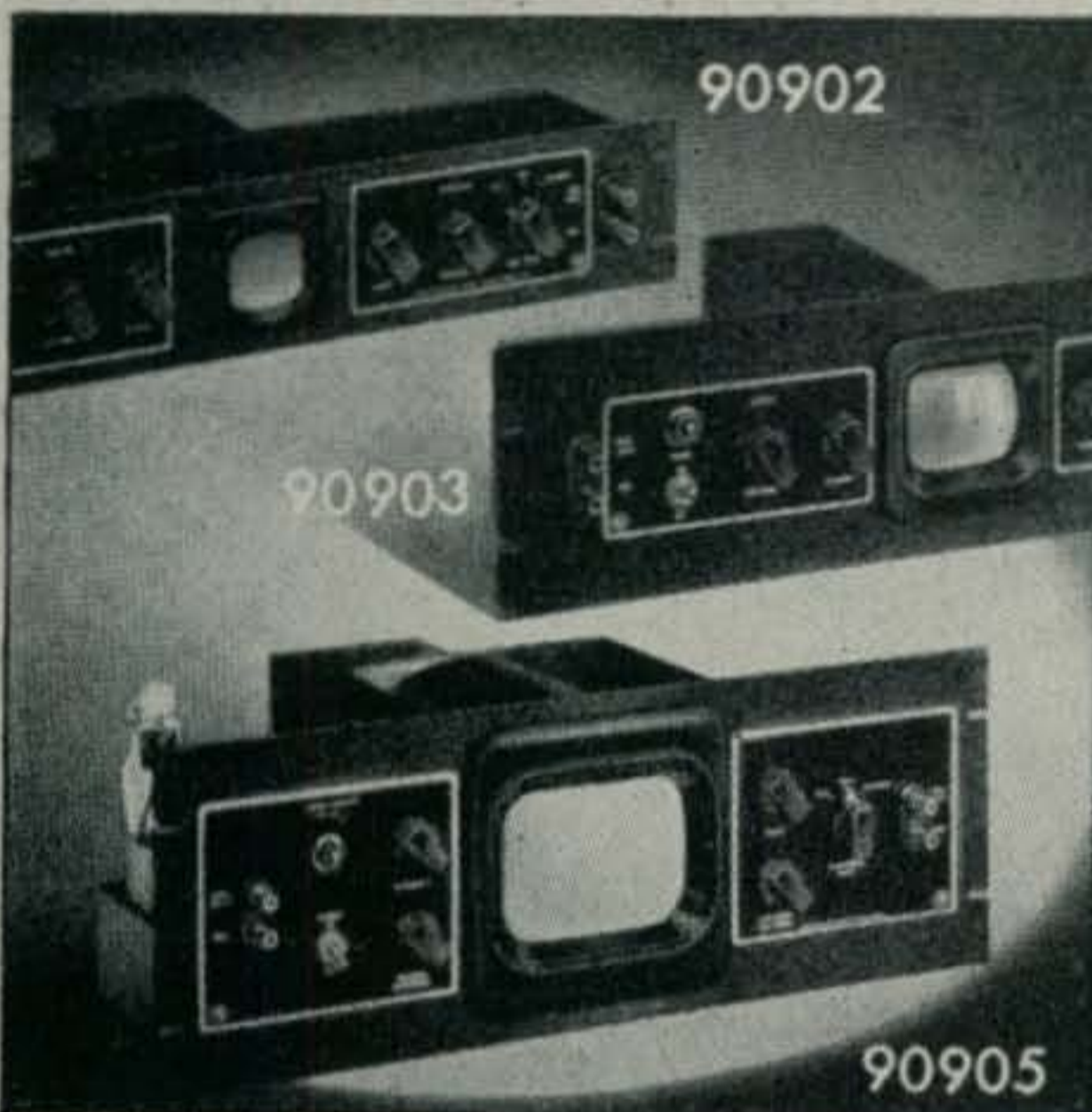

### 90900 Series Cathode Ray Oscilloscopes

The No. 90902, No. 90903 and No. 90905 Rack Panel Oscilloscopes, for two, three and five inch tubes, respectively, are inexpensive basic units comprising power supply, brilliancy and centering controls, safety features, magnetic shielding, switches, etc. As a transmitter monitor, no additional equipment or accessories are required. The well-known trapezoidal monitoring patterns are secured by feeding modulated carrier voltage from a pickup loop directly to vertical plates of the cathode ray tube and audio modulating voltage to horizontal plates. By the addition of such units as sweeps, pulse generators, amplifiers, servo sweeps, etc., all of which can be conveniently and neatly constructed on companion rack panels, the original basic 'scope unit may be expanded to serve any conceivable industrial or laboratory application.

**JAMES MILLEN  
MFG. CO., INC.**

MAIN OFFICE AND FACTORY  
**MALDEN  
MASSACHUSETTS**



## ★ ★ Letters ★ ★

### Amateur Radio for Public Service

Headquarters, 18th Fighter Wing,  
Clark Air Force Base, APO 74

Editor, *CQ*:

As your publication is designed for amateur radio operators about amateur radio operators, I am taking this occasion to inform you of the outstanding service rendered by four amateur stations to the 18th Fighter Wing at Clark Air Force Base, Luzon, Philippine Islands.

Recently when four fighter aircraft were missing during bad weather on a navigational training flight to Formosa, these short-wave stations responded to the emergency by remaining on the job almost constantly for a period of four days to relay vitally needed local weather information to assist an extensive aerial search culminating in a difficult ground rescue operation.

The stations which served so unselfishly were: KA1AI, a 1,000-watt station operated at Clark Air Force Base by M/Sgt Stanley Gier of the Special Services Section for the benefit of military personnel; KA1CD, a private set owned by Major Hugh D. Avary, Chief of Prosthetics in the Dental Clinic at Clark Air Force Base; C3EA, operated near Taikao, Formosa, by Sgt/1st Cl. Al Hattlestad of the Army Advisory Group with Headquarters at Nanking, China; and J2NZI, operated by Captain Melvin R. Jones in Japan.

In view of the fact that there was no other source of weather information available in the vicinity of Formosa, Sgt/1st Cl. Hattlestad observed and reported weather conditions every hour on the hour in addition to reporting the progress of the search mission. Having no relief operator, he worked 18 hour stretches, sleeping three or four hours and returning to the air for another 18 hours throughout the emergency.

M/Sgt. Gier at KA1AI at Clark Air Force Base stayed by his radio board to receive messages from 1800 to 0800 and then Major Avary took over reception during the daytime hours.

Atmospheric conditions precluded direct contact with the Philippines, so that it was necessary to set up a system of relay through station J2NZI in Japan. Again there was no relief operator, and Capt. Jones stood by almost constantly for three days and nights to relay messages from Formosa to the Philippines.

I am sincerely appreciative of the cooperation my organization received from these men, and I wish to commend these amateur radio operators for their unselfish service in time of emergency.

Robert C. Oliver  
Brigadier General, USAF,  
Commanding


### Single Sideband Forever

Rt. 1, Box 231A, San Mateo, Calif.

Editor, *CQ*:

In the November issue of *CQ*, W1BGJ objects to the efforts being made to bring the advantages of single-sideband transmission to the attention of amateurs. Similar objections have accompanied every attempt to improve the art, but always without success. The famous old cry, "Spark forever—THWCW" has its counterpart as each new development comes along. (*QSY to page 6*)

**CQ**

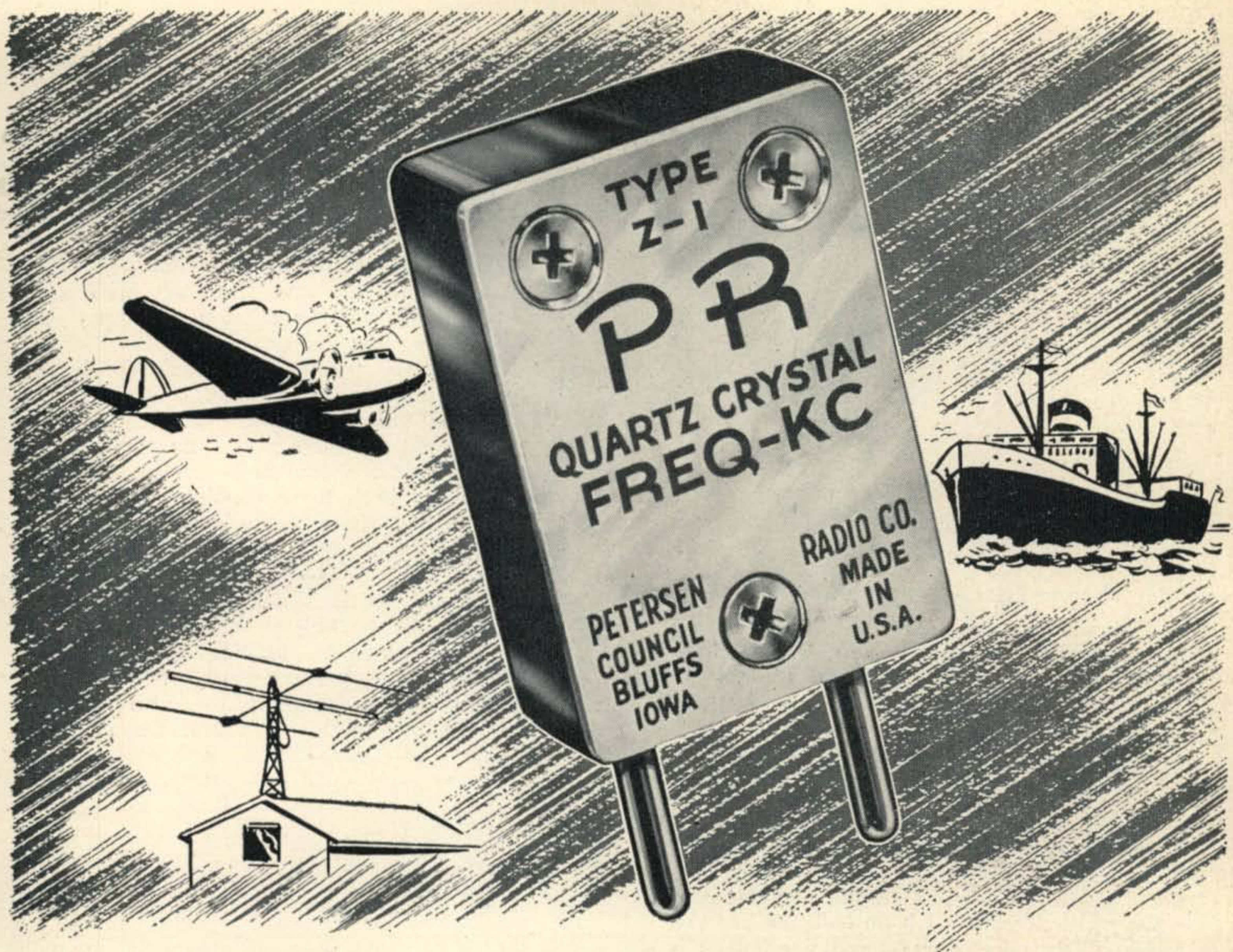

## LAND, SEA and AIR

PRs stand the gaff! Wherever you go you find these fine precision crystals doing their jobs with honor . . . meriting the praise of engineers, operators and technicians. Yes — you can depend on PR for perfect frequency control . . . at low cost . . . for all amateur, commercial and industrial services.

10 METERS, Type Z-5, \$5.00 • 20 METERS, Type Z-3, \$3.75 • 40 & 80 METERS, Type Z-2, \$2.75

# PR




**PRECISION  
CRYSTALS**  
USE "PR"  
and KNOW where You Are!

**PETERSEN RADIO COMPANY, INC., 2800 W. BROADWAY, COUNCIL BLUFFS, IOWA**

# Heavier Windings

ON NEW

## JOHNSON HAM INDUCTORS

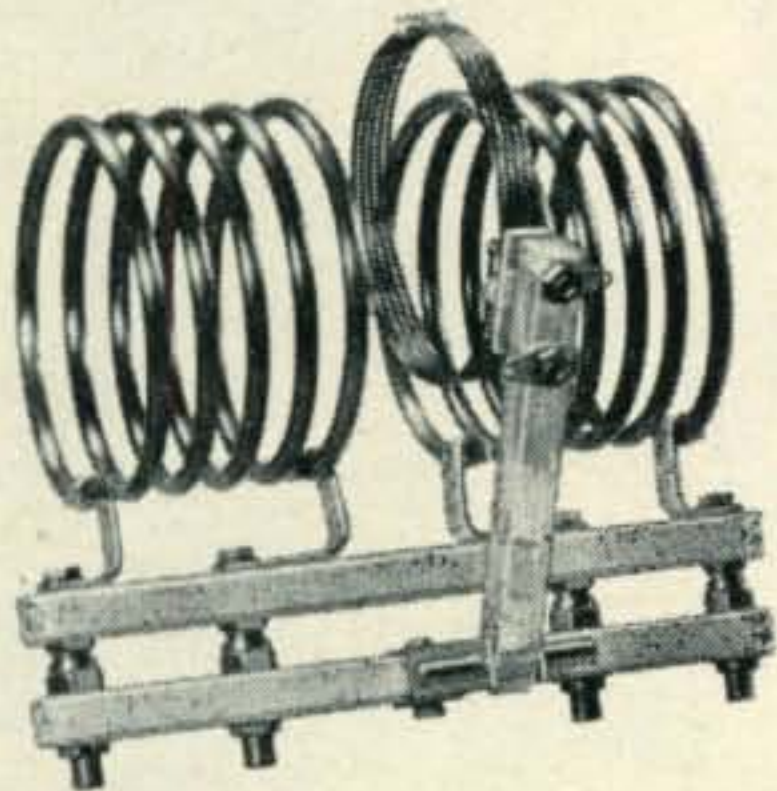

### Lower Loss — High Efficiency

If it's efficiency you want, you'll insist on the new JOHNSON Ham Inductors. Coil windings are a wire size **larger** than on most available inductors — resulting in less heating, lower loss and consequently higher efficiency.

For instance, the 1000 watt twenty meter inductor, pictured above, is wound with .250" diameter copper tubing, not wire. It is intended to match low voltage high current tubes — efficiently! Extra heavy size steatite plug and jack bars insulated by clear polystyrene — not conventional plastic — also result in additional efficiency.

Only with JOHNSON Ham Inductors can you match coil to tube. Another exclusive feature is the matching of link to line with the new JOHNSON "plug-in" swinging link assembly. These outstanding inductors are also available in semi-fixed models.

Remember, too, that the new JOHNSON Inductors and Plug-In Link Assemblies fit all conventional inductor assemblies.

### LOADED WITH FACTS



The new JOHNSON "Air Wound Ham Inductor Catalog" contains information and tables which will enable you to select the correct inductor, link or links for your individual application. The booklet is a virtual storehouse of information on Q considerations, tube-inductor matching,

link-line impedance matching, antenna coupling, etc. Get it at your dealer or write JOHNSON for a copy of this important reference manual today. It's yours for the asking.



# JOHNSON

*a famous name in Radio*

E. F. JOHNSON CO.

WASECA, MINN.

Because WIBGJ's objections are based on emotional grounds rather than on facts, they are fairly easily answered. He asks several questions:

Q: Is our present investment to be thrown in the waste can?

A: No, only the high-power modulator. File it alongside the rotary gap and the chemical rectifier. The portion of the power bill saved by not using the modulator and by not running the final amplifier wide open during every transmission will pay for the SS equipment.

Q: If SS is so potent, why don't the broadcast, short-wave phone, etc., stations use it?

A: Services that are being squeezed for kilocycles or must have maximum performance from their equipment *do* use it. Amateur radio has both these problems.

Q: Don't hams have enough trouble keeping ahead of the F.C.C., general public, etc. already?

A: Judging from the sound of the phone bands, the F.C.C. is well in the lead. We can close the gap by making more effective use of the space we have. SS does not enter into our relationships with the general public, except where it may help to reduce BCI complaints.

The letter in question closes with some sweeping statements to the effect that hams do not have the technical knowledge or money to get, among other things, a *receiver* that will work on SS. If I may be pardoned, I would like to use my own log book to shed some light on that subject.

My station has been operated spasmodically with SS in the 3.9 and 14.2-mc bands for the past six months. The peak power has varied between 200 watts and 1 kilowatt. During this period, 77 contacts have been made while using SS transmission. In all except two or three cases, contact was established "cold" without the aid of AM, FM or c.w. Twenty contacts were on 3.9 mc., the remainder on 14.2 mc. Four of the stations contacted were unable to copy the SS signal. Three more stations were only partially successful in copying the signal. One of the operators who reported "no copy" had removed the b.f.o. tube from his receiver before the war and could not locate it. The remaining 70 stations reported no difficulty in copying the SS signal after the first exchange of tuning instruction, where that was found necessary. There has been, therefore, a 91 per cent return in successful QSOs. *In no case were any of the stations contacted using any special receiving gadgets.*

An attempt has been made to keep a record of the types of receivers on which successful reception has been reported. Although the record is far from complete, it shows that good results have been obtained with the BC-312, BC-342, HRO, HQ-129, HQ-120, RME-69, RME-45, 75A, Super Pro, and NC-101X. It appears that, in the proper hands, almost any receiver will do a creditable job on an SS signal.

From the transmitting end, the results have been most satisfying. The most consistent report received has been on the apparent lack of QRM from AM and NBFM stations once the SS sig-


*(Continued on page 91)*





*I Will Show You How to*  
**LEARN RADIO**  
 Servicing or Communications  
*by Practicing in Spare Time*

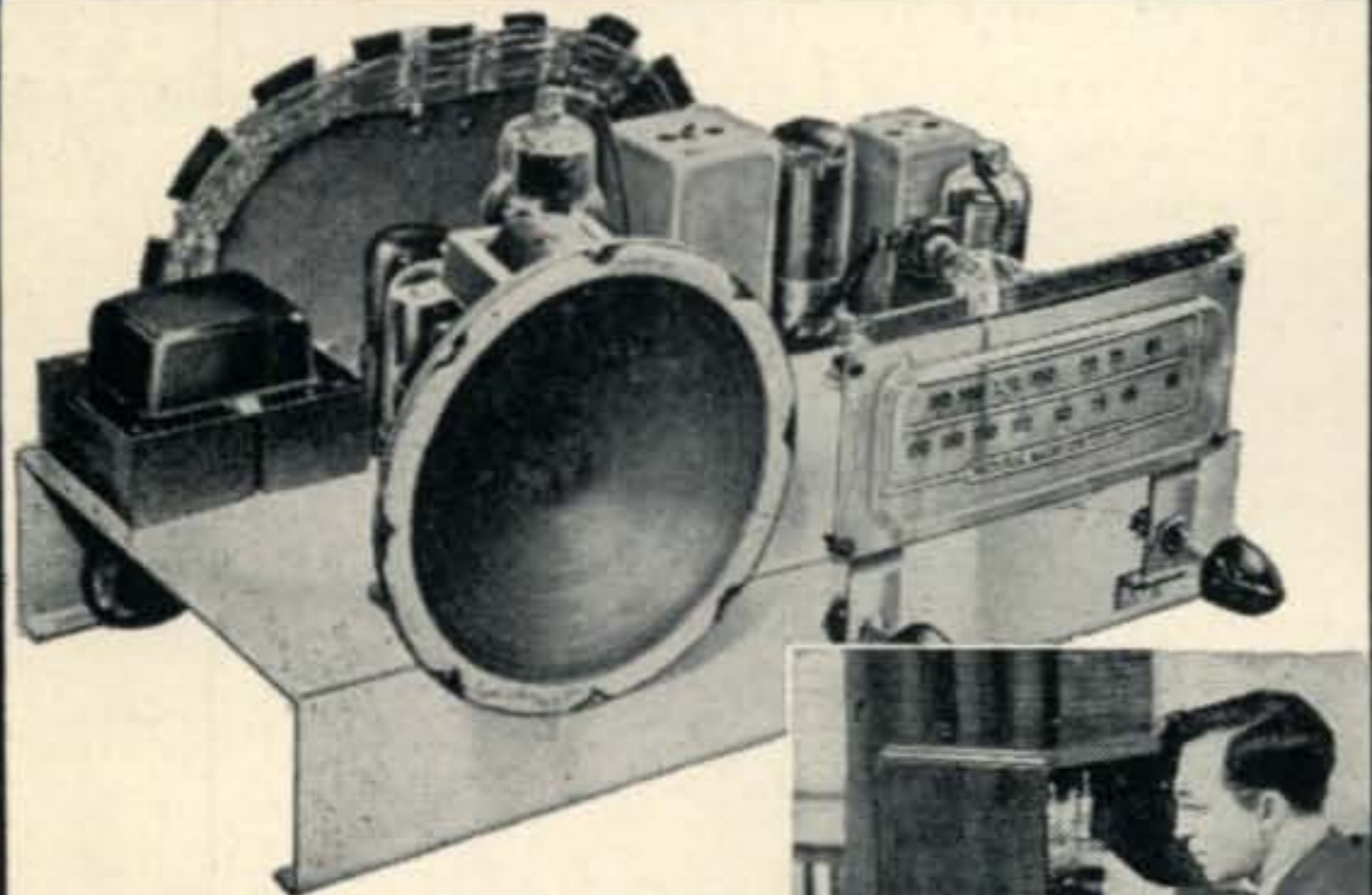*I Send You  
 Many Kits of  
 Radio Parts*



**YOU PRACTICE RADIO  
 SERVICING**

You build this modern Radio as part of my Servicing Course. I send you the speaker, tubes, chassis, transformer, loop antenna, **EVERYTHING** you need to build this modern Radio Receiver. Use it to make many tests, get practical experience.



**YOU PRACTICE RADIO  
 COMMUNICATIONS**

I send you parts to build this Transmitter as part of my new Communications Course. Conduct actual procedure demanded of Broadcast Station Operators, practice interesting experiments, learn how to put a transmitter on the air.



**NEW**


**YOU BUILD THIS TESTER**



as part of my Servicing Course. It soon helps you **EARN EXTRA MONEY** fixing neighbors' Radios in spare time.

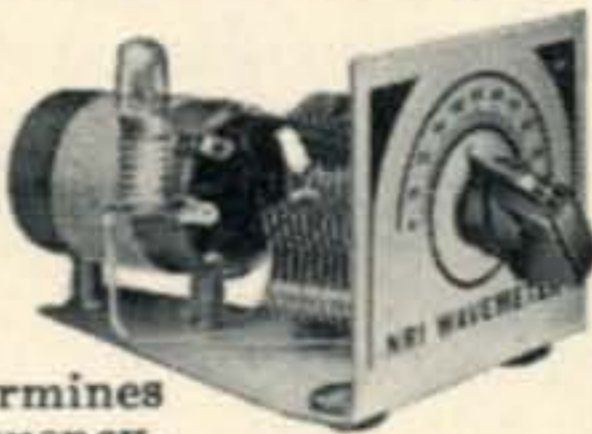**BUILD THIS WAVEMETER**

as part of my **NEW** Communications Course. Use it with Oscillator you also build that furnishes basic power to transmitter and determines transmitter frequency.



**I TRAINED THESE MEN**

**Good Job In Radio Station**  
 "Am Chief Engineer of Radio Station **WORD** in charge of 4 men. Owe all I know about Radio to **NRI**."—**CLYDE J. BURDETTE**, Spartanburg, South Carolina.

**Has Own Radio Business**  
 "Now have two Radio shops servicing about 200 sets a month. Have largest service establishment in Southeastern Missouri."—**ARLEY STUDYVIN**, DeSoto, Mo.

**KNOW RADIO · Win Success**  
**I Will Train You at Home · SAMPLE LESSON FREE**

Want a good-pay job in the fast-growing Radio and Television Industries, or your own money-making Radio-Television shop? I've trained hundreds of men **WITH NO PREVIOUS TRAINING** to be Radio technicians. I can do the same for you. Or now you can enroll in my **NEW** practical course in Radio-Television **COMMUNICATIONS**—learn to be a Broadcasting and Communications technician. You get practical Radio experience with **MANY KITS OF PARTS** I send you in my train-at-home method. All equipment yours to keep.

**Make Extra Money In Spare Time**

As part of my Radio Servicing Course, I send **EXTRA MONEY** booklets starting the day you enroll. Make extra money fixing Radios in spare time while training. Then start your own Radio sales and service shop

or get a good-pay job in Government, Police, Aviation or Marine Radio, Broadcasting, Public Address work, etc. Or think of amazing Television opportunities. Already manufacturers are producing over 100,000 sets a month. New stations going on the air everywhere! Television is America's fastest-growing industry and men who know it will be in demand.

**Get Actual Lesson And Book Free**

My **DOUBLE FREE OFFER** entitles you to actual **SAMPLE LESSON** and my 64-page book, "**HOW TO BE A SUCCESS IN RADIO-TELEVISION-ELECTRONICS**," both **FREE**. Mail coupon now. See how quickly, easily you can start. **J. E. SMITH**, President, Dept. **9AF7**, National Radio Institute, Pioneer Home Study Radio School, Washington 9, D. C.

**VETERANS**

**GET THIS TRAINING  
 UNDER G. I. BILL**

**Good for Both - FREE**

**MR. J. E. SMITH**, Pres., Dept. **9AF7**  
 National Radio Institute, Washington 9, D. C.  
 Mail me **FREE** Lesson and 64-page book.  
 (No salesman will call. Please write plainly.)

NAME..... AGE.....

ADDRESS.....

CITY..... ZONE..... STATE.....


Check If Veteran

APPROVED FOR TRAINING UNDER G. I. BILL



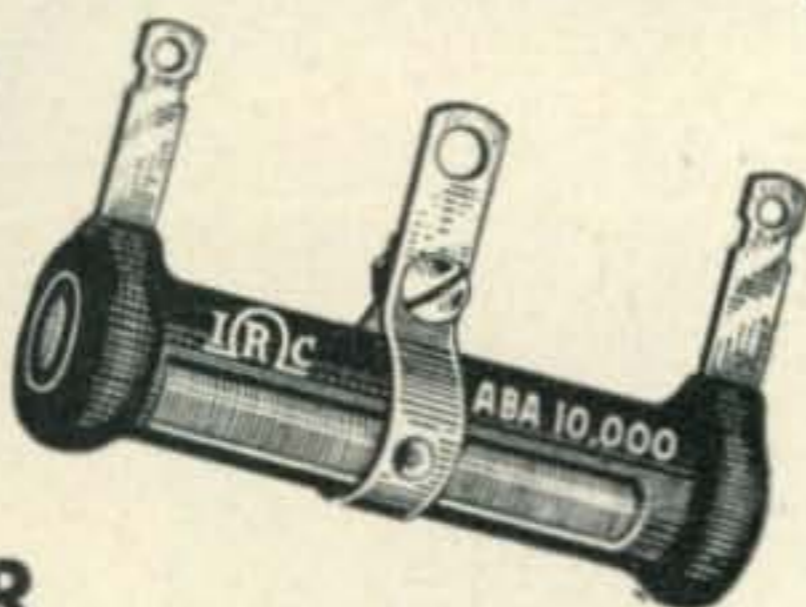**MY COURSE INCLUDES TELEVISION**

**CHOOSE THE RESISTORS  
SPECIFIED FOR MOST  
CRITICAL ELECTRONIC  
CIRCUITS**



**IRC POWER  
WIRE WOUND RESISTORS**

for exacting, heavy-duty applications. Uniformly wound with highest grade alloy wire on tough, ceramic tubes. Coated with climate-proof cement, specially developed to provide rapid heat dissipation and maximum moisture protection. Rugged terminals are securely attached, and heavily tin dipped for easy soldering. Available in fixed or adjustable types in full range of sizes, ratings and terminals—10 to 200 watts.



**IRC PRECISION  
WIRE WOUND  
RESISTORS**

for dependable accuracy (standard 1%). Winding forms of non-hygroscopic ceramic with high insulation qualities, mechanical strength and low coefficient of expansion. Non-inductive winding impregnated with special varnish which improves insulation—eliminates breakdowns and shorted turns. Fully protected against high humidity. Low noise level. Minimum temperature coefficient of .002% per degree C. Available in a wide selection of ranges and types.

When you order heavy-duty or close tolerance resistors, ask for IRC Power Wire Wounds or IRC Precisions—the same accurately manufactured resistors specified by electronic engineers.



**INTERNATIONAL  
RESISTANCE CO.**

401 N. Broad St., Phila. 8, Pa.

IN CANADA: INTERNATIONAL RESISTANCE COMPANY LTD.,  
TORONTO, LICENSEE



Feenix, Ariz.  
AIR MALE SPESHUL

Deer Hon. Ed:

Golly oh gollies I are hoping that I are in times to catching next editions of your magazines before it are being pressed so Scratchi are ables to getting an ad in your Classifried Ads colyum. So if you are not too busy filling out QSL cards please rushing following ad right down to printer. Here are copy:

LOST—ONE SIDEBAND of 20 meter single-sideband transmitter. When last seen sideband are in vicinity of 14,220 kc. Sideband badly needed on acct. transmitter now are having no carrier and no sidebands. Anybuddys finding same please contacting post hasty Scratchi, Box 73, CQ Magazines.

Scratchi are not knowing what are happening, but I are now having 1/c transmitter that are not being much good. Inasmuch as SSB transmitter are being without much carrier, and only having one sideband, when one sideband are missing Scratchi are not having much left. I can be talking like sixty into mike and I are getting nothnig but weak tonsils.

This are all comings about when my XYL-to-be are telling me to get modern rigs and toss out my old stuff. Lil are interested in using rig, and I are figuring Scratchi are being smart if are following her advice. I are reading all articles on single-sideband and are deciding it are for me. However, it not being duck soupy to understand same, Scratchi are in quandry.

One day are moving frequency of old transmitter out of dx end of band and coming up in legal part of band. I are heering some feller back east who are using SSB, so I are getting in contact with him and asking all kinds questions. He are being smart cookies, I guess, as he are not answering my foolish questions, but he are giving me complete talking-to on single-sideband. I are even finding that I can receive his SSB signals on my regular receiver.

Gollies gee, Hon. Ed., he ar able to changing from single-sideband to AM to narrow-band FM in nothing flat, like gal in French bathing suit disrobing. This are really convincing me, so I are asking how I can building same rig, and so this feller are sending me complete circuit diagram.

After a cupple of weeks of feverish activity, and with help of Brother Itchi, I are getting rig all finished and tuned up. My oscillyscope that I had bought on surplus market are proving reel peachy as I can seeing the various waveforms

(Continued on page 90)

30 kv tested dropping resistor completely enclosed in handle.

2-inch diameter removable Bakelite safety flange.

1 3/4-inch long Polystyrene nose.

One inch nickel-plated brass contact pin.

4 1/4-inch long Bakelite grip has only .02  $\mu$ a leakage at 10,000 vdc.

Husky wear resistant 48-inch flexible lead, 22 kv breakdown.

**ONLY \$9.95**

**NOW! USE THIS DC VOLTAGE MULTIPLIER WITH YOUR SYLVANIA POLYMER AND YOU HAVE A KILOVOLTMETER!**

Now you can extend the dc range of your Sylvania Poly (Multi-Purpose) Meter to 10,000 volts! To convert your Polymer to this high voltage class, merely replace your present low voltage probe with the new Sylvania DC Voltage Multiplier, and Polymer ranges will be multiplied by 10!

The 1,000 vdc range setting will read 10,000 vdc full scale. The 300 vdc range setting will read 3,000 vdc full scale.

This accessory extends your Polymer applications to: Television Circuits, Transmitter Plate Voltages, Experimental Power Supplies, Industrial Electronic Equipment, Electronic Photographic Equipment, and other high dc voltage applications. Economically priced at only \$9.95! See your Sylvania dealer today. Sylvania Electric Products Inc., Emporium, Pa.

**ONLY \$8.95**

(dc voltage multiplier extra.)



**Poly (Multi-Purpose) Meter**

This Sylvania instrument (Model 134Z), provides in one unit the means of making a multitude of electrical measurements and tests. Electrical values measured include audio, ac and rf voltages (up to 300 mc); dc voltages from 0.1 to 1,000; direct current from 0.1 milliamperes to 10 amperes; resistance from 1/2 ohm to 1,000 megohms.


**SYLVANIA ELECTRIC**

ELECTRONIC DEVICES; RADIO TUBES; CATHODE RAY TUBES; FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES; LIGHT BULBS; PHOTOLAMPS

Follow the Leaders to

**Eimac**  
TUBES  
The Power for R-F


# ESSENTIAL IN MODERN CIRCUITRY

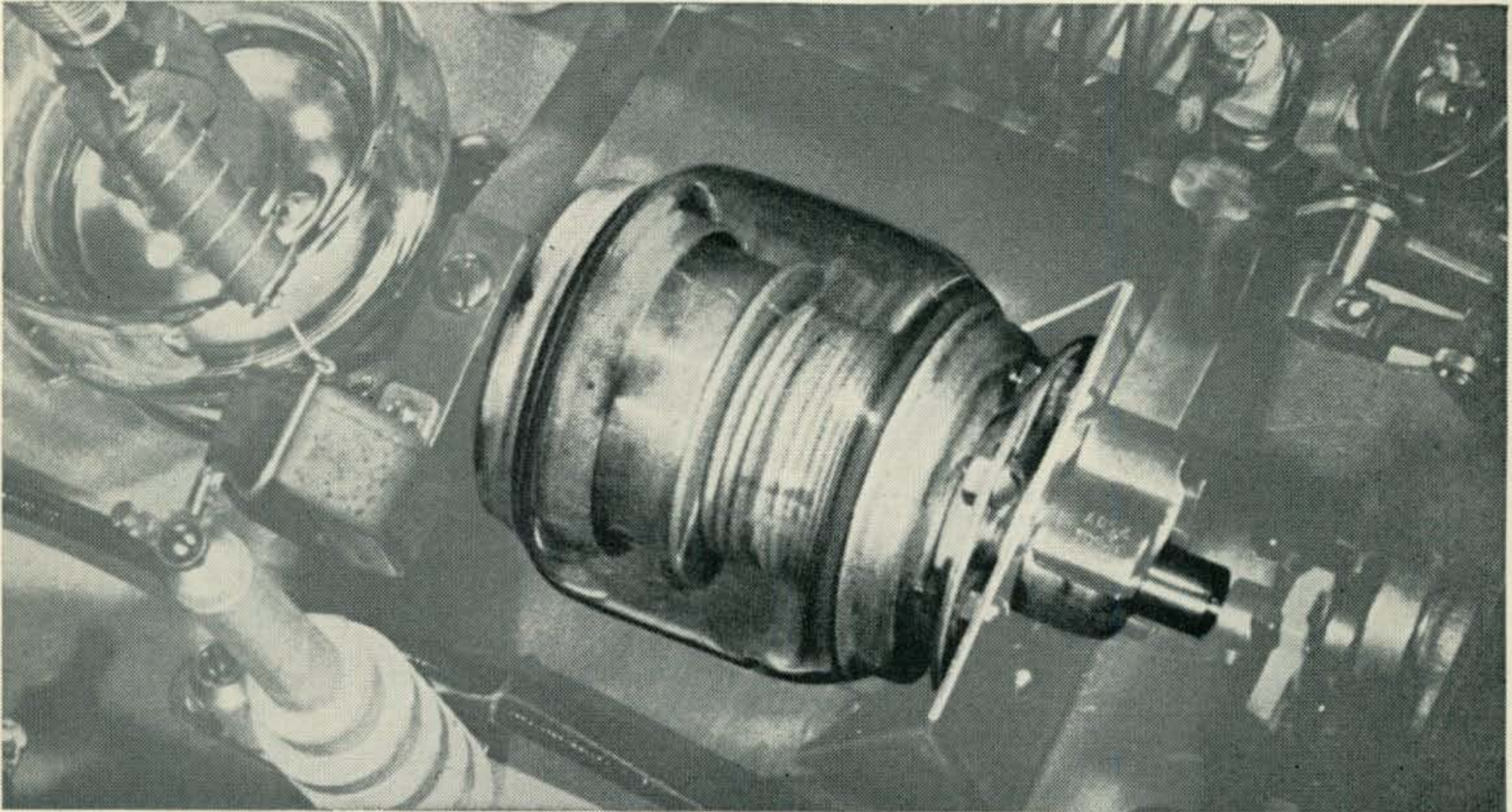

EIMAC VVC 60-20 in an ultra-compact 4-250A 1 KW Amplifier.


Consider the advantages . . . and Eimac Variable Vacuum Capacitors become the essential component in modern circuitry.

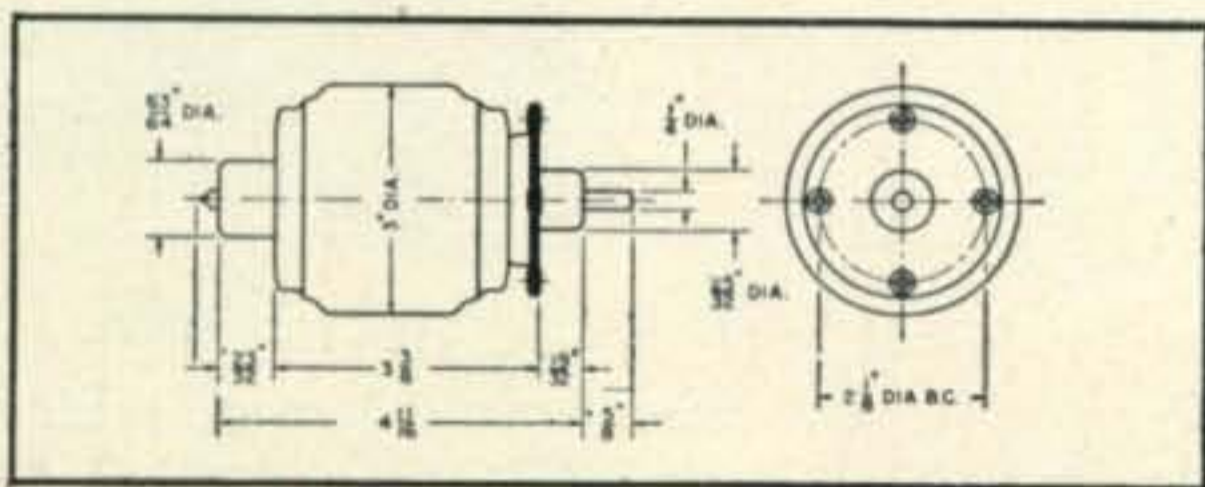- Extremely compact size reduces equipment bulk. Type VVC 60-20 is less than one-sixth the size of air-dielectric capacitors with similar ratings.



- Structural rigidity eliminates electro-mechanical vibration.
- Low-torque tuning mechanism.
- Unaffected by dusty or humid atmospheres. Ideal for industrial application.

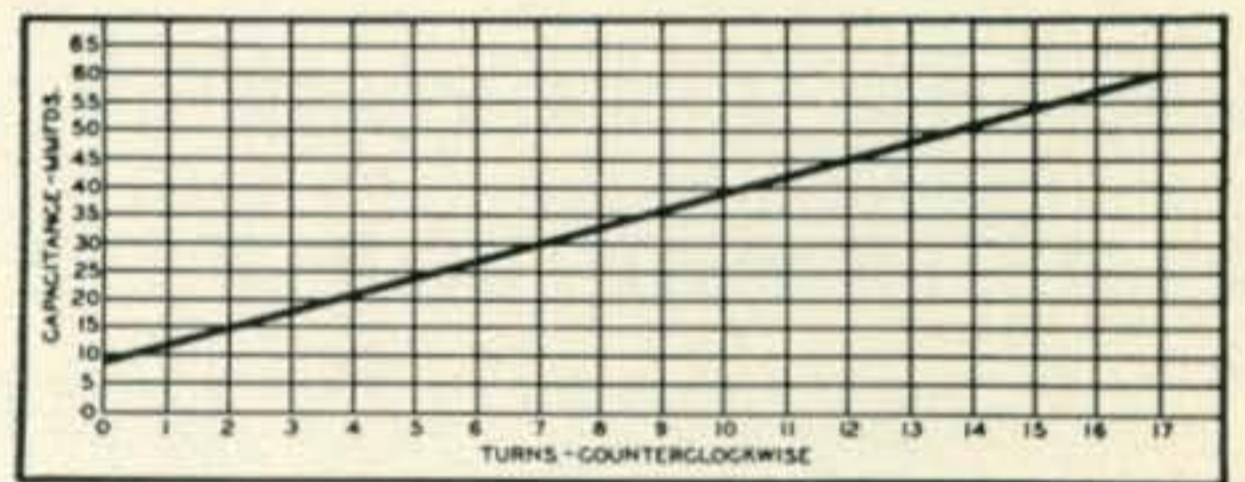- Capacitance variation is linear with shaft rotation.



- Low temperature coefficient. Negligible change in capacitance due to temperature variance. (.004 mmfd. per degree cent.)

Eimac variable vacuum capacitors are immediately available. In addition to the type VVC 60-20 illustrated here, there are types VVC2 60-20 and VVC4 60-20.

#### GENERAL CHARACTERISTICS

|              | Capacity    | R-F Peak Voltage | Maximum RMS Current |
|--------------|-------------|------------------|---------------------|
| VVC 60-20    | 10-60 mmf.  | 20-KV            | 40 amp.             |
| VVC2-60-20   |             |                  |                     |
| Parallel     | 20-120 mmf. | 20-KV            | 80 amp.             |
| Split-stator | 5-30 mmf.   | 40-KV            | 40 amp.             |
| VVC4-60-20   |             |                  |                     |
| Parallel     | 40-240 mmf. | 20-KV            | 160 amp.            |
| Split-stator | 10-60 mmf.  | 40-KV            | 80 amp.             |

## EITEL - McCULLOUGH, INC.

206 San Mateo Ave., San Bruno, California

Export Agents: Frazar & Hansen, 301 Clay St., San Francisco, California

# ZERO BIAS

E D I T O R I A L

## **CQ's World-Wide DX Contest**

**W**E DON'T LIKE to blow our own horn any more than most people like to listen to braggarts. But with pardonable pride we'd like to tell you just a little about CQ's first World-Wide DX Contest. The DX fans will get more details in the DX column. But we want the non-DXers to also know about this event.

Six months ago, after deliberation consuming many hours, CQ's DX Committee (W6QD, W6ENV, W6SA and W6DI) decided the time was ripe to hold a truly international DX competition. Meetings were held with prominent DX men throughout the country, and outstanding DXers abroad were consulted. Rules and regulations were hashed over for several months. In order to devise a plan that would be fair to foreign operators it would naturally work a hardship on Ws, for the simple reason that the sole object of other big American-sponsored contests has been to see which DX station could *contact the most Americans*. In a demonstration of cooperation and goodwill (particularly rare in this day where self-interest seems to be the motivating force behind most decisions) rules were agreed upon which favored no one country—and the result of this international fairness placed a definite handicap on Americans. No longer would Ws be the object of all the attention from DX in a DX contest. The strategy was to lure out more and better DX—to give everyone a good time.

From the time of the first announcement in August CQ, through the wide foreign circulation of CQ, through the cooperation of most of the radio societies of the world, and through the cooperation of amateurs who passed on the rules and regulations to isolated DX stations, the word was spread. Propagation conditions for the phone week-end were only fair, for the c-w week-end they were superb. To say the contest was a success is putting it mildly. It was worthy of all the adjectives Hollywood reserves for its multi-million-dollar spectacles. The logs have been pouring in for several weeks now, logs from Somalia, Tristan da Cunha, Gambia, Macau, Formosa, Siberia—from pole to pole (actually, not just literally, for competing were VP8AM in Antarctica and VE8s sitting at the other end of the world).

We're just five years old with this issue of CQ, but if entries from over 100 countries in our first contest is any indication, CQ gets around.

## **How Not to Lick TVI**

Repeatedly the editorials in CQ have discussed TVI in all its phases. Just two months ago, on a very optimistic note, we reported some of the excellent progress that has been made in not only reducing TVI, but in improving public relations. Our own experience had indicated this trend, and we passed it on to our readers. We may be cor-

rect in talking for one small New York community—but the violent reaction of readers everywhere else underscores the deterioration of the general situation, not the improvement.

What is happening? We can tell you in a very few words. The hams are quitting, giving up, closing down—and without a fight! We don't mean "fight" neighbors. We never implied that course of action was wise. When we say "fight" we mean make every effort with the tools on hand to lick the problem technically. Fight if necessary any unscrupulous servicemen, any trouble maker in the community who points his finger at the amateur with complete disregard for the truth, even the occasional amateur who says the "h" with everyone except himself. Why the plain unvarnished truth is that most amateurs are going off the air in TV serviced communities without making even a serious attempt to apply the most basic remedies to their transmitters. And many of them have taken this defeatist view because of the discouraging results a few of their fellow hams may have had, or the completely intolerant, uncompromising attitude of most neighbors.

Let's stop and take stock for a moment. At a recent hamfest we attended where there were close to 700 New York and New Jersey amateurs present, an A.R.R.L. official made an appeal to the boys to stay on the air. Deserting the bands in droves, he pointed out, was the worst possible approach to TVI—it places the ham in an even weaker position than he is already. He spoke well and made his point extremely strong. Yet when he finished the MC got up and, with a condescending nod to this official, said it's all very well to talk about not going off the air, but . . .

But what? Here is a typical letter from an amateur in Detroit.

*24915 Fairmont, Dearborn, Mich.*

*Editor, CQ:*

*A year ago when we read of TVI troubles of the boys on the Eastern Seaboard, our reactions were that it was too bad—but remote. As you know, the expansion of television has been rapid. Predictions within the industry are that by 1952 they will have better than 50 per cent coverage of the country.*

*Television in this area has resulted in a marked reduction of amateur radio activity. Although the average amateur already has quite a large investment in equipment, he has always been eager to yield to the influence of magazines and advertisers for newer and better equipment. But now he is reluctant to add to his investment until assured of his position with reference to TV.*

*Mention of your new TVI elimination handbook was news. I hope it provides commercial corrective approaches and does not rely entirely*  
(Continued on page 86)



Left to right: Collins 75A-1 receiver, 310A-3 exciter with speaker above, 30K-1 transmitter

## ***Sitting Pretty***

● The owner of a group like this has the best performing half-kilowatt outfit money can buy.

Operating in the 80, 40, 20, 15, 11 or 10 meter bands, he can run 500 watts of stable c-w, or 375 watts of clean, intelligible phone into his PA amplifier. He has bandswitching in all transmitting circuits except the antenna tuning network, where one plug-in coil covers 80 and 40 meters, and another covers 20, 15, 11 and 10. He has very accurate Collins PTO control right on his desk, in the 310A-3 exciter.


It is often said that you can spot a Collins 30K-1 transmitter on phone as soon

as you hear it, and that it seems to have more sock than its rated power. One reason is well engineered speech clipping, which permits running the audio gain at high level, with 100% modulation. Another reason is found in good audio design and fine components, providing remarkable clarity of voice transmission.

Add the sensitivity, stability and tuning accuracy of the 75A-1 receiver, and you have the ideal combination, whether for DX or maintaining schedules.

Get in touch with your Collins dealer. If you do not know him, we will be glad to give you his name and address.

FOR SUCCESS IN AMATEUR RADIO, IT'S . . .

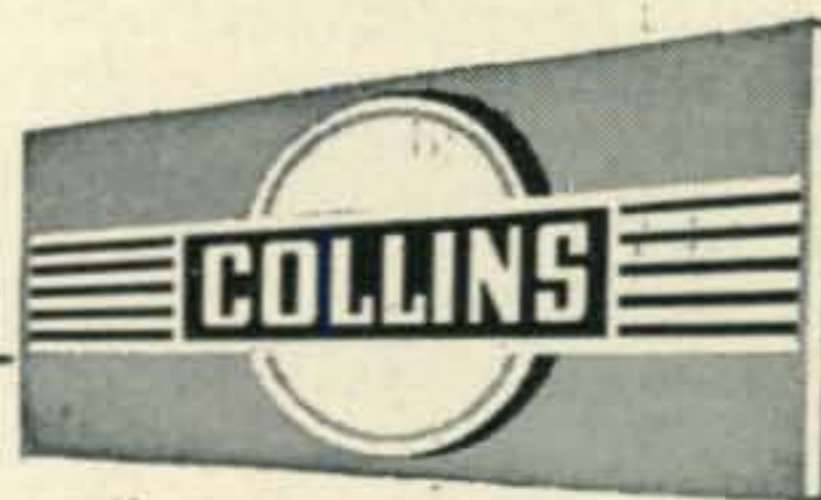

**COLLINS RADIO COMPANY, Cedar Rapids, Iowa**


11 West 42nd Street, New York 18, New York

458 South Spring Street, Los Angeles 13, California
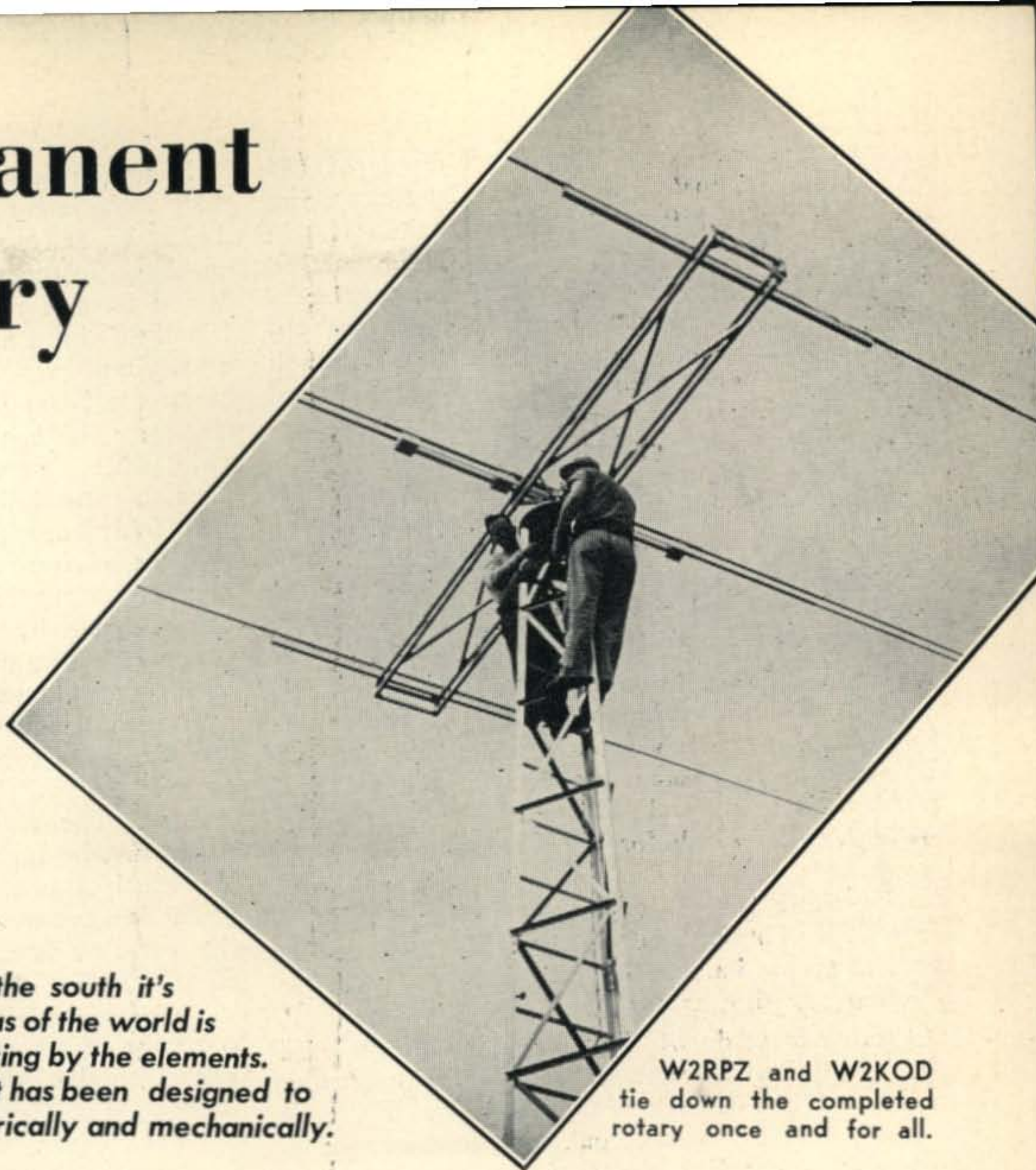
# A Permanent Rotary

LAWRENCE LeKASHMAN  
W2IOP\*

*In the north it's snow and ice, in the south it's frequent high winds. In few areas of the world is any antenna immune from buffeting by the elements. Here is a compact rotary that has been designed to give top-notch efficiency electrically and mechanically.*



W2RPZ and W2KOD tie down the completed rotary once and for all.

**S**OMETHING NEW in rotaries? Not at all—it's a very ordinary three-element close-spaced 14-mc rotary. But this beam is worth a story because it shows how simple the construction and adjustment of a parasitic array can be.

Like many amateurs, because of the tremendous amount of antenna literature available, the author was confused by the myriad ideas presented. Every system had something in its favor. To decide which design should be used we prepared a balance sheet, not unlike one you might use in working on a family budget. The items to be covered were not many—minimum over-all size (both spacing and element length), maximum physical strength, and great physical durability.

Minimum physical size dictated a close-spaced array. Initial reflections ran the gamut from our tiny 144-mc vertical dipole to W2GWE's 4-element 14-mc rotary, and then to some of the commercial arrays we had inspected at Rocky Point. Sober thought, rough measurements of our lot, and a careful inspection determined that the over-all boom length should be held to approximately 14 feet if we were to have an installation that was not out of proportion to its surroundings.

Because some of our friends swear by arrays with all elements driven, and others are sold on parasitic beams, we next turned our attention to the pros and cons of the two arrangements. A

careful perusal of the amateur literature disclosed contradictory and inconclusive information although much of it was undeniably excellent. Discussions with the proponents of each type only served to muddle the question even more. We talked to our experts and such phrases as "mutual and self-impedance," "electric intensity at a point in the far field," "induction field," "image antenna a distance  $d$  under the ground," etc., left us rather numb. But we did manage from this discussion to obtain references to several excellent articles on the subject in the radio engineering literature.<sup>1, 2, 3, 4</sup> We must confess that we skimmed through quite a bit of these references, but were successful in obtaining the information we were seeking from graphs found in the references.

From Brown's classic article<sup>1</sup> we marked down in our ledger that the theoretical gain of a single-section two-element driven array with the elements spaced .125 wavelength excited 180° out of phase is 1.65 in field strength or 2.72 in power (field strength squared = power). In db this represents

1 G. R. Brown, "Directional Antennas," *Proceedings of the I.R.E.*, Jan. 1937.

2 J.D. Kraus, "Antenna Arrays with Closely Spaced Elements," *Proceedings of the I.R.E.*, Feb. 1940.

3 Ronald King, "The Field of a Dipole with a Tuned Parasite at Constant Power," *Proceedings of the I.R.E.*, July 1948.

4 "Transmission Lines, Antennas and Wave Guides," King, Nimmo and Wiley, McGraw Hill.

\*Managing Editor, CQ.

a gain over the reference half-wave dipole of 4.36 db. We noted that with .05 wavelength spacing and  $170^\circ$  phase shift the calculated gain is 1.9 in field strength (5.6 db) but knew of no method for obtaining the required phasing and equal current relationship. From the same paper we observed that with  $90^\circ$  phasing the field strength gain is 1.41 (power gain of 2 or 3 db). We noted that a quadrature phase relationship and quarter-wavelength spacing provides a unidirectional pattern, whereas the  $180^\circ$  phasing furnishes the conventional bidirectional figure eight pattern.

However, we were more impressed by the figure references showing the performance of a single driven element and one parasitic element; a theoretical gain of 5.6 db with a drive impedance of 14 ohms looked good.

From Kraus's paper<sup>2</sup> we obtained further information on the driven array using  $180^\circ$  phasing. This author has taken into account the practical problem of losses and his figures show a gain of the order of 3.75 db for the famous 8JK type array.

The third paper<sup>3</sup> is quite comprehensive, and from it we obtained data on the effect of the ratio of length to diameter on the behavior of two-element parasitic arrays.

From our study of the literature we concluded that the driven arrangement is inherently broader band, and it will operate over a wider frequency range. On the other hand, the combination of superior gain and high front-to-back ratio is an advantage of the parasitic array. If we could be content to stick to one frequency on 14 mc for both receiving and transmitting we would have decided on a two-element parasitic array carefully tuned for optimum front-to-back ratio on the operating frequency. Because we classify high front-to-back ratio as a "must" we finally determined that ours would be a 3-element parasitic array using one-tenth wave spacing.

Since the bulk of our operating is on c.w., we wanted optimum performance between 14,000 and 14,150 kc, and we estimated from the values given in the references that the feed point impedance would have a resistive term somewhere between 8 and 20 ohms, and a reactive term of reasonably small but, we must confess, unknown value when the beam was excited from 14 to 14.4 mc. To raise the center impedance of the beam to a point where it could be fed directly with plentiful coax, a folded dipole was used as the radiator. The folded dipole gave us an effective center impedance of four times the nominal center impedance, resulting in a substantially flat line when fed with 50-ohm coax. Thus 7-foot spacing between reflector and director and the radiating element was automatically fixed.

Element length could not be compromised. We are firm in our belief that shortening, no matter by what means, should be done only as a last expedient. The extremely low radiation resistance should not be further reduced by center loading of shortened elements. By standard formula<sup>5</sup> the element lengths were determined for 14,050 kc. For the reflector it was 35', for the dipole radiator 33' 4", and for the director 31' 6".

There essentially you have the ingredients of our very effective beam. Simple—and you'd hardly expect another word of explanation as being necessary. But there are bound to be questions in the mind of any ham putting up a beam for the first time. How do I tune it? Suppose it doesn't load? What about the standing wave ratio? How long will it take to WAZ?

#### Tuning, Loading, SWR

Questions like those are duck soup for the non-expert. He can get his array to work and never worry why. We had the advice of plenty of ex-

<sup>5</sup> Reflector=492/fmc  
Radiator=492/fmc x 95%  
Director=492/fmc x 90%

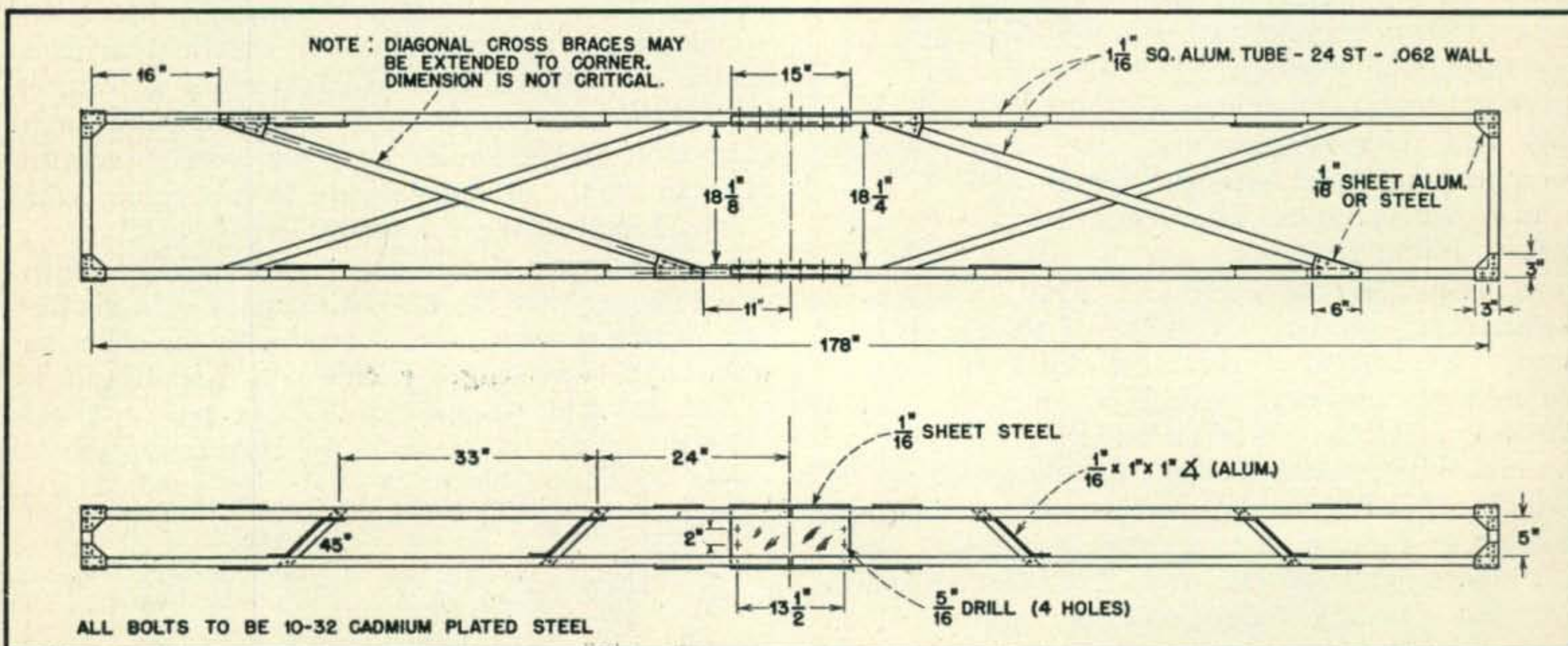


Fig. 1. Mechanical drawing of the boom. The two 7' halves comprising the boom are fastened to the sheet steel center plate by six 10-32 cadmium plated  $1\frac{3}{4}$ " steel bolts both top and bottom. The bolts are locked in with lock washers and locking nuts. Variations of the dimensions given may be required for different types of rotators.



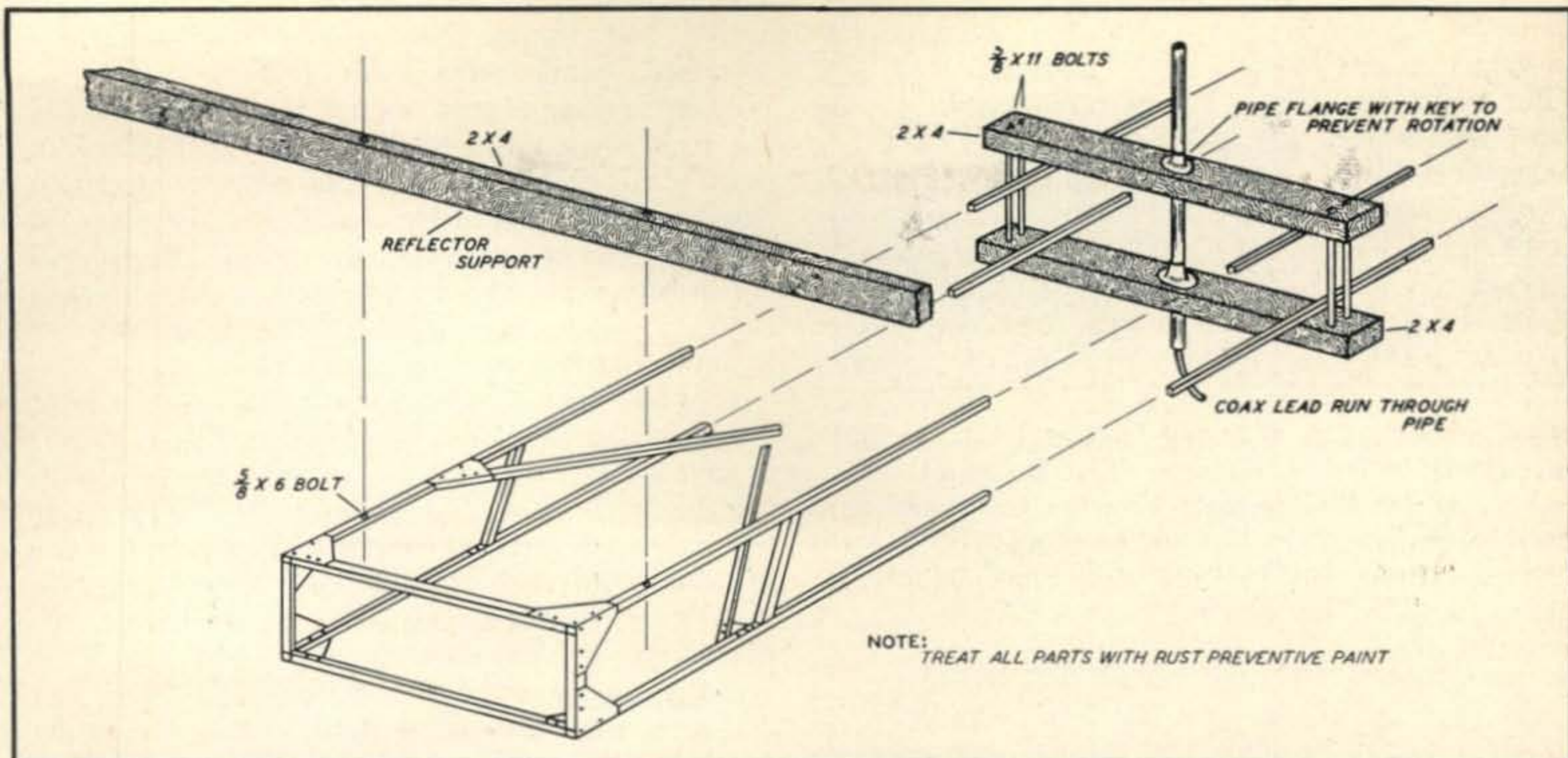


Fig. 2. End detail of the boom is shown in this perspective. Also illustrated is a simple adapter for securing a second beam to the same boom. It is recommended that if a second beam is used it be placed at right angles to the 14-mc unit. The over-all size of the 2 x 4 element support will be dictated by the type element used as explained in the text.

perts and finally had to take our pick as to which answer best suited our purposes. We didn't tune the beam—well, that is, not exactly. The completed beam was put up and checked out. Performance was excellent. It was then deliberately detuned and retuned employing a field strength meter under fairly good conditions. The final beam adjustments agreed so closely with the original "calculations" that our advice is don't readjust the finished beam.


Radical changes as indicated by a field strength meter after a beam has been put up do not necessarily prove anything. They might prove that surrounding objects have various degrees of reflection. They might prove that the level (height) of the measuring instrument was too different from the beam. But unless the beam is completely in the clear and the field strength meter equally so, the measurements may lead more to grief than to glory. We know that this advice will lead to considerable controversy. We can only advise others on the strength of personal experience.

Standing wave ratio and beam loading can be lumped under the same department of misinformation. High amplitude standing waves, if you have them on the feed line, are bad. But frequently not even your best friend can tell you whether you do or don't have them. Measuring SWR on coax is a tough proposition without a slotted line, or similar device. The SWR on this beam is certainly tolerably low. You can accept that figure or question it, but you can't measure it without the elaborate gear.


Now your beam may not load when you first couple the rig to it. You can readily make it load by placing in series a small variable condenser in the shield side of the coax at the pick-up link, tuning until you get the beam loaded, or you can

deliberately leave the coax feed line long and trim it until maximum loading occurs at the center frequency you want. Drop those eyebrows, brother—this is definitely not an indication of a high standing wave ratio. On the contrary, it has nothing to do with the SWR. It can be compared to tuning a Zepp feeder. You have tuned out the reactance of the line and pick-up link by either the series condenser or the pruning. And watch yourself on that pruning; a few inches at a time will do the job.

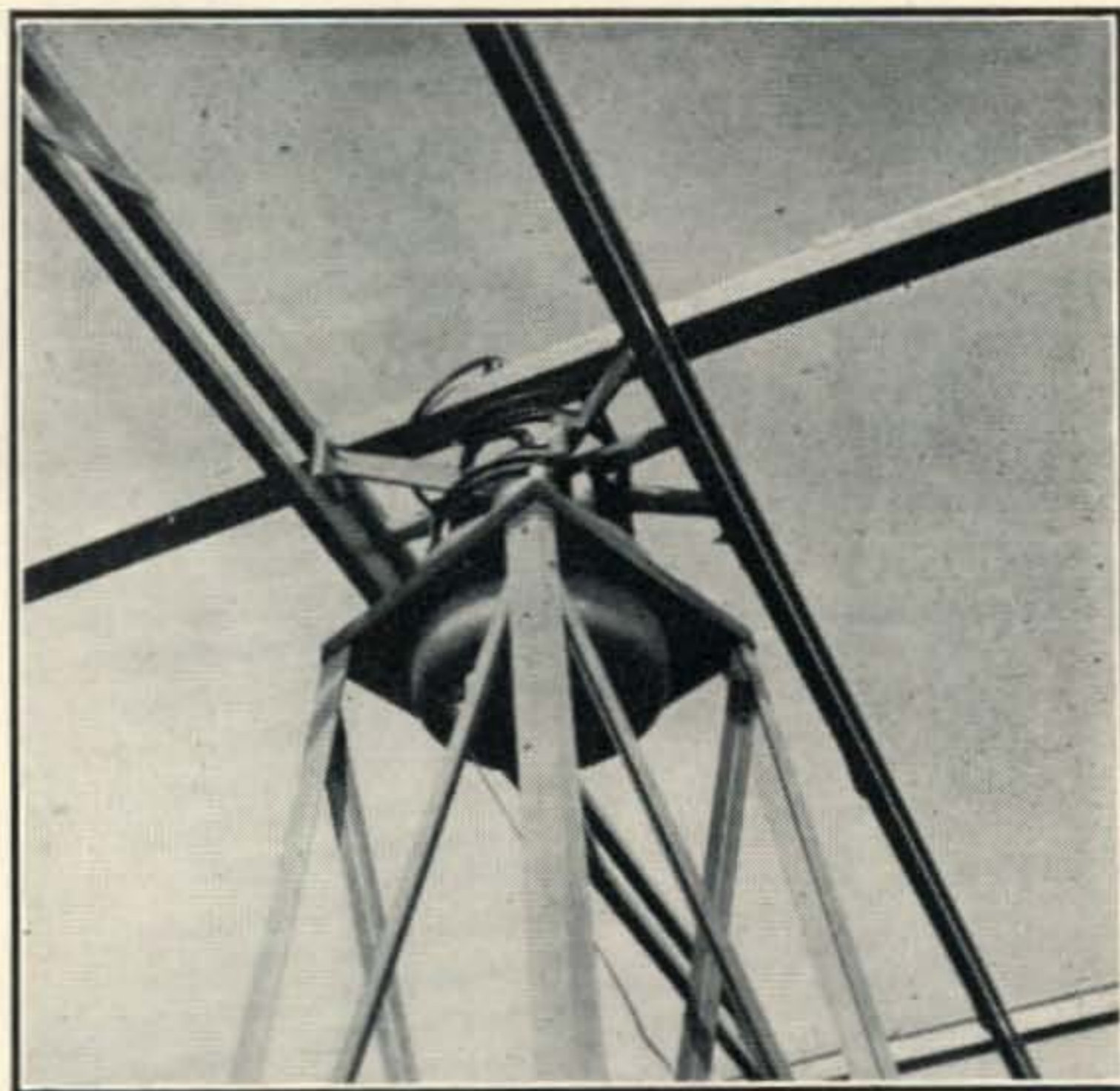Let us dwell on this standing wave problem.



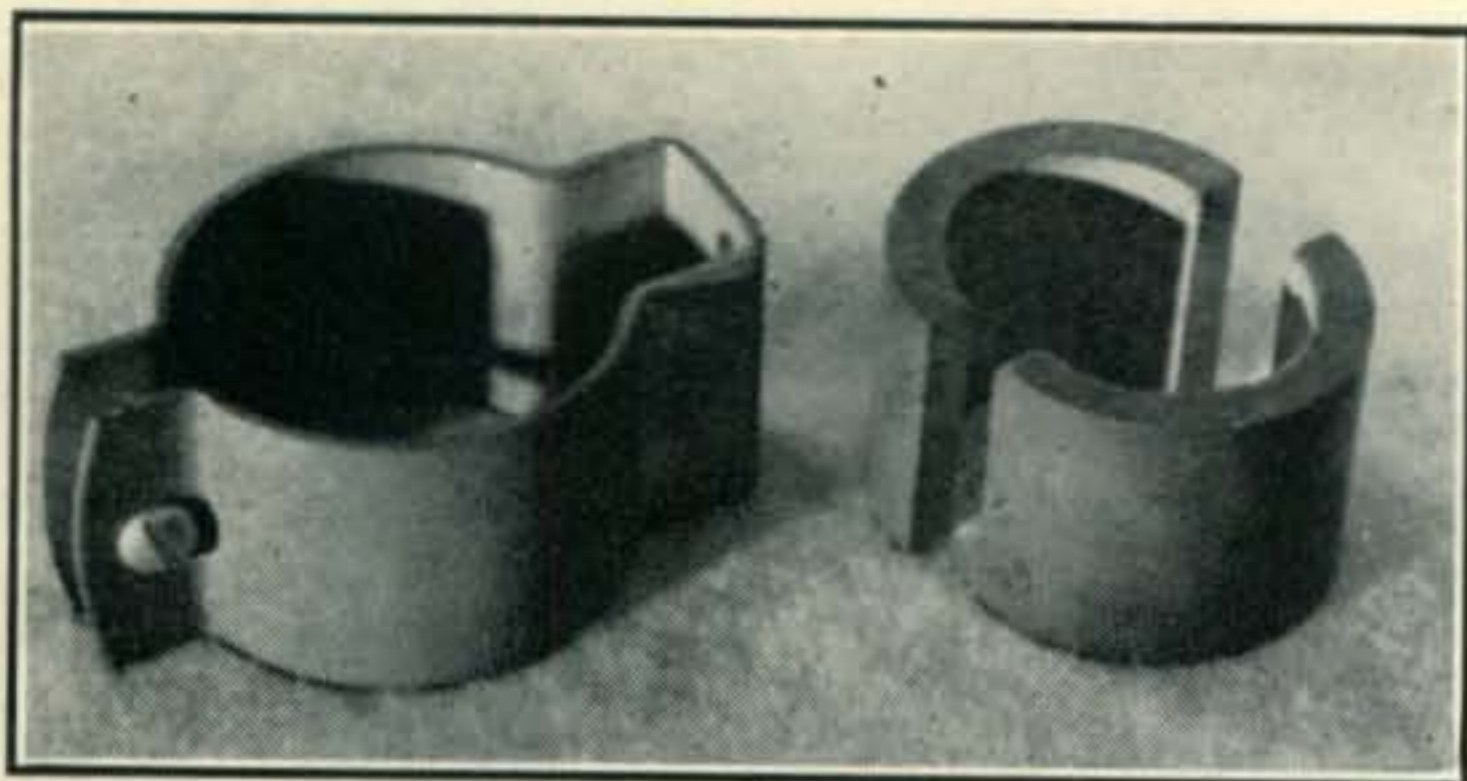The spider top of the rotator secures to the steel center plate of the boom with eight 5/16" bolts. This particular installation was a 28-mc beam which omitted the cross braces. A coax matching section is wound around the rotator.



Premax type 10-C insulated mounting clamp with special  $1\frac{1}{4}$ " inside diameter Mykroy insert. The insert insulates the elements from the boom and any good dielectric material may be used. The clamp itself is secured to the boom with wood screws, no smaller than No. 10  $\frac{3}{4}$ " long.

It is not generally appreciated that even if the resistive term of the antenna feed impedance is equal to the surge impedance of the transmission line, the SWR will be unity only if the reactive term is zero. For example, if the transmission line is 50-ohm coax, if the antenna impedance at the feed point is 50-ohm resistive and zero ohms reactive (radiator exactly the correct length) the SWR is unity. If, on the other hand, the antenna impedance is complex, comprised of a 50-ohm resistive term and a 50-ohm reactive term, it may be shown that for the particular example the SWR is 2.6.<sup>4</sup>

Consider an antenna being driven by a transmission line which electrically is exactly an integral multiple of a half-wavelength long. The impedance at the transmitter end is exactly the antenna impedance. Because the SWR is almost never—practically speaking is never—unity, as we reduce the length of the transmission line, inch by inch, the impedance at the transmitter varies in magnitude and sign. Thus, by pruning the transmission line it is generally possible to find a length that will either present a pure resistive impedance, or will present a resistive impedance plus a capacitive reactance that will tune out the inductive reactance of the pick-up link and the inductive reactance of the changeover relay if used. In a similar manner the series condenser may be employed to resonate the link (and relay lead) inductance in conjunction with the happenstance reactance of the random length transmission line.

It's not new, but while telling this story we might mention how we treat the antenna change-over problem so that the beam can be used on the receiver as well as the transmitter. It is possible to use any relay for coax switching provided you mount the relay directly at the link. This offers a minimum change in impedance and you'll be surprised how little it affects the loading. As a test try clipping the coax directly to the link and then to the link through the closely mounted relay. The change in loading should be negligible. Keep common on the relay the grounds and the center conductors. You can use a single-pole double-throw relay, switching just the center con-

ductor and leaving the outer conductors (the grounded braid) permanently tied together.

Amateurs are always asking about unbalance in the transmission line when feeding a beam with coax. It is important that the coax transmission line leave the beam at right angles to the plane of the beam for at least one half wavelength. Parallelism between coax line and beam induces antenna currents on the outside of the coax, distorts the radiation pattern and reduces efficiency.

It is true that an unbalanced condition does exist when feeding with coax—however, on 14 mc the magnitude is completely infinitesimal. A bazooka can be made for those who want to prove to themselves that they have put the last fraction of a db into desired radiation. Interchangeably, a trombone balancing section<sup>6</sup> may be used but is likewise unnecessary on the low frequencies.

#### Mechanical Gain

Electrically you can see that the beam is simple. Mechanically there can be almost as many possible ways of doing a job as there are individuals who want to put up such a beam. We wanted great strength without an offensive looking structure. While we had no particular objection to using guy wires on the boom, for appearance sake their elimination would be desirable.

Again, having many friends versatile in many fields proved a great advantage. W2VHS, who has a great reputation locally for his handiwork, was consulted and undertook a cooperative building program to turn out a boom. We supplied all of the moral support—Joe did all the work. The result is a handsome and extremely rugged boom. Details of the construction are shown in *Fig. 1*. This boom was designed specifically to go with a Gordon Rotomount. Were a different type rotator employed, some alteration in dimensions might be desirable. For example, the width might be increased or made smaller.

The material used to construct the boom is  $1\frac{1}{16}$ " square aluminum with a  $\frac{1}{16}$ " thick wall. This is standard stock available from any metal supply house. Gusset plates and the center support plates were made from steel sheet  $\frac{1}{16}$ " thick. If we were doing the job over again we would have used aluminum sheet rather than the steel. It is important to avoid contact of dissimilar metal to aluminum on out-of-door installations because of electrolysis. In our installation profuse painting retards electrochemical action.

From the detail of the center support it can be seen where it is necessary to have available a brake to make the right angle bend. If no local shop has this bending tool (and generally an automobile body repair shop, metalsmith, etc., will have one) then the piece may be constructed by clamping the metal between two pieces of  $\frac{3}{4}$  to 1-inch board or  $\frac{3}{8}$ " cold rolled steel to a work bench, allowing sufficient metal for flanges to protrude beyond boards or steel—and gradually bend the flange by striking the metal with a block of wood

<sup>6</sup> Bach, "The Trombone T", *CQ*, March-April, 1947.

until a smooth square right angle is obtained. Bolts can be used, but for the added strength, welding is recommended. It is well to keep in mind if using bolts, to insure that they do not weaken stress points under load. Where practicable, place them in a vertical position. Where this cannot be done, don't fail to use reinforcing strips of aluminum, or a large washer under the head and nut of all horizontal bolts. The brace numbers labeled *A* are bent from 1 x 1 aluminum angle. The degree of their pitch is not critical, although we used a 45° slant.

Make liberal use of zinc chromate compound or red or white lead on all bolts before installation. When the beam is completely assembled, metal parts other than the aluminum should likewise be painted with a rust protective paint. Over this should be used a good grade of aluminum paint. The aluminum itself, of course, won't rust, but the steel gusset plates (if used instead of aluminum) and steel center support will, if not adequately protected. For instance, for assembly hardware we used zinc plated steel. But the plating proved very inadequate and they soon started to rust. So paint on all the hardware is a must. For hams located in particularly damp or salty climates even the aluminum should be painted. Special aluminum protective paint is available, as are the other rust preventive paints, at any large hardware or paint store.

The support for the elements is dictated by the elements themselves. On one of the beams patterned after this one, Premax corrugated steel elements are used. They require greater support than aluminum and the cross boom consisted of 8' lengths of 2 x 4. Each 2 x 4 is mounted on edge, a bolt passing through it and the top member of the aluminum boom. Since it is necessary, or at least desirable to countersink the bolt head, when the final installation is made the hole should be filled with plastic wood. Otherwise water, etc., will collect at this point possibly weakening the wood unnecessarily.


For aluminum elements the wooden cross pieces can be smaller. In the beam illustrated they are Workshop 20-meter tapered elements. The support structure for them measures 6' over-all. There is no noticeable sag in even the longest element. The folded dipole is mounted horizontally; that is, the two elements comprising it are side by side. This reduces the mounting problem, and in no way affects the efficiency of the beam. These elements want to be as close together as practical, in our case 4 inches center-to-center. Blocks bolted to the main support hold the folded dipole. In our ex-


General construction details are shown in this end view. The elements were off-set on the boom because the top of the rotator protruded at exact center. This unbalance was compensated for by placing the shortest element (director) farthest out on the boom. The ends of the folded dipole are strapped together with an aluminum band that is tapped and screwed into the elements.

perience with beams the Premax hose-type clamp proved extremely effective; it is light, economical, as well as strong. Unfortunately the inserts available from Premax fit only their corrugated steel elements. Therefore, if Premax clamps are used with another manufacturer's elements, Workshop in this instance, a substitute insert must be made. In looking around for a suitable material we hit upon Mykroy, an excellent dielectric material equal to the steatites, but with the property of being easily tooled. Round stock was obtained and drilled carefully using slow speed drills and water for lubrication. The result was a Mykroy insert as shown in the photo. Since all the clamps are secured on the 1¼" portion of the elements, only one size was required. Other materials could be used, a good grade of bakelite coated with Polystyrene dope, etc. O. D. of the stock is 1½".

The balance of the job is simple. You put the beam together, get a careful and husky crew of local hams together and drag it up to the top of the tower. A light duty block and fall is very handy. For connections to the folded dipole we soldered lugs on the coax on the ground and then made a mechanical connection to bolts provided on the elements for that purpose. These connections were then coated liberally with Amphenol polystyrene cement.

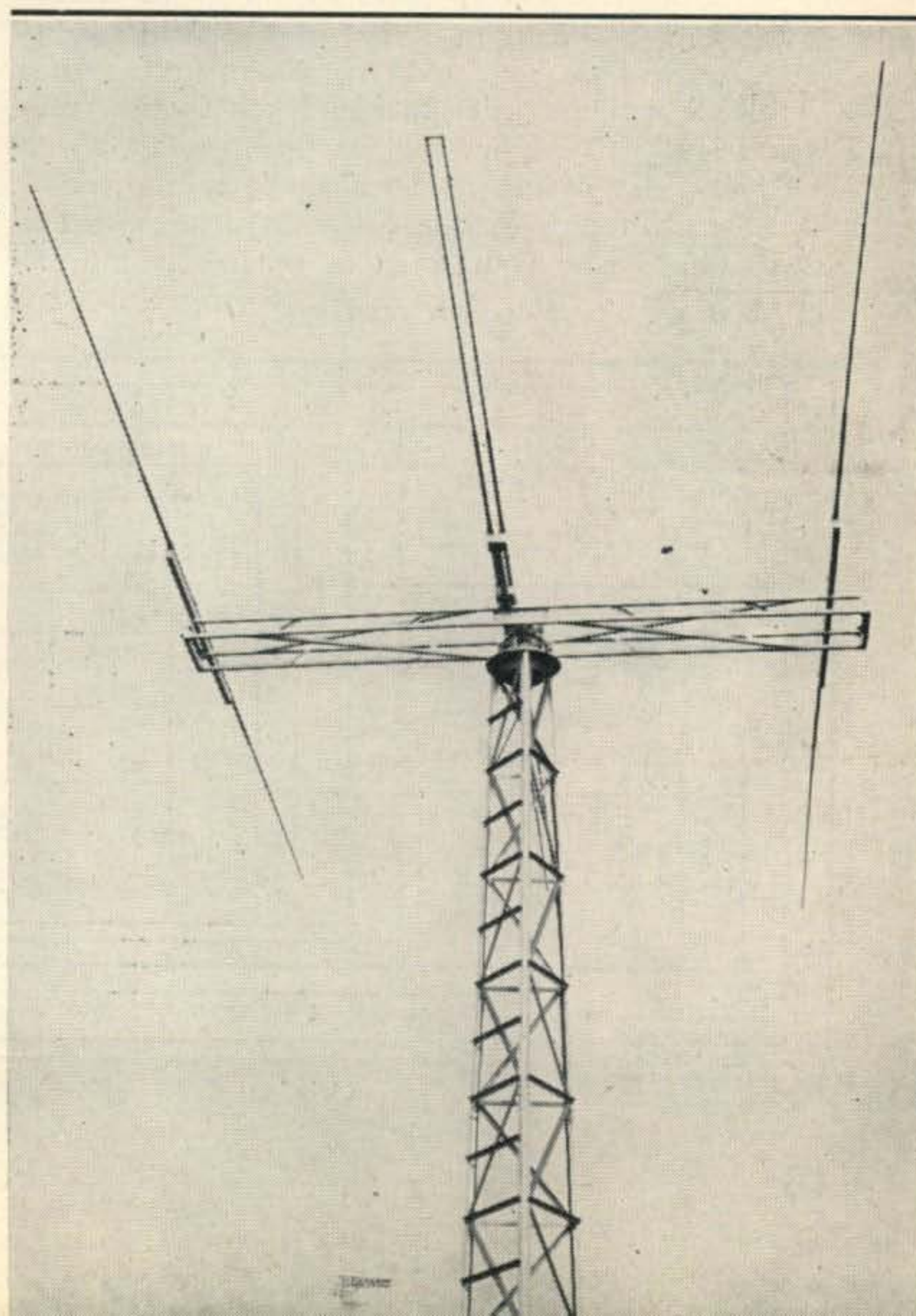The finished product is a handsome structure. Even disinterested neighbors have been forced to admire its very utilitarian beauty. More important, DX stations who can't even visualize it have attested to its potency. Rugged and effective—that's what your beam will be if you duplicate this job.



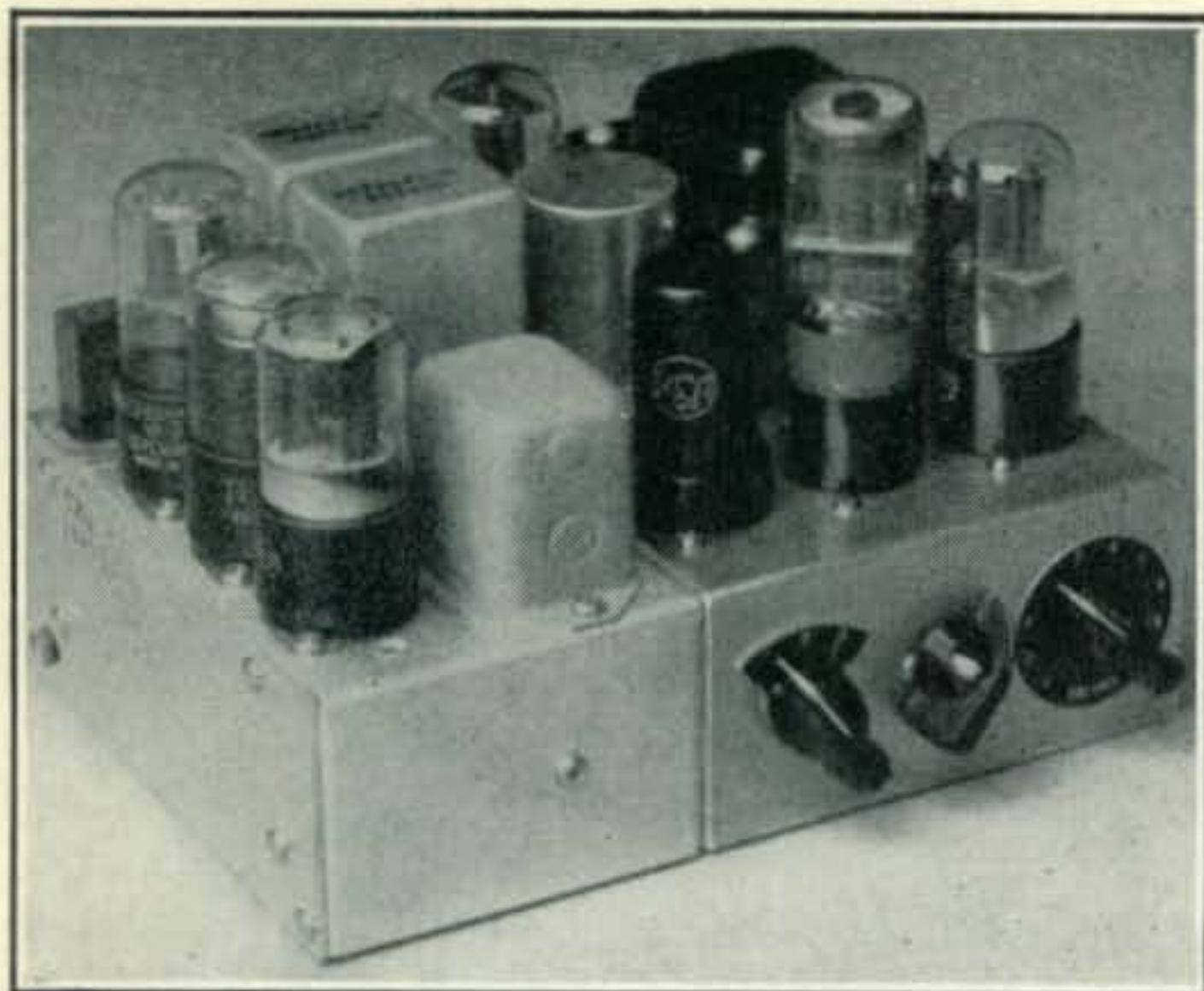

Controls on the auxiliary chassis are, left to right: power control and function switch, harmonic peaking amplifier, and audio amplifier gain control.

# Frequency Standard

A. W. HORST, W9CUX\*

**T**HE M.C.W.-C.F.I. unit is a compact little combination audio oscillator and crystal controlled secondary frequency standard that was incorporated in the popular AN/ART-13 transmitter. A number of war surplus stores have offered these sub-assemblies as a separate item both with and without the 200-kc crystal. Crystals seem to be rather scarce but are available in some stores a modest investment.

For a small cash outlay plus a moderate amount of conversion, you may own an excellent secondary frequency standard. Briefly, the converted unit performs the following useful functions:

1. Serves as a precision frequency standard which provides an S9+ signal on your receiver dial at every multiple of 50 kc from 50 kc to about 20 mc and S7 through 30 mc. Maximum error *without warm-up* is in the order of a few cycles at 1000 kc. This signal may also be modulated by the 1000 cycle audio oscillator contained in the C.F.I. unit in order to identify it in the presence of other signals.

2. Provides visual or aural indication of zero beat between any of the 50-kc harmonics and a small input from your v.f.o. or other oscillator.


\*1031 Pine St., St. Charles, Ill.

3. Supplies a 1000 cycle audio output whose wave-form and stability is far better than the familiar whistle or prolonged "hello-o-o-o-o" commonly used when checking the speech amplifier or modulation envelope on an oscilloscope.

The C.F.I. unit as purchased may be used as a frequency standard merely by supplying it with proper filament and plate voltages. However, it was my own experience that the harmonic strength dropped off rapidly above the broadcast band. In order to remedy this, it was decided to incorporate a harmonic amplifier in the additional chassis which would house the power supply. This chassis eventually took the form shown in the photograph. It has the same height and depth as the C.F.I. unit and is approximately 4½" wide. One of the side plates was removed from the C.F.I. unit and used as a template for drilling the adjoining side of the new chassis. This partition became common to both units and the spare side of the C.F.I. unit was filed in the hardware box for future reference.
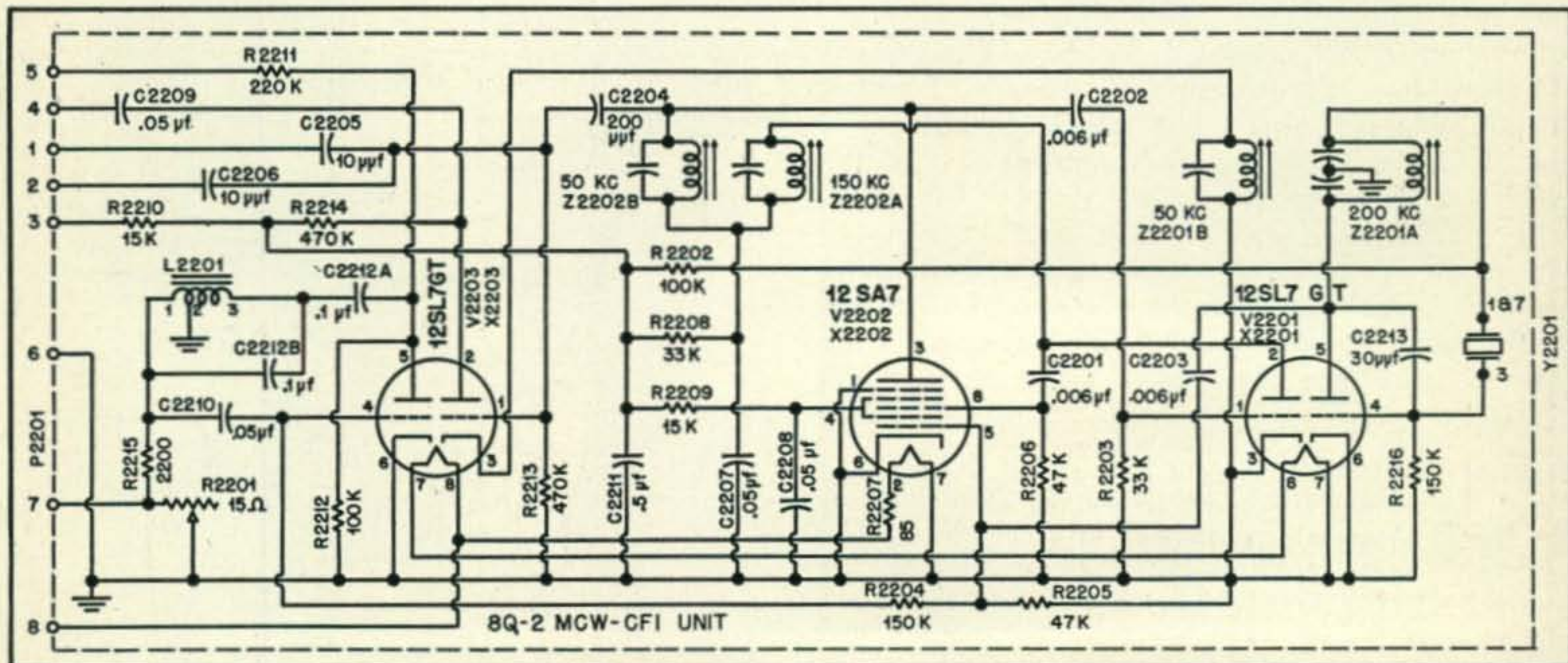
## Improving the Output

The first harmonic amplifier tried was of the conventional type using a 6V6 tube with a tapped coil and bandswitch in the plate circuit tuned with




Original C.F.I. unit before start of modification.

Rear chassis decks contain binding posts for comparison signal input and output for aural monitoring. Jack is for 1000-cycle audio output.
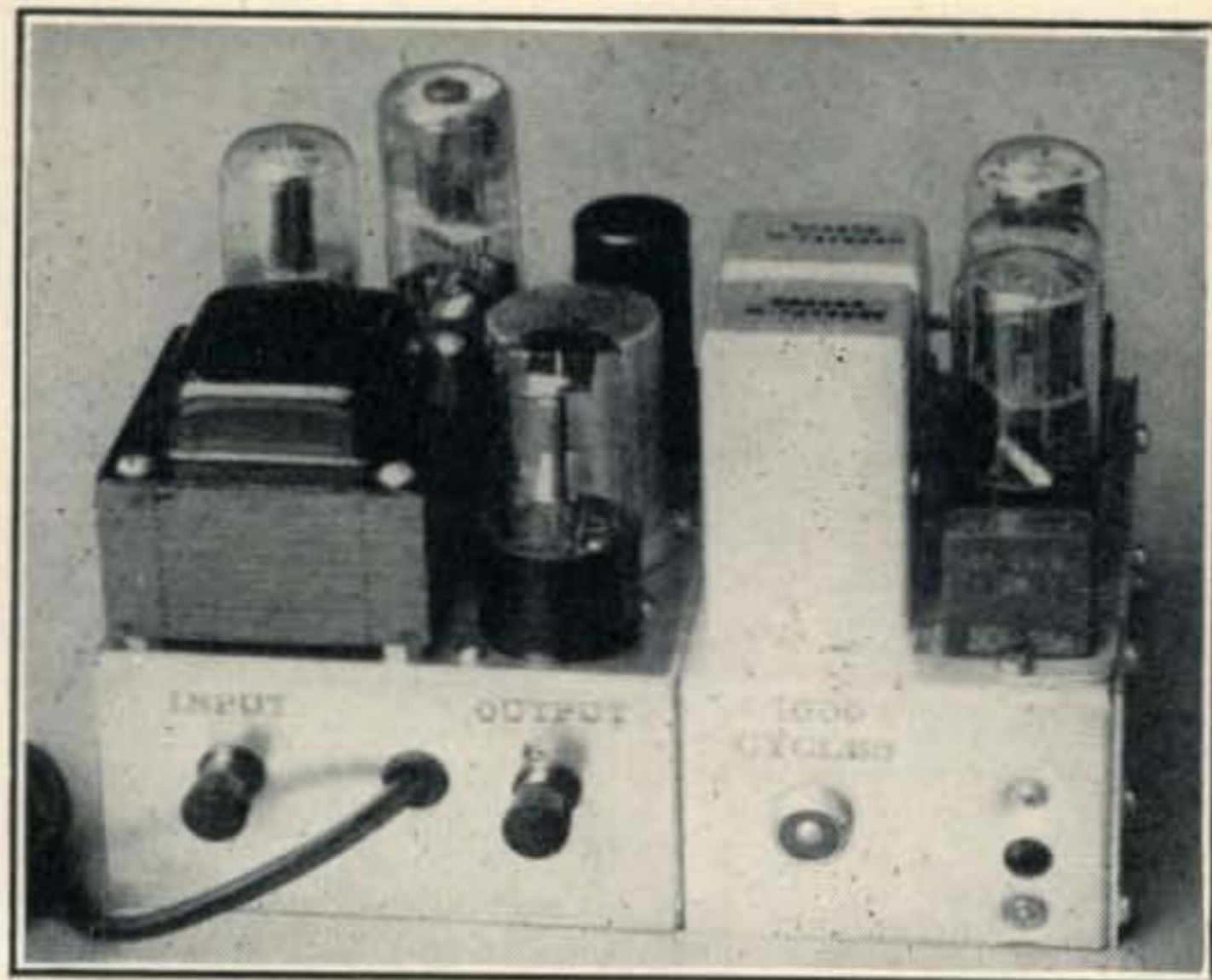
# from a C. F. I. Unit

With this unit on your operating desk you can take down "off limit" signs on the band edges.



a variable capacity. Output was only mediocre and in addition it was necessary to re-tune the tank circuit to cover the 3.5-4.0 mc band. This led to experiments with a 2.5-mh choke in the plate circuit operating as an untuned amplifier. Results were promising and this finally led to the use of a 2.5-mh choke shunted by a small variable condenser which peaks the harmonic strength for the band desired. Further experiments with the r-f choke led to the conclusion that 2.5-mh is about optimum size and chokes made by National and Centralab performed satisfactorily. The tube was changed to a 6SJ7 with equal output and considerably lower current drain. Although decidedly unconventional, the circuit seems to be stable in operation and not critical as to components. Furthermore, it requires no bandswitch and delivers a wide band of output frequencies for a given tuning adjustment.<sup>1</sup>


At about this stage of the experiments it was decided to investigate the 1000 cycle audio oscillator with the object of imposing a distinctive audio modulation on the r-f marker signals. This audio oscillator originally operated as a warning signal indicating that the crystal calibrator was not oper-

<sup>1</sup> A 6AC7 pentode amplifier stage employing a 500-1000 ohm plate resistor and series peaking, feeding a cathode follower, likewise may be used as a harmonic booster.—Ed.


ating. As long as an r-f signal of normal magnitude appeared on the No. 1 grid of the 6SA7, the bias voltage developed across the 47K grid resistor, R2205, was applied to the grid of the audio oscillator through the 150K resistor, R2204, and blocked this tube. By simply removing the lower end of the 150K resistor from the 47K resistor and tying it to ground, the audio oscillator operates in a normal manner. Next, it was determined that several volts of audio were available at either end of the oscillator coil so an audio coupling condenser was connected from the grid end of this coil to the screen of the 6SJ7 harmonic amplifier. This resulted in a pleasing modulation of about 20% on the calibrator signals which makes them easy to identify among the mess of heterodynes in the amateur phone bands.

Since it is often desirable to sneak up on a band edge with your v.f.o. while the receiver is tuned to a choice DX signal, further experimenting was done in order to add a detector and a visual resonance indicator. This resulted in the incorporation of a 6SN7 and 6E5. One-half of the 6SN7 operates as a plate detector and the other half as an audio amplifier.

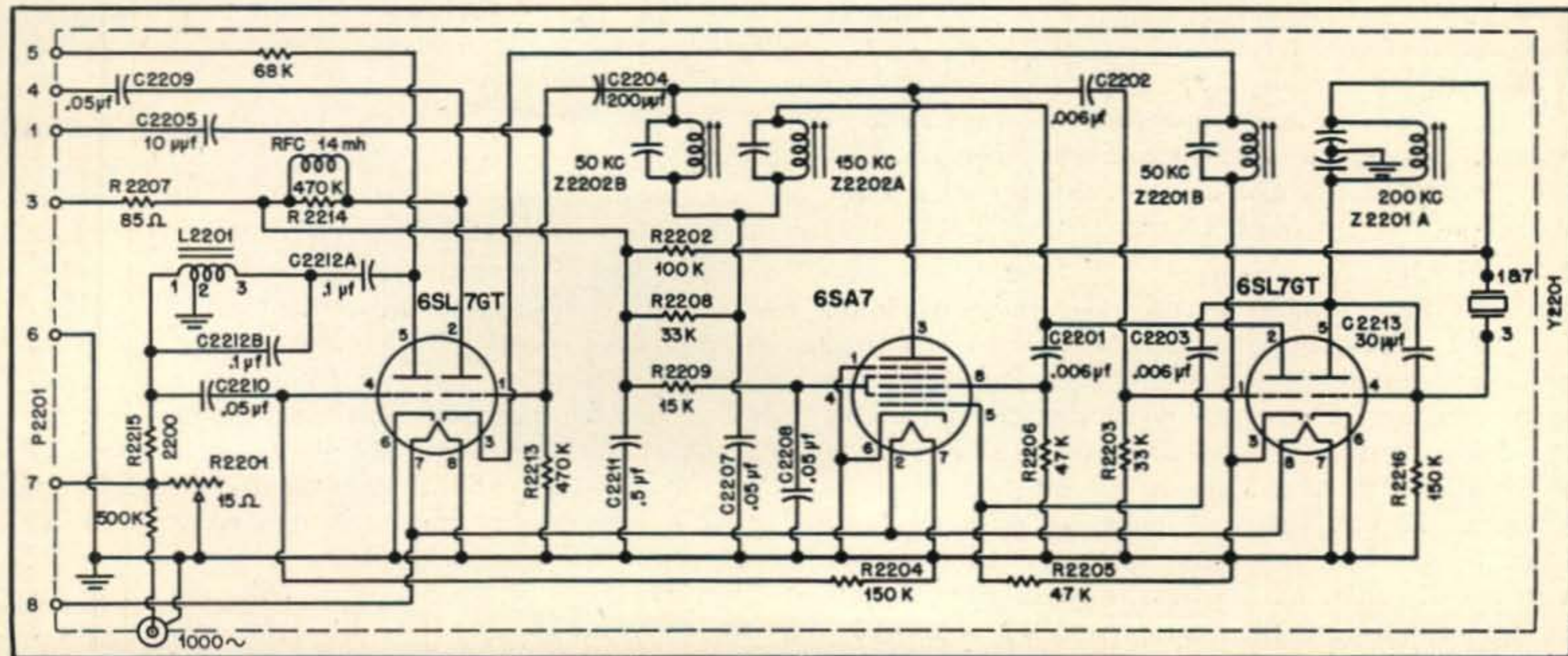The grid of the first section of the 6SN7 is



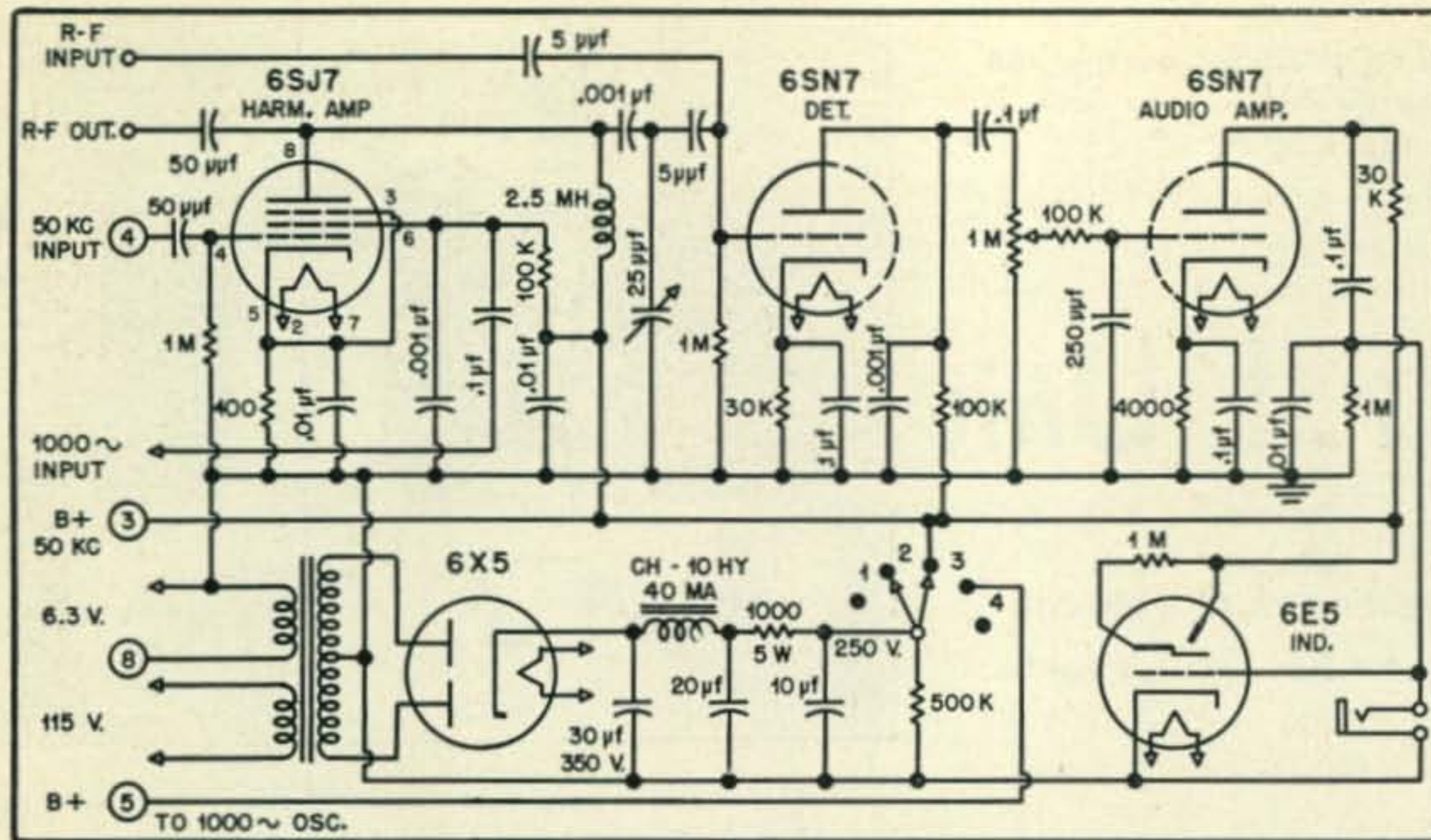Modified C.F.I. unit after conversion is completed.



Power supply, harmonic amplifier and visual indicator. Numbered terminals connect to corresponding numbers on C.F.I. connector plug.

coupled to the calibrator harmonic amplifier through a  $5\text{-}\mu\text{f}$  capacitor and to an external binding post through another  $5\text{ }\mu\text{f}$ .

This allows a small signal voltage from a v.f.o. or other source to be mixed with the corresponding harmonic of 50 kc to obtain an audio beat note in the plate circuit. This, in turn, is fed through the 1-megohm gain control to the audio amplifier section of the tube and the audio output appears across the 30K plate resistor. A phone jack coupled to this plate through a  $.1\text{-}\mu\text{f}$  condenser permits aural monitoring with phones or a small speaker. Visual indication of resonance or near-resonance is accomplished by the 6E5. Circuit constants in the detector and audio amplifier are chosen so that the shadow angle begins to close when the v.f.o. approaches a 50-kc multiple within about 5 kc. This angle continues to close until the difference frequency has been reduced to a few cycles per second. It then opens and closes at the beat frequency until absolute resonance has been reached. In practice, in using this gadget in connection with a BC-696A v.f.o., the point where the shadow breaks open and starts to follow the individual beats is extremely sharp and the accuracy of comparison is many times that of the indication on the 1629 eye tube in the BC-696A where you merely tune for the widest shadow angle.

In order to establish the upper frequency limit for this method of comparison, it was tried in connection with a Meissner Signal Shifter. At near-resonance the eye closed fully through 7 mc and about half through 14 mc.

#### How To Do It

A few notes on the actual conversion work on the C.F.I. unit may be in order here. The original and converted schematics show the changes in the heater wiring. The tubes were changed to 6 volt equivalents in order that a single heater voltage could be used throughout. In the interest of economy, the 12 volt tubes which came with the unit could be used by choosing a power transformer with two 6 volt windings or a 6 and a 5 volt winding and connecting them in series. 12 volt equivalents would then be used on the auxiliary chassis

except for the rectifier which would be connected across only one of the windings.

There is nothing critical about the power supply and components can vary considerably from those shown on the schematic. The filament winding should be able to supply at least 2 amperes and the high voltage should be approximately 250 volts with a drain of 35 or 40 ma.

The 50-kc output available at terminal No. 4 of the output plug was increased somewhat by shunting the 470K ohm resistor,  $R2214$ , in the plate circuit of the final 6SL7 with a 14 mh r-f choke. This raises the voltage on the plate of the tube considerably while maintaining a relatively high impedance load at radio frequencies. In order to further increase the available plate voltage, it was also found worthwhile to replace the 15K wire wound resistor,  $R2210$ , with an 85-ohm resistor,  $R2207$ , which was previously removed from the heater circuit. The 85-ohm resistor is just sufficient to reduce the arc at the switch contacts.

Resistor  $R2211$  in the B+ lead of the audio oscillator section of the 6SL7 was changed from 220K to 68K with an increase in plate voltage and corresponding increase in audio output. These changes are desirable because the ART-13 supplied about 400 volts to the plug connections while there is only 250 volts available from the conversion power pack.

The tapped switch in the plate supply lead is a little unorthodox in that the rotor feeds two adjacent contacts at each position. With the rotor in the extreme counter-clockwise position, all sections are off. In the next position plate voltage is supplied to all tubes except the audio oscillator. Number 3 position continues to supply plate voltage to all tubes included in number 2 position, and, in addition, puts the audio oscillator in operation so the output of the harmonic amplifier now has the 1000 cycle modulation. Continuing the switch to No. 4 position, the plate supply is removed from all tubes except the audio oscillator.

Referring to the circuit you will note that the 1000 cycle audio output is brought out to No. 7 pin on the connecting plug. This output is control-

able by the small 15-ohm variable resistor, *R2201*. Observation of this output on a scope showed that it possessed a very respectable waveform and therefore might be useful in itself around the shack. Accordingly, this was tied to a standard microphone receptacle mounted on the back of the chassis through a half megohm resistor. The series resistor was added in order to raise the output impedance to approximate that of a diaphragm type crystal microphone. The output across a 1-megohm load with the 15-ohm control at maximum is between 10 and 20 millivolts. This is enough to drive the average speech amplifier to full output.

#### Adjustment and Performance

A little time should be spent in becoming familiar with the adjustment of the permeability tuning slugs in the C.F.I. coils. The tuning screw labeled "200-kc" is adjusted only to bring the 200-kc crystal into zero beat with WWV or a broadcast station on a multiple of 50 kc. The other slugs are peaked for maximum output. It is advisable to do this by observing the S-meter reading on the station receiver set at a high order harmonic, say 14 mc, since this adjustment has some control over the output waveform. Because the waveform determines the harmonic content of the amplifier, it will be found that following this procedure will result in considerably greater output at high frequencies than will result from tuning for maximum 50-kc output as observed on an oscilloscope.

A brief explanation of the regenerative frequency divider circuit employed in the C.F.I. is as follows: The 200-kc crystal controls the grid of the oscillator section of *V2201*. The plate circuit of this tube is also tuned to 200 kc and supplies excitation at this frequency to the No. 1 grid of the 6SA7 mixer. The plate circuit of the 6SA7 is tuned to 50 kc and in turn excites the grid of the tripler section of *V2201*. The 150-kc tank in the plate circuit of this tube feeds back to the No. 3 grid of the 6SA7. This frequency mixed with the 200 kc on the No. 1 grid results in a sustained 50-kc output in the 6SA7 plate circuit. In its original application, this 50-kc output was mixed with an incoming signal from the transmitter on the grid of the first section of *V2203* and an audio output obtained from its plate circuit. This was brought out through an .05- $\mu$ f capacitor to terminal No. 4 on the connector plug. This triode in the conversion serves as an additional amplifier and 50-kc excitation for the harmonic amplifier is taken from terminal No. 4.


A little experimenting should be done regarding the coupling between the harmonic amplifier and the station receiver. An SX-28 is used here and a single wire run from the output post of the calibrator to the antenna post of the receiver has proved satisfactory. If too much coupling is employed, it will scatter "birdies" throughout the bands.

With the receiver tuned to a 50-kc harmonic in any of the amateur bands it will be noticed that

there are a number of peaks encountered as the 25- $\mu$ f tuning condenser is adjusted. These will vary somewhat in strength and it is only necessary to observe the S-meter to pick the strongest peak. Generally speaking, the less the resonating capacity used, the broader will the band of frequencies covered without readjustment.

Like any other oscillator there is a certain amount of drift during warm-up and operation. However, due to the extremely low temperature coefficient of these low frequency crystals the total drift as observed at 1000 kc will only a few cycles from a cold start to normal operating temperature. The unit was run continuously for 8 hours and reset to zero beat after the first 2 hours. The greatest subsequent difference with WCFL on 1000 kc was observed to be about 3 cycles per second. This stability coupled with the ability to establish absolute zero beat between 50-kc harmonics and corresponding points on your v-f-o dial should enable the owner of a stable v.f.o. to utilize the last couple of kilocycles on any band edge without fear of out-of-band operation. Since all of the amateur band edges are, at present, multiples of 50 kc, operation within 5 kc of any of these spots will give a partial closure of the tuning eye which can be observed from time to time during transmissions as reassurance against drifting out of the band.

The converted C.F.I. is a great convenience in retracking the station receiver because of its ability to supply modulated signals every 50 kc without readjustment whereas the average signal generator must be reset for each check point and in addition is not sufficiently accurate on higher frequencies. Another daily use at W9CUX, in connection with the receiver, is to set the main dial so that the bandspread dial calibration comes out on the nose. It is also very interesting to check some of the DX phone boys leaning over the edge at 14,300 kc and then hear them tell the other fellow that their frequency is 14,297 kc.

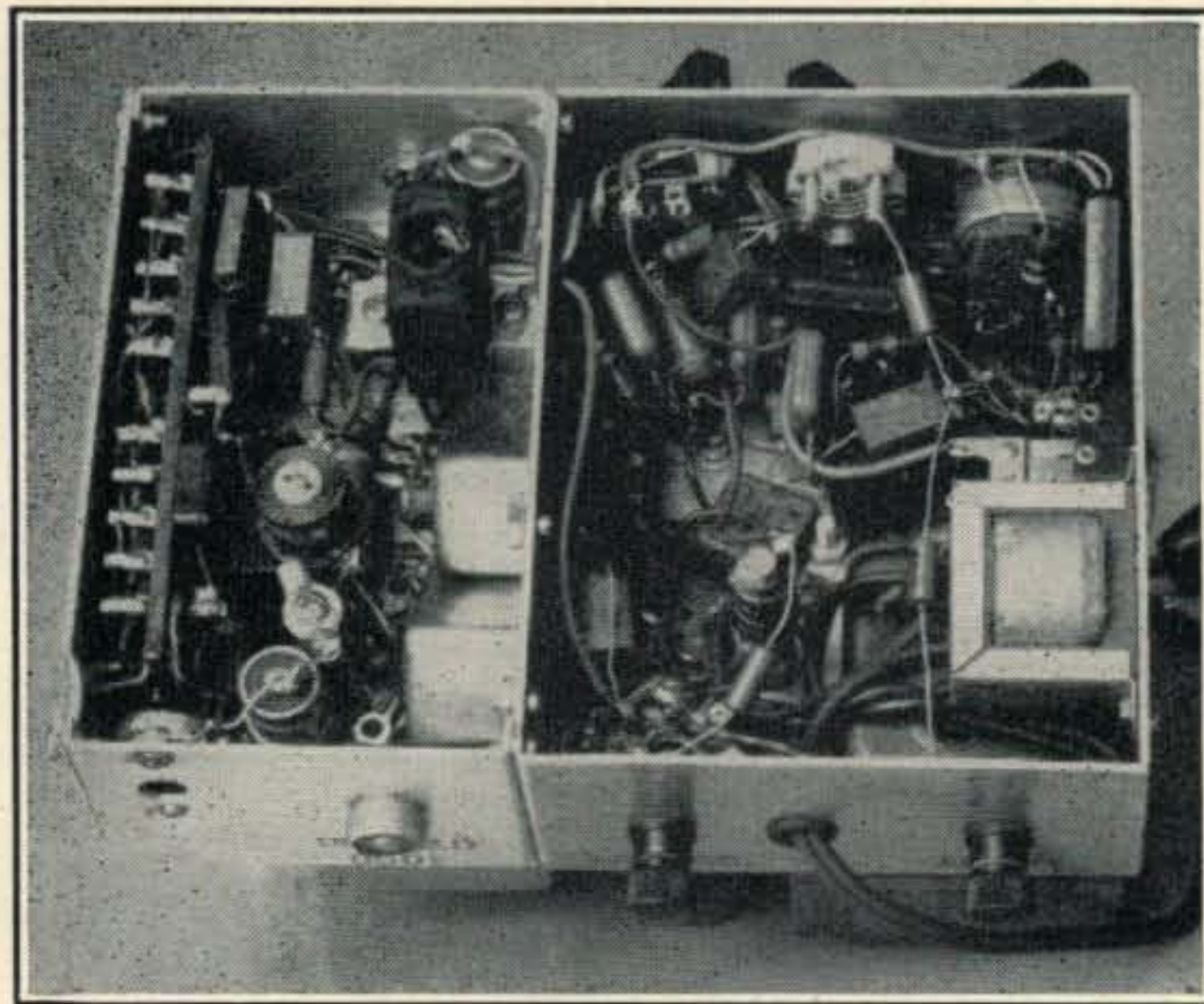

Bottom view of the converted C.F.I. and associated circuits. Note the Jones connector used to bring the connections from the auxiliary unit to the C.F.I.



Photograph A. Front view of the beginners' 6, 10 and 11-meter converter. Essentially a single-dial converter, the middle knob is used only to peak the incoming signal.

GEORGE H. FLOYD, W2RYT\*

## Beginners' Converter

### For 6, 10 and 11 Meters

*For radiophone operation and for c-w DX on 10, the newcomer will want his receiver to tune through 54 mc. Here is a simple unit to give this extended coverage.*

IN THE PROCESS OF building and accumulating radio equipment many beginning amateurs find themselves in the position of having a home-built receiver which has been doing an excellent job on 80, 40 and 20 meters, but which will not work on 10 meters, despite parts juggling or any manner of coil rewinding. This is to be expected in many cases because the higher-frequency bands require different construction techniques. The implication is that it is more difficult to build high-frequency receiving gear, but this is not particularly true if a moderate amount of care is used in construction.

The most logical and certainly the simplest way for a beginner to obtain a receiver for the 6 and 10-meter bands is to use a converter which will work into the receiver he already has. Any type of low-frequency receiver, when used in conjunction with a converter, becomes a superheterodyne type of receiver.

#### General Consideration

The converter about to be described will receive signals in the 27 to 30-mc region or the 50 to 54-mc region and convert them to a frequency of approximately 14 mc. This output may be fed into a 20-meter receiver, which will act on the 14-mc signal in the usual manner, detecting it and amplifying it audio-wise. Fourteen megacycles, which is the intermediate-frequency (i.f.) of the superheterodyne receiver formed by this combination, was chosen so that the converter could be used with practically any low-frequency receiver, especially those which use bandspread plug-in coils covering only a limited frequency range.

A converter to be used in this manner should have moderately good sensitivity and be simple

in design, but as a prime consideration it should be easy to build and to get working properly. The beginners' 6, 10 and 11-meter converter was designed with these three points in mind.

#### Electrical Details

With reference to the circuit diagram, *Fig. 1*, the circuit is built around a single miniature tube, the 12AT7. This tube is actually two triodes in one envelope. Despite the fact that a "12" appears in the tube type number a filament voltage of either 6.3 or 12.6 volts may be used.

One triode section of the 12AT7 (pin connections 1, 2 and 3) acts as the mixer, and the other section is the local oscillator. When the 10-11 meter coils are used, the oscillator operates over a frequency range from 41 to 44 mc so that incoming signals from 27 to 30 mc produce a frequency difference in the mixer of exactly 14 mc. This latter frequency appears in coils *L1* and *L2* and is sent on to the receiver. When the 6-meter coils are employed, the oscillator operates from 64 to 68 mc, so that incoming 50 to 54 mc signals again produce a difference frequency of 14 mc.

In order to better understand the operation of the converter, assume that the 10-11 meter coils are in place and that a 30-mc signal is coming in the antenna. *Coil A* accepts this signal, and when condenser *C1* is properly tuned, the coil and condenser resonate broadly at 30 mc and place this signal on the first triode section grid (pin 2). If at the same time condenser *C10* is adjusted so that *Coil B* and *C10* resonate at 44 mc, then the second section of the tube will oscillate at 44 mc. Due to internal and external coupling this 44-mc signal from the oscillator will now also appear on the grid of the first section (pin 2).

\*Tube Division, G.E. Co., Schenectady, N. Y.



The first section will now act to mix the 30 and the 44-mc signals, and the result will be a 14 and a 74-mc signal. These two resultant signals will appear in the plate circuit of the first section. However, *L1* and *C4* (plus other capacitance) are resonant at approximately 14 mc, so it is this signal that is passed on to the coupling coil *L2* and then to the receiver.

Condenser *C10*, which is connected to the main dial (*Photograph A*) is the main tuning control. *C1*, which is controlled by the knob directly below the main dial, is a broad tuning control which is used only to peak the signal once it has been tuned in.

Coil *A* is padded with three different condensers—*C1*, *CA2* and the combination of *CA1* and *CA3* in series. The purpose of the two series condensers, *CA1* and *CA3*, is to provide an impedance matching device for the antenna, similar to that popularized by the R-9'er<sup>1</sup>. Adjustment details on this matching will be discussed later.

Coil *B* employs condenser *CB* for padding and *C10* for tuning. The third plug on this coil allows the oscillator cathode to be connected to a tap on the coil. The mixer cathode is not connected to the mixer coil, but instead connects to ground through *R2*, which acts as a bias resistor.

Condensers *C3* and *C5* (even though they are both grounded) are in series, and in conjunction with *C4* act to tune coil *L1* to resonance at 14 mc.


Because of the low voltage and current requirements of the 12AT7 tube, it seemed desirable to include a power supply in the converter design. To do this, it was necessary to add only a selenium rectifier, two resistors and a condenser. *R6* is a current limiting resistor, which protects the rectifier, *X*. *R7* takes the place of a choke, and with condenser *C11* becomes the filter system. *C11* is a double condenser, each section being rated at 40  $\mu$ f at 450 volts.

The connection to the 117-volt a-c line is unusual but is designed so that fuses will not be blown. The spring clip is first fastened to a good

ground connection and then the a-c plug is inserted in an a-c socket. Switch *S* is turned on, and if the pilot lamp does not light, it is only necessary to reverse the a-c plug. The power supply is designed to be used on a-c lines only. If d.c. is available, the power supply may be omitted, and the positive d-c voltage fed through a fuse directly to the junction of resistors *R3* and *R4*. The negative lead would connect to the chassis. Transformer *T* should be omitted, and the filament of the 12AT7 energized by four 1.5-volt dry-cell batteries.
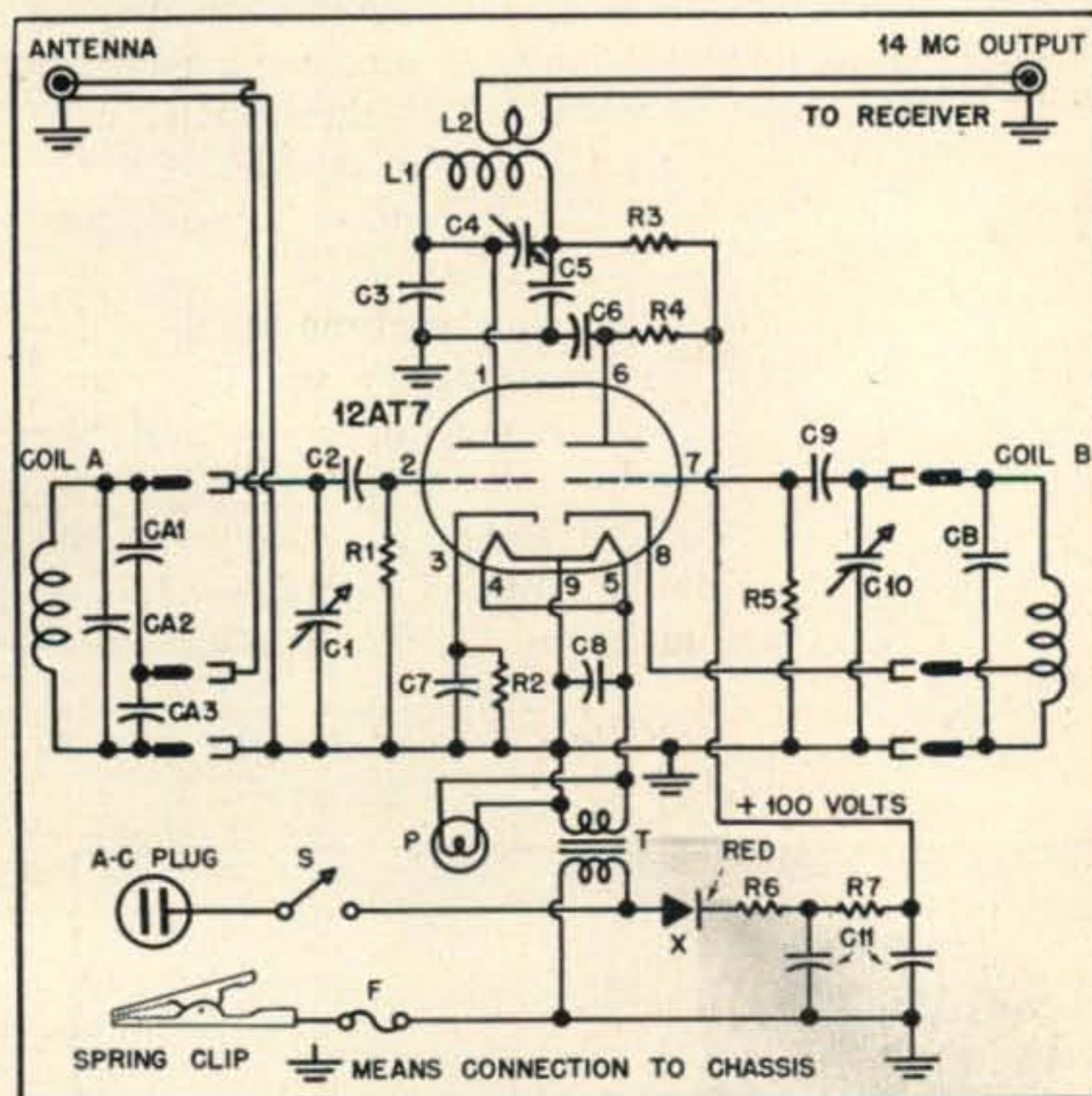
#### Construction

The first step is to procure all of the parts listed under the diagram of *Fig 1*. It is desirable to get parts which are exactly like those listed. One reason for this is that the converter described used those very parts and the builder is therefore assured that his converter should work in a similar manner. Furthermore, if the converter does not work the first time it is tried, the builder knows that this is due to an error in wir-



1 G-E Ham News, Vol. 1 No. 4.

Fig. 1. Circuit diagram of the beginners' 6, 10 and 11-meter converter.

*C1*, *C10*—15  $\mu$ f, variable (Hammarlund HF-15).  
*C2*, *C3*, *C9*—50  $\mu$ f, mica or ceramic.  
*C4*—12-120  $\mu$ f, mica compression variable (ICA-612).  
*C5*, *C6*, *C7*, *C8*—500  $\mu$ f, mica.  
*C11*—40-40  $\mu$ f, 450 volts, electrolytic (Sprague EL240).  
*CA1*, *CA2*, *CA3*, *CB*—Ceramic condensers, see Coil Table.  
*F*—1/2-ampere fuse.  
*L1*—11 turns No. 18 enamel wire space wound on 1/2 inch diameter polystyrene rod.  
*L2*—4 turns insulated wire wound over *L1*.  
*P*—6.3-volt pilot light.  
*R1*—1 megohm, 1/2 watt.  
*R2*—1500 ohms, 1/2 watt.

*R3*—5000 ohms, 1/2 watt.  
*R4*—50,000 ohms, 1/2 watt.  
*R5*—10,000 ohms, 1/2 watt.  
*R6*—25 ohms, 1/2 watt.  
*R7*—2500 ohms, 2 watts.  
*S*—SPST toggle switch.  
*T*—Filament transformer, 6.3 v. @ 1.2 amp. (Stancor P-6134).  
*X*—100-ma selenium rectifier (G.E. 6RS5GH1).  
 G.E. 12AT7 tube.  
 9-pin tube socket.  
 4 x 4 x 2 inch chassis.  
 7 x 7 x 2 inch chassis.  
 8 3/4 x 9 inch panel.  
 Main dial (National MCN).  
 Knob (National HRS-2).  
 4 x 4 x 1/4 inch piece of polystyrene.  
 Six-inch length of 1/4-inch rod for

shafts.  
 Twelve-inch piece of 1/2 inch diameter polystyrene rod.  
 Six-inch length of 300-ohm twin-conductor cable.  
 2—1/4 inch solid shaft couplings.  
 2—Female coaxial line chassis connectors (Amphenol 83-1R).  
 2—Male coaxial line plugs (Amphenol 83-1SP).  
 1/4-inch panel bushing.  
 6—Banana jacks.  
 12—Banana plugs.  
 Alligator clip for ground connection.  
 A-C plug.  
 Fuse holder.  
 6-32 machine screws and nuts, and soldering lugs.

ing, or some other similar type of trouble, but is not due to substitution of parts which were not specified.


With the exception of *R6* and *R7*, the resistors may be values close to those specified, instead of exact values. For example, *R4* may be 47,000 ohms instead of 50,000 ohms. Also, larger wattage resistors than those specified may be used, although it may be more difficult to get these wired in properly, because of their larger size.

It is important that all condensers be of the value specified. Condenser *C4* may have a range greater than that specified, as long as it covers the range from 12 to 120  $\mu\text{mf}$ . Condensers *C2*, *C3*, and *C8* may be either mica or ceramic condensers, although the latter are preferable from the size standpoint. Similarly, condensers *CA1*, *CA2*, *CA3* and *CB* should preferably be ceramic condensers, although mica condensers will work in most cases.

Note that condenser *CA1* (see *Coil Table*) is actually two condensers, 5  $\mu\text{mf}$  for the 6-meter coil and 5  $\mu\text{mf}$  for the 10-11 meter coil. Similarly, *CA3* is 50  $\mu\text{mf}$  for 6 meters and 50  $\mu\text{mf}$  for 10-11 meters. *CA2* consists of a 5  $\mu\text{mf}$  and a 10  $\mu\text{mf}$ -condenser in parallel for 6 meters, and a 25- $\mu\text{mf}$  condenser for 10-11 meters. For padding coil *B*, the 6-meter condenser *CB* is 25  $\mu\text{mf}$  and 10  $\mu\text{mf}$  in parallel, and for 10-11 meters *CB* is a 50- $\mu\text{mf}$  and a 25- $\mu\text{mf}$  condenser in parallel.

The next step in the construction of the converter is to study the photographs and diagrams. *Photograph B* clearly shows the side and the rear of the converter. *Photograph C* is a detail view of the radio-frequency section of the converter, and must be studied carefully before construction is begun. *Photograph D* is on under-side view.

*Fig. 2* gives the drilling details for the 4 x 4-

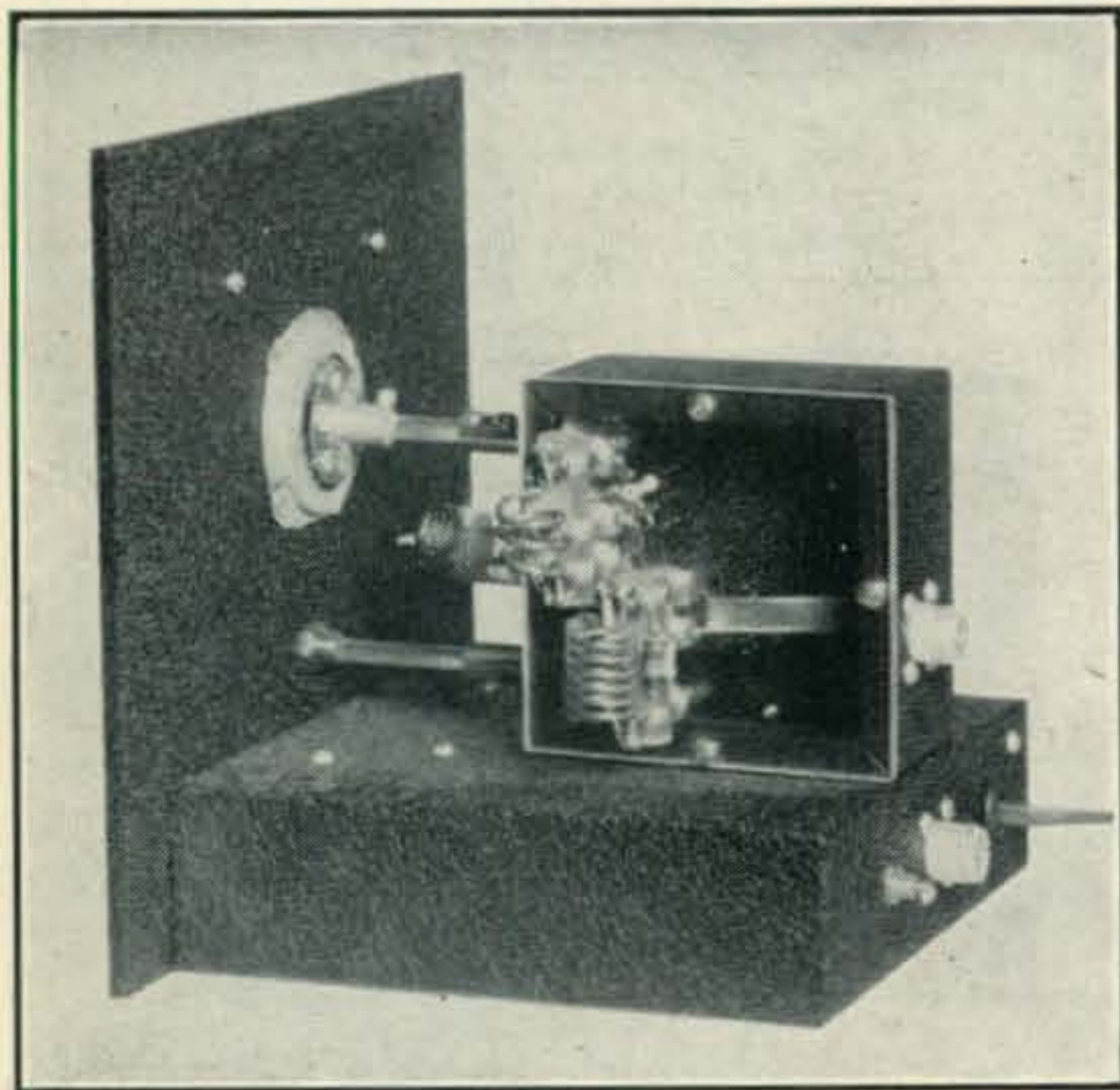

Photograph B. Right-side view of the converter. Because the coils are mounted on a piece of transparent insulating material, the inside of the r-f chassis is visible. The six-meter coils are in place.

inch polystyrene coil mounting board, and *Fig. 3* is the drilling layout for the top of the large chassis (*Fig. 3A*) and the drilling layout for the front panel (*Fig. 3B*). The *Coil Table* shows how to make the coils, and also gives the values for the condensers which are mounted on the plug-in coils.

Once the builder has read and understood this article, he is ready to start the actual construction. The first job is the construction of the radio-frequency chassis. The two sides should be removed from the 4 x 4 x 2-inch chassis, and the 4 x 4 x  $\frac{1}{4}$ -inch piece of polystyrene should be placed against the side of the chassis and the location of the four mounting holes determined. Following this, the six holes for the banana jacks should be carefully drilled as per *Fig. 2*. The size of these holes will be determined by the type of banana jack, but in most cases will be  $\frac{1}{4}$  inch diameter holes.

Next, refer to *Photograph C* and drill the holes for the miniature 9-pin socket and condensers *C1* and *C10*. All are mounted on the vertical center line of the front of the chassis, the two condenser centers being three-fourths of an inch up from the bottom and down from the top of the chassis, and the socket center being in the exact center of the front of the chassis. The two mounting holes for the socket flange should be in a horizontal plane, so that pins 1 through 4 are below and pins 5 through 9 are above. Mount two soldering lugs under each socket mounting screw, and scrape the paint where the socket fits against the chassis so that a good ground connection is made.

Drill the hole in the rear of the chassis for the coaxial connector, and the holes in the bottom of the chassis for mounting it to the main chassis. These holes are on the center line of the chassis and  $1\frac{1}{2}$  inches apart. The rear hole is  $1\frac{1}{4}$  inches from the rear of the chassis. A third hole  $\frac{1}{4}$  inch in diameter is also drilled in the bottom of the small chassis. This hole is  $\frac{1}{2}$  inch back from the front of the chassis and  $\frac{1}{4}$  inch in from the left side (as seen from the front of the panel).

The socket and the two variable condensers should next be mounted. The builder is now ready to begin the important part of the construction—that of the r-f section. For best results, follow the directions exactly, remembering that every lead should be as short as possible. It is a wise precaution to draw a pencil mark on the circuit diagram after completing a connection. This mark should be made directly over the line representing the connection just made, and preferably the marking should be done with a colored pencil. This type of record insures that all connections will be made. Refer to *Photograph C*, and proceed as follows:

Connect *R2* and *C7* in parallel, connecting one end to pin 3 and the other end to the lower ground lug on the right (as viewed from the rear). All

directions mentioned will be as viewed from the rear, that is, as in *Photograph C*. The pin numbers shown in the circuit diagram refer to the location of the socket pins as viewed from the bottom of the socket. Looking at the bottom of the socket, the first pin clockwise from the gap between the pins, is pin 1. The pins are then numbered 2 through 9, going around clockwise.

Connect the rotor of *C1* to the lower ground lug on the left. Connect a one-foot piece of wire to pin 6, push it up under *C10* and bring it down along the right side of the chassis and out the  $\frac{1}{4}$ -inch hole. Connect *C6* to pin 6 and ground the other end to the upper ground lug on the right. Connect *R5* to pin 7 and ground the other end to the upper ground lug on the right.

Connect pin 4 to pin 5 and connect another one-foot piece of wire to this junction, running the wire in the same place as the other wire. Connect *C3* to pin 1 and ground the other end on the lower ground lug on the right. Connect a one-foot piece of wire to pin 1 and run it down and out the  $\frac{1}{4}$ -inch hole. Connect a wire to the center post of the tube socket and run it to pin 9 and then to the upper ground lug on the right. Connect *R1* to pin 2, and ground the other end to the lower ground lug on the left.

Connect *C2* to pin 2 (by attaching it to the lead of *R1*) and connect the other end to the stator of *C1*. Connect *C9* to pin 7 (by attaching it to the lead on *R5*) and connect the other end to the stator of *C10*. Connect the rotor of *C10* to ground by soldering it to the upper ground lug on the left.

Next, put the six banana jacks on the 4 x 4-inch polystyrene piece, placing a large soldering lug under each jack, with the lug facing toward the rear. The top jack of *coil A* should have two soldering lugs on it, one facing the front and the other facing the rear. Fasten the polystyrene piece to the small chassis, as shown in *Photograph B*.

Connect a wire from the bottom jack of *coil B* to the top jack of *coil A* (the two closest jacks) and bring this wire to the lower ground lug on the left. Use as little heat as possible in soldering to the jack lugs, to prevent the polystyrene from melting. Connect the top jack of *coil B* to the stator of *C10*. Connect the bottom jack of *coil A* to the stator of *C1*. Connect pin 8 to the middle jack of *coil B*. Cut the 300-ohm twin-conductor cable to the proper length, and connect one lead from the middle post of the coaxial connector to the middle jack of *coil A*. The other lead goes from a ground lug on the coaxial connector to the top jack of *coil A*. Connect *C8* to pin 5 and the other end to the upper ground lug on the right. Tighten the banana jacks which may have loosened.

The wiring is now complete on the r-f chassis, and it may be put aside for assembly later. The remainder of the wiring is not critical, and for that reason detailed instructions will not be given. If the circuit diagram has been marked as mentioned before, it is apparent that there are very few connections yet to be made.

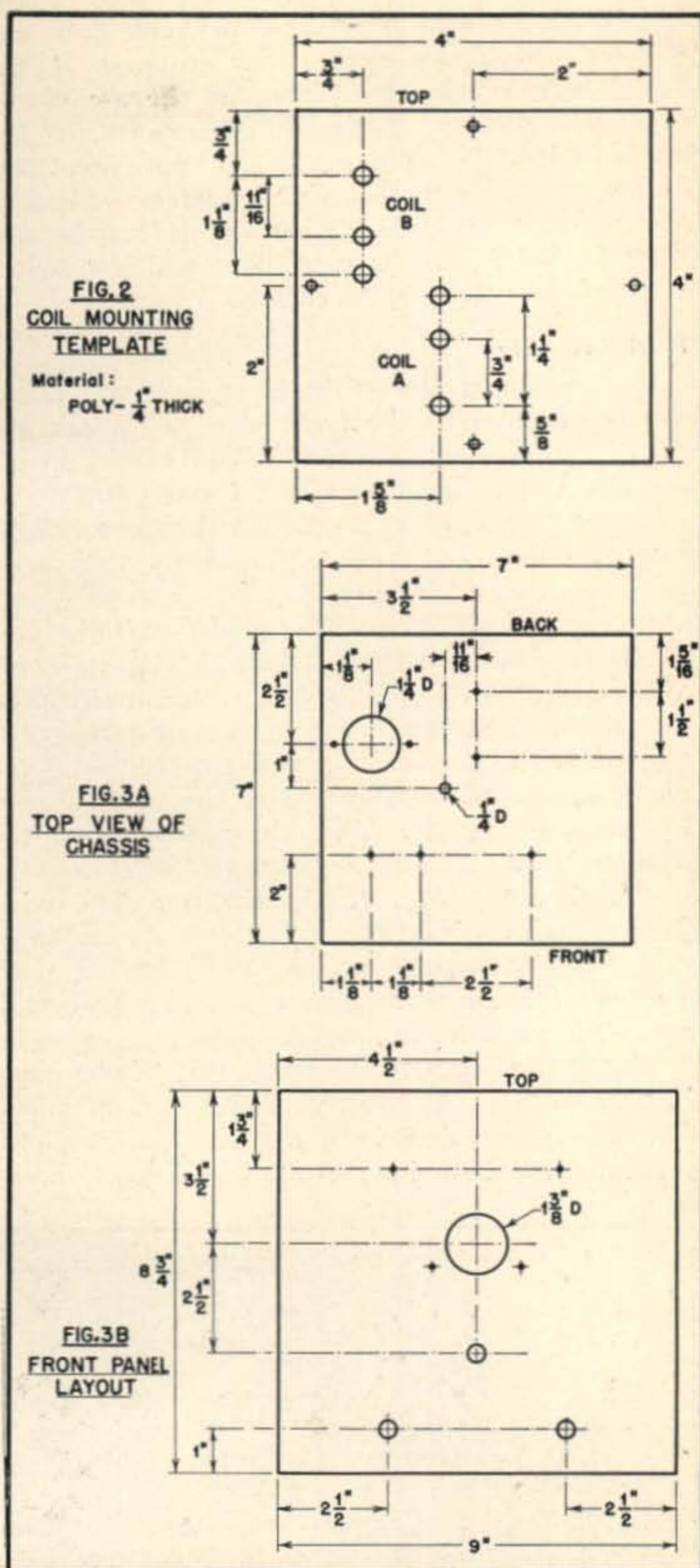


Fig. 2. Drilling details for the coil-mounting board.  
Fig. 3. Chassis and front-panel drilling layout.

The large 7 x 7 x 2-inch chassis should now be drilled on the top as shown in *Fig. 3A*. The rear should next be drilled as shown in *Photographs B* and *C*. The coaxial connector is in the exact center, condenser *C4* is two inches in from one side and the a-c cord hole is  $1\frac{3}{8}$  inches in from the other side. Next, place the small chassis temporarily on the large chassis, and check to see if the two shafts for *C1* and *C10* fall as specified in *Fig. 3B*. Drill the front panel as shown in *Fig. 3B*. If the panel is Masonite or similar material, the  $1\frac{3}{8}$ -inch hole will cause no trouble. However, if a metal panel is used, the builder might find it necessary to borrow a socket cutter or punch.


Place the front panel against the large chassis and locate the hole centers for the pilot light and the a-c switch. Referring to *Photograph A*, the screw between the pilot light and the a-c switch is used to hold a clamp which supports the a-c cord under the chassis. It is not necessary, although it adds to the wiring neatness. Remove the small chassis and complete the drilling by cutting the holes for the pilot light and a-c switch in the front of the large chassis.

#### Final Assembly

Put the tuning dial on the front panel and fasten the front panel to the large chassis. Mount the small chassis. Cut the  $\frac{1}{4}$ -inch rod to the proper lengths and use as shafts for *C1* and *C10*. Mount *C11*, rectifier *X*, transformer *T* and the fuse block. Refer to the various photographs for details on this mounting procedure.

Cut a  $1\frac{3}{4}$ -inch piece from the half-inch diameter polystyrene rod length and drill and tap one end. Wind 11 turns of No. 18 wire on the top end of this form, as shown in *Photograph D* and as explained in the parts list. Screw this coil onto the rear machine screw which holds the small chassis to the large chassis. Wire the remainder of the converter, by referring to *Photograph D* and the circuit diagram, *Fig. 1*. As the last step, wind four turns of insulated wire around *L1* and connect this wire to the coaxial connector, one lead going to the center conductor and the other to a ground lug on the connector.

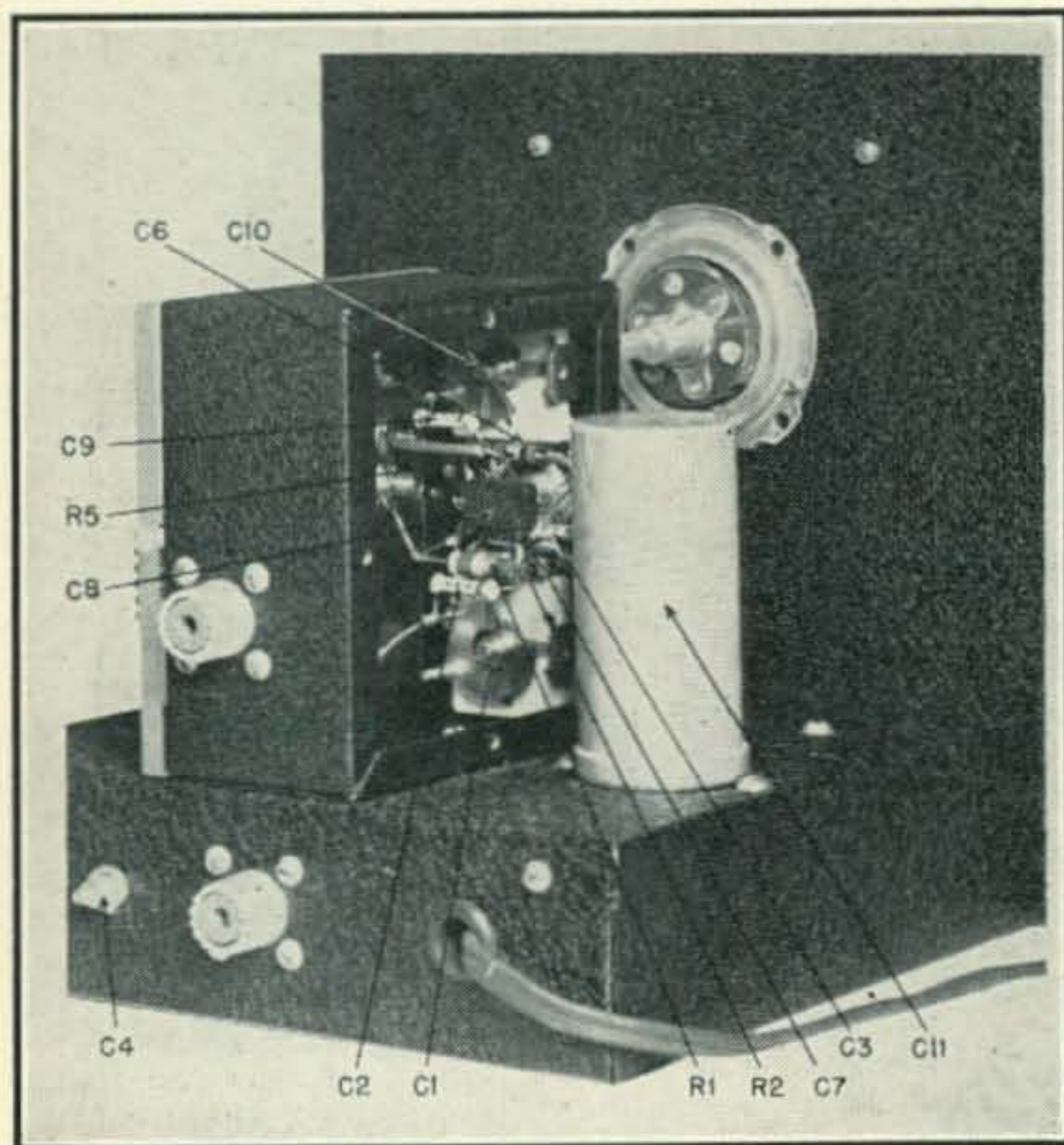The final constructional job is that of the plug-in coils. Cut the polystyrene rod as shown in the *Coil Table*, and drill holes for the banana plugs. Note that *coil A* and *coil B* are of different dimen-



Photograph C. Detail view of the inside of the r-f chassis. Component parts are marked as an aid in identification. The short leads resulting from this type of construction add to the converter efficiency.

sions and the banana plugs are spaced differently. Wind the coils as shown and solder the proper condensers across the coils as shown in *Photograph B*. After soldering, tighten the banana plugs so that the softened polystyrene can flow around the screw and hold it tightly.

#### Converter Testing

Connect the converter to the a-c line as explained previously, and turn on the a-c switch. The filament of the 12AT7 should be visible. If a voltmeter is available, measure the voltage from chassis to the junction of *R3*, *R4* and *R7*. The voltage should be approximately 100 volts. If it differs materially from this figure, turn the converter off and check the wiring.

The next step is to connect the converter to a receiver. A piece of coaxial cable (as short as possible) is best, although other types of shielded wire will serve. Do not use wire which is not shielded as the unshielded wire will serve as an antenna for the receiver, and cause undesired signals to be heard. If a 6-meter transmitter is available, plug in the 6-meter coils, or if a 10-meter transmitter is available, use the 10-11 meter coils.

Turn on the receiver and converter and let them warm up for several minutes. Do not put an antenna on the converter. Tune the receiver to 14 mc. Turn on the receiver b.f.o. Set *C1* on the converter to approximately mid-scale. Turn on the transmitter after removing the transmitting antenna, and tune the transmitter final to resonance. The transmitter is now putting out a signal which will be used as a tune-up signal.

Tune the main dial on the converter until a signal is picked up. Reduce the r-f gain on the receiver until the signal is just audible, and peak this received signal by adjusting *C4*. If a signal is not heard when the main tuning dial has completely covered the condenser tuning range the oscillator is not covering the proper frequency range, or is not oscillating. Check the connections and the coil. Once the oscillator is made to oscillate the frequency of oscillation can be varied by pushing the turns together on *coil B*, or pulling them apart. This is not advisable unless the builder is certain that the oscillator is on the wrong frequency.

When the transmitter signal can be received and the i-f tuning (*C4*) has been completed, *C1* can now be adjusted for maximum signal strength. Make a mental note of this position, as the tuning of this control will not change much when using any one set of coils.

The next step is the calibration of the main tuning dial. This is most easily accomplished by borrowing a variable frequency r-f generator, such as a v.f.o. Set the r-f generator on the frequency the transmitter had been on and without connecting it to the converter in any way, see if the converter will pick up the signal. If not, it will be necessary to couple it into the antenna input of the converter.

Set the frequency of the r-f generator at one

| COIL TABLE                             |        |        |
|--|--------|--------|
|  | COIL A | COIL B |
| GENERAL CONSTRUCTION                   |        |        |
| 6 METERS                               |        |        |
| 10-11 METERS                           |        |        |
| CAPACITANCE EXPRESSED IN $\mu\text{f}$ |        |        |

end of the band and tune the main dial until this signal is picked up by the converter. The front of the dial can be removed so that a pencil mark can be made on the dial face. Continue this process in half-megacycle steps until calibration is complete. It may be found that the amateur band does not center on the dial. This may be corrected by squeezing the coil turns on *coil B* together, or pulling them farther apart. If, for example, the 27-mc point is too far toward the center, that is, the band is moved too far to the right, the turns on *coil B* should be pulled apart. Conversely, if the band is shifted toward the left, the coil turns should be squeezed together. This handling of the coil turns should be done a very slight amount at a time, so that the frequency is not changed too much.

After calibration, it is desirable to check for "pulling" of the oscillator frequency by the mixer. This should not occur if the schematic was followed faithfully. With a signal tuned in, control *C1* should be changed so that the signal is weaker in the receiver. The main tuning dial should now be retuned for maximum signal strength. If a change in signal strength can be effected by the main tuning dial, then the oscillator frequency is being changed when *C1* is tuned. If this effect is serious, the oscillator voltage should be reduced by increasing *R4*.

#### Antenna Adjustment

The importance of an antenna cannot be stressed too greatly. All receiving devices depend upon the antenna to pick up a signal, and the best receiver will not function without an antenna. Efficient antennas for 6 and 10 meters are easy to construct. If a transmitting antenna is available, this may be employed for reception by using a double-throw double-pole switch or relay.

The best antenna is at a disadvantage unless it is matched to the receiver. It is for this reason that *coil A* is designed with an antenna matching network. To adjust this network, tune in a steady signal which is being received on the antenna. Do not use a source of r-f in the shack, as most of this energy will not come in the antenna. One of the local hams may be willing to put his transmitter on the air and talk to you (when the band is closed) while you adjust the converter.

When the signal is received, peak up *C1* and tune the receiver for the best signal strength. Turn down the audio gain until the signal is just audible. Next, place a 10- $\mu\text{f}$  condenser in parallel with *CA3* on the coil in use. If this brings up the audio, repeat with a larger condenser, such as a 25- $\mu\text{f}$  condenser. Experiment until the audio is as loud as possible. If the addition of capacitance does not increase the audio level, replace *CA3* with a 10- $\mu\text{f}$  condenser, then again add capacitance in parallel. The range of capacitance should be between 10 and 150  $\mu\text{f}$ . Some value in that range should cause the converter to best match the antenna and feeder system.


Because the audio level may change appreciably as the above tests are made, and yet not be too noticeable to the ear, a more sensitive test would be to measure the audio output of the receiver with an output meter. Of course, a steady modulation would be required on the received signal. If the receiver has an S-meter, this would be even more sensitive as a peaking device.

#### Final Notes

If a standby switch is desired, which will remove plate voltage from the converter, but leave the filament hot, this may be added between *X* and *R6*.

No IN-OUT switch is provided on this converter, as the design would have become more complicated.

(Continued on page 87)

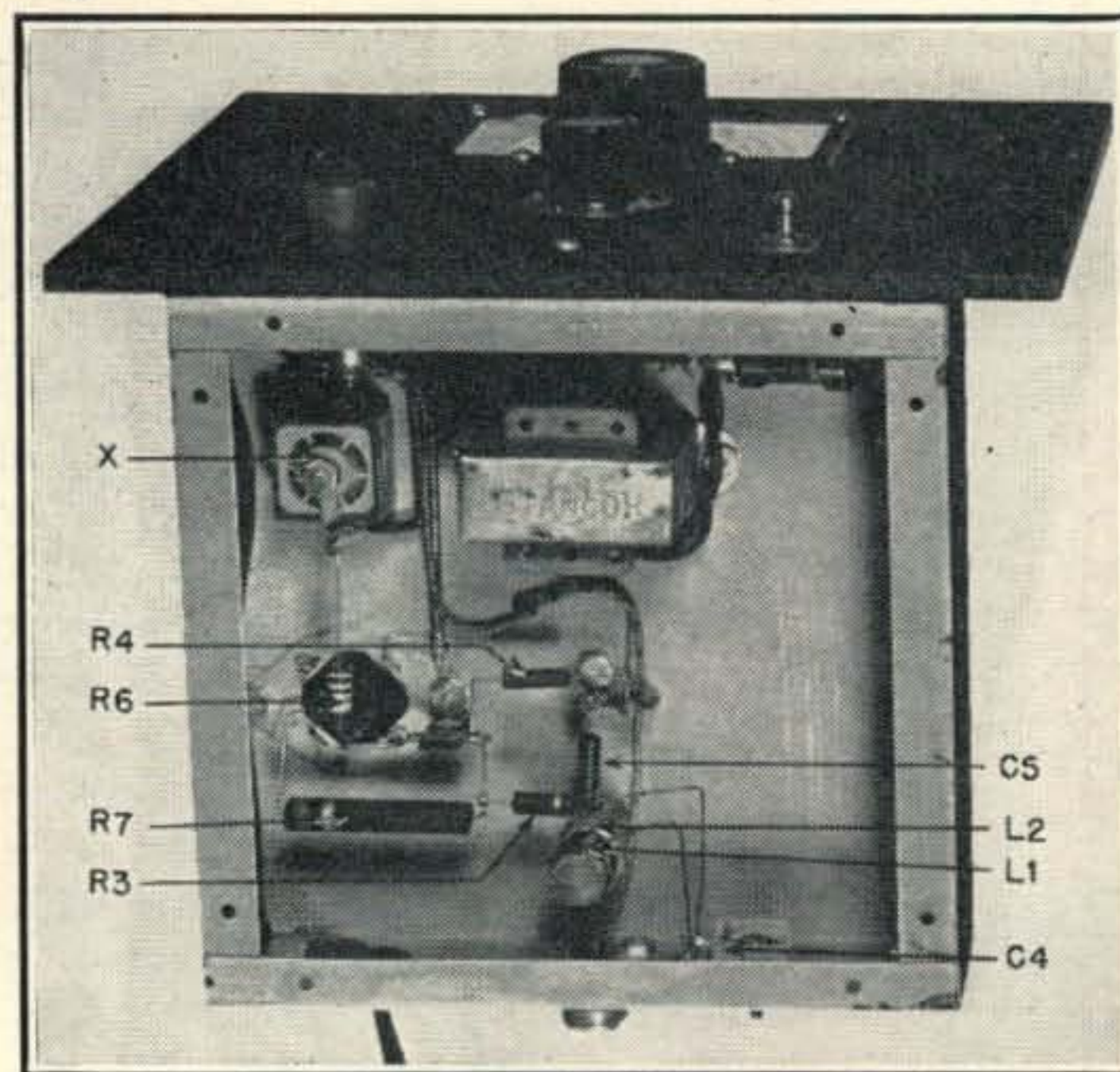

Photograph D. Underside view of the converter. There is very little wiring required because most of it is in the r-f section.

# Land of Sunshine--and YLs

LOUISA B. DRESSER, W2OOH\*

## CQ's YL Editor reports on a visit to the W6s

**C**ALIFORNIA, here we come—land of sunshine, kilowatts—and *really* hospitable YLs! Our five-day visit, during which we attended the Southwestern Division Convention, October 2 and 3, and met many of the YLs in the Los Angeles area, was packed with activity.

How did this W2 happen to be in California? Well, it was essential for the OM, W2IU, to attend the I.R.E. West Coast Convention in Los Angeles the end of September, and a little persuasion convinced him that it would be a golden opportunity for the XYL to go along so we could both take in the amateur convention, too, and get a little vacation, as well.

The latter evolved into several days' stopover at Grand Canyon—a la the great American tourist! After marveling at this magnificent freak of nature from its rim and depths, we were further impressed with its grandeur by flying directly over the entire length of the Canyon to Lake Mead and Hoover Dam before heading across the Rockies to California. Climbing steadily higher to their crests, suddenly the mountains dropped sheer, and verdant San Bernardino Valley lay before us extending mile on mile to the Pacific, its rich cultivated land and oil fields strewn with cities clustered around the heart that is Los Angeles. Checking in at the Biltmore that evening, September 28, produced a deluge of notes, messages and phone calls—a royal welcome from the YLs!

### Visiting Ham Shacks

Thursday morning, bright and early, we hastened to Santa Monica to meet Vada Letcher, W6-CEE, who was to be our "official" hostess for the day. Vada first drove us to see Maxine Willis, W6UHA, president of the Los Angeles YL Club. There we enjoyed a long rag-chew, and Maxine served a delicious luncheon (umm, such strawberry shortcake that gal makes; OM W6TS certainly is lucky!) Then we put W6UHA on 10 phone for VK and ZL contacts for the fun of working DX from the West Coast. Running 900 watts, using a rotary beam, and having practically noise-free reception, Maxine is a consistent DXer.

Later Vada took us to visit Helene Leonard, W6QOG ("Helen with an e on the end," as she lighly explained on phone). Helene and OM W6MBD just about live ham radio, as one might guess from their elaborate set-up. Each has a complete station containing a roomful of equipment, in separate rooms connected by intercom, with the

overflow (2-meter gear, etc.) accumulating in the living room!

After several 100 per cent qsos on 10 from W6MBD (with signal reported as 40 db above S9!), Vada took us to her home QTH in Venice where she and OM W6HWM also operate mostly on 10—when TVI, which all of the girls complained of, isn't too serious. Vada, formerly from Nebraska, loves the social side of ham radio, but took her hamming seriously enough to attend night school last year in order to achieve that coveted ticket.

Last call for the day was to Compton to visit Clara Dishong, W6TDL, her QTH being readily located by spotting her looming 10-meter beam. Clara is one amateur who almost welcomed TVI for, after months of time-consuming sessions of handling traffic for GIs overseas, she is glad to take a brief rest from transmitting (she still listens for DX) while she and her OM rebuild the station in a new shack apart from their house.

Naomi Turk, W6YZU, who lives near by, came to join the rag-chew and brought her youngest jr. op, only a few months old. We marvel at Naomi when we think of her making W.A.Z. (the only YL to do so to date), the while taking care of four jr. ops! Between W6YZU and OM W6-LEE, there is a real DX household.

On the following day, Friday, Lenore Conn, W6NAZ, met us in Hollywood and showed us the famous Hollywood and Vine (and Sunset), and the broadcast studios, including NBC where she is an actress. For some time Lenore has had her own television show Sunday evenings for which she does the researching and writing, and plays the lead, too—aren't we proud of her! Oh, yes, both she and OM W6MSC have TVI at home, but still they both love working at television professionally. And the TVI doesn't prevent them from arranging numerous skeds between GIs out on the Pacific Islands and their families back home.

After lunch at the Brown Derby, Lenore drove us to see Carol Witte, W6WSV, in South Pasadena, whom we hadn't visited except via correspondence since the early war days back at A.R.R.L. Formerly W9WWP in Chicago, Carol had worked for the Navy Department in Washington, D. C., before becoming a member of the staff at QST, then leaving West Hartford to join the Waves. Now living in an apartment where no antennas are allowed on the roof, Carol and OM W6WSW

(Continued on page 88)

\*Assistant Editor, CQ.



Above: YLs participating in Tom Regan's "Community Broadcaster" program over KXLA. L. to r., standing: Lenore, W6NAZ; Rosemary, W6PJF; Clara, W6TDL; Maxine, W6UHA; W2OOH; Helene, W6QOG; Violet, W6CEE; Eleanor, W6AAL, and Mary, W6AVF. Seated: Johnny, W6PAP; John, W6BKY; Tom Regan, and ARRL Vice President McCargar, W6EY.



Above: L. to r.: Evelyn, W6NZZ, in charge of convention YL activities; Rosemary, W6PJF, 6th district YLRL chairman; Maxine, W6UHA, president of the Los Angeles YL Club. All YLRL members wore identifying leis during the Southwestern Division Convention.



Left: Gathering for the YL luncheon. L. to r.: Bertha, W6MA; Clara, W6TDL; Verma, W6JOJ; Ida, W6BIS; Carol, W6WSV; Ruth, W6WQK; Louise, W6VWR.



Left: Jessie, W7TBR, and Gertrude, W7KOY, from Phoenix, Arizona. Inset: Florence, W6AET.



Above: visiting YL nam snacks included visiting jr. YLs. Left: Ruth, W6WQK, holding Jerlyn, and right, Carol, W6WSV, with 4-month old Marcia.




Above: rag-chewing before the luncheon. L. to r., standing: two XYLs, and Maxine, W6UHA. Seated, Vada, W6CEE; Marie, W6SPX; Violet, W6CEE; Mary, W6AVF; Enid, W6UXF; two XYLs, and Clara, W6TDL.

Right: "Round-up" following the luncheon. L. to r., standing: Naomi, W6YZU; W2OOH; Ruth, W6WQK; Vada, W6CEE; Wilma, W9POZ/6; Marie, W6SPX; Eleanor, W6AAL; Jessie, W7TBR; Verma, W6JOJ; Enid, W6UXF; Clara, W6TDL; Mary, W6AVF; Maxine, W6UHA; and Louise, W6VWR. Seated: Lenore, W6NAZ; Rosemary, W6PJF; Helene, W6QOG; Ida, W6BIS; Evelyn, W6NZZ; Neva, W6YXI, and Carol, W6WSV.



Convention photos courtesy W6NAZ.

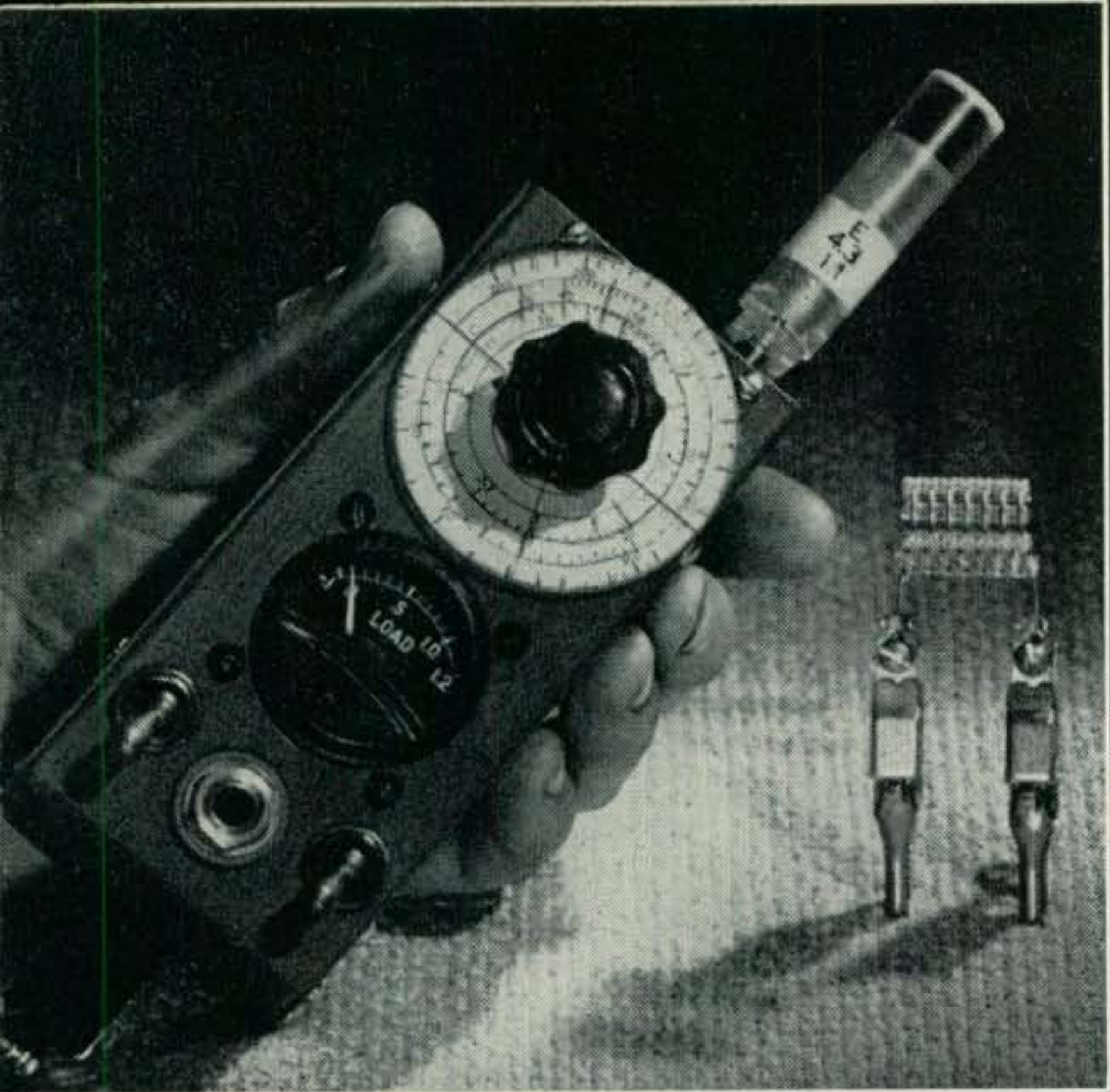

# Applications of

WILFRED M. SCHERER, W2AEF\*

Typical grid-dip oscillator with a continuous tuning range of 2 to 300 mc, this improved self-contained model of W2AEF's Dipper will be described in February.

**R**ESPONSE TO THE author's description of the "Dipper" and W6WB's grid-dip oscillator story has been tremendous. This instrument is fast becoming more popular as an indispensable and necessary piece of equipment for the radio amateur or engineer. A good many inquiries have been received asking for more detailed information pertaining to its applications. This article describing the uses of the grid-dip oscillator is in response to this widespread interest.

Although the operation of the Dipper, and it may be considered a typical grid-dip oscillator, has previously been described,<sup>1</sup> it might be well to briefly review its employment as four different basic instruments.

1. *Grid-dip oscillator (g.d.o.)* for use as an oscillating frequency meter to determine the resonant frequency of de-energized r-f circuits.

Plate potential is applied to the g.d.o. and it becomes an r-f oscillator. A d-c meter in the grid return indicates relative power. When a circuit, resonant at the oscillator frequency, is coupled to the "probe" inductance, power is absorbed from the oscillator by the resonant circuit and is so indicated by a dip (decrease) in the grid meter reading. The Dipper, employed in this manner, may then be used to check the resonant frequency of a circuit *without the application of power to the circuit in question*. This results in a considerable saving of time, and a definite assurance of correct frequency adjustment of a circuit is obtained. Circuits may be checked or pretuned before completion of the unit in which they are to be used. Only minor trimming is generally required under actual operation. Guesswork or "cut and try" methods are eliminated. Possible damage to components during initial tune up and adjustment is eliminated.

\*100 E. Palisade Ave., Englewood, N. J.

1 Scherer, "The Dipper," *CQ*, May 1947.

Bane, "About Grid-Dip Oscillators," *CQ*, March, 1947.

2. *Oscillating detector* for determining the fundamental or harmonic frequencies of energized r-f circuits.

Plate potential is applied and the instrument is again an r-f oscillator. Instead of observing the grid-meter reading, a pair of phones is inserted in the phone jack and an audible beat may be heard when the instrument is tuned to the fundamental or harmonic frequency of a source of r.f. The frequency may be read directly from the calibrated dial.

3. *Tuned r-f diode or non-oscillating detector* for use as an absorption-type frequency meter. No plate potential is applied and the internal tube is used as a diode. The grid meter is then in the diode load circuit and will read up-scale (current increase) when the instrument is tuned and closely coupled to a source of r-f energy.

4. *Signal generator*. The g.d.o. may be employed for this purpose generally in place of a standard signal generator, except where special shielding or a known r-f output voltage is required.

## Methods of Coupling

Correct methods of coupling the Dipper to circuits under test are shown in *Fig. 1*. When used as a g.d.o., harmonics of lumped-constant resonant circuits will not be indicated; however, other resonant frequencies are sometimes indicated. These will be due to other resonant circuits formed by circuit wiring, stray capacitances, etc. In most cases these will occur at a higher frequency. On the other hand, harmonics of antennas, transmission lines, etc., will be indicated as will be explained later in the text under the heading "antennas."

When looking for the grid dip, it will be noted that the grid current reading slowly varies as the Dipper frequency dial is rotated; however, correct resonance is indicated when the meter takes a sharp or pronounced dip.

It is suggested that the user of the Dipper at first set up test *L/C* combinations, short test antennas, etc., and check them with the instrument in order to become familiar with the coupling methods and with the general behavior and operation of the unit.

## Applications

*Receiver tuned circuits*. Use the Dipper as a g.d.o. Remove power from the receiver and resonate each tuned circuit to the desired frequency as indicated by the meter dip. Gang tuned circuits should be aligned for tracking by checking at each



# the Grid-Dip Oscillator

**How many amateurs are completely overlooking the countless uses of this easily built piece of test equipment? If you think your shack is complete without one, just read on.**

end of the ganged range. A check at one or two points in between will also be helpful. Methods of electrically obtaining the desired bandspread or tracking will not be explained here. Reference may be made to any good radio text book.

Following the above procedure, power may be applied to the receiver and the g.d.o. employed as a signal generator for checking final alignment. A very short antenna should be connected to the receiver input terminals and the Dipper should be placed on the bench removed from nearby conductors, and where body movements are least apt to affect the r-f signal from the instrument. Some sort of indicating device such as an "S" meter or v.t.v.m. at the receiver detector must be used. Where this is not available, tone modulation may be applied to the Dipper and alignment made according to aural indications. If the r-f signal is too strong, the receiver antenna may be shortened, or the Dipper may be removed to a more remote or partially shielded location.

Where a superheterodyne type of receiver is involved and, if the receiver fails to function, it is quite possible that the receiver local oscillator is not working. This may be checked by employing the Dipper as an r-f diode detector or absorption-type wave meter. Couple it to the oscillator coil and, if the meter does not go up-scale when the instrument is tuned to the resonant frequency of the oscillator tank, the oscillator is not functioning. An alternative method having greater sensitivity and capable of more accurate frequency measurement is to use the Dipper as an oscillating detector and listen for the local oscillator beat in the headphones.

**Transmitter tuned circuits.** Use instrument as g.d.o. with plate power removed from transmitter and proceed to adjust tanks to desired frequency as done with receiver circuits. Tubes should be in place, and where capacitive coupling is used between stages, the grid circuit associated with the following tube should be completed.

After the above procedure, plate power may be applied and final alignment made according to grid and plate meter indications. R-f power at correct frequency in each tank may be checked by employing Dipper as diode absorption frequency meter, or it may be utilized as an oscillating detector. Due to its greater sensitivity in the latter state, care must be exercised not to mistake audible beats from some other energized r-f circuit. This may be checked by moving the instrument closer to the circuit under test and noting whether or not the

beat increases in volume. If it does, the beat heard is from the desired circuit. Harmonics also may be heard, so it is wise to check for the beat heard at the lowest frequency.

**Neutralization.** Use Dipper as diode absorption-type meter and proceed to neutralize in the manner normally employed when using absorption-type wavemeter, or as with similar indicating device, i.e.:

Remove plate power from amplifier stage to be neutralized, and apply power to stage driving the grid. Loosely couple the Dipper to the amplifier tank, tune the instrument to the driving frequency and check for the presence of r.f. in the tank as indicated by a rise in the Dipper meter current. Adjust neutralizing capacitor until no reading is seen on the meter.

Another method may be utilized when employing the instrument as a g.d.o. Remove all plate power from the transmitter. Couple Dipper to grid tank of stage to be neutralized, or, in the case of capacitive coupling, to the preceding plate tank (it is assumed that the tank has already been tuned to correct frequency). Couple fairly close and leave Dipper set in position with its meter deflected at bottom of the resonant dip. Neutralization is then indicated when rotation of amplifier plate tank capacitor has no reaction on the deflected meter reading.

**Parasitic oscillations.** Apply power to transmitter and use Dipper as oscillating detector while listening on headphones for beat of parasitic oscillation. When parasitic frequency has thus been determined, as read from the Dipper scale, remove power from transmitter and use instrument as g.d.o. to locate circuits or components, such as r-f chokes, circuit wiring, etc., resonant at parasitic frequency.

**Parallel resonant traps.** Use Dipper as g.d.o. Trap may be tuned or checked either before or after connecting it in desired circuit. If tuned be-

To ensure that the desired circuit is being measured by the g.d.o. the g.d.o. should be suitably coupled and the frequency varied until the dip is obtained. Then moisten one finger with saliva and touch an ungrounded point on the test circuit. The g.d.o. meter should indicate a change in resonance. Lack of g.d.o. meter reaction when the test circuit is touched indicates that the indicated resonance is of another circuit. Be sure power is off before touching test circuit with finger.

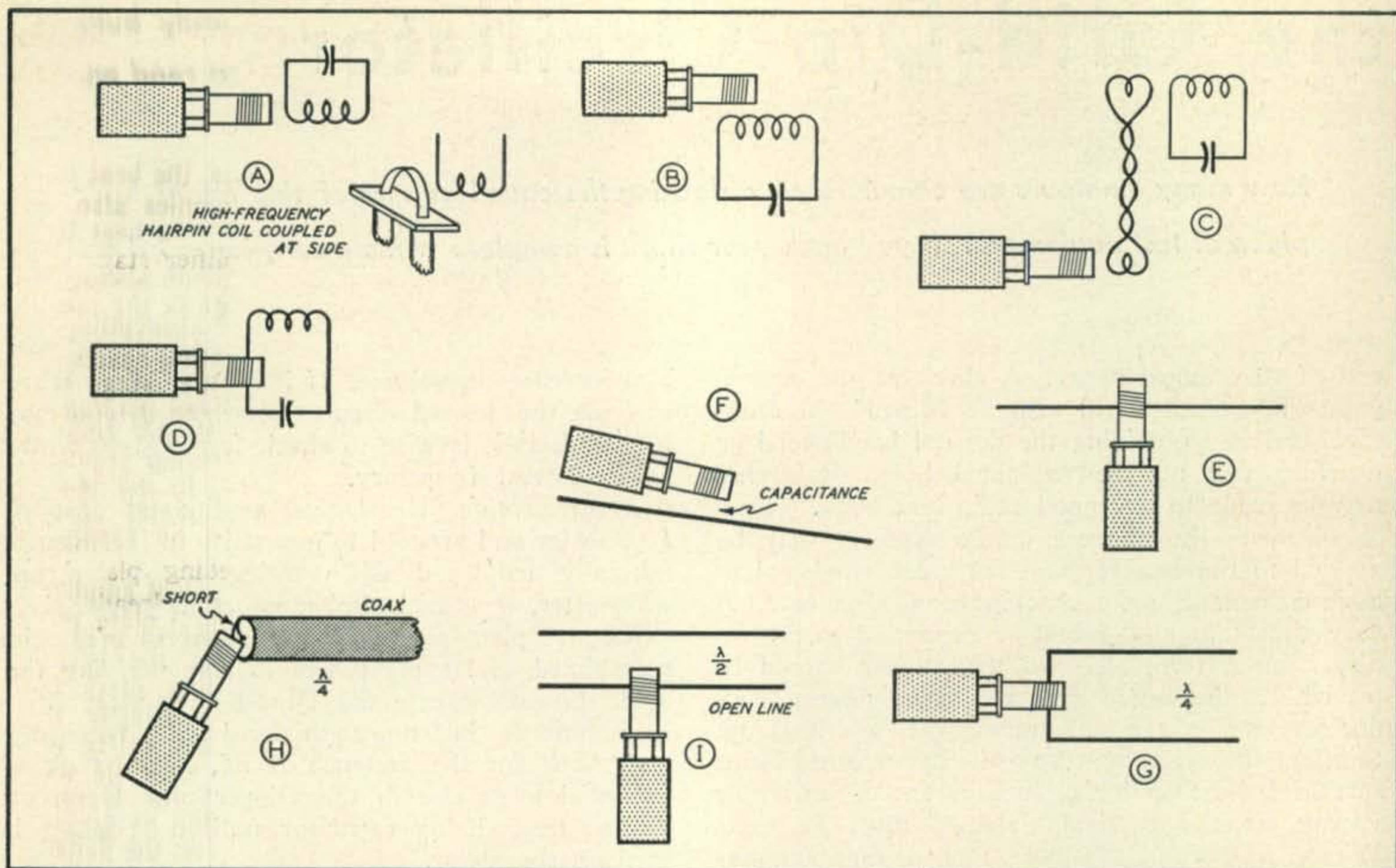


Fig. 1. Proper methods of coupling the Dipper to circuits under test. Wherever possible use method shown at A. Method at B should be used as an alternate. If the coil is so located (such as in a shielded can) that normal coupling methods cannot be used, link coupling as at C may be used, or sufficient coupling may often be made to an ungrounded lead from the inductance as at D and E. If several coils are located at close proximity and prevent accurate readings, short out the undesired inductances. As an additional precaution to check measurement of desired circuit, detune it to confirm readings. Inductive coupling shown at E should be used for antennas or any other straight wire. Capacitive coupling for this purpose is shown at F. Use G for shorted quarter-wave open lines (or odd multiple thereof). For quarter-wave shorted coax lines use H. For open or shorted half-wave lines use I. For half-wave coax lines see text. In all cases, greatest accuracy is realized when coupling is as loose as possible, consistent with obtaining sufficient indication of dip.

fore installation, adjustment will remain correct upon installation if its inductance is physically removed from other conductive components which may alter the inductance value. This is not usually the case, so further minor adjustment will probably be required after installation. When in the circuit, it is possible that its resonant frequency may be quite a bit off as indicated by the Dipper. Actually the trap itself will still be tuned to approximately correct frequency but the g.d.o. reading may not be obtainable due to stray capacitance across the trap having a circuit  $Q$  higher than that of the trap itself. This tends to swamp out any reading obtainable with the meter; however, an effective trap should have good  $Q$  and high  $C$ , in which case, correct reading will be observed.<sup>2</sup>

Final precise adjustment may be made by applying power to circuit and by tuning trap under actual operation for desired effect. In many cases this will not be necessary as pretuning is quite accurate.

**Series resonant traps.** Follow same general procedure as with parallel resonant traps. To check or tune prior to installation, trap may be first connected as a parallel trap. At high frequencies or

where the trap inductance is low, the lead completing the parallel circuit should be of large wire or wide copper ribbon to keep its inductance low, and care should be taken not to permit this lead to be positioned so as to add stray capacitance. Leads to be used upon final installation must also be included when external measurements are being made.

**Measure circuit  $Q$ .** Use the Dipper as signal generator. Connect a v.t.v.m. across the circuit to be measured. Couple instrument to circuit (Fig. 1A) and resonate for maximum or peak reading on v.t.v.m. Note frequency at which this occurs. Then shift the Dipper each side of resonance to the frequency where the voltmeter reading drops to approximately 70.7% of that at resonance. Note the frequency of these two points and calculate the

circuit  $Q$  from  $Q = \frac{f_r}{\Delta f}$ , where  $f_r$  is the resonant

frequency and  $\Delta f$  is the difference between the "off resonance" frequencies just found. The original coupling of the Dipper should be adjusted for a convenient maximum reading on the v.t.v.m. and then should be left fixed at this position for the remainder of the procedure.

When the circuit  $Q$  is quite high, it may be

necessary to check the Dipper frequencies with a calibrated receiver, because the "off resonance" points will occur too closely together for accurate reading on the instrument scale.

*Relative circuit Q* at a given frequency. Use Dipper as g.d.o. and observe character of the dip—whether broad or sharp. The sharper the dip, the higher the *Q*.

*Measurement of capacitance.* Several methods may be employed. All involve the use of the Dipper as a g.d.o.

The most generally useful method requires preliminary calibration using each of the Dipper coils. A small jig must be made (Fig. 2) into which may be plugged any one of the coils. Capacitors of known value are connected across the coil by means of the alligator clips. Then the resonant frequency resulting from the combination of each known capacitor and each coil is recorded.

An alternative method of calibration is to connect the jig and coil across an accurately known small mica capacitor of 1000  $\mu\mu\text{f}$ . Find resonant frequency and mark a point at this frequency coinciding with 1000  $\mu\mu\text{f}$  on a chart—double logarithmic paper should be used. Then mark a point corresponding to 250  $\mu\mu\text{f}$  at twice the resonant frequency just found. Place another mark at a point corresponding to 62.5  $\mu\mu\text{f}$  at four times the original frequency. Place a fourth mark at a point corresponding to 4000  $\mu\mu\text{f}$  at one half the original frequency. Draw a line between the four points and calibration will be complete. A typical chart, showing calibrating points, is shown in Fig. 3. Due to the distributed capacitance of the coils, a slight error will be encountered at very low capacitance measurements. Likewise, due to self inductance of large capacitors, a small error will be found when measuring these. Errors will be negligible for most practical purposes.

Measurements below 50  $\mu\mu\text{f}$  are generally not obtainable because resonance at these values usually falls out of range of the coils left available for frequency checking. If lower capacitance range is desired, then make a separate coil with alligator clips so any one of all the Dipper coils will be available for finding resonance. The one shown in the photograph consists of 7 turns of a B & W 3002 Miniductor. This will permit continuous frequency coverage together with complete capacitance coverage of from 5  $\mu\mu\text{f}$  to .01  $\mu\text{f}$ .

To check an unknown capacitor, it is then only necessary to clip the jig, with a coil inserted, across the unknown value component. Find the resonant frequency and refer to the calibration chart for value of capacitor with the coil employed. For over-all accuracy, it is best to employ one of the coils from the medium frequency range. When using the jig or "standard inductance," the alligator clips should be connected as near as possible to the unknown capacitor itself. Even a short lead from the capacitor will add inductance and cause a slight error.

For these measurements, in a great number of cases, the capacitor need not be removed from the

circuit in which it is wired unless the capacitor is heavily loaded.

Another method, similar to that above, is to employ a known inductance and find the resonant frequency with the unknown connected across it.

Then  $C_x = \frac{1}{4\pi^2 f^2 L}$  where *f* is the resonant frequency in cycles and *L* is the inductance in henries.  $C_x$  will be in a farads.

A third method, for capacitors up to about 1000  $\mu\mu\text{f}$ , requires an inductance which is shunted by a calibrated variable capacitor. The capacitor is set at maximum and the resonant frequency of the circuit is found. The unknown capacitor is then connected across the variable and the capacitance of the latter is decreased to a point where the circuit resonates at the original frequency. The difference between the first and last settings of the calibrated variable capacitor is the value of the unknown.

*Measurement of inductance* of r-f coils. Connect a capacitor of known value across the coil and use the Dipper as a g.d.o. to find the resonant frequency of the resulting *L/C* combination. The inductance of the coil may be calculated from

$L_x = \frac{1}{4\pi^2 f^2 C}$  where  $L_x$  is in henries, *C* is known

capacitor in Farads; or reference may be made to an *L/C*-resonance chart.

Due to the distributed capacitance of the coil, some error will result; however, if the value of the known capacitor is fairly high, the error will be negligible.<sup>3</sup>

*Relative Q of capacitors or inductances* at a given frequency may be noted by observing the character of the dip, as previously described.

*Antennas.* Use Dipper as g.d.o. Coupling should be made at a low impedance or high current point as shown at Fig. 1E. This point, for a half-wave

<sup>3</sup> In measuring small values of inductance, be sure to employ a low inductance standard condenser, connected to the unknown coil by wide ribbon, in order to obtain accurate results. —Ed.

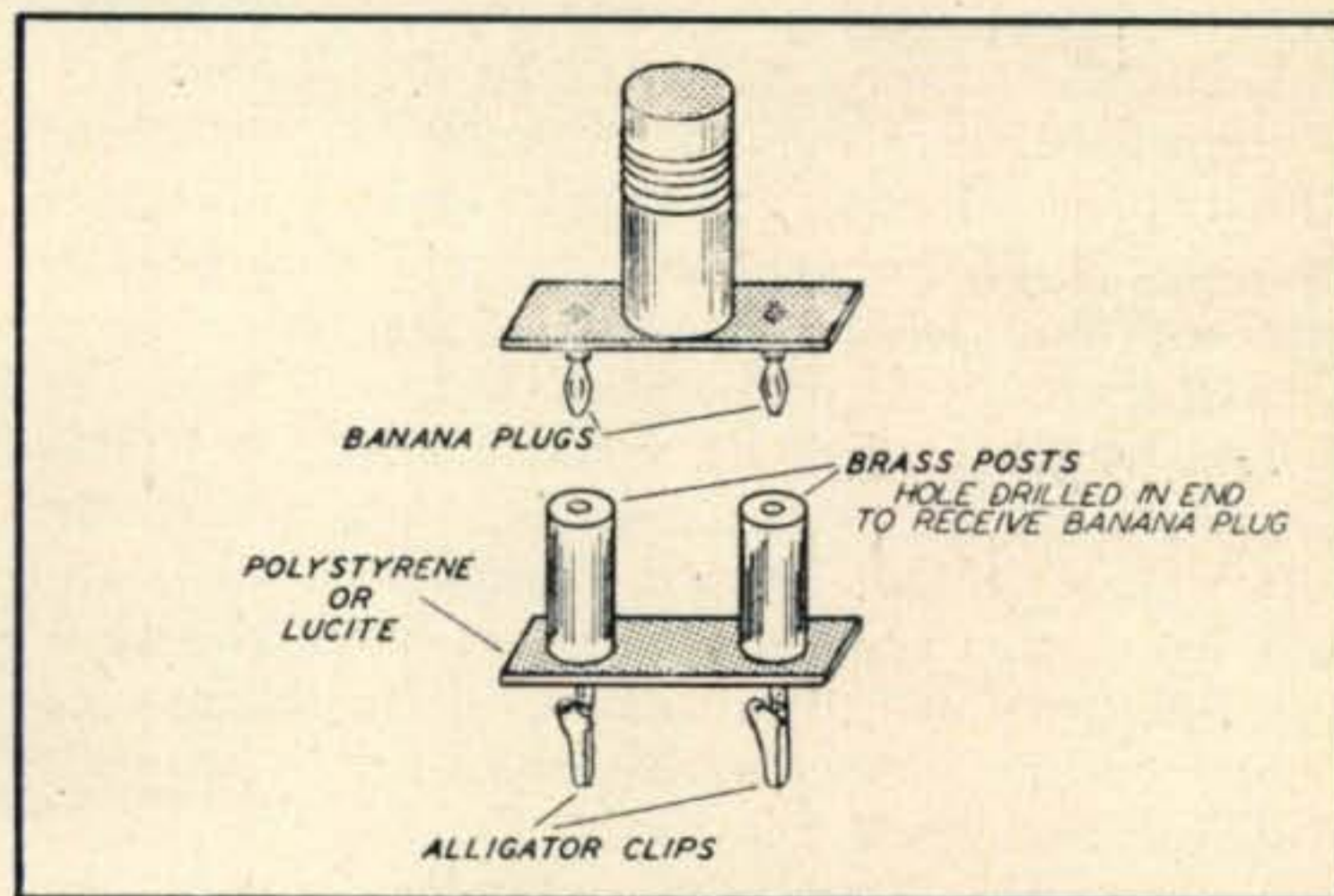


Fig. 2. Jig for coils used in capacitance measurements. Where measurements are generally to be made of capacitors not wired in circuits, the jig may be mounted on a small stand placed on the bench.

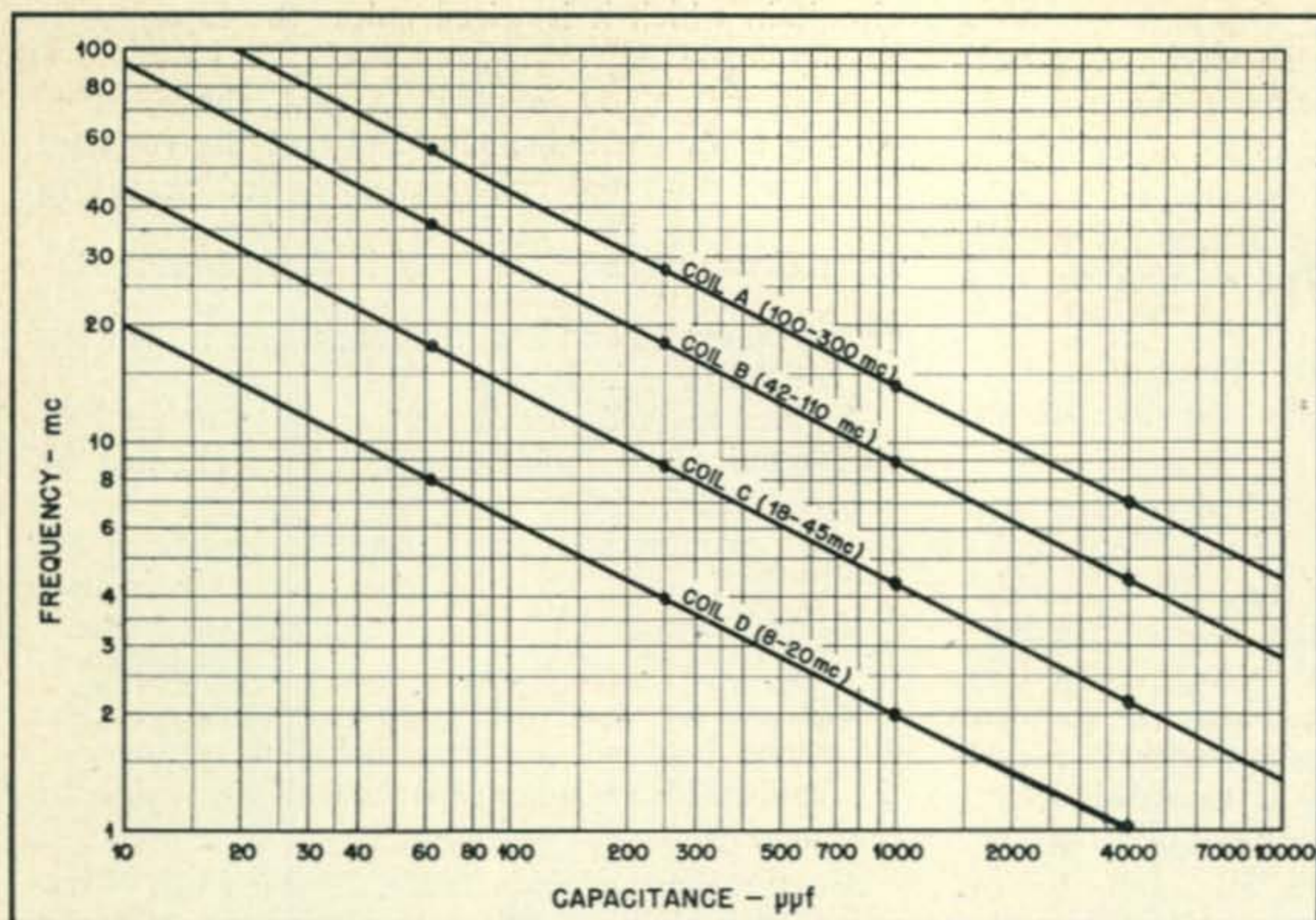


Fig. 3. Typical calibration chart for capacitance measurements, subject to limitations set forth in text. Calibrating points as described in the text are so indicated.

antenna, is at the center, and for longer wires is at points odd quarter wavelengths measured from either end. It will be observed that a full-wave antenna will not be a half-wave at exactly half its resonant frequency. This is because the end effects are found only at the antenna ends and will be absent at other points when the antenna is a full wave or more long. It is therefore always necessary to measure an antenna under the conditions desired (relating to physical and electrical length). Measurement should be made with the antenna placed as near as possible to its ultimate operating position. Checks with the Dipper on a given antenna at different heights or positions will show an amazing difference in antenna resonance.

If it is physically impossible to reach a low impedance point, a check may be made at a high-impedance or high-voltage point. Capacitive coupling should be used as shown at Fig. 1F. If the high-impedance point involved is one of the ends, the end effect will be altered due to the presence of the instrument and the resonant frequency of the antenna will slightly decrease. This must be taken into consideration when making measurement, i.e., the reading indicated by the Dipper will be slightly lower than true antenna resonance (with Dipper removed away from end). This difference will be about 1 to 3% and will be encountered only when checking at the ends.

In all cases it is helpful to keep in mind the physical length in feet vs. electrical length (half-wave, full-wave, etc.) as calculated approximately by formula. Unlike lumped resonant circuits, antenna harmonics are detected when using the Dipper. As previously mentioned, these harmonics will not occur at exact multiples of a half-wave.

When measurement is made, the feeders should be disconnected from the antenna. Unless the feeders happen to be perfectly matched or terminated, true antenna resonance will not be indicated because unmatched feeders or incorrectly terminated feeders will present either a positive or

negative reactance and will, therefore, alter the electrical length of the antenna.

When the antenna element is of very large diameter, such as is often found in rotating beams, sufficient coupling to the Dipper may not be obtained and some difficulty will be encountered in finding a reading. This condition may sometimes be relieved by jumping a foot or so of the antenna at the center with a small diameter wire and coupling to this wire.

If the antenna is to be normally used with its center open, close it with the shortest possible wire during measurement. This must be done also with the folded dipole. The short may later be removed, if required, when feeders are connected.

*Tuned or resonant feeders*, such as used in the Zepp antenna. Use Dipper as g.d.o. and check for desired resonance at the series or parallel tuned circuit on the transmitter end of the feeder. If resonance at the desired frequency is not obtainable, alterations may be made in the tuned circuit or the feeder length according to the actual resonant frequency found. Care must be exercised not to become confused by other resonance indications. It must be remembered that a Zepp is actually a long wire antenna partially doubled back on itself and resonance can therefore be noted at frequencies both higher and lower than the desired one.

*Untuned or non-resonant feeders*. After the antenna has been adjusted to the correct length, an untuned feed line may be connected employing some system of matching. Correct match may be obtained by making adjustments while employing a transmission impedance bridge<sup>4</sup> or a standing-wave-ratio meter<sup>5</sup> and using the Dipper (set at antenna resonant frequency) as the signal generator.


(Continued on page 91)

<sup>4</sup> Jones, "Balanced R-F Impedance Measuring Set," *CQ*, October 1945.

Tiffany, "A Universal Transmission Bridge," *QST*, December 1947.

<sup>5</sup> Pattison, Jr., Morris, Smith, "A Standing Wave Meter for Coaxial Lines," *QST*, July 1947.

# The Other Fellow's Station-W1BB

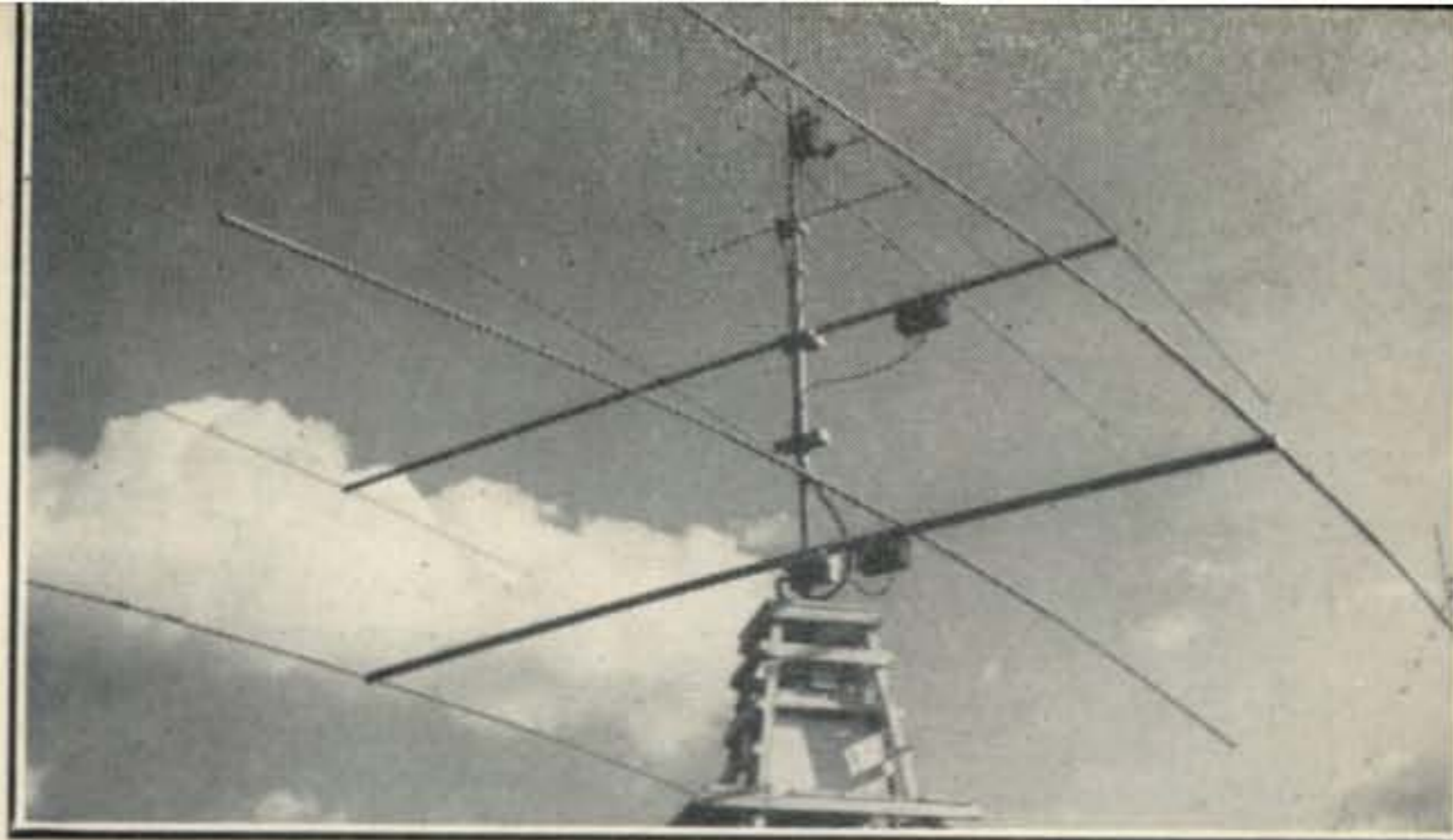

**T**RYING to describe W1BB in even one entire issue of *CQ* is about as simple a task as putting a kilowatt in a suitcase. Stewart S. Perry first became active in 1912 using the call "SS." Officially licensed in 1917 he has been active pretty much since then with spark rigs, audions, etc.

The station now being operated under the call W1BB is in reality many stations under one roof. On his roof are no less than 11 different antennas for all bands from 80 to 1¼ meters. The rotary illustrated covers 2, 6, 10 and 20. To top it off is a vertical quarter-wave whip for 15 meters. Each individual beam is mounted so that it can be taken down separately to work on if necessary. Each beam is individually fed with coax brought to a control panel in the shack. Automatically the antennas are switched through a coax relay to whichever transmitter is in use. W1BB is mighty proud of this antenna installation which is a remarkable demonstration of how much gear can be hung on one rotator. Some of the other features of his antenna installation include remote controls on the roof for testing from that position, automatic stops, and a brake for high-wind conditions.

W1BB features a separate complete r-f section on each band. QSY is almost instantaneous and requires merely the insertion of the proper plugs in the control panel. Each transmitter is rated at 250 watts phone and 500 watts c.w. E.C.O. or crystal is available on all bands. On the small table which comprises a separate operating position is an emergency setup using a Harvey UHX-10, NC-200 and SW3 operated from a vibrapack. In the basement, connected to the radio room wiring through a control box is a 600-watt gasoline generator. This will handle one of the large transmitters for emergency communications.

The operating position was in reality designed for maximum convenience and utility—not to make visiting hams drool. On it is the beam con-

trol box, HRO, variac enabling instant QRP, a pushbutton safety switch which will kill all power upon contact, crystal/e.c.o. master unit with 25 crystal positions, Hallicrafters 5-10 for 6-meter work, National 1-10 and an emergency receiver for 144 mc. In the stand on casters is the NC-200 emergency receiver and monitor, Meissner Signal Shifter as a spare v.f.o. or as a low powered battery operated transmitter, battery operated SW-3, and Panadaptor. To the extreme left is a broadcast receiver and record player. Among the miscellaneous gear is a charging panel, emergency low power transmitter with single wire Marconi antenna and tuning unit on the wall. This piece of gear is ready to go at all times. Everything in the station is controlled remotely from a 6-volt storage battery and relay circuits.


In this ham's paradise you'd expect to find W1BB all the time. But when not earning his living as a sales engineer for Worthing Pump and Machinery Corp., you might find him out on his boat with his fine family. The XYL Alice, and Jim and Skip are pretty well used to ham radio by now. But even when vacationing around the country W1BB works all bands. His automobile is completely equipped for portable and mobile operation—2 through 80. Rig is 20 watts with a 6L6 final. An NC-173 serves as a receiver; for 2 a TR-4. This past summer on a 6-week trip to California W1BB operated portable in all U.S. Districts and kept nightly schedules with W1BDU on 7 or 14 mc. And they never missed a sked! At that time operation was portable only, with F.C.C. notification been given at each stop-over, but next year W1BB says he'll do it mobile.

We didn't tell you about the 600-meter receiver or the 200-watt phone-c.w. rig for ordinary portable work like Maine vacation trips. But this thumbnail sketch should prove that W1BB is an old-timer who has lost none of his enthusiasm and still takes his hobby seriously.


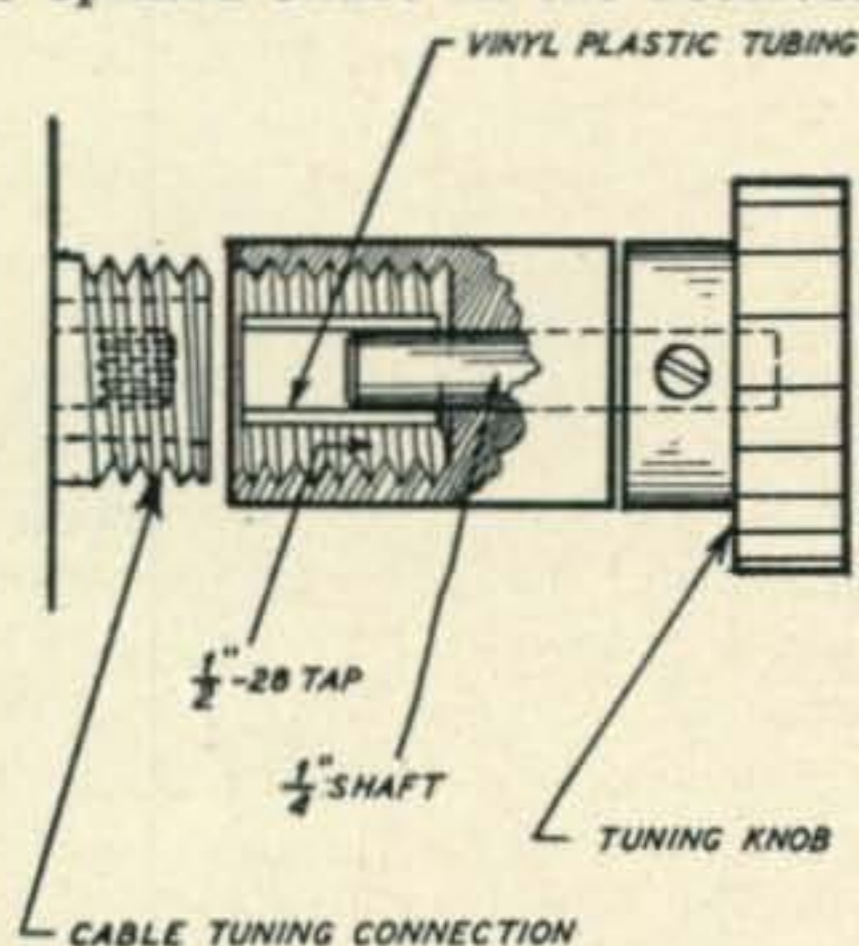
## 274N Receiver Tuning Knob

This is a homemade tuning adaptor for the 274 N series receivers. The shaft and tuning knob are standard items. The only special parts are a piece of vinyl plastic tubing, the inside of which should be slightly smaller than  $\frac{1}{4}$  inch, and the adaptor fitting itself which is machined out of ordinary brass, or even aluminum. This adaptor is  $\frac{3}{4}$  inch in diameter and  $\frac{3}{4}$ -inch long. One end is tapped to a depth of  $\frac{3}{8}$  inch with a  $\frac{1}{2}$  inch, No. 28 tap. A  $\frac{1}{4}$ -inch diameter hole is reamed on through to the other end. The length of the  $\frac{1}{4}$ -inch shaft should be such that the end of the shaft butts against the end of the splined shaft in the receiver tuning fit-




ting and the plastic tubing fits evenly over both shafts when the adaptor is screwed onto the receiver fitting.

The plastic tubing retains its elasticity indefinitely and there is no noticeable backlash in tuning the receiver. For convenience a crank may be added to the tuning knob if desired.

T. C. Freedom, W3HVE

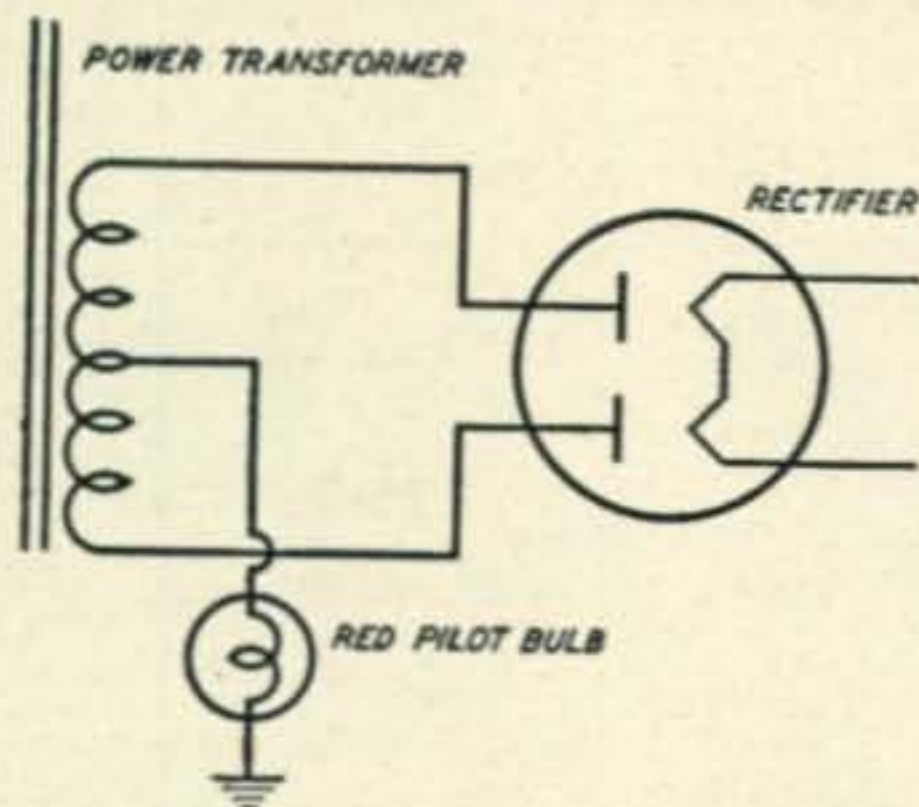
## High Voltage Pilot Bulb

A simple panel light indicator for high voltage power supplies can be made by inserting a dial light in series with the secondary center-tap of the



high voltage transformer. The pilot bulb should have a current rating suitable for the drain on the supply. When current is being drawn the pilot will light, and in addition will act as a fuse.

F. C. Johnston, VK3EL

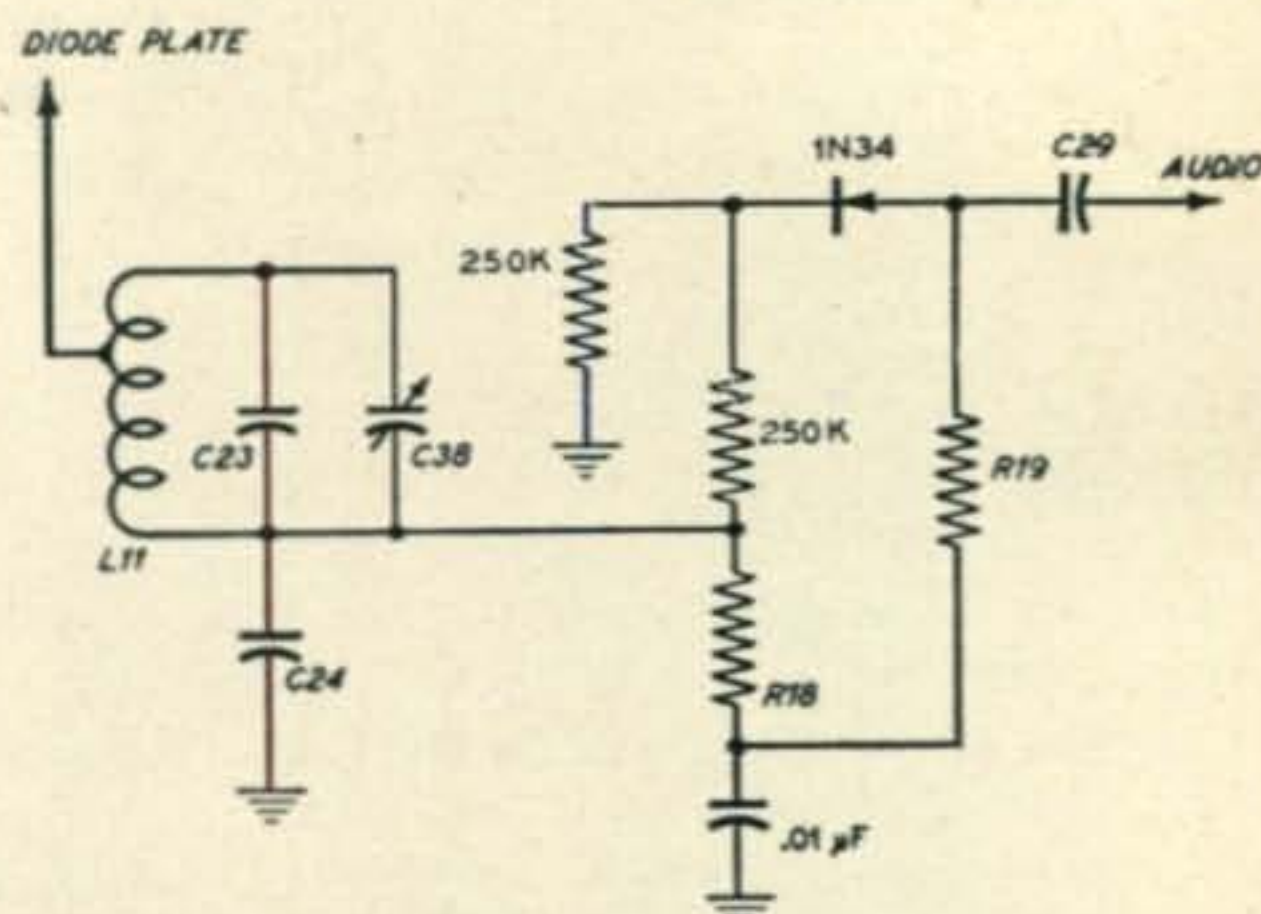


## Noise Limiter for the SCR-274N Receivers

This is the simplest and most effective noise limiter I have used with 274N command receivers. The circuit calls for the addition of two resistors, a 1N34 crystal diode and a paper condenser. The noise limiter is of the self-adjusting series type and does not require a removal switch from the circuit since the quality and signal loss are negligible. The noise limiter may be wired into the receiver in about five to ten minutes.

Don Jeppesen, WØQFZ
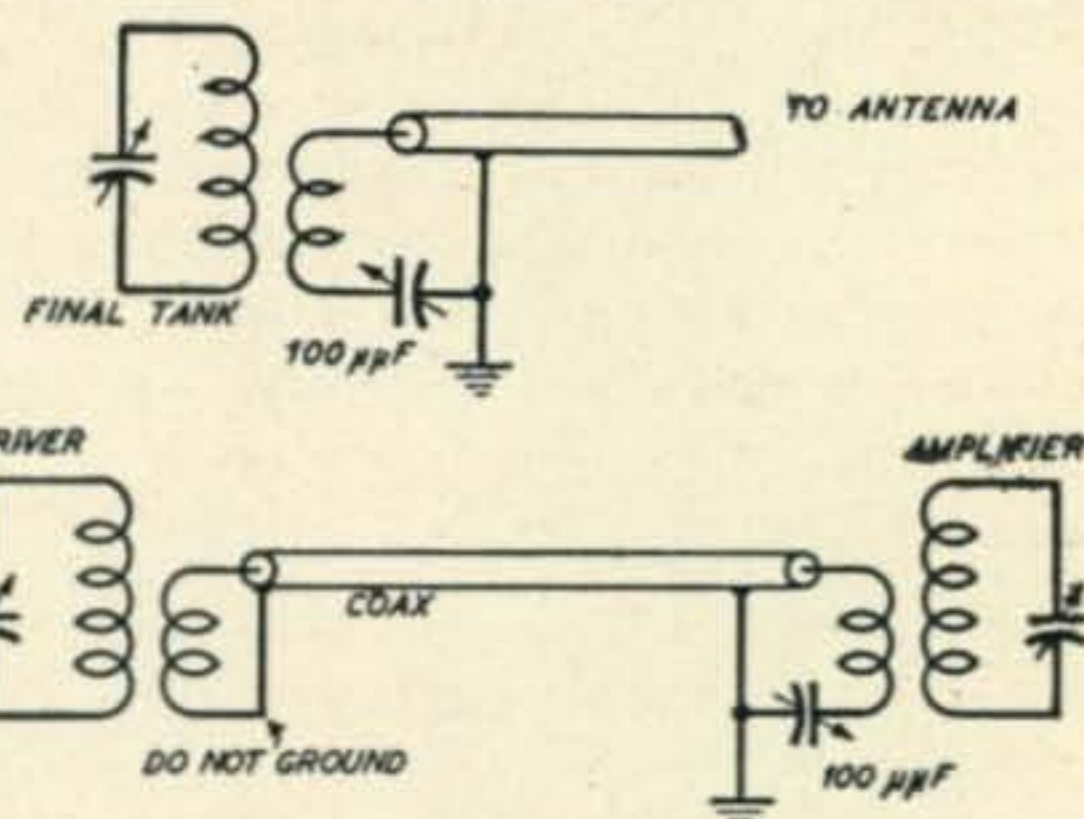
## Tuning Out Coax Cable Reactance


This little trick does not seem to be sufficiently well appreciated by the average amateur, although it has been used to good advantage in commercial and military radio equipment. Better coax cable




matching and transfer characteristics can be obtained by inserting a variable tuning condenser between the return of the link and ground. This condenser is tuned for maximum loading, which in this case means minimum reactance in the link. Maximum power transfer may be obtained with minimum coupling by using this method.

A particular instance of its effectiveness was in trying to drive a pair of 4-125A's to 700 watts input with an 807 doubler. Without the tuning condenser in the link return between these two stages I could only obtain 10-ma grid current. Tuning out the reactance brought the 4-125A grid current up to over 20 ma. It is equally effective when trying to load a beam feed with coax line.

Ken Chase, W2MA

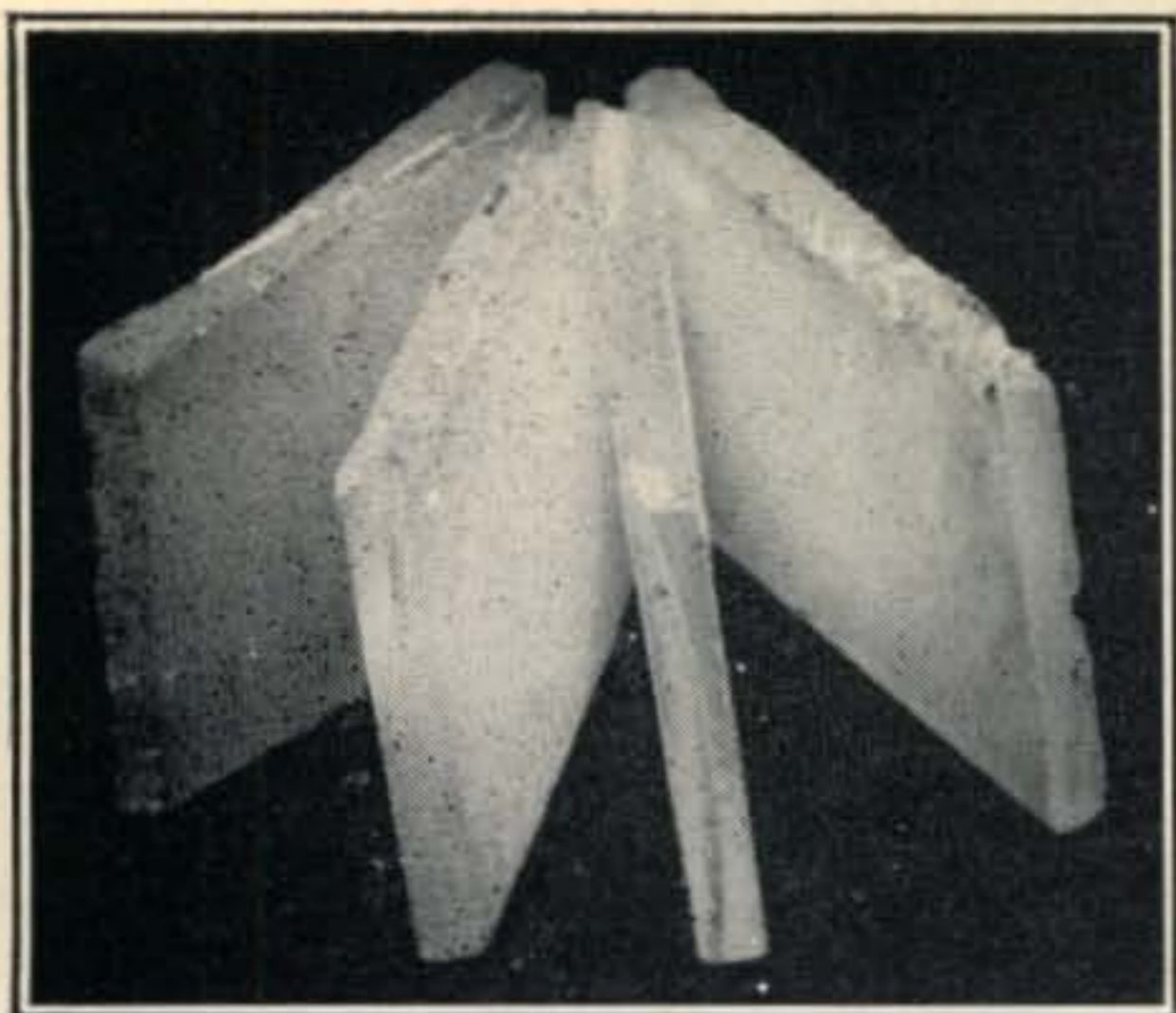

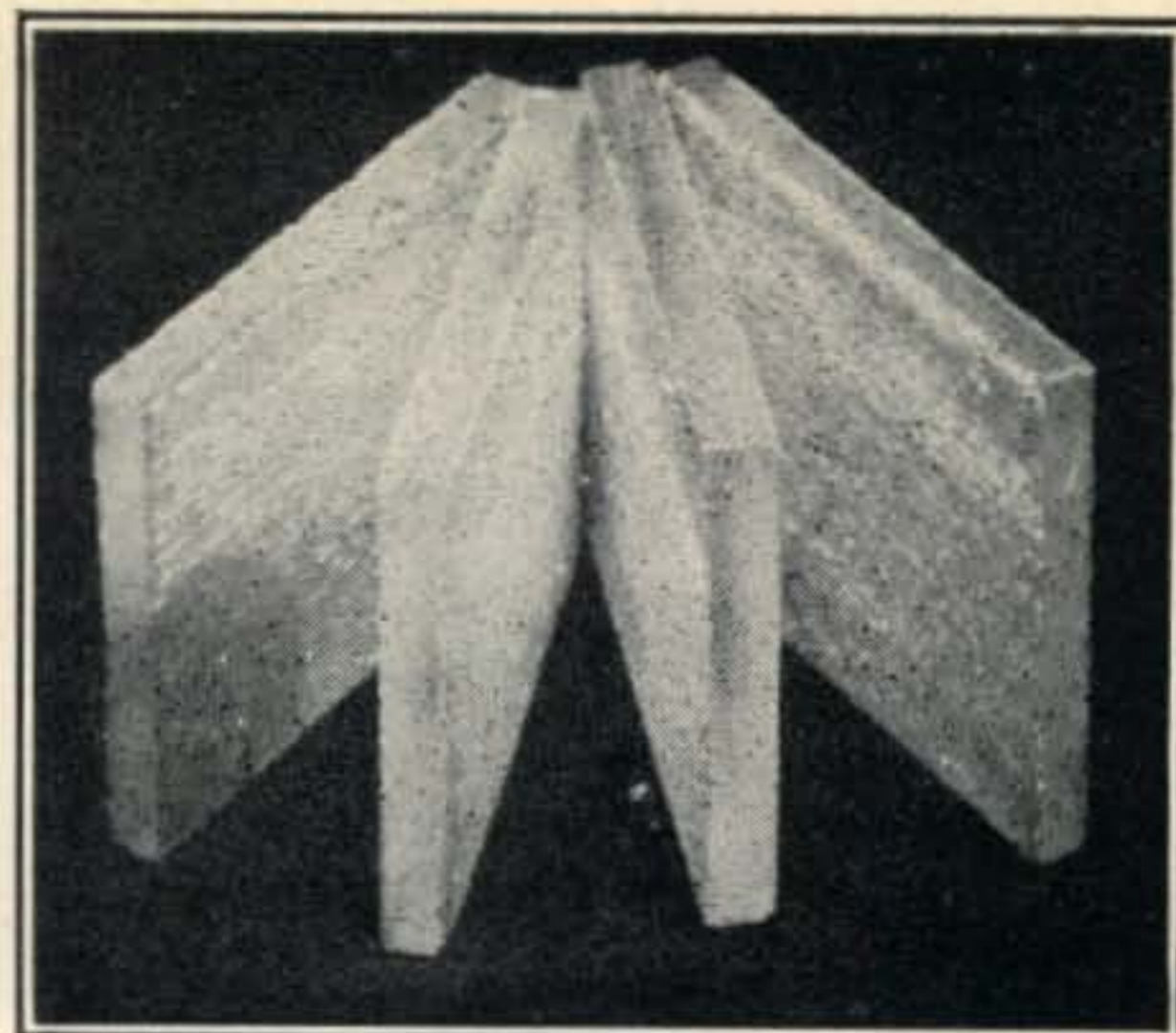Good and poor rough blanks. The jagged uneven edges of the poor blanks readily distinguish them from the uniform even edges of the good blanks.



# Crystal Grinding Simplified

E. W. JOHNSON, W2UXA, ex-W9RAB\*

*Taking the mystery out of a job most amateurs have been reluctant to tackle.*

**M**ANY ARTICLES ON CRYSTAL GRINDING have appeared in amateur magazines since Herb Hollister set forth his arguments for and against the X and Y cut plates in a 1930 *QST*. There were some even before that time, and plenty since then. The sad part of the story is that the current information contained in articles, the handbooks and manufacturers' instructions, is undeniably confusing. They vary widely—and drastically—in their recommendations as to what to do and how to do it. It seems that the correct approach is indicated, so let's look at this problem of amateur crystal finishing from a logical standpoint, and take up the questions of what we want to do, how to do it, some of why we do it and what we do it with. The techniques described are based on sound war-born experience with large scale crystal production that have also proven to be equally adaptable to the small scale operations of an amateur grinder.

In order to simplify things, we will confine our discussion to the almost universally used AT and BT cuts in the region of 3 to 10 mc. As far as the average amateur is concerned, the chief difference between these two cuts is in the fact that frequency for frequency, the BT cut is somewhat thicker (about 30%) than the AT. In other words, a 1000-kc AT cut is about .066" thick, while a BT cut at the same frequency is about .100" thick. Also from a practical standpoint, the BT is probably easier to handle for a beginner as it is less prone to frequency jumps and spurious responses; on the other hand, the AT cut is somewhat more active and has a better temperature-frequency coefficient.

\*Signal Corps Engineering Laboratories, Fort Monmouth, N. J.

Sometimes one will encounter an alleged AT or BT cut that is a real "drifter." The chances are pretty good that it will turn out to be a "miscut"—an AT blank for instance cut at the correct AT angle but from the BT side of the Z or optical axis of the raw quartz crystal. They can usually be identified by their frequency-thickness coefficients.

## The Blank

Blanks should have their major surfaces virtually plane parallel, with a convex contour not exceeding a few ten-thousandths of an inch at 3.5 mc and correspondingly less at 7 mc. Under no circumstances should the major surfaces be allowed to become even slightly concave, nor should it be

| FREQUENCY-THICKNESS CONSTANTS (K)  |       |
|--|-------|
| $F \text{ (in kc)} = \frac{(K)}{\text{THICKNESS IN THOUSANDTHS OF AN INCH}}$ |       |
| CUT  | K     |
| AT CUT   | 65.5  |
| BT CUT   | 98.4  |
| AT MISCUT  | 94.5  |
| BT MISCUT  | 74.0  |
| X CUT  | 112.6 |
| Y CUT  | 77.3  |

Fig. 1. For the various type crystal cuts the frequency is directly proportional to the thickness.

permitted to become wedge shaped. (Why? Try and get any decent level of activity out of such a blank! Or if you do get any activity, see how many frequencies you may have!)

In outline they can be either square or rectangular, but the adjacent edges in any case should be reasonably close to right angles—as much so as you can make them using a common steel square for checking. (Why? Better activity as a result

of less interference with the motion of the blank.) Or you can make them round and naturally forget about the squareness.

Thickness and contour can be checked with a micrometer—a very, very handy tool for the amateur crystal grinder. One reading to .001" will do, as you can interpolate .0001" points, but one reading directly to .0001" is much better. Irregularly

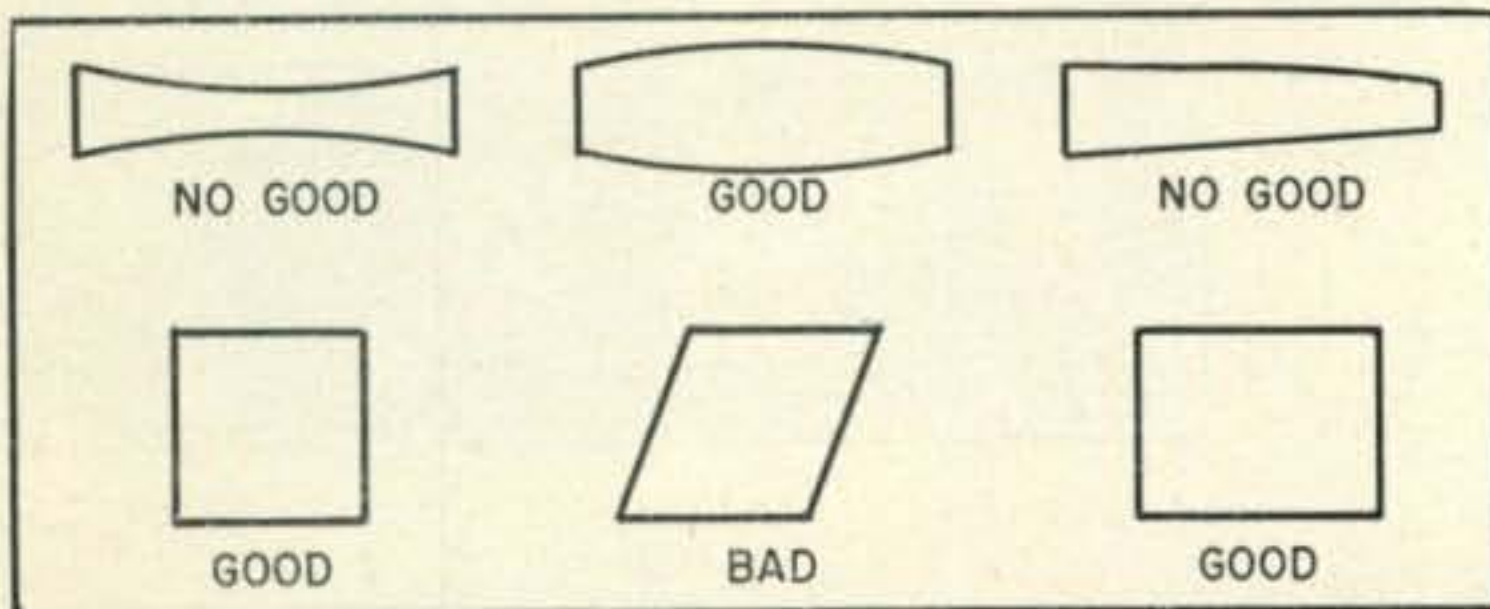


Fig. 2. Proper operation of a crystal is vitally effected by its shape. (Defects exaggerated.)

shaped plates can and will often oscillate satisfactorily, but for uniformly best results watch the contour (keep it slightly convex) and keep them reasonably square-cornered. The finished plate should be small enough to easily fit the intended holder without binding at the edges, and large enough so that at least about half the area of the "lands" in each of the corners of the electrodes is covered. For freedom from frequency shift due to vibration or shock, the plate and electrodes should be a good fit in the holder cavity—maximum clearance of the order of .01. In no case should the quartz plate be larger than the electrodes. When finished, the edges should be free from cracks, large chips and incipient fractures. Small chips appear to be of little consequence at the lower frequencies (about 3.5 mc, for instance) but apparently become increasingly important as the frequency goes up. Moreover, cracks, chips and fractures are potential sources of trouble such as complete failure, poor activity, erratic behaviour or frequency jumping. If the chips are small, and the material has broken away cleanly, they are not of too great concern; however, if in doubt, the best thing to do is get rid of them. You can round off the corners and edges slightly if you want to.

#### Grinding

The ordinary flat of plate glass is fine for hand grinding, as is the often-described figure of eight motion. So, too, are the little glass gadgets known as "dops" sometimes supplied with kits and to which the blanks are "sweated" for grinding. Personally, I prefer to use my fingers—not one finger, pressing in the center of the blank (it is very, very easy to make a 7-mc BT blank concave by putting pressure only in the center of the blank), but two—actually the thumb and forefinger exerting equal pressure on areas near diagonally opposite corners. Make a few figure eights, rotate the blank 90° so you can put pressure on the corners "unused" in the previous operation, make an equal number of figure eights, turn it another 90° and continue until your thumb has been on all four corners. Slight irregularities in contour can be

smoothed out by the application of greater pressure on the high spots, and if the center gets too high, then place one finger in the center and make the necessary number of figure eights to bring the contour back to where it belongs. And, if your plate has a reasonably good contour to begin with, confine subsequent grinding to but one side and your chances of ruining it are vastly decreased. How much pressure? Take it easy. Use a moderate amount, for haste makes waste in the form of cracked and wedge-shaped blanks.

#### Finishing to Frequency

Blanks can be finished to frequency by grinding, as described above, or by etching. If you grind, use the finest abrasive that will do the job; 303 to 304 optical flour is suitable and should be available from a local optometrist. A few ounces will finish a lot of crystals! Coarser abrasive can be used if you have to move the frequency a relatively long way—say 50 kc at 7 mc or 20 kc at 3.5 mc. Etching, however, offers many advantages over grinding and is strongly recommended. A well etched crystal will be for all practical purposes free of aging effects—you won't have to take it out and clean it frequently in order to make it percolate satisfactorily. You can use hydrofluoric acid if you want to, but it is *DANGEROUS* stuff to work with and have around, even when you are well equipped to handle it. Ammonium bi-fluoride, or one of the similar patented compounds (such as Safe-T-Etch) are just as effective and much safer and easier to use. If you should spill any of a fluoride solution on yourself, wash it off with copious quantities of warm water. There is really not much of an excuse for using hydrofluoric acid, as the bi-fluoride is usually available from local drug stores or chemical houses. Containers for etching solution should preferably be of lead or copper, but glass or crockery will do in a pinch except for hydrofluoric acid. Don't leave it in glass or crockery any longer than is necessary, as prolonged exposure will result in the bottom dropping out or holes being eaten through the side or bottom or some such phenomena. Use a saturated solution; start out with half a cup of


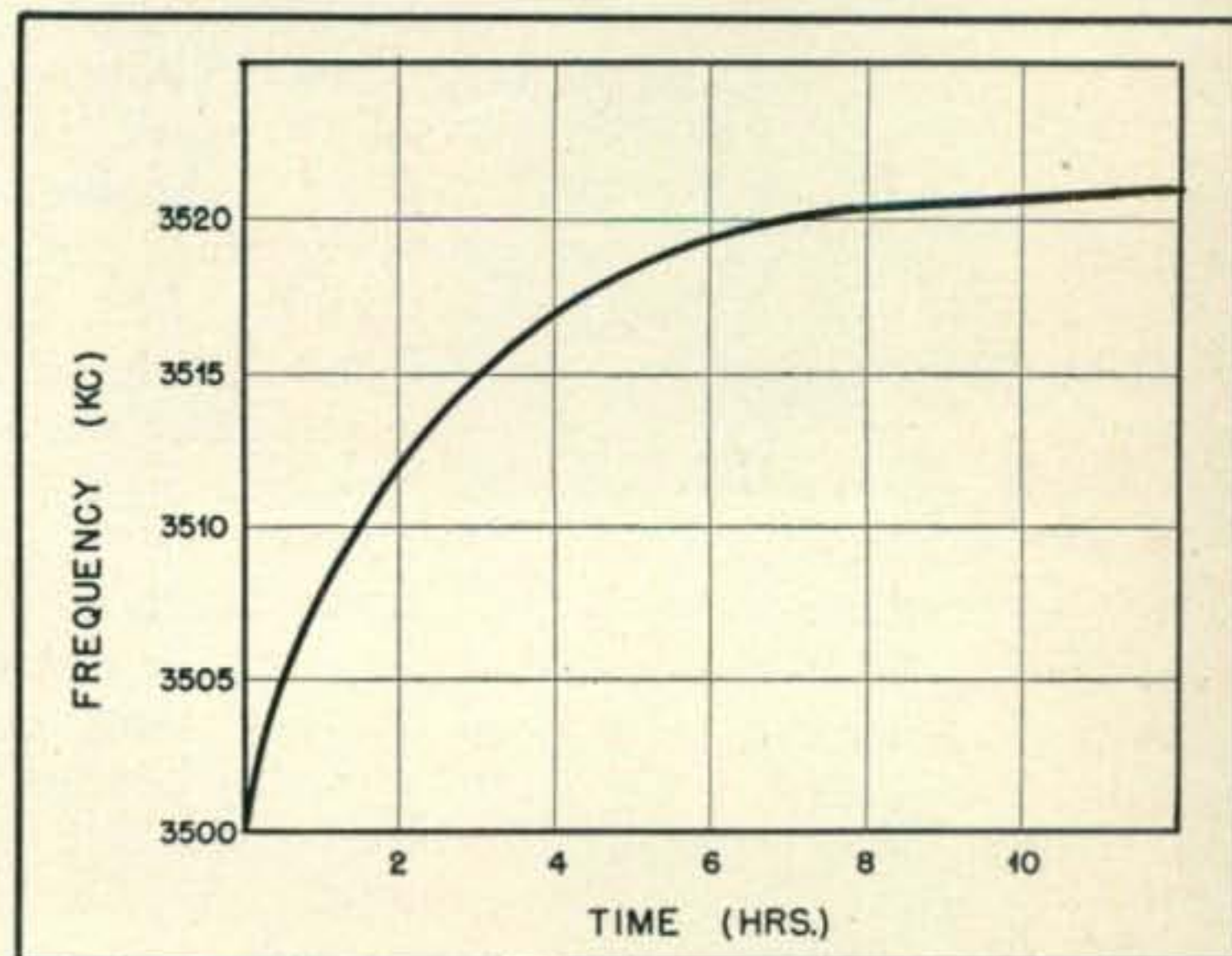


Fig. 3. The curve shows a typical change in frequency over a given time for a crystal being etched.

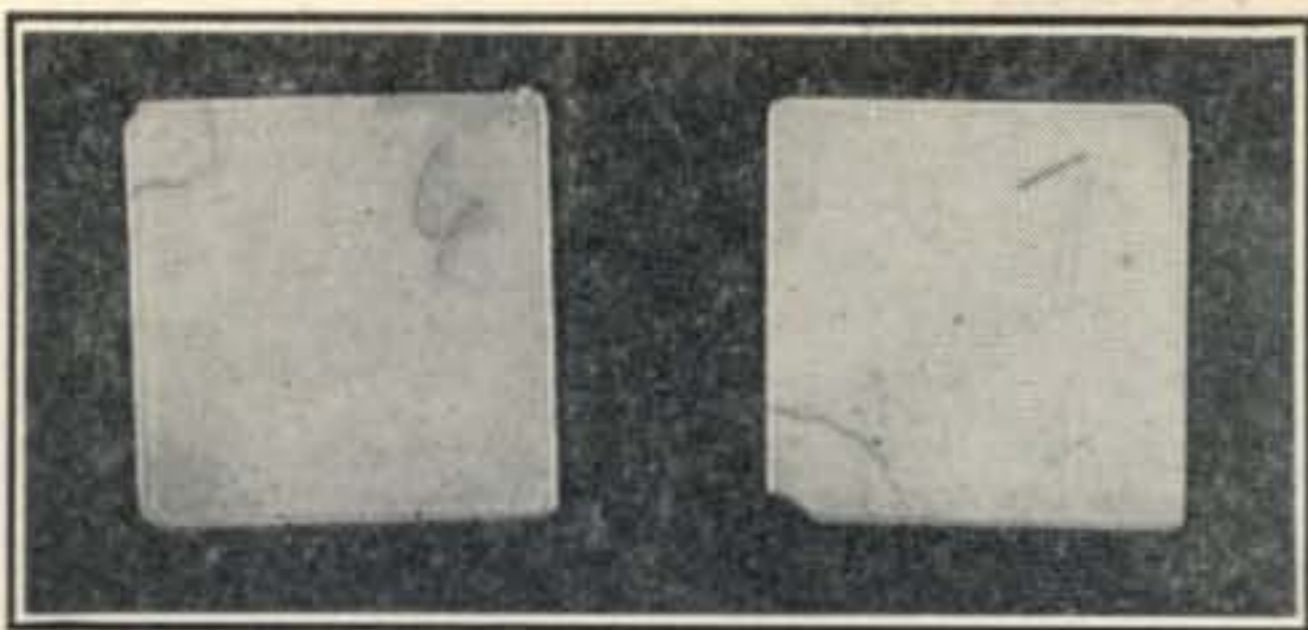



Typical examples of poor blanks. Note the chipped and cracked corners. By proper grinding they can be restored to useful activity.

etching compound and add just enough water (preferably warm to hot) to completely dissolve it. Surprisingly little water is required. Use it at room temperature, but if you are in a hurry, you can speed up the etching rate considerably by keeping it at about 120° F. If kept in a copper or lead container, it will keep its strength almost indefinitely and a cupful will etch plenty of crystals. Use a little basket made of copper wire to hold the crystal in the etch pot. Rinse the plate thoroughly in warm or hot water as soon as you take it out of the etch, then scrub it vigorously with a toothbrush and a detergent soap, such as Dreft or Swerl. Air drying is greatly preferred over drying with any sort of a cloth. Incidentally, use the toothbrush technique before etching, and before testing or mounting whether you finish to frequency by grinding or by etching. If possible, handle the plate with tweezers—preferably plastic—but if you use your fingers, touch only the edges. Cleanliness cannot be overemphasized!

The rapidity with which crystals will change frequency when etched depends upon several factors:

- The original finish of the blank (surface condition).
- The frequency of the blank.
- The temperature of the etch.
- The concentration of the etch.
- The type of cut.

In general, they etch very, very rapidly at first, gradually slowing up as the kilocycles come off. The first 5 kc at 3.5 mc and the first 15 at 7 mc go fast, even at room temperature—a matter of minutes, in fact. If you want a crystal that is really free from aging, it is best to figure on taking at least 15 kc off a 3.5-mc blank, and about 30 kc off a 7-mc blank. You can easily etch a 3.5-mc AT blank about 75 or 100 kc and a 7-mc BT blank about 150 to 200 kc. The rate of etching curve will look something like that shown in *Fig. 3*.

Grinding the crystal again after etching will void the results of etching in so far as the prevention of aging is concerned; if you want a good stable crystal, make sure that you have etched the previously noted minimum amounts after the last grinding.

Contrary to popular belief, an AT or BT cut plate is capable of oscillating at more than one frequency. They are normally operated in what is called the thickness shear mode, but can be made

to oscillate in flexure or face shear along the length and width dimensions, and at frequencies that are quite low (around 100—300 kc) in the average high frequency plate. From a practical standpoint, this means that when our edge dimensions are such that harmonics of these low frequency modes coincide with the thickness-shear frequency, we get either a dip in activity or a completely dead crystal. Furthermore, these different modes will all have different temperature-frequency coefficients; this in turn means that it is entirely possible to have a crystal that has perfectly good activity at one temperature, alter this activity greatly if the temperature is changed by even a few degrees. Do not dismiss the effects of these low frequency harmonics lightly; their effect is very pronounced at 3.5 mc, but somewhat less at 7 mc. In fact, at 7 mc, the chances of getting, with random dimensions, a crystal with good activity, are pretty good—perhaps 5 out of 10 won't need any further work on them after the edge chips and cracks are removed. The chances on 1 mc are about 1 in 10, and at 3.5 mc, about 3 in 10. This coupling effect between the low and high frequency modes can be pretty well explained as follows:

If you keep the thickness (frequency) constant, change an edge dimension and plot the data, you get something like this. (Remember, it's just an example.)

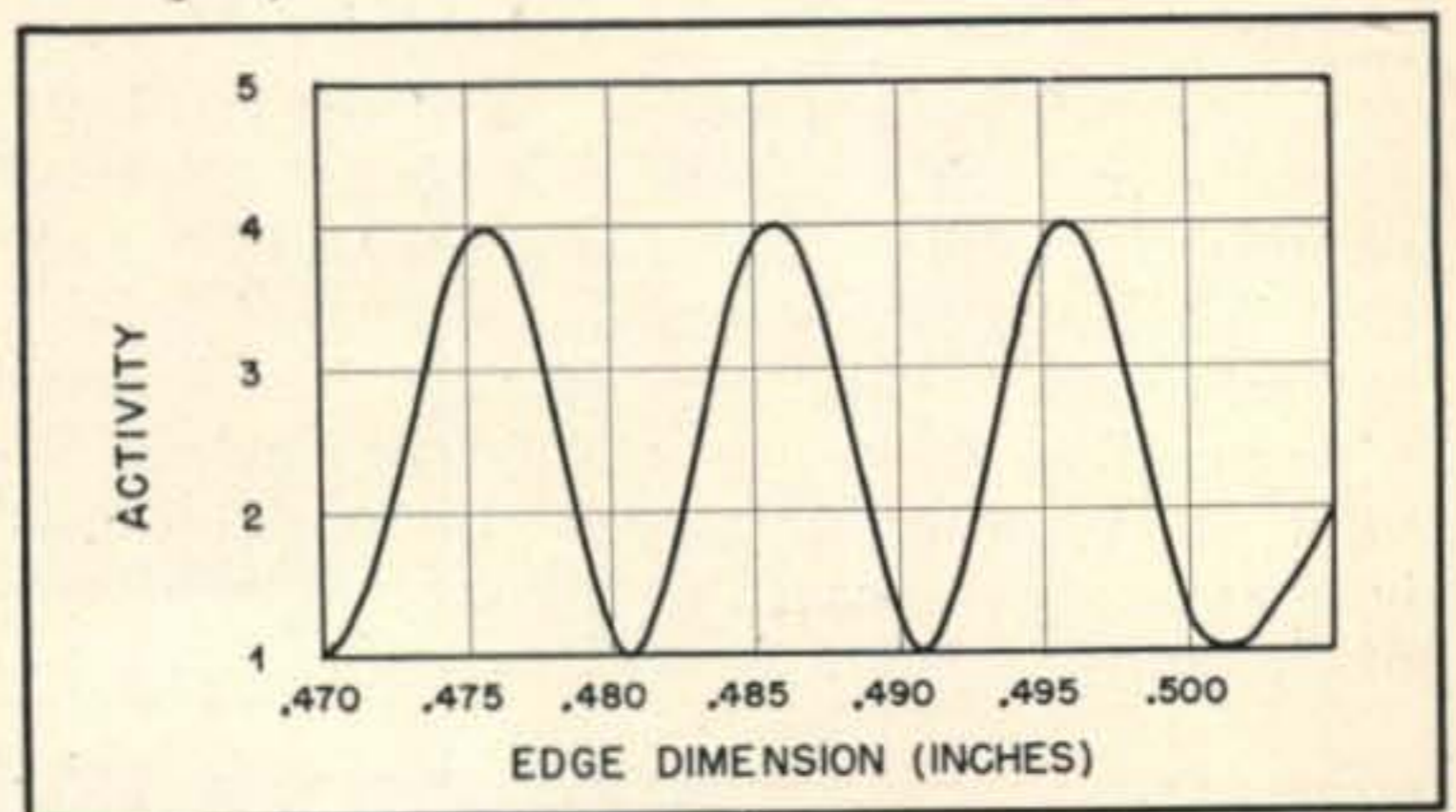


Fig. 4. A change in edge dimensions of a blank while the thickness is held constant can result in a marked change in crystal activity.

If you keep the edge dimensions constant and change the thickness (frequency) you get something like this: (Again, this is only an example.)

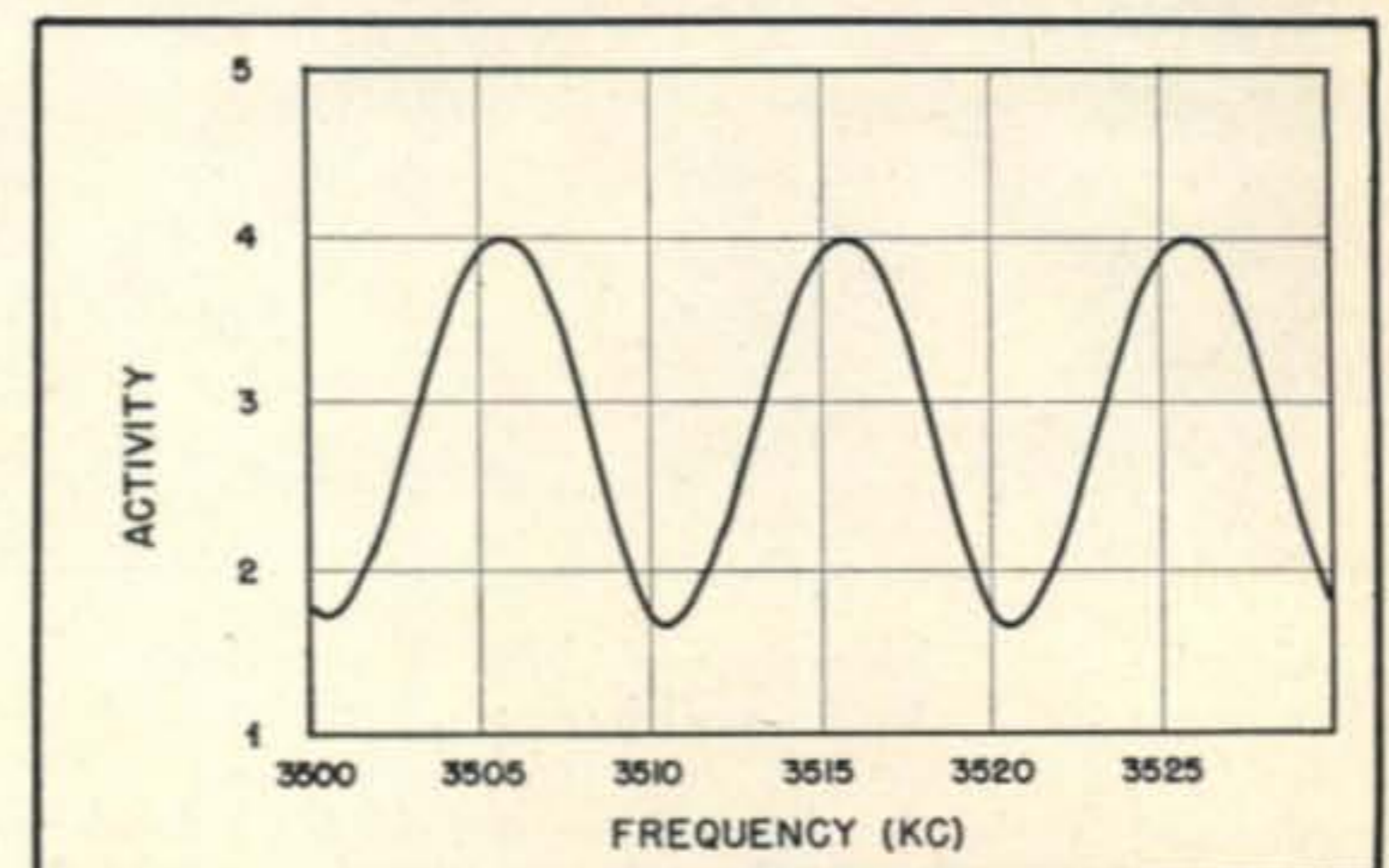


Fig. 5. Holding the edge dimensions constant and altering the thickness can effect the frequency and activity as shown on the graph.

In actual, practice, you would find that the curves you get are not quite as smooth and regular as those shown. This is due to the fact that we have two linear dimensions and several flexure or shear modes to deal with, plus other effects; the result is that a real graph would show a lot of lesser dips and peaks superimposed on the main trace.

What does all this mean to the chap grinding his own crystals? Simply this: the principal factors affecting the activity of a crystal at a given frequency, assuming that it is otherwise in good shape, are the edge form and dimensions. In other words, the *first* thing you do to bring activity up under those circumstances is to start working on the edges. Work on but one edge at a time, and a little bit at a time; check results frequently. Once you get what appears to be the maximum activity from working on one edge, start working on the other and keep at it until you get either a maximum or satisfactory activity. This work on the edges can be straight edge grinding, keeping all surfaces as close to right angles as is possible, or you can bevel the edges. Beveling of all edges is highly recommended. Slope of the bevel is relatively unimportant—somewhere around 45° to 60° is satisfactory—but stay away from excessive “knife edges” or “saw tooth edges” which are potential sources of trouble from chips and cracks. (See Fig. 6).

The tools for edge grinding? Preferably a bonded abrasive, such as a fine grit diamond hone or the fine emery paper sometimes known as “crocus cloth,” but you can use a glass plate and a fairly coarse abrasive. Do most of your beveling and edge grinding before you make your final adjustment to frequency as removal of much material in the process will cause a substantial upward shift of frequency. There is one exception—you will



Abrasive may be removed from the surface of a crystal by the use of a dish of warm water, a jar of soap, and a brush. A very small amount of soap is placed on the brush. The crystal is then scrubbed vigorously until all the abrasive is loosened. The loosening of the abrasive may be accomplished more quickly by dipping the crystal into warm water several times during the scrubbing process.

find that one edge of an AT cut plate is much more frequency-sensitive than the other; in fact, if you keep working on this edge, you will probably find that you can sometimes make the frequency *decrease* by several to a score or two kilocycles, all in one jump. This is an often useful trick, but it takes experience to make it work right!

#### Electrodes

Electrodes for AT and BT cut plates are made so that they come in contact with the oscillator plate only at the four corners. This is done deliberately, since contact at the center of the crystal will keep it from oscillating if enough pressure is applied to keep it firmly clamped so that it will not shift between the electrodes. The air gap between the crystal and the electrodes is usually of the order of a few ten-thousandths of an inch with about .0003" a practical minimum. The spring

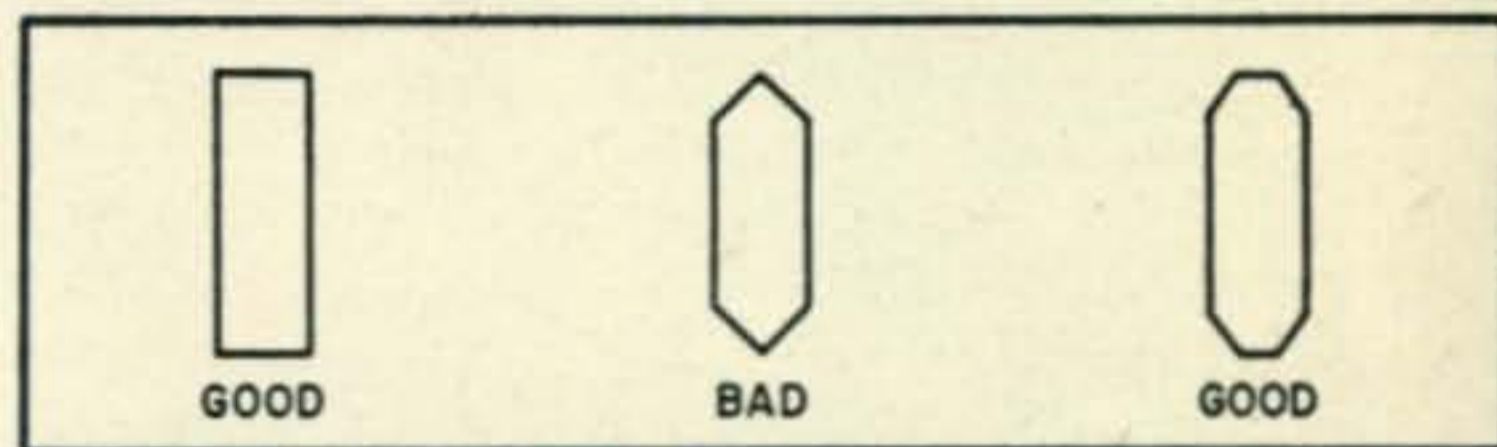


Fig. 6. The shape of the edge of the blank is important to obtain maximum activity.

should exert a pressure of from 2 to 6 pounds on the crystal-electrode “sandwich,” and there should be no marked change in activity when this pressure is applied. If there is, it means that either the dimensions, the contour or the electrodes are probably not what they should be. Most commercially manufactured electrodes are pretty good, so if you have low activity don't blame them unless you are pretty sure that they may be defective. Try different combinations; rotate the crystal 90° at a time between the electrodes and see if you get any change in activity; do the same for the electrodes. In other words, find the position of the crystal and the electrodes where you get the best activity. This procedure will tend to compensate for any slight irregularities that may exist in either electrodes or crystal. Cases where electrodes that are not otherwise defective can kill activity are:

- Where the air gap between the center of the electrodes and the crystal is so small—or non-existent—that they touch and consequently dampen the vibrations of the crystal. Too much contour on the crystal can do this.
- Too much air gap. This is a pretty rare case at the frequencies we are dealing with and with commercial electrodes.
- Resonance. This can happen, and does. If the air gap is such as to make the air column between the crystal and the electrode resonate at the crystal frequency, the oscillations of the crystal are very effectively damped. There are two practicable remedies for this trouble—either change the frequency of the crystal or change the air gap. The latter can be done

(Continued on page 93)

# Monthly DX Predictions - January

OLIVER PERRY FERRELL\*

**T**HE METHODS DESCRIBED in National Bureau of Standards Circular 462 ("Ionospheric Radio Propagation")<sup>1</sup> making use of the C.R.P.L.—D series ("Basic Radio Propagation Predictions")<sup>1</sup> permits a fairly accurate estimate of radio transmitting conditions to be predicted in advance. Also of special interest to the radio amateur are the modifications outlined in an article in the November, 1948, issue of *CQ*.<sup>2</sup> Using the methods described in this latter text the following analysis was prepared based on these parameters:

- A. 1000 watts effective radiated power.
- B. Antenna gain factor 1.
- C. Noise discrimination factor 1.
- D. Service gain factor c.w. to phone 14 db.
- E. Receiving location free from man-made noise.

## West Coast to South Africa

**40 meters:** The very high atmospheric noise level persists during the South African summer months. Their signals may be heard in the United States, but only the strongest Americans will get through between 1745 and 1900 PST. **20 meters:** Fair to good phone opening from 1645 to 1845 PST. C-W signals from 1345 to 1915 PST. **10 meters:** This is still not a good time of year for working this path. Very high absorption levels leave only a few weak signals between 0645 and 0830 PST. Conditions improve slightly towards the end of the month.

## West Coast to Southeastern Asia

**40 meters:** High atmospheric noise levels at far end of the path plus considerable auroral belt absorption keep signals down in the mud. Maybe a few weak signals getting through just before sunrise, but not to be depended upon. **20 meters:** Short opening from 0845 to about 0945 PST. Phone signals just readable. **10 meters:** Fairly consistent opening starting at about 1545 PST. Band probably will not close until after 1815 PST. Good signal strengths, though somewhat stronger during the first hour of the opening.

## West Coast to Middle East

**40 meters:** When ionospheric conditions are quiet there may be signals from 1730 to 1945 PST. This is a decidedly poor opening in any case. **20 meters:** Slow buildup opening starting between 0645 and 0730 PST with band closing just before 1000 PST. Phone signals during the first hour. **10 meters:** No predicted opening. MUF should not exceed 22 mc. Possibly a few scattered signals during the last week around 0800 PST.

## West Coast to Central South America

**40 meters:** Fairly high noise level at far end of path, but fair opening from before 1800 to 0030 PST the following day. Some signals until 0230 PST. Best conditions after 2230 PST. **20**

\*Assistant Editor, *CQ*.

<sup>1</sup> Available from the Superintendent of Documents, Government Printing Office, Washington 25, D.C.

<sup>2</sup> "A New Method of Predicting Band Conditions" O. P. Ferrell, *CQ*, November, 1948, page 26.

**meters:** Consistent good opening 1700 to 0130 PST the following day. Also a few scattered signals around 0500 PST, though mostly c-w quality. **10 meters:** Band opens around 0645 PST with strong signals. Conditions dip around 1000 PST, but build to strong peak between 1445 and 1630 PST.

## West Coast to Europe

**40 meters:** Considerable auroral absorption with weak signals principally around 2200 to 2345 PST. Possibility of some of the stronger signals also being heard around 1700 PST. Not a particularly good band for this path on a prediction basis.

**20 meters:** Fairly good opening around 0645 PST. Decreasing signal strengths until band closes at about 1215 PST. There may be some difficulty with atmospheric noise at far end of the path.

**10 meters:** On ionospherically quiet days a good opening with strong signals starting at about 0745 PST. Band will generally close around 0930, but may remain open frequently until after 1015 PST.

## Midwest to Western Australia

**40 meters:** Noise level and predicted field strengths are about equal, but expect to hear signals from 0400 until 0915 CST. Peak time 0445 to 0730 CST. **20 meters:** Fairly good opening starting around 0845 CST as local MUF increases. Signals probably heard until about 1130 CST, though peak time is 0915 to 1015 CST. **10 meters:** MUF is low at far end of the path. Weak to fair signals possible on less than 15% of the month between 1845 and 1930 CST. Conditions improve during the last of the month.

## Midwest to Western India

**40 meters:** Much the same conditions as predicted during December with a few weak signals 1900 to 2015 CST. **20 meters:** Band opens sharply around 0745 with good signals. Phone until 0900 CST, c.w. until 1015 CST. **10 meters:** No openings directly predictable, possibly one or two around 0715 CST, but very far from dependable. MUF generally less than 24 mc.

## Midwest to Mediterranean Areas

**40 meters:** No openings predictable. Auroral absorption is too high. **20 meters:** A few weak c-w signals 0700 to 0830 CST. Better c-w conditions starting 1030 CST to 1415 CST. Peak with possibly readable phones 1245 until 1400 CST. **10 meters:** A very good opening on ionospherically quiet days from 0745 until 1015 CST.

## East Coast to Australasia

**40 meters:** Good opening 0330 until 0830 EST. Peak expected 0445 to 0730 EST. **20 meters:** The MUF at the near end of path is low, but opening starts gradually on the direct path around 0830 EST. Good phones until 0945 EST, c.w. possibly to 1015 EST. **10 meters:** Regular absorption levels are very high during this season, but a few weak to fair strength signals may get through between 1615 and 1915 EST. Peak is during the latter two hours.

(Continued on page 86)

# DX



## AND OVERSEAS NEWS

Conducted by HERB BECKER, W6QD\*

**T**HE FOLLOWING is a last minute recap of approximate scores and other news about our first World-Wide DX Contest. Since W2IOP is the boss, and since he scored more points than I did, and since he has most of the Contest information anyway, this is given to you with that well-known LeKashman touch.

Where to start, that is the question. Biggest thrill I got was reading over C8KY's log. He was active only in the phone contest, and as you all know Perry Ferrell let conditions misbehave that week-end. He more than made up for it the following week, though. Among the lucky Ws to work Zone 23 were W2SAI, W3BES, W8KML, W0AN, and W8HUD. Although we were promised greater activity from stations in Zone 23, so far C8KY's log is the only one from that zone on hand.

While the phone week-end may have been disappointing to many, there seemed to be plenty of stuff on—if you could raise it. Some of the juicier prefixes competing on phone include C, VS6, ZD1, 3, 4, KX6, VP2 (Grenada), CT1, 2, 3, YS, YN, 4X4, KP6, C3, J2, 9, HR, HP, HA, TG, VQ2, 4.5, CP, HL, CR9, CX, VR2, ST, IS, ZB1, 2, LX, MI13, MD1, ZS3, AR8, ZE2, ZC1, OQ5, VU, VP8, etc. That "etc." stands for just about every prefix in Europe, South America, North America, and Central America, with a fat sprinkling of the rest of the world. We didn't hear a lot of the stuff in the States, but my, oh my, take a gander at the DX stations' logs. It is early to speculate on the winners, but some of the top claimed scores are: ZS6CT, 31,284; PY2AC, 124,068; W6SA (W6SA and W6SZY ops), 47,790; W6GRL, 38,752; VQ4ERR, 28,224; G2PU, 90,628; ZS2CI, 54,982; W7ESK, 32,712; KH6IJ, 23,200; C1CH, 47,320; W8HUD, 52,682; W8DAW, 38,755; W8KML, 55,875; W6AM, 22,659.

The c-w week-end defies description—a terrible admission on the part of an editor who is supposed to have as many adjectives handy as the average W6 has watts. On the last tally the logs on hand indicate participation by over 100 countries. Why even this broken-down old DX man (please compare my score with W6QD's) has spotted better than a half-dozen countries that would have been new ones for me. Before I say another word let me tell you about our good friend Bert Brown, W4FU. Right after the contest Bert was asked by ZD9AA to do him a little favor and pass a message on to CQ. Unsuspecting Bert told him to go right ahead—and that's how come we have the complete log of ZD9AA on hand—calls, reports, time, et al.

A lot of the gang objected to including 3.5 mc

\*Send all contributions to Herb Becker, 1406 South Grand Ave., Los Angeles 15, Calif.

in the contest, but on the East Coast anyway, from 80 right through 10, there was DX aplenty to work. Of all the bands in general use, 14 mc seemed to show the poorest performance. 10 and 40 in the United States anyway, ran neck and neck for honors, if a quick analysis of logs on hand is any indication. While it is true that the most DX was worked on 20, 10 and 40 showed activity that was a joy to listen to. In our best hour we worked over 30 Europeans on 40, and most of them were S7/9! At no time during the contest was there a dead band—that is, if you had the endurance, there was always an open band. But since OM Becker has a long column this month anyway, and since we're going to write up the contest completely in a couple of months, for the moment let's just look at some of the claimed high c-w scores reported.

|        |          |        |        |        |        |
|--------|----------|--------|--------|--------|--------|
| W2IQG, | 289,680* | W4KXN, | 96,446 | W5GEL, | 48,650 |
| W4KFC, | 277,736  | G5CW,  | 95,438 | HK3CK, | 46,057 |
| KH6IJ, | 259,483  | VE3QD, | 93,600 | W1JYH, | 42,959 |
| W6SZY, | 231,105* | W0NUC, | 92,105 | W8AZD, | 42,768 |
| HB9CX, | 227,458  | W8ZY,  | 85,620 | W3GHD, | 42,552 |
| PY2AC, | 205,140  | W1RY,  | 84,785 | W2IMU, | 42,456 |
| KG6DI, | 210,000  | VE4RO, | 83,622 | LB8R,  | 42,330 |
| W8WZ,  | 202,500  | VE4RC, | 83,622 | VE4XO, | 41,184 |
| W2FBA, | 192,072  | EI9J,  | 83,121 | J2AHI, | 40,272 |
| W8JIN, | 187,354  | W9NII, | 78,923 | W3BEN, | 39,312 |
| W2BXA, | 177,840  | W6AM,  | 73,580 | KH6QH, | 39,274 |
| CE3AG, | 176,252  | W6EPZ, | 71,898 | W2HMJ, | 38,940 |
| W6GRL, | 169,680  | W4KVX, | 69,680 | W9CIA, | 37,248 |
| W9IU,  | 137,175  | W0AIW, | 68,328 | VE7ZM, | 37,180 |
| W6RM,  | 132,854  | W1BIH, | 64,416 | OK1RW, | 37,164 |
| W0DAE, | 130,262  | W6IBD, | 61,548 | TI2KP, | 37,064 |
| W9LM,  | 123,900  | W6OMC, | 61,084 | W6BPD, | 36,816 |
| GW3ZV, | 121,626  | W1CJH, | 59,220 | W2EMW, | 36,240 |
| ZC1CL, | 118,000  | TF3EA, | 58,000 | VE6MZ, | 35,482 |
| KH6MI, | 117,264  | W5KC,  | 57,794 | W2UFT, | 33,553 |
| VE7HC, | 111,338  | W7GUI, | 54,720 | W6QD,  | 32,996 |
| LU5BM, | 108,342  | W2QCF, | 53,680 | VE1EA, | 32,012 |
| W2IOP, | 108,120  | W9LVR, | 49,875 | KL7PJ, | 31,920 |
| W6LDJ, | 105,544  | W3JTC, | 49,770 | W3ARK, | 30,400 |
| W9PSR, | 101,780  | W3JKO, | 49,248 | W6SRF, | 30,305 |

\* Multiple-Operator Station

Last month, W6ENV came to the rescue and churned out the column when I had to hit the road again to cover the Northern part of this state of ours. Sometimes it gets rather rugged trying to do the column without having it conflict with the necessary business trips yours truly must make at regular intervals. With such a masterful job as Andy has done on the last couple of occasions, I am sure Larry wouldn't mind if, sometime, I just kept going on a continual trip.

Congratulations to the following for making W.A.Z.

|    |       |                    |    |     |
|----|-------|--------------------|----|-----|
| 83 | G6ZO  | Chris Amundsen     | 40 | 157 |
| 82 | LA7Y  | Jim M. Kirk        | 40 | 180 |
| 84 | W3LOE | Robert Cheek       | 40 | 194 |
| 85 | W6SN  | William A. Lippman | 40 | 196 |
| 86 | W6AYZ | Roy D. Mayes       | 40 | 147 |
| 87 | W6DZZ | Edward J. Hoetzel  | 40 | 161 |
| 88 | W6UCX | John R. Linden     | 40 | 137 |

None of the above really need much of an introduction, as their calls have been heard time and again on the air working the stuff. LA7Y had a little delay, since no country list was received, however, a quick exchange of airmail brought the necessary list of countries. You might be interested to know that Chris has never exceeded 40 watts input to his 807 which he uses in the final . . . the receiver is an AR-88. G6ZO received his 40th card and rushed them to us. They probably arrived just in time, because Jim is now a newly married man, which situation, they tell me, is not particularly conducive to DX. He may have a different formula, however . . . W3LOE and W6SN with 194 and 196 countries respectively, jumped quite a ways up in the Honor Roll in this issue. I think, too, you fellows should know that W6AYZ, who lives in a little town near Sacramento, is a brother of old W6BYB, and more recently D4AVW. Both of the boys are DXers from away back. W6DZZ, another old-timer, will no longer be heckled by the boys at the joint where he works. W6UCX really applied himself during the past year or so, and, obviously, it has paid off. Yes sir, 88 certificates thus far, and more coming without a doubt.

#### No Marathon 1949

After weighing all factors, we have decided against running the DX Marathon again in 1949, though this will disappoint many. I appreciate you fellows being interested enough to send in your comments, both for and against. Everyone seemed to think the Marathon was a swell idea for the past year, but they seem to think that it would probably be just as well to take a year's rest.

Those of you who have been participating in the 1948 DX Marathon should get your final revisions in without waiting too long. As a matter of fact, any additions or revisions postmarked later than 60 days from December 31, will not be allowed.

First, let me say that Guy Dennis, W6DI is coming along very well, although at this writing he is still in the hospital. For those who didn't read last month's DX column we reported the unpleasant news of the accident which befell Guy. The home made bomb that was discovered in his yard, and which he had in his left hand when it exploded, could have killed him. By the time you read this, he will probably be back on the air knocking off a couple of new ones. I should mention again that when the accident happened, Guy was in the process of cooking up the December totals of the Marathon; therefore, no changes have been made until this issue.

To get a little assistance on bringing the Marathon up to date, I thought I had better lower the boom on another committeeman, W6SA. Upon phoning his office it was learned that, "He is off for a week to have an operation or something." This was all news to me, but after a little sleuthing on the part of operative 1492, he was found to have gone to the hospital to have something called an appendix removed. By the time we found the right hospital, he had been discharged. We finally caught up with him, though, and dumped the whole Marathon file in his lap. Since he was going to be home for a few days recuperating, we figured he

might as well be doing something for the good of the cause.

Today, I gave W6ENV a blast on the phone, and since he is custodian of the Honor Roll, I wanted to know how this was coming along. Well, he had been in bed for three days with Virus X (that's a sickness!), so everything was just dandy. Anyway, he is on the mend, and unless W2IOP or the printer falls flat on his face, we will have the Honor Roll, Marathon, and DX column this month.


A group of the boys in New York have formed a club called the "39'ers." According to the advance notice of their first meeting, it is supposed to be significant of the usual zone score on the East Coast. The first meeting was run by W2BJ, and they have it understood that anyone in the club who makes W.A.Z. has to buy a round of beers for everyone, in order to remain in good standing.

WØPNQ, who used to operate *KL7MH* on a small island 1500 miles west of the mainland, has just finished his new kw rig, using an 833 in the final. In fact, it was completed the day before the DX contest, during which he grabbed himself four new ones: *MP4BAB*, *VP8AM*, *I1BCB*, and *KM6AJ*. PNQ is having a little private DX contest with WØRBA . . . No doubt, that's the reason for the new rig.

W1NMP's activities have hit a new all-time low; however, he says the sigs emanating from his new jr. op, around 2 a.m., are hitting a new all-time high . . . but, Stan can't seem to hook up with Zone 26. I wish somebody in Zone 26 would work W1NMP and get him out of the dumps, or whatever he is in.
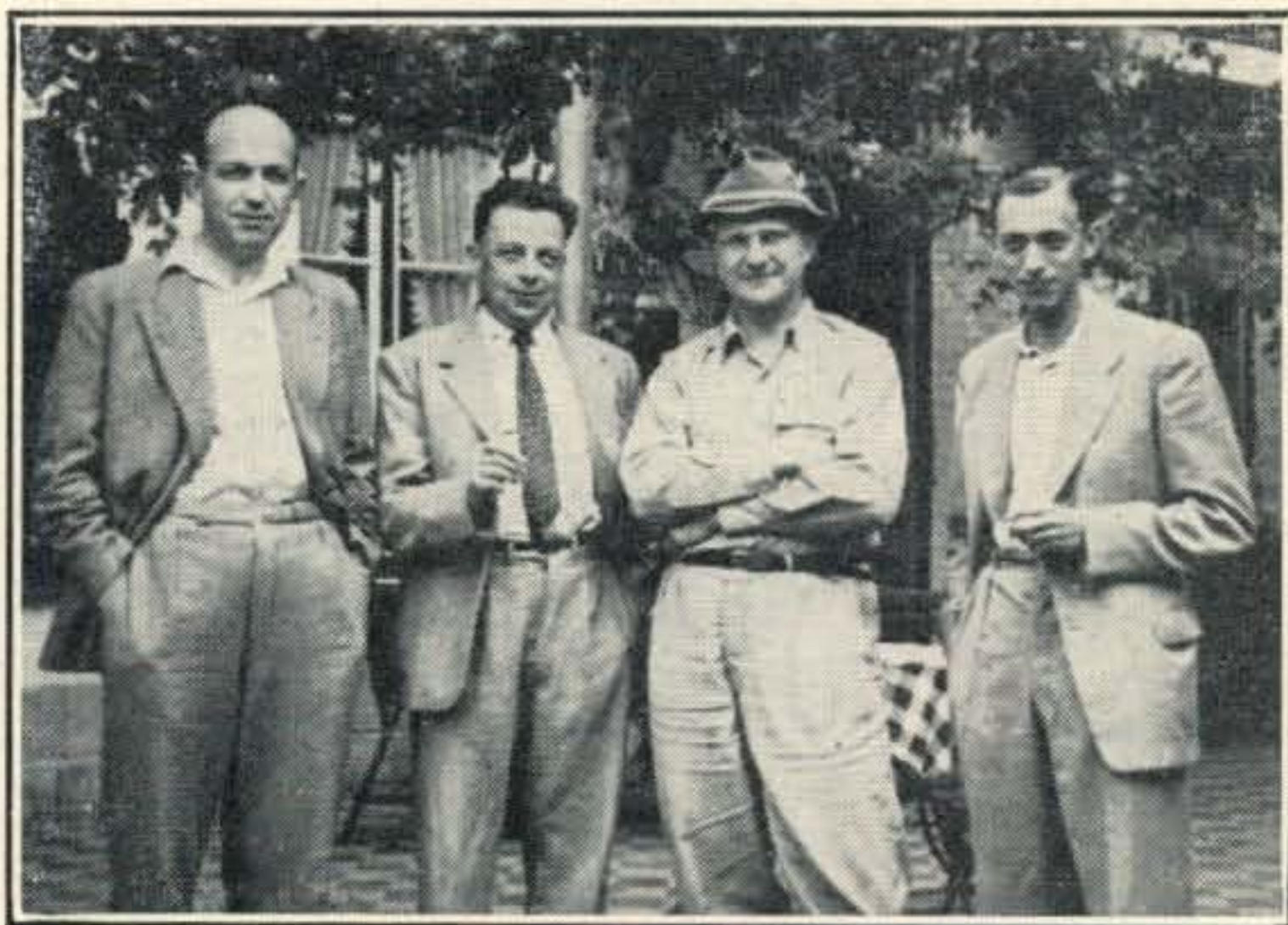
#### Patience is a Virtue

*HC1AW* and *ZP3AW* . . . What about him? Those of you who think *ZP3AW* was a phoney and will never QSL had better quit worrying. He was definitely in Paraguay and will eventually get a QSL card to everyone he has worked. The same thing goes for his present station, *HC1AW*. He is a DX man at heart and well knows the scarcity of ZP QSL cards. It is not a question of getting around to sending cards, but it is simply a matter of not being able to do so until he returns to the States. Just be patient, gang . . . you'll get a card.



Four well-known Belgian DXers. Left to right: ON4AU, ON4US, ON4UT, ON4JW.



Horace Greer, W6TI, has just wired that he has received 51 cards from AC4YN, which were sent to him via VU2GB. Gerry Balantine, VU2GB, says that the India Radio Amateur League will handle all cards for VU2, VU7, AC3, and AC4. After what WINMP thinks, I know I shouldn't say this, but what the heck, here goes . . . VU2GB goes on to say, "Have the WIs any xmtrs to put out their calls? Send a W6 xmtr to Rhode Island . . . it would enlighten that state." Hmmm! You figure it out. . .

I can't figure out what happened to W2OEC, operated by W6COD. Just get a load of this chatter he puts in a letter. "I am beginning to believe that the Sardinians are very restless about the canning factories of New Jersey. I can't think of any other reasons why the ISIs won't return my calls. Will 'CQ IS1' work? My smile has increased, with SP8XA being the cause. That 'X' in the call scares me a little. They don't have any FM experimental stations, do they? If so, Major Armstrong should hear of this. Turkey must be waiting for Thanksgiving, cuz TA3FAS is still in there kicking." All of that is from W6COD, op at W2OEC . . . and, for the love of mike, don't blame me.

Another old-timer back on the air, and making his way up the Honor Roll, is W9LI. As Jim says, 20 years is a long time to stay in moth balls.

All of you want to know what we are doing with the Palestine situation. Do we count ZC6 and ZC8 separately? Or . . . are Israel and Arab-held Palestine different countries. The answer . . . is "no." Now don't blow a fuse. When you think of the situation there as it stands now you will

have to admit it is rather touchy. We have nothing definite as to the the eventual boundaries . . . nor do we have any assurance that everyone will recognize the division of Palestine. In short, it is not a matter of life and death that we decide immediately if they should be two different countries. Let's take it easy and when we do decide we'll be certain that it will stick. Israeli is listed on our new country list in error.

We hear that after January 25, there will be no more American stations in the Philippine Islands. Someone said they won't license Americans after that date, because we won't license Philippines in this country. If this goes through, it may be a little tough to work a KA.

WØRBA says there is no contest anymore with WØPNQ, since he got the 833 final. He says CR6AW opened shop on November 6, and can be found on the low end of 20, T7. This will take some of the burden off of CR6AF, CR6AI, and CR6AQ.

W6ODD has been sending his cards for operation as F18 and CR8. If you haven't received yours yet, better get after him. W9LM says that he got a card from W8OZG/C6, who admits he is a bottlegger, as well as apologizing for crossing up W9LM as to what zone he was in. He tops it off by wanting to play chess by letter with W9LM. I can't think of a better way to spend the next 45 years.

W7HXG says he has just put up a new 3-element wide-spaced 20-meter plumber's nightmare, and until he gets a motor for rotating the antenna, it will stay fixed on South America.

(Continued on page 72)

## DX MARATHON

|            |        |        |        |        |        |         |         |         |         |         |        |       |
|------------|--------|--------|--------|--------|--------|---------|---------|---------|---------|---------|--------|-------|
| C.W. PHONE | W6KYV  | 34—82  | WØCMH  | 30—18  | W2PQJ  | 32—91   | Zone 20 | W9WCE   | 27—69   |         |        |       |
| Zone 1     | W6QWL  | 32—83  | W5CPI  | 29—75  | W8JM   | 29—68   | SVIRX   | 31—93   | W5ERY   | 26—73   |        |       |
| KL7KV      | 32—65  | W6ZZ   | 32—79  | WØAZT  | 29—60  | W2OM    | 29—65   | Zone 25 | WØSBE   | 26—61   |        |       |
| KL7KI      | 19—31  | W6BIL  | 32—65  | W5EWZ  | 29—51  | W1MRP   | 28—81   | J2AHI   | 18—35   | VE3BBZ  | 24—52  |       |
| VE8AS      | 14—18  | W6LER  | 32—53  | W8MQR  | 28—57  | W3AQT   | 28—59   | Zone 27 | W8LFE   | 16—23   |        |       |
| KL7CZ      | 12—12  | W6MXN  | 30—72  | W9MZP  | 28—49  | W4TO    | 27—95   | KG6AI   | 28—51   | Zone 5  |        |       |
| KL7DE      | 8—11   | W6CID  | 27—39  | W5ZD   | 27—75  | W2BF    | 27—72   | Zone 30 | W1JCX   | 35—127  |        |       |
| Zone 2     | W6EYC  | 25—47  | WØUOX  | 27—57  | W4JUJ  | 27—60   | VK2DI   | 40—147  | W1NWO   | 35—124  |        |       |
| VO6EP      | 38—134 | W6OKL  | 24—55  | W8BF   | 25—68  | W1CJH   | 26—66   | Zone 31 | W4ESP   | 35—110  |        |       |
| VO6J       | 15—38  | W6AGT  | 24—144 | W9EHS  | 24—56  | W4ALJ   | 26—52   | KH6IJ   | 39—102  | W1ATE   | 35—97  |       |
| Zone 3     | W6VAT  | 24—37  | W8LFE  | 23—38  | W3RJS  | 25—52   | KH6LF   | 36—96   | W1FJN   | 33—97   |        |       |
| W6PFD      | 40—189 | W6MGZ  | 23—29  | W5JPC  | 22—45  | W21OP   | 23—47   | KH6NB   | 36—72   | W4HA    | 32—104 |       |
| W6SN       | 40—185 | W7PK   | 21—49  | W8NKU  | 21—46  | W2PUD   | 23—40   | Zone 32 | W2RGV   | 31—76   |        |       |
| W6ENV      | 40—184 | W6MIO  | 19—22  | W9KMN  | 15—13  | W4IK    | 21—46   | ZL1HY   | 33—82   | W2IUU   | 30—72  |       |
| W6ITA      | 40—179 | W6UXF  | 17—18  | Zone 5 | W1HJ   | 21—44   | ZL2GX   | 32—96   | W2DYR   | 29—78   |        |       |
| W6NNV      | 50—161 | Zone 4 | WIENE  | 39—163 | W4CY   | 21—43   | ZL1QW   | 20—39   | W2PQJ   | 25—54   |        |       |
| W6KRI      | 40—155 | W9VW   | 40—153 | WINMP  | 39—159 | W1QCJ   | 21—38   | Zone 36 | W1CJH   | 23—52   |        |       |
| W6AM       | 40—153 | W8EWS  | 40—150 | W3DPA  | 39—145 | W8NPZ   | 18—41   | FESAB   | 32—78   | W1EQ    | 22—52  |       |
| W6RM       | 40—148 | WØYXO  | 40—146 | W1BIH  | 39—133 | W4BRB   | 16—36   | Zone 37 | W2BF    | 20—44   |        |       |
| W6OMC      | 40—147 | W9IU   | 39—175 | W1AB   | 39—121 | W4HKJ   | 13—21   | VQ3HGE  | 39—122  | Zone 6  |        |       |
| W6PQT      | 40—131 | W9NDA  | 39—167 | W3DRD  | 38—138 | Zone 7  | TG9JK   | ??—80   | Zone 38 | XE1AC   | 34—33  |       |
| W6WKU      | 40—121 | W9LM   | 39—157 | W1JYH  | 38—132 | Zone 8  | Zone 8  | ZS2X    | 39—126  | Zone 7  |        |       |
| W6UCX      | 40—127 | W5ASG  | 39—152 | W3IYE  | 37—120 | Zone 8  | Zone 8  | PHONE   | TG9AD   | 22—35   |        |       |
| W6SRU      | 40—117 | W8SDR  | 39—130 | W3EPV  | 37—110 | KP4HU   | 29—113  | Zone 3  | Zone 8  | Zone 8  |        |       |
| W6HZT      | 40—115 | WØGKS  | 39—123 | W3OCU  | 36—140 | KU4AD   | 28—65   | W7HTB   | 38—117  | KV4AD   | 27—55  |       |
| W6UZX      | 40—114 | W9GA   | 39—106 | W4JFE  | 36—137 | KP4KD   | 21—48   | W6DI    | 37—141  | Zone 10 |        |       |
| W6JRU      | 40—113 | W9LNM  | 39—133 | W1AWX  | 36—104 | Zone 10 | OA4AK   | 36—116  | W6CHV   | 32—97   | OA4AK  | 30—68 |
| W6FSJ      | 40—92  | WØEYR  | 38—120 | W2TJF  | 35—125 | Zone 11 | Zone 11 | W6ITA   | 31—90   | Zone 13 |        |       |
| VE7ZM      | 39—119 | VE3QD  | 36—132 | W1BFT  | 35—111 | Zone 12 | Zone 12 | W6PXH   | 30—100  | CE3AB   | 31—99  |       |
| W6ANN      | 39—109 | W9CIA  | 36—121 | W2EMW  | 35—110 | Zone 12 | Zone 12 | W6AM    | 27—52   | Zone 14 |        |       |
| W6QD       | 39—97  | W9TB   | 36—89  | W2RGV  | 34—101 | CE3AG   | 39—133  | Zone 4  | G3DO    | 35—106  |        |       |
| W6GAL      | 38—140 | WØDU   | 35—118 | W3WU   | 34—98  | CE7AA   | 35—33   | W9NDA   | 36—111  | Zone 14 |        |       |
| W6WWQ      | 38—81  | W8GLK  | 34—103 | W2AW   | 34—95  | Zone 14 | Zone 14 | W9RBI   | 35—117  | F8DC    | 28—47  |       |
| W6LN       | 38—72  | W4HA   | 34—116 | W4LVV  | 33—119 | F8BS    | 39—149  | W9HUD   | 34—109  | Zone 25 |        |       |
| W6MI       | 36—83  | WØSBE  | 33—95  | W2WW   | 33—87  | G3DO    | 39—121  | W5ASG   | 32—99   | J2AHI   | 19—31  |       |
| W6MUF      | 36—77  | W9WCE  | 32—96  | W2MEL  | 33—87  | ON4MS   | 35—76   | W8NK    | 31—70   | Zone 31 |        |       |
| W6OEG      | 35—80  | WØCFB  | 32—90  | W3NOH  | 32—108 | EA5BE   | 29—73   | W5LWV   | 29—71   | KH6NB   | 26—48  |       |
| W6CTL      | 35—96  | W8KPL  | 32—85  | KH6PY  | 38—94  |         |         |         |         |         |        |       |

# VHF

# UHF

Conducted by VINCE DAWSON, JR., WØZJB\*

**E**VEN THOUGH THE MUF in November did not reach the peak it did a year ago, several openings into DX land has rewarded the die-hards, who remained active on 6 meters, during the winter lull in activity.


Naturally, during the winter months, the v-h-f bands suffer from loss of activity, but with all the 2-meter lads active during the past summer, little did anyone imagine these stations would pile back on the lower frequencies in search of DX. In order to help restore 144-mc activity around Erie, Pa., W3AU, W3GV, W3NOJ, W3QKI, and W3WBM have mailed out a circular letter to approximately 50 stations in Western N. Y. Pa., Ohio, Michigan and Ontario. Two evenings each week, namely Mondays and Thursdays, are the nights designated for getting together, the time is between 2100-2300 EST. DX is not the main reason for these get togethers, which stimulate lots of contacts and rag-chews. All 2-meter stations in this area are urged to set aside these evenings and make a few contacts.

#### F-2 Openings

As mentioned previously, a few of the 50-mc gang were sufficiently active to take advantage of several F-2 openings that occurred in November.

Indications, in late October, were that the MUF might swing over the 50-mc boundary any day. The first opening reported to us was a contact between G5BY and ZS1P, Nov. 1, between 0918-1004 EST. Signals had a slow rolling fade from S7 to the noise level. ZS1P was last heard at G5BY around 1009 EST, when the signal settled into the noise and disappeared. G5BY mentions

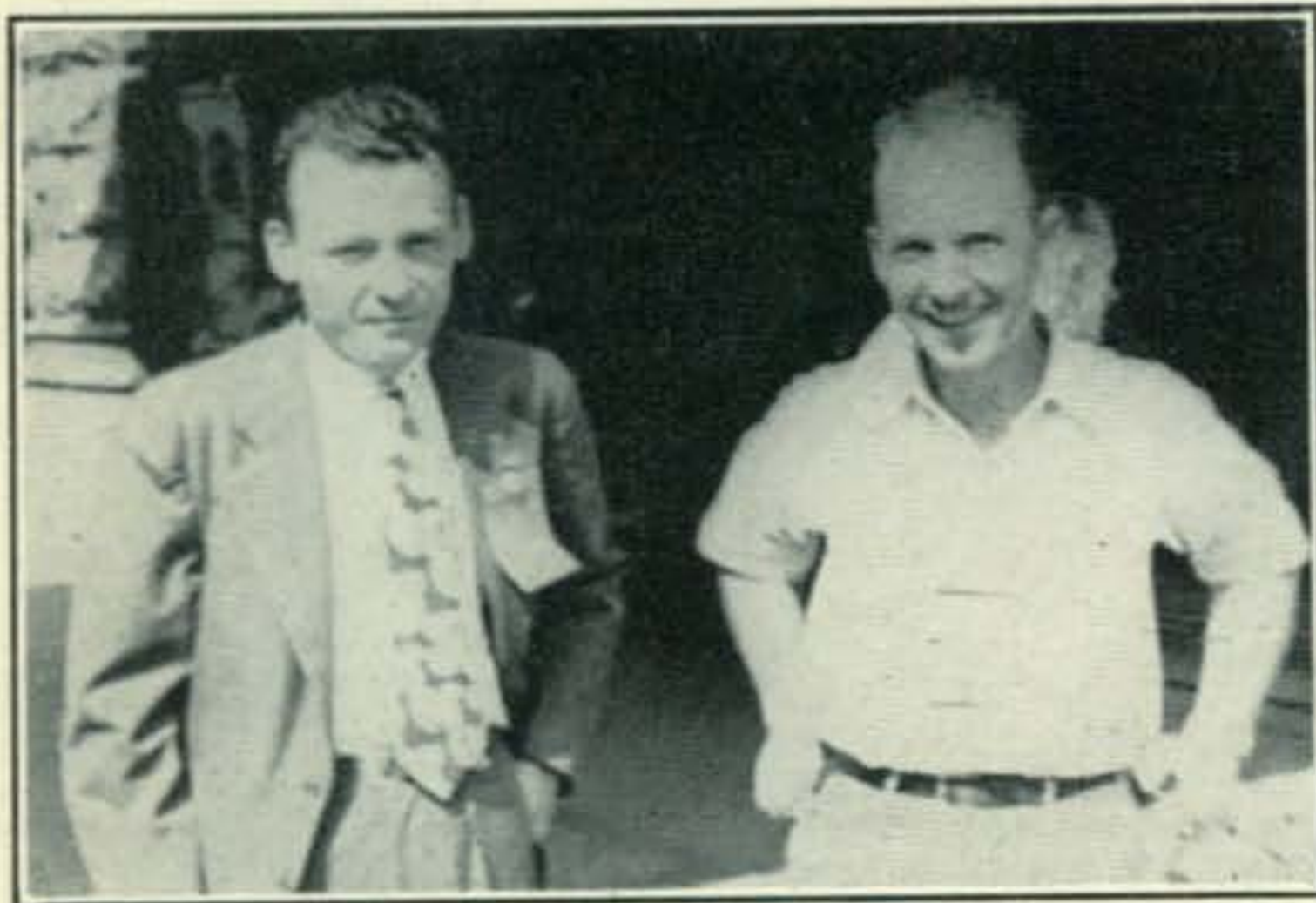*\*Send all contributions to Vince Dawson, Box 827, Gashland, Mo.*



OA4AE and W9ALU. Two top-notch 6-meter DX men talk it over at Milwaukee.

that the peak MUF days for the North Atlantic path in October, were the 22, 25 and 27, when harmonics up to 47 mc were heard. On Nov. 13, the MUF was up to 48 mc at 1300 EST, and on Nov. 17, WKI7 came through on 48.5 mc. Within 30 minutes the MUF had dropped back 9 mc and the Ws went out on 28 mc at the same time; WWV was sending Ns during this period.

Nov. 9, between 1110-1140 EST, the California and Washington paths to the east coast appeared to be open for Ferrell in Philadelphia. Numerous diathermy and other harmonics were found in the 50-51 mc spectrum, as well as, the rebound scatter from the Zenith FM station in Chicago on 45.1 mc. The latter is usually a good indication that the MUF is exceeding 50 mc. During this same date W7QLZ heard signals up to 48.7 mc, W5ML heard harmonics from the northeast up to 47.4 mc around 0900 CST; while W7HEA heard FM stations around 46 mc. Later in the evening the 50-mc band was open via Es from Wyoming to the middlewest.

The trans-continental path across the U.S. was open on Nov. 13, when W7DYD near Seattle worked, from 1135-1145 PST, W2BYM with S5 signals. Nov. 14 was better for W7DYD, when he worked W2BYM, VE1QY, and heard W1CLS, between 0940-1158 PST. The signals from VE1 were S9, while the W1s were much weaker. During this opening W2BYM was heard calling VE7CN. Nov. 15 W7DYD had contacts with W1CLS, W1ATP, and W1FMH, between 0955-1028 PST with fair conditions.

On Nov. 21 HC2OT, ex-W5DNN, worked into W5-W8. Although reports are not complete at this writing, W5AJG worked him at 0900 CST with S9 signals for Leroy's eighth country. At W5AJG the 85' 4-element beam was 12 db better than the same type of antenna at 35'. W5AJG also mentions that HC2OT was coming into W5 on Nov. 20, although Leroy was unable to be active on that date. In Metamora, Ill., W9ALU had his beam on G land at 0900 CST, Nov. 21, when HC2OT was heard off the ends. HC2OT peaked S9 for about 4 minutes, then faded out. W8CMS, W8MVG and W8NQG also worked HC2OT on Nov. 21, with S9 signals.

See Report Section for further information on the openings, as reported by dates.

#### 50-mc Notes

Charles Rice, W8MVG, has been hearing very weak signals up to 50.2 mc almost daily. These carriers peak on Africa, but bad QSB prevents identification. Tone modulated signals are sometimes heard right up to 50 mc.

In California Ray Bloemer, W6QG, has been missing some of the 50-mc DX because of WGBA-



Ample connections  
for coils and leads

Steatite frame bars

Right angle drive

Steatite insulated rotor

Rotor grounded  
at center

NATIONAL LMT Condenser

## new heavy duty condenser gives BETTER CONTROL OF HARMONICS

Now, for the first time, a heavy duty transmitting condenser that completely eliminates troublesome closed loops, vastly simplifying the problem of unwanted harmonics. The rotor shaft is completely insulated from the end plates. Absolutely no extraneous capacity! Rigid and stable construction. Long leakage path (higher safety factor). Plates and parts are extra heavy with highly polished rounded edges to prevent flash-over. Adjustable stator plate mounting and end bearings. Multi-fingered spring contact. Center tap ground makes this condenser ideal for push-pull operation. Available in single-stator, double-stator, or double-stator right angle center drive models. Same capacities as National TML Condenser.

*The National LMT Condenser is only one of many National precision components. See your dealer or write for catalog.*

**National**  
© **NC** EST. 1914  
**NATIONAL COMPANY, Inc.**  
MALDEN, MASSACHUSETTS

FM in Springfield, Mass., on 48.1 mc, although it is a good marker and indication that 6 meters is open. The thing that Ray complains about is that they always drag out the national anthem, and while he is standing at attention, the 50-mc band opens and closes before he can sit down.

Tom Stence, W8NQG, says that his heart stopped beating for 5 minutes on Nov. 21 at 1003 EST, for he called CQ on six with his beam pointed south and HC2OT answered him, on what Tom thought was a very dead and lonely band. Tom requests no flowers, just more nice surprises like that, for the v-h-f heart is plenty strong at his QTH.

VE7CN says that on the recent transcon openings on Nov. 13-14-15 a very interesting thing happened. VE7ABO, who is 100 miles farther away and the same distance from any active 6-meter station, heard W1CLS, HPC, FMH, ATP, as well as W7ERA, DYD, LMF, VE7CN, AEZ and VE7NM. The receiver was an SX-43 with a long wire antenna. No doubt the W7s and VE7s were being received via scatter rebound, while the W1s were F-2 hop, yet VE7CN was unable to hear any of the rebound scatter, nor as many of the W1s.

In Sheridan, Wyo., W7JRG says that the lack of aurora openings for him is something to comment on. Ken has watched the band whenever it appeared probable that aurora reflections might occur, but to date his only contacts are via Es, for there just isn't any F-2 or locals to work. After listening to the horrible QRM on the lower frequencies, Ken is convinced that 6 meters is the band for him and is now trying to promote some local activity, for he well remembers the FB QSOs he had with such members of the 50-mc fraternity as W9ZHL, W4FWH, W6IWS and W6BPT.

Ed Gessert, W5ELL, in Albuquerque, is now off the air due to moving to a new QTH. Getting back on the air will be quite a bit of work for Ed, as it involves building a shack in the garage, putting up two towers and installing a heater in the shack.

W5AJG says the QSL business is too good, for it bites into his operating time on the v-h-f bands. Both W5AJG and W5ML in Oil City, La., are having a feud these days, both trying to outdo the other.

Things have been quiet around W6-land according to W6AMD. Roy did hear an FM sta-

tion on 49 mc on Nov. 14 from 1102-1126 PST, but nothing came through in the 50-mc region.

W8LBH is trying to work up a 6-meter net in Ohio, anyone interested contact Bud for further information. W8LBH has a 522 converted to 50 mc, feeding into a 3-element workshop beam, with which he has worked 21 states.

Basil, at VE5NC, has a new converter using a 6J6 and 6C4 that covers between 28-47 mc, which feeds into a 522 i-f strip. The ratio detector isn't doing so well, but for AM works well above 40 mc. A regular communications receiver with sharper i.f.'s is used on 28-30 mc, but the broad response of the 522 i.f. above 30 mc is an advantage, in that additional selectivity is not of much use and the tuning of the converter becomes less critical. The highest MUF Basil has heard so far this year is 44.5 mc.

In Tulsa the 6-meter gang meets nightly at 2000 CST, then looks for W5HTZ, W5GNQ and W5HLD, all around 100 miles away. Activity is up on 50 mc in Tulsa with these on: W5WI, HFY, FFW, OPI, MEY, OOJ and W5LEI. W5LEI found out how to open the 6-meter band by just calling plenty of CQs when short-skip is in on 28 mc. Of course the other end of the deal is to have the W7s in Arizona working on their receivers and happen to tune you in. This happened with both W7OWX and W7QLZ when W5LEI was heard on Oct. 29.

W9NJT is operating on 6 meters exclusively and does the same as everyone else, complains that activity is too low. Don has as locals to depend on, W9OFL and W9VZP, the rest of the gang having gone to W6QDs land of DX. But that's not as exciting as v.h.f. says W9NJT, for anyone with 15 watts tied to their bed springs can work DX. Well at least that's a new way of putting it; W6QD please copy.

#### Propagation Log

Oct. 26—Ionospheric conditions unsettled, but MUF across Atlantic reached 42.1 mc while trans-continental MUF reached 42.7 mc. Some sporadic-E during late evening in the southwest. W6IWS worked VE7AEZ. W7QLZ worked W5GNQ, W5HTZ, W5EHR, W5LEI and heard several W4s. W6AMD worked W5ZZF. W5LEI also worked W7OWX and W7FFG.


Oct. 27—Mild ionospheric disturbance, various path MUFs did not exceed 39.0 mc.

Oct. 28—W5ML worked W9ALU at 0920 CST on a quick sporadic-E opening. Peak Atlantic




Left to right: W4JBE, W2-TP, unidentified, W8QYD, W4SBF, W0WGZ, W0-VIK, W9JIL, and W5HLD. Photographed after the v-h-f meeting conducted by W0ZJB at the National A.R.R.L. convention.
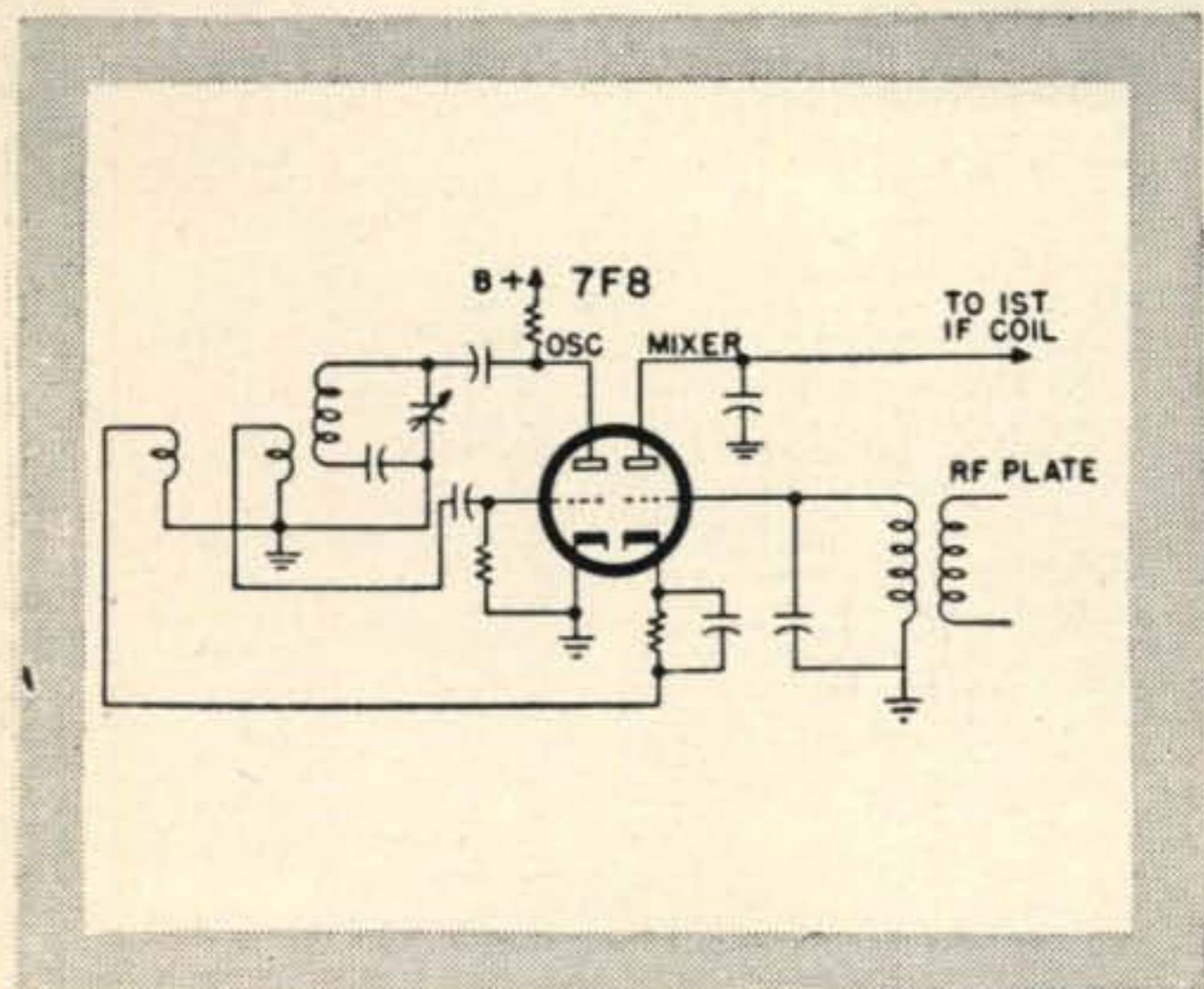
# Two Reasons Why the SX-43 Is Extra-Hot on 6 Meters --



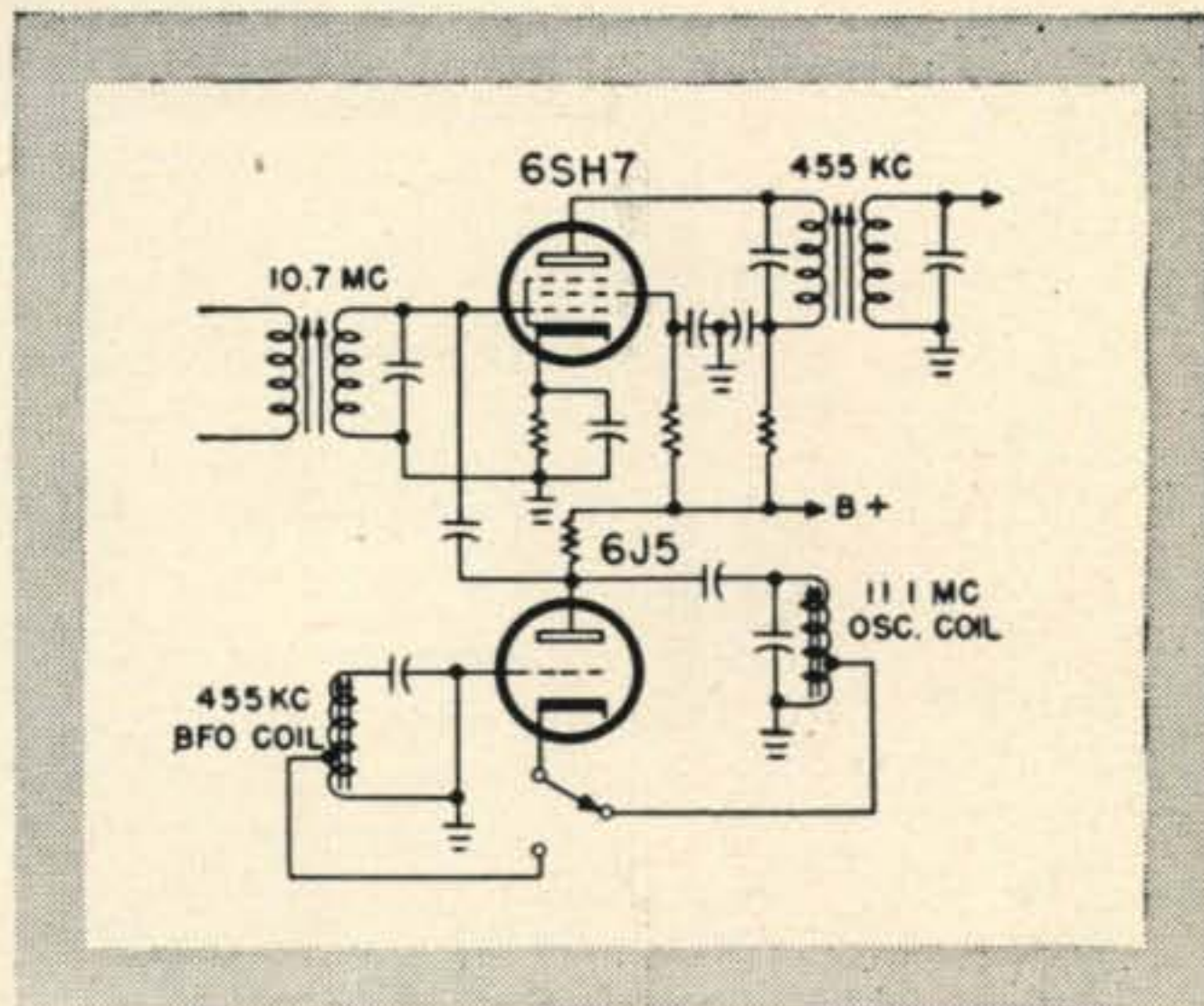**TRIODE MIXING . . .** in the first detector. This quieter method of conversion greatly boosts the signal-to-noise ratio because there's almost no first detector "hiss." Inductive coupling (rather than electronic) of the oscillator signal avoids multi-grid noise in the sensitive 50-Mc range.



**DOUBLE SUPERHET . . .** After two stages of IF at 10.7 Mc, this 6SH7 makes a second conversion down to 455 kc for ample selectivity, plus complete absence of images. The 6J5, which is used as BFO on other bands and otherwise idle on this band, acts as local oscillator. No extra tubes, yet plenty of extra performance!



SX-43 \$189.50

**Before you buy, see and try the SX-43.** Compare its features . . . learn the thrill of its superior performance. At its price, it's the hottest thing available—by far.

**Range 540 kc to 55 Mc plus FM Band 88—108 Mc;** other features include calibrated bandspread, one stage tuned RF, temperature compensated oscillator, crystal filter, two stages IF, tuning meter, two stages audio; 10 tubes plus rectifier.

## the hallicrafters co.

4401 W. Fifth Ave., Chicago 24, Ill.

**Manufacturers of precision radio and television equipment.**

MUF just under 46.0 mc, trans-continental MUF about 41.0 mc.

Oct. 29—Conditions ionospherically quiet, but MUF did not appear to go above 44.0 mc on any path.

Oct. 30—Same as above, but probably did not exceed 44.5 mc.

Oct. 31—Same as above, but probably did not exceed 43.5 mc.

Nov. 1—G5BY worked ZS1P at 0918 EST. Northwest MUF lower than 40.0 mc. W6QG heard Hawaiians on 46.2 mc at 1330 PST. W6AMD worked W5JLY at 2222 EST during the onset of a moderate ionosphere storm.

Nov. 2, 3, 4, 5 and 6—Conditions poor to fair, some ionospheric disturbance during first three days. Peak MUF reported only 42.4 mc on any path.

Nov. 7—Conditions improved greatly over day before, but peak was only 44.5 mc.

Nov. 8—Northeast MUF up to about 46.0 during morning. W8CMS worked W5HTZ at 2258 EST via some thin sporadic-E.

Nov. 9—Ferrell thinks 6 meters was open around 1115 EST for trans-continental F2 work. Carriers were heard up to 51.0 mc. W6QG reports MUF exceeding 46.5 mc at same time. Very good sporadic-E opening during the evening between W7 and W9, WØ. W7ILL and W7JRG worked over 20 different stations from 1907 to 2153 MST.

Nov. 10—North Atlantic MUF shot up to over 47.0 mc during the early morning. Ferrell heard Stockholm, Paris, and London TV and FM until 1115 EST. W6QG and W7QLZ heard FM stations up to 46.0 mc from the east coast. W5ML heard up to 46.5 mc from the southeast. W9ALU worked W5JLY at 2311 EST.

Nov. 11—Trans-Atlantic conditions slightly down, but trans-continental MUF was over 46.5 mc. Conditions were ionospherically quiet.

Nov. 12—Trans-Atlantic MUF exceeded 45.5 mc from 1005 until after 1130 EST. Trans-

continental MUF was about 45.5 mc. Lower W7 and W6 to W5 was open from 1845 to after 1930 PST.

Nov. 13—Trans-Atlantic MUF was above 47.0 mc. At 1355 EST W7DYD heard W2BYM, finally making contact at 1435 EST. VE7CN heard signals up to 50.3 mc. W2BYM heard him, but no contact was made. W7QLZ and Ferrell both were inside the skip and heard signals only up to 45.0 mc.

Nov. 14—Trans-Atlantic MUF again exceeded 47.0 mc, but no one seems to get through on 50.0 mc. VE7CN worked W2BYM on c.w. at 1445 EST. W6AMD heard an FM station on 49.2 mc at 1402 EST. W7DYD worked W2BYM. VE1OY and W1CLS until 1458 EST. Ferrell, W7QLZ and W6QG again were inside the skip and heard nothing above 46.5 mc. Band opened for sporadic-E W1 to W4 and eastern W5 from 2100 to 2200 EST. W5JTI, W4LNG and W4GMP were on.

Nov. 15—W7DYD and W6QG both heard the FM station on 48.1 mc from 1240 EST. Later from 1255 to 1328 W7DYD worked W1CLS. W1ATP and W1FMH. VE7CN also worked W1CLS. VE7ABO heard numerous W1 signals and considerable rebound scatter back from W7 and VE7 signals. This opening preceded ionosphere storm by about eight hours. W7QLZ reports sporadic-E to W5 around 2140 EST. W1CLS worked VE7CN on phone and c.w., plus W7ERA, VE7AEZ and VE7NM. W6IWS also heard W1CLS.

Nov. 16—Trans-continental MUF exceeded 49.0 mc around 1245 EST, but no 6-meter signals were reported as getting across. Conditions unstable.

Nov. 17—Conditions again unsettled, but MUF reached to 43.0 mc during the mid-day. A W8 to W5 sporadic-E opening from 1900 until 1945 EST.

Nov. 18—W6QG had a short opening (it was about time) working W1CLS at 1255 EST and hearing W1HMS. W7QLZ heard signals up to

(Continued on page 80)

## 50 MC HONOR ROLL

| CALL  | S. | C. | CALL    | S. | C. | CALL  | S. | C. | CALL    | S. | C. |       |    |    |
|-------|----|----|---------|----|----|-------|----|----|---------|----|----|-------|----|----|
| W9ZHB | 48 | 6  | WØINI   | 42 | 3  | W2RLV | 37 | 6  | W6AMD   | 34 | 3  | W1AF  | 27 | 5  |
| WØZJB | 48 | 4  | W7HEA   | 42 | 3  | W5FSC | 37 | 6  | W7JPA   | 34 | 2  | W7ACD | 27 | 2  |
| WØNFM | 47 | 5  | WØKPK   | 42 | 2  | W5JTI | 37 | 5  | W7JRG   | 27 | 2  | W7JRG | 27 | 2  |
| W9QUV | 47 | 4  | W8QYD   | 41 | 4  | W4EQR | 37 | 4  | W1HDQ   | 33 | 6  | W5LGB | 26 | 3  |
| W6UXN | 47 | 3  | W3CIR/1 | 41 | 3  | W5VV  | 37 | 4  | W6PUZ   | 33 | 4  | WØDNW | 26 | 2  |
| WØUSI | 47 | 3  | W5ML    | 41 | 3  | W6IWS | 37 | 3  | W4WMI/4 | 33 | 3  | WØYKX | 26 | 2  |
| W6WNN | 47 | 3  | W8ZVY   | 40 | 7  | W6OVK | 37 | 3  | W4DRZ   | 33 | 3  | W7BOC | 26 | 2  |
| W4GJO | 46 | 4  | W4QN    | 40 | 4  | W9NJT | 37 | 3  | W7KAD   | 33 | 3  | WØUEL | 26 | 2  |
| W9DWU | 46 | 3  | W1LLL   | 40 | 4  | W7DYD | 37 | 2  | W3MKL   | 33 | 2  | W6NAW | 26 | 2  |
| WØDZM | 46 | 3  | W4FBH   | 40 | 3  | W9UNS | 37 | 2  | W1CLH   | 32 | 3  | W7QLZ | 25 | 3  |
| W9ZHL | 45 | 6  | WØSV    | 40 | 2  | W7FDJ | 36 | 3  | W5WX    | 32 | 3  | VE1QZ | 24 | 6  |
| W1CLS | 45 | 5  | W4GIY   | 40 | 2  | W3OR  | 35 | 6  | W6FPV   | 31 | 3  | W5LIU | 24 | 3  |
| W7BQX | 45 | 4  | W5JLY   | 39 | 10 | W1GJZ | 35 | 5  | W4HVV   | 30 | 2  | G5BY  | 24 | 19 |
| W9PK  | 45 | 3  | W1CGY   | 39 | 6  | W6BPT | 35 | 4  | WØDER   | 30 | 2  | XE1KE | 23 | 6  |
| W8NSS | 45 | 3  | W6ANN   | 39 | 3  | W1JLK | 35 | 4  | W4FNR   | 29 | 3  | W9AB  | 23 | 4  |
| W7ERA | 44 | 4  | WØDKS   | 39 | 3  | W9VZP | 35 | 4  | W8MVG   | 29 | 6  | W8YLS | 22 | 3  |
| W7FFE | 44 | 4  | WØYSJ   | 39 | 2  | W9UIA | 35 | 3  | W5ELL   | 29 | 2  | W7CTY | 22 | 2  |
| WØQIN | 44 | 4  | W4GMP   | 39 | 2  | W5HF  | 35 | 3  | VE1QY   | 28 | 4  | W8LBH | 21 | 2  |
| W5VY  | 43 | 11 | W2AMJ   | 38 | 6  | W5HTZ | 35 | 3  | W9FKI   | 28 | 4  | W5HVP | 20 | 3  |
| W5AJG | 43 | 8  | W5FRD   | 38 | 6  | W5HTZ | 35 | 3  | W4FQL   | 28 | 3  | VE7CN | 17 | 2  |
| W4EQM | 43 | 3  | W2IDZ   | 38 | 5  | W2BYM | 34 | 4  | W1ATP   | 28 | 3  | VE7CN | 15 | 2  |
| W9ALU | 42 | 5  | W3OJU   | 38 | 5  | W3RUE | 34 | 3  | W5ESZ   | 28 | 2  | W8EP  | 14 | 2  |
| WØBJV | 42 | 3  | W4FID   | 38 | 4  | WØJHS | 34 | 3  | W9MBL   | 28 | 2  | KH6PP | 5  | 7  |

**HARRISON HAS IT!**

# 73 FOR YOUR MOST HAPPY AND SUCCESSFUL 1949 AD!



... And we can make you happy by giving you the best damned service for all your requirements — every standard item that's made and FB bargains in Harrison Select Surplus, too.

Remember — Harrison Has It!

## FB GEAR!—SOME SMASHING PRICE REDUCTIONS

### RECONDITIONED RECEIVERS

As one of the biggest distributors of Ham equipment in the country, we always have on hand a wide selection of good trade-ins—of special appeal to the value conscious buyer.

Many are "like new" at substantial savings. The receivers listed here are reconditioned and in perfect operating order. Of course, satisfaction is guaranteed!

|                                     |          |
|-------------------------------------|----------|
| BUD VFO-21 with 2 sets coils.....   | \$ 37.50 |
| HALLICRAFTERS S-38 .....            | 37.50    |
| HALLICRAFTERS S-40A .....           | 80.00    |
| HALLICRAFTERS SX-43 — less speaker  | 152.50   |
| RME-45 — with speaker.....          | 125.00   |
| RME VHF-152 .....                   | 64.00    |
| RME DB-20 .....                     | 54.00    |
| NATIONAL NC-173 — with speaker..... | 145.00   |
| NATIONAL NC-183 — with speaker..... | 215.00   |
| NATIONAL HRO-7T COMPLETE.....       | 240.00   |
| HAMMARLUND HQ-129X — with speaker   | 135.00   |
| SONAR CFC .....                     | 39.00    |
| SONAR XE-10 .....                   | 32.50    |

The ones listed above are the "pick of the crop"—come in and look over our "as is" SUPER BAR-GAINS!


At any time within a month, you can return your used receiver and I will allow you full credit toward the purchase of a new receiver.

### NEED ANY MOBILE GEAR

|   |          |
|---|----------|
| ABBOTT—TR-4B 2-meter xmtr-rcvr for fixed station or mobile. Regular net \$52.00. Special.....   | \$29.95  |
| Kit of tubes for TR-4B including HY75.....  | \$6.95   |
| GONSET—JUST RELEASED! Model "3-30" Mobile Converter—Continuous coverage 3 to 30 MC. Same size as the famous "10-11".....                | \$39.95  |
| The latest Model "10-11".....   | \$39.95  |
| Gonset Noise Clipper.....   | \$8.25   |
| HARVEY-WELLS—TBS 50 (with all tubes).....   | \$99.50  |
| TBS-50A With speech amp. for xtal mike.....   | \$121.25 |
| LYSCO—Brand new mobile phone xmtr—8 watts output—Requires 6V at 2A, up to 350V at 110 MA. Wired and tested, less tubes and accessories. |          |
| Model 129 — 27 to 29.7 MC.....  | \$23.95  |
| Model 175 — 3750 to 4009 KC.....  | \$23.95  |
| Kit of three tubes for LySCO mobile xmtr.....   | \$4.98   |
| STANCOR—ST203A 10-Meter Mobile Kit.....   | \$44.70  |
| Kit of 5 tubes required for ST203A.....   | \$8.30   |
| SUBRACO—The new improved MT-15X, complete with tubes, xtal, connectors and microphone.....  | \$89.95  |

### ACCESSORIES

|  |         |
|--|---------|
| 96" Stainless steel whip antenna (AS-196) with insulated bumper mount. (NA).....                   | \$7.05  |
| VIBRATOR PACKS—FULLY FILTERED—6 Volt DC input. 300 Volt, 100 Milliamperes output.....              | \$14.95 |
| 400 Volt, 150 Milliamperes output.....   | \$31.20 |
| CARTER MAGMOTOR MAS-420—6 volt DC input, 400 volts, 200 MA output. Very compact!.....              | \$38.42 |
| CARTER GENEMOTOR 420A—6 Volt DC input, 400 volts, 200 MA output. Continuous rating!.....           | \$39.34 |
| T-17B—Made by Shure, this model that we offer has superior quality and pickup characteristics..... | \$1.98  |

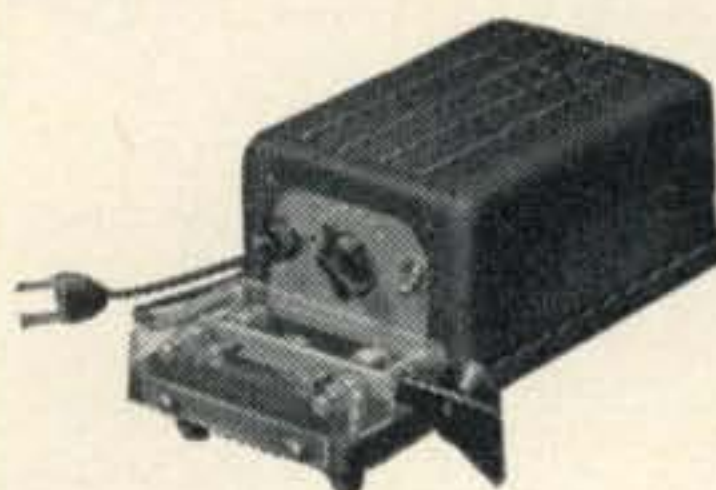

### "MON-KEY"

Have a tape-perfect fist! The electronic MONitor-KEYer makes uniform dots, dashes and spaces—speed variable from 8 to 45 WPM. Built-in speaker permits monitoring and code practice. Internal keying relay.

Complete with tubes for 110 Volts AC-DC  
In New York Only Harrison Has It! **\$29.95**

### TRANSMITTER SPECIALS

HALLICRAFTERS BC610E—Late model, factory modified for 10-meter operation. Reconditioned and guaranteed! Complete with speech amplifier and coils for 10-20-10-89. **\$895.00**

(\$5.00 extra for crating, if shipped)

SUPREME AF-100 AM-FM-CW! 100 watt carrier on AM phone! Built-in VFO. Regular net \$550.00 One new demonstrator available for only **\$450.00**

TEMCO RA (2-A) Deluxe 150 watt phone and CW xmtr. VFO! A beautiful rig. Regularly priced at \$603.75, a new demonstrator is available with coils for 10 meters. This is a real BUY! **\$450.00**

### WE SHIP TO ANY PART OF THE WORLD!

Please send ample for postage. We refund every cent not used. Deposit required on all C.O.D. orders unless you are one of my regular customers. Happy to fill any order but please try to make them more than \$3.00.

### Save 50% on Vitamite Batteries



Rechargeable miniature wet cells for hobby or radio use. Leak-proof, non-spill, extremely long life! **SPECIAL**

|                             |               |
|-----------------------------|---------------|
| 2.2 V—Wt. 1 oz. Reg. \$2.35 | <b>\$1.20</b> |
| 2.2 V—Wt. 6½ oz. Reg. 5.00  | <b>2.50</b>   |
| 4.4 V—Wt. 4½ oz. Reg. 5.00  | <b>2.50</b>   |

Charger with clips to operate from 110V AC. This charger can be used to trickle charge any battery up to 6 volts. Complete..... **\$1.95**

### DC DIRECTION INDICATING SYSTEM

Works on 6 to 15 volts DC—only 50 MA 3" diameter, 360° compass dial has luminous pointer and characters. Panel mount. Excellent for beam or wind indicator, etc. Brand new! Full instructions included.

|  |               |
|--|---------------|
| Transmitter and indicator.....               | <b>\$7.45</b> |
| Set of two AN plugs.....                     | <b>.98</b>    |
| Xfmr and rectifier for 110V AC operation.... | <b>1.97</b>   |

### HARRISON HAM-A-LOG

Don't miss another issue of the Ham-A-Log! Pages packed with Ham news and hints. Outstanding buys in standard and HSS parts and equipment. Send us your name and call today!



**HARRISON**  
RADIO CORPORATION

11 WEST BROADWAY, NEW YORK 7

Phone the Lucky 7's — BArlay 7-7777



Conducted by LOUISA DRESSER, W2OOH\*

**B**ACK IN THE April, 1946, issue of *CQ*, when this column was first initiated, one of the objectives set forth by Amelia, W2OLB, was "getting more of a voice for the YL in ham affairs." Whether or not this column has had any influence in this direction, one can only surmise, but it is becoming increasingly apparent that the YLs are receiving more recognition from brother hams.

For instance, the occasion of a hamfest and dinner held recently by the Chester Radio Club at Walbers on the Delaware, Essington, Pa., was, according to club secretary Anabel Gifford, W3NNS, "the first time in the area that the YLs participated in an affair of this sort."

To get in on their good fortune, we joined forces with W3 YLs for the evening, where we met Anabel, W3NNS; Jean Hauff, W3INL, and Adele Burnham, W3OCH, and renewed acquaintance with Mae Burke, W3CUL.

Mae, we learned, was the Chester Club's first YL member, having joined the club back in 1931. She came up with her ticket in 1932, but after a number of years let her license lapse. When the bands opened up after the war she again became interested, and OM W3VR suggested, "Why don't you see if you can get your old call back?" Sure enough, she did, and for the past two years has been active on 80, 40, 20 and 10 c.w., and 10 phone. On 20 and 10 c.w. she runs 250 watts, and 50 watts on 40 and 80. To date Mae has worked

60 countries, has WAS and WAC. She also is active in two traffic nets, one of them the Eastern Shuttle Net at 10:30 a.m. every day, of which, by the way, Tillie, W3NHI, is net control.

Adele, W3OCH, and her OM, W3NYN, are on the air with a converted police transmitter, an S40 receiver and a 3-element Workshop beam, and find they are really getting out with their signals. As Anabel described it: "They have a new QTH, a new beam, and live in Delaware—with all the world before them!" Working a YL in Delaware must be like snagging rare DX!

Jean, W3INL, was our featured YL of the Month in this column in October *CQ*. Since that writing she and OM W3GHS have put up their 70-ft. high 6-element 10-meter rotatable beam, with the stacked 6-element 144-mc beam above it, and Jean is keeping W3INL on the air on 2 meters. Pix of the new beam left us drooling!

Following the hamfest, Anabel and OM Giff took us home with them for the night, and early the next morning we had W3NNS on the air for DX and W contacts, including an FB QSO with Annette, W4LKM, on 10 (so sorry we couldn't stay long enough for the YLRL net!). Between QSOs we gleaned from Anabel how she started in ham radio.

OM W3AAW has been on the air since 1923, but it wasn't until he started operating 5-meter portable-mobile before the war that Anabel became interested. At that time, also, they were using a 2-meter station in a plane, the equipment for which was so big that Anabel was the only one small enough (she's all of 4 ft. 9 in. tall!) to fit in beside it. From the plane she experienced the fun of calling "CQ airborne" and hearing every ground station within range come back to her. After 10 was opened at the close of the war and she heard "all those nice people" she knew she just had to get her license. When the prized ticket finally arrived, Anabel rushed gleefully to the phone to tell the OM, who was at work, that her call was W3NNS. "Ah," came the reply, "Now No Socks"—which, she confesses, is *practically* the case! Though we must add, Giff is perfectly happy with the state of affairs.

For the past year and a half Anabel has been very active on 10, spending every minute of the day she can at the rig. With a 4-element wide-spaced rotary, 125 watts, e.c.o., and an HQ-129X, she keeps her log well filled. Anabel has many regular skeds, among them one with Ruth, W5IZL, and all last year she kept a daily one with Mary, D4ATR (now F7AH). Anabel handles a good deal of traffic, and loves all operating, as is attested by her A-1 Operator and Rag-Chewers' Club certificates.

(Continued on page 70)



YLs attending the Chester (Pa.) Radio Club hamfest. Standing: W3OCH, Adele, and W3INL, Jean. Seated: W3CUL, Mae, and W3NNS, Anabel.

—Photo by W3ADV

# VALUES GALORE MORE FOR YOUR MONEY

## EVERYTHING FOR THE HAM - Distributors of amateur radio equipment and parts.

### MIRACLE KIT VALUE

Good for 2 KW.  
SPECIAL COMBINATION



ALL FOR  
**\$9.95**

#### Kenyon Filament Transformer

Primary 117 V. AC.—50-60 cycle Secondary. Will operate two 304TL's etc. Sec.: 5 Volts, C.T. at 60 amps. Shpg. wt. 26 lbs. 2-304-TL's and 1 filament trans.....**ONLY \$9.95**

One of the most Sensational Values we've ever offered!

#### NAVY TRANSMITTER GP-7

125 watt xmtr., self-contained AC, 400 cycle power supply; uses suppressor grid modulation for phone, VFO controlled, 803 in final; built of std. parts.

Bargain priced.....**\$9.95**. Add **\$1.** for packing.

Can be adapted to radio controlled devices. Was used by pilots to flash a signal lamp on aircraft instrument panel when in range of a beacon transmitter. Responds to modulated signals over a variable range of 62 to 80 Mc. Tube plates and filaments operate directly from 24 V. DC. Can be adapted for radio control of experimental apparatus opening garage doors, etc. Circuit diagram and parts list included on either model shown below. BC-357—contains 12C8 and 12SQ7 tubes and sensitive relay (size 5 $\frac{5}{8}$ " x 5 $\frac{1}{4}$ " x 3 $\frac{1}{4}$ ").



**\$2.95** or 2 for **\$5.00**

Sensational Closeout!

**HUNDREDS OF USES**

Thousands of Valuable Parts

#### R-5/ARN-7 COMPASS RECEIVER

Very late model ADF receiver. Includes broadcast band. Frequency 100 to 1750 kc. in 4 bands. 5-gang tuning capacitor. With 15 tubes: 4—6K7, 1—6L7, 1—6J5, 2—6B8, 2—6F6, 1—6N7, 1—6SC7, 2—2051, 1—5Z4. Schematic Furnished. Like new. SPECIAL..**\$19.95**



2 for.....**\$35.00**


### SEND FOR OUR BIG BULLETIN!

#### SCOOP


110 Mc. REC.

BARGAIN

BC-733 D Localizer Receiver

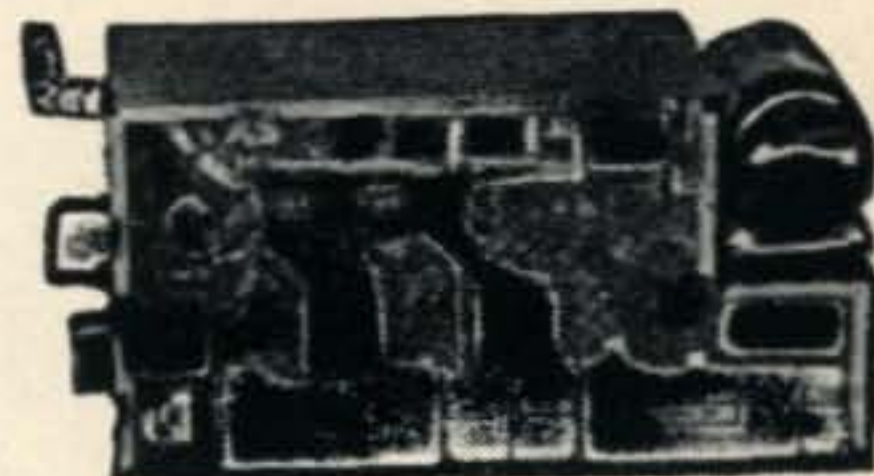

Freq. 108-110 Mc. Tube complement 10 tubes—1—12SQ7, 2—12SR7, 1—12A6, 1—12AH7GT, 2—12SG7, 3—717A. NEAR NEW CONDITION. Companion to the glide path receiver. Also contains 90 and 150 cycle band-pass filters. Has the best AVC system yet developed can use parts or use as a model for construction. 10 tubes, crystals, relays, etc. Schematic included. Don't pass this up. With dynamotor. Only **\$3.95**—2 for.....**\$6.50**

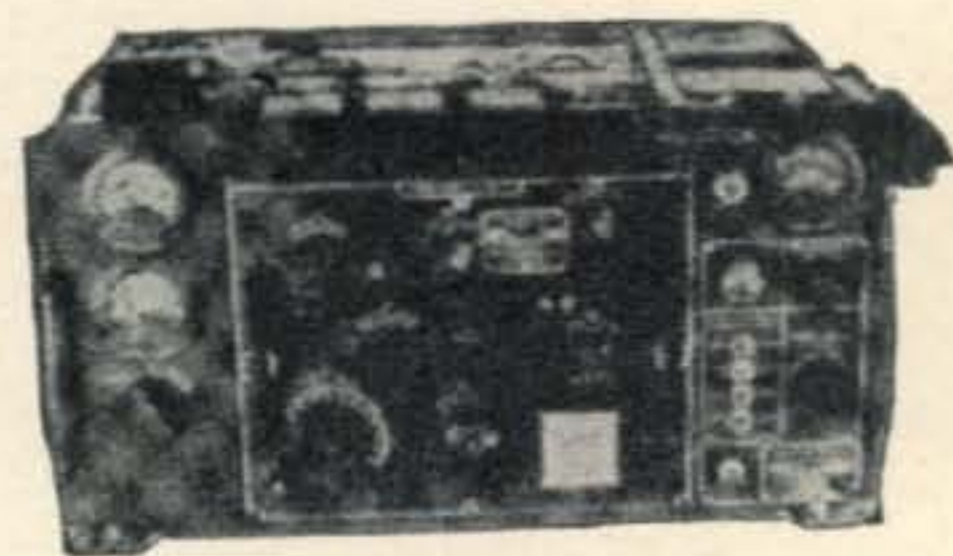

USED

## SPECIAL

Brand New JAN Inspected

**EIMAC 304TL**

**SUPER VALUE 2 FOR \$1.50**

**BETTER ORDER 4 OR MORE TODAY**

**While They Last — Any Quantity**

SUPER SPECIAL

BRAND NEW  
EIMAC 304TH

**\$3.95**  
ea.

JAN INSPECTED

TERMS: F.O.B. Pasadena unless postpaid. No C.O.D.'s under \$2.00. 25% deposit on ALL Orders. All C.O.D.'s shipped by Rail Express. Save freight and C.O.D. fees by sending full price with order and we will ship by fast truck, transportation collect. Californians include 2% sales tax. **BE SURE TO ASK FOR OUR BIG SPECIAL BULLETIN**

# DOW RADIO

1759 EAST COLORADO BLVD.  
PASADENA 4, CALIFORNIA  
Tel. Sycamore 3-1196—L. A. Ryan 16683

# PARTS AND PRODUCTS

R E V I E W

## Exciter-Transmitter

The Hunter Manufacturing Co., Inc., Iowa City, Iowa, is now making a bandswitching v-f-o controlled permeability tuned exciter with an output of 20 watts from 3.5 to 29.7 mc. Featuring



direct frequency reading, individually calibrated scales for all bands, integral crystal calibrator, low impedance link coupled output, excitation control, standby monitoring position, and control circuits for a final amplifier, the unit is housed in an attractive gray cabinet.

## Portable Wire Recorder

Air King Products Co., Inc., Brooklyn, N. Y., are now manufacturing a new portable wire recorder. Model A-725 wire recorder is a complete unit including amplifier and speaker; has immediate playback; records from microphone, radio, phonograph or telephone; incorporates automatic shut off at end of play or rewind; makes perman-



ent recordings or erases automatically when recording over used wire; has plug for cable to record from radio or phonograph; safety lock to prevent accidental erasures. The carrying case is blue gray leatherette, trimmed with nickel hardware. Compact and lightweight, the recorder weighs only 21½ pounds and measures 13¾" x 12" x 9".

## A. F. O.

The new Millen 90711 consists of a 6SK7 compensated electron coupled oscillator of exceptional stability and low drift, a 6SK7 broad-band buffer or frequency doubler, and a 6AG7 tuned amplifier which tracks with the oscillator tuning. The 90711 contains a regulated power supply.

Output sufficient to drive an 807 is available on 160, 80 and 40 meters and reduced output is available on 20 meters. Low impedance output terminals are on the rear of the chassis. A cable and adaptor provide output at high impedance on 160, 80, 40, or 20 meters. A switch on the front panel selects the frequency range to be covered. Good bandspread with a separate scale on the dial is provided on the 80, 75, 40, 20, 12, 11, and 10-meter bands. The full vision calibrated illuminated vernier dial has a separate scale for each of the seven bands plus a 0 to 100 scale.



A switch, separate from the tuning range switch, selects the output band. This enables any tuning range to be used with any output band. A function switch on the front panel can turn on the oscillator alone, the entire v.f.o., or can select remote control so that the v.f.o. can be controlled by the station master transmit-receive switch. Since the output is isolated from the oscillator by two stages, zero frequency shift occurs when the output load is varied from open circuit to short circuit.

## New Literature

A 4-page condensed bulletin of Electro-Voice microphones, stands and accessories is now made available by Electro-Voice, Inc. In this bulletin, the majority of popular E-V models are illustrated and described for quick reference. It includes cardioid dynamic and crystal microphones, broadcast and general-purpose dynamic and crystal Mobil-Mikes, differential microphones, velocity microphones, contact mike, and low-cost multi-purpose Century Microphones. Also includes E-V button-control floor stands, desk stands and mounts, and accessories. A copy of this Bulletin No. 103 may be obtained by writing to Electro-Voice, Inc., Buchanan, Mich.



Happy New Year from all the gang at



**HARVEY**



**NATIONAL NC-57**

540 kc to 55 mc with separate 6SG7 RF amplifier. Bandsread tuning and simple 5-position band switch. Built-in speaker. Shipping Wt. 31 lbs.

**\$89.50**



**SUBRACO  
10 meter XMITTR**

Compact mobile xmittr for "dashboard" mounting. Measures only 5 1/2" x 4 1/2" x 6 1/2", weighs only 6 lbs. Designed to operate at 30 wts. input. Uses 6V6 Tritet xtal osc. quadrupling from 7 to 28 mc driving 2E26 Class C mod. amp. High level Class B modulator capable 17 watts audio. Built-in Coax antenna relay; p.t.t. switch. All controls front panel including illuminated meter, xtal jack, etc. Plate requirements: 300-400 volts at 140-180 ma. Shpg. wt. 8 lbs. Less tubes

**\$79.95; including complete set tubes..... \$87.50**



**MILLEN 92105 SSSR**

Selectable single sideband reception will remove 95% of your QRM difficulties. Use with any rcvr having 455/456 IF. Other IF by changing crystals to your IF. Shpg. Wt. 10 lbs.

**\$75.00**

**HALLICRAFTERS TV**

Push-button tuning covers all 13 channels. Model T-54 in steel cabinet with 7" kine tube. Shpg. Wt. 50 lbs.....


**\$189.50**

Model 61. With 10" kine tube. Shpg. Wt. 65 lbs.....

**\$289.95**

Model T-60, projects 12" x 16" picture. Shpg. Wt. 125 lbs.....

**\$595.00**

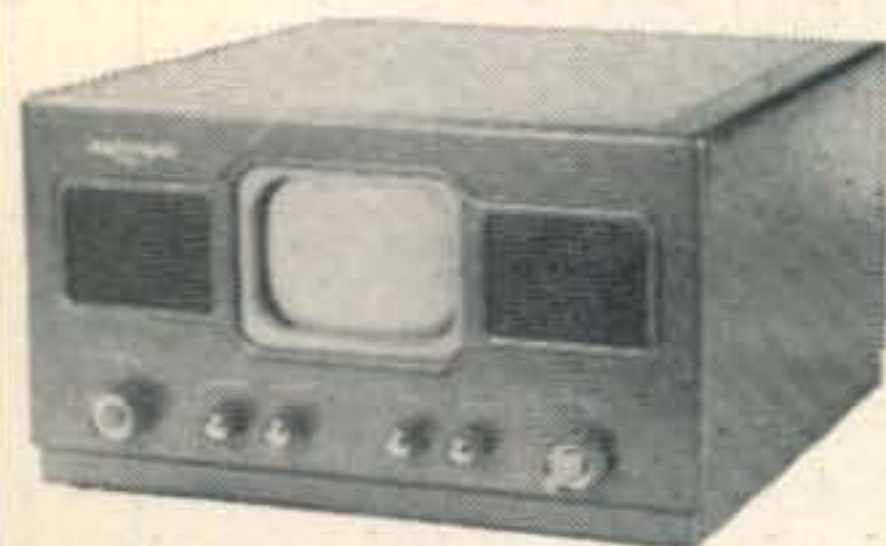

**NATIONAL TV**

All channels, 2 speakers, automatic gain control. Vernier fine tuning. Model 7-M, steel cabinet. Shpg. Wt. 50 lbs.....

**\$189.50**

Model 7-W, same in fine mahogany cabinet. Shpg. Wt. 50 lbs.....

**\$199.50**

**RADIO CRAFTSMEN  
TUNER**

FM and AM with automatic frequency control. T. R. F. Stage on both AM and FM. Model RC-8.

Shpg. Wt. 20 lbs.....

**\$110.00**

Model RC-2 Hi-Fi audio amplifier. Shpg. Wt. 30 lbs.

**\$39.00**




**GE FM TUNER**

Only a few left of this unusual buy. Covers 88-108 mc range, uses guillotine tuning. Designed for export and tropicalized, has power inputs for 110 to 250 volts 60 cyc. Shpg. Wt. 30 lbs.

**HARVEY SPECIAL PRICE**

**\$49.50**

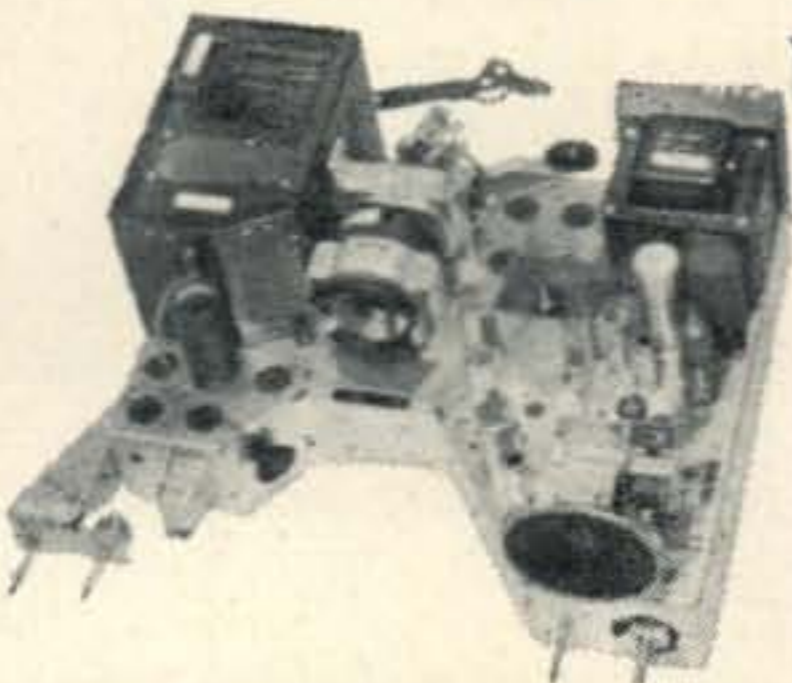

**TECHMASTER TV KIT**

Exactly the same as the RCA 630TS chassis, complete kit of parts, including pre-wired and aligned RCA front end, condensers, resistors, punched chassis, new and improved, sockets mounted, etc., all tubes including kine, complete manual with service notes, all RCA. (Free circuit and parts list on request). Shpg. Wt. 85 lbs.


**\$198.50**



**COLLINS 32V-1**

Desk xmittr, VFO controlled, band switching, gang tuned. Rated 150 watts input on CW, 120 on phone. Shpg. Wt. 133 lbs. Complete

**\$475.00**

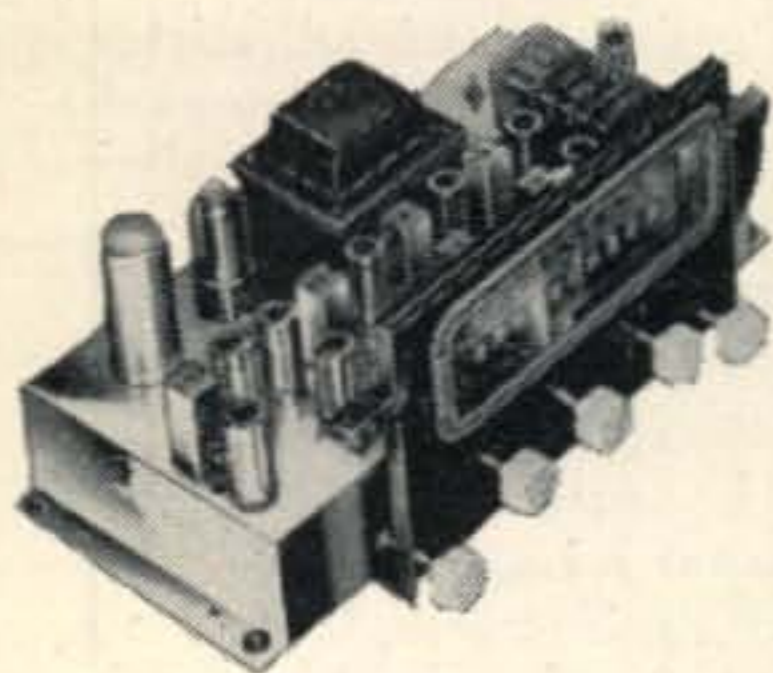

Telephone:

Luxemburg 2-1500

All in stock for immediate delivery.

**HARVEY  
RADIO COMPANY INC.**

103 West 43rd St., New York 18, N. Y.

NOTE: All prices are Net, F.O.B. N.Y.C. and are subject to change without notice.

# PRECISION TEST EQUIPMENT

(Government Surplus Release)

## Low Voltage CIRCUIT TESTER Model 1-42

Here is an instrument that any mechanic that works on automobiles, boats, or airplanes would be proud to own and we offer it at a fraction of its original cost. The low voltage circuit tester is a self-contained trouble-shooting device for making a complete and rapid check of the generator—battery circuit, including any current and voltage regulators which may be used. Battery voltage, regulator and cut-out settings, and generator performance can all be easily determined.

This tester is enclosed in a gray heavy-gauge metal box with a strong hinged top that, when opened, is supported by a slide rod and when closed, is latched by clamps. There is a carrying strap attached to the box.

This instrument was manufactured for the Quartermaster's Corps, United States Government Ordnance Department under the most rigid specifications. It is comparable in beauty and dependability to instruments made today that sell for many many more dollars than our price. Electric Heat Control Company, Cleveland, Ohio, or the Heyer Products Company, Inc., Belleville, New Jersey manufactured these for the Army. Although the unit you receive may be made by either of these companies, it will be practically identical to the unit made by the other company and all are made under Heyer Products Company's design and according to Government specifications.

This low voltage circuit tester is 11 3/16" wide x 9 9/16" deep x 7 1/2" high and can be used on either a 6 volt or 12 volt system. There is a metal chart attached to the lid of each unit which is easily readable while using the instrument. This chart shows settings of all controls and gives operation instructions to be used in conjunction with the operating manual which is included with the tester. One can quickly determine and correct trouble with this instrument. There are two battery leads with drive-in connectors (with spikes—lead coated) 8' long; ammeter lead (3-wire) complete with calibrated shunt, 6' long; voltmeter leads with alligator clip connectors and rubber insulators 8' long, and field rheostat leads with alligator type connectors and rubber insulators 5' long. The direct reading meter scale 4" in diameter with color-coded scales, along with the

push-button switch, voltage selector (3-circuit toggle switch), meter polarity switch, utility switch, voltage-ammeter scale selector switch, field rheostat, regulator test selector switch, multisection load resistor, is used to control all operations and functions of this instrument. The master meter reads 0-60 volts and 0-60 amperes. One switch box indicator has following ranges; 0-9 volts and amperes, scale deviation—0-9 range in 1/10th of a volt, 0-18 in 2/10th's of a volt, 0-60 in 1 volt and ampere division, 0-9 in .05th of a volt and ampere. They are brand new. Each weighs approximately 14 pounds. The price that we quote is only made possible because of the fact that they are Government surplus and this company bought them at a "steal". Remember, this is truly the finest of instruments and we cannot over-emphasize that we believe it is the best bargain ever offered.



Price

**\$29<sup>50</sup>**

Terms: Cash  
With Order




**Radio Co**  
130 W. New York St.  
Indianapolis 4, Ind.

Unless Otherwise Stated, All of  
This Equipment Is Sold As Used  
**CASH REQUIRED**  
**WITH ALL ORDERS**  
Orders Shipped F.O.B. Collect

**ELECTROLYTIC CONDENSERS  
ALUMINUM CANS**

|                  |           |             |
|------------------|-----------|-------------|
| 30 Mfd.          | 450 volts | <b>60c.</b> |
| 20 Mfd.          | 450 volts | <b>50c.</b> |
| 40 Mfd.          | 450 volts | <b>75c.</b> |
| 50 Mfd.          | 350 volts | <b>50c.</b> |
| 2500 Mfd.        | 3 volts   | <b>25c.</b> |
| 100 Mfd.         | 25 volts  | <b>50c.</b> |
| 50 Mfd.          | 10 volts  | <b>45c.</b> |
| 1000 Mfd.        | 15 volts  | <b>45c.</b> |
| 30 Mfd.          | 150 volts | <b>35c.</b> |
| .14 Mfd.         | 50 volts  | <b>15c.</b> |
| 100 Mfd.         | 300 volts | <b>75c.</b> |
| 100-100-100 Mfd. | 35 volts  | <b>65c.</b> |
| 20-20-20 Mfd.    | 25 volts  | <b>35c.</b> |

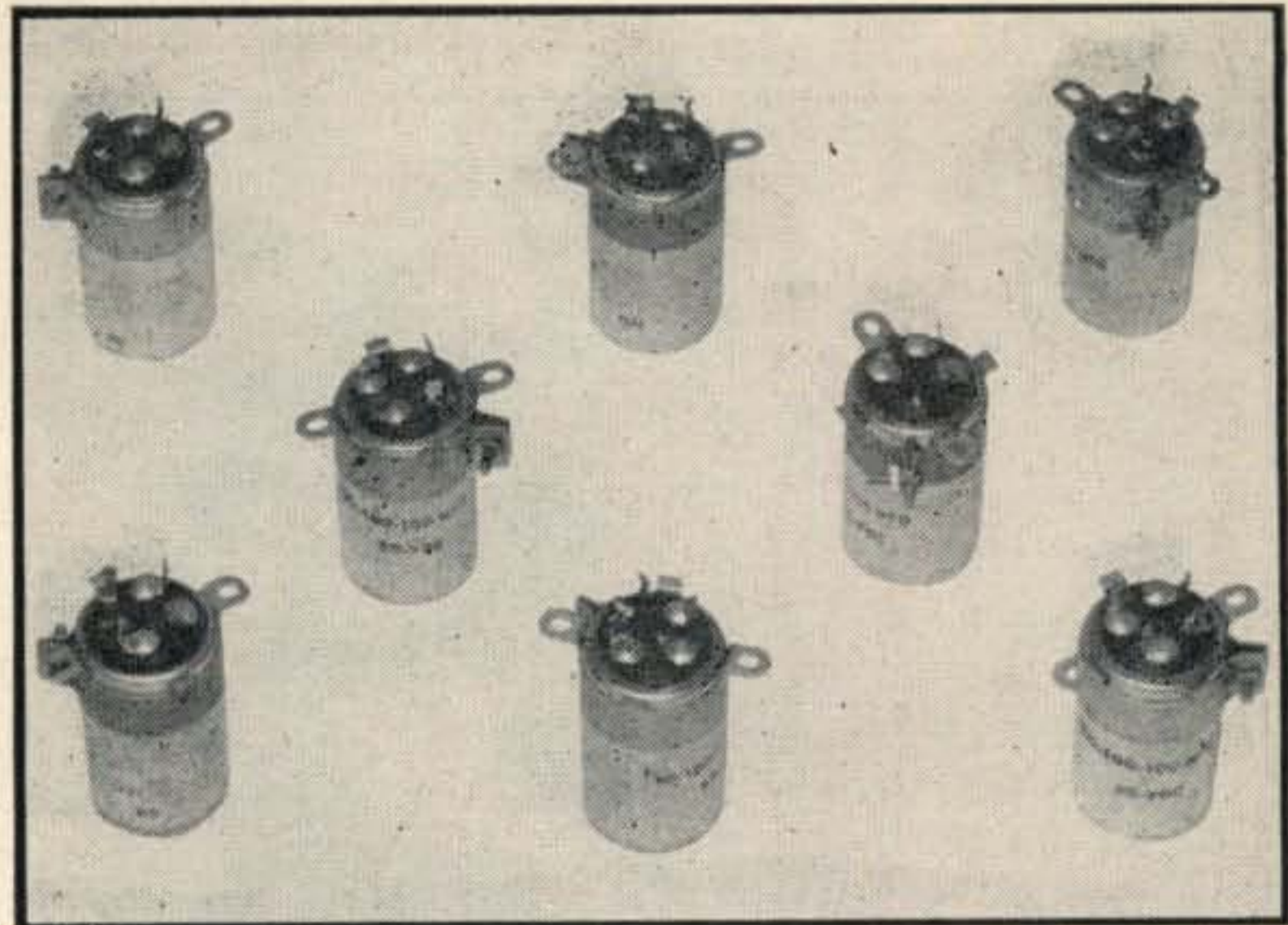


**HIGH VOLTAGE CONDENSERS**

|          |                      |                |
|----------|----------------------|----------------|
| 1 Mfd.   | 10,000 volts Aerovox | <b>\$15.00</b> |
| .25 Mfd. | 20,000 volts Aerovox | <b>\$ 4.95</b> |

**METERS (NEW)**

|                  |                                 |               |
|------------------|---------------------------------|---------------|
| General Electric | 0-15 Ma. DC 3½" Round           | <b>\$2.95</b> |
| Westinghouse     | 0-500 Ma. DC 3½" Round          | <b>3.50</b>   |
| General Electric | 0-10/250 Ma. DC 2½" Round       | <b>2.50</b>   |
| Westinghouse     | -10/+6 DB 3½" Round             | <b>7.50</b>   |
| Westinghouse     | 0-5 Amp. TC 3½" Round           | <b>4.50</b>   |
| Triplet          | 0-500 V. AC 3½" Square          | <b>6.00</b>   |
| Simpson          | 0-150 V. AC 2½" Round           | <b>3.50</b>   |
| Triplet          | 0-75 AC Amps 3½" Round          | <b>7.50</b>   |
| Westinghouse     | 0-3 Amp. RF (less TC) 2½" Round | <b>3.50</b>   |

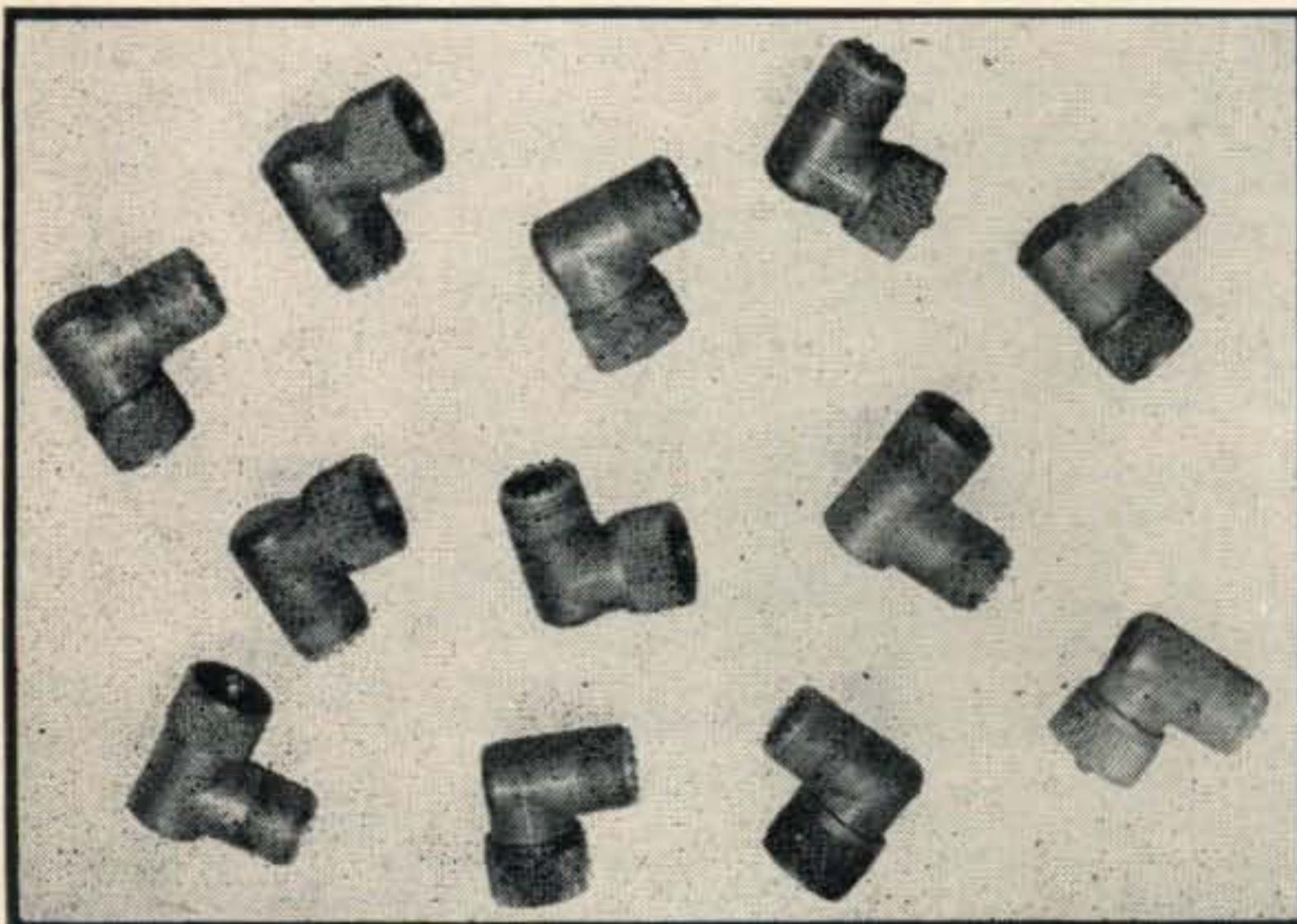**AMPHENOL LOW-LOSS UHF CONNECTOR for . . .**




**AMPHENOL LOW-LOSS UHF CONNECTOR** for RG type cable. Rugged construction, heavily silver plated, provides easy assembly and positive connection. Type 83-1AP Angle Plug Adapter polystyrene insert, pin and socket—very special.....**20c each**

**Type 83-1R Receptacle**, chassis type, low-loss Mica filled insert, very special, .....**30c. each.**

## CRYSTALS IN STANDARD 5-PRONG SOCKET HOLDERS

| 10 Meter<br>Ham Band | Odd<br>Frequencies |
|----------------------|--------------------|
| 7120.....\$ .55      | 5450.....\$ .50    |
| 7130......55         | 5560......50       |
| 7140......55         | 5810......50       |
| 7160......55         | 7660......50       |
| 7180......50         | 7670......50       |
| 7210......50         | 7680......50       |
| 7220......50         | 7690......50       |
| 7240......50         | 7700......50       |
| 7250......50         | 7710......50       |
| 7260......50         | 7920......50       |
| 7270......50         | 7940......50       |
| 7290......50         | 7950......50       |
| 7280......50         | 7970......50       |
| 7300......50         | 7990......50       |
| 7310......45         | 8245......50       |
| 7320......45         | 8248......50       |
| 7330......45         | 8250......50       |
| 7340......45         | 8261......50       |
|                      | 8252......50       |

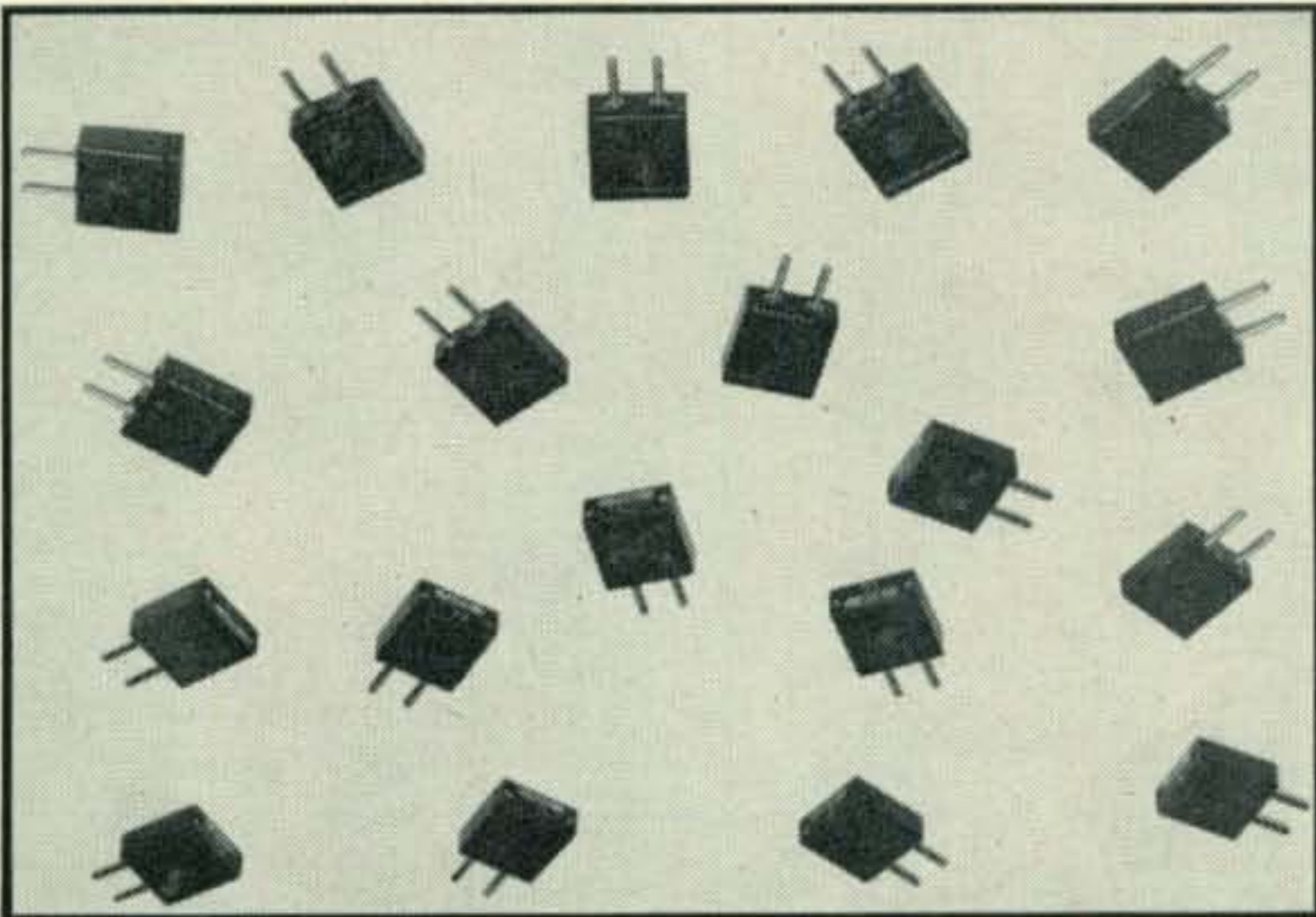

| 2 Meter Ham Band |                 |
|------------------|-----------------|
| 8351.....\$ .75  | 8476.....\$ .75 |
| 9356......75     | 8477......75    |
| 8357......75     | 8480......75    |
| 8360......75     | 8486......75    |
| 8361......75     | 8488......75    |
| 8362......75     | 8520......75    |
| 8367......75     | 8530......75    |
| 8400......75     | 8540......75    |
| 8450......75     | 8541......75    |
| 8451......75     | 8542......75    |
| 8452......75     | 8547......75    |

| 20 Meter<br>Ham Band |  |
|----------------------|--|
| 7120.....\$ .55      |  |
| 7130......55         |  |
| 7140......55         |  |
| 7160......55         |  |
| 40 Meter<br>Ham Band |  |
| 7120.....\$ .55      |  |
| 7130......55         |  |
| 7140......55         |  |
| 7160......55         |  |
| 7180......50         |  |
| 7210......50         |  |
| 7220......50         |  |
| 7240......50         |  |
| 7250......50         |  |
| 7260......50         |  |
| 7270......50         |  |
| 7280......50         |  |
| 7290......50         |  |
| 7300......50         |  |

| 2 Meter<br>Ham Band |  |
|---------------------|--|
| 8065.....\$ .75     |  |
| 8092......75        |  |
| 8100......75        |  |
| 8103......75        |  |
| 8104......75        |  |
| 8105......75        |  |
| 8110......75        |  |
| 8114......75        |  |
| 8115......75        |  |
| 8120......75        |  |
| 8124......75        |  |
| 8126......75        |  |
| 8130......75        |  |
| 8194......75        |  |

### A TREMENDOUS BARGAIN — QUARTZ CRYSTALS WITHOUT HOLDERS

Get an assortment of these and grind to your own frequencies or use them as they are. .5X.6" B-cut lapped on faces and squared on edges (Ready to use). We will give you an assortment of these from approximately 13 thousandths of an inch to 24 thousandths of an inch whereby you can grind to frequencies desired.

These crystals are now ground to the approximate following frequencies:

|      |      |      |
|------|------|------|
| 3500 | 5300 | 6800 |
| 3700 | 5600 | 6900 |
| 3900 | 5800 | 7300 |
| 4100 | 6000 | 7400 |
| 4300 | 6200 | 7500 |
| 4600 | 6300 | 7800 |
| 4900 | 6700 | 7900 |

Formula for converting thicknesses of B-cut crystals to frequency is as follows:  
 $F = 98.4 / T$  where F is frequency in kilocycles and T is thickness in inches.

**AN ASSORTMENT OF 20 DIFFERENT THICKNESSES — \$2.50**

## CONCERT MASTER RADIO TUBES — NEWLY MANUFACTURED

### Brand New Radio Tubes (not surplus)

Each tube is individually beautifully boxed. Standard radio tube guarantee, backed by the manufacturer and also by Esse Radio Company.

**55c-  
ea.**

|        |         |        |        |         |        |
|--------|---------|--------|--------|---------|--------|
| 1L4    | 6J7G    | 50L6GT | 6AT6   | 6U6GT   | 25Z5GT |
| 1R5    | 6K6     | 50Y6   | 6AU6   | 6U5G    | 25Z6GT |
| 1T4    | 6Q7GT   | 84/6Z4 | 6A7    | 6U7G    | 35/51  |
| 5Y3GT  | 6SA7GT  | 1A5GT  | 6A8GT  | 6U6G    | 35L6GT |
| 7AF7   | 6SK7GT  | 1C5    | 6BA6   | 6V6GT   | 35Z3   |
| 35W4   | 6SQ7GT  | 1H5GT  | 6BE6   | 6X4     | 36     |
| 39/44  | 6X5GT   | 1N5GT  | 6C5    | 6Z4     | 42     |
| 501    | 12A8GT  | 1P5GT  | 6C6    | 12BA6   | 43     |
| 1S5    | 12AT6   | 1V     | 6C8G   | 12F5GT  | 45     |
| 1U5    | 12BE6   | 2A5    | 6D6    | 12J7GT  | 47     |
| 3A4    | 12J5GT  | 3Q4    | 6F5GT  | 12K7GT  | 51     |
| 12SR7  | 12SA7GT | 3Q5GT  | 6H6GT  | 12Q7GT  | 57     |
| 26     | 12SK7GT | 5U4G   | 6K7GT  | 12K8GT  | 58     |
| 35Z5GT | 12SQ7GT | 5X4    | 6K8GT  | 12SF5   | 71A    |
| 80     | 14X7    | 6AC5GT | 6P5GT  | 12SG7   | 76     |
| 5W4GT  | 35B5    | 6AQ5   | 6SC7GT | 12SJ7GT | 75     |
| 5Y4G   | 41      | 6A8GT  | 6SP5GT | 24A     | 77     |
| 6F6GT  | 50A5    | 12SF7  | 6SJ7   | 25L6GT  | 78     |
| 6J5GT  |         |        |        |         | 85     |

**89c-  
ea.**

|          |         |         |        |      |       |
|----------|---------|---------|--------|------|-------|
| 0Z4      | 6L6GA   | 7H7     | 6C4    | 5Z3  | 6SL7  |
| 0Z4G     | 7E5     | 7Q7     | 6C5    | 6AC4 | 6SN7  |
| 6B8      | 7K7     | 7Y4     | 6F6    | 6AL5 | 6Y6   |
| 6F8      | 2050    | 14A7    | 6H6GT  | 6AL6 | 7A4   |
| 6T7GT    | 1Q5     | 14B6    | 6K8GT  | 6BA6 | 40    |
| 6Q6GT    | 1T5     | 14Q7    | 6SC7   | 2051 | 83    |
| 6S7G     | 2A3     | 25AC5GT | 6SG7   | 6AG5 | 182B  |
| 6J8G     | 2A7     | 25A7GT  | 6SH7   | 30   | 183   |
| 7C7/1232 | 5Z4     | 35L7GT  | 6SJ7   | 31   | 482B  |
| 1LA4     | 6AC7    | 117Z3   | 1L4    | 37   | 483   |
| 1LA6     | 6B4G    | 35Y4    | 5Y3GT  | 38   | 1C6   |
| 1LC6     | 6C8G    | 117Z6   | 27     | 39   | 1R4   |
| 1LD5     | 6D8G    | XXL     | 6SA7   | 56   | 1J6   |
| 1LE3     | 6S8GT   | 35B8    | 12SA7  | 57   | 6AG5  |
| 1LN5     | 7A4/XXL | 12SN7   | 6SK7GT | 76   | 6T8   |
| 7X7/XXFM | 7A7     | 12SJ7   | 6SQ7   | 89   | 6B7   |
| 70L7     | 7B6     | 12SH7   | 6J5GT  | 1S4  | 6T7   |
| 117L7GT  | 7B7     | 12SG7   | 12J5   | 2B7  | 12AG7 |
| 117P7GT  | 7C5     | 12AU6   | 1G4    | 5V4  | 6Z7   |
| XXFM     | 7C6     | 6SR7    | 1U4    | 6A3  | 19T8  |
| 6L6G     | 7C7     | 6BH6    | 3V4    | 6R7  |       |

SURPLUS TUBES that are not sold as new or in containers but will be checked by us before we ship them to you and will be found in excellent condition or we will not ship them.

Tremendous bargains if you can use quantities.

|            |                     |            |                   |
|------------|---------------------|------------|-------------------|
| 7F7 .....  | \$25.00 per hundred | 6SL7 ..... | 25.00 per hundred |
| 7C5 .....  | 25.00 per hundred   | 30 .....   | 35.00 per hundred |
| 7Y4 .....  | 25.00 per hundred   | 12A6 ..... | 25.00 per hundred |
| 6L6 .....  | 50.00 per hundred   | 1625 ..... | 25.00 per hundred |
| 5T4 .....  | 25.00 per hundred   | 1629 ..... | 25.00 per hundred |
| 5R4 .....  | 25.00 per hundred   | 6C5 .....  | 25.00 per hundred |
| 6SA7 ..... | 25.00 per hundred   |            |                   |

**NEW  
VOLUME CONTROLS**

|   |        |
|---|--------|
| 1 megohm, carbon 1" shaft.....                | \$ .35 |
| 1000 ohms, carbon, screw-driver shaft.....    | .35    |
| 20 ohms, wire-wound, 1" shaft.....            | .35    |
| 500,000 ohms, carbon, 2" shaft.....           | .35    |
| 1000 ohms, wire-wound, 2" shaft.....          | .35    |
| 6000 ohms, with switch, carbon, 1" shaft....  | .40    |
| Dual 25000 ea., wire-wound, 1" shaft.....     | .35    |
| Triple 25,000-50,000-20,000, carbon, 1" shaft | .70    |

**NEW  
RESISTORS - WIREWOUND**

|  |        |
|--|--------|
| 3 ohms, 20 watt.....                   | \$ .10 |
| 2500 ohms, 20 watt.....                | .10    |
| 1/2 ohm, 20 watt.....                  | .10    |
| 11269 ohms, 100 watt (has 5 taps)..... | .35    |

**NEW  
RESISTORS - CARBON**

|                               |                |
|-------------------------------|----------------|
|                               | per<br>hundred |
| 100 ohms, 1/2 watt.....       | \$3.00         |
| 120 ohms, 1/2 watt.....       | 3.00           |
| 220 ohms, 1/4 watt.....       | 3.00           |
| 270 ohms, 1 watt.....         | 3.00           |
| 470 ohms, 1/4 watt.....       | 3.00           |
| 480 ohms, 1/2 watt.....       | 3.00           |
| 1200 ohms, 1/2 watt.....      | 3.00           |
| 6800 ohms, 2 watt.....        | 3.00           |
| 12,000 ohms, 2 watt.....      | 3.00           |
| 21,000 ohms, 1/4 watt.....    | 3.00           |
| 56,000 ohms, 1/4 watt.....    | 3.00           |
| 85,000 ohms, 1/4 watt.....    | 3.00           |
| 150,000 ohms, 1 watt.....     | 3.00           |
| 270,000 ohms, 1/2 watt.....   | 3.00           |
| 830,000 ohms, 1/4 watt.....   | 3.00           |
| 1,200,000 ohms, 1/2 watt..... | 3.00           |
| 5,600,000 ohms, 1/4 watt..... | 3.00           |

**NEW  
CONDENSERS**

|  |        |
|--|--------|
| .5 mfd. 600 V., Oil, 3/4"x1 1/4"x2".....                                       | \$ .20 |
| .5 mfd. 400 V., paper 1" dia. x 2 1/4".....                                    | .25    |
| 5.2 mfd. 50 V., Chicago Ind. Cond. Corp.,<br>Oil, 1 x 2 1/2 x 3".....          | .25    |
| 4 mfd. 600 V. GE Pyranol, 1"x2 1/2"x3".....                                    | .50    |
| 2 mfd. 600 V., Aerovox Oil, 1"x1"x3 1/2"....                                   | 1.25   |
| 8 mfd. 600 V., Chgo. Ind. Cond. Corp., Oil,<br>1" x 4" x 5".....               | 1.50   |
| 1 mfd. 4000 V., C-D, Oil, 2"x4"x7".....  | 4.00   |
| .20 mfd. 600 V., mica.....   | .50    |
| 4 mfd. 1000 V., Oil, C-D or Aerovox, 1" x<br>2" x 7".....                      | 2.50   |
| 30 mfd. 330 V. AC, GE pyranol.....   | 3.00   |
| 2 mfd. 1000 V., C-D, Oil, Single hole mount-<br>ing, 1 1/2" dia. x 4 1/2"..... | 1.75   |
| 4 mfd. 600 V., C-D, 1 1/2" x 4 1/2", single<br>hole mounting.....              | 1.25   |
| 140 mmfd., variable, padder screwdriver ad-<br>justable.....                   | .25    |
| 7-17 mmfd., variable tuning, 5 plate, 2"<br>shaft, 1/4" dia.....               | .25    |
| .1 mfd. 400 V., paper Aerovox.....   | .15    |
| .14 mfd. 50 V., paper.....   | .15    |
| .1 mfd. 1500 V. paper.....   | .20    |
| .05 mfd. 400 V. paper.....   | .15    |

**LIP MICROPHONE**

Lip microphone, made by Western Electric, Navy type CW-51071, with instruction sheet, brand new .....\$1.50

**TYPE 813 TUBES**

|                                  |            |
|----------------------------------|------------|
| Type 813 tubes (New).....        | \$5.95 ea. |
| Type 813 tube sockets (New)..... | .50 ea.    |

**TELRAD 18-A FREQUENCY  
STANDARD**



Checks signals in the range of 100 Kc. to 45 Mc. with a high degree of accuracy. Self-contained power supply is 110, 130, 150, 220, and 250 V. 25-60 cycle AC. Complete with tubes, dual crystal, and instruction book. Brand new. Price .....\$39.50

**TUBES**

Minimum order \$10.00

|            |            |            |            |
|------------|------------|------------|------------|
| 6SN7 ..... | \$ .35 ea. | 12A6 ..... | \$ .35 ea. |
| 714 .....  | .30 ea.    | 1625 ..... | .30 ea.    |
| 7C5 .....  | .30 ea.    | 1629 ..... | .35 ea.    |
| 7F7 .....  | .30 ea.    |            |            |

**MAGNESYN INDICATOR**

To be used for beam antenna. Practically same as I-81-I Selsyn indicator. 15-25 V. 60 cycle AC. 3" size. Excellent condition .....\$1.85 ea. Plug for connection..... .50 ea.




**BC-348 COMMUNICATIONS RECEIVER**

6 bands, 290-500 Kc. and 1.5-18 Mc. 2 stages RF, 3 stages IF, BFO, crystal filter, manual or AVC. Complete with tubes and 24 V. dynamotor. These receivers have been thoroughly checked in our work-shop and found in excellent condition.


**\$149.50**

## C-1 AUTO PILOT COMPONENTS

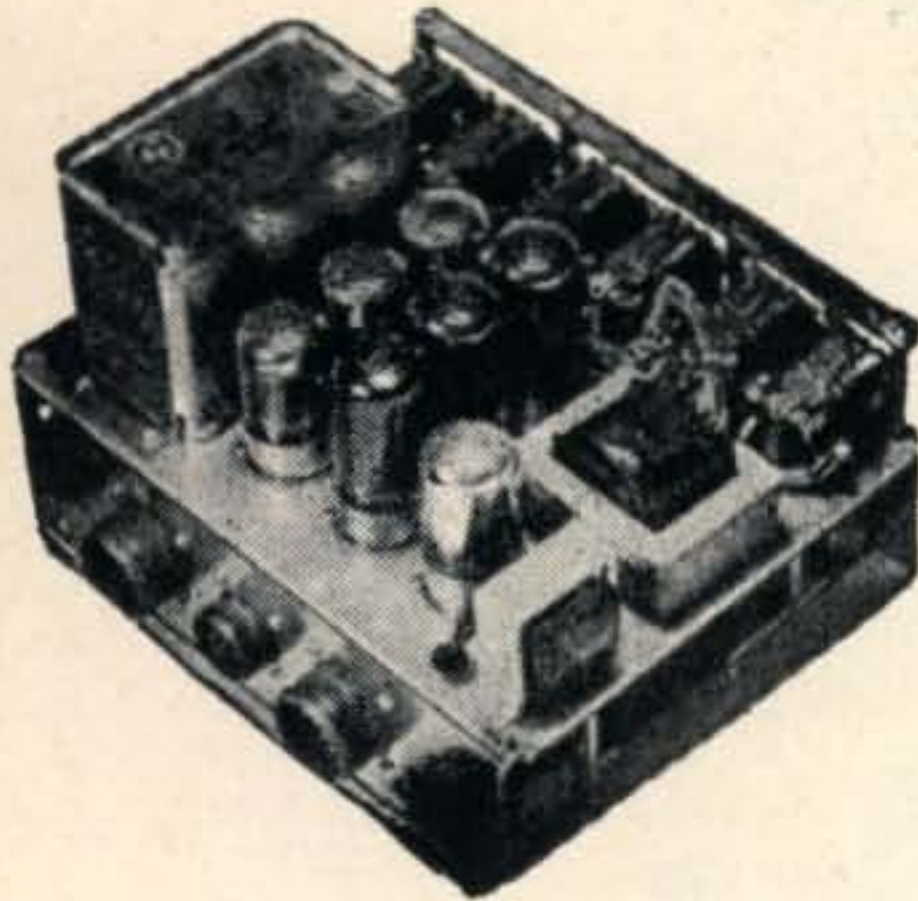
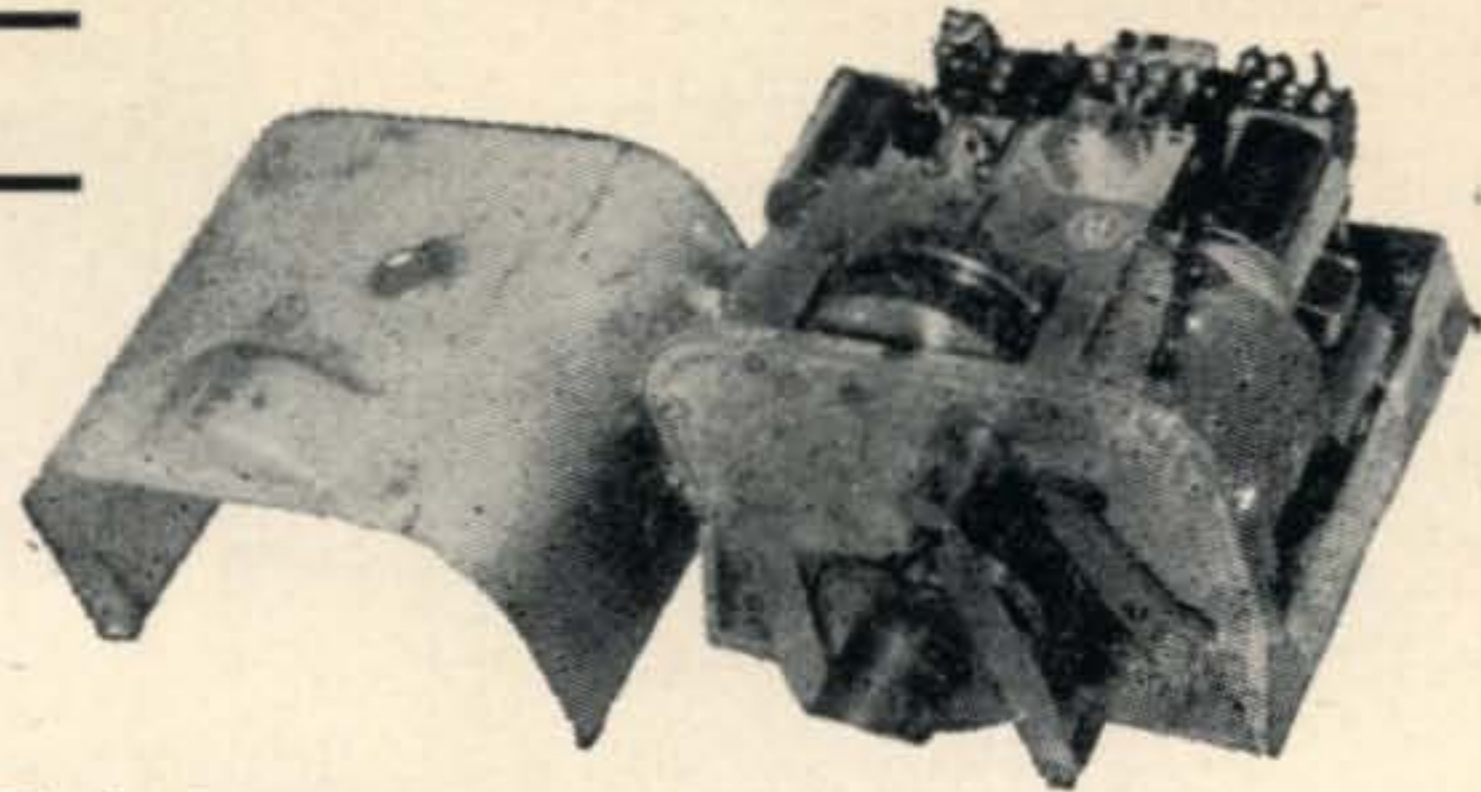
### C-1 AUTO PILOT AMPLIFIER

Used to control operation of servo unit in response to signals received from gyro unit and control unit. The complete amplifier includes one rect. 7Y4, 3-7F7's for amplification and control, 3-7N7's for signal discrimination, 1 power transformer, 6 relays, 4 control pots, chokes, condensers, etc. Convert for use on radio controlled models, doors, etc. Operates from 24 V. DC. Size, 9 1/4" x 6 1/4" x 7 5/8". Complete.....**\$6.95**



### C-1 SERVO UNIT

Use to rotate beam antenna, actuate boat rudder control, etc. Contains 24 V. motor, clutch, relays, etc. Reversible. Size overall approx. 10 1/2" x 8 1/2" x 6 1/2".  
Price .....**\$12.50**



### C-1 GYRO

Part of the C-1 Auto Pilot which is sold separate and may be used to conduct many interesting and amusing experiments. Operates from 24 V. DC or may be operated for short periods on 110 V. AC. Gyro will run for approx. 15 minutes after actuating. Size—approx. 8"x8 1/2"x8 1/2". Price.....**\$8.95**

|                         |                    |
|-------------------------|--------------------|
| 813 tube sockets.....   | <b>\$ .75</b> each |
| 866 tube sockets.....   | <b>.50</b> each    |
| Acorn tube socket.....  | <b>.25</b> each    |
| Octal tube sockets..... | <b>.15</b> each    |

|   |                      |
|---|----------------------|
| Microswitches type WZ-23LT1 normally closed. Packed 10 to carton. (New) .....                 | Carton <b>\$2.50</b> |
| Type R-RS normally closed. Packed 10 to carton. (New).....                                    | Carton <b>.250</b>   |
| Headphones HS-16-A, high impedance. Made by Trimm with 5' cord and phone tips. Brand new..... | <b>3.50</b> each     |

### OIL CONDENSERS

|  | EACH          |
|--|---------------|
| 7.5 Mfd. 300 V. AC, G.E. Pyranol.....  | <b>\$1.50</b> |
| 30 Mfd. 330 V. AC, G.E. Pyranol.....   | <b>3.00</b>   |
| 2.5 Mfd. 300 V. DC, Chicago-Industrial | <b>.50</b>    |
| 1 Mfd. 5000 V. DC, G.E. Pyranol.....   | <b>4.50</b>   |
| 1 Mfd. 5000 V. DC, G.E. Pyranol.....   | <b>3.75</b>   |
| 1 Mfd. 3000 V. DC, Chicago Industrial  | <b>2.00</b>   |
| 1 Mfd. 250 V. DC, RCA.....             | <b>.25</b>    |
| .5 Mfd. 600 V. DC, RCA.....            | <b>.25</b>    |
| 4 Mfd. 600 V. DC, RCA.....             | <b>1.35</b>   |
| 2 Mfd. 1000 V. DC, RCA.....            | <b>1.35</b>   |
| 4 Mfd. 300 V. DC, RCA.....             | <b>.35</b>    |
| 8 Mfd. 600 V. DC, G.E. Pyranol.....    | <b>1.50</b>   |
| 8 Mfd. 600 V. DC, Chicago Industrial   | <b>1.50</b>   |
| 2 Mfd. 600 V. DC, Aerovox.....         | <b>.35</b>    |
| 5.2 Mfd. 50 V. DC, Chicago Industrial  | <b>.35</b>    |
| 4 Mfd. 1000 V. DC, C-D and Aerovox     | <b>1.35</b>   |
| 4 Mfd. 60 V. DC, G.E. Pyranol.....     | <b>.50</b>    |

### PAPER CONDENSERS

|                                 |                   |
|---------------------------------|-------------------|
| .0475 Mfd. 200 V. Aerovox.....  | <b>\$ .10</b> ea. |
| .0035 Mfd. 1000 V. Aerovox..... | <b>.15</b> ea.    |
| .1 Mfd. 400 V. Aerovox.....     | <b>.15</b> ea.    |
| .05 Mfd. 400 V. Aerovox.....    | <b>.15</b> ea.    |
| .5 Mfd. 400 V. Aerovox.....     | <b>.15</b> ea.    |
| .001 Mfd. 1000 V. Solar.....    | <b>.15</b> ea.    |

### CO-AXIAL CABLE

For high frequency low-loss, trouble-free, weather proof, durable service. Fully shielded, cut to length. Brand New.


|                             |               |
|-----------------------------|---------------|
| RG8/U-52 ohm (marked RG8/U) |               |
| Price—100 ft. for.....      | <b>\$4.95</b> |
| RG8/U-52 ohm (unmarked)     |               |
| Price—100 ft. for.....      | <b>3.95</b>   |
| RG29/U-ohm (marked)         |               |
| Price—100 ft. for.....      | <b>3.95</b>   |

## SURPLUS RADIO CONVERSION MANUAL

Edited and printed by Techno-Graphic Publications. It contains 115 pages, size is 7" x 10½", printed on good paper stock, covers well bound. A partial list of contents includes complete information on the conversion of the following popular war surplus items: BC-221 Frequency meter, BC342, BC312, BC348, BC946B, SCR274N, SCR522, BC1068A receivers, BC412 cathode ray oscilloscope, BC645 transceiver for citizen's band, SCR274N transmitters, SCR522 transmitter, TBY transceiver, various dynamotors, and a cross-index on tube numbers, frequency allocation chart, electronic surplus index with listing of over 135 items and descriptions or functions or frequencies or tube line-ups etc. of same. Circuit diagrams of original items, and of converted jobs, together with values of various component parts abound in the manual. The text is clear, concise and easy to read and follow. The price per copy is.....**\$1.25**
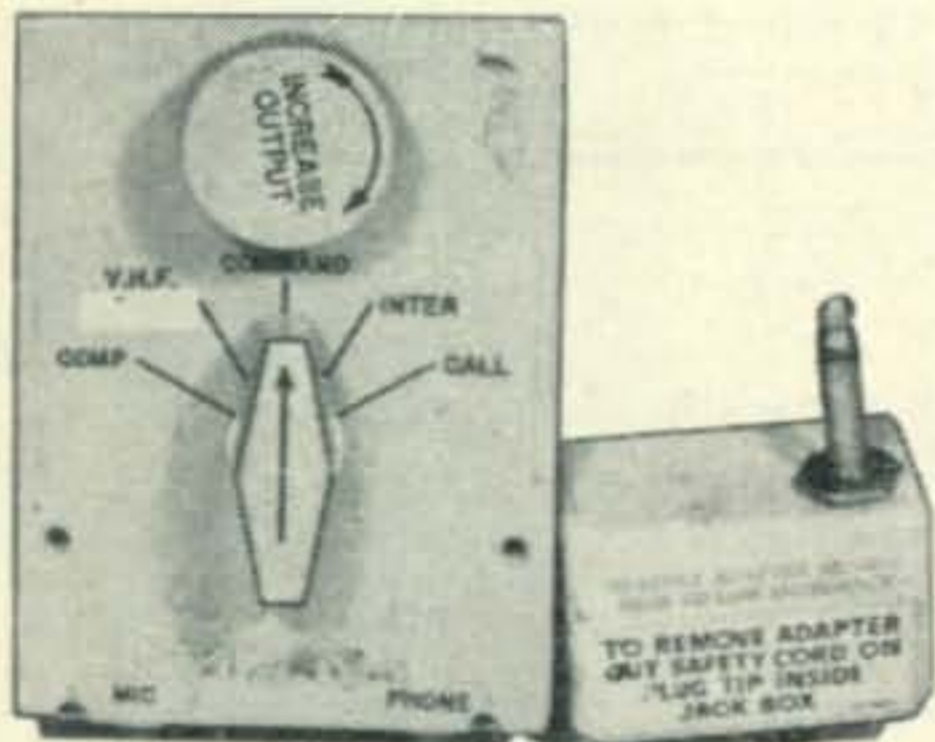
## ULTRA-VIOLET FLUORESCENT COCKPIT LIGHT ASSEMBLY

Air Corps type C-5, 28 V. DC operated. Black plastic case about 1½" dia. x 3" long. Has adjustable mounting flange, 3 foot two conductor shielded cord and plug. Includes bulb. Brand new.....**\$1.00**




### JACK BOX BC-1366

Contains 2-pole 5-position switch, rheostat, two phone jacks, etc. In aluminum case 3½" x 4¾" x 2¼". Complete with head-phone set adapter to match high to low impedance. Price .....**\$1.25**

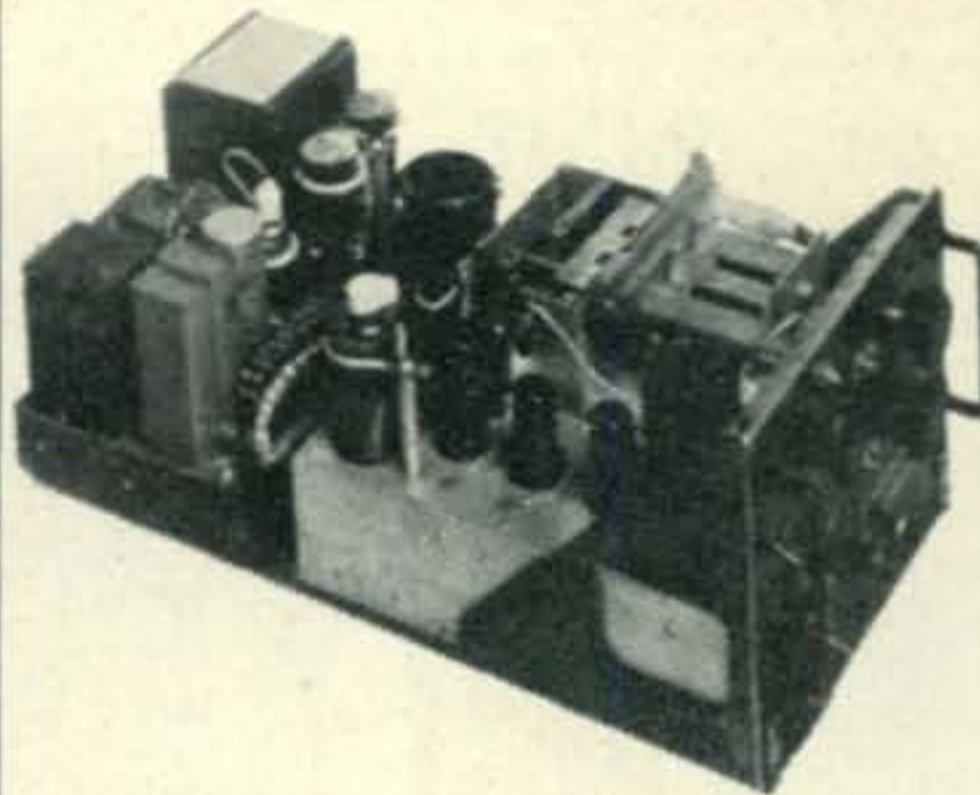
### CAPACITOR: 2000 Mfd.

10% + infinity. Working voltage 50 V. DC. Test voltage 50 V. DC. Electrolytic. Bakelite case, hermetically sealed. Max. dimensions 2-1/16" dia. x 4¾". Soldering lug type terminals. Price.....**\$1.25**



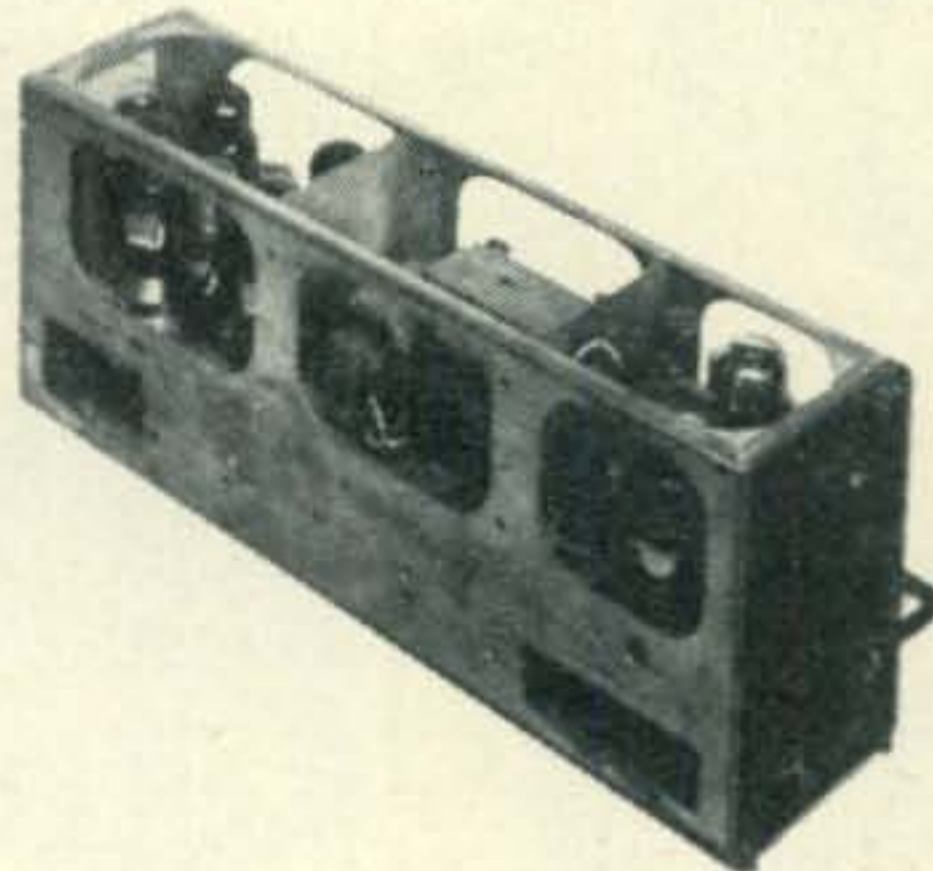
### T-26 APT-2 RADAR TRANSMITTER

Contains tunable VHF circuit using 2—JAN CTL 703A's or 368AS tubes. Other tubes are: 2—5R4GY's, 1—2X2, 1—807, 1—6AG7, 2—6AC7's and 1—931A. Other parts such as 24 V. DC motor and blower, HV. condensers and transformers, terminal strips and Amphenol connectors, knobs, fuse holders, etc. make this unit invaluable for parts alone. Weight approx. 45 lbs. Size 21" L x 10½" W x 7¾" H, in metal case. ....**\$9.75**


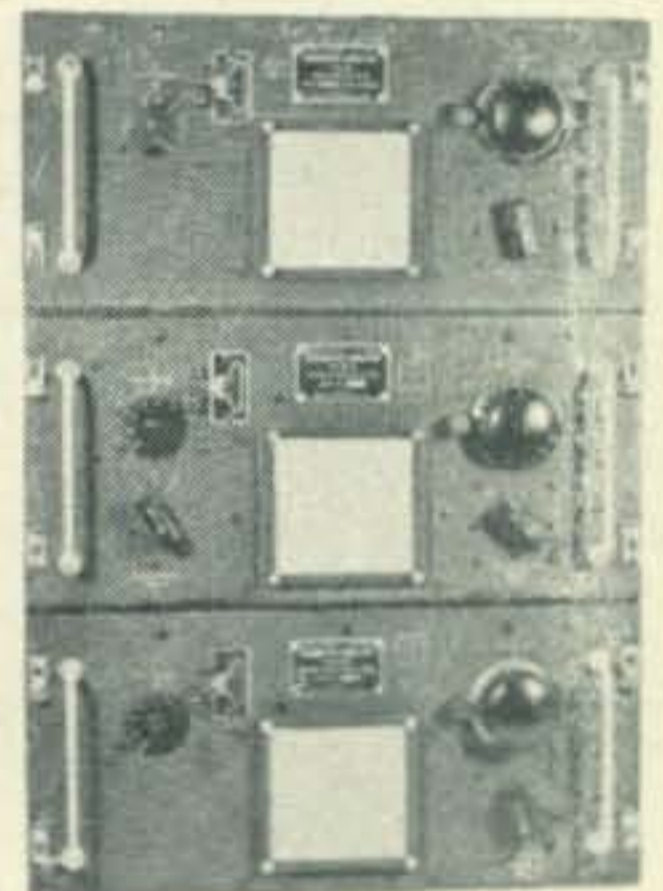
### PP-2/APQ-5 POWER UNIT

400 cycle, 115 V. Contains 10 tubes as follows: 2—5U4G's, 1—6A5GT, 4—6Y6G's, 1—6SL7GT, 2—VR150-30 and numerous condensers, transformers and resistors. Weight 17 lbs. Size 21" L x 5¼" W x 7¾" H. Price....**\$5.75**



### BC-375 GE MOPA TRANSMITTER

The most famous of all surplus transmitters. Was used by the Army bombers and ground stations during the War. Frequency range is covered by means of plug-in tuning units as shown below. Each tuning unit has its own oscillator and power amplifier coils and condensers, and antenna tuning circuits all designed to operate at top efficiency within its particular frequency range. Transmitter and accessories are finished in black crackle, and the milliammeter, voltmeter, and RF ammeter are mounted on the front panel. **Frequency Range:** 200-500 Kc. and 1500-12,500 Kc. (Will operate on 10 and 20 meter band with slight modification). **Oscillator:** self-excited, thermo-compensated, and hand calibrated. **Power Amplifier:** neutralized class "C" stage, using 211 tube, and equipped with antenna coupling circuit which matches practically any length antenna. **Modulator:** Class "B"—uses two 211 tubes. **Power Supply:** Dynamotor which furnishes 1000 V. at 350 Ma. Conversion instructions and diagram for 110 V. AC furnished upon request for.....**\$1.00.**

**PRICES:** As follows—

|   |                |
|---|----------------|
| Transmitter only .....  | <b>\$19.50</b> |
| Tuning units TU-6B, TU-7B, TU-8B, TU-9B,<br>TU-10B, TU-26B, choice..... | <b>2.50</b>    |
| Dynamotor PE-73C .....  | <b>4.95</b>    |
| Antenna tuning unit (BC-306A).....                                      | <b>4.95</b>    |





## MARKER-BEACON RECEIVER

Can be adapted to radio controlled devices. Was used by pilots to flash a signal lamp on aircraft instrument panel when in range of a beacon transmitter. Responds to modulated signals over a variable range of 62 to 80 Mc. Tube plates and filaments operate directly from 24 V. DC. Can be adapted for radio control of experimental apparatus opening garage doors, etc. Circuit diagram and parts list included on either model shown below: BC-357 — contains 12C8 and 12SQ7 tubes and sensitive relay (size 5<sup>3</sup>/<sub>8</sub>" x 5<sup>1</sup>/<sub>4</sub>" x 3<sup>1</sup>/<sub>4</sub>").

Price .....**2.95**

BC-1033—contains 6SH7, 6SL7 and 12SN7 tubes, sensitive relay (size 5<sup>3</sup>/<sub>8</sub>" x 5<sup>1</sup>/<sub>4</sub>" x 3<sup>1</sup>/<sub>4</sub>").



Price .....**\$3.50**

## AIRCRAFT RADIO RANGE FILTER

For helpful reduction of QRM on crowded CW bands. When attached to output of any communications receiver:

- 1—Will pass signal of 1020 CPS, eliminating others.
- 2—Will pass voice frequencies and eliminate 1020 CPS code signal.

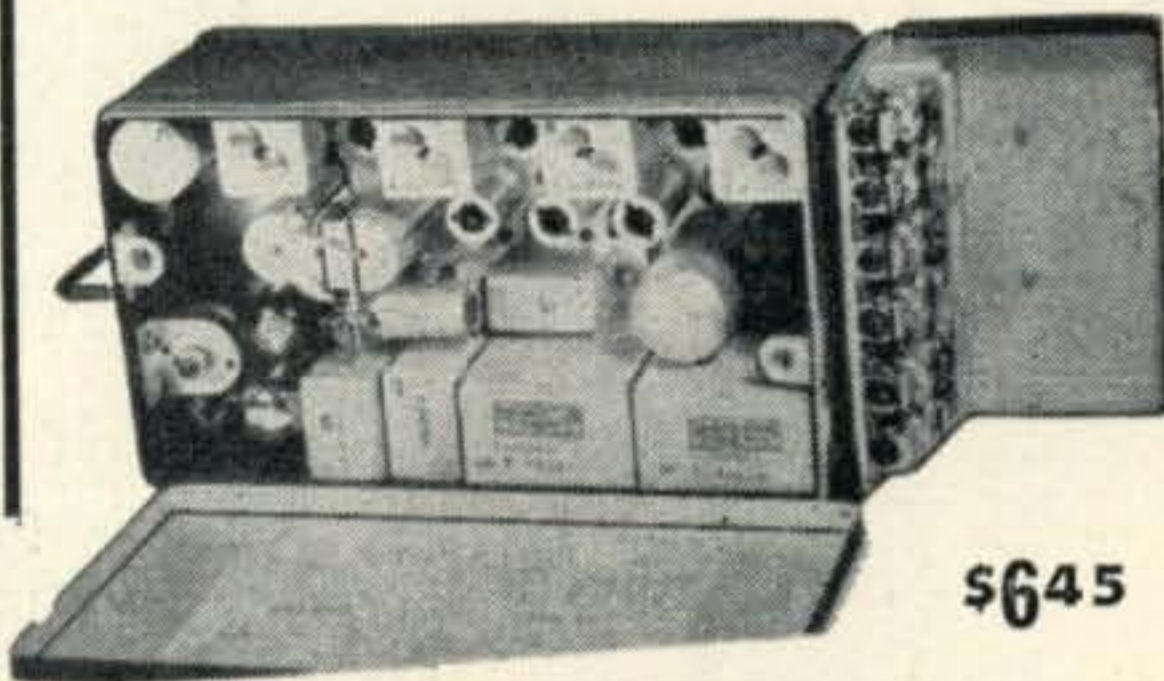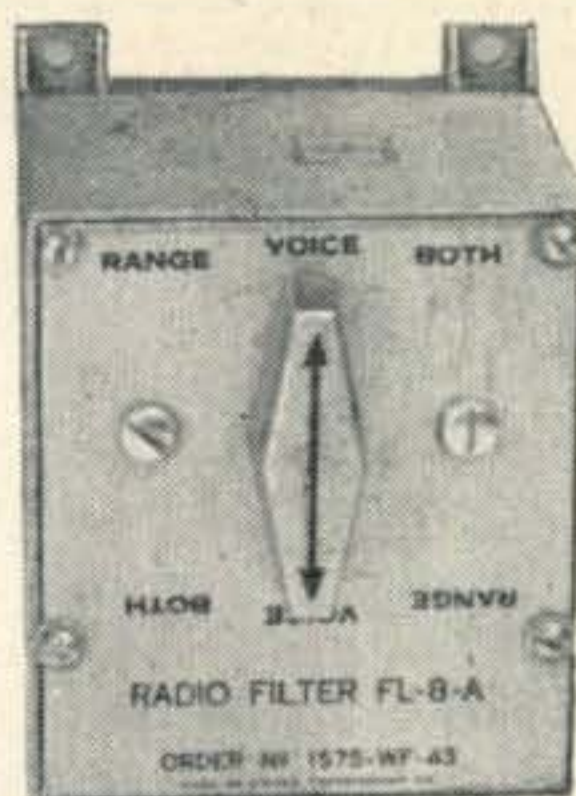Compact, light weight, with switch. Size 2<sup>3</sup>/<sub>4</sub>" x 2<sup>5</sup>/<sub>8</sub>" x 3<sup>3</sup>/<sub>4</sub>". Price .....**\$2.25**




**\$645**

## R-89/ARN 5A GLIDE PATH RECEIVER

Formerly used for blind landing but adaptable to many other uses such as receiver for new police or citizen's band. Band of operation 326-335 mc. on any of three pre-determined crystal controlled frequencies. Contains eleven tubes, 6 relays, and other valuable parts. For 24 V. DC operation. Size 13<sup>3</sup>/<sub>4</sub>" x 5<sup>1</sup>/<sub>4</sub>" x 6<sup>3</sup>/<sub>8</sub>". Price, complete as shown.


## APN-1 RADIO ALTIMETER

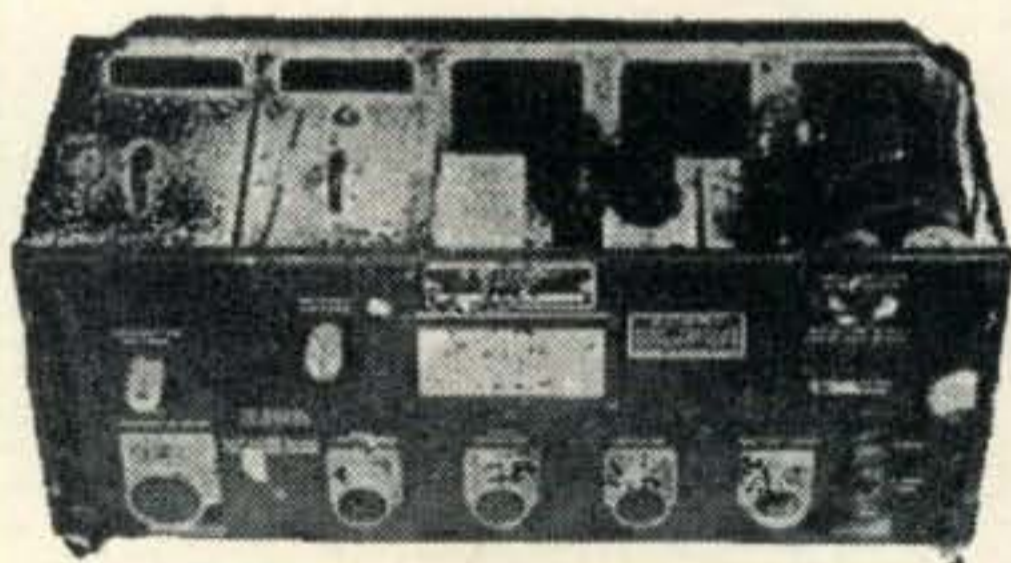

A complete 460 mc. radio receiver and transmitter which can be converted for ham or commercial use. Tubes used and included: 4-12SH7, 3-12SJ7, 2-6H6, 1-VR150, 2-955, 2-9004. Other components such as relays, 24 volt dynamotor, transformers, pots, condensers, etc., make this a buy on which you cannot go wrong. Complete in aluminum case 18" x 7" x 7<sup>1</sup>/<sub>4</sub>".

Price .....**\$8.95**

## T-39/APQ-9 RADAR TRANSMITTER

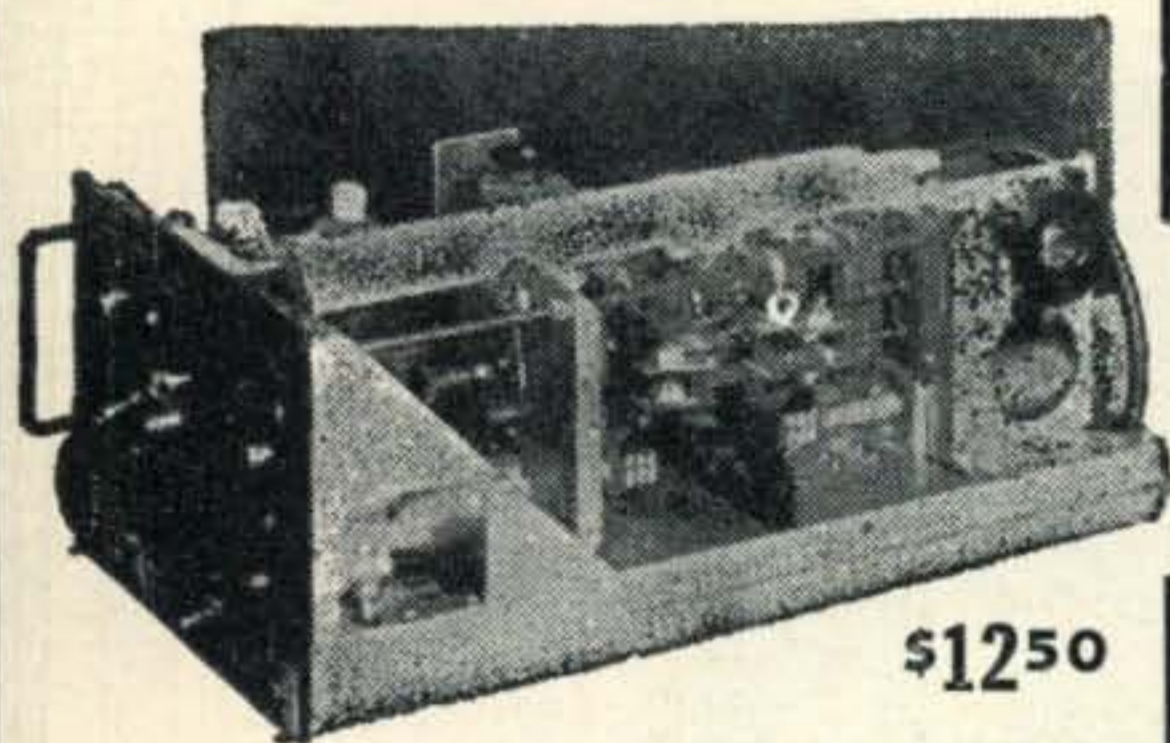

**\$1250**

Contains many excellent parts for the VHF experimenter such as a cavity oscillator using 2-RCA 8012 tubes rated at full output to 500 Mc. Tubes are forced air cooled by 24 V. DC motor, which is easily converted for 110 V. AC operation. Other valuable parts such as a pair of 807's, 2-6AC7, 1-931 and 1-6AG7 tubes; ceramic switch, potentiometers, gears, revolution counter, etc.

Lapp  
800 lb.  
safe  
working  
load  
insulators


**.95**

Lapp  
heavy  
duty  
insulator  
with  
strap  
mounts.

**165**
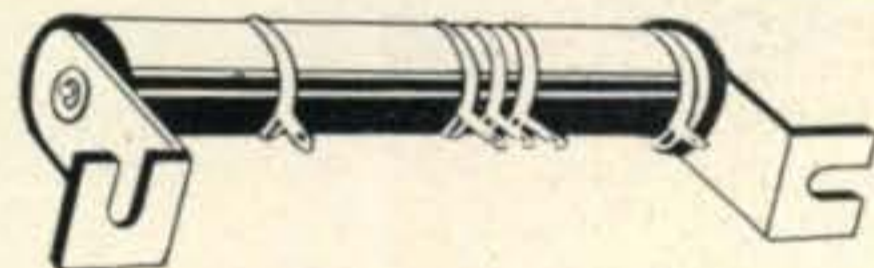
## LS-3 Loudspeaker

6" PM type, in rugged metal case for indoor or outdoor use. Weather proof. Has 4000 ohms to voice coil transformer. Case is felt lined. Price .....**\$6.50**



## WIRE WOUND VOLTAGE DIVIDER RESISTER

100 watt tapped at 3,000, 10,500, 10,523, 10,546, 11,296 ohms. With mounting clips.


Price, New.....ea. **65c**


## MG-149F INVERTER

(Holtzer-Cabot  
Elect. Co.)

Input 24  
V. DC  
36 amps.  
Output  
115 V.  
400 cy.  
AC, 500  
V. A.  
Output  
at 90%  
P.F.

**\$12.95**

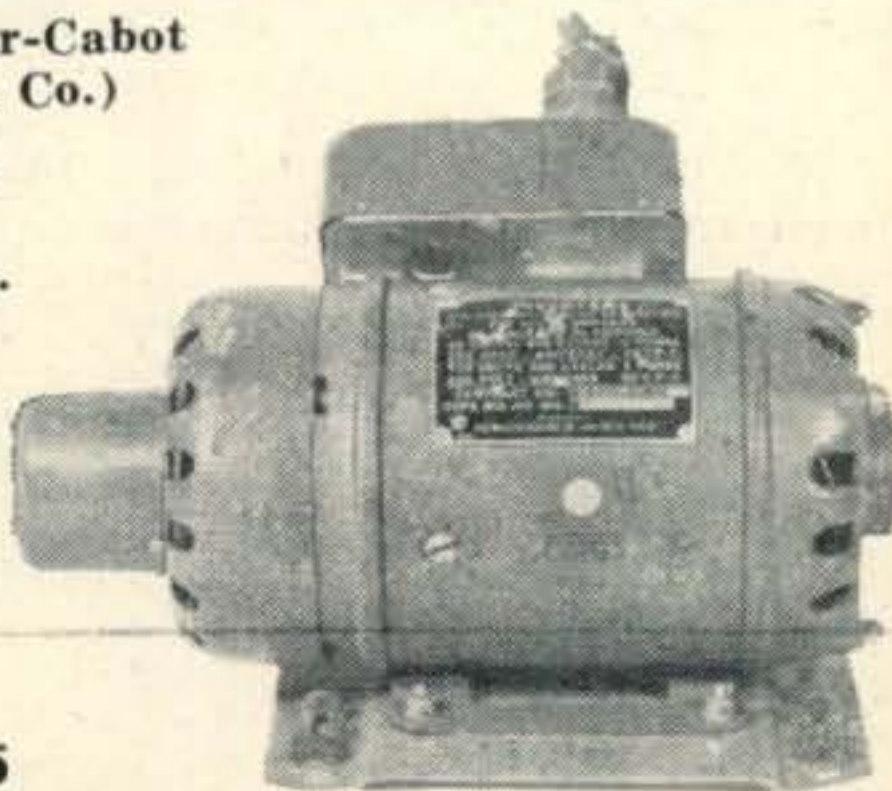

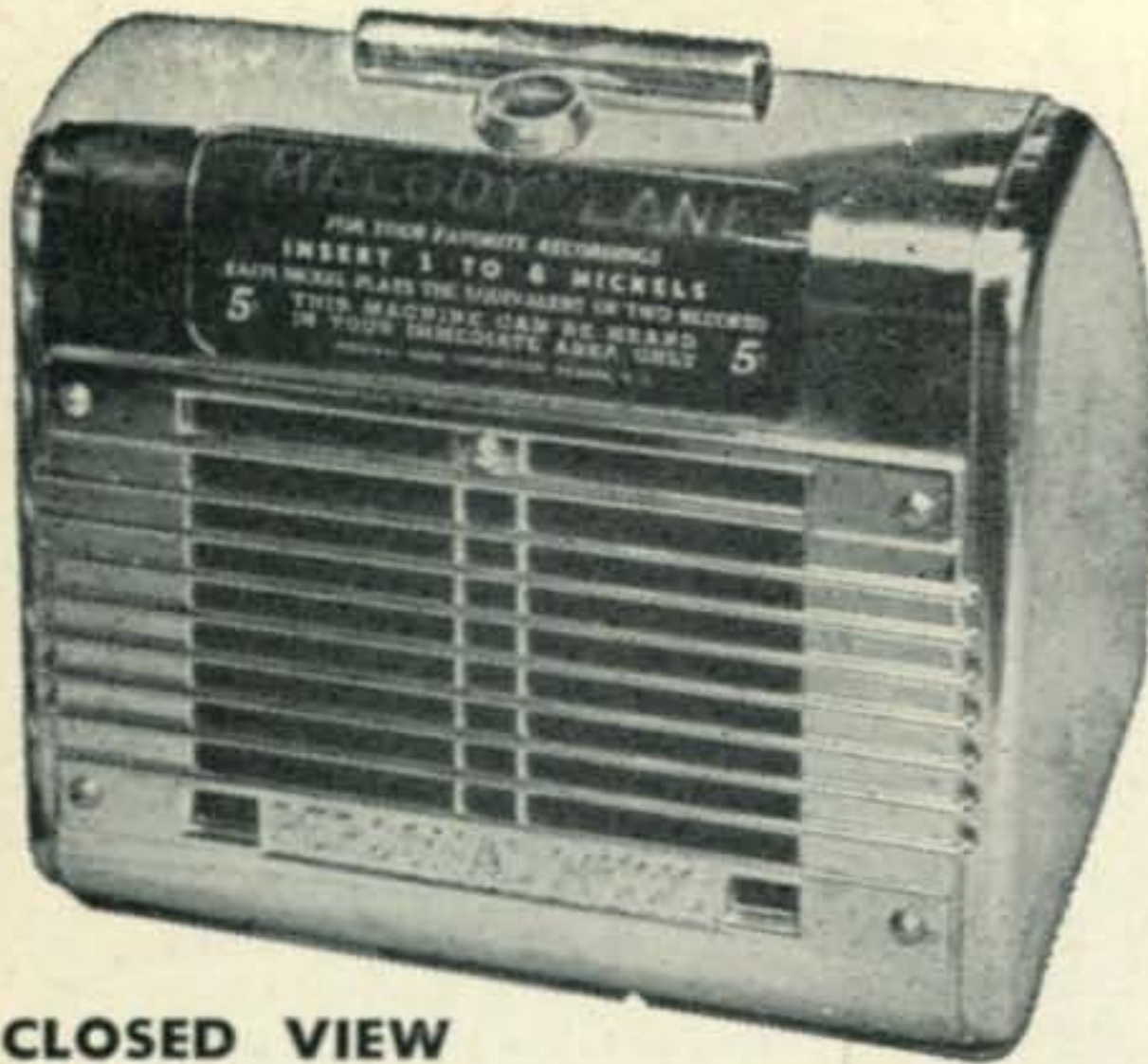

CLOSED VIEW




OPEN VIEW

**REMOTE CONTROLLED COIN INSERT AND SPEAKER BOX**

- Made by Personal Music Corp. Newark, N. J.
- Model F
- 24 Volt operated, fused
- Weight 6½ lbs.
- Size 4¾ x 7½ x 5½" high


- Sloping front
- PM Speaker 5" size
- Has 2 Pilot Lights for illumination
- Finished in chrome metal and grill with red plastic
- Accepts 1 to 6 nickels
- Each 5c coin gives about two phono records of music
- Should be mounted on a flat base
- Has Haydon Mfg. Co. timer
- Has provision for locks (lock furnished)
- Easily removable coin box, size 6" x 3½" x 1½"
- Requires 4 wires from power unit
- A beautiful piece of equipment that could be build to house coin operated radio.
- Worth several times our asking price.
- Price brand new.....**\$6.95**

**(HRU) DC POWER SUPPLY**

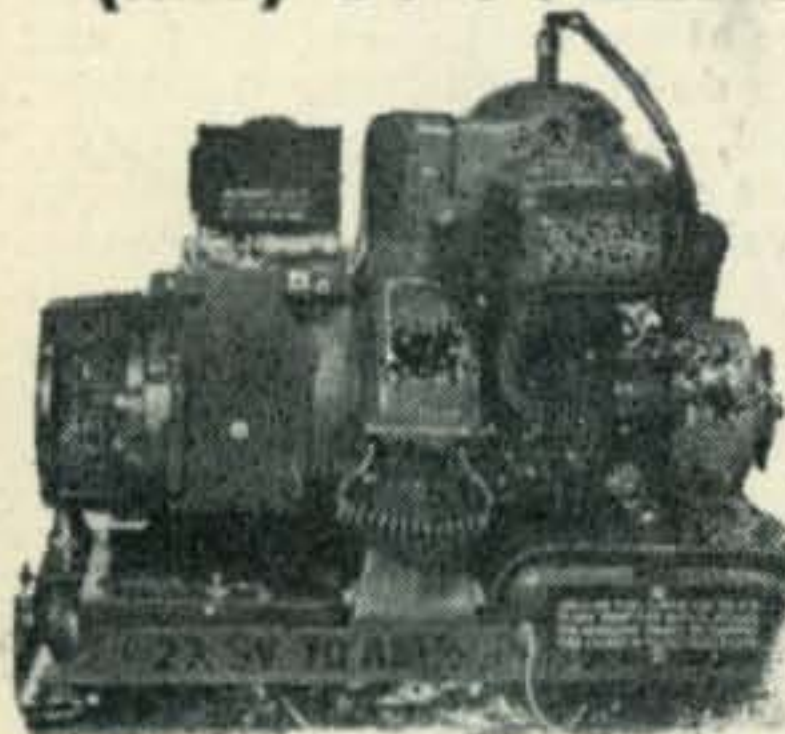

24-28 V. at 70 amp. 2000 watts gasoline engine generator with electric starter. Power supply which can be used to operate 24-28 V. equipment, start

airplane engines, charge batteries, as a welding machine, lighting system, or for amateur radio station. 21½", 17½" x 24½". Wgt., 115 lbs.....**\$89.50**

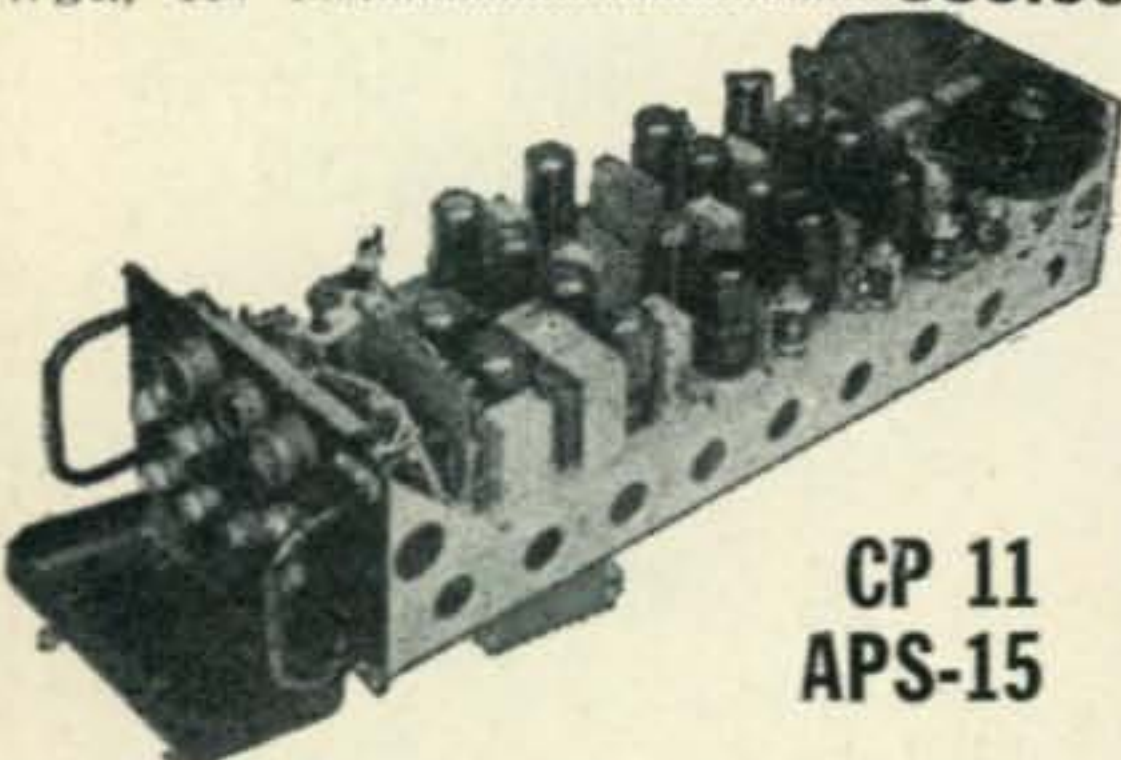


**CP 11  
APS-15**

Contains 13—6SN7-GT's, 3 6SA7-GT's 1—5Y3-GT; 24 V. motor and blower (will operate on 110 V. 60 cy.); 4—one megohm precision wire-bound resistors; 80—86 Kc. crystal. Wgt. approx. 25 lbs.

Price .....**\$9.75**

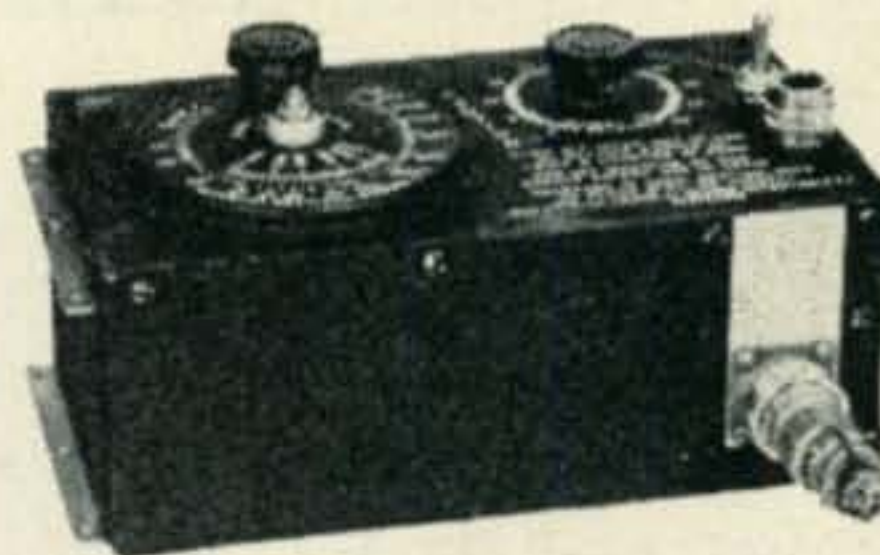**CARBON THROAT MICROPHONE**


Ideal for plane, portable, or mobile operation, also for construction of lie detectors, toys, etc. You can't afford to be without a few at the price. Adjustable elastic strap fits any neck. Works into 200 ohm impedance input circuit. Used, but in good condition. Price .....**40c**



**INTERVALOMETER**


Electronic timing device. Was used for releasing bombs at intervals. Ideal for dark-room timer, model train controller. (Contains pilot relays, switches, pilot lights resistors knobs, etc.) Price .....**\$2.25**

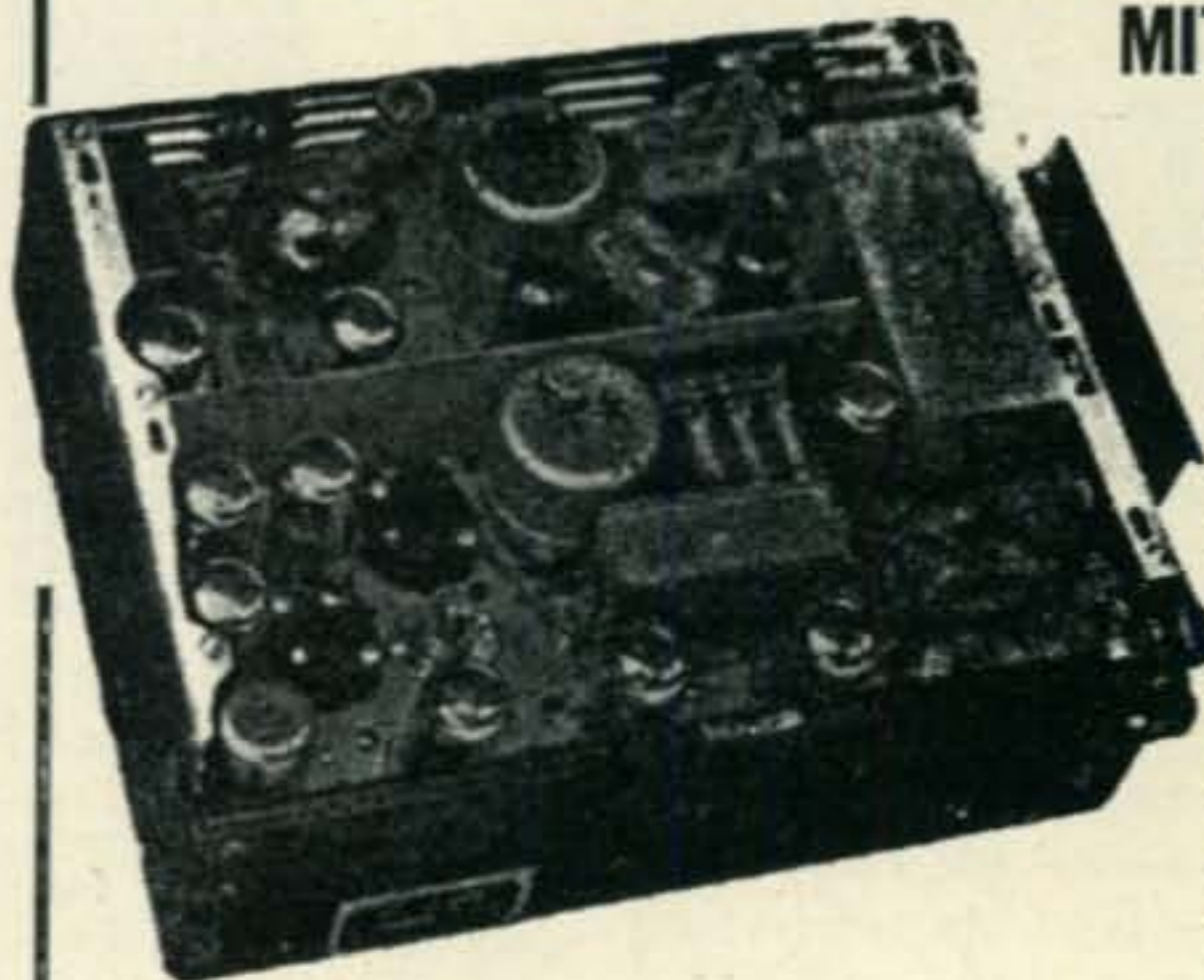**BC-645 ULTRA HI-FREQUENCY TRANSMITTER-RECEIVER**




You read about it recently in QST! Originally operated in the frequency band from 450 to 500 Mc. Can be converted to 120 Mc. amateur band. Consists of complete transmitter and modulator system, and receiver.

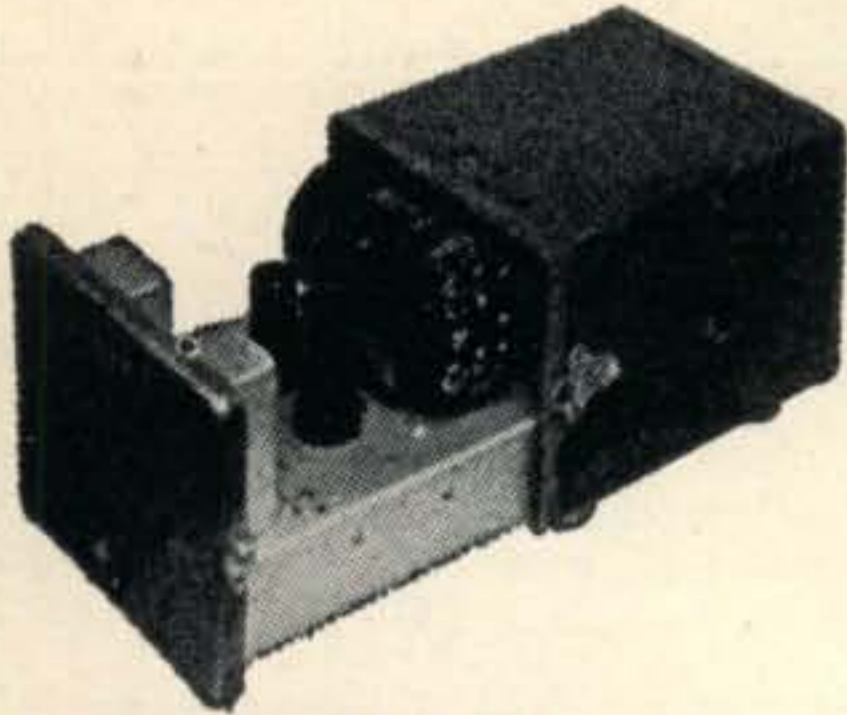See QST magazine Feb. 1947 p. 15 for conversion to work in fixed location or as mobile station for new citizen's band or amateur frequencies in 450 to 500 MC range. Complete, Brand New with 15 tubes....**\$15.00**


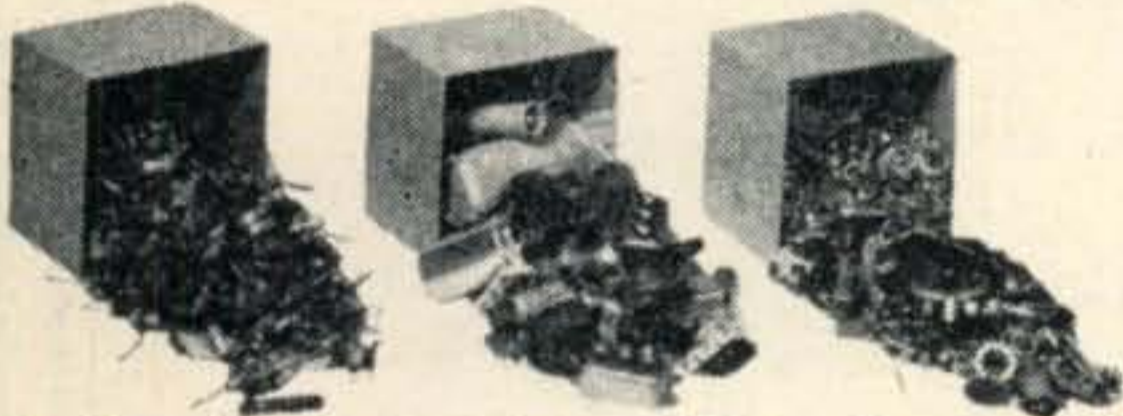
### INTERPHONE AMPLIFIER


Beautifully constructed in gray finish sturdy metal cabinet. Operates on 24 V. input. Complete with dynamotor. Has 1-6V6 and 1-6SJ7 tube, volume control, carbon or magnetic microphone input. Fastened to sturdy resilient mounting on rubber. Size 6" x 7" x 9". Shipping weight 14 lbs. .... **\$3.45**



A—Insulated Resistors. Kits of assorted resistors of various wattages and values. Some gold band resistors. 100 for **\$1.25** 500 for **\$5.49**  
 B—Condenser Kit. Contains assortment of 25 various condensers including 2-2Mfd. 600 V. filters, 1-1000 Mfd. 15 V. filter 4-1 Mfd. 400 V. paper by-pass, 3-3 gang midget trimmers. etc. .... **\$2.65**  
 C—Hardware Kit containing about 5 lbs. of radio hardware including nuts, bolts, washers, shafts, gears, grommets, lugs, screws, spacers. It is a gold-mine of invaluable parts ..... **\$1.95**



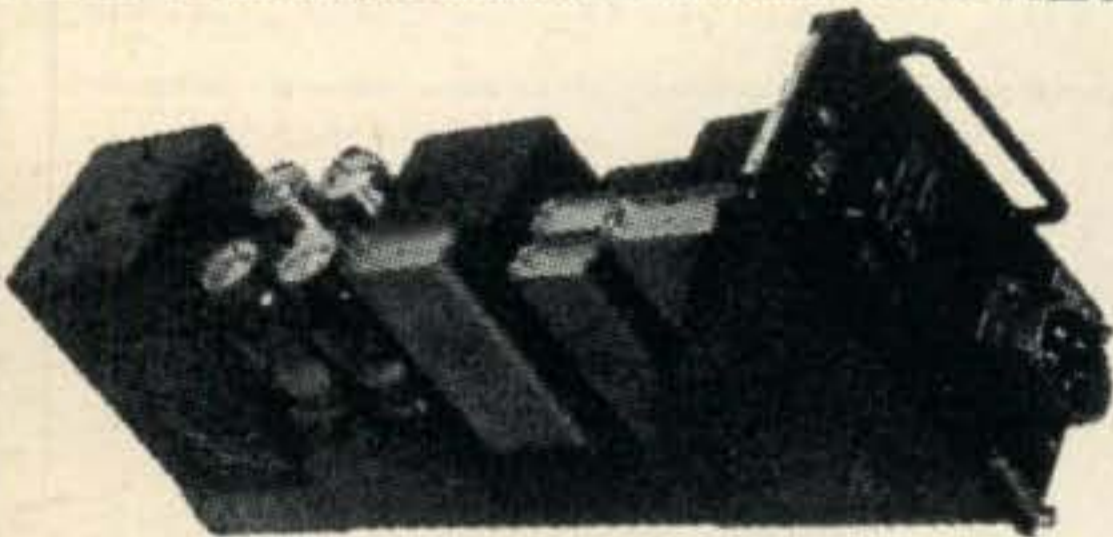
D—Resistor mounting lugs and terminal strip kit. Assorted sizes and shapes. Many, Many, Many. .... **\$1.00**  
 E—Tube Socket Kit. 25 or more assorted sockets having various usable sizes. **1.50**  
 F—Switch Kit consisting of assortment of 10 rotary and toggle switches. Price ..... **1.25**



### PP-51/APQ-9 RECTIFIER POWER UNIT

400 cycle 115 V. Contains 4-5R4GY, 2-4Mfd. 1000 V. DC condensers, 2-1 Mfd. 1500 V. DC condensers, 400-2600 cycle power transformer, resistors, etc. Weight 38 lbs. Size 21" L x 5 5/8" W x 7 3/4" H. Price ..... **\$7.95**

### BLOWER MOTOR ASSEMBLY

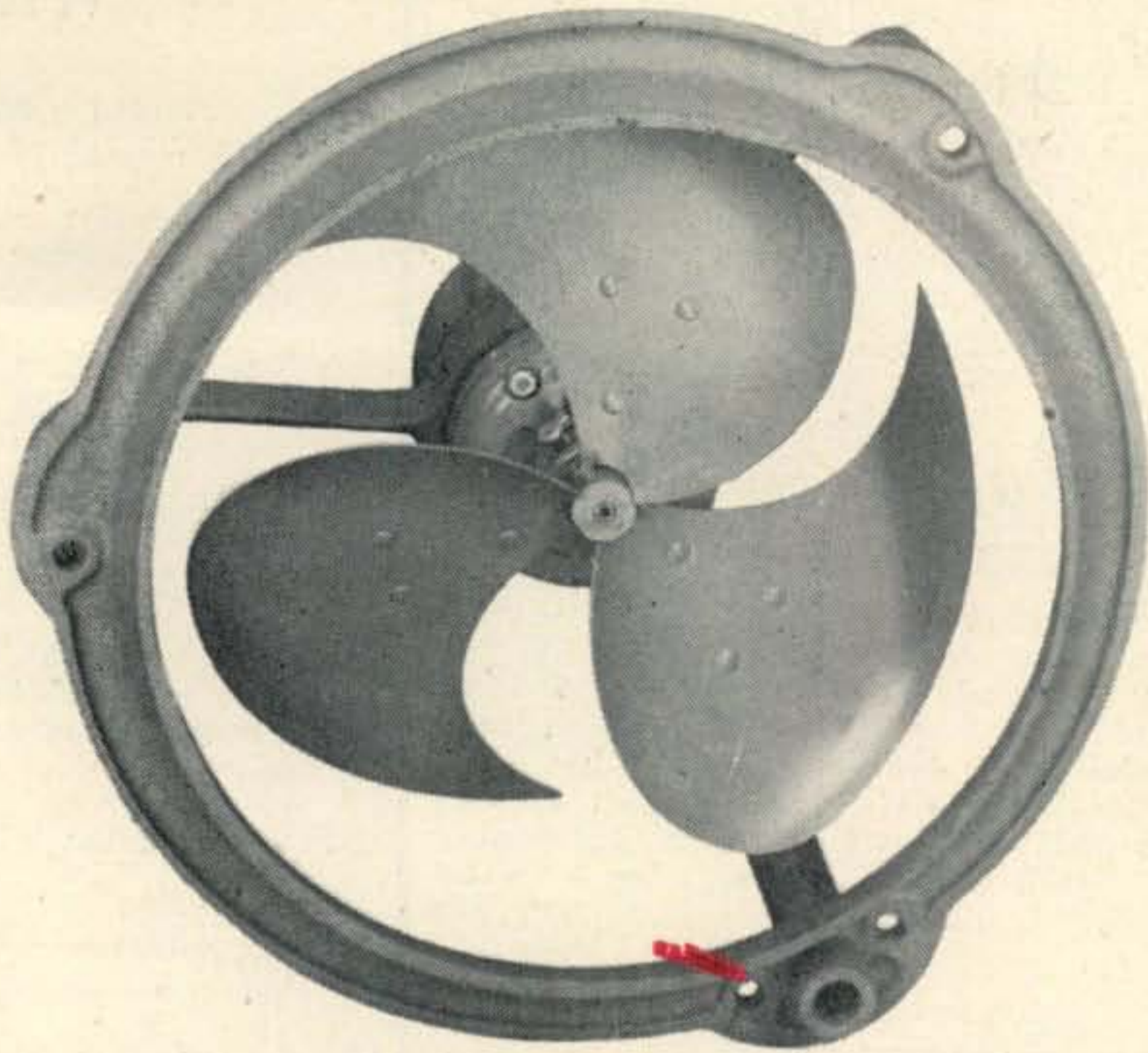

Maximum dimensions 12 1/4" dia. x 7 3/4". Input voltage 80-110 V. AC. Frequency 50-60 cycle single phase. Rpm. 1550 at 110 V. AC. Finish, 1 coat Navy gray Glyptal over 1 coat of zinc chromate primer. (New). Price..... **\$15.00**

### ARGON BULBS

2 watt, 110 Volt, Edison base. Ideal for R.F. indication, night light. Brand new, Box of ten..... **\$2.00**



CONDENSER, 2 Mfd. at 600 V. DC, oil-filled, made by Aerovox. Size 1 3/8" x 1 5/8" x 4 3/4" high overall. Has mounting screws and porcelain standoff insulators. Brand new. Price ..... **\$ .70 each**




CONDENSER, 4 Mfd. at 300 V. DC oil-filled, made by RCA. Size 2 x 2 1/4 x 3 3/4" high, with mounting flanges attached. Brand new. Price **\$ .70 each**

### BC-314
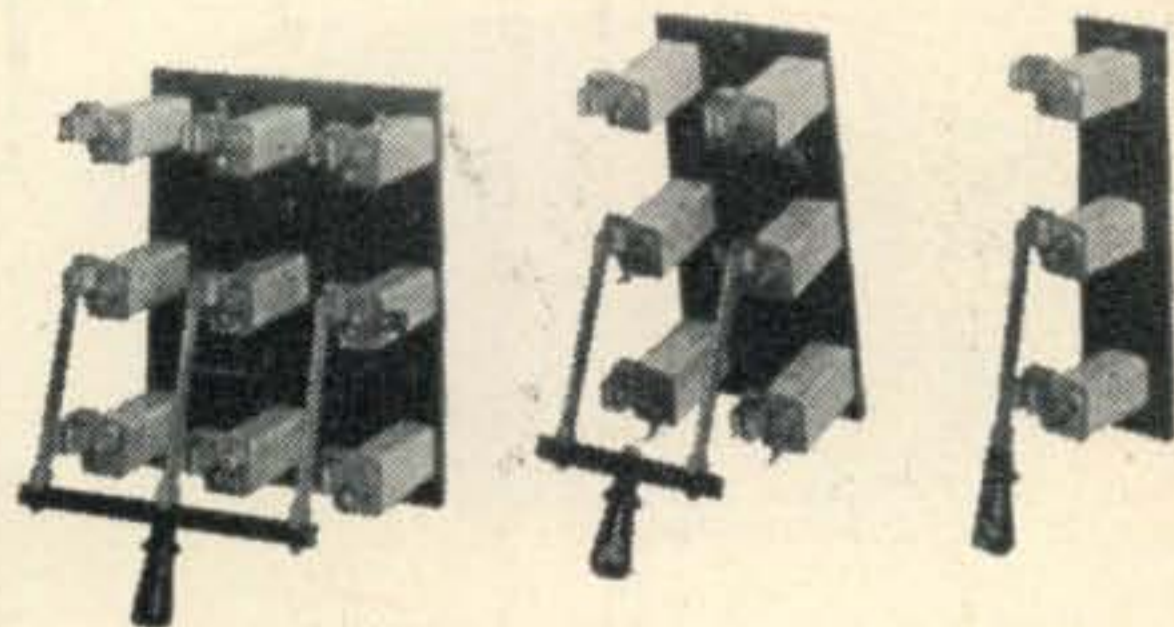
#### RECEIVER

Frequency coverage 150-1500 Kc. — 4 ranges, two RF stages, 1st detector, two IF stages, 2nd detector, RF oscillator, CW oscillator and audio. Total 9 tubes. 14 V. DC at 5.3 amps. input to dynamotor. Easily converted for 110 V. AC. Use headphones or speaker or both. New, with manual **\$99.50** Used ..... **79.50**



### ANTENNA KNIFE SWITCH

Single Pole Double Throw..... **\$1.00**  
 Double Pole Double Throw..... **1.25**  
 Triple Pole Double Throw..... **1.50**



**RECEIVER  
TUNING HEAD  
CRV-23253**

Used with CRV-46151 Receiver for vernier tuning. Has beveled dial with hairline cursor. Bands are 200-560, 560-1600, 1600-4450, 4450-9050 Kcs. Each band spread over about 280 degrees of dial edge. Has provision for flexible tuning shaft or can be adapted for direct drive on any tuning shaft. Black crackle finish. Size 5" x 3" x 2" overall. Brand new.....**\$1.50**



**PILOT'S  
CONTROL  
BOX TYPE  
CRV-23254**

Used with CRV-46151 Receiver for remote control of volume, selection of any one of six frequency bands, as off/on switch or selection of C.W. and M.C.W. and M.V.C. or A.V.C. Black crackle finish. Size 2" x 2 1/2" x 5" high. Brand new.....**\$1.50**



**INDICATOR SCOPE  
ID-41/APQ-13**

About 6" diameter by 15" deep. Contains 1-5FP7, 1-6AK5 tube, 5 Grain of Wheat 3 V. pilot lights, magnetic deflection yoke, condensers, resistors, potentiometers, sockets .....**\$7.50**


**WIRE AND CABLE**

- (A) 3 stranded conductor side of a shield. Each about 30" long. ....**20c** each
- (B) 2 conductors of stranded wire. Each strand about No. 8 gauge. Rubber covered twisted and cloth braid outer cover. ....**\$7.00** per 100 ft.
- (C) Heavy duty rubber covered 2-stranded conductor flexible. Ideal for 110 V. AC power leads for heavy electrical machinery. ....**\$10.00** per 100 ft.
- (D) 3 conductors of number 20 enameled cotton covered wire. Color coded, completely shielded. Moisture and fungus proofed. Ideal for intercom work.....**\$2.00** for 50 ft.  
**\$8.00** for 250 ft.
- (E) 4 strands of braided wire each rubber covered and color coded, one strand being shielded cotton and cambric outer wrapping. ....**\$5.00** for 100 ft.
- (F) 4 conductor wire No. 18 wires stranded rubber covered. ....**\$6.00** for 100 ft.
- (G) 4 conductor wire No. 18 wires stranded shielded rubber covered. ....**\$7.00** for 100 ft.
- (H) 2 conductor wire solid rubber conductor twisted No. 18. ....**\$1.50** for 100 ft.
- (I) 3 conductor field telephone wire twisted. **\$5.75** for 525 'roll

**COMMAND SET COMPONENTS**

- Transmitter, 4-5.3 Mc., with tubes and crystal.....Price **\$9.00**
- Transmitter, 5.3-7 Mc., with tubes and crystal.....Price **9.00**
- Receiver, 3-6 Mc. with tubes and dynamotor.....Price **10.00**
- 4-tube modulator with tubes and dynamotor.....Price **5.75**
- 3-tube modulator with tubes and dynamotor.....Price **4.00**
- Antenna meter and condenser control box.....Price **2.50**
- Single receiver control box with dial and crank Price **1.75**
- Triple receiver control box with dials and cranks Price **2.50**
- Single receiver rack .....Price **1.00**
- Double receiver control box with dials and cranks Price **2.00**
- Double receiver rack .....Price **1.50**
- Double transmitter rack ..... Price **1.50**
- Transmitter control box with switch and key.....Price **2.00**

**TURBO AMPLIFIER**

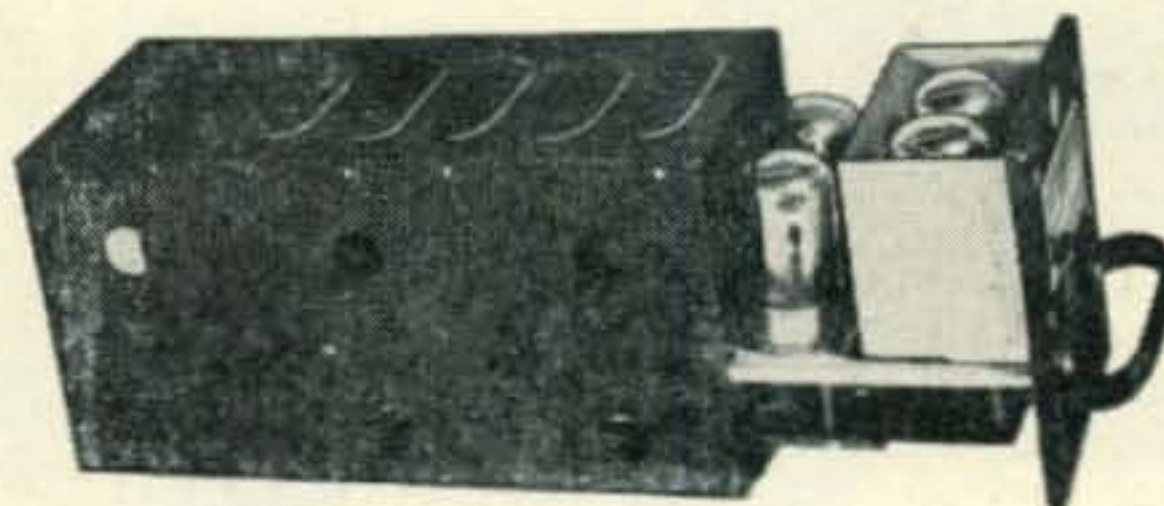

Used for parts—shipped complete with the following tubes: 2-7C5's, 1-7Y4, 1-7F7.


Price .....**\$1.75** ea.

## CABLE CONNECTORS AND PLUGS

| Manufacturer | Type          | Price   |
|--------------|---------------|---------|
| Amphenol     | AN3101-16-10P | .50 ea. |
| Amphenol     | AN3101-18-18S | .70 ea. |
| Amphenol     | AN3101-22-5S  | .60 ea. |
| Amphenol     | AN3102-22-15P | .60 ea. |
| Amphenol     | AN3102-28-10P | .60 ea. |
| Amphenol     | AN3102-32-5P  | .60 ea. |
| Amphenol     | AN3106-18-11S | .65 ea. |
| Amphenol     | AN3106-18-18P | .65 ea. |
| Amphenol     | AN3106-24-6S  | .80 ea. |
| Amphenol     | AN3106-24-7P  | .90 ea. |
| Amphenol     | AN3106-32-5S  | .90 ea. |
| Harwood      | AN3108-14S-*  | .65 ea. |
| Aero         | AN3103-14S-2S | .65 ea. |
| Cannon       | AN3108-14S-2S | .65 ea. |
| Amphenol     | AN3108-14S-2S | .65 ea. |
| Amphenol     | AN3108-18-12P | .80 ea. |
| Amphenol     | AN3108-22-5S  | .80 ea. |
| Cannon       | AN3108-22-5S  | .80 ea. |
| Amphenol     | AN3108-24-6P  | .90 ea. |
| Amphenol     | AN3108-24-16S | .80 ea. |
| Cannon       | AN3108-24-16S | .80 ea. |
| Amphenol     | AN3108-32-5P  | .90 ea. |
| Amphenol     | AN3108-28-10P | .90 ea. |



## WILLARD LEAD ACID CELLS

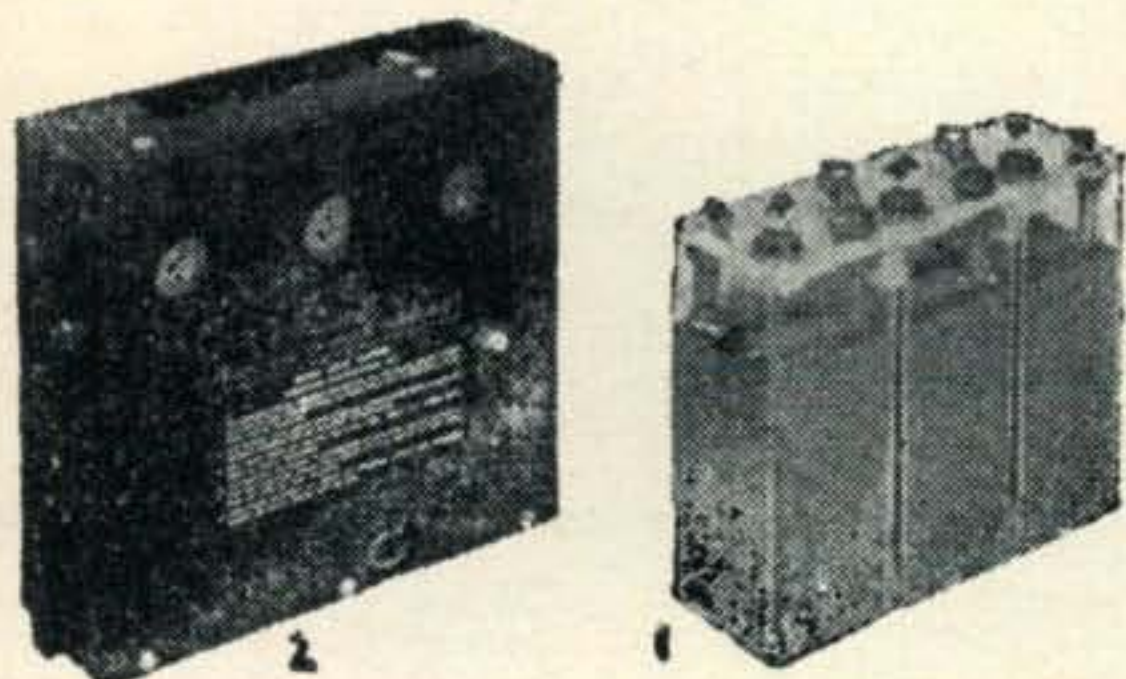

- 6 V. (New) (Dry-charged).....\$3.00
- 6 V. (In metal carrying case) (Add electrolyte specific gravity 1.625) (Drugstore). \$4.00


## 24V—L-350 AMP LEECE NEVILLE AIRCRAFT GENERATOR for HEAVY DUTY WORK

24 V L-3—50 Amp—Leece Neville aircraft generator for heavy duty work. Can be used on automobiles, etc. for that 24V rig. Weight 24 lbs. — 5" diameter—11" long — (3/4" diameter; 1" length shaft). Brand new.....\$17.50

## TRANSFORMER

Transformer, 110 volts 60 cycle input; output being two secondaries—each giving 14 volts at 11 amperes, which can be used alone, in parallel, or in series for various voltage and current combinations. Size about 3 1/2" x 3 1/2" x 4" high. Ideal for operation of propeller pitch motors used for beam antenna rotation. Shipping weight 7 lbs. Manufactured for our company. Brand new .....\$5.95

## BC-733D LOCALIZER RECEIVER

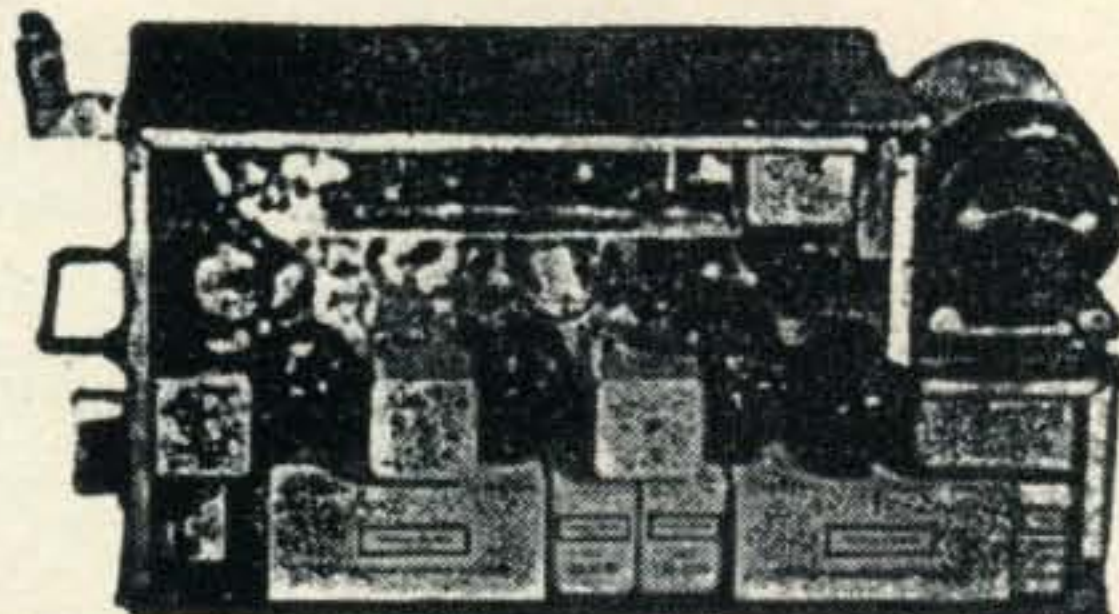

A part of aircraft blind landing equipment. Operates on any six of its predetermined crystal controlled frequencies in the range of 108120 mc. Contains 10 tubes, three of which are WE-717-A's—and crystals. Ideal receiver for conversion to 144 mc. ham band or mobile telephone bands. For 24 V. DC operation. Size 14 1/2" x 7" x 4 5/8". Price with dynamotor.....\$5.95

**HONE and WHETSTONE**  
HUNTER'S and FISHERMAN'S SPECIAL! ALSO  
FOR HOME WORKSHOP and MACHINE SHOP



Fine quality, high-grade knife, fishhook, tool and hand-axe sharpener and polisher. U.S. Government surplus. Light weight (weight less than 1 ounce). Size, 1/2 inch wide x 4 inches long. One-half of instrument is finest possible whetstone and other half is cork rust remover and polisher. Any trapper, hunter, fisherman, hobbyist or machinist cannot afford to pass up this bargain.



**15c**  
EACH

ORDER NOW

**RECTIFIER ASSEMBLY**

Selenium 15 amps. maximum continuous DC current inductive load for continuous duty. Maximum AC input 46 V. RMS single phase. DC output maximum 34.9 Volts. These rectifiers were used in Navy type CLG-20341 rectifier power unit which delivered 6-12-24 Volts DC current at 15 amps. Maximum dimensions 4 3/8" dia. x 12 3/4" long.

Price New.....**\$12.50**

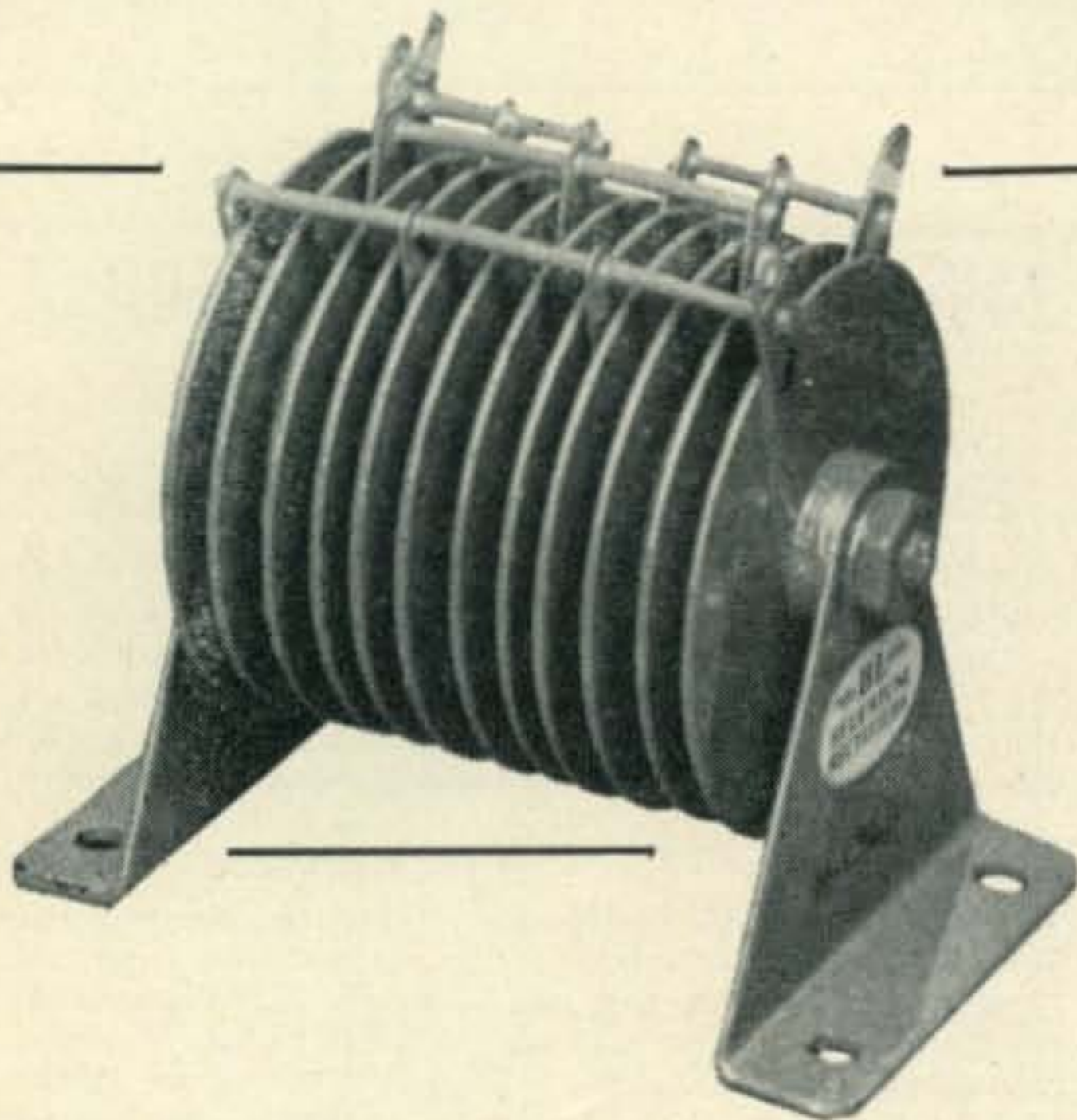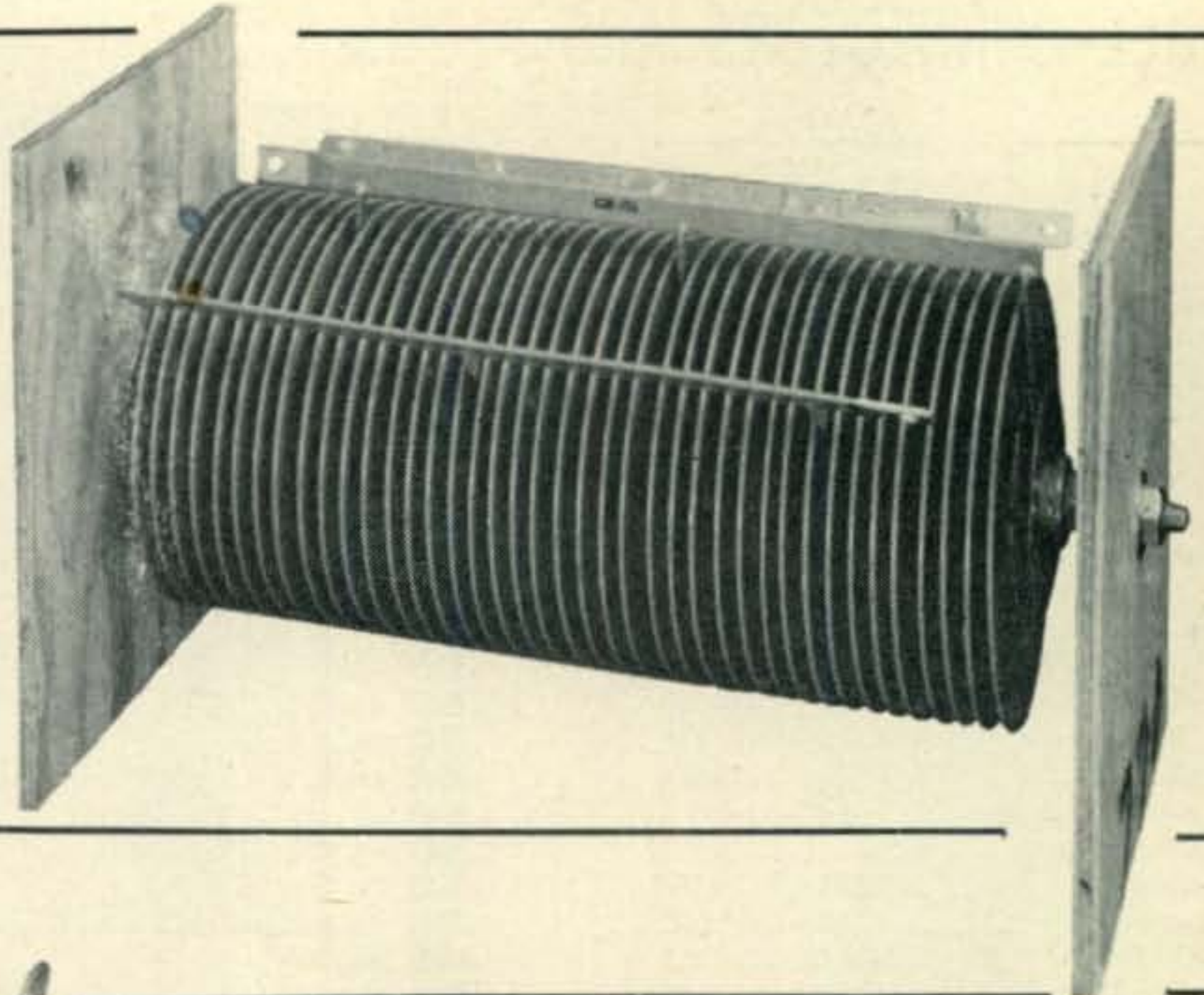

**RECTIFIER SELENIUM**

Maximum AC 60 cycle sine-wave. Input 13 Volts; output 9 Volts. Continuous current rating 2 amps. with inductive or resistive load. Maximum dimensions 3 1/8" x 1 1/16" x 1 1/16". 12 square plates bridge circuit. (New).

Price.....**\$4.00** ea.

**BL - SELENIUM RECTIFIER**

Type 23751, half-wave. Use 2 of these for full-wave circuit converting 110 V. AC to 135 V. DC at .75 amps. or parallel for higher current ratings. Voltage output controlled by condenser across output.

Brand new. Price.....**\$1.75** ea.



**WESTINGHOUSE RECTIGON BATTERY CHARGER BULB**

Style 289416, 6 ampere rating. For replacement in most chargers or for building power supply to use on D.C. operated equipment. Brand new.....**\$2.50** ea.

# MINE DETECTOR SCR-625 *BRAND NEW*

## Attention: Lumbermen, Prospectors, Miners, Plumbers, etc.



Below is a description of one of the finest metal detecting Mine Detectors ever built.

Operates in the manner of aural and visual method.

If you are looking for metal buried in logs, pipes in the ground, ore bearing rocks, underground cables, metallic fragments in scrap materials, metallic money buried or hidden in undetermined places this Mine Detector will probably surpass anything that was ever built. The United States Forestry Service has recommended procedure for using this detector to find concealed metal in tree logs and other timber products. Our government is reported to have paid several times the amount of our prices. They originally were sold by War Assets to jobbers for \$166.00.

Unit consists of a balance-inductance bridge, a two tube amplifier and a 1000 cycle oscillator. The presence of metal disturbs the bridge balance resulting in a volume change of the 1000 cycle tone. Tubes used are low battery drain types such as 1G6 and 1M5. The circuit may be modified for control of warning signals, stopping of machinery etc., when metal is detected.

Operates from two flashlight batteries and 103 v (B). However a power supply operating for 100 v may be used.

This unit is brand new and comes complete with spare tubes, spare resonator and instruction manual—in wooden chest 8-1/4 inches x 28-1/4 inches x 6 inches. Weight in operation is 15 pounds. Packed in original overseas container.

We do not know exactly what the deepest possible penetration would amount to when this detector is used but we have had customers who have bought the detectors with the expectations that the detector would locate metallic objects buried several feet under the ground or under water and we have had absolutely no complaints whatsoever regarding the detector not living up to the customers expectations.

Price **\$79<sup>50</sup>**  
Shipping Weight 125 Pounds

We can not over emphasize our belief that if an Army surplus mine detector could solve your problems in detecting metal this detector should fill the bill.

NOTE: Batteries are not furnished, we can supply for \$4.50 extra.

**ESSE**

*Radio Co*  
130 W. New York St.  
Indianapolis 4, Ind.

Unless Otherwise Stated, All of  
This Equipment Is Sold As Used  
**CASH REQUIRED**  
**WITH ALL ORDERS**  
Orders Shipped F.O.B. Collect

# MERIT

## news


### Merit Plate Transformers

MERIT LEADS AGAIN!

Now! Merit Plate Transformers, open and sealed types, for small transmitters, amateur, or experimental use, provide you with transformer equipment unequalled . . . for dependability—for economy. Shown below are four more leaders in the Merit quality line—your best buy, by all odds!

BUY THEM FROM YOUR  
MERIT DISTRIBUTOR TODAY!

Open Type Mounting "D"

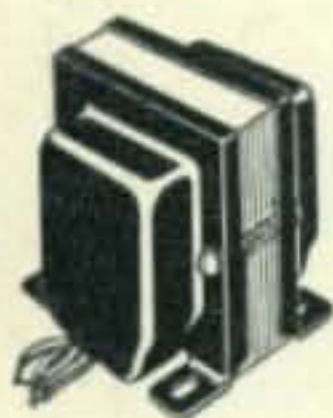

| Type No. | Net Price | Sec. Rms. Volts                     | Sec. DC Volts  | Sec. DC MA |
|----------|-----------|-------------------------------------|----------------|------------|
| P-3157   | \$6.90    | {660-660} <sup>†</sup><br>{550-550} | {500}<br>{400} | 250        |
| P-3159   | 8.10      | {900-900}<br>{800-800}              | {750}<br>{600} | 225        |

<sup>†</sup>Has 40-volt bias tap

Sealed-in Type Mounting "H"



| Type No. | Net Price | Sec. Rms. Volts       | Sec. DC Volts | Sec. DC MA |
|----------|-----------|-----------------------|---------------|------------|
| P-4057   | \$9.60    | {660-660<br>{550-550} | **500<br>400  | 250        |
| P-4059   | 10.80     | {900-900<br>{800-800} | {750<br>{600} | 225        |

\*\*Has 40-volt bias tap

PRODUCTS OF MERIT



FINE  
RADIO  
PARTS

# MERIT

COIL & TRANSFORMER CORP.

ANNIVERSARY  
25

4429 NORTH CLARK ST., CHICAGO 40, ILL.

## YL's FREQUENCY

(from page 52)

### YL of the Month

In keeping with the increased recognition afforded YLs these days, we were greatly interested to read this note in W6QD's DX column some time ago: "The Radio Club of Peru recently celebrated its 17th anniversary, and for the first time it admitted YLs to the affair. Possibly responsible for this was the ham spirit shown by OA4D who is the first Peruvian YL operator."

OA4D is Clemencia Palma of Lima, Peru, who tells a most interesting story of how she came to be a radio amateur.

"My brother, Ricardo (now OA4M)," writes Clemencia, "is in broadcasting, and has always been interested in everything concerned with radio. He acquired his station equipment—which afterward he transferred to me—during the last months of 1940, the year in which

he became a radio amateur, with the call OA4D. Near his house there

lived a German fellow who spent the entire day listening to German news broadcasts, and at times my brother caused QRM

to his reception. Taking revenge for the interference my brother caused

him, every time Ricardo went on the air the German fellow would turn

on his electric razor, or some other motor, in order to interfere with my

brother's reception. You can well understand how angry that QRM made Ricardo, so he decided to

bring his equipment to my house and operate here

"Since that time I have become the third operator of OA4D, my brothers being the first two operators. Then came the QRT for all the North

and South American stations, with the exception of Paraguay and one amateur in Uruguay, CX3-

CN. As I like radio so much, I asked and obtained permission from my government to operate my station during the QRT, and from time to time I contacted the ZP amateurs and my very good friend, CX3CN."

A member of a well-known family in Peru Clemencia is the granddaughter of Ricardo Palma, one of the most famous of Peruvian writers. Her father, Clemente Palma, was also a writer and a journalist.

Clemencia, herself, is secretary to the general manager of a mining company which buys all kinds of minerals and exports them to the U.S.A. and Europe. "My work," she adds, "is very interesting but it takes so much of my time that I cannot

spend much on the air, though I usually operate my station from 9 p.m. (OA) onward, usually a about 14,400 kc."

Right now OA4D consists of an HT-9 transmitter, a 3-element rotary beam, and an HQ-12 receiver with an RME preselector.



Clemencia Palma,  
OA4D,  
YL of the month.



# BOB HENRY HAS IT IN STOCK AND OFFERS YOU A! BETTER DEAL!



Henry Radio stores in Butler, Missouri and 11240 West Olympic Blvd., Los Angeles, California have complete stocks of amateur, FM, Television, Short Wave, Communications, Recording, and other radio equipment. I promise you lowest prices, complete stocks, quick delivery, easy terms, generous trade-ins. I promise that you will be satisfied on every detail. Write, wire, phone or visit either store today.

*Bob Henry*  
WOPARA

## A FEW OF THE ITEMS I STOCK ARE:

|                         |           |
|-------------------------|-----------|
| Collins 75A             | \$ 375.00 |
| Collins 32V             | 475.00    |
| Collins 310B-1          | 190.00    |
| Collins 310B-3          | 215.00    |
| Collins 30K-1           | 1450.00   |
| National NC-57          | 89.50     |
| National NC-173         | 189.50    |
| National NC-183         | 268.00    |
| National HRO-7T         | 292.50    |
| National HRO-7C         | 372.45    |
| National HFS            | 142.00    |
| National NC240D         | 236.25    |
| Hallicrafters S38       | 49.95     |
| Hallicrafters S53       | 89.50     |
| Hallicrafters S40A      | 110.00    |
| Hallicrafters SX43      | 189.50    |
| Hallicrafters SX42      | 295.00    |
| Hallicrafters SX62      | 289.50    |
| Hallicrafters S47       | 229.50    |
| Hallicrafters S51       | 149.50    |
| Hallicrafters S58       | 59.50     |
| Hallicrafters S55       | 129.50    |
| Hallicrafters S56       | 110.00    |
| Hallicrafters T54       | 189.50    |
| Hallicrafters HT18      | 110.00    |
| Hallicrafters HT19      | 359.50    |
| RME HF-10-20            | 77.00     |
| RME VHF-152A            | 86.60     |
| RME DB22A               | 71.00     |
| Hammarlund HQ129X       | 177.30    |
| Gon-Set 10-11 converter | 39.95     |
| Stancor ST-203-A        | 44.70     |
| Hunter Cyclemaster      | 169.50    |

Millen, Sonar, Bud, Gonset, Silver, Premax, WorkShop, Amphenol-Mims; Jensen, Meissner, Browning; I have everything.

Some prices slightly higher on the west coast.

### LOW PRICES

I guarantee to sell to you as cheap as you can buy anywhere.

### COMPLETE STOCKS

Hallicrafters, National, Hammarlund, Collins, Millen, RME, Meissner, Meck, Gordon, Amphenol-Mims, RCA, Vibroplex, Sonar, all other amateur receivers, transmitters, beams, parts, etc. If it is amateur or communications equipment—I can supply it.

### QUICK DELIVERY

Mail, phone, or wire your order. *Shipment at once.*

### EASY TERMS

I have the world's best time sale plan because I finance the terms myself. I save you time and money. I cooperate with you. Write for details.

### LIBERAL TRADE-IN ALLOWANCE

Other jobbers say I allow too much. Tell me what you have to trade and what you want.

### TEN DAY FREE TRIAL

Try any receiver ten days, return it for full refund if not satisfied.

### FREE NINETY DAY SERVICE

I service everything I sell free for 90 days. At a reasonable price after 90 days.

### FREE TECHNICAL ADVICE

and personal attention and help on your inquiries and problems.

Butler 3, Missouri

# HENRY RADIO STORES

11240 Olympic Blvd.  
LOS ANGELES 25  
CALIF.

'WORLD'S LARGEST DISTRIBUTORS OF SHORT WAVE RECEIVERS'

## DX

(from page 45)

This will, of course, allow him to clean up that continent, and then he might as well swing it over to Africa.

W3FYS heard, via *CE3HQ*, that there are no CE6 stations active on c.w. So, it looks like if any of you fellows want to get the "W.A.C.E." certificate, you are going to have to get into the 6th district with phone.

*VK9NR* on Norfolk Island is working over the 20-meter band and puts in a good signal. Usually around 14050 and T8. As yet Norfolk isn't on the official list of countries but looks as though you better work him . . . "just in case." He is ex-*VK3NR* and will be there for a couple of years so don't feel badly if you miss him on your first 2X2 call. Norfolk is located midway between New Caledonia and New Zealand.

Out of the Northern California DX club's "DX'er," I swipe the following: *W9GMD/KJ6* is now *KP4DX*, but will be glad to QSL any of his KJ6 contacts who didn't receive a card . . . *VP4TAF* is now *KV4AG*, and he will be glad to do likewise for any of his VP4 contacts. I also see where *W6WB* has hopes of squeezing something out of *ZD7AA*, who, while active, claimed he was on St. Helena Island. I have seen Bane perform some remarkable things, but many of you will remember when "ZD7AA" made a mistake in signing off from a QSO, thus: "de W . ." etc. he hasn't been heard on the air since. The Northern California DX Club now has around 47 members, and most of them are really bonafide and ultra-rabid DX men. This old fossil *W6PB* edits their "DX'er," and I guess he ought to do a good job since he is one of the real old-timers out here. I can remember, in 1921, when he was signing 6VK on spark. When he was up too late on school nights, his mother would pull the main switch, and then it was, "To bed, Daniel!" I'll bet this strikes a familiar sound with many of you . . . same here.

*KL7KV* says that DX really comes hard in Anchorage. The town has a population of 20,000, and Bill says there are 120 licensed amateurs there . . . of course, not all of them are active.


### Credit Due

In the November column, we ran an operating code to be used by foreign DX men. We lifted this out of the "F.E.A.R.L. News," and complimented them for running it, as it was essentially the same as we have preached off and on for a couple of years. However, it develops that I didn't read far enough in the "F.E.A.R.L. News," otherwise I would have discovered it was the A.R.R.L. who set up these seven operating rules. Far be it from me to dish out credit to the wrong party; therefore, I am taking this opportunity to state that the boys at A.R.R.L. spent some time pinning down the operating code in seven clear-cut paragraphs that, if used by the DX man overseas, will go a long way toward eliminating some of the pitiful operating practices that have existed during the postwar period.

*W3JKO* says he is going to handle the QSLs for *SP8XA*, who, incidentally, is now operating

# For BOTH

## MOBILE & FIXED STATION USE

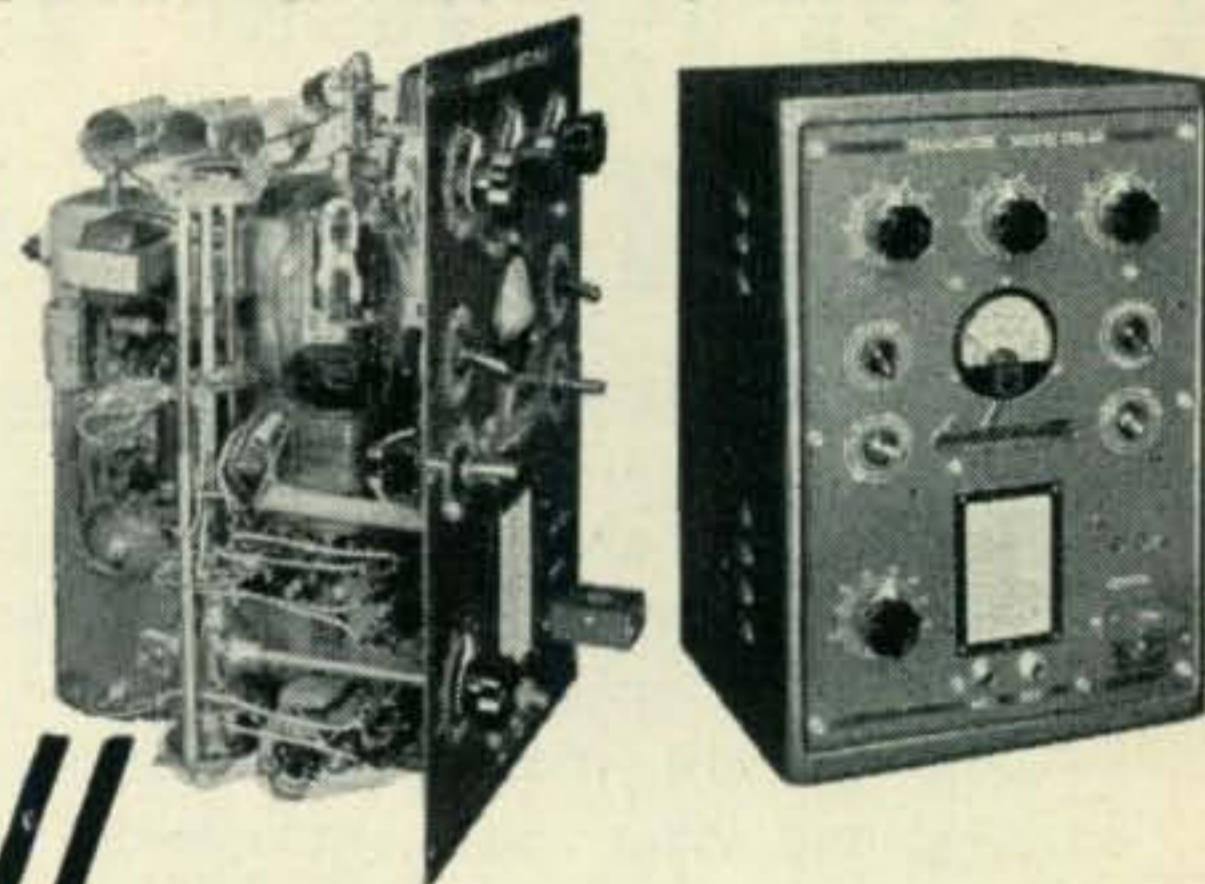

# Harvey - WELLS

### TBS - 50

### TBS - 50A

Now that mobile phone can be used on all amateur bands (except 40 meters) the TBS-50 & TBS-50A become more adaptable than ever before because it is ideal for use in automobiles, trucks, boats, camps, etc.

50 WATTS

8 BANDS

PHONE OR CW

(Class B. Modulation)

NO PLUG-IN COILS

80, 40, 20, 15, 11, 10, 6 and 2 METERS

(Completely wired and tested — not a kit)

Crystal controlled on all bands, yet requires no oscillator or multiplier tuning. Operates from AC pack or Dynamotor Supply for mobile work. New, beautiful black crackle finish.

TBS-50..Complete with tubes, only **\$99.50**

### THE NEW TBS-50A

Incorporates a small three tube preamplifier with sufficient gain so that any high impedance microphone having an output level of approximately -50 db can be used.

TBS-50A, complete with tubes only

**\$121.25**

Send for catalogue describing Harvey-Wells Transmitters, Power Supplies, Preamplifiers and Rack Panels

**Harvey - WELLS**  
**ELECTRONICS, INC.**  
**SOUTHBRIDGE,**  
**MASSACHUSETTS**



# ±1db

## 20-20,000 CPS




### The ALLIED 20 Watt Phono Amplifier An Engineer's Dream—Sensibly Priced

Here's the audio amplifier experts appreciate. It's the *big* buy in high fidelity. *Check the curves:* Note the range of the two tone controls, offering flexible compensation. *Look at the facts:* Less than 2% harmonic distortion at full 20 watts, virtually none at room levels. Up to 10 db adjustable volume expansion independent of volume control setting. 8 db of inverse feedback. Hum is 'way down—80 db below 20 watts. Dual phono input with 78 db gain. Matches anything—output impedances 4, 8, 16, 250 and 500 ohms. For record reproduction or for operation with a radio tuner, there's nothing finer at anywhere near this low price!

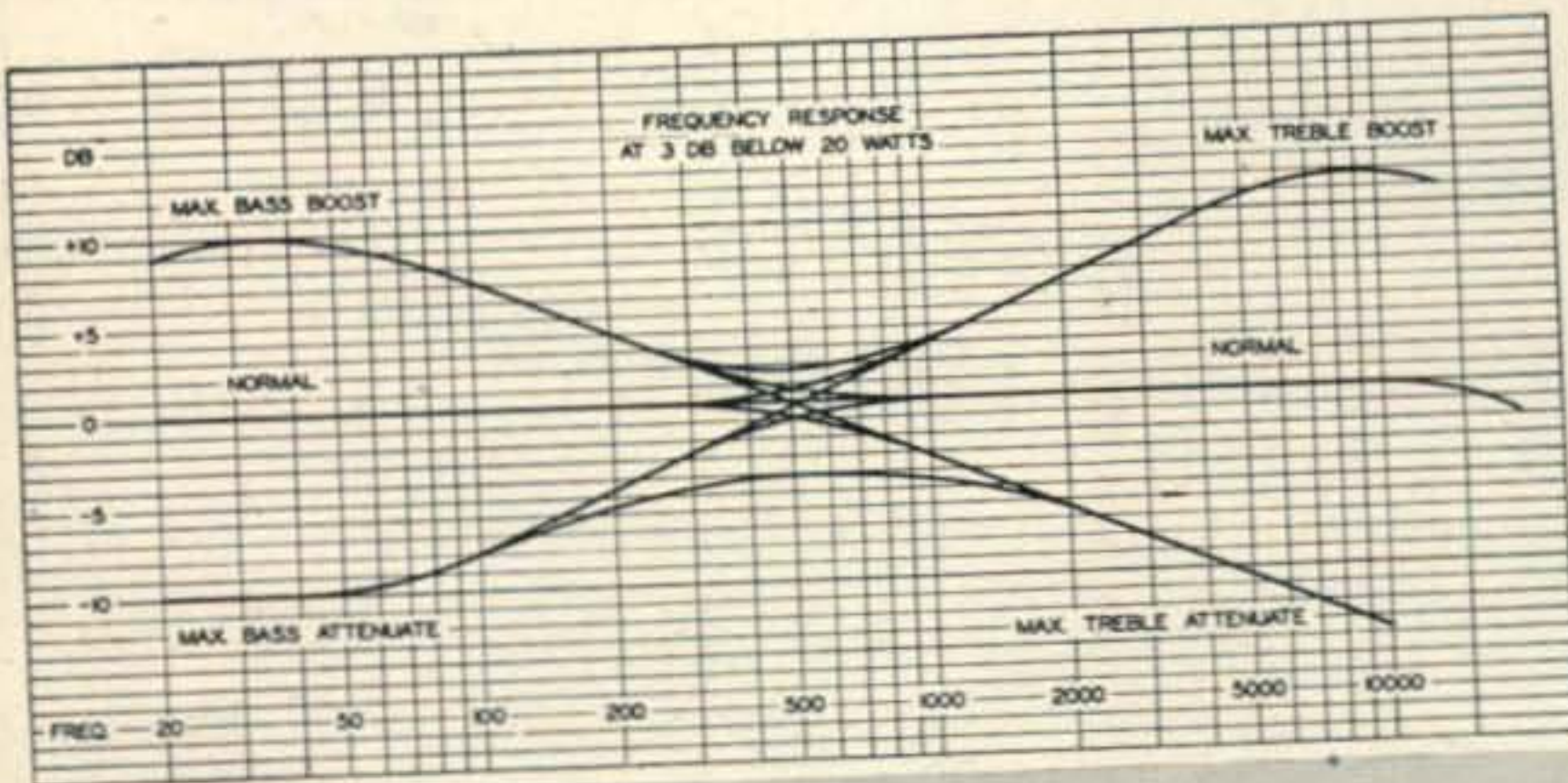93-103. 20 Watt Amplifier complete with tubes. NET, f.o.b. Chicago ..... **\$59.95**

Terms: \$11.99 down, \$5.09 monthly for 10 months



### Send for the Leading Amateur Buying Guide

You'll find everything you want in receivers, transmitters, instruments, parts and station equipment in our up-to-the-minute 180-page Catalog. Get it today. And get every buying advantage at ALLIED—fast shipment, money-saving values, top-quality equipment, ideal easy-payment terms, square trade-in deals and down-to-earth help from ALLIED's old-time Hams. For full satisfaction, get and use the ALLIED Catalog!

### Have Every Buying Advantage

- World's Largest Stocks
- Top-Quality Gear
- Money-Saving Prices
- Ideal Time Payments
- Square Trade-In Deals
- Speedy Shipment
- Ham-to-Ham Service

Keep Your ALLIED Catalog Handy

# FREE



ALLIED RADIO CORP., D. L. Warner, W9IBC  
833 W. Jackson Blvd., Chicago 7, Ill., Dept. 16-A-9

- Send FREE 1949 ALLIED Catalog
- Enter order for 20 Watt High-Fidelity Amplifier Enclosed \$.....  Full Payment  Part Payment (Bal. C.O.D.)
- Send Time Payment details and order blank.

Name.....

Address.....

City..... Zone..... State.....

# ALLIED RADIO

*Everything for the Ham*

on c.w. approximately 28,150 kc. Bob says he is sixteen years of age, and his father is a prewar ham. In any event, do not try to send any cards directly to SP8XA.

VE7HC told me that near the end of the contest, he kept pouring down the coffee trying to keep his eyes open. I guess he kept them open alright, after glancing at his score. Gord said one of the biggest surprises of the contest was after hearing CT2AB being called by a W6, he spent fifteen minutes trying to locate the CT2, with no success. He then decided that he was wasting time, so tossed out a quick CQ. Sure . . . you guessed it! Back came CT2AB.

Some fellows have been askig about MD1A, TR1P, and MD2. They are all the same country and come under the listing of "Libya" in the country list. A common question involves Cyrenaica, Libya, and Tripolitania. These are not separate countries.

If any of you boys want to work another CE7, that is, another one besides CE7AP who is on the Island of Tierra del Fuego, Chile. He is William "Bill" Shorethorse, W6DOK, of Los Angeles. Bill is no newcomer, having operated the first part of this year on 20 c.w. as KP4FX, and prewar, he was on 20 phone as KA6FB. CE7AP is very QRP as the transmitter consists of a 6L6GA with 3.5-watts input . . . His source is a 12-volt storage battery. He operates on 7006 and 14,010.

ZL2GX is still waiting for a card from Zone 17 to give him W.A.Z. Jock uses a pair of 75Ts and the antennas used are two 8JK Twin 3s. He


was lucky enough recently to grab C8KY for Zone 23. ZL1HY, although having worked C8KY sometime back, worked him again during the phone section of our recent DX contest. He also grabbed VO6EP in Zone 2 in the c.w. section. Ah . . . Zone 2 . . . Where have I heard that before???

WØNUC got a letter from OY8IGO which gives with a little info. Says he . . . "my power is now 35 watts . . . was 15. We pay about 20 cents per kwk. It is hard to get the right chassis made up here and so it is made in Copenhagen. Takes about a month to get it. You (NUC) were my contact NO. 996 and the second WØ. I am still the only active OY although OY5WS has just been licensed but at present is wireless operator on a trawler. OY8LA has returned to Denmark and is using OZ8LA now.

If you work LU9AL . . . wait 'till you see his QSL. You're in for a treat. It's about 8½ x 11 but I won't tell you more. Go and work him. W2IOP got one . . . so any of you should be able to.

I previously mentioned about G8VB but here's something else. Harold is an artist on 3.5. mc. Recently he established the first G-KP4 QSO when he worked KP4ES. If any of you stay up late enough you might listen for G8VB who is always between 3740 and 3760 kc.

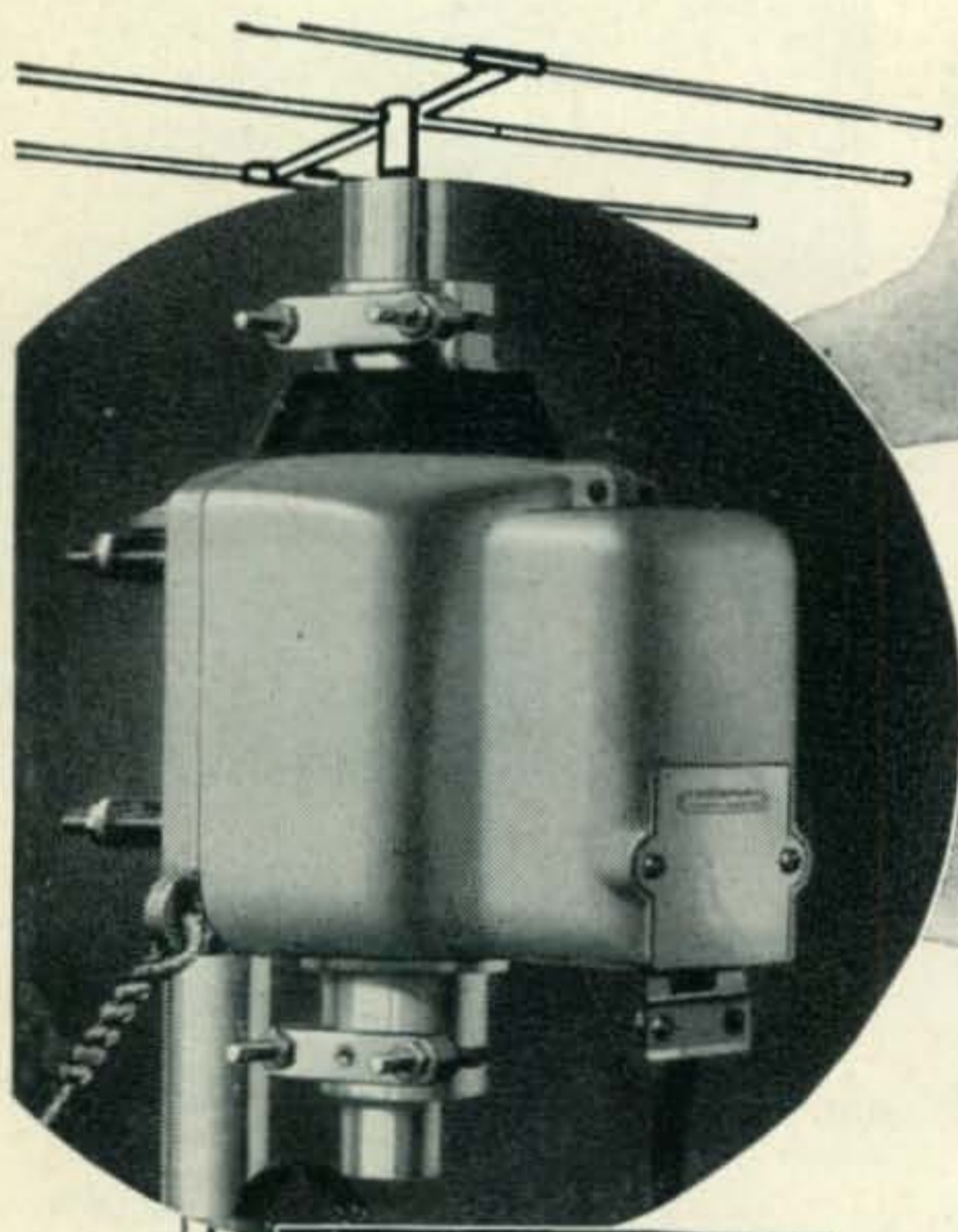In VE3QD's column in "Xtal" he writes "Heard ZC1CL and VS4AC (Laccadive Islands) in QSO the other evening. You should have heard the QRM when they finished . . . everyone in the band was calling one or the other." I imagine so . . . but what about this VS4AC guy . . .



**alliance**  
TENNA · ROTOR

Model ATR

Fits most types of antenna

Size of rotor unit 7¾" x 5¼" x 8"  
Size of control box 5" x 5"  
Approx. weight 12 lbs.  
Special 4 conductor interconnecting cable available at 5½¢ per ft. list price.

**AMATEURS—**

Get this first mass-produced Antenna Rotator!

**GETS STRONGER SIGNALS!**

**ROTATES TV AND FM ANTENNA**

LIST PRICE **\$39.95**



Amateurs—the new Alliance Tenna-Rotor will rotate most antennas from 50 m. c. upwards. Tenna-Rotor is a "beaming" device to give you positive control of rotation—select the exact spot for "peaked" reception! Operates in any weather—is quick and easy to install—consists of a fully enclosed electrically driven rotor, connected to plastic control box which plugs into any 110 volt, 60-cycle house circuit. A simple two-way selector switch rotates your antenna clockwise or counter-clockwise through 365° and stops it at any desired point on the compass! Rotor unit resists corrosion.

Ask your dealer for Tenna-Rotor!

**alliance motors**

ALLIANCE MANUFACTURING COMPANY • ALLIANCE, OHIO  
Export Department: 401 Broadway, New York, N. Y., U. S. A.

# HERE COMES LEO!

And he's offering the **MOST COMPLETE HAM CATALOG** ever assembled! Just off the press—write for your **FREE** copy today!

## WORLD FAMOUS WRL XMTRS! GLOBE TROTTER



Unconditionally guaranteed 40 watt input kit including all parts, power supply, chassis panel and streamlined cabinet.

Less Tubes **\$69.95**

Wired **\$79.50**

(1 set of Coils, Meters, Tubes, \$17.49 extra)

## GLOBE KING

Unconditionally guaranteed 275 Watts phone and CW. An advanced design XMTR giving efficient performance on 10 - 11 - 15 - 20 - 40 and 80 meter bands.

Ready to go— **\$379.45**  
Kit form

Wired **\$399.45**

Write for information on NEW 150 Watt Globe Champion.



**LEO I. MEYERSON**

**WØGFQ**

**CU ON 20 - 10 & 75 METERS**

### E-Z PAYMENTS

WRL offers the lowest E-Z Payment Plan in the country. Any responsible person with a steady job can buy on time from Leo. **No red tape—no delays!** Financing our own paper saves you money!

### LIBERAL TRADE-INS

Leo offers more—use your present equipment as a trade-in. Tell me what equipment you have—what equipment you want—let's trade.

### PERSONAL SERVICE

WRL is the World's Most Personalized Radio Supply House for the amateur. Getting acquainted with Leo will help you get on the air faster and for less money.

## GIANT RADIO REFERENCE MAP

Just right for your control room wall. Approximately 28" x 42". Contains time zones, amateur zones, leading shortwave stations, monitoring stations. Mail coupon today & **25c**

Save Money On Reconditioned Equipment—Write For Our Big List!

**FAST SERVICE  
ON FOREIGN ORDERS**

WRITE—WIRE  
PHONE 7795

WORLD RADIO LABORATORIES  
744 West Broadway  
Council Bluffs, Iowa

C-1

Please send me:  
 Radio Map  
 New Catalog

- 40 Watt Globe Trotter Info.  
 150 Watt Globe Champion Info.  
 275 Watt Globe King Info.

Name .....

Address .....

City..... State.....

**World Radio**  
LABORATORIES INCORPORATED  
COUNCIL BLUFFS, IOWA

If any of you fellows work W3AYS ask him about his antenna problems. He's using some sort of a long wire with a tuning system, which of course, changes from a band to band. He likes the long wire stuff over some of the others. W6EPZ says that as bald as he is he is still losing hair over trying to get QSL cards out of Zones 18 and 19. Better get a bottle of Vitalis and hang on a while longer.

Those of you who worked VO2CJ may like to know he is now back in the States. While in VO2 he was running 120 watts into a pair of 807s and worked 30 zones and 67 countries . . . which to him was a heap of fun.

W9BZB goes after the 10 phone type of DX but sadly admits that these were heard but not worked . . . EA4FC, 28,350, SV0WB 28,350, and VQ8AE 28,300. KL7PJ worked about 430 stations during the Contest and is going to QSL via the bureaus. This will save time and a little dough . . . and as Chuck says, "I'm going to QSL 100 per cent whether they want 'em or not."

W2EMW has the Contest and the good conditions which we arranged, to thank for two new ones . . . ST2FU and VP8AM. G6QX has his rotating dipole working now picked off KL7KV for his first Zone 1 QSO. Bob says he hopes this will get him out of the booby spot in the Honor Roll.

ET3AB is back in England and the QTH will be found . . . oh, you know where. Well, anyway apparently he was supposed to be the QSL manager for the ET3 gang and relates that ET1IR and ET1JJ do not hold valid licenses. Says he

received over 200 QSL cards for these stations but doesn't say whether or not he got them to these boys. According to W4HA . . . 4X4AA is Joe of ZC6LA and who says there are three other 4X stations on looking for contacts.

W0NUC tells me that one of the Zero quartet W0GKS, has sold out. Yep, sold out the works. Doesn't have anything around the joint pertaining to ham radio. Something about this just doesn't sound like Doc. Let's get him back. . . whatdya need Doc, a toob? Another Zero, W0UOX, is climbing up the ladder of DX and it won't be long before he'll be giving all these guys a run for top spot. Leo . . . that's NUC . . . goes on to say that he's sleeping better since he took out insurance for wind, fire and lighting damage.

Everybody seems to be working AC3GG but no one knows where the heck he is and until we know . . . we ain't accountin' it. Just hold off sending that one in for credit 'till you hear more from us. Remember ZD7AA . . . well! W6TMP passes on the dope that HL1BA is being called "boot-legger" but insists he will QSL when he gets back to the States. W8ZY barged in to see W4FU a while back and guess who else barged in . . . W6GRL. Bet it was pretty deep around there for a while.

KH6LF tells us that Johnston Island may be void of ham radio for a while. Seems as though the two boys that have been there, W4DGW and KJ6AB, have been transferred. He said efforts are being made to secure a ham for there, and one of the boys now stationed on Johnston is taking his ham exam, but, of course, at this time, we

## WORKSHOP

### 10 over 20 Stacked Array with Rotator and Indicator

This combination is the last word in amateur antenna equipment: —

- High Gain
- Light Weight
- Rugged Construction
- Aluminum Alloy Elements
- New Model Rotator with Solenoid Brake
- Matches Directly to 72 Ohm Line




**THE WORKSHOP ASSOCIATES, Inc.**

Specialists in High-Frequency Antennas

52 NEEDHAM ST., NEWTON HIGHLANDS 61, MASSACHUSETTS

# Build YOUR OWN TEST EQUIPMENT
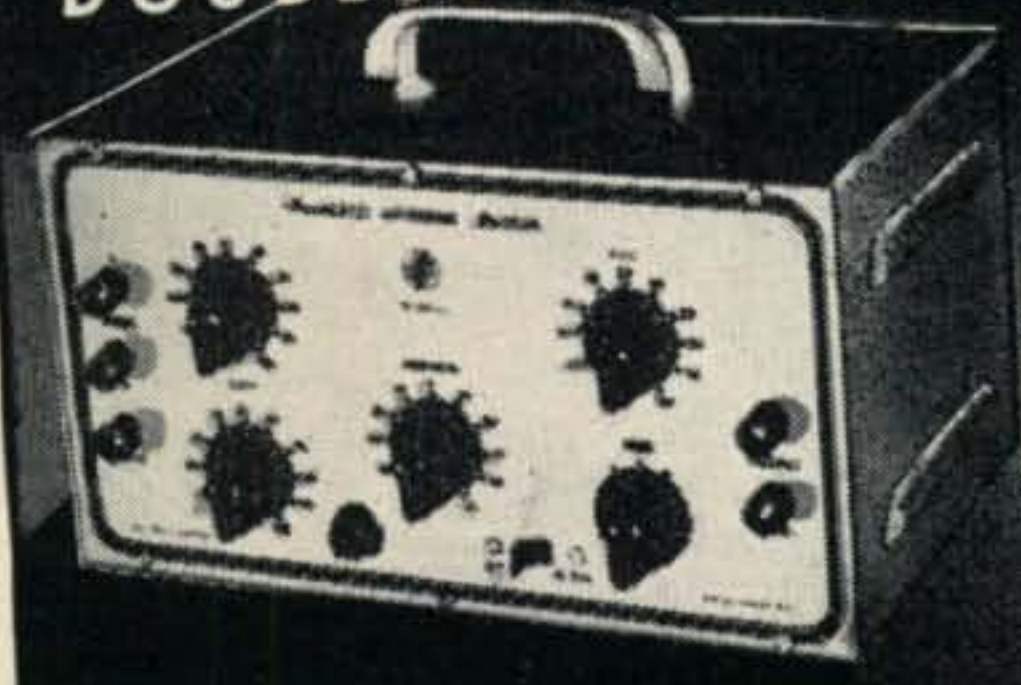
## Heathkit ELECTRONIC SWITCH KIT DOUBLES THE UTILITY OF ANY SCOPE




**\$34.50**

See two separately controllable traces with individual inputs on any scope. See both the input and output traces, locate distortion, phase shift, etc., immediately. Individual gain controls and positioning control. Coarse and fine sweeping rate controls. Complete Heathkit matches others, with 5 tubes, All metal parts are punched, formed and cadmium plated. Complete with tubes, all parts, detailed blueprints and instructions. Shipping Wt. 13 lbs.  
**Nothing ELSE TO BUY**

## HEATHKIT CONDENSER CHECKER KIT

**\$19.50**

*Nothing ELSE TO BUY*

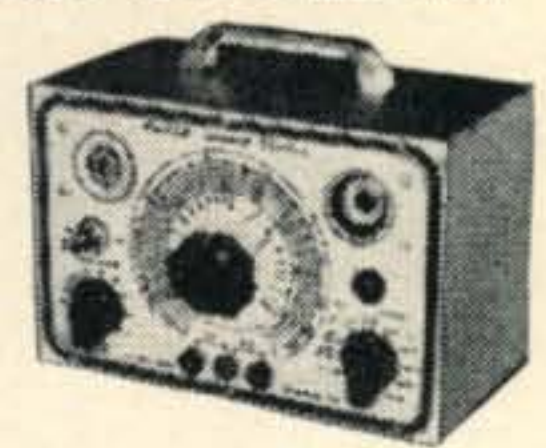

A condenser checker anyone can afford to own. Measures capacity and leakage from .00001 to 1000 MFD on calibrated scales with test voltage up to 500 volts. No need for tables or multipliers. Reads resistance 500 ohms to 2 megohms. 110V 60 cycle transformer operated complete with rectifier and magic eye indicator tubes. Easy quick assembly with clear detailed blueprints and instructions. Small convenient size 9" x 6" x 4 3/4". Wt. 4 lbs.

## HEATHKIT SIGNAL GENERATOR KIT



**\$19.50**

**NOTHING ELSE TO BUY**

Every shop needs a good signal generator. The Heathkit fulfills every servicing need, fundamentals from 150 Kc. to 30 megacycles with strong harmonics over 100 megacycles covering the new television and FM bands. 110V 60 cycle transformer operated power supply. 400 cycle audio available for 30% modulation or audio testing. Uses 6SN7 as RF oscillator and audio amplifier. Complete kit has every part necessary and detailed blueprints and instructions enable the builder to assemble it in a few hours. Large easy to read calibration. Convenient size 9" x 6" x 4 3/4". Wt. 4 1/2 lbs.

## HEATHKIT SIGNAL TRACER KIT



**\$19.50**

*Nothing ELSE TO BUY*

Reduces service time and greatly increases profits of any service shop. Uses crystal diode to follow signal from antenna to speaker. Locates faults immediately. Internal amplifier available for speaker testing and internal speaker available for amplifier testing. Connection for VTVM on panel allows visual tracing and gain measurements. Also tests phonograph pickups, microphones, PA systems, etc. Frequency range to 200 Mc. Complete ready to assemble. 110V 60 cycle transformer operated. Supplied with 3 tubes, diode probe, 2 color panel, all other parts. Easy to assemble, detailed blueprints and instructions. Small portable 9" x 6" x 4 3/4". Wt. 6 pounds. Ideal for taking on service calls. Complete your service shop with this instrument.

## HEATHKIT SINE AND SQUARE WAVE AUDIO GENERATOR KIT

The ideal instrument for checking audio amplifiers, television response, distortion, etc. Supplies excellent sine wave 20 cycles to 20,000 cycles and in addition supplies square wave over same range. Extremely low distortion, less than 1%, large calibrated dial, beautiful 2 color panel, 1% precision calibrating resistors, 110 V 60 cycle power transformer, 5 tubes, detailed blueprints and instructions. R.C. type circuit with excellent stability. Shipping weight 15 pounds.



**\$34.50**

*Nothing ELSE TO BUY*

## THE NEW HEATHKIT VACUUM TUBE VOLTMETER KIT


The most essential tool a radio man can have, now within the reach of his pocketbook. The Heathkit VTVM is equal in quality to instruments selling for \$75.00 or more. Features 500 microamp meter, transformer power supply, 1% glass enclosed divider resistors, ceramic selector switches, 11 megohms input resistance, linear AC and DC scale, electronic AC reading RMS. Circuit uses 6SN7 in balanced bridge circuit, a 6H6 as AC rectifier and 6 x 5 as transformer power supply rectifier. Included is means of calibrating without standards. Average assembly time less than four pleasant hours and you have the most useful test instrument you will ever own. Ranges 0-3, 30, 100, 300, 1000 volts AC and DC. Ohmmeter has ranges of scale times 1, 100, 1000, 10M and 1 megohm, giving range .1 ohm to 1000 megohms. Complete with detailed instructions. Add postage for 8 lbs.



**\$24.50**

*Nothing ELSE TO BUY*
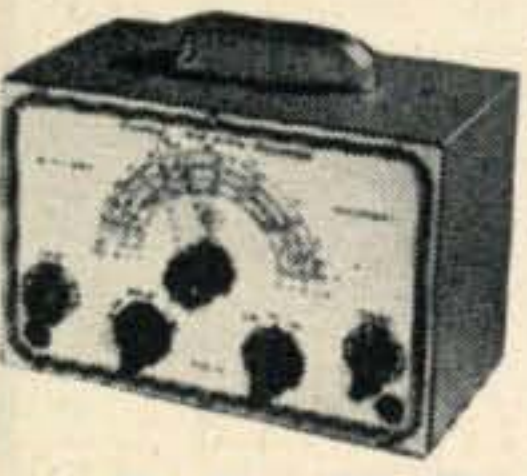
## HEATHKIT FM AND TELEVISION SWEEP GENERATOR KIT




**\$24.50**

**NOTHING ELSE TO BUY**

### THE BASIC FM AND TELEVISION SERVICE INSTRUMENT

At the lowest cost possible, anyone can now service FM and television receivers. The Heathkit sweep generator kit operates with oscilloscope and covers all necessary frequencies. A few pleasant hours assembling this kit puts any organization in position to share the profits of the FM and TV boom. Every part supplied — grey crackle cabinet, two color calibrated panel, all metal parts punched, formed and plated. 5 tubes, complete detailed instructions for assembly and use. Shipping weight 6 lbs.
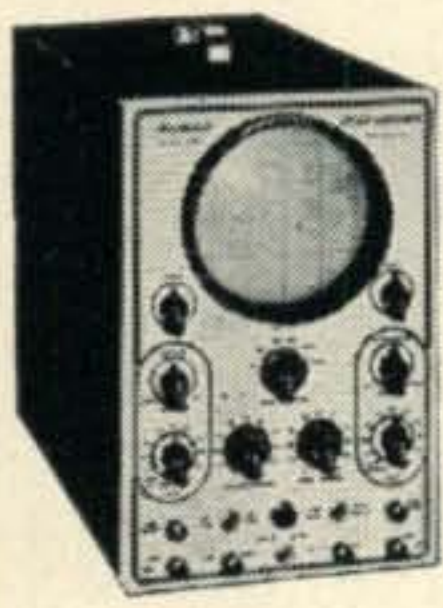
## The NEW 1948 HEATHKIT 5 INCH OSCILLOSCOPE KIT



**\$39.50**

**NOTHING ELSE TO BUY**

New improved model of the famous Heathkit Oscilloscope. Building an oscilloscope is the finest training for television and newer servicing technique and you save two-thirds the cost. All the features and quality of instruments selling for \$100.00 or more. Supplied complete with cabinet, two color panel, 5BP1 tube, 2 5Y3 tubes, 2 6SJ7 tubes and 884 sweep generator tube. Power transformer supplies 1000V negative and 350 volt positive. Sweep generator 15 cycles to 30 M. cycles. Has vertical and horizontal amplifiers. Oil filled filter condensers for long life. Complete blueprints and instructions included.



The **HEATH COMPANY**

DEPT. Q . . . BENTON HARBOR, MICHIGAN

have no way of knowing whether he passed or not. I can think of a good many thousand DX men hoping he passes the exam.

The other day, *TI2BF* dropped in to see the boss, *W2IOP*, that is, and kicked a few words around with him for awhile. No, he hasn't left Costa Rica, in fact, he is in charge of communications there for T.A.C.A. Airlines.


*W7BE* has packed up his foot locker and headed for *KH6*. Bill, while stationed in Washington for 18 months, did a good piece of DX and made *W.A.Z.*, *DXCC*, and worked *160C* with maximum input of 400 watts. He will probably be in the islands for three years, and it will be interesting to see what kind of a DX record he can pile up there.

I hope all of you, on this continent, as well as those overseas, will pardon me if I seem to get a little enthusiastic about the first World-Wide DX Contest just concluded. We of *CQ* do not want to take any particular credit, because, after all, we are just hams, but it does indicate that we did our best to follow any comments or suggestions which you fellows have made to us during the past year. Generally speaking, it adheres pretty much to the thinking of the majority of you. Since I took great pains to select a DX committee with very broad shoulders, we can stand any criticism you might choose to make.

Activity at *W6QD* during the c-w weekend was somewhat spotty. Night time conditions, putting it mildly, were lousy, as it was impossible to do any 40 meter work, due to this terrific power leak that reminded me very much of one of the old Ford spark coils used in 1920. The *XYL*, however,

seemed highly pleased when, out of a clear sky, I decided to hit the hay at a reasonably early hour. She thought at least a power leak has some merit. Anyway, I'll have you know that I really cracked down on Zone 2 again, making it doubly certain they will stay in the log. The day after the contest, a group of my neighbors were in a huddle on the sidewalk, and as I drove past, all I could hear was, "And did you have trouble on channel 2 over the week-end?" Oh, well, maybe I should have settled for a couple of 9s. I sincerely hope you fellows had a Merry Xmas and that this New Year will be a happy one . . . if DX is good I'm sure it will be. 73.

|                  | QTHs   |
|------------------|--|
| <b>CE7AP</b>     | <b>Wm. R. Shorethose, Casilla 26-D, Punta Arenas, Chile</b>                |
| <b>CWTO1</b>     | <b>Bill Spencer, c/o B.W.T., Shanghai, China</b>                           |
| <b>EA3MA</b>     | <b>Box 1312, Barcelona</b>   |
| <b>EA7AU</b>     | <b>94 Palmas, Seville</b>  |
| <b>ET3AB</b>     | <b>D. Golding Esq., No. 7, Pretoria Rd., Southsea, Hampshire, England</b>  |
| <b>HC7KD</b>     | <b>Box 340, Quito, Ecuador</b>   |
| <b>HK3CT</b>     | <b>Box 3831, Botota, Columbia</b>  |
| <b>HS1LA</b>     | <b>Via W6RRG</b>   |
| <b>MD4BPC</b>    | <b>Hargesa, British Somaliland, c/o Post Office</b>                        |
| <b>PK4DA</b>     | <b>c/o W2SNN, Yonkers, New York</b>  |
| <b>SP8XA</b>     | <b>c/o C. R. Shaffer, W3JKO, Riva, Md.</b>                                 |
| <b>TR1P</b>      | <b>AP0 231, c/o Postmaster New York</b>                                    |
| <b>VO2CJ</b>     | <b>Lt. R. Phelps, Jr., USN, Squadron VP-62, N.A.S. Patuxent River, Md.</b> |
| <b>VP2GJ</b>     | <b>Via W1FTX</b>   |
| <b>VQ4ALF</b>    | <b>Box 3024, Mombasa, Kenya Colony</b>                                     |
| <b>W6DLX/KW6</b> | <b>291 Jefferson, Vallejo, California</b>                                  |
| <b>YN1RO</b>     | <b>153 AACS, APO 3024, c/o P.M. New Orleans</b>                            |
| <b>ZC8PM</b>     | <b>Via W2AIS</b>   |
| <b>ZD1PW</b>     | <b>c/o GPO, Waterloo, Sierra Leone</b>                                     |

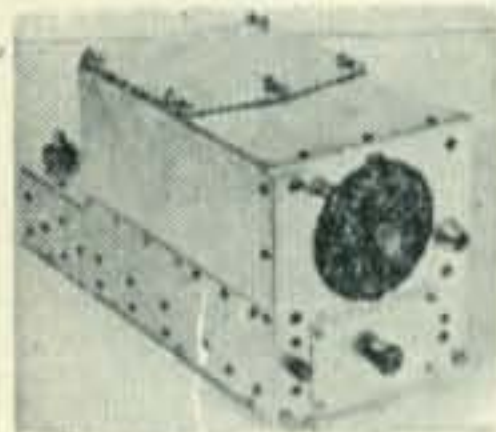

#### COMMAND RECEIVERS:

**BC-455**—6 to 9.5 MC—USED.....\$6.95  
**BC-454**—3 to 6 MC  
 USED: \$4.95 NEW: \$6.95

**TUNING CRANK**  
 for Command Rec. ....\$ .65 Ea.

**TRIPLE RECEIVER RACK**..\$1.25 Ea.

#### TRANSFORMER FOR RECEIVERS

115 Volt, 60 cycle Primary; Sec. 250-0-250 Volt, 50 MA; 6.5 Volt and 24 Volt, with AC Schematic. Price: NEW..\$2.95

#### AC POWER SUPPLY & SPEAKER

Completely wired power supply and speaker with volume control C.W. and on & off switch, housed in metal cabinet. For command receivers, with connections to plug into receiver or rack, and 110 Volt, 60 cycle line. Voltage output: 250 Volt 50 MA 6.3 V and 24 V. Price: Completely wired..\$14.95  
 Price: Kit of Parts only.....\$ 9.95



#### MOBILE DYNAMOTORS FOR RECEIVERS

P.M. Field Dynamotors, operate 6 Volt DC input; Output 240 Volt 50 MA. Normally 12-24 Volt Input; Output 500 Volt 50 MA. Size: 4" W. x 3" D. x 7 1/2" L. Price: NEW....\$1.95

#### COMMAND TRANSMITTERS AND RECEIVERS

**BC-696**—3 to 4 MC. Price: USED.....\$14.95  
**BC-457**—4 to 5.3 MC. NEW: \$8.95 USED:..... 5.95  
**BC-458**—5.3 to 7 MC. NEW: \$7.95 USED:..... 5.95  
**BC-456**—MODULATOR for Comm. Trans. USED:..... 2.50

#### TRANSFORMER FOR COMMAND TRANSMITTER

Primary 110 Volts 60 cycle; Sec. 525-0-525 Volt 250 MA; 12-12 or 24 Volt, 3 amp., 5 Volt, 3 amp. Price: NEW..\$9.95  
**DUAL TRANSMITTER RACK**—Price: NEW.....\$1.25 Ea.

#### MOTOR CONTROL RHEOSTAT

Heavy-duty, wire wound control for regulating speed of AC or DC motors, toy trains, etc. 150 Watt, 8.28 ohms, 5 amps. Price .....\$1.75

#### SELSYN TRANSMITTER AND INDICATOR

Ideal as Radio Beam position indicator for Ham, Television, or Commercial use. Complete with I-82 five-inch indicator, Autosyn Trans., 12 Volt 60 cycle Transformer, and wiring instructions. Price: NEW .....\$7.95  
 Price: I-82 Indicator only.....\$4.95

**METER SWITCH** — Battery Balancing Switch used to read battery voltage and to switch load from one battery to another. Contains Weston 2" Meter 0 to 15 DC Volts, switch DPDT—20 amp. 125 V, pilot light indicator, and pull sw. Case size: 4" x 6 1/4" x 2 3/4".

Price: NEW .....\$2.95



#### CHOKES

**CHOKE**—5-20 H—500 MA (Swinging) 5000 V. Test.....\$7.95  
**CHOKE**—8 H—500 MA—Filter—5000 V. Test.....\$8.50

#### DYNAMOTORS

| INPUT       | OUTPUT             | STOCK NO. | PRICE   |
|-------------|--------------------|-----------|---------|
| 9 V. DC     | 405 V. 95 MA       | DM 635 X  | \$ 3.95 |
| 12 V. DC    | 220 V. 100 MA      | D 402     | 3.95    |
| 12 V. DC    | 440 V. 200 MA      | D 401     | 7.95    |
| 12 V. DC    | F/SCR 522          | PE 98     | 12.95   |
| 28 V. DC    | F/SCR 522          | PE 94     | 7.95    |
| 12/24 V. DC | F/No. 19 MARK II   | P/S No. 3 | 9.50    |
| 13/26 V. DC | F/BC-645           | PE 101    | 2.95    |
| 28 V. DC    | 400 Cycle Inverter | MG-149F   | 12.95   |
| 12/24 V. DC | 500 V. 50 MA       | USA/0151  | 1.95    |
| 28 V. DC    | F/Comm. Receivers  | DM 32     | 1.95    |

**SELSYNS:** 110 Volt 60 cycle—78411—Size V.....\$5.95 Pair  
 2J1G1—110 Volt 60 cycle—Instructions .....\$3.00 Pair

#### TRANSFORMERS

Primary 110 Volt 60 cycle; 24 Volt Sec. 1 amp.....\$1.95  
 Primary 110 Volt 60 cycle; 24 Volt Sec. .5 amp..... 1.50  
 Primary 110 Volt 60 cycle; 14-14 Volt Sec. 7 1/2 or 15 amp. 4.95  
 Primary 110 Volt 60 cycle; 12 Volt Sec. 1 amp..... 1.50

#### TUNING UNITS

TU-17 or TU-25 for BC-223. NEW .....Each \$4.50  
 TU-5 for BC-191 — BC-375. NEW ..... 3.95  
 TU-7-8-9-10 or 26 for BC-191 — BC-375. NEW ..... 2.95  
 RF Unit for BC-312—1st, 2nd or 3rd..... 1.50  
 Detector Assy. BC-348-Q ..... 1.25

ADDRESS DEPT. CQ • ALL PRICES ARE F.O.B., LIMA, OHIO • 25% DEPOSIT ON C.O.D. ORDERS

**FAIR RADIO SALES** • • **132 SOUTH MAIN ST. LIMA, OHIO**



# DYNAMOTORS



| Type      | Input |          | Output |      | Radio Set | Price     |
|-----------|-------|----------|--------|------|-----------|-----------|
|           | Volts | Amps     | Volts  | Amps |           |           |
| BD 77KM   | 14    | 40       | 1000   | .350 | BC 191    | \$20.00N  |
| PE 73     | 28    | 19       | 1000   | .350 | BC 375    | \$14.00LN |
| DM 21     | 14    | 3.3      | 235    | .090 | BC 312    | \$24.50N  |
| DM 21CX   | 28    | 1.6      | 235    | .090 | BC 312    | \$ 3.45N  |
| DM 25     | 12    | 2.3      | 250    | .050 | BC 367    | \$ 3.45N  |
| DM 28R    | 28    | 1.25     | 275    | .070 | BC 348    | \$ 2.49LN |
| DM 33     | 28    | 7        | 540    | .250 | BC 456    | \$ 8.75N  |
| DM 42     | 14    | 46       | 515    | .110 | SCR 506   | \$ 5.50   |
|           |       |          | 1030   | .050 |           | \$ 6.50LN |
|           |       |          | 2/8    |      |           |           |
| PE 55     | 12    | 25       | 500    | .400 | SCR 245   | \$ 5.25LN |
| PE 86     | 28    | 1.25     | 250    | .060 | RC 36     | \$ 3.95   |
| PE 101 C  | 13/26 | 12.6/400 | 400    | .135 | SCR 515   | \$ 5.25N  |
|           |       | 6.3      | 800    | .020 |           |           |
|           |       |          | 9 AC   | 1.12 |           |           |
| BD AR 93  | 28    | 3.25     | 375    | .150 |           | \$ 4.95N  |
| 23350     | 27    | 1.75     | 285    | .075 | APN-1     | \$ 3.50N  |
| 35X045B   | 28    | 1.2      | 250    | .060 |           | \$ 3.50N  |
| ZA .0515  | 12/24 | 4/2      | 500    | .050 |           | \$ 3.95N  |
| B-19 pack | 12    | 9.4      | 275    | .110 | Mark 11   | \$ 9.95N  |
|           |       |          | 500    | .050 |           | \$ 14.95N |
| D-104     | 12    |          | 225    | .100 |           | \$ 8.95N  |
|           |       |          | 400    | .200 |           |           |
| DA-3A*    | 28    | 10       | 300    | .260 | SCR 522   | \$ 8.95N  |
|           |       |          | 150    | .010 |           |           |
|           |       |          | 14.5   | 5    |           |           |
| #5053     | 28    | 1.4      | 250    | .060 | APN-1     | \$ 3.95N  |
| DA-7A     | 26.5  |          | 1100   | .400 | TA-2J     | \$25.00N  |
| CWD-21AAX | 13    | 12.6     | 400    | .135 |           | \$17.50N  |
|           | 26    | 6.3      | 800    | .020 |           |           |
|           |       |          | 9      | 1.12 |           |           |

\*For PE 98 Less Filter Box  
N—New LN—Like New

SCR-610 11-10 METER PORTABLE/MOBILE RIG  
SCR 610 portable transmitter-receiver, 27 to 38.9 mc, crystal controlled, using FM for efficient operation. Unit consists of Xmtr-rcvr BC 659 and power supply PE 97 . . . operating from 6 or 12 vdc. Slightly used, excellent condition. Less Xtals, Antenna or handset .....**\$25.00**

### XMTR TUNING UNITS

For BC 610: TU 47 (2-2.5mc); TU 48 (2.53 mc); TU 53 (8-12 mc). Each.....**\$1.75**  
For BC 223AX: TU 17 (2-3 mc); TU 18 (3-4.5 mc). Each .....**\$1.95**  
6-Section Ceramic Stack: 10-460 mmf, for Collins Art-13 .....**\$ .69**

### ROTARY BEAM COMMUTATOR

6 Slip rings 3" dia. 1/2" wide each mounted in low loss form. Each ring brought out to pin. Inside dia. 1 1/2". New .....**\$5.45**

### INSTRUCTION MANUALS

BC 312, BC 342.....**\$1.25**  
SCR 281 .....**\$1.25** Mark II ..... **1.00**  
SX-32 ..... **1.00** SCR 508 ..... **1.00**

### VIBRATORS

TR 1210, 12 vdc, 5 pin.....**\$1.00**  
OAK V-6675, 24-32 vdc, 7 pin.....**1.00**  
Mal. Type G534C, 12 vdc, 5 pin..... **1.00**  
Mal. Type G629-C, 12 vdc, 4 pin..... **1.00**  
Radiart VR2, 6 v. DC. 6-pin special..... **1.00**  
Mfrs. quantities available.

### HEADSETS

Dynamic mike and headset combination. A high quality, efficient unit, used in B-19 tank Xmtrs. Mike and phones complete, new.....**\$2.75**  
R-15 headsets: 8000 ohms impedance, rubber cushions. Comes with 8' cord and plug PL 55. New.....**\$2.95**  
Headbands: HB-1, HB-4, HB-30. New.....**25c** each

### 30' US ARMY SIGNAL CORPS RADIO MASTS

Complete set for the erection of a full flat top antenna. Of rugged plymold construction telescoping into 3 ten-foot sections for easy sowing and transportation. A perfect set-up for getting out. Supplied complete: 2 complete masts hardware, shipping crate. Shipping wt. approx. 300 lbs. Sig. Corps 2A289-223-A. New .....**\$39.50** per set


### CONVERSION COILS FOR ARC-5 TRANSMITTERS

| M.O. Coils        | P.A. Coils        | Antenna Loading Coils | Freq. Range |
|-------------------|-------------------|-----------------------|-------------|
| <b>\$1.00</b> ea. | <b>\$1.00</b> ea. | <b>\$.85</b> ea.      |             |
| 6029              | 7247              | 6033                  | 3-4 Mc.     |
| 6030              | 9293              | 6034                  | 4-5.3 Mc.   |

CONVERSION KIT, consisting of 1-MO coil, 1-PA coil, 1-ANTENNA COIL, in any one particular frequency range .....**\$2.00**  
ARC No. 4990, variable xmtg capacitor, 22-.4—145 mmf, .05" spacing, 11 rotors. Each.....**\$1.00**  
ARC 5632 Var. Xmtg. capacitor, 29.2—117 mmf. .06" spacing, 16 rotors, worm drive: 9:1....**\$1.00**
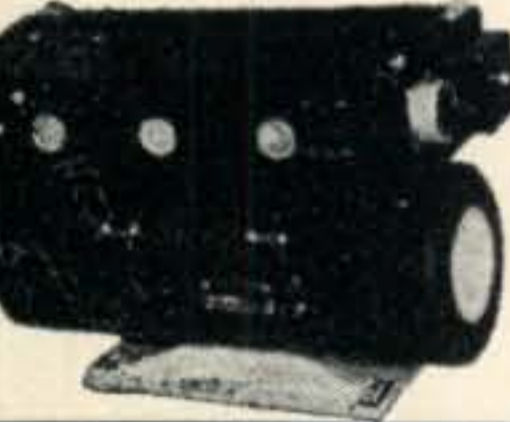
### 80 METER VFO KIT

ARC-5, Xmtr M. O. parts and circuit for that new VFO-exciter. Kit consists of the following: 1-6029 M.O. coil; 1-5632 tuning condenser; 1-4990 padding cap. 1-ARC-5 Xmtr. schematic. Complete kit .....**\$2.75**



PE 218 INVERTERS  
Input: 25128 VDC at 92 amps. Output: 115 volts at 1500 volt-amps. 380-500 cycles. New .....**\$49.95**  
Used, ex cond. ....**\$25.00**

### OIL CONDENSER

|   |                |
|---|----------------|
| 1. mfd. 10 KDVC 14F191.....                                   | <b>\$15.00</b> |
| .6 mfd. 15 KVDC, 25F585-G2.....                               | <b>8.70</b>    |
| .5 mfd. 6000 vdc .....  | <b>12.50</b>   |
| .25 mfd. 20,000 vdc .....                                     | <b>17.50</b>   |
| .0 mfd. 1000 VDC .....  | <b>1.79</b>    |
| x10 mfd. delta connected synchro-capacitor, 90v60 cycles..... | <b>4.95</b>    |
| 1 mfd. 6000 vdc, 25F509-G2.....                               | <b>6.50</b>    |

### GREAT TUBE VALUES!

|         |        |            |       |         |       |               |        |
|---------|--------|------------|-------|---------|-------|---------------|--------|
| 01-A    | \$ .45 | 5FP7       | 3.50  | 562     | 90.00 | 9004          | .47    |
| 1B24    | 4.85   | 5JP2       | 8.00  | 615     | .89   | 9006          | .47    |
| 1H5     | .55    | 5J30       | 39.50 | 703-A   | 7.00  | CEQ 72        | 1.95   |
| 1N5     | .69    | 6AC7       | 1.00  | 704-A   | .75   | EF 50         | .79    |
| 1T4     | .69    | 6C4        | .58   | 705-A   | 2.85  | F-127         | 20.00  |
| 2C21    | .69    | 6G         | 2.00  | +707-B  |       | FC 258A       |        |
| 2C22    | .69    | 6K7        | .55   |         | 20.00 | GL 562        | 165.00 |
| 21J21-A |        | 6L6GA      | 1.00  | 714AY   | 25.00 | GL 562        | 75.00  |
|         | 25.00  | 6SC7       | .70   | 715-B   | 12.00 | FC 271        | 40.00  |
| 2J22    | 25.00  | 6SL7       | 1.00  | 720BY   | 50.00 | GL 562        |        |
| 2J26    | 25.00  | 6V6        | .79   | 720CY   | 50.00 | GL 562        | 75.00  |
| 2J27    | 25.00  | 7C4        | 1.00  | 721-A   | 3.60  | GL 623        |        |
| 2J31    | 25.00  | 7E5        | 1.00  | 723-A/B |       | GL 623        | 75.00  |
| 2J32    | 25.00  | 7E6        | .72   |         | 12.50 | GL 697        |        |
| 2J38    | 25.00  | 10Y        | .60   | 724B    | 1.75  | GL 697        | 75.00  |
| 2J39    | 25.00  | 12A6       | .35   | 725-A   | 25.00 | ML 100        |        |
| 2J55    | 25.00  | 12GP7      | 14.95 | 726-A   | 15.00 |               | 60.00  |
| 3J31    | 55.00  | 12K8Y      | .65   | 800     | 2.25  | QK 59         | 65.00  |
| 2X2/879 | .69    | 12SF7      | .49   | 801-A   | 1.10  | QK 60         | 65.00  |
| 3A4     | .65    | 12SR7      | .72   | 804     | 9.95  | QK 61         | 65.00  |
| 3BP1    | 2.25   | 15R        | 1.40  | 815     | 2.50  | QK 62         | 65.00  |
| 3C24    | .60    | 28D7       | .75   | 836     | 1.15  | *RCA 932      |        |
| 3C30    | .70    | 30 (Spec.) | .70   | 837     | 1.95  | VR 91         | .65    |
| 3D6     | .79    | 45 (Spec.) | .59   | 843     | .59   | VR 130        | 1.25   |
| 3CP1/S1 |        | 39/44      | .49   | 860     | 15.00 | VR 135        | 1.25   |
|         | 3.50   | 35/51      | .72   | 861     | 40.00 | VR 137        | 1.25   |
| 3D21-A  | 1.50   | 227A       | 3.85  | 874     | 1.95  | VU 120        | 1.00   |
| 3DP1    | 2.25   | 225        | 8.80  | 876     | 4.95  | VU 134        | 1.00   |
| 3EP1    | 2.95   | 268-A      | 20.00 | 1005    | .35   | WL 532        | 4.75   |
| 3FP7    | 1.20   | 355-A      | 19.50 | 1619    | .21   | WN 150        | 3.00   |
| 3GP1    | 3.50   | 417A       | 25.00 | 1624    | .85   | WT 260        | 5.00   |
| 3Q5     | .79    | 530        | 90.00 | 1629    | .35   | +with cavity: |        |
| 5BP1    | 1.20   | 531        | 45.00 | 1961    | 5.00  | Cavity only   |        |
| 5BP4    | 4.95   | 532        | 3.95  | 8012    | 3.95  | 5.00          |        |
| 5CP1    | 3.75   | 559        | 4.00  | 9002    | .65   | *Photocell    |        |

**131-Q COMMUNICATIONS EQUIPMENT CO. PHONE DI-9-4124**  
LIBERTY ST. ALL MERCHANDISE GUARANTEED. Mail orders promptly filled. Rated Concerns Send P.O.  
NEW YORK 7, Manufacturers' Quantities In Stock  
N. Y. Rated Concerns Send P.O.  
Send Money Orders or Check. Only Shipping charges sent C. O. D. **"COMSUPO"**

## KEY CLICKS

In the article "Near Grazing Incidence Reflection at 144 Mc," December, 1948, page 36, the third paragraph should read: "Isopleths have been drawn to show the *vertical* variation in the refractive index." It is obvious from *Fig. 2* that the ordinate scale is in altitude and thus, the isopleths show a cross-section of the lower atmosphere in terms of refractive index.

In response to many inquiries it should be pointed out that the pilot lights used as band indicators on the Gold-Plated Special described in October *CQ* are a stock Drake Manufacturing item, model number 5,  $1\frac{1}{32}$ " jewel pilots with amber coloring. In the parts list the audio-frequency oscillator transformer used with the 12AU7 audio oscillator was unmarked. It should be a midget interstage a-f transformer.

## V.H.F. — U.H.F.

(from page 50)

49.6 mc, but still seemed to be inside the 6-meter skip.

*Nov. 19 and Nov. 20*—Conditions appeared unsettled, though trans-continental reached 46.5 mc for over several hours. HC2OT reportedly worked into W5.

*Nov. 21*—Honors belong to HC2OT for working W5AJG, W8CMS, W8MVG and W8NQG. He was also heard by W9ALU. Signals were in from 0950 until 1055 EST. Trans-continental

MUF did not exceed 45.0 mc.

*Nov. 22*—Tremendous signals were heard from Europe between 40.0 and 46.0 from 0915 until 1130 EST, but no 6-meter signals are reported to date of writing.

### What has the Moon to do with it?

Recently an idea has been circulating around that long-range 2-meter DX openings could be predicted according to the phases of the moon. The original suggestion was made by responsible amateurs after establishing a *prima facie* correlation. Since this is quite an intriguing subject, our propagation expert, Perry Ferrell, has reviewed the scientific literature and written the following analysis.

"In the first place, the moon does not produce a sizable tide in our atmosphere at sea level. Nor can the so-called F-region ionospheric tide be correlated with 2-meter DX.

"Getting at the root of the problem was quite simple. As you may well imagine, our Weather Bureau people are quite interested in the lunar effects, since if it affected 2-meter DX, it must also affect the weather. While we may not have many concrete 2-meter observations, we certainly have plenty of weather records. An exhaustive examination of the barometric readings at Batavia was made by J. Bartels in the late twenties. To all appearances no correlation existed. Bartels was, of course, searching for some change in the pressure between the time of the new moon and the first quarter, or between the full moon and the last quarter. Theory indicated that the gravitational field of the moon would slightly pull out

# NEW YEAR SPECIALS

CD-501A CABLE for PE 103A—BC 654A.....NEW \$1.95

HS-30 HEADSET complete with matching transformer, 6 ft. cord, and PL-55.....BRAND NEW \$1.95

HS-30 HEADSET .....NEW .95

HAND SWITCH—SW 141T with extension cord CD-318B, PL 68, Throat Mike plug.....NEW \$0.29

ANTENNA KNIFE SWITCH SPDT—Cutler Hammer.....NEW .49

SURPLUS RADIO CONVERSION MANUAL, 115 pages of circuits, etc. ....POSTPAID 2.50

ANTENNA AN-160—2000-6000 kc, 9 insulators and jumpers, 100 ft. long .....NEW 1.00

ARB RECEIVER 195-9050 KC. 28VDC.—COMPLETE with Manual .....NEW \$44.95

HS-23 HEADSET .....NEW \$3.25.....USED \$0.69

HS-33 HEADSET .....USED .89

HEADSET ADAPTER MC385D High to Low Impedance.. .35

EXTENSION CORD—CD 307A with PL 55 and JK 26 .....NEW .49

MOTOROLA Control Head .....NEW 2.50

### IDEAL MOBILE POWER SUPPLY

PE 237—Heavy duty vibrator power supply, 6, 12 or 24v input. 525v, 95 ma; 105v, 42 ma; 6.5v, 2 amp; 6v, 500 ma; 1.3v, 450 ma; small supply 100v, 17 ma; 1.35-450 ma with tubes, shock mounted.....BRAND NEW \$29.50

K-7 GUN MOUNT ASSEMBLY, ideal mount for beam antenna, cable control.....NEW \$5.95

50 Ft. RG34U with connector.....NEW 2.95

250 Ft. PHOSPHOR BRONZE stranded transmitting antenna wire .....NEW 3.95

BC-1306 SMALL COMPACT TRANSMITTER, 3800-6500 KC, 3A4, 2E22, less cover. Can be used with PE 237, GN58.....NEW \$9.95

T-17 MIKE .....NEW \$1.50.....USED \$0.75

SCR-274 REMOTE TUNING HEAD, 3 crank.....1.00

DYNAMIC HEADSET and MIKE, P.O. Mark 11.....NEW 1.95

MN 26 RADIO COMPASS RECEIVER, tubes 15—1500 KC .....USED 18.95

BC-348 MOUNTING BASE .....POSTPAID \$2.50

BC-348 OUTLET PLUG .....POSTPAID .80

BC-348 MNTG. BASE & OUTLET PLUG.....POSTPAID 3.00

BC-224 RECEIVER, 12 V.D.C. Input, Excellent condition.\$79.50

### TUBE SPECIALS

5BP1 .....\$1.15

5BP4 .....2.50

5CP1 .....2.50

872A .....1.00

2X2 ......75

75TL .....2.50

250TH .....\$17.50

304TL .....90

316A .....79

807 .....1.25

1616 .....1.00

VT-127A .....2.95

THROAT MIKE.....\$0.50

JOHNSON Variable Capacitor 250 F20 .....NEW 1.95

CRANK for 274N RECEIVERS .....60

I-82 SELSYN INDICATOR—5"—360° scale, Good condition 2.95

1st, 2nd, 3rd I.F. from SCR 522, 12,000 kc \$0.35; 3 for \$1.00

2nd & 4th I.F. from BC 348, 930 kc. .... .35; 3 for 1.00

I.F. Transformer from SCR 300..... .35; 3 for 1.00

12 In. CERAMIC INSULATORS, 1 in. Diam.....NEW \$0.25

12 In. CERAMIC SPACER.....NEW .20

T-32 DESK MIKE.....NEW \$3.50.....USED 1.95

OVERLOAD RELAY—Potter Brumfield, 10 ma. 5,000 ohm D.C. trip; 115v A.C. 60 cy. reset.....NEW 3.95

### TRANSFORMERS

5v at 190 amperes 115 v, 60 cycle, Input.....USED \$12.95

200-0-200 at 60 ma; 6.3v 3 amps, output, 115 volt, 60 cycle input .....NEW 2.50

100 watt Class B modulation transformer P.O. BC 375 .....NEW 2.95

SOUND POWERED CHEST SET .....NEW \$5.95

CRY TUNING UNIT 2.3 to 4.2 M.C., ideal M.O., P.A. and antenna tuning unit for mobile 70-80 meters.....NEW 7.50

5" P.M. COMPARTMENT SPEAKER, 25 watts 50-6000 ohms, Waterproof, Used, Excellent.....8.95

ROTATING ANTENNA RC-224 for 10 cm. parabola. Complete with 2—28 V.D.C. motors. Easily converted to 115 V.A.C. for any beam. Approx. 1 RPM.—Conversion instructions included. Shipping weight 200 lbs. Good Condition.....\$24.50

TERMS: F.O.B. Pasadena, unless postpaid. 25% deposit on all C.O.D. orders.

1060-2 NO. ALLEN AVENUE PHOTOCON SALES PASADENA 7, CALIFORNIA

### STORAGE and DRY BATTERIES

**EVEREADY Hevi-Duty Minimax BA43 p/o**  
SCR284 90/45 & 1 1/2 V for Recvr & Xmtr use  
w/octal socket & handle 2 3/4 x 4 3/4 x 6 1/4",  
7.3 lbs. metal case triple sid pkg Late '47  
date ..... Ea \$1.39  
2 for \$2.49; 10 for ..... \$10.00  
BR18/BB52/5oz/36V S'Bat \$1.49; 8 for \$10  
BURGESS 3V F2BP/late '47 date 5 for \$1  
BB54/2V 27 amp WILLARD S'Bat...1.98  
WILLARD 4V/40AH/TBY S'Bat...5.95  
BB206U/2V 11AH WILLARD S'Bat...1.89  
WILLARD 6V/25AH/7 1/2 L. 2 1/2 W. 6 1/2 H.  
3.49  
BAT'Y ACID (R.Exp only) 1 pt... .59;  
2 pts... .98

### RADIO, RADAR SETS



BC457 Xmtr AS IS Less  
Tubes ..... \$3.49  
BC456 Modulator AS IS Less  
Tubes ..... 1.49  
BC456 Modul w/Tubes&Dyn  
Good Used ..... 4.98  
BC375 or BC191Xmtr, AS IS less Tubes  
& TU ..... 7.95  
BC375 Good Used w/tubes & 1 TU 12.95  
Collins ART13 Sp Amp, less tubes 4.50  
Same w/CLIPPER KIT, tubes, data,  
NEW ..... 8.25  
TA12 Xmtr BENDIX 40W used LN\* 29.95  
BC1162&3 p/oRC150, 150-210Mc w/tubes  
NEW ..... 25.95  
BC1206 Setchel Carlson BattyRcvr 200-  
400Kc Good Used w/tubes (5) SPE-  
CIAL ..... 3.95  
GIBSON GIRL XMITTER ..... 4.95  
USN ABF/SCR695 Rcvr&Equip LN\* 9.95  
BC1066 UHF Batty Rcvr NEW.... 9.95  
BCI-196 SigGen UHF Bat NEW... 5.95  
BC906 p/oIE46 Fq Mtr & Monitor  
NEW ..... 29.95  
BC1073 Wave Mtr. 150-210Mc Used.10.95  
APS13 Rcvr Xmtr, less tubes LN\* 6.95  
BC433/MN26 Radio Compass Receiver  
Used ..... 21.95  
X Band WAVEMETER 30CM  
Maguire ..... 16.95  
723AB OSC MTG & Transition to Two  
type N coaxial fittings (BG9U etc) 4.95  
723AB Osc Mtg & adj Cavity & Coax  
term ..... 3.95  
PARALLEL TUNABLE COAX CAVITY  
w/adj hat 300-400Mc LN\* ..... 4.95  
Audio Band Pass Filters 60, 90 or 150  
cyc 20DB cutoff HIQ CSD \$2.25 ea.  
3/4.95  
UTC Band Pass Filters 854, 1024, 1250  
cycles .....ea. \$1.95, 3 for \$4.50  
Pulse Xformer H&V BTO, GE, Ray-  
theon, UTAH, specify ..... 1.49

### BASIC ALL-ELECTRONIC VTVM KIT

An ultra-sensitive tester; similar to RCA  
VoltOhmyst Jr. Includes PRECISION res-  
istors. 4"Sq GE 200microamp meter  
(reads 2-10-30-100-1000VDC; 10-30-100-  
300-1000 VDC; 1000/10000/100000/meg/  
10megohms). 11megohm input resistance.  
Full data & schematic. Less case..\$19.95

### AMPLIFIER KITS



**Biggest Amplifier Kit Buys**  
—Never Before at these Low  
Prices!!

**HIGH FIDELITY**—A Hi-Fi circuit with  
perfect linear response, phase inverter &  
full tube complement featuring 2-2A3  
PP output, 6SJ7 and 6SN7. All parts,  
tubes, controls, diagram & remarkable  
RCA Audio Amplif Chassis described be-  
low. Less Output Xfmr. **THIS IS A  
TRULY GREAT BARGAIN AT \$14.95**

**17.5 WATT AMPLIFIER KIT**—Similar  
above with all major components except  
2-1619/6L6 delivering 17.5 Watts.

**14 WATT AMPLIFIER KIT** — Similar  
above except 2-6V6GT delivering 14  
Watts. 17.5 or 14 Watt Kit, less output  
Xfmr, ONLY .....\$12.95

**RCA AUDIO AMPLIFIER CHASSIS for  
AMPLIFIER KITS** above. Heavy duty  
porcelain chassis. Gray rustproofed  
7 1/2x12 1/4x2 1/4". 9 Amphenol sockets incl.  
6 octal, 3 inpts, cutout for pwr transf  
& choke. Chassis marked for 2mic, Vol,  
Tone, Fuse, Tubes (7). Complete with  
8FP triple section Electrolytics.



### KIT 866A's & Xformer



in 115VAC/50-60cy. Output  
2.5VCT/10 Amps 10KV insul  
w/JOHNSON sockets &  
TUBES. SPECIAL.....\$5.95  
GE872A's & Xfmr 12.5KV  
insul & sockets. ....\$12.95

### TUBE SPECIALS! JAN & STANDARD

6C4, 12A6, VR92.....\$ .23  
954, 956, 957 ..... .33  
10 for...\$2.98; 10 for...25.00  
388, 955, 1625, 9001, 9003, 9006.... .40  
2X2, 6H6, 6H6GT, 6SA7GT,  
7C4/1203A ..... .49  
1LN5, 1P5GT, 6AC7, 6K6GT, 6SH7,  
6SN7GT, 6V6GT, 12SG7, 24G/3C24, 826,  
1613/6F6X, 2050 ..... .69  
2C40/446A, 6K5GT, 6L7, 6SL7..... .75  
6AB7/1853, 6AK5, 211C, 215A, 866jr .89  
REL36 ACORN sim 6J4 gnd grid.. .96  
5T4, 6B4G, 807, 816..... 1.15  
3BP1, 5FP7, 9JP12..... 1.49  
9LP7, 710A/8011 ..... 2.69  
G.E. GL434A similar 7C29/1KW... 7.95  
120P7 GE Magnetic defl TELEVISION  
Crt & data. Special \$12.95; 2 for \$25.00;  
10 for .....\$115.00



**WRITE FOR COMPLETE TUBE LIST**  
Send "TAB" all inquiries—Quantity  
Prices.

**BASIC FOTOFASH KIT**—Complete Pwr  
Supply incl cndrs, tubes, xfms, circ  
diag, all instructions & FOTOFASH lamp  
& reflector. For 115VAC. Only...\$29.95  
**STUDIO KIT**—Famed Air Corps 1503  
Set for 115VAC or battery w/2 lamps &  
refls. ....\$53.95  
**FOTOFASH** Cndrs 8mfGE660VAC/3000  
DC intermitnt 4/11.95; 16mf/660AC/3000  
DC 7.95; 15mf/330AC/2000DC 4.50; 25mf/  
330AC 7.95; 16mmPAN50film GSAP cam  
54 rolls 5.49; 16MMPANfilm GSAP 10  
rolls 1.49.

**Antenna AN-30 Telescopic  
Whip COLLAPSES 12" to 9 ft**  
New O'Seas pkgd ea.....\$1.49;  
2 for 2.49.  
Antenna AT5/ARR1, AT1/APN2  
30cm/12" lg w/COAX conctn w/  
watprf gasket & flange for mo-  
bile mtg ea. 98c; w/PL259 \$1.24  
Antenna AN130B Spring Swiveled  
Whip END LOADED 33" lg  
ea. 1.25; 2 for ..... 1.98  
Antenna P108/LU3 12cm lg w/  
Coax fitting, each..... 1.98  
Antenna AS23/APwcoax ftg.2.98  
Antenna MS49-54, 18 ft whip 3.98

**HIPOWER VAR ANT NETWK 1001A**—  
1 KW RF New 1.5 to 7 mcs convertible  
to HiFreqs. PiNetwk adjustable IN &  
OUTpt Csd 15x15x23" rackMtg Ribbon  
coil & 250 mmf/7000V cndsr RFmtr,  
insltres Tech Manual. Will match most  
ants. Brand new, ready to use...\$12.95  
Same, coil req's recementing ..... 9.95  
Same, broken coil, oth'wise OK... 8.95  
**Const V'Regul NEW RAYTHEON** in 95-  
130V 60cy outpt 115V 60Watt Csd \$10.95  
**RAYTHEON** in 198-242V/50-60 cy outpt  
220V/500W 1/2% regltn Rack Mtg...\$36.00  
**SOLA const V'Reg** USN csd in 95-190V/  
50cy outl 25-220V2K/17.4A Const Duty  
LN .....\$130.00  
Same NEW USN cost \$369, Only \$162.

**BLOWERS** — 100CFM/28VACDC \$4.95;  
100-CFM/12VACDC \$4.95; 250CFM/28V  
ACDC & Xfmr115VAC \$10.95; 40CFM/  
28VACDC4500'/min veloc \$3.25; Blower  
Xfmr 12 or 28V—115V AC.....\$1.69  
**XTAL DIODES and THER-**  
**MISTORS—VARISTOR—1N34**  
\$1.08; 2/\$2.10; 10/\$9.85; 1N21,  
21A, 22, 23, 23A ea. \$1; 12/  
\$10; 1N21B, 1N26 \$2 @ 10 for  
\$17.50; 1N35 Dual-Diode \$2.29;  
D168391 Therm Compensator \$2;  
3/\$5; D170396 HF pwr meas  
90c; 3/\$2.50; 1C Bulb Time  
Delay 90c; 3/\$2.50; VARISTOR CW20259  
Type 38C .....\$2.98

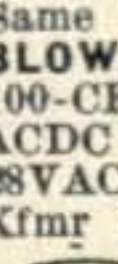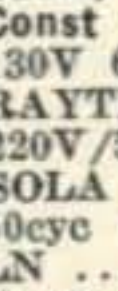

Delay 90c; 3/\$2.50; VARISTOR CW20259  
Type 38C .....\$2.98

### PRECISION RESISTORS

Write Qty Prices. We ship types in stock.  
0.116 to 95000 ohms, ea. 30c; 10 for \$2.50;  
100000 to 950000 ohms, ea. 40c; 10 for \$3.50;  
1 Meg. to 20 Megs, ea. 75c; 10 for....\$6.50  
Vacuum Prec Resistors HiVolts .12, .25, .6,  
.75, .83, .99, 1, 1.5, 2, 3, 3.75 megohms 1/2%  
accy SPECIAL \$1; 10 for.....\$7.50  
Vacuum 12 meg 10KV9W \$1.35; 10/  
\$10. MVZ8/20W 30 Meg 25KV \$1.98;  
6/\$10. MFB105/1 Meg 1/2% accy JANR  
29 \$1.98; 6/\$10. Type 2/20 meg JANR  
29/20KV 1/2% accy .....\$29.95  
**IRC ATTENUATORS**—100000 ohms 20  
pos \$2.98; 250000 ohms 20 pos.....\$4.98

### POPULAR METER BUYS!



200 microamp DC GE 4" sq.  
5 scales AC&DCV & ohms  
Red & Black K.E. pointer  
NEW .....\$7.95

| Range                          | Description                 | Each   |
|--------------------------------|-----------------------------|--------|
| 5 Ma                           | Tuning GE 2 1/2" B'Csd      | \$1.49 |
| 1 Ma                           | DeJur 2 1/2" Bklt Csd       | 3.95   |
| 25&2.5 Ma                      | GE Galvnmtr zero ctr        | 3.95   |
| 1 Amp                          | RF 2 1/2" GE Bklt Csd       | 3.95   |
| 5or9Amps                       | RF 2 1/2" GE/Wstg. B'Csd    | 3.49   |
| 750 Ma                         | RF 2 1/2" Csd extCpl Wstn   | 3.49   |
| 15 Amp                         | DC 2 1/2" Csd Hoyt          | 2.95   |
| 240 Amp                        | DC 50 MV mvt 2 1/2" B'csd   | 2.49   |
| 30 Volt                        | DC AN 2 1/2" B'Csd Wstg     | 2.49   |
| 10,000 V                       | DC 1000 ohms/V 3 1/2" B'C   | 12.95  |
| 150 Volt                       | AC 25-125cyc 2 1/2" Wstg&GE | 3.95   |
| 7.5 Volt                       | AC 3 1/2" BkltSq. RA35 Wstg | 4.49   |
| 15 Volt                        | AC 3 1/2" BkltSq. Wstn476   | 4.95   |
| 1-82 360°                      | Bendix Autosyn              | 4.95   |
| TestLeads&Clips 8ftinsltd      | 30A 49c; 3/                 | 1.20   |
| TestLeads&RedBlack Insul Prods |                             |        |
| HiQual                         |                             | 49c    |

### Complete TV Voltage Supply Kits

**High, Low & Filament Voltages**—Featur-  
ing Herm Sld W.E. USN oil filled  
XFMR Inputs 105, 115, 125 VAC 50-425  
cps Outputs 600 VCT or 300VCT/175Ma  
and 6.3V/10A, 5V/8A, 2.5/3A, 5V/3A.  
H.V. insulated.  
**10000V, 300VDC & ALL Filaments Supply**  
**Kit**—Above Xfmr & 2-3B24 Doubler-Rect  
& 5U4G rect. & All cndrs, sockets, choke  
& data "TAB" Special .....\$29.95  
**5000V, 300VDC & ALL Filaments KIT**—  
Same Xfmr plus 5U4G&3B24 rectifiers,  
cndrs, choke & sockets, diagram..\$21.95  
**Transformer Only** ..... 16.95

### High Accuracy

### CRYSTAL FREQUENCY STANDARDS

|                   |                    |
|-------------------|--------------------|
| 100Kc .....\$5.98 | 5000Kc .....\$3.98 |
| 200Kc ..... 3.98  | 4700Kc ..... .98   |
| 500Kc .....12.98  | 81.95Kc ..... 1.98 |
| 1000Kc ..... 4.49 |                    |

### CRYSTALS Mounted FT243 exacting S.C.

| Specs  |                        |
|--------|------------------------|
| 3525Kc | 4190Kc 5235Kc          |
| 3735Kc | 4780Kc 5485Kc          |
| 3980Kc | 5030Kc ea. 98c, 3/\$2. |

Write for other frequencies.  
**CRYSTALS Mounted htr Ovens HiAccy**  
Stability—5010, 5025, 5055Kc, ea. \$14.98

### SYNCHRO-DIFFERENTIALS TYPE 5/ 115V/60cy .....\$7.95

### SYNCHRONOUS REPEATER TYPE II, 115V/60cy Bronze Units, pr...20.00

### AUTOSYNS TYPE 5/50V/60cy, pr. 9.95

### SYNCHRO DIFFERENTIAL TYPE 5/50V ..... 4.95

**AUTOSYNS AY1&5/28V-400cy** can  
be used 24V/60cy & instructions  
TWO for ..... 4.50  
New Type 5 BENDIX Autosyn 115  
VAC/60cy O'Seas pkgd Var Mfrs  
4 1/2x3 1/4" 5 lbs. per PAIR.....\$12.95

### TELEVISION COMPONENTS

A. V'Outpt Xfmr sim RCA204T2...\$2.98  
B. Utah 9318 H'BlkgOsc Xfmr H'sld 1.49  
C. UTC88662 V'BlkgOsc Xfmr H'sld 1.29  
D. Erie HiV Cndsr 500mmf 10KV... .40  
D. Jeffers HiV Cndsr 500mmf/20KV .75  
E. Yoke MagnDeflec simRCA201D1.. 4.59  
F. FocusCoil for MagnFocKinescps.. 3.95  
G. HiV Flybak H'OutXFMRsim  
RCA211T1 ..... 5.49

\$3. Min. FOB N. Y. C.  
Add Post. & 25% deposit.  
Money Back Guarantee.  
Return Mdse. Prepaid.

"TAB"

Dept. 1Q, 6 Church St.,  
New York 6, N. Y., U.S.A.  
WORTH 2-7230

"TAB"

WRITE FOR  
"TABOGRAM"  
SPECIALS

the earth's atmosphere and this would be reflected as a change in the over-all atmospheric pressure at sea level. Actually, the pressure fluctuation was so small that it was completely swamped in the everyday hourly air mass movements across the station. However, to make a long story short, this pressure fluctuation was finally detected and under these circumstances it should be classed as a triumph for statistical methods.

"It was shown that the average lunar pressure wave at the equator was only plus or minus 0.01 mm (normal pressure 760.0 mm at 0° C.). This corresponds to a so-called adiabatic heating of 0.015° C. between the first quarter and full moon. If we extrapolate this to the latitude of Washington, D. C. it means that the air temperature increases 0.02° F when the moon is full and right overhead.

"Naturally, this in itself is far too small to have any effect on 2-meter DX by a factor of several hundred. Any other lunar effects at sea level are unknown, and since 2-meter DX depends strictly upon weather conditions it would indeed be strange if the Weather Bureau had not already discovered them."

That seems to solve that.

#### 144-mc Notes

We have received several requests that we double check the distance record for the 144-mc band. Some operators have wondered if the span between W2TDW/4 (Clingman's Dome, Tenn.) and W2RH (Port Chester, N. Y.) was not more than equal to the record between WØWGZ (Grimell, Iowa) and W3GV (Erie, Pa.).

#### 144-Mc Honor Roll

|       |    | States | Dist. |    |    | States | Dist. |
|-------|----|--------|-------|----|----|--------|-------|
| W8UKS | 15 | 6      | W9LWE | 8  | 5  |        |       |
| W8WJC | 14 | 6      | W1CTW | 7S | 2D |        |       |
| W8WXV | 13 | 5      | W9IPO | 8  | 5  |        |       |
| WØNFM | 12 | 4      | W3GV  | 8  | 5  |        |       |
| W1JFF | 12 | 4      | W4FBJ | 7  | 5  |        |       |
| W1IZY | 12 | 4      | W8PYY | 7  | 4  |        |       |
| W1PIV | 12 | 4      | W9PK  | 7  | 4  |        |       |
| W3KUX | 12 | 5      | WØBZE | 6  | 3  |        |       |
| W3RUE | 11 | 5      | WØGOK | 6  | 3  |        |       |
| W9BBU | 11 | 5      | W8DRZ | 5  | 4  |        |       |
| W3GKP | 10 | 5      | WØWG  | 5  | 4  |        |       |
| WØIFB | 9  | 6      | WØRNC | 4  | 2  |        |       |
| W9AB  | 9  | 5      | WØKPQ | 3  | 2  |        |       |
| W9ZHB | 9  | 4      | WØDDX | 3  | 2  |        |       |
| W2JPA | 9  | 4      | WØMZH | 3  | 2  |        |       |
| W1CTW | 9  | 3      | WØZJB | 1  | 2  |        |       |

Based upon geographic coordinates the record is 649.4 miles between WØWGZ and W3GV, while the distance from Clingman's Dome, Tenn., falls slightly short of this, equalling only 614.9 miles.

WØBZE has moved near WØRSI and has a complete rebuilding job to do before he will be back on the air. Smitty adds that Arnold, WØWGZ, is now working for Collins Radio, having just graduated from Iowa State College with a B. S. in electrical engineering.

Here's a little inside information on a recent 2-meter expedition which took place from Wayah Bald Mt. near Franklin, N. C., on Oct. 16-17. Using a 4-element horizontal beam and 15 watts of power to a 522, W4KHL worked W4KMK, Greenville, S. C.; W4FQI, Oak Ridge, Tenn.; W4LNB and W4ENL in Chattanooga, Tenn.; and heard W4NVW of the same city. In Atlanta, Ga., the stations worked were: W4LMF, LSX,

**CQ**  
**BINDERS**  
**\$2<sup>00</sup>**

Here at last is a binder using modern postwar materials at prewar prices. Designed to provide instantaneous reference to your monthly copies of CQ. An unusually fine library finish that will stand up under constant use.

- Rich red Dupont Fabricord—stainproof and washable
- Backbone gold stamped with CQ and year
- Any year specified in order will be gold stamped
- Center channel to keep magazines fastened in position
- \$2.00 each postpaid. Foreign orders add 25c per binder

CQ—Radio Magazines, Inc.  
 342 MADISON AVE., New York 17, N. Y.

Enclosed find \$..... for..... Binders

Name..... Call.....

Address.....

City..... Zone..... State.....

Year Wanted  1945  1946  1947  1948  1949 Stamping: CQ  Plain

# THE HAMS' SUPER MARKET




## TELRAD SECONDARY FREQ. STANDARD

Complete self contained, dual xtal, multivibrator and harmonic amplifier. Calibrates with WWV or broadcast stations for high accuracy. 100 kc - 45,000 kc. 1000-100-10 kc check points. A MUST for the operating desk.....**ONLY \$29.50**
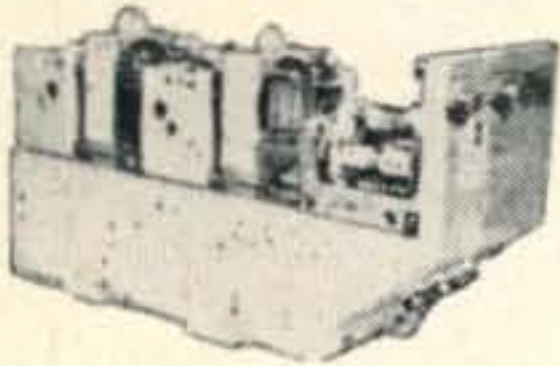
## 1068A/1161A HIGH FREQ. RECEIVER

14 tube high gain, 2 rf stages, 5 stages IF, 4 mc IF band suitable for TV, internal AC supply. Simple conversion for 2 meter use, with instructions.....**\$29.50**




## ARC/5 HIGH FREQ. TRANSMITTER

1625 xtal. 1625 mult, 832A mult, 832A final. Ideal 2 meter rig, 6 and 10. Motor turret band switch, perfect for 4 band remote operation. Nothing finer for mobile use and superior to 522. 6x12x8. 6 lbs., with tubes.....**ONLY \$17.50**
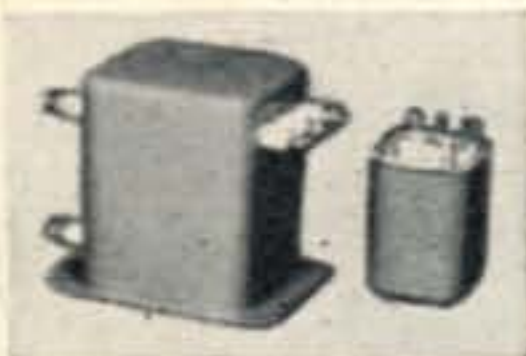
## ARC/5 RECEIVER

Get this popular set while it is still available. Complete with 6 tubes, dynamotor, in original factory cartons, less front dial, a GOLD MINE of beautiful parts. 3-6 mc or 6-9 mc. **ONLY \$3.50!** With dial 6-9 mc.....**\$6.95**



## ART13 MODULATION SET

Will modulate 300 w, compact hypersil, herm., 2:1 ratio, 10:1 screen wdg. Class B 811, TZ49 etc. to 813 or pentodes, triodes. Guaranteed finest mod. set ever available. Complete with driver transf.....**ONLY \$ 6.50**

With RCA tubes 813 and two 811.....**ONLY 16.50**

## BC 314 RECEIVER

4 bands, 150 - 1500 kc, 2 rf stages, low freq. IF, a natural for double conversion or converter, complete with 12v dynamotor, slightly used but fine shape. **\$24.50**

## VIBRAPACK

Mallory, synchronous, requires no tube. 12v input, 260v at 80 ma out. Complete with vibrator. **\$4.95**

## BEAM MOTOR

Reversible prop, 24-35v, 3/4 rpm, with conversion sheet. ....**\$12.95**

## HIGH VOLTAGE SUPPLY KIT

Thordarson 3600 vct at 350 ma, 2 filter chokes, 2 oil condensers, 2.5 v at 10 A, sockets, resistors, etc. A beautiful 1500 vdc supply nowhere equaled. **ONLY \$29.50**

## MODULATION XFORMERS

Kenyon 225 w. audio 16,000 ct to 7,000, 5,000, 3500 ohms \$12.50; 200 w. audio PP 811 to 813 etc. \$8.50; 60 w. audio PP 807 to PP 807 etc. \$3.75; PP 6L6, 807 to 807, 829B etc.....**\$2.50**

## VARIABLE TRANSMITTER CONDENSERS

Cardwell XE240XD, split stator, 120 mmf effective, .1 gap 4000v, polished plates, List \$26.25. Our Price \$4.95.

Cardwell M0180BD, split stator, 90 mmf eff. .05 gap 1600v pk, perfect all around tank or grid condenser, List \$10.10. **ONLY \$2.25.**

Cardwell MR260BD, split stator, 130 mmf eff., .03 gap 1200v pk, \$1.50.

Cardwell neutralizer, dual 2-2.8 mmf, spacing can be

increased for lower capacity, ideal push-pull use. **ONLY 35c.**

Cardwell single 80 mmf, .08 gap \$1.25.

BUD Junior, 150 mmf .05 gap 89c

BUD Midget, 3-15 mmf, easily ganged 45c.

100 mmf midget 1" shaft 55c.

100 mmf midget, with dust cover, for stable trimmer, screw adj. 50c.

25 mmf midget, double spaced, screw adj. 50c.

## ELECTROLYTIC CONDENSERS

### SEALED CAN TYPE

|                   |                                    |
|-------------------|------------------------------------|
| 125 mf 350 wv 69c | 20-20 mf 150 wv 35c                |
| 10 mf 300 wv 33c  | 4x4 mf 400 wv 55c                  |
| 10 mf 450 wv 35c  | 30-39mf 150 wv 100-100mf 25 wv 45c |
| 2500 mf 2 wv 35c  | 2400 mf 50 wv 1.10                 |
| 30 mf 450 wv 75c  | 15 mf 150 wv 25c                   |

3690 vct at 350 ma, for that 1500 vdc supply, Thordarson 19.50

1000 vct at 220 ma, 5v at 3A, 2.5v at 5A 3.95

830 vct at 125 ma, 5v at 3A, 6.3v at 6A, 6.3v at 1A, 20v at .6A, GE 2.89

500 vct at 90 ma, 5v at 3A, 6.3v at 3A, open core 1.95

600 vct at 100 ma, 5v at 3A, 6.3v at 3A 2.75

400 vct at 40 ma, 5v at 3A, 6.3v at 3A 1.75

675 vct at 150 ma, 5v at 3A 2.00

870 vct at 250 ma, plate trans. 3.25

650 vct at 150 ma, 5v at 3A, 6.3v at 5A, 10v bias 2.95.

1300 vct 160-200 ma, 5v at 2A, 2.5 at 2 A,

2.5 at 2 A 5.75

## FILAMENT TRANSFORMERS

Thordarson, cased 2.5 vct at 19A, 10 vct at 3.25 A, 5 v at 3 A, 5 v at 3 A, 6.3 v at 1 A .....**\$4.95**

11.5 v at 11.5 A or more, for 10 v xmitting tubes GE ..... **2.95**

10 v at 5 A, for xmitting tubes..... **2.75**

6.3 v at 5 A cased..... **1.60**

2.5 v at 10 A, 10,000 v ins. cased..... **3.50**

## POWER TRANSFORMERS

# SURPLUS RADIO, INC.

44-31 Douglaston Pkway.

Douglaston, L. I., New York

Flushing 7-9173

# STAHL SEZ!

There's a Reason Why We Add Hundreds of New Names to our ever-growing list each month. See our Values!

## TRANSMITTER-RECEIVER

Navy Model ABA-1 (CG-43AAG)  
Army Model SCR-515A  
Known as the BC-645

### 450 MC—15 TUBES, Brand New

Can be easily converted for phone or CW 2-way communication. Covering the following bands: 420-450 MC ham band, 450-460MC for fixed or mobile, 460-470MC for citizens, 470-500MC television experimental. Size 10½x13½x4¾. Contains 15 tubes: 4—7F7, 4—7H7, 2—7E6, 2—6F6, 2—955, 1—WE-316A door knob.

Here is what you get:

BC-645 with 15 tubes  
Dynamotor Keyer Unit,  
CWD-12AAX  
Remote Control Unit  
CG-23ABJ  
Instruction Book

**\$12<sup>95</sup>**  
Complete

Complete set of plugs, antennas and rack mountings for control box.....**\$3.95**

## IFF EQUIPMENT

### 1293B Signal Corp Scope Unit

Consists of 5" Cathode Ray Tube and 24 Tubes 1221A Indicator consists of high & low Voltage supply—8 tubes, electric eye & Selsyn indicator 110V-60 cycle AC—can be converted into an excellent scope. Shipping weight 500 lbs. Brand New in Original Case. Special.....**\$49.50**

Prompt Delivery—25% deposit required on C.O.D. orders. Shipped F.O.B. New York.

Write Dept. CQ-1

# MICHAEL STAHL, INC.

39 Vesey Street  
New York 7, N.Y. Tel. WOrth 4-2882

KIP, LNG, and W4GMP; W4NWA in Dahlon-ge, Ga., was worked also. The receiver was a VHF-152A ahead of a BC-312. W4KHL also moved to Clingman's Dome, Tenn., but it was raining cats and dogs hence no signals were heard, and no one has reported hearing W4KHL/4. Roy, W4KHL, adds the Atlanta gang is begging for skeds and will make them with anyone interested enough to write the Atlanta Radio Club, or members just mentioned.

Bob Cook, W2JPA, has worked 9 states and 4 districts, and adds that he would like to run skeds with fellows that are west of him. W2JPA runs 100 watts with two 5-element beams, one vertical to passify the east coast and the other horizontal.

As luck would have it, the Midwest V-H-F Club of Chicago held its first annual 2-meter QSO party, on October 23-24, and conditions were perfect. Stations in four states were able to contact each other, the band sounding more alive than it had for weeks. Numerous stations outside the Chicago area had many nice contacts, so all the gang in the area are looking forward to many more of the same contests. That's one way of getting activity, for all had a good time.

Conditions in England on 145 mc were wonderful on Nov. 11-12-14, according to G5BY, due to a warm air stream from the south, which sent the temperature to 14 degrees above normal. All signals up to 190 miles were S9 and G5BY worked PAØZQ and PAØPN around 2140 GMT. Both distances being well over 400 miles, which no doubt will add to G5BY's laurels, as it is a new G-DX record on 145 mc. On Nov. 12, G5BY, heard both ON4FT and F8BY but no contact was made.

W9JMS contacted W7JRG on 50 mc and convinced W7JRG to try horizontal on 144 mc. Ken adds this isn't to let the east coast fellows down, but the seventh district is closer to the middle-west.

W9ALU, advises that his current project is the W2PAU 2-meter preamplifier described in May-August *RCA Ham Tips*, using a push-pull neutralized 6J6. Hod adds that it works wonders on any converter.

From Tulsa, Okla., W5LEI says that 2 meters is going again and that W5DFU has a new 48-element beam that not only rotates but moves up and down several wavelengths. W5DFU runs 200 watts and wants skeds with interested 2-meter parties, of course vertical polarized!

### 220-mc Notes

Cal Hadlock, W1CTW, has 7 states and 2 districts on this band. Cal is having bad luck as all the activity in W2, on 220 mc, has moved to 420 mc. Cal, W1CTW, still believes that the fellows are overlooking a good bet as he has been able to work into W2 on 220 mc, when not a thing was coming in on 2 meters. How can we put over the idea that v-h-f operation means three bands instead of two or one, this is the cry of W1CTW. Well, Cal, if the jokers that invented the SCR-522 had only included the 220-mc spectrum on the gismo, no doubt the QRM would be the same as on 144 mc-or would it? Let's hope that more of the fellows can visualize the possibilities and help to create activity for you, soon that is!!

W7QLZ says that there is no activity on 144

**OUT THEY GO!** Just received a large shipment of rotator motors at a greatly reduced cost to us. We're passing our savings onto you with this low price.



**¾ RPM, HI-TORQUE  
ELECTRIC MOTOR**

**\$2<sup>95</sup>**

Brand New Surplus!  
Guaranteed!

Gov't Cost  
**\$40**

POSTPAID  
U.S.A.

- Operates on 110V AC, 60-cycles (Requires only 12 MFD condenser).
- Reversible. Self-locking clutch. Quiet.
- With Full Instructions.
- FB for that new QUAD.
- FOR ROTATING HAM, FM, TELEVISION ANTENNAS AND MANY OTHER USES.

**ALVARADIO, Dept. Q-14**

903 S. Alvarado

Los Angeles 6, Calif.

# TURRET ASSEMBLIES

## PIONEERED BY B & W

Still Preferred by Discriminating Amateurs



WRITE FOR BULLETINS giving full details on:  
 B&W "Baby" Turrets (up to 35 watts)  
 B&W "Band Hoppers" (up to 75 watts)  
 B&W 75-watt Turrets  
 B&W 150-watt Turrets

Through the years, the Turret line, as first developed and introduced by B&W, has been improved and enlarged—and has consistently grown in popularity! If you are building a new rig or revising your present one, start by selecting the B&W Turret that offers all these advantages and more!

- Pre-assembled, pre-wired and tested at the factory. Quick to install and quicker to shift bands for you after installation.
- Select 80, 40, 20, 15, 11 or 10 meter band by the flip of a switch. (11 and 10 meter bands covered by 10 meter coil.)
- Switch design shorts unused coils—eliminating absorption effects.
- Complete assembly arranged for 3/8" hole panel mounting—provides panel control for quick, positive band switching.
- All B&W Turret types may be tuned on all bands by condensers having an effective capacity of 50 mmfd.

### BARKER & WILLIAMSON, Inc.

Dept. CQ-19 237 FAIRFIELD AVE. • UPPER DARBY, PENNA.

CQ is written "of, by and for the amateur." Subscribe now and be sure of getting the comprehensive monthly issues as soon as they are published. You can't go wrong!

**One Year.....\$3.00    Two Years.....\$5.00**

in U.S., U.S. Possessions, Canada and countries in the Pan American union. All others \$4.00 per year.



**CQ-RADIO MAGAZINES, INC.**  
**342 MADISON AVE., NEW YORK 17, N. Y.**

Enclosed find \$..... for a..... year subscription

to be sent to:                       New                       Renewal

Name..... Call.....

Address.....

City..... Zone..... State.....

mc, but lots of the gang have converted the APT-5 and APS-13 units for 420-mc operation. The Phoenix gang meet nightly at 2000 MST, with a personal gathering at the Acme Electric Store each Wednesday, led by W7KJT. The net operates on 435 mc, with simple dipoles being used at the present, but several of the gang have parabolics up, using a screen reflector. The gang in Phoenix, now active on 420 mc includes: W7KWO, W7MIV, W7KTJ, W7MIW, and W7QLZ.

## DX PREDICTIONS

(from page 41)

### East Coast to Eastern Asia

*40 meters:* Erratic opening centered around 0530 EST. Possible peak about 0630 EST, but still not to be depended upon daily. *20 meters:* Band opens suddenly around 1645 EST with readable phones. Signal strengths decrease slowly with band going out about 2130 EST. Peak conditions 1715 to 1830 EST. *10 meters:* Short opening with fairly strong signals from 1745 to 1845 EST. Active only on ionospherically quiet days.

### East Coast to East Indies

*40 meters:* Conditions depend on the extent of auroral zone absorption. Possible openings between 0545 and 0745 EST. Some improvement towards the last of the month. *20 meters:* Very weak signals at both ends of this path on the direct route. Band appears likely to open around 0830 EST depending on near end MUF. Scattered and

erratic signals may actually be heard and worked up until 1400 EST, but not to be depended upon. Possible secondary opening centered around 1800 EST. *10 meters:* During less than 40% of the entire month the band may open between 1745 and 1830 EST with fairly strong signals. The MUF is just outside the low edge of this band. Erratic conditions, at best.

### East Coast to Central South America

*40 meters:* Band opens slowly as absorption level drops down after 1815 EST. Peak conditions centered about midnight. *20 meters:* First opening 0545 EST with fair signal strengths, though these will drop into the noise level before 0830 EST. Band reopens after 1530 EST with signals building up to the peak 1930 to 2130 EST. Possibly a few scattered c-w signals from 2200 to 0315 EST the following day. *10 meters:* Band opens sharply around 0730 EST. Signals lose from 6 to 8 db during the mid-day, but build to a good peak between 1445 and 1630 EST.

## ZERO BIAS

(from page 11)

*on amateur methods. I'm looking for a little "down to earth" practicality that will keep my hobby from becoming a nuisance to myself and to my neighbors.*

*James B. Strang, W8NFR*

The above letter was written within one month after the first TV station went on the air in that metropolis. It describes a typical reaction, one

# TELEVISION INTERFERENCE

## Its Causes and Cures

A new Handbook by Radio Magazines, Inc., covering in detail the important facts of TVI. The TVI Handbook is edited to fill the pressing requirements of amateurs and other technicians confronted with the problems of TV interference, or otherwise unsatisfactory television reception. Included in its thorough treatment of causes and cures are a comprehensive set of TV screen photos depicting all types of reception, many case histories, preventative design data, and other equally pertinent facts. It is a vital publication for radiomen wherever TV is on, or about to go on the air.

**Price 50c postpaid, or order from your local dealer.**

CQ—Radio Magazine, Inc.  
342 MADISON AVE., New York 17, N. Y.

Enclosed find \$..... for..... copies of the TVI Handbook

Name.....

Address.....

City..... Zone..... State.....



that pretty well mirrors the thinking of the average amateur. And in general we are forced to agree completely with this attitude.

But what? There is much that can be done if only the gang can be made to realize it. The many published articles contain material that *does* work. Read W2GVZ's letter:

337 Hamilton Ave., Glen Rock, N.J.

Editor, CQ:

I just wrote to W2GWE to thank him for his article in June CQ re TVI, because it helped me to cure my TVI completely, and I am very grateful.

By following his instructions concerning the various stubs, plus using a 56-mc and a 70-mc wavetrap in series with the plate of the final, I eliminated TVI from a set only 100 feet from my antenna, much to our mutual delight. Radiation from the transmitter itself did not enter into the picture as my Collins 30K is very well shielded. It cost me thirty hours of effort, but it surely was worth it, and I now feel very smug.

Thanks for publishing a very helpful article on a difficult problem.

Pat Jessup, W2GVZ

Yes, this editorial is an appeal, it is a plea—try to clean up your rig; try to explain the amateurs' rights to your neighbors; help track down TV dealers, servicemen, or just plain viewers who are misrepresenting the facts—above all, don't think the cause is hopeless.

## BEGINNERS CONVERTER

(from page 27)

When the receiver is to be used in the regular manner, the converter must be disconnected from the antenna posts of the receiver and the regular receiving antenna placed on the receiver.

When the receiver dial is tuned, the main tuning dial on the converter will have to be retuned in order to receive on the same frequency. This means that the calibration on the converter will hold good for only one setting of the receiver dial. Therefore, make certain that the receiver is always tuned to the same frequency when the converter is being used.

The converter need not be turned off when changing coils, as there is no d-c voltage present on the coils.



The beginners' 6, 10 and 11-meter converter may be used on 2 meters. Operation on this band is not especially recommended, however, because the coil construction is rather critical and much experimentation may be necessary. Further, it was found that oscillator pulling could not be completely eliminated. This means that the calibration would not hold, as the frequency of the oscillator would change whenever C1 was tuned.

For those that are willing to experiment, and have the necessary equipment for experimentation, the information on coils for the 2-meter band is as follows:

*Coil A:* The coil is one turn of No. 12 wire, made the same size as the 6 and 10-11 meter coils. CA1 is 5  $\mu\mu\text{f}$ . CA2 is zero (none used). CA3 is 50  $\mu\mu\text{f}$ . (QSY to page 88)

## New PIONEER CHASSIS PUNCH

(Pat. Pending)

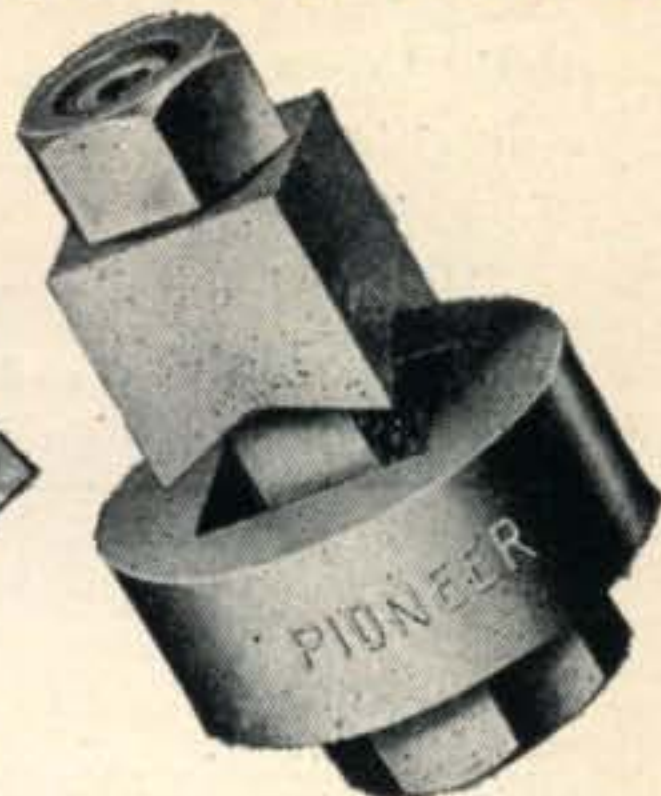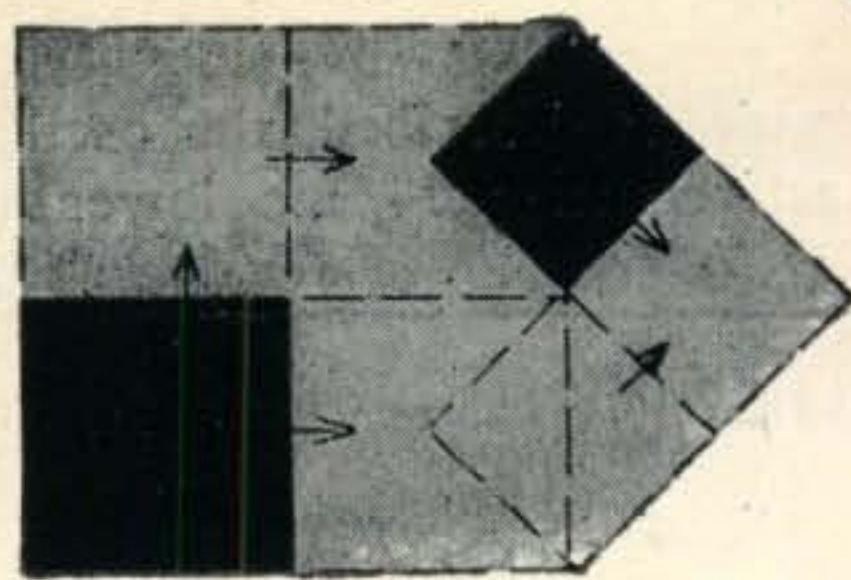

### CUTS ANY SIZE LARGER SQUARE OR ANGULAR HOLE

For Transformers, I.F.'s, Plugs, Binding Post Strips, Sockets, Etc.

Banished forever is hand hack sawing or filing of holes for hard to mount parts. Sizes to meet every need.

SIMPLE HAND WRENCH SCREW ACTION



|       | SQUARE |        |     |     | ROUND  |     |     |        |        |       |        |         |        |       |        |
|-------|--------|--------|-----|-----|--------|-----|-----|--------|--------|-------|--------|---------|--------|-------|--------|
| SIZES | 5/8    | 3/4    | 1/2 | 5/8 | 11/16  | 3/4 | 7/8 | 1      | 1 1/16 | 1 1/8 | 1 5/32 | 1 11/64 | 1 3/16 | 1 1/4 | 1 1/2  |
| NET   | \$2.95 | \$3.50 |     |     | \$1.95 |     |     | \$2.15 |        |       | \$2.30 |         |        |       | \$2.65 |

Buy it at your favorite distributor

**PIONEER**



BROACH COMPANY  
LOS ANGELES 15, CALIF.

## "B & B" MODULATOR UNIT MODEL 500

AM  
PHONE  
QUALITY  
WITH  
NB-FM.



Designed for direct coupling to the VFO or crystal socket of a conventional crystal controlled pentode or triode oscillator. You get NB-FM operation with your present rig, without expensive speech equipment. You can run your phone rig on CW ratings. Clears up most BCI troubles. Not an exciter, does not eliminate or duplicate any of your present equipment. Amateur net, complete with tubes and instructions: **\$18.95**  
See Your Distributor today, or write direct.

"B & B" Electronic Co.

1140 Shenandoah St., Los Angeles 35, Calif.

**Coil B:** The coil is a 1¼-inch long piece of No. 12 wire, connected directly across from one outside lug to the other. The tap is made at the point on this wire directly above the third lug. CB is 5 µf.

With the coils made as described, the oscillator will oscillate on a frequency 14 mc lower than the incoming signal.

## LAND OF SUNSHINE — AND YL's

(from page 28)

have a dipole strung up in the attic and get out as best they can on 40 with an ARC-5 and a BC-348.

Louise Willomitzer, W6VWR, of Arcadia, was at Carol's, too, and we all had a gratifying rag-chew. Lou, we were intrigued to learn, was formerly a New Yorker, as was Lenore (W2NAZ)—Lou being in Lenore's first radio class in AWVS. Lou is a whiz at c.w., and during the war was a Signal Corps radio operator at Governor's Island, N.Y.

Later, on Friday, we visited Ruth Mask, W6-WQK, at Glendale. Ruth and OM W6VRC have already licked their TVI and are active on 10 phone. Ruth is a registered nurse, but during the war she put her radio knowledge to good use by working for the Army as a junior engineer at the Presidio in San Francisco.

We were having such a superb time visiting the YLs we could hardly tear ourself away to take in any of the I.R.E. activities with the OM, but after missing the get-together party the evening before, on Friday we did take in the "nite of fun" at Slapsie Maxie's famous night spot on the "Strip."

### YL's Attend Convention

Saturday's dawn brought the first day of the Southwestern Division Convention. Registration at the historic Alexandria Hotel started early, and among the first of the YLs we met was Evelyn Scott, W6NZZ, of Long Beach, who was in charge of the YL activities, assisted by members of the L.A. club under the direction of President Maxine Willis, W6UHA. Evelyn and OM W6KTS run the Scott Radio Supply in Long Beach. Many of the hams attending the Convention have been Scott

customers for years, and Evelyn even remembers some who were shooed out of the store when they were youngsters with fingers itchy for a spare part or two!

Bertha Wallace, W6MA, XYL of widely known W6AM, was there early, too, for she was in charge of the YL luncheon that day.

Next among the YLs we met was Rosemary Robin, W6PJF, 6th district chairman for YLRL, who traveled all the way from Stockton with OM W6INP to attend the Convention. Rosemary is the "Lone Ranger" in Stockton, the only YL thereabouts, and has been ever since she received her ticket some time before the war. The mother of two jr. ops, she operates on 80 meters most of the time, but she likes 2 also, and is now getting set up to be on 10 phone and 40 c.w., explaining, "At heart I am really a c-w 'man'—but gosh, phone is lots of fun, too!"

Shortly after we registered, publicity chairman W6PAP gathered a group of OMs and YLs and conducted us to station KXLA to participate in Tom Regan's "Community Broadcaster" program, in an attempt to explain to the BCLs some of the mysteries of ham radio, and particularly the YL's interest in it.

By this time all the licensed YLs were togged out with gay crepe paper leis—in blue, rose, green, or yellow—with silver diamonds bearing the letters YLRL, the work of art of Clara, W6TDL, and her OM. The leis provided a colorful touch when we all gathered at Bullock's Department Store for the luncheon and fashion show, both of which were tops.


There we met many more of the YLs—including Verma Cobb, W6JOJ; of Baxter, formerly W1KTY; Wilma Pappila, W9POZ/6, hailing from Illinois; Mary Klein, W6AVF, an x-ray technician of Monterey Park, now on 10 and studying for class A; Dorothy Williams, W6QLM, a 10-meter gal from Los Angeles, and Marie Mandroian, W6-SPX, also of Los Angeles. Marie and OM W6-RLX, are on all bands with a kw rig, using a four-element beam on 10 and 20, and sixteen-element array on 2 meters. They also operate 2 and 10 mobile.

Most of the members of the Los Angeles YL

## SPECIAL VALUES AT REAL SAVINGS!
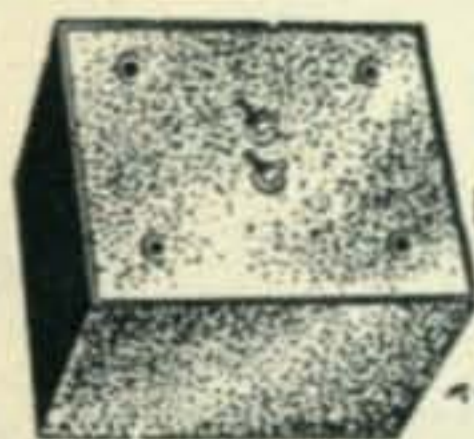
### 400 MA CHOKE

12 H., 90 ohm DC. 12 lb. net, 4½" x 5¾" x 4¼".



4 mtg. holes, 2 center terminals, hermetically sealed.

Only \$3.85



### DC AMMETER

0 to 15 Amps, DC. 5" x 4" in size. Basic movement approx. 12 Ma. Has Mirror Scale. Includes test leads and black crackle metal carrying case. Overseas packed.

\$3.95 ea.

Lots of 10 — \$35.00


### TRANSFORMER

Primary, 115 Volt 60 Cycle.

Secondary, 24 Volt 10 Amp-eres. Encased.

\$4.75 ea.

Lots of 10 \$45.00

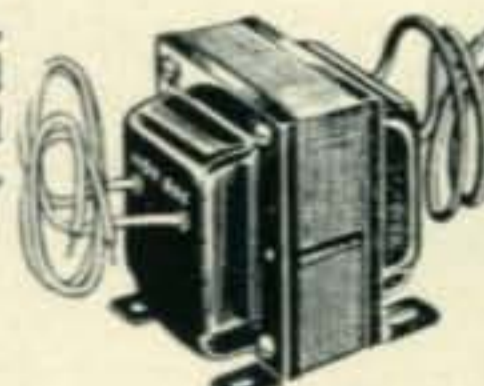

**RELIANCE Merchandizing Co.**

ORDERS F.O.B. PHILA.  
Dept. Q, Arch St. at 23rd

Rittenhouse 6-4927  
Philadelphia 3, Pa.

Club were present. In addition to those mentioned earlier there was Enid Aldwell, W6UXF, of L.A., 6th district YLRL chairman last year, and a crack c-w operator. Another hobby of Enid's is raising flowers, and the waxy white gardenia she wore to the luncheon was the first of the season from her garden.

Another club member is Nina Henry, W6AAL, a telephone operator of Baldwin Park, who for her hobby prefers the key. Nina first became interested in radio twenty years ago when her brother was learning code in the Boy Scouts, but it was only recently that she renewed her interest, got her license, and came up with an "A" call.

A number of the Los Angeles YL Club members attending have already been written up in these pages at one time or another, but among the newer members we met Ida Carney, W6BIS, of San Pedro, treasurer of the L.A. Club. Ida's favorite bands are 10 phone and 80 c.w., on which she runs about 400 watts, and she also does a little 6-meter mobile operating when possible.

Not all of the girls were able to be present and among those we missed were Sandy Sarver, W6-YRL, of Van Nuys, and Helen Cook, W6MWO. Helen, former president of YLRL, was just out of the hospital, but she sounded chipper indeed when we talked with her via landline.

Up from San Diego especially for the occasion was Neva Fredenburgh, W6YXI, vice president of the San Diego YL Club, while Gertrude Pond, W7KOY, and Jessie Olson, W7TBR, came all the way from Phoenix, Arizona.

But we discovered that not all of the YLs taking in the Convention went to the luncheon. One, a "brand new" YL, was Genevieve Malette, W6EHA, of Santa Monica, who received her ticket just a few days before the Convention. And Florence Jones, W6AET, of Altadena, admitted that "instead of attending the luncheon like I should have, and for which I sold tickets, there I was down at Kierulff Radio with all the gang of 'buzzards' from 3956 kc, then over to open house at Radio Products Sales, Radio Tel, and Radio Specialties. And if you ask me if I enjoyed the raffles, my answer is that I won a Hallicrafters receiver! So maybe I'm not disappointed at being absent from the luncheon after all."

Florence, who works for the Navy Department, has been on the air for fifteen years, having learned code at the age of nine. She is strictly a c-w operator—80, 40, 20 and 10, with most of her time spent on 20 and 10, for she is a DXer at heart, adding: "My most choice bit of DX is DA7RF, a Polish boy I used to qso before the war, and a contact that has turned into a lasting friendship. Present equipment at W6AET consists of a GO-9 with v.f.o., running 400 watts input, and a BC-348Q receiver, the rig sitting on a 67" long table she built herself. Her OM, W6DOB, is a television engineer, so as with many another W6 ham couple we met, they live radio practically 24 hours a day.

(QSY to page 90)

## SAM'S SURPLUS TRANSMITTERS

|  |             |           |
|--|-------------|-----------|
| T20/ARC-5 4 to 5.3 mc.....                             | \$ 4.95     |           |
| T22/ARC-5 7 to 9.1 mc.....                             | 7.95        |           |
| Special—Both for .....                                 | 11.95       |           |
| BC375 with tubs.....                                   | \$ 12.95    |           |
| BC447E 500 watt CW.....                                | 139.50      |           |
| 274N Series 2.1 to 3 mc.....                           | 4.95        |           |
| BC 457 4 to 5.3 mc.....                                | 4.95        |           |
| BC 458 5.3 to 7 mc.....                                | 4.95        |           |
| BC 459 7 to 9.1 mc (new).....                          | 12.95       |           |
| <b>RECEIVERS</b>                                       |             |           |
| MN-26C Radio Compass.....                              | \$ 19.95    |           |
| BC 454 3 to 6 mc (new).....                            | 5.95        |           |
| BC 455 (new).....                                      | 9.95        |           |
| BC 683 27 to 39 mc FM.....                             | 18.95       |           |
| <b>MODULATORS</b>                                      |             |           |
| MD-7/ARC-5 push-pull 1625's.....                       | \$ 7.95     |           |
| BC 456 .....   | 2.95        |           |
| <b>FILTER CONDENSERS</b>                               |             |           |
| 4 Mfd 600 volt.....                                    | \$ .79      |           |
| 10 Mfd 600 volt.....                                   | 1.19        |           |
| 8 Mfd 2000 volt.....                                   | 3.95        |           |
| 2 Mfd 2500 volt.....                                   | 2.39        |           |
| 1 Mfd 4900 volt..... (NATIONAL MFG.)                   | 2.95        |           |
| 2 Mfd 4000 volt.....                                   | 3.95        |           |
| 3 Mfd 4000 volt.....                                   | 4.95        |           |
| 2 Mfd 5900 volt.....                                   | 5.95        |           |
| <b>TRANSFORMERS 115 V. 60 CY. PRI.</b>                 |             |           |
| 250 vdc 150 ma, 6.3 v at 5 a, 5 v at 3 a....           | \$ 3.95     |           |
| 6.3 v ct at 15 a.....                                  | 3.95        |           |
| 250 vdc at 70 ma, 6.3 v at 3 a, 6.3 v at 3 a           | 2.95        |           |
| 33 v at 150 ma, 6.3 v at 6a, 5 v at 3 a....            | 1.95        |           |
| 24 vct at 2 a filament.....                            | 2.95        |           |
| 3200 v 300 ma No. C.T. \$ .895 - Two for               | 15.95       |           |
| <b>DYNAMOTORS</b>                                      |             |           |
| PE-103 6/12 vdc to 500 v at 160 ma with-               | \$ 7.95     |           |
| out base .....   | 4.95        |           |
| DM-34-D 12 vdc to 220 v at 80 ma.....                  | 1.49        |           |
| 274-N Receiver dynamotor.....                          |             |           |
| <b>MISCELLANEOUS</b>                                   |             |           |
| FL-8 Audio Filters, see June CQ.....                   | \$ 1.39     |           |
| BC 434 Compass Rec Control Head.....                   | 2.39        |           |
| 500 kc crystals.....                                   | 1.95        |           |
| EE-8 Field Telephone, Used, excel.....                 | 9.95        |           |
| EE-8 Field Telephone, New.....                         | 13.95       |           |
| 12 v vibrapacks, 300 v at 100 ma natl. adv.            | 3.95        |           |
| BC 375 Tuning Units.....                               | 2.49        |           |
| Modulation Xformers 807PP.....                         | 4.49        |           |
| <b>TUBES</b>   |             |           |
| 2X2 \$ .89   | 6SH7 \$ .79 | 832A 3.95 |
| 3AP1 2.49  | 6SN7 .89    | 860 4.95  |
| 5Z3 .79  | 6J7 .79     | 861 12.95 |
| 6AJ5 .89   | 75TL 2.95   | 866A 1.10 |
| 6AK5 .89   | VT127A 2.95 | 872 .97   |
| 6L6 1.25   | 807 .89     | 954 .59   |
| 6L6G .89   | 810 4.95    | 958 .59   |
| 6SC7 .89   | 813 7.95    | 1616 .89  |
|  |             | 5BP4 2.95 |
| Filter Mobile Gen. cuts out gen. noise. Special \$1.00 |             |           |

## ESEGE SALES COMPANY LTD.

Distributors Electronic Parts  
1306 Bond Street at Pico Los Angeles 15, Cal.  
Terms: Cash With Order — Prices Subject to Change

## FREE! BIG 180-PAGE BARGAIN GUIDE

### SAVES YOU REAL MONEY ON RADIO, TELEVISION, ELECTRONICS & TOOLS!

Why pay more for equipment when you can get it for less, direct from the world's largest radio-electronics supply organization? Order everything you need from this famous 180-page money-saving catalog, and pocket the difference! Rush coupon today for your free copy.

#### Lafayette-Concord, D'pt. CA-9

100 8th Ave. New York 13 901 W. Jackson Blvd. Chicago 7 265 Peachtree St. Atlanta 3, Ga.

Please rush FREE Catalog No. 89

Name .....

Address .....

City..... Zone..... State.....



## EASY TO LEARN CODE

It is easy and pleasant to learn or increase speed the modern way—with an **Instructograph Code Teacher**. Excellent for the beginner or advanced student. A quick, practical and dependable method. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready, no QRM, beats having someone send to you.



**ENDORSED BY THOUSANDS!**  
The **Instructograph Code Teacher** literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the **Instructograph System**. Write today for full particulars and convenient rental plans.

## INSTRUCTOGRAPH COMPANY

Dept. C, 4701 SHERIDAN ROAD, CHICAGO 40, ILL.

## RADIO

Technician and Radio Service Courses  
**FM and TELEVISION**

**American Radio Institute**

101 West 63rd St., New York 23, N. Y.

Approved Under GI Bill of Rights

Licensed by New York State

## Ham Headquarters in Westchester County

All Standard Lines of Parts, Tubes, Transmitters and Receivers carried in stock

**Westchester Electronic Supply Co., Inc.**

333 Mamaroneck Ave. White Plains, N. Y.

Telephone:

W.P. 9-5766

W.P. 9-5767

## BUY ROYAL BEAMS FOR TELEVISION, FM and AMATEURS

(Designed by W9RBI First Wis. DXCC Winner)

Royal TV FM Beams All-Aluminum \$8.95 to \$28.95

Royal DeLuxe All-Aluminum Beam 3 EL WS 12' Boom

Junior... \$17.95 Senior... \$22.95

Royal Paul Bunyon (wood boom 8') Beam 3 EL. Junior

... \$11.95 Senior... \$14.95

Aluminum Beam Connectors (can be clamped or bolted to boom, supports elements).....3 for \$2.75

**New Tubes Bargains Price**

6C4, 1625, 1626, 1629...39.....3 for \$1.00

6V6GT/g, 6J6, 5UG4, 836A, 6AG5, 24G......68

6L6G, 83V, 807, 304TL......98

3FP7, 5BP1... \$1.39. 813, V7OD, 304TH.....6.95

Complete 4 tube kit for Command Xmitters.....1.29

RG8/U Cable 52 ohms per 100 ft.....2.95

BC 454 Receiver 75 fone 80 CW.....5.95

Webster-Chicago Wire Recorder Model 78.....99.96

Cash or 25% with order, balance C.O.D. Add postage. Write for flyer.

## ROYAL RADIO SUPPLY

1802 Frazier St. R 4 Madison 5, Wisconsin

## SEE GREENWICH FIRST

New Surplus Co-Axial Relay—Complete with all Co-Ax fittings, cables, plugs, and spares. Housed in small metal case 5" x 3" x 3". A complete modification kit to provide additional channels on existing Radio equipment is included in this deal. Solenoid voltage 12 or 24V. D.C. Schematic and T.O. included. Don't miss on this desirable surplus item—Complete Kit—Brand New—Original Pack. Only.....**\$3.95**

New Bulletin off press—write

**GREENWICH SALES CO.**

59 Cortlandt St. Digby 9-3813 N. Y. C. 7, N. Y.

Saturday evening brought more activity, with many of the YLs serving as hostesses at the dance. Here, also, we met Downs Wright, W6WMA, a recently licensed YL from Trona.

On Sunday, activities were climaxed with a banquet and entertainment, at which the YLs were star performers. Violet Sasse, W6CEE, a recent high school graduate, secretary and youngest member of the L.A. YL club, played several accordian solos, while Lenore, W6NAZ, acted with W6LIP in lively skits, including one depicting "ma and pa" with their first television receiver experiencing ham-caused TVI.

During the entertainment we sat next to W3GV and his XYL, who turned out to be W3KPE—"Kitchen Police Everyday," as Isabelle Bliley expresses it. Though not very active on the air because of caring for her jr. ops, Isabelle, if she wishes, can operate her OM's station from 80 to 2 meters, on the latter W3GV being an outstanding experimenter. Isabelle and her OM were on a real vacation trip, an automobile tour through the West, but were keeping in touch with their five jr. ops back home in Erie, Pa., by talking with them over the air from friends' stations along the way—good old ham radio!

Altogether thirty YLs attended the Convention—a record turnout! And now it's back to the subway circuit again for us, but our visit to the W6 YLs shall always remain a high-light.

## SCRATCHI

(from page 8)

when I are going from AM to FM to SSB. Lil are being there for big ceremony when Scratchi are putting rig on air, and when Lil are seeing how new rig are working it are all I can do to keeping her from christening it with bottle of tequilla.

Then, Hon. Ed., comes the big tragedy. I are turning rig on after a couple of weeks of it working like sixty only this time it are working only on one cylinder. Of course, you are understanding, Hon. Ed., that it are no easy stuff to telling when SSB rig are working or not. In first place, are having practically no carrier, and unless speaking into mike, are having no outputs. So, when Scratchi not speaking into mike, are having practically no outputs which should be having, but when speaking into mike are still having practically no outputs, which should not be having, if you are following me. Louder I am speaking into mike, less of what I should be having is coming out.

Oscilloscope are showing that having nearly no carrier but are showing at same time that are having no sideband, so somewhere Scratchi are losing his sideband. This is why are riting hastily so you can advertising same so maybe Scratchi are getting sideband back and getting on air again.

Respectively yours,  
*Hashafisti Scratchi*

P.S. Please disregarding ad for your Hon. Mag. as Lil are just coming in shack and finding trouble. It seems mike cord are not plugged in audio input hl jack.

H. S.

## LETTERS

(from page 6)

nal is properly tuned in. The report is received so frequently that it must be given some weight.

The most revealing contact to date was a solid one-hour coast-to-coast QSO with W3MBY on a Saturday afternoon, with SS being used on both ends. To those who operate 14-mc phone the mere mention of the day of week and time is sufficient, but to those who are not familiar with the joys of 14-mc phone it might be mentioned that the band is a veritable bedlam at this time. The way W3MBY's beautiful SS signal stood out above the grinding and gnashing left not the slightest doubt that SS is here to stay. The receiver on this end? About 35 dollars' worth of surplus and junk-box parts with an ordinary detector and b.f.o.

Let's give SS a try on its merits. The objectors need have no fears—if it won't do what is claimed, it won't last.

R. Leigh Norton, W6CEM

## GRID-DIP OSCILLATOR

(from page 34)

The transmission bridge or the s-w-r meter should employ a meter of full scale sensitivity of 200  $\mu$ a, or less, for most accurate readings. Coupling to the Dipper should be as loose as possible consistent with obtaining sufficient reading. If the coupling is too tight, the Dipper frequency calibration may be slightly shifted and it will have to be brought back to the correct point while listening to its beat on a receiver.

After the feed line has been adjusted for correct s-w-r or match, the antenna frequency should be again checked. With the feeder correctly matched, antenna resonance should remain the same with and without feeder connected. When checking with feeder connected, the antenna resonant dip will not be very pronounced due to loading by the feeder. Other more pronounced dips may be found. These will be feeder resonance at or near the operating frequency and may be correctly ascertained by lengthening or shortening feeder and observing frequency change of these other dips. Antenna frequency should remain constant.

*Tuning the parasitic beam.* Use the Dipper as g.d.o. and adjust driven element for resonance. The feeder should be disconnected and the parasitic elements should be set at their calculated correct length. If the driven element is open at the center, close it. After this element has been properly set, connect and match feeder as described above (open antenna center if matching system so requires.). The parasitic elements may then be adjusted using the Dipper as the signal generator coupled to the feed line and observe readings on a receiver (with an "S" meter) connected to a short antenna some distance away. Relative field readings in actual "S" units then may be obtained after each adjustment. As when matching feeder, coupling to the Dipper should be as loose as pos-

10 FREQUENCIES WITH A TWIST OF THE KNOB



THE NEW JOHNSON  
**INSTANT**  
Crystal Selector

Amateur Net  
**\$3.48**

With the new JOHNSON "Instant Crystal Selector" you can QSY with the speed of an ECO and still enjoy all the advantages of xtal control! Unit accommodates all crystals with  $\frac{1}{2}$ " spacing. With adaptors you can also use up to six of your upright  $\frac{3}{4}$ " spaced crystals, plus four with  $\frac{1}{2}$ " spacing. Extra position on switch for ECO.

Unit comes complete, ready for mounting on the front panel of your rig. Bracket permits vertical or horizontal mounting of xtals. Mounting board available separately at \$1.86.




# JOHNSON

E. F. JOHNSON CO. WASECA, MINN.


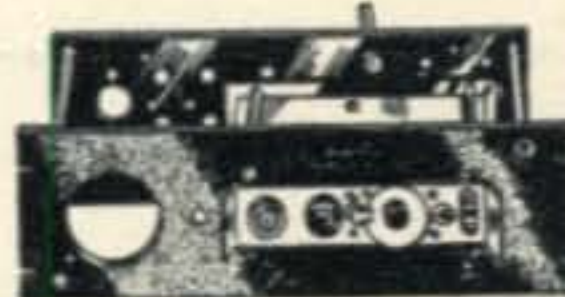
## BARGAIN SPECIAL

25 to 40 Watt **EXCITER**  
10 to 80 METERS FOUNDATION KIT



Engineered around the BC-610 series of plug-in tuning units. Described in the 11th edition Radio Handbook. Completed exciter uses 6AG7 crystal or electron coupled oscillator, 6L6 buffer-doubler and 807 amplifier. Kit includes four tuning units (illustrated at right above with cover removed), special  $5\frac{1}{4}$ " aluminum relay rack panel, socket for plug-in units and special hardware, together with full instructions and diagrams for assembling complete exciter. **\$9.95**  
No. 31A28, FU-40 Foundation, SPECIAL

**PARTS KIT.** Everything needed to complete exciter except tubes and power supply. Includes all mica condensers, resistors, RF chokes, sockets, meter switch, 0-200 ma meter, key jack, and miscellaneous parts. **\$9.31**  
No. 31A28A, SPECIAL Per Kit, Each



### FREE Catalog

Many other BARGAINS in this BIG NEW 1949 B-A Catalog.

Latest developments in Radio and Electronic parts and devices, newest Ham gear.

Write if you have not received it—Cat No. 491 FREE on request.




**BURSTEIN-APPLEBEE**  
1012-14 MCGEE STREET, Company  
KANSAS CITY 6, MISSOURI

# WANT A GOOD FIST?

Flawless CW can be yours with the sensational **MON-KEY**

**\$29.95**

**Your Cost**

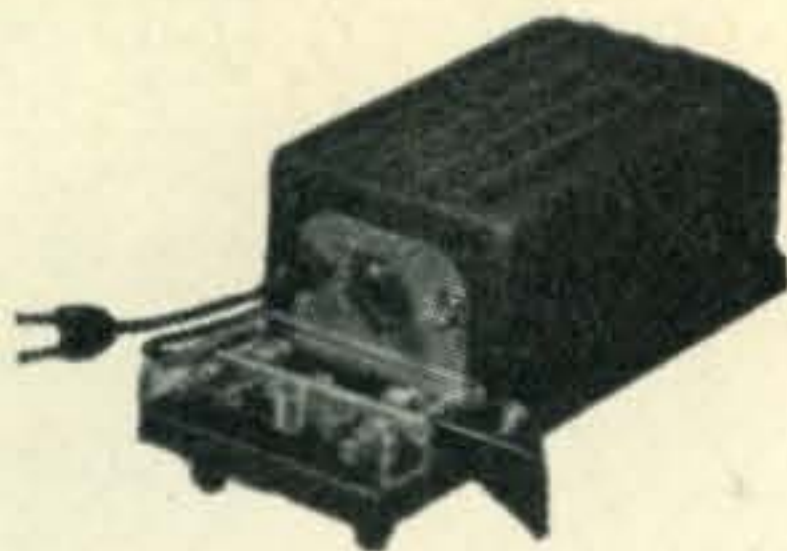

No weights to adjust—Automatic dots and dashes—Speed 8 to 45 words per minute—three tubes—built-in monitor—operation 115v A.C. or D.C. Everything you've ever wanted in a key. Order your sensational new MON-KEY from us today.

Be sure to send your name to us to receive FREE monthly BROADCASTER newspaper.

10%  
CASH  
WITH  
ORDERS



509 Arch St. Phila. 6, Pa.

PHONE  
LOmbard  
3-9225

In Northern California it's  
**SAN FRANCISCO RADIO & SUPPLY CO.**  
Public Address Equipment  
Short-Wave Receivers • Transmitters • Television

Headquarters For Amateur Radio Supplies  
20 Years Dependable Service.  
1280-1284 Market St., San Francisco 2, Calif.

## WANTED

Western Electric Vacuum Tubes, Types 101F, 102F, 272A, 274A or B, 310A or B, 311A, 313C, 323A, 328A, 329A, 348A, 349A, 352A, 373A, 374A, 393A, 394A, 121A Ballast Lamps. Box 91, CQ Magazine

## WANTED

W. E. Carrier Telephone and Carrier Telegraph Equipment and components. Filters, repeating coils, transformers, equalizers. Type CF1, CF2, H, C, and other carrier equipment, telephone and telegraph repeaters. Box 93, CQ Magazine

## ROTARY BEAM CONTROL CABLE No. 8C

8 CONDUCTORS: 2 No. 16, 6 No. 20 tinned, stranded copper; rubber insulated; color coded. TOUGH, WATERPROOF RUBBER JACKET. Overall braided tinned copper ARMOR SHIELD 1/2" O.D. NEW FINEST GRADE MATERIAL. Continuous lengths up to 400 ft. PRICE 10c/ft. F.O.B. Chicago Warehouse.

**TRANS-WORLD RADIO-TELEVISION CORP.**  
6639 S. Aberdeen St. Chicago 21, Illinois  
Phones: AUstin 7-4538 ENglewood 4-4454

## WANTED

TRCI Equipment, T14 Transmitters, R19 Receivers, AM8 Amplifiers, PP13 Power Units. Box 94, CQ Magazine, 342 Madison Avenue, New York 17, N. Y.

sible. It is a good idea to occasionally check the actual frequency of the instrument on the receiver.

After the parasitic elements have thus been tuned, disconnect the feeder and go through the entire tuning up operation again and make the necessary readjustments where required. If the beam is located so that surrounding objects are likely to cause detuning as the beam is rotated (this may be checked during antenna and parasitic element tuning), it may be advisable to do the final retuning with the beam positioned either towards the direction in which it will be mostly used, or where the greatest degree of rotation has the least effect.

Needless to say, the transmitter may be used as the signal generator in place of the Dipper during the above adjustments; however, the employment of the Dipper for this purpose is more convenient, because the entire operation may be handled right on the roof by one person, or wherever the beam is located. The use of the Dipper also keeps the band free from unnecessary QRM.

*Quarter-wave shorted lines.* Use Dipper as g.d.o. and couple for open wire lines as at Fig. 1G, and for coaxial lines as at Fig. 1H. When trimming lines for correct length, fittings to be eventually used for connections should be installed on the end of the line. The approximate frequency of the line may be determined by rough calculation. Other resonant points can be found, however. These will be at three times the fundamental quarter-wave, where the line is then three quarter-waves long, or five times the fundamental quarter-wave, etc.

*Quarter-wave open lines.* For open-wire lines, connect a short at one end and measure as for quarter-wave shorted line. Due to the length of the short, the actual electrical length of the line (used as an open line) will be slightly in error depending on the line spacing. The closer the spacing, the smaller the error.

For coax lines, place short on line and measure as quarter-wave shorted line. The short should be as direct and short as possible from inner conductor to shield in order to avoid errors. Fittings should also be included. Remove the short after measurements are completed.

*Half-wave shorted lines.* For open-wire lines, couple at center as shown at Fig. 1I. For coax line, measure for quarter-wave shorted line at half the calculated or desired frequency. Resonant frequency thus found must be then multiplied by 2 for a resulting half-wave shorted line.

*Half-wave open lines.* For open-wire lines, couple at center as shown at Fig. 1I. For coax line, short one end and measure for quarter-wave shorted line at half the calculated frequency. Resonant frequency thus found must be multiplied by 2 for the correct length of the line after short is removed; provided the short is made direct as mentioned above.

*Check standing waves.* Aside from employing the Dipper as the signal generator in conjunction with a s-w-r meter, open-wire feed lines may be checked for the existence of standing waves by

using the instrument as a diode detector. A flat line is indicated when the meter reading remains constant as the Dipper "probe" coil is moved along the line. Care must be used to maintain uniform distance or coupling between coil and line. Where the Dipper coil is protected by an insulated sleeve, the coil form may be held against the line for maintaining uniform coupling.

This method is the same as that using a neon bulb, crystal detector or other similar device.

*Relative field-strength meter.* Use Dipper as diode detector. Connect a short antenna to one of the coil posts through a 5-30  $\mu\mu\text{f}$  capacitor. The instrument's frequency calibration will shift some, so the dial will have to be rotated for maximum reading of the received signal. Actual frequency calibration is unimportant for this purpose. Sensitivity of the Dipper as a field meter is not as great as that of some other devices, but it will, nevertheless, be helpful in most cases.

The Dipper may be employed for a number of other measurements, principally when utilized as a signal generator. Its use as a g.d.o. will be quite obvious and self suggestive for measurement of many other types of equipment and circuits. The applications herein described are those which will be generally most useful.

## CRYSTAL GRINDING

(from page 40)


either by changing electrodes or by carefully lapping down the electrode lands, taking care to maintain equal plane surfaces on the lands.

You can also make substantial frequency changes by changing the air gap. The greater the air gap, the higher the frequency. Changes of a few hundred cycles at 3.5 mc and a kilocycle or so at 7 mc are perfectly feasible and the technique affords an often used and practical means of accurately adjusting a crystal to frequency. This is the principle usually utilized in many of the commercial "variable frequency crystals."
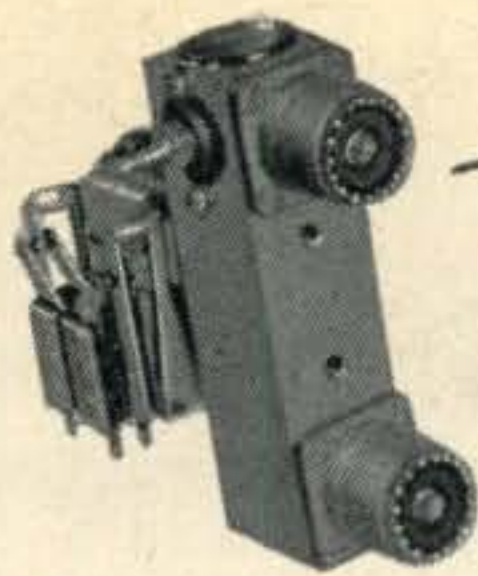
### General

A crystal is a frequency controlling device—not a source of r-f power. Let the crystal take it easy and you'll get a steady carrier and freedom from chirps, yoops, excessive drift and other annoying phenomena.

As for stability under varying temperature conditions (remember that the harder you drive a crystal, the more it heats internally!), the common practice of specifying drift in terms of cycles per megacycle per degree centigrade doesn't mean a thing unless the temperature range is specified, and you know the shape of the temperature-frequency curve. So called "low-drift" crystals may actually have a practically zero coefficient over a very limited temperature range on certain parts of the curve. The reason for this is that the temperature-frequency curve of AT and BT cuts is anything but linear over an extended temperature range, although it approaches linearity over a very restricted part of the temperature-frequency curve.



## ADVANCE COAXIAL RELAYS

*for minimum line loss...*

Extra high efficiency in antenna switching makes ADVANCE small Coaxial Relays ideal for mobile and other low power transmitters.

Designed for 50 ohm RG cable, these ADVANCE Relays maintain a VSWR ranging from 1.04 : 1.00 at 80 mc, to 1.40 : 1.00 at 300 mc, with max. rating of 250 watts.

A variety of terminal positions are available.

*Write for  
descriptive folder  
on all ADVANCE  
Radio Relays*



**ADVANCE ELECTRIC & RELAY CO.**  
1260 WEST SECOND STREET \* LOS ANGELES 26, CALIFORNIA



**R & M's GOT IT!**

**NO MORE SEARCHING  
FOR HARD-TO-GET**

**SURPLUS RADIO  
EQUIPMENT**

Three large warehouses stocked with thousands of govt. radio surplus equipment and parts, priced at a fraction of original cost.

*Write for complete price list. Individual data supplied on specific equipment.*

**R and M  
RADIO COMPANY**



1426 N. Quincy St., Dept. C, Arlington, Va.

# Classified Ads

Advertising in this section must pertain to amateur radio activities. Rates: 25c per word per insertion for commercial advertisements. 5c per word for non-commercial advertisements by bona fide amateurs. Remittance in full must accompany copy. No agency or term or cash discounts allowed. No display or special typographical ad setups allowed. "CQ" does not guarantee any product or service advertised in the Classified Section. Closing date for ads is the 25th of the 2nd month preceding publication date.

PERSONALIZED book matches . . . call letters or name and address . . . samples with prices. Miss Amanda Martin, Box 1123, Rochester 3, N. Y.

QSL CARDS: New, original, exciting. New modern designs exclusive with us from one to multiple color cards. Your own design reproduced at small additional charge. Our prices are the most reasonable, consistent with quality work. Fast service. Send for free samples of price list. The W2PEO Press, 24 Villa Road, Larchmont, N. Y.

CALL LETTER PLATES, aluminum. 6½" x 2¾". 1¼" raised letters on black background. \$1.00. Hawkins Radio Company, 621 E. 31st St., Kansas City 3, Mo.

FREE SAMPLES of QSLs-SWLs. W1HJI, Box 32, Manchester, N. H.

SALE: Amertran plate transf 6200 v. 750 ma. ct. Two 450TH. Three 2 mfd 5000 v. filter condenser, one rectifier, fil. transf 5 v, at 25 A 25000 v. ins. Two 872 and sockets. All new for \$100.00. Write 131 S. Benita Ave., Redondo Beach, Calif.

10 & 6 METER BC222 mobile rigs. Two complete sets. Ready to operate. Tune 28-52 mc. \$60. R. Hayos, 219 W. 81st., New York City.

BIG STOCKS: New and reconditioned Collins, National, Hallicrafters, Hammarlund, RME, Millen, Sonar, Meck, other receivers, transmitters, etc. Reconditioned S38 \$35.00, S40 \$59.00, S53 \$59.00, NC46 \$59.00, NC240D \$149.00, DB20 \$29.00, VHF152 \$59.00, RME84 \$69.00, RME45 \$99.00, HQ120X \$99.00, HQ129X \$139.00, Meck T60 \$89.00, DB22A, HF-10-20, SX43, SX42, SX28A, S36, HT18, HT9, BC610, NC173, NC183, HRO, other receivers, transmitters, VFOs. Easy terms, Shipped on trial. List free. Henry Radio, Butler, Missouri.

FOR SALE: Hallicrafters SX28 communications receiver. Jack for FM and phono. Perfect condition. Best offer. Dr. Henry W. Radom, 113 West 42 Street, New York 18, N. Y.

WANTED: ART/13. Preferably unconverted. State condition and price. WØDNW, 210 W. Second, North Platte, Neb.

BC 348-Q, BUILT-IN Q-5er, 1852 RF stage, noise limiter, external power supply, etc. Make offer. W4MVM, Chickasaw, Ala.

BC-348-M RECEIVER, BC-459 transmitter, 110 volt power supply for both. \$50. W. Kirchhoff, 485 Pelham Road, New Rochelle, N. Y.

QSLs? SWLs? Made-to-order! Samples 10¢. Sackers. W8DED, Holland, Michigan.

CRYSTALS: Precision, low drift mounted units, 3500 to 9000 kilocycles, ±5 kilocycles \$1.00. Exact frequency \$1.50. Specify mounting. Write for quotations all other frequencies. Breon Laboratories, Williamsport, Penna.

FOR SALE: 2 PE-103 generators. 1 new in original crate—\$12.00; 1 used—\$9.50. 2 Westinghouse radiation meters, 0-3, \$2.50 each. 1 Weston milliammeter, 0-250, less shunt—\$2.50. W2ADC.

QSL's, SWL's. MADE the way you want them. Samples? W9BHV QSL Factory, 857 Burlington, Frankfort, Indiana.

ALUMINUM TUBING for antennas, 11 ft. lengths x 5/8" OD, 24ST (rigid), \$1.50 per length. Metalcraft Toy Co., Paul Brown Bldg., St. Louis.

FOR SALE: CREI introductory and advanced course. New condition—\$55.00. Sonar XE-10—\$25.00. Sonar CFC exciter—\$35.00. Robert J. Barone, 1618 Bay Court, Brooklyn, N. Y.

SELL: 500 watt 115 volt remote start Fairbanks Morse light plant. Used very little. \$200. ARC-ARN 7 radio compass—\$20. Welte, W7HJM, Hingham, Mont.

GF11/RU-16, brand new and complete, xmtr covers 2000-9050 kc, receiver 195-13575 kc. Receiver partially converted to a.c. for external power supply. Complete outfit with dynamotor, spare tubes, etc. as shipped by manufacturer \$50.00, xmtr and dynamotor only \$30.00, receiver and coils to cover 195-13575 kc with power supply \$35.00 Receiver only \$25.00. Hollis Button, Valley City, No. Dak.

BC348J, BRAND NEW in original crate, including shock mount base, manual, not used or tampered with—\$75.00. f.o.b. W9CCF, 328 Center, Waupaca, Wisc.

BINDERS FOR YOUR CQ ISSUES available! Rich red Dupont Fabricord, stainproof and washable. Backbone gold stamped with CQ and year—1945, 1946, 1947, 1948, 1949 specified in order. Center channel to keep magazines fastened in position. \$2.00 each postpaid. Foreign orders—add 25c per binder. Plain binders on special order at no extra cost.

QSLs QUALITY CARDS priced right. Samples. W9UTL, 1768 Fruitdale, Indianapolis, Ind.

OUR BUSINESS . . . Buying, totally and completely refinishing and selling . . . amateur radio transmitters. Transmitter Exchange, Wakefield, Rhode Island.

10-METER 3-ELEMENT BEAMS—\$19.50. Send card for free information. Riverside Tool Co., Box 87, Riverside, Illinois.

AMATEUR RADIO LICENSES. Complete theory preparation for passing amateur radio examinations. Home study and resident courses. American Radio Institute, 101 West 63rd Street, New York City.

QSLs. Samples for stamp. Henry L. Carter, Jr., W2RSW, 747 S. Plymouth, Rochester 8, N. Y.

WANTED: Aircraft Radios; BC-348, AN ART-13, RTA-1B, AN/APN-9, R5A/ARN-7, AN/ARC-1, AN/ARC-3, SCR-718, BC-788-C, I-152, MN-26-C. Tests set with TS or I prefix. State quantity, condition and best price first letter. HI-MU Electronics, Box 105, New Haven, Conn.

QSLs, SWLs. Quality cards. W5FAY Press, 6118 Goliad, Dallas, Texas.

WHY WAIT? Join N.A.R.C. today. The best \$2.00 investment ever made for the good of the amateur. Send your application with handle, QTH and class of license to: National Amateur Radio Council, Inc., 23 Main Street, Champaign, Illinois.



FOR SALE: One new HQ129X complete with speaker and manual \$134.50. One new NC-240D complete with speaker and manual \$199.50. One NC-46 complete with speaker and manual, slightly used, \$69.50. Ward Lantis, W4LEB, 2207 Millye St., Westwood Hills Add., Kingsport, Tenn.

AF-100 SUPREME transmitter for sale, like new, used 3 months, \$375. R. Cabanillas Jr., Room 803, 9 Maiden Lane, N. Y.

FOR SALE OR TRADE: Mobile rig including Stancor ST203A, Gonset converter with noise clipper, also 19B22A. Want scope, prop pitch motor, BC-221 frequency meter or what have you? Bernard R. Bailey, W7MEG, 514 Third St. West, Billings, Mont.

FOR SALE: HT-9 transmitter in excellent condition, coils for 80-20-10 m, spare tubes, instruction book crystals, \$300. Local buyer preferred. L. F. Brown W2JJD, 37-30 81st Street, Apt. D-5, Jackson Heights, L. I., N. Y.

COLORTONE QSLs! Snappy! Bright! Different! Beautiful samples free! Colortone Press, Tupelo, Miss.

BARGAINS—NEW AND USED TRANSMITTERS—Receivers—Parts. New 150 watt phone \$199.00; 60 watt phone \$99.00; Globe Trotter \$57.50; Abbott TR-4 \$29.50; HT-9 \$295.00; MB-611 \$59.00; Silver 701, 800, 801, 802, \$29.50 ea.; NC-173, SX-28 \$149.00 ea.; HQ-129X, HRO \$139.00 ea.; RME-45, SX-25 \$99.50 ea.; RME-9D \$39.50; SX-24 \$75.00; BC-348, S-40 \$65.00 ea.; S-20R \$49.00; NC-44, S-38 \$35.00 ea.; many others. Large stocks—trade-ins. Free trial. Terms financed by Leo, WØGFQ. Write for catalog and best deal to World Radio Labs, Council Bluffs, Iowa.

SELL MACKAY 167-BY kilowatt. Finest power and audio components. \$500 or best offer. Local purchaser only. W. C. Thomas, 40 North Road, White Plains, N. Y.

WANTED: Teletype 1/40th HP synchronous motor. W6ITH, Moraga, Calif.

WANTED: BC-224-A instruction manual or schematic. Lewis Denson, W4LYE, Route 1, Box 395, Anniston, Alabama.

WANTED: QST—all issues prior to December 1924. Write giving details, condition and price. Ed Newman, 214 Munro Blvd., Valley Stream, L. I., N. Y.,

WANTED: HRO bandsread coils. Write airmail giving price. Bill Scarboro, 2K2AA, Nuie Island, Pacific.

COMPLETE PORTABLE RECORDING UNIT—Presto K8 recorder with built-in 3 channel mixer, Webster 78 wire recorder, microphones, auxiliary equipment, all A-1 condition. Sell units separately, or as complete unit. Also ARC/5 receiver power supply. W3KJL, 720 N. Webster Ave., Scranton, Pa.

ALUMINUM TUBING, angles, channels and pipe. Write for list. Willard Radcliff, Fostoria, Ohio.

SACRIFICE—Cash wanted. Receiver NC240D and speaker used 2 months, \$180; frequency meter BC221, \$33; transmitter, phone-cw, 150 w. 80-10 complete audio and power supply all enclosed in 28" Par-Metal gray crackle cabinet, \$120; wire recorder, Webster portable, new, \$118; new spare plate transformer, Thordarson 1500 v. @ 500 ma., \$29. G. L. Schultz, W2EJB, Essex Falls, N. J. Caldwell 6-4394.

DB22A, VHF-152A, HF-10-20, (all slightly used) bargains! W8QJC, P. O. Box 218, Holland, Mich.

COMMAND SETS: ARC-5/274N transmitters, 3-4 mc. new \$14.95, used \$9.95; 7-9.1 mc. new \$12.95, used \$8.95; 2-3 mc., 4-5.3 mc. or 5.3-7 mc. new \$9.95, used \$6.95. Receivers, 190-550 kc., 520-1500 kc. or 1.5-3 mc. new \$15.95, used \$12.95; 3-6 or 6-9.1 mc. new \$9.95, used \$7.95. Splines 25c, crank knobs 75c. Used sets in excellent condition—satisfaction guaranteed. W5EAL, 1110 Winbern, Houston 4, Texas.

Note: In W5EAL's November classified ad a line of copy was inadvertently omitted so that the ad incorrectly read "Receivers, 190-550 kc, new \$9.95, used \$7.95." The correct advertisement appears immediately above this notice.



*"It's KENYON Transformers For My Rig Because They Always Put Out!"*



- Hams everywhere specify KENYON "T" Line Transformers! Manufactured under rigid standards, all KENYON transformers are constructed of the finest grades of material plus the skill and long experience of a highly trained competent operating staff.
- All KENYON transformers are checked progressively in the course of manufacture and are laboratory-tested upon completion to insure satisfaction. Yes, KENYON "T" Line Transformers meet the most exacting requirements of critical purchasers. For skillful engineering, progressive design and sound construction—Specify KENYON for top performance in your rig!


**KENYON TRANSFORMER CO., Inc.**

840 BARRY STREET  
NEW YORK, U. S. A.

# JOHNSON
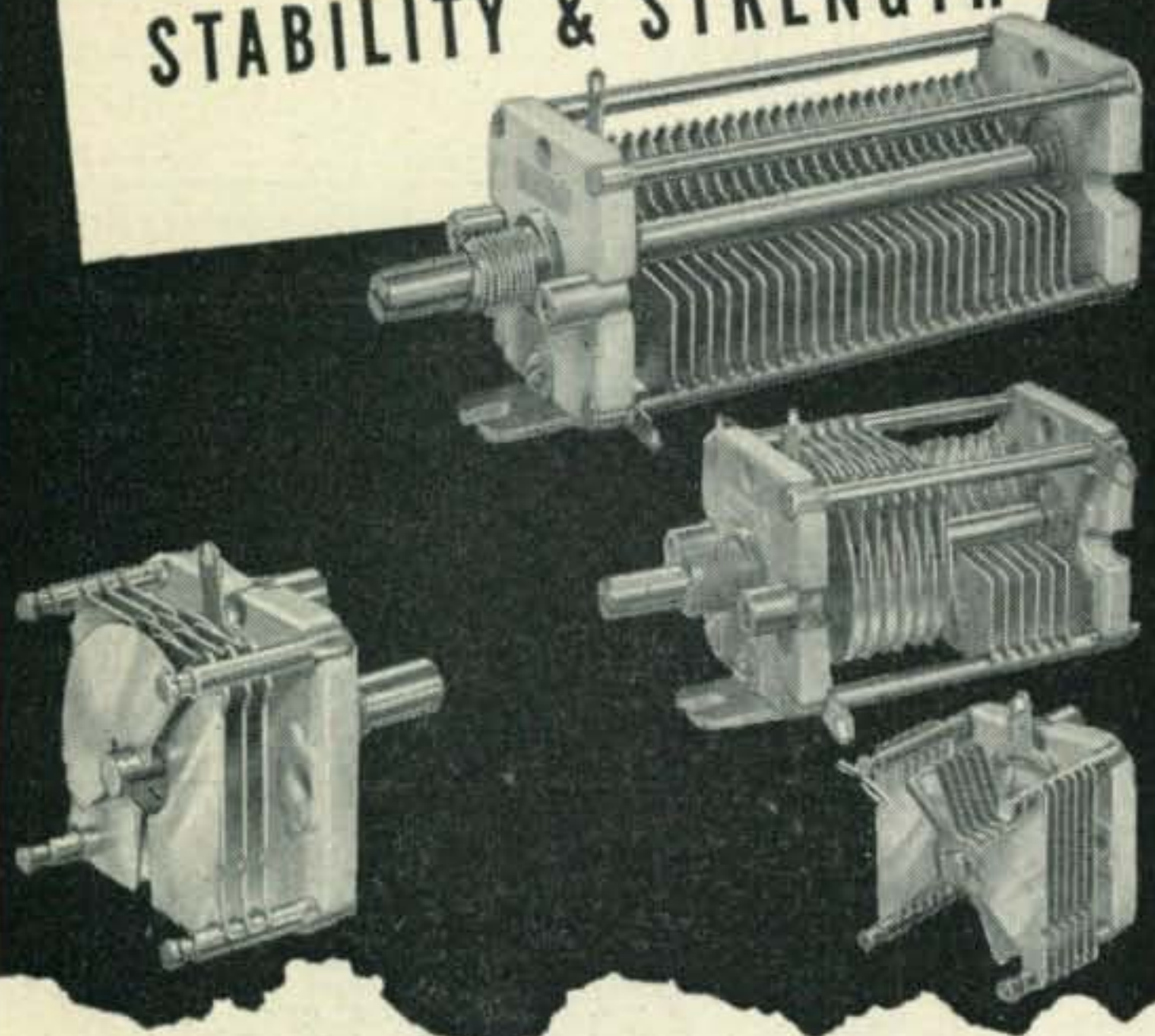
## 167 Variables ...

CERAMIC SOLDERED  
for  
STABILITY & STRENGTH



Peak efficiency, plus permanent maintenance of capacities—even under severest operating conditions such as portable-mobile operation—is assured in JOHNSON'S new line of 167 Variables. The use of perfected ceramic soldering eliminates the need for eyelets, nuts or screws. There is nothing to work loose, causing stator wobble and fluctuations in capacities!

Available in .030" and .080" spacings for all types of communications equipment having tuned circuits operating as high as 500 mc.

**Single Type** — Available in six models: 2.8 to 11 mmf, 3.5 to 27 mmf, 4.6 to 51 mmf, 5.7 to 75 mmf, 6.8 to 99 mmf, 11.6 to 202 mmf.

**Dual Type** — Available in three models: 3.5 to 27 mmf, 4.6 to 51 mmf, 6.8 to 99 mmf.

**Differential Type** — Available in three models: 2.8 to 11 mmf, 3.5 to 27 mmf, 4.6 to 51 mmf.

**Butterfly Type** — Available in three models: 2.8 to 10.5 mmf, 4.3 to 26 mmf, 6.5 to 51 mmf.

Other Capacities and spacings available on special order. Write for new JOHNSON 167 Variable Catalog.

# JOHNSON

*a famous name in Radio*

E. F. JOHNSON CO., WASECA, MINN.



## CQ Ad Index

|  |             |
|--|-------------|
| Advance Electric & Relay Co.....         | 93          |
| Alliance Manufacturing Co.....           | 74          |
| Allied Radio Corp.....                   | 73          |
| Almo Radio Company.....                  | 92          |
| Alvaradio Supply Company.....            | 84          |
| American Radio Institute.....            | 90          |
| Barker & Williamson.....                 | 85          |
| Bee Bee Electronic Co.....               | 86          |
| Bud Radio, Inc.....                      | 2           |
| Burstein-Applebee Company.....           | 91          |
| Collins Radio Company.....               | 12          |
| Communications Equipment Co.....         | 79          |
| Dow Radio, Inc.....                      | 53          |
| Eitel-McCullough, Inc.....               | 10          |
| Electro-Voice, Inc.....                  | Cover 2     |
| Esege Sales Co., Ltd.....                | 89          |
| Esse Radio Company.....                  | 56-69 incl. |
| Fair Radio Sales.....                    | 78          |
| General Electric Co. (Ken Rad Div.)..... | 1           |
| Greenwich Sales Company.....             | 90          |
| Hallicrafters Company.....               | 49          |
| Harrison Radio Corp.....                 | 51          |
| Harvey Radio Company, Inc.....           | 55          |
| Harvey-Wells Electronics, Inc.....       | 72          |
| Heath Company.....                       | 77          |
| Henry Radio Stores.....                  | 71          |
| Instructograph Company.....              | 90          |
| International Resistance Co.....         | 8           |
| Johnson, E. F. Co.....                   | 6, 91, 96   |
| Kenyon Transformer Co., Inc.....         | 95          |
| Lafayette-Concord.....                   | 89          |
| Merit Coil & Transformer Corp.....       | 70          |
| Millen, James Mfg. Co.....               | 4           |
| National Company, Inc.....               | 47, Cover 3 |
| National Radio Institute.....            | 7           |
| Petersen Radio Company, Inc.....         | 5           |
| Photocon Research Products.....          | 80          |
| Pioneer Broach Company.....              | 86          |
| Radio Corp. of America (Tube Div.).....  | Cover 4     |
| Reliance Merchandizing Co.....           | 88          |
| R & M Radio Company.....                 | 93          |
| Royal Radio Supply.....                  | 90          |
| San Francisco Radio & Supply Co.....     | 92          |
| Stahl, Michael, Inc.....                 | 84          |
| Surplus Radio, Inc.....                  | 83          |
| Sylvania Electric Products, Inc.....     | 9           |
| Tab.....                                 | 81          |
| Trans-World Radio-Television Corp.....   | 92          |
| Westchester Electronic Supply Co.....    | 90          |
| Workshop Associates, Inc.....            | 76          |
| World Radio Laboratories, Inc.....       | 75          |
| Y M C A.....                             | 96          |

### RADIO

OPERATING • SERVICING • CODE  
TYPING • VIBROPLEX  
FM • TELEVISION


APPROVED FOR VETERANS  
Send for Catalog



TRADE & TECHNICAL SCHOOL  
229-237 W. 66 St. New York, N. Y.

see inside . . .

then decide . . .

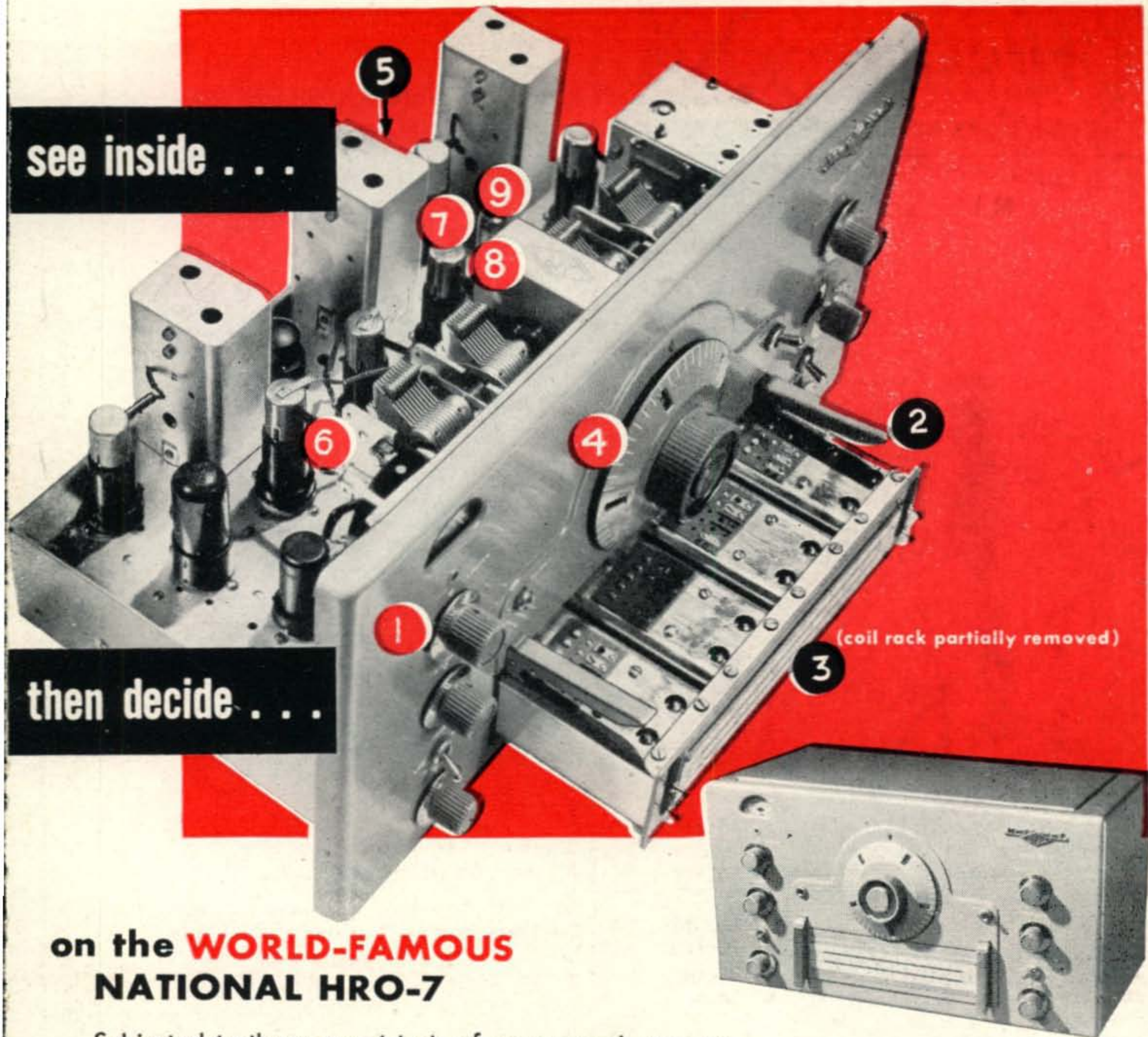

## on the **WORLD-FAMOUS** **NATIONAL HRO-7**

Subjected to the severest tests of government, commercial and amateur use for 14 years, the basic HRO design has set a new high in receiver performance. Now, here it is in its newest, finest form. As always the major components are National designed and made.

**RANGE:** 1.7 to 30 mcs. (Additional coils available for 50 to 430 kcs, 480 to 2,050 kcs, 30 to 35 mcs.)

**SENSITIVITY:** 1 microvolt or better.

**IMAGE REJECTION:** Better than 30 db at 30 mcs.

**SIGNAL-TO-NOISE RATIO:** Exceeds 16 db with 5 microvolts input.

**AVC CHARACTERISTIC:** to  $\pm 10$  db between 1.0 and 100,000 microvolts input.




**NATIONAL COMPANY, Inc.**  
MALDEN, MASSACHUSETTS

- 1 Automatic adjustable-threshold noise limiter.
- 2 Lever handles for coil set changing.
- 3 Slide rule calibration on all coil sets.
- 4 500-degree micrometer dial (effective scale length 12 feet). 400 degrees of bandspread on 80, 40, 20 11-10 meters.
- 5 Accessory socket and switch for NFM adaptor or phonograph.
- 6 Two tuned RF stages.
- 7 Two IF stages.
- 8 Precision gear drive eliminates backlash.
- 9 Voltage-regulated high frequency oscillator for exceptional stability.

**\$312.86** (Complete with coils and power supply, less speaker)

# Champions!

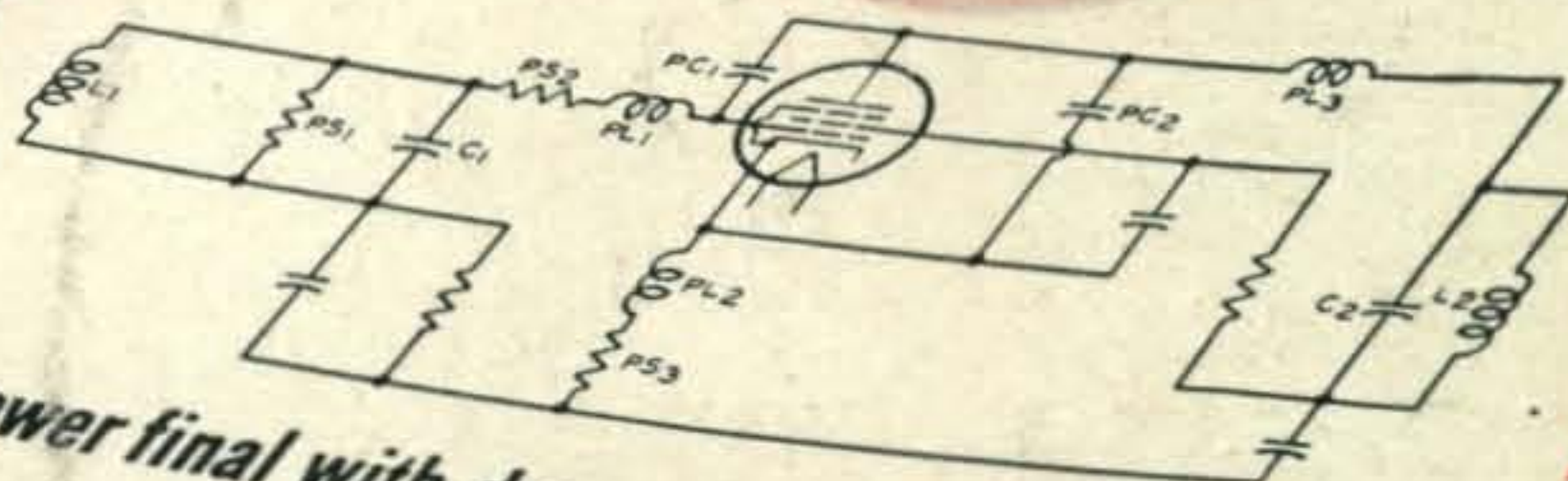

*Typical beam power final with degenerative stabilization*

THE FOUNTAINHEAD OF MODERN  
TUBE DEVELOPMENT IS RCA

## Still unmatched . . .

## in price – power – performance

● No wonder RCA 807 and 813 beam power tubes are today's favorites for finals! These huskies require less drive and deliver more output at lower plate voltage, than any other similar tube types within a comparable price range. You get the *same* results with fewer stages, smaller driver tubes, and a less elaborate power supply.

What's more, RCA 807's and 813's—like all RCA beam power tubes—are excellent for quick-change, multi-band transmitters because they sel-

dom require stabilization in well-designed circuits. Where difficulties may arise, permanent stabilization on all bands is simply achieved by neutralization or degeneration . . . at no sacrifice in efficiency.

To get the most out of *your* beam power tube be sure to read the article on stabilization in the May-June 1947 issue of *Ham Tips*. See your Tube supplier for a copy, or write RCA, Commercial Engineering, Section 38AM, Harrison, N. J.



**TUBE DEPARTMENT**

**RADIO CORPORATION of AMERICA**

**HARRISON, N. J.**