

December 1965

75¢

ICD


CQ



The Radio Amateur's Journal

**Happy
Holidays
old
man**



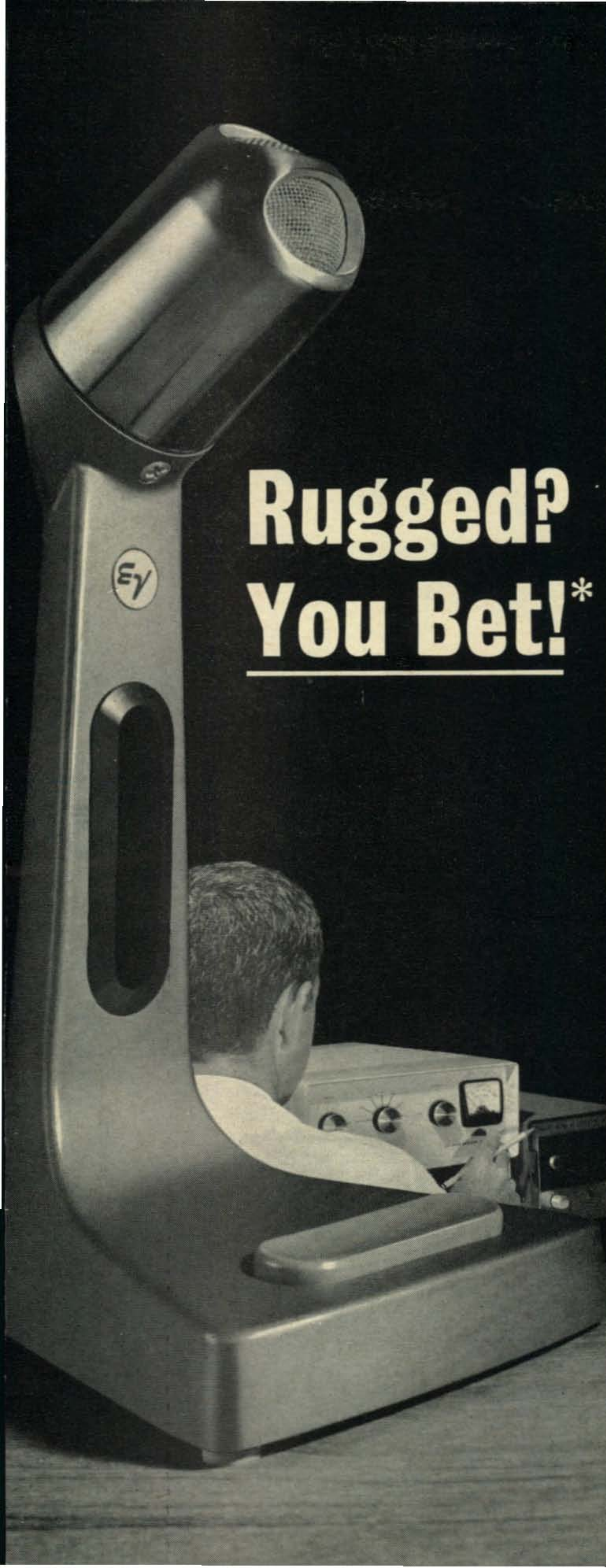


Rugged? You Bet!*

TOUCH-TO-TALK
COMMUNICATIONS
MICROPHONES

Model 619 Dynamic \$28⁵⁰_{net}

Model 719 Ceramic \$16⁵⁰_{net}

 These new beauties are tough. No fragile plastics or lightweight metal. A 400-ton high-pressure die casting machine turns two pounds of molten metal into a solid stand that laughs at heavy service. And tough baked enamel plus heavy chrome plating guarantees lasting good looks.

Just touch the big bar to talk. It latches on with a simple, sliding motion. Or move it to the grip-to-talk position on the stand riser in just minutes, with only a screwdriver. The DPDT telephone-type leaf switch will last a million calls or more. It operates both voice and relay circuits, with optional electronic switching available at the end of the 619 (Hi-Z) and 719 cable.

All models are omnidirectional, and come complete with heavy-duty cable. Most economical is the Model 719 ceramic. Response is from 80 to 7,000 cps at -56 db output.

For top quality, choose the Model 619 dynamic models with exclusive E-V Acoustalloy diaphragms. Smooth, peak-free response from 70 to 10,000 cps at -56 db output insures highest talk power and full modulation. Choose either Hi-Z or balanced Lo-Z model.

Try one of these rugged new beauties today. You'll find that your rig never sounded — or looked — so good!


ELECTRO-VOICE, INC.
Dept. 1252G, 618 Cecil Street
Buchanan, Michigan 49107

Electro-Voice®
SETTING NEW STANDARDS IN SOUND

*We cover our bet with a *lifetime* guarantee. If any 619 or 719 ever fails, just send it to us. We'll repair it at nominal cost. But if there's even a hint that our workmanship or materials weren't up to par, the repair is on the house — even 30 years from now! Fair enough?

For further information,
check number 1, on page 106

*Bye
Bye
Birdie*

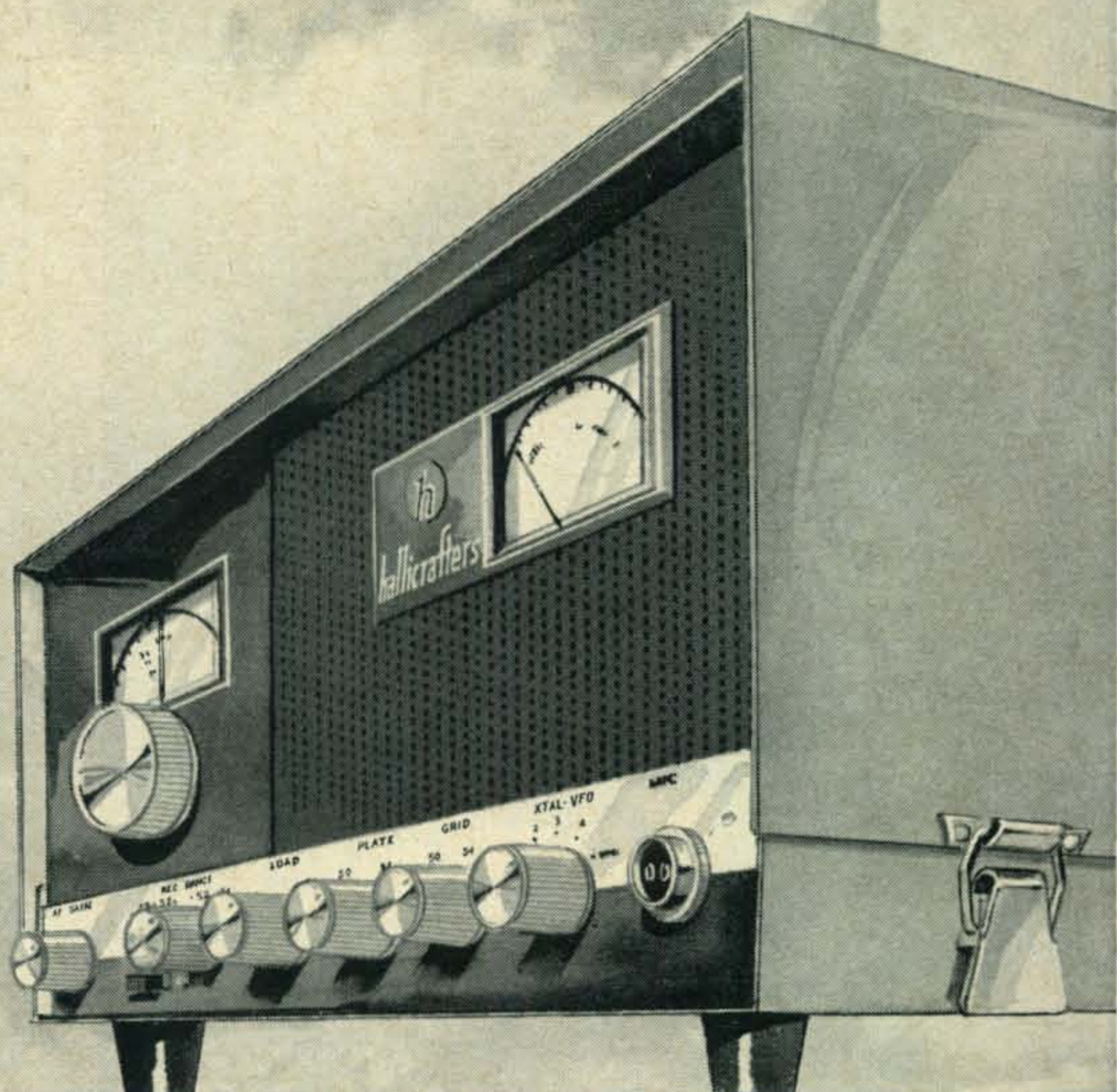

Efficient filters and selected injection frequencies make the NEW SR-46 and SR-42 VHF transceivers virtually immune to FM and TV interference.

Interference-free reception is only one of many advantages in the new SR-46. Complete six meter band coverage is another. Or full two meter coverage, if you prefer, in the companion SR-42 unit. Both give you double the usual bandspread, through use of dual tuning ranges. A neutralized nuvistor front end boosts sensitivity, and eleven tuned circuits increase selectivity while suppressing interference. Push to talk, of course.

Thorough field testing, before production, by hundreds of operators, assures you of years of trouble-free performance. It all adds up to your top VHF value. See the SR-46, or the SR-42, at your distributor today.

FEATURES

Frequency Coverage: 50 to 52 Mc and 52 to 54 Mc (144 to 146 Mc and 146 to 148 Mc in the SR-42). **Power Input:** 10-12 watts. **Power Supply:** 115 VAC and 12 VDC (vibrator and line cord optional extra). **Transmitter Crystals:** high frequency type; provision for four (one furnished), plus external VFO, switch-selected from front panel. **Tubes:** 10, plus zener diode oscillator control and four diodes (11 tubes, 2 zeners and four diodes in the SR-42). **"S" Meter** automatically switches to RFO. **Cabinet:** "snap-off" type for easy access. **Size:** 5½" high, 12¼" wide, 8¼" deep. **Shipping Weight:** 17 lbs. **Amateur Net Price:** \$189.95.

New SR-46

SIX METER VHF TRANSCEIVER
and SR-42 for two meters

Export: International Div., Hallicrafters.
"Available from Gould Sales in Canada"

For further information, check number 2, on page 106

*"Quality through
Craftsmanship"*



hallicrafters

5th & Kostner Aves., Chicago, Ill. 60624



The Radio Amateur's Journal

STAFF

EDITORIAL

RICHARD A. ROSS, K2MGA
Editor

ALAN M. DORHOFFER, K2EEK
Associate Editor

IRVING TEPPER
Technical Editor

WILFRED M. SCHERER, W2AEF
Technical Director

MARCIA HIGGINS
Assistant Editor

CONTRIBUTING

FRANK ANZALONE, W1WY
Contest Calendar

ROBERT M. BROWN, K2ZSQ
VHF

WALT BURDINE, W8ZCV
Novice

GEORGE JACOBS, W3ASK
Propagation, Space

ALLEN KATZ, K2UYH
VHF

BYRON H. KRETZMAN, W2JTP
RTTY

A. EDWARD HOPPER, W2GT
USA-CA

URBAN LE JEUNE, W2DEC
DX

ALFRED G. SMITH, WA2TAQ
Club Forum

LOUISA B. SANDO, W5RZJ
YL

CHARLES J. SCHAUERS, W6QLV
Ham Clinic

BUSINESS

SANFORD R. COWAN
Publisher

JACK N. SCHNEIDER, WA2FPE

RICHARD A. COWAN, WA2LRO
Advertising Representatives

HAROLD WEISNER, WA2OBR
Circulation Manager

PRODUCTION

CARY L. COWAN
Production Manager

RUTH SOKOLOW
Art Director

TABLE OF CONTENTS

28	HARMONIC RICH 100 KC CRYSTAL CALIBRATOR <i>Wilfred M. Scherer, W2AEF</i>
31	HUM REDUCTION..... <i>James Ashe, W2DXH</i>
32	OSCAR NOTES..... <i>Wilfred M. Scherer, W2AEF</i>
33	USING AUDIO CONTROLLED A.G.C. FOR IMPROVED RECEIVER SELECTIVITY <i>James E. Taylor, W2OZH</i>
35	CIRCUIT BOARDS—QUICK AND EASY <i>Wilfred M. Scherer, W2AEF</i>
37	RTTY FROM A-Z, PART XVII..... <i>Durward J. Tucker, W5VU</i>
40	MODERN CIRCUIT DESIGN FOR VHF TRANSMITTERS, PART II..... <i>H. C. Barber, W6GQK; W. I. Orr, W6SAI; R. Rinaude, W6KEV; R. Sutherland, W6UOV</i>
46	NEW AMATEUR PRODUCTS
48	"BRUNO PUTS ISRAEL INTO SPACE" <i>Uri Berneah, 4X4OC/W6</i>
49	CQ REVIEWS: THE TRANSCOM SBT-3 TRANSCEIVER <i>Wilfred M. Scherer, W2AEF</i>
52	THE CARE AND FEEDING OF LINEARS <i>Wells Chapin, W2DUD/8</i>
54	CQ AWARDS HONOR ROLL
57	A HALF WAVELENGTH VERTICAL <i>William E. LaFarra, W5ZCC</i>
59	A QUIET WEEKEND WITH THE JET-SET..... <i>Sylvia Margolis</i>
62	PEOPLE AND PLACES
109	INDEX TO CQ VOLUME 21—1965


DEPARTMENTS

18	ANNOUNCEMENTS	68	PROPAGATION
20	CLUB FORUM	85	RTTY
66	CONTEST CALENDAR	83	SPACE
63	DX	79	USA-CA
74	HAM CLINC	71	VHF
12	LETTERS	87	YL
77	NOVICE	7	ZERO BIAS

Offices: 14 Vanderventer Avenue, Port Washington, L. I., N. Y. 11050. Telephone: 516 PO 7-9080.

CQ—(Title registered U. S. Post Office) is published monthly by Cowan Publishing Corp. Second class postage paid at Port Washington and Garden City, New York. Subscription Prices: U. S. A., Canada and Mexico, one year, \$5.00; two years, \$9.00; three years, \$13.00. Pan-American and foreign add one dollar per year. Entire contents copyright 1965 by Cowan Publishing Corp. CQ does not assume responsibility for unsolicited manuscripts. Please allow six weeks for change of address. Printed in the United States of America.

SSB *problems solved here*

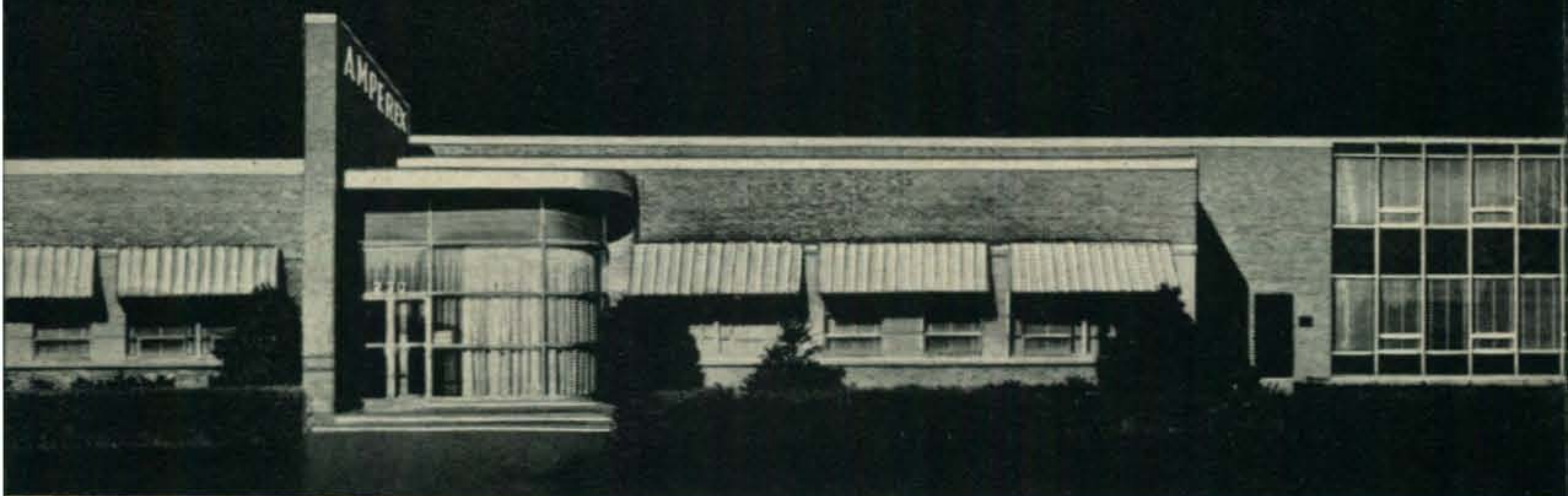

Amperex status as the source of more tube types for Single Sideband Suppressed Carrier Service than any other producer, didn't just happen. Leadership has been achieved as the result of a deliberate and continuing program of engineering research and intensive laboratory testing from which has emerged a distinctive and clearly superior comprehension of SSB

technology and SSB applications for any power level from 5 watts to 5 kilowatts PEP.

From internal tube geometry to overall envelope design, AMPEREX SSB Tubes are *Performance Tested, Performance Rated and Performance Guaranteed* for optimum linearity and minimum intermodulation distortion at *full Single Sideband power ratings*.

like this...



SSB TYPE NO.	7378	SD568*	8637	8505	8579	8163
Useful Peak Envelope Plate Power Output (watts)	167	180	76 (PTTS)	57	110	700
3rd Order Intermodulation Distortion (db) (without feedback)	35	30	25	30	30	35
5th Order Intermodulation Distortion (db) (without feedback)	40	35	35	43	40	40
Typical D.C. Plate Voltage (volts)	750	2000	600	750	600	2500

Illustrated are six new communication types of a line of more than 20 AMPEREX "Performance-Rated" SSB tubes with power ratings from 5 W. to 5 Kw. PEP. Watch for releases of new SSB tubes now in prototype stage. Write for technical data sheets. Applications engineering assistance available. AMPEREX Electronic Corp., Tube Division, Hicksville, L. I., N. Y. 11802.

AmpereX®

*Conduction cooled version of the 8321/4CX350 in development.


For further information, check number 5, on page 106

NOW! A TRI-BAND SSB TRANSCEIVER KIT FOR 179.9




NEW EICO 753 SSB/AM/CW TRI-BAND TRANSCEIVER

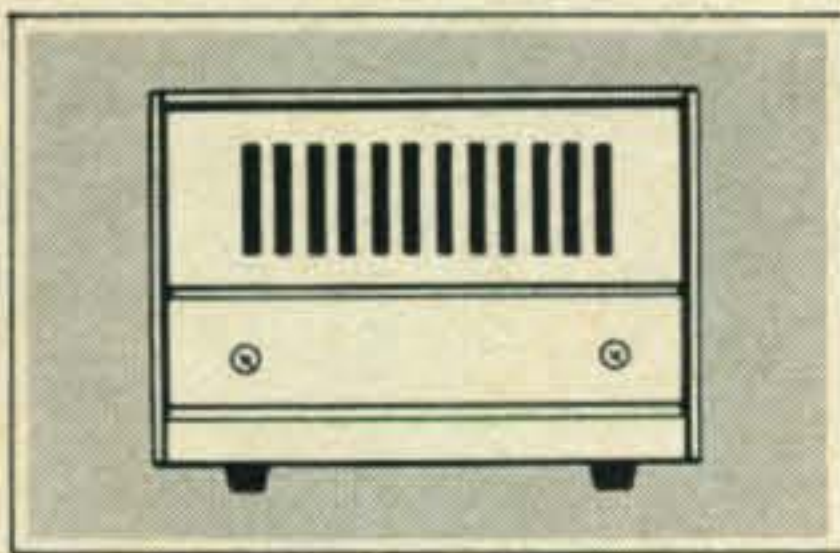Power Supplies Tailored for
Optimum Performance
of the 753.



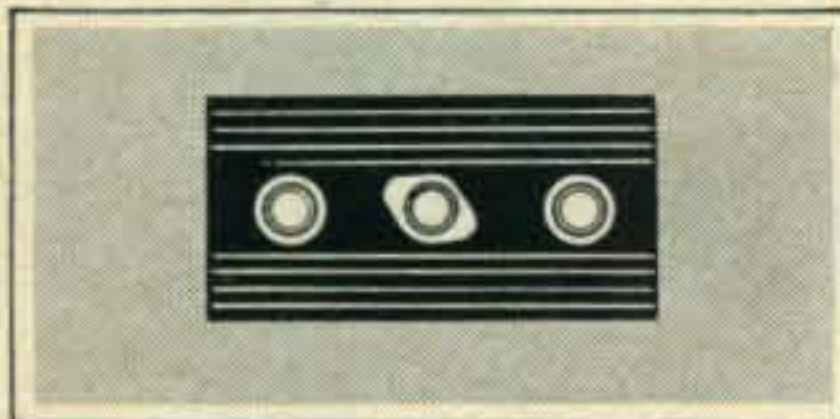**Model 751 Solid State AC
Supply/Speaker Console.**
Matching table-top companion
unit. Built-in PM speaker.
Kit \$79.95 Wired \$109.95



**Model 752 Solid State Mobile
Supply.**
For use with 12 volt positive or
negative ground systems. Fully
protected against polarity re-
versal or overload.
Kit \$79.95 Wired \$109.95

Build the finest of SSB/AM/CW tri-band transceivers with 200 watts of SSB punch and every wanted operating facility, plus the extra reliability and maintenance ease inherent in kit design. Assembly is made faster and easier by VFO and IF circuit boards, plus preassembled crystal lattice filter. Rigid construction, compact size, and superb styling make this rig equally suited for mobile and fixed station use. The new EICO 753 is at your dealer now, in kit form and factory-wired. Compare, and you will find that **only the 753 has all these important features:**

- Full band coverage on 80, 40 and 20 meters.
- Receiver offset tuning (up to ± 10 kc) without altering transmitter frequency.
- Built-in VOX.
- Panel selected VOX, PTT & STANDBY.
- High level dynamic ALC to prevent flat-topping or splatter and permit the use of a linear amplifier.
- Automatic carrier level adjustment on CW and AM.
- Dual ratio ball drive permits single knob 6:1 rapid tuning and 30:1 vernier bandspread (over 10 degrees of scale).
- Position of hairline adjustable on panel.
- Illuminated S-meter/PA Cathode Current Meter and tuning dial.
- Fast attack, slow decay AGC.
- Grid-block break-in CW keying.
- Product detector for SSB and CW, triode detector for AM.
- TR relay with auxiliary contacts for use with high power linear amplifier.
- Includes mobile mounting bracket.

ADDITIONAL SPECIFICATIONS

FREQUENCY COVERAGE: 3490-4010kc, 6990-7310kc, 13890-14410kc. SSB EMIS- SIONS: LSB 80 and 40 meters, USB 20 meters. RF POWER INPUT: 200 watts SSB PEP and CW, 100 watts AM. RF POWER OUTPUT: 120 watts SSB PEP and CW, 30 watts AM. OUTPUT PI NETWORK MATCHING RANGE: 40-80 ohms. SSB GEN- ERATION: 5.2 Mc crystal lattice filter; bandwidth 2.7kc at 6db. STABILITY: 400 cps after warm-up. SUPPRESSION: Carrier-50db; unwanted sideband-40db. RECEIVER: Sensitivity 1uv for 10db S/N ratio: selectivity 2.7kc at 6db; audio output over 2 watts (3.2 ohms). PANEL CONTROLS & CONNECTORS: Tuning, Band Selector, AF Gain, RF Gain, MIC Gain with calibrator switch at extreme CCW rotation, Hair- line Set (capped), Mode (SSB, AM, CW, Tune), Function (Off, Standby, PTT, VOX), Carrier Balance, Exciter Tune, PA Tune, PA Load, Receiver Offset Tune, MIC input, phone jack. REAR CONTROLS & CONNECTORS: VOX Threshold, VOX delay, VOX sensitivity, Anti-VOX sensitivity, PA Bias adjust, S-Meter zero adjust, power socket, external relay, antenna connector, key jack, accessory calibrator socket. METERING: PA cathode on transmit, S-Meter on receive. SIZE (HWD): 5 $\frac{3}{8}$ " x 14 $\frac{1}{4}$ " x 11 $\frac{1}{4}$ ". POWER REQUIREMENTS: 750 VDC at 300 ma, 250 VDC at 170 ma, -100 VDC at 5 ma, 12.6 VAC at 3.8 amps.

The Model 753 is an outstanding value factory-wired at \$299.95.

EICO

For FREE Catalog and 753 Spec. Sheet write to EICO Dept.
CQ-12, 131-01 39th Ave., Flushing, N. Y. 11352

For further information, check number 6, on page 106



ZERO BIAS

As the year 1965 approaches an end, I find myself with a lot of random thoughts about *CQ* and ham radio, many of which could be the basis of a full-blown editorial. But lacking the room to fully expound upon the wonders of the ham world, bear with me as I wander aimlessly through my thoughts . . .

1965 saw the delivery of every last one of the long-promised Arne Trossman Top Honors CHC Plaques. Contrary to K6BX fabrications, *CQ* was not about to force plaque winners to purchase their own awards . . . FCC Docket 15928 will probably go unrulled on for most of 1966. The sometimes angry and well-researched commentaries on the proposal by hundreds of amateurs have evidently given the Commission a vast number of new views to consider. My guess is that a second, more palatable proposed rule-making will be offered up by next fall . . .

Whatever happened to the Institute of Amateur Radio (frequently referred to as the W2NSD Benevolent Society)? Great promises were made for a new order in amateur radio, but it seems that none have materialized. Where's the money? . . .

Some great publicity recently for ham radio in New York: Station WHN (50,000 watts, 1050 kc, New York) featured "H for Ham Radio" on its "Information From A to Z" series Oct. 27 and 28. Tapes of the 6½ minute broadcast (prepared by the *CQ* staff) are available in very limited quantity from *CQ* for a 3½" reel of good recording tape and return postage. Permission has been granted for other stations to use the tape after proper editing . . . And speaking of publicity, "The Bedford Incident" publicity tie-in for ham radio, announced last month, is doing a fantastic job in all parts of the US except our own New York City area. A few clubs such as the Westchester ARA have tackled the job locally, but most remain cool to the idea. Can't figure out why, when reports coming in from coast-to-coast indicate stations being set up in the lobbies of over 125 theaters by November 10. If you missed last month's ZERO BIAS, dig out November's *CQ* and read it . . .

Congratulations to EICO on their 20th Anniversary. It's no mean feat to compete for 20 years in the radio and electronic business. Ask our publisher, he's been at it for 21 years now with *CQ* . . .

Two live-wire groups have come into their own in 1965: The International Amateur Radio

Club (IARC), and the fledgling National Award Hunters Club (NAHC). IARC is based in Geneva and is most ably directed by John Gayer, HB9AEQ. The club's station, 4U1ITU at ITU Headquarters needs no introduction. IARC is dedicated to improved international understanding through amateur radio, and improved international understanding of amateur radio through personal diplomacy. I'd be hard put to name a man I'd rather see represent ham radio internationally than HB9AEQ. Membership is open to all amateurs . . .

The NAHC is a group of dedicated wallpaper seekers who have joined together to pursue this exciting hobby-within-a-hobby in a progressive and unencumbered manner—unencumbered by the self styled "fearless leader," K6BX, that is. The 200 member club was formed in January of this year by WB2FEQ and WA2SAZ, who were promptly drummed out of CHC by K6BX for daring to take issue with his policies. NAHC President is WB2FEQ. Membership is open to all amateurs, and with membership goes the right to vote for the men who will guide the club's policy. A monarchy is thus a practical impossibility, unlike CHC . . .

Project OSCAR has been honored for its efforts in promoting peaceful international communication among radio amateurs, by the Institute of International Communications of Genoa, Italy. On Columbus Day, Oct. 12, the "Christopher Columbus Award" was received for Project OSCAR by W6SAI and W6UF. OSCAR IV is now being readied for launch. For late information on what form the new satellite is likely to take, see page 83.

The year 1965 has witnessed a tremendous rate of growth in the number of *CQ* achievement awards issued. The WAZ Rolls increased by about 280, WPX gained 130 and USA-CA surprised us all with nearly a 50% increase in awards to 696, up from 479 last year. That alone is enough to make one wonder about the true value of K6BX's high pressure PR tactics. Space prevents us from including the WPX Honor Roll this month, but it will appear in January.

We'd like to take this opportunity to wish the thousands of fine folks that read *CQ* a Very Merry Christmas, from all the people who have the pleasure of preparing it for you each month: Bill, W2AEF; Al, K2EEK; Irv Tepper; Hal, WA2OBR; Dick, WA2LRO; Jack, WA2FPE; Marcia; and myself. 73, Dick, K2MGA



PRESENTING THE COMPLETE



MARK I LINEAR AMPLIFIER


Five Band, 2000 watts PEP input. Uses two Eimac 3-400z or two Amperex 8163 triodes.

PRICE \$425
TUBES \$ 68

SWANTENNA 5 BAND MOBILE ANTENNA

Remote switching from inside car. 500 watt rating.

MODEL 55 . . . \$95

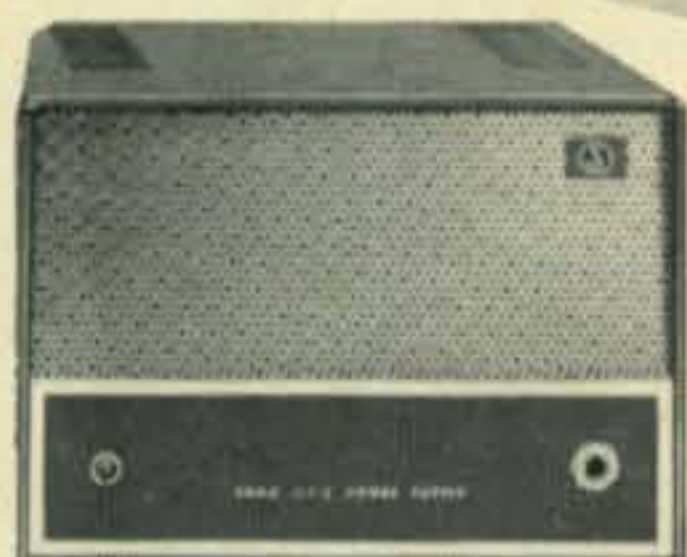

MATCHING AC SUPPLY

with speaker, phone jack.

MODEL 117-XC \$85

MODEL 230-XC
for 230 volts \$95

DC MODULE Converts AC supply to 12 volts DC for portable or emergency operation.

MODEL 14X \$55



12 VOLT DC SUPPLY

For mobile or portable operation. Negative ground standard. Positive ground available on special order.

MODEL 14-117 . . . \$120



MODEL 400 SSB TRANSCEIVER 5 BANDS 400 WATTS

Includes many deluxe features. Designed to use the highly stable, full coverage Model 420 VFO in fixed station, the miniature Model 406 VFO for mobile, or the Model 405 for MARS operation.

\$399

PLUG-IN VOX UNIT

for either
transceiver

MODEL VX-1 \$35

CRYSTAL CALIBRATOR

KIT \$199

SIDEBAND SELECTOR

KIT \$

Kits for Model only. Model 40 includes these features

SWAN SPEAKS YOUR LANGUAGE

ASK THE MAN WHO OWNS ONE

SWAN LINE



MARS OSCILLATOR

5 fixed channels, pre-set and locked to any frequency. May be used directly with Model 400 Transceiver or with Model 350 and Model 22 adaptor.

MODEL 405 \$45



MOBILE VFO

Miniature size. Covers phone bands. Makes it possible to trunk mount the transceiver.

MODEL 406 \$75

REMOTE CONTROL KIT

For trunk mounting of transceiver.


MODEL RC2 \$25



MODEL 350 SSB TRANSCEIVER 5 BANDS 400 WATTS

Built in full coverage VFO with 5 kc calibration. The greatest transceiver value ever offered the radio amateur.

\$395

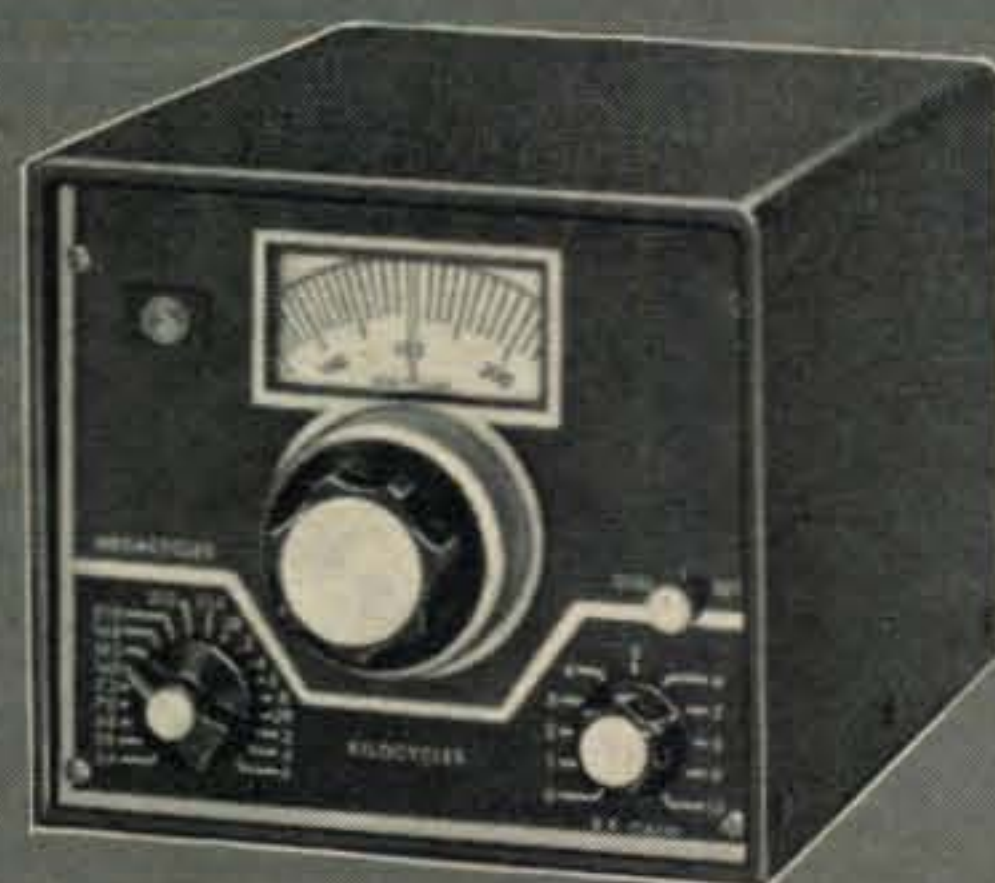

FULL COVERAGE VFO

20 ranges, 200 kc each, 2 kc calibration. Matches 350 and 400 transceivers in size & styling.

MODEL 420 \$120

DUAL VFO ADAPTOR

Provides for the addition of second VFO for separate control of transmit and receive frequencies. May plug into either 350 or 400 transceiver.

MODEL 22 \$25

**Merry
Christmas**

from all the gang

at SWAN


For further information, check number 9, on page 106

FOR COMPLETE
INFORMATION
SEE YOUR DEALER



ELECTRONICS CORP.
Oceanside, California

Designed for

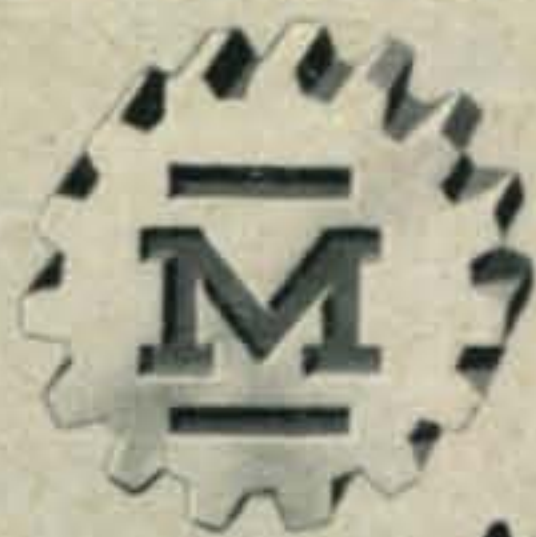

Application



**The No. 90651
GRID DIP METER**

The No. 90651 MILLEN GRID DIP METER is compact and completely self contained. The AC power supply is of the "transformer" type. The drum dial has seven calibrated uniform length scales from 1.5 MC to 300 MC plus an arbitrary scale for use with the 4 additional inductors available to extend the range to 220 kc. Internal terminal strip permits battery operation for antenna measurement.

**JAMES MILLEN
MFG. CO., INC.**

MAIN OFFICE AND FACTORY
**MALDEN
MASSACHUSETTS**



Ham Fellowship

AMATEUR Radio to me means Fellowship, pure and simple. Oh, of course, it means other things, too. Like being the most engrossing and enlightening hobby I've ever been engaged in; educational, too.

I'm proud to call myself a member of this grand and glorious fraternity—this fraternity of fellowship and good will. In all my association with Amateur Radio I can say without reservation, I have yet to meet an 'unfriendly ham.'

The following incident, which is by no means incidental, will further attest to the fact that this is true fellowship.

Several months ago, the XYL and I were involved in a near fatal auto accident. After a month of confinement in the hospital, I came home to find a whole new antenna farm planted out in my back yard and on my desk in the ham shack was an SB-33 Transceiver—to supplement my limited one-band ARC-5—ready to go, mine to use and enjoy for the duration of my convalescence! All this, compliments of the Fresno Amateur Radio Club. I can't praise this organization too highly. To give so unselfishly of their time, efforts and treasured equipment is truly an expression of fellowship.

Small wonder why I hesitate not to extend this testimonial to Amateur Radio. *WB6ETR*

Israeli Licensing

ANUMBER of license changes have been made in Israel during the past few years and especially this past year. For any ham planning a vacation in Israel with some intention of firing up his rig during his stay, should read the following and act accordingly.

1. Any foreign ham can operate a station in Israel (his own or an Israeli station) by applying directly to the Ministry of Posts. Address: Ministry of Posts, (Posts, Telegraph, Telephones and Radio), 37 Yehuda Hayamit Street, Jaffa, Israel.

2. The request for permission to operate in Israel must contain the following: a photostatic copy of the ham's license, a statement relating to length of intended operation, *e.g.*: Sept. 1st, 1965 until Nov. 1st, 1965. Intended QTH, *e.g.*, Telaviv, Haifa, etc. If mobile operation is intended, this must also be mentioned at the same time of application.

3. So far, foreign hams have not been charged for a temporary license. (Israeli hams are charged \$3.00 for a 2 year license.)

There are 3 types of licenses issued (aside from club stations):

A—Class A (equivalent to U.S. Extra Class), permitted up to 500 watts input.

B—Class B (equivalent to U.S. General Class), permitted up to 75 watts input.

C—Class C (equivalent to U.S. Novice Class), permitted up to 10 watts, c.w. only, and limited to the 40 meter band.

Tnx 4X4FV.


NEW FROM INTERNATIONAL

VHF/UHF UNITIZED TRANSMITTERS 50 mc—420 mc


International's new unitized VHF/UHF transmitters make it extremely easy to get on the air in the 50-420 mc range with a solid signal. Start with the basic 50 or 70 mc driver. For higher frequencies add a multiplier-amplifier. All units are completely wired. Plug-in cables are used to interconnect the driver and amplifier.



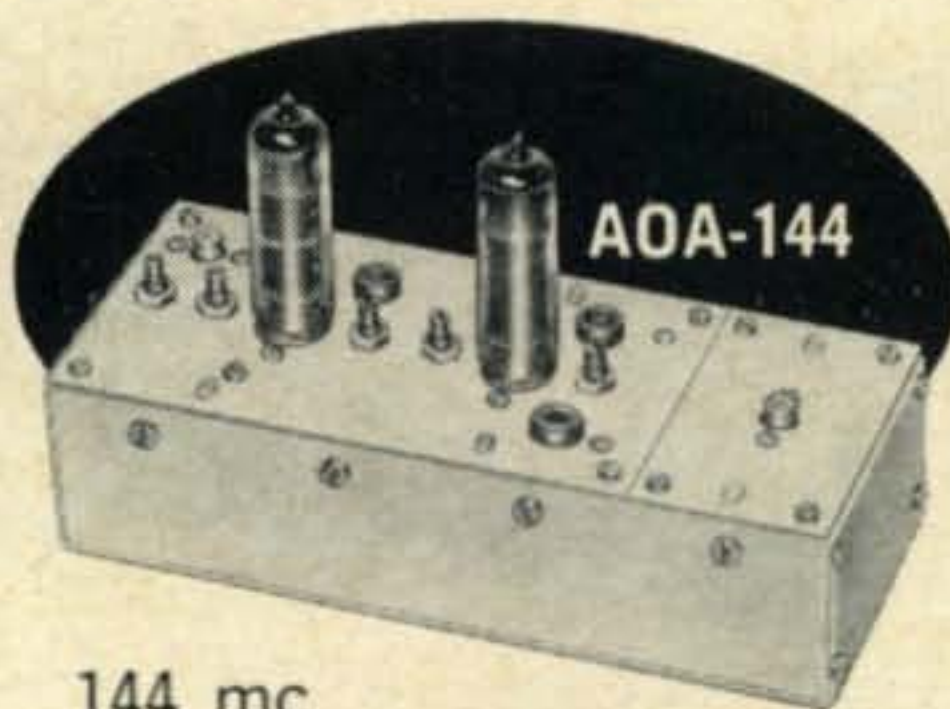
AOD-57
50 or 70 mc
DRIVER/TRANSMITTER
The AOD-57 completely wired with one 6360 tube, two 12BY7 tubes and crystal (specify frequency). Heater power: 6.3 volts @ 1.2 amps. Plate power: 250 vdc @ 50 ma.
AOD-57 complete.....\$69.50



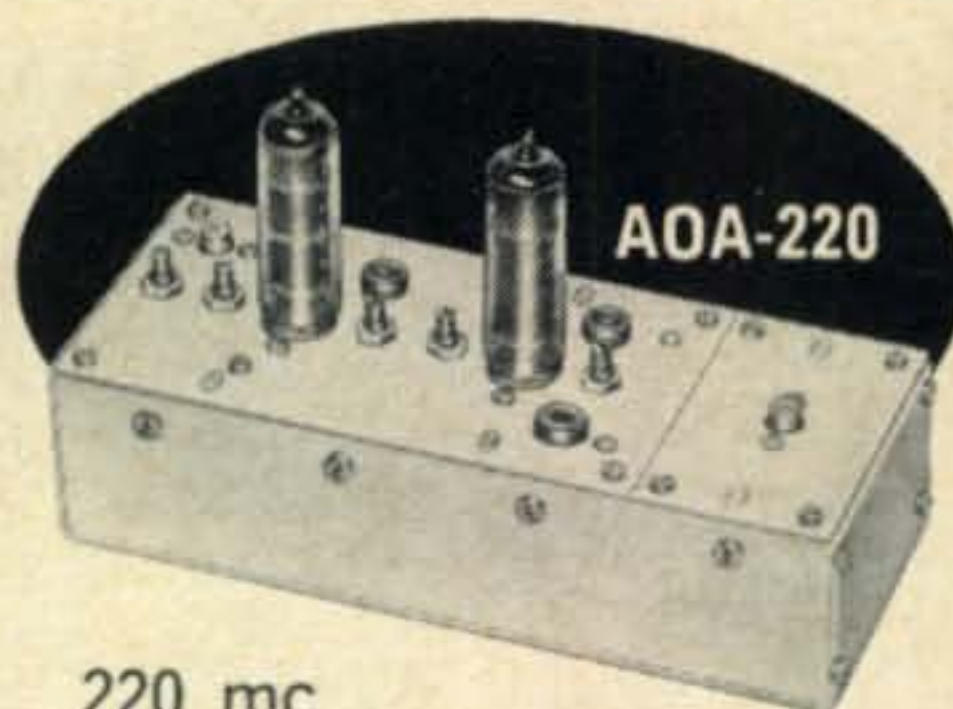AOA-144
144 mc
MULTIPLIER/AMPLIFIER
The AOA-144 uses two 6360 tubes providing 6 to 10 watts output. Requires AOD-57 for driver. Heater power: 6.3 volts @ 1.64 amps. Plate power: 250 vdc @ 180 ma.
AOA-144 complete.....\$39.50



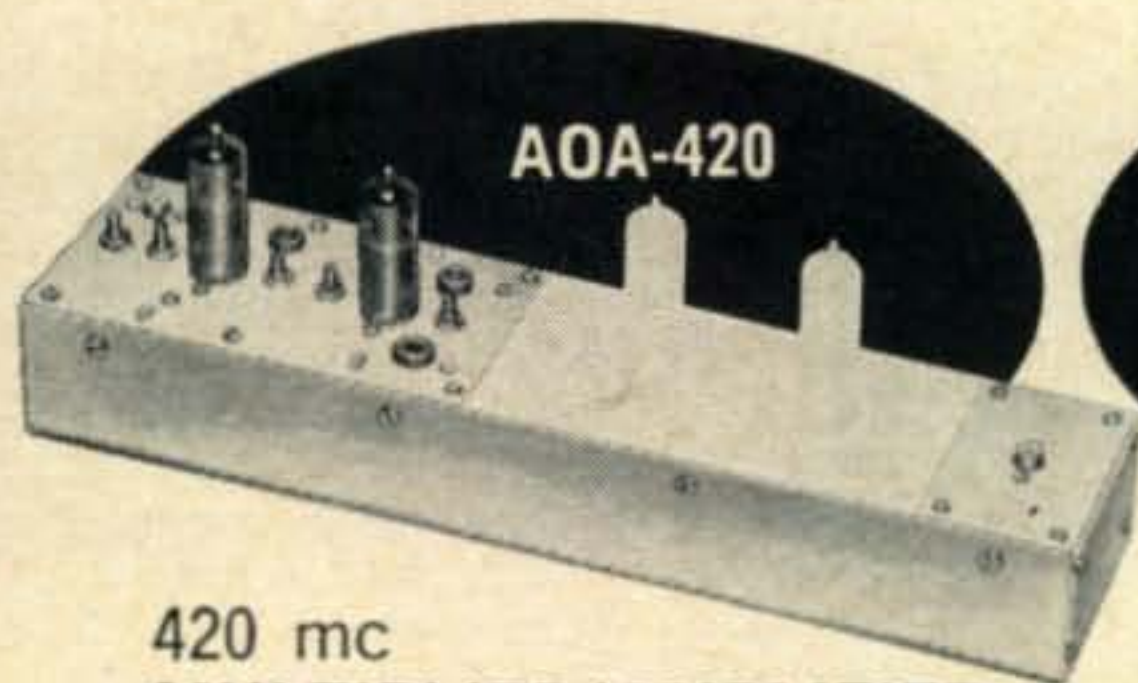AOA-220
220 mc
MULTIPLIER/AMPLIFIER
The AOA-220 uses two 6360 tubes providing 6 to 8 watts output on 220 mc. Requires AOD-57 for driver. Heater power: 6.3 volts @ 1.64 amps. Plate: 250 vdc @ 150 ma.
AOA-220 complete.....\$39.50




AOA-420
420 mc
MULTIPLIER/AMPLIFIER
The AOA-420 uses two 6939 tubes providing 4 to 8 watts output on 420 mc. Requires AOA-57 plus AOA-144 for drive. Heater: 6.3 volts @ 1.2 amps. Plate: 220 vdc @ 130 ma.
AOA-420 complete.....\$69.50



ARY-4
RELAY BOX
Four circuit double throw. Includes coil rectifier for 6.3 vac operation.
ARY-4 Relay Box
complete\$12.50



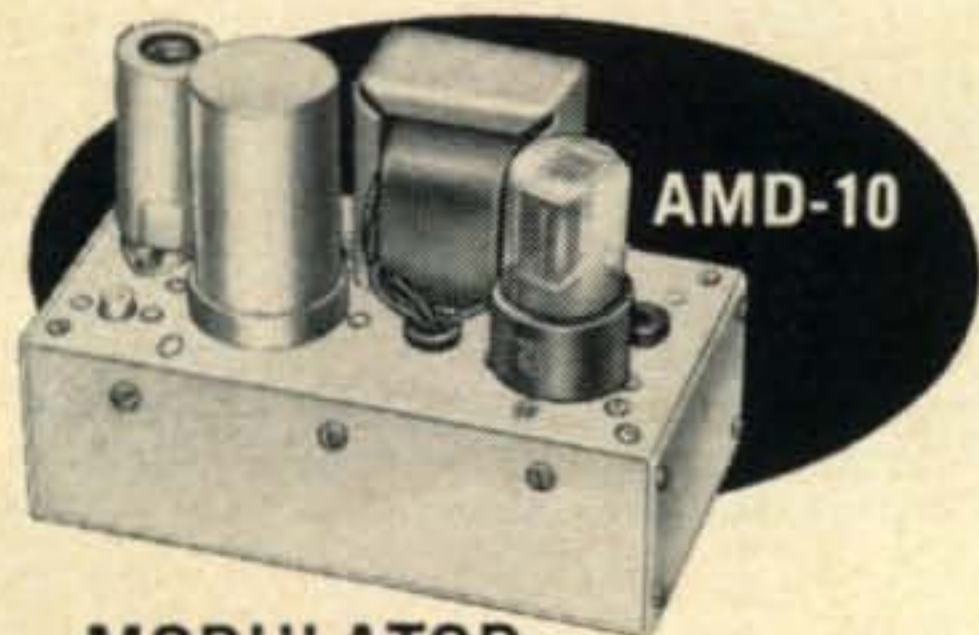APD-610
FILAMENT SUPPLY
The APD-610 provides 6.3 vac @ 10 amperes.
APD-610 complete.....\$9.50



AMD-10
MODULATOR
The AMD-10 is designed as a companion unit to the AOA series of transmitters. Uses 6AN8 speech amplifier and driver, 1635 modulator. Output: 10 watts. Input: crystal mic. (High Imped.) Requires 300 vdc 20 ma, no signal, 70 ma peak: 6.3 vac @ 1.05 amps.
AMD-10 complete\$24.50

COMPLETE TRANSMITTER

6 METERS	50 mc	AOD-57
2 METERS	144 mc	AOD-57 PLUS AOA-144
	220 mc	AOD-57 PLUS AOA-220
	420 mc	AOD-57 PLUS AOA-144 PLUS AOA-420

**INTERNATIONAL
CRYSTAL MFG. CO. INC.**
18 NORTH LEE — OKLA. CITY, OKLA.

Order Direct
from International


For further information, check number 11, on page 106

ROHN

sets the standard

for CRANK-UP TOWERS

Why settle for less than the best?

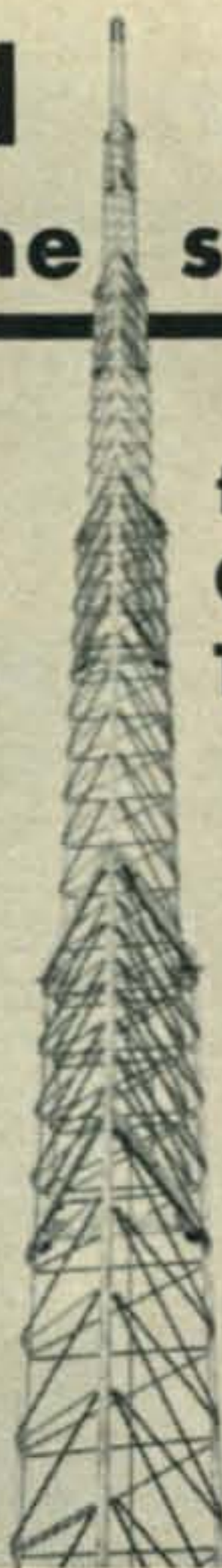

TWO CATEGORIES TO CHOOSE FROM

Standard Duty Guyed in
Heights of 37 - 54 - 88 - 105
and 122 feet

Heavy Duty Self Supporting
and Guyed in Heights of
37 - 54 feet (SS)
71 - 88 feet (guyed)

ROHN has these 6 IMPORTANT POINTS:

Ease of Operation—roller guides between sections assure easy, safe, friction-free raising and lowering. **Strength**—welded tubular steel sections overlap 3 feet at maximum height for extra sturdiness and strength. Unique ROHN raising procedure **raises all sections together**—uniformly with an equal section overlap at all heights! **Versatility**—designed to support the largest antennae with complete safety and assurance **at any height desired!** **Simple Installation**—install it yourself—use either flat base or special tilting base (illustrated above) depending on your needs. **Rated and Tested**—entire line engineered so you can get exactly the right size and properly rated tower for your antenna. The ROHN line of towers is complete. **Zinc Galvanized**—hot dipped galvanizing a standard—not an extra—with all ROHN towers! Prices start at less than \$100.

SEND FOR ROHN TOWER HANDBOOK

—\$1.25 Value

—**ONLY \$100** postpaid (special to readers of this magazine). Nearest source of supply sent on request. Representatives world-wide to serve you. Write today to:



ROHN Manufacturing Co.

P. O. Box 2000

Peoria, Illinois

"World's Largest EXCLUSIVE Manufacturer of Towers; designers, engineers, and installers of complete communication tower systems."

For further information, check number 12, on page 106

12 • CQ • December, 1965

LETTERS TO THE EDITOR



The Bedford Incident

Editor, CQ:

After reading the leading item in ZERO BIAS in the November issue, I felt constrained to write and share with fellow hams my own rather shattering experience in a similar set-up.

My shack was prominently quartered in the lobby of one of the most modern movie palaces in a large resort town. The manager of the theater was most co-operative in every way, and I felt certain that I would be exposing the face of Amateur Radio to the public in its best possible light, and that this would impel the aforementioned public to clasp Ham Radio to its collective bosom.

I arranged with a friend nearby to borrow his brand new Collins S-Line, and got a crew of three others to help with the antenna installation. We erected a twenty foot mast, rotator and tri-band beam, together with a pair of half-wave dipoles for 40 and 80 meters. Late that night after the last show, we established contacts on all bands and ascertained that our v.s.w.r. was optimum, ranging from unity match to no more than 1.7 to 1. It seemed that everything was just about as perfect as could be, and that our exhibition could not fail to live up to our great expectations.

The theater was literally packed with patrons. The picture was scheduled to start at 7 P.M., and we fired up at 6 o'clock. At 6:15 we started passing the traffic, and were gratified to see a rather long queue of prospective customers. Afterward, we tried to reconstruct the chronology of the thing just as it happened. When the curtains opened and the newsreel went on, we still had about a dozen people in line. We continued with the traffic in a normal fashion. Suddenly we were aware of peculiar sounds coming from the direction of the theater auditorium. A group of uniformed ushers converged like a flight of geese toward our corner of the lobby. Two assistant managers and a security policeman raced toward us. A gaggle of hysterical citizens, irate and abusive, made threatening gestures.

Was this the same group of co-operative, enthusiastic souls who had given their blessing a short half hour ago?

We checked our cable to make sure that we had remembered to install the low-pass filter. Yes, everything was in order. But was it? We shut down, not wishing to compound the situation. A quick phone call to the emergency number of the company which had installed the sound equipment at the theater disclosed the fact that the system had not been filtered.

A classic case of MPI (Motion Picture Interference). That was the end of the noble experiment. We sadly dismantled the station, and slunk away into the darkness, unwept, unsung.

I can hear, in my mind's ear, that menacing snarl, amplified a thousand fold. I can see, in my mind's eye, that threatening and ugly mob, magnified into a multitude.

ASTATIC offers **2** new SUPER TALK POWER MIKES



for CB, Ham and other communications

Model 531

A top performer at low cost. Response characteristic carefully calculated to give maximum clarity and intelligibility; minimizes interference in adjacent channels.

Model 539

A high quality true noise cancelling microphone with lip guard positioning at low, low list. Features 360° differential cancellation of background noise for sharp, clear speech. Lip bar maintains uniform close spacing necessary for consistent modulation and maximum cancellation.

Both microphones high output —50 db. Hi-Z ceramic element has wide temperature tolerance and immune to humidity. Completely shielded for minimum hum pickup. DPDT switch gives both signal and relay control. High impact case has rectangular hangup bracket — will not rattle or scratch mounting surface.




*See your distributor
or write us for
complete information.*

ASTATIC CORPORATION CONNEAUT, OHIO 44030 U. S. A.

In Canada: Canadian Astatic Ltd., Toronto, Ontario

Export Sales: Roburn Agencies, Inc., 431 Greenwich Street, New York 13, N. Y., U. S. A.

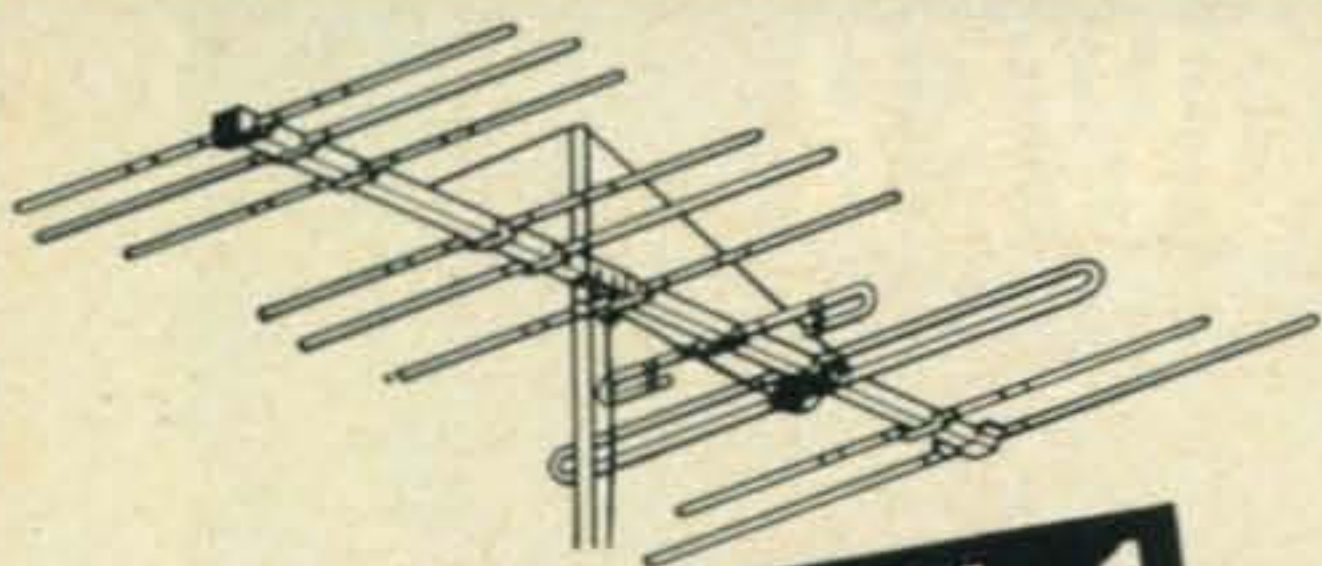FINCO 6 & 2 Meter Combination Beam Antennas




2 ANTENNAS in 1

MODEL A-62 · 300 OHM

On 2 Meters:	On 6 Meters:
18 Elements	Full 4 Elements
1-Folded Dipole Plus Special Phasing Stub	1-Folded Dipole
1-3 Element Colinear Reflector	1-Reflector
4-3 Element Colinear Directors	2-Directors

Amateur Net \$33.00
Stacking Kit \$2.19

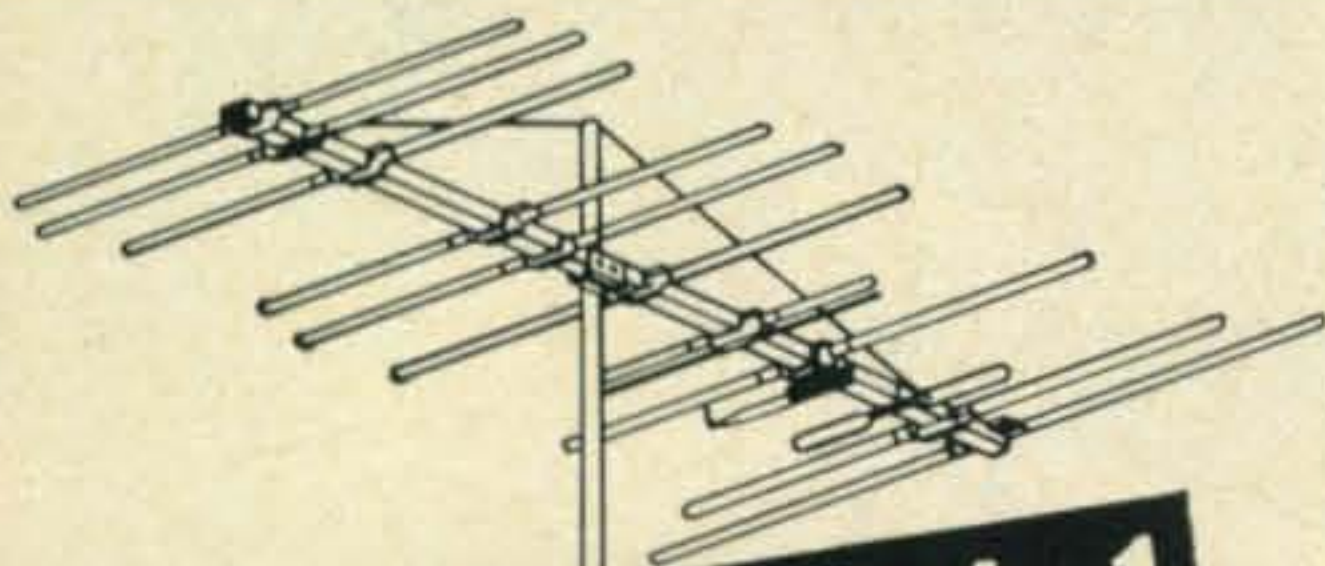

2 ANTENNAS in 1

MODEL A-62 GMC · 50 OHM

On 2 Meters:	On 6 Meters:
Equivalent to 18 Elements	4 Elements
1-Gamma-Matched Dipole	1-Gamma-Matched Dipole
1-3 Element Colinear Reflector	1-Reflector
4-3 Element Colinear Directors	2-Directors

Amateur Net \$34.50
Stacking Kit \$18.00

MODEL AB-62 GMC

On 2 Meters:	On 6 Meters:
Equivalent to 30 Elements	Equivalent to 6 Elements

Amateur Net \$52.50

Also:

- 5 New 6 Meter Beams
- 3 New 2 Meter Beams
- 1 New 1 1/4 Meter Beams

Gold Corodized for Protection Against Corrosion
See Your Finco Distributor or write for Catalog 20-226

The FINNEY Company - Bedford, Ohio

I can see the formation of ad hoc committees, demanding Congressional Investigations. I can imagine Mayors, Aldermen, Councilmen, Committeemen, Freeholders and Busgesses, seeking local injunctions against Amateur Radio within town limits. I can smell the acrid tar, bubbling merrily away, and I can see the slit-open pillows, ready to disgorge their content of eiderdown.

Please, fellows, if you do get in on "The Bedford Incident" make sure that the sound system of the theater is adequately filtered. Run some tests while the projectionist is operating, otherwise you may regret the whole thing.

Dave Mann, K2AGZ/K3WOO
1 Daniel Lane
Kinneton, N.J. 07405

The National Award Hunters Club

Editor, CQ:

The Arne Trossman Top Honors Plaque arrived at my QTH a short while ago. I can't express the thrill I had upon receiving the plaque—you and CQ are to be congratulated for the fine work of following up on this award. It already hangs in the shack right above the trophy I received for the World High score in the 1963 CQ 12 Hour VHF Contest.

I am no longer a CHC'er, having resigned to CHC President WA2PWI on Jan. 19, 1965, contrary to reports published by K6BX that I was "kicked out" of CHC on Feb. 25, 1965. My XYL Louise, WA2SNT, also resigned on that date, but is still carried on the CHC Membership rolls. Perhaps if CHC President WA2PWI/WA1AKE/WB2FTQ (they're all his!) would be more precise in doing his duty, this situation could have been avoided.

I also want to thank you and W2GT for the write-up of the "National Award Hunters Club" in Sept. CQ. Our membership has grown by leaps and bounds—200 members in seven months—and includes 5 Top Honors winners and represents five countries.

The current *Xtra* [sic] *News Letter* (K6BX Editor/Publisher) contains an item claiming that NAHC is being sued by Europe's AHC (Award Hunters Club). On the contrary, we have been pleased to receive a letter of congratulations from AHC General Secretary John Velamo, OH2YV, on the formation of an awards club free of ties with K6BX.

Again, thanks for the Top Honors Plaque and the support given to NAHC.

Harry "Smitty" Smith, WA2SAZ
108-24 71st Avenue
Forest Hills 75, N. Y.

RTTY From A to Z

Editor, CQ:

The record seems to show that fine authors of articles such as Durward Tucker's "RTTY From A to Z" series get little enough recognition. My point here is simply to say my own thanks for the tremendous job he has done, and to hazard the guess that the woods are full of grateful RTTY hams like me.

To duffers like me, RTTY is an endless source of wonder and joy, and as a retired attorney, I have plenty

R FOR LATE MAIL

Is your mail tired and lagging behind? Add a little zip to your mail by liberally applying your ZIP code number to all correspondence. The results will amaze you.



SBE

**a KW ssb
station**

**only 64½
cents per watt**

The brilliant new **SB-34**, SSB 4-band transceiver serves as your receiver and exciter... the new matching **SB2-LA** Linear furnishes the big bang! This advanced design power combo costs you only 644.50, unquestionably the lowest cost per watt obtainable! But this is only part of the value story. **SB-34** has a **built-in power supply, 117V AC and 12V DC**... needs no separate inverter... connects directly to the 12V car battery when you want the added pleasure of 4-band mobile transceiver operation. **There's just no comparable value!**

SB2-LA LINEAR AMPLIFIER . . 249.50

Husky, heavy-duty, with 1KW P.E.P. input capability on 80-40-20-meters, 750 watts on 15 meters, this exceptionally compact amplifier matches SB-34 in general size and appearance. Operates perfectly with SB-34 but can boost the output of any SSB exciter to a full KW. AC power supply is built-in.

4-bands, 80, 40, 20, 15 meters • Full band switching • Passive grid input for resistive load to exciter. Drive: 60W or more depending upon the linear amplifier power output • Low plate voltage (800 volts) and high plate current • Easier on capacitors, rectifiers, power transformers • Safer under environmental extremes • High filter capacity for dynamic regulation • Built-in antenna relays (2), internal blocking bias • HI/LO power and TUNE/OPERATE switches • Panel meters for output and plate current • Six parallel-connected 6JE6's are used in amplifier • 115V AC power supply (built-in) is all-solid-state. Size: 5¼"H, 11¾"W, 11⅝"D. Wgt, 35 lbs. (apprx).


SB-34 TRANSCEIVER 395.00

New... advanced... with important plus performance features! Transistors and diodes replace vacuum tubes (except for the 2-6GB5's in PA and 12DQ7 in RF driver) — equipment size is reduced greatly — current drain lowered substantially. Example: **SB-34** draws only 500 ma on receive standby.

Built-in supply for 12V DC and 117V AC • Power input: 135 watts P.E.P. (Slightly lower on 15 meters) • Frequency range: 3775-4025 kc, 7050-7300 kc, 14.1-14.35 mc, 21.2-21.45 mc • 23-transistors, 18-diodes, 1-zener, 1-varactor, 2-6GB5's PA, 1-12DQ7 driver • No relays — solid state switching — breakthrough! USB or LSB selectable by panel switch • Collins mechanical filter — transmit/receive • Delta receiver tuning • Solid-state dial corrector • prewired for VOX/100kc calibrator accessories — both units are optionally available. Single-knob dual-speed tuning. Size: 5"H, 11¼"W, 10"D. Weight 20 lbs. (Approx).

SIDEBAND **SBE** ENGINEERS

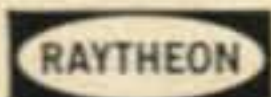317 ROEBLING ROAD, SOUTH SAN FRANCISCO, CALIF.



Export sales: Raytheon Company, International Sales & Services, Lexington 73, Mass, U.S.A.

For further information, check number 15, on page 106

FOR MOBILE VERSATILITY

A MOBILE
ANTENNA
FOR EVERY
INSTALLATION

The most versatile, complete line of mobile antennas for the amateur market. Complementing the well known line of standard Heliwhips (160 through 6 meters) are the tri-band HW-3, which with accessory elements permits instant choice of three of the bands from 80 thru 10 meters; and the KW line of high power Heliwhips for 40 through 10 meters. Also, the HWD line of portable or fixed station short dipoles for 40 through 10 meters, 8 to 16 feet long, rated 1 KW. CV-3147, CVS-2144 fixed and mobile 2 meter gain verticals.



GO PRO GO MARK

MARK PRODUCTS

DIVISION OF DYNASCAN CORPORATION

5439 W. FARGO AVE. • SKOKIE, ILL. 60076 • (312) OR 5-1500

of time to enjoy the everpresent possibilities.

It may well be that RTTY owes its power to generate much of its thrill to the devotion given it by Mr. Tucker and other top hams. There's Merrill Swan, Bob Weitbrecht, Herb Hoover, Wayne Green, Irv Hoff, Mr. RTTY in Michigan, Ralph Leland, and locally, Ed Koch who make RTTY the unparalleled ham activity it is. Thanks to Ralph and Ed the state of Michigan leads in RTTY activity and Midland County leads the state in "RTTY Bugs."

As I sit here enjoying the added knowledge of the art of RTTY you have so generously imparted, my wish to you would be that a thousand more of us would write you and extend our deep thanks.

C. E. Price, W8HPR
Pinewood Farm
Hemlock, Mich.

The Big Radiation Controversy

Editor, CQ:

I have read the letter by SP4 Gerald V. Griffith (LETTERS, Sept.) relative to the big controversy about K8IKA ("Learn By Mistakes," May, CQ) and the reaction he received. Gerald makes several statements which are not true and some assumptions which I do not believe can be substantiated.

In talking of conduction heating, he transfers from inorganic metals to biologic material, some physical facts, and such a transfer cannot be made. The skin effect on a wire or piece of metal is not the same as the skin resistance of the human body. There is a dissipation of r.f. energy in the body which does not take place to the same degree in metal, even in a so-called chassis ground. His wet finger and thumb is still much smaller than the area of mucus membrane in the mouth; and by his theory, all energy went through these points without a burn, yet the small amount which reached the fillings in the teeth was sufficient to cause a burn. I don't believe it.

In Glassers big two volume *Medical Physics* the subject of "Conduction Heating" is not even mentioned. I do not believe it occurs in biological material.

Ultraviolet burn is not a thermal burn; it is frequency dependent, and only certain wave lengths will cause damage. Sunburn is due to ultraviolet, not thermal effect.

X-ray reactions are also not thermal burns, nor are they ultraviolet burns, but are due to ionizing radiation, that is gamma rays, or beta rays, and with some isotopes, alpha rays. Since ionization cannot occur below a voltage of about 15 kvp, this type of reaction can be ruled out.

Harold W. Morgan, M.D., KØJTP
1312 Fourth S.W.
Mason City, Iowa

Sugar Coated Metering

Editor, CQ:

Mr. DeMaw, W8HHS, went a bit too far in "Sugar-Coated Metering" in the Sept. issue. This method is fine as long as the meter series resistor is at least 50 times as large as the series resistor across which the voltage drop is developed—that is, down to 50 ma full scale for the 1 ma movement discussed. The error will then not exceed the 2% uncertainty inherent in the meter.

Any attempt to increase the sensitivity beyond this point will result in low reading, however. In Chart 2, for instance, it is evident that when the meter reads full scale there will be 5 ma through the 500 ohm resistor plus 1 ma through the shunting meter for a total of 6 ma, or a 20% error on the low side. Similarly, the error is 10% at 10 ma full scale and 4% at 25 ma full scale.

If round-value resistors, such as 500 ohms, are to be used, accurate measurements on ranges below 50 ma demand a 100 microamp movement.

Remsen T. Schenck
Franklin Hill Road
RFD 3, Bangor, Pa. 18013

Used Callbooks

Editor, CQ:

The other day a DX station asked me if I had an old USA *Callbook* which I no longer needed and if so, would I be willing to send it to him. I did not have one but was able to obtain one from a friend and am sending it to this station along with a DX *Callbook* which I am replacing currently. This gave me an idea. I am sure there are numerous *Callbooks* passed from hand to hand and eventually discarded. I am equally certain there are deserving

For further information, check number 16, on page 106



**This HF Single Sideband Transceiver
meets Full Military Requirements
and is available off-the-shelf
at a commercial price.**

It is the RF Communications Model RF-301

Now nomenclatured AN/URC-58

The Model RF-301, SSB Transceiver was designed by RF Communications as a company product without government support. It was designed to be used by military customers in military applications. Now in production, it can be bought in quantities from one unit up with short delivery (averaging 30 to 90 days) at a very modest price. The RF-301 costs about one-third of that normally paid for military transceivers with similar characteristics.

RF-301, SSB TRANSCEIVER

Brief Specifications

Frequency Range: 2 to 15 Mc
Synthesizer: Can be tuned to 1 Kc increments. Provisions for unlocking synthesizer and tuning continuously.
Power Output: 100 watts p.e.p. and average
Stability: 1 part 10^6 standard, 5 parts 10^8 optional
Modes: USB, LSB, AM, CW. Also FSK with adapter.
Power Input: 115/230 volts, 50/60 cycles standard. 12 or 24 volt DC with additional built-in module.
Size: 7 $\frac{3}{4}$ x 17 x 14 $\frac{3}{4}$ inches • **Weight:** 59 pounds

*Please contact us
for further details.*



R F COMMUNICATIONS, INC.

1680 UNIVERSITY AVENUE • ROCHESTER, NEW YORK 14610

For further information, check number 17, on page 106



THE UNIQUE

Joystick

VARIABLE FREQUENCY ANTENNA

The DX Antenna for
any QTH!

Hear and work that spicy DX with the Joystick—End the frustration of "hunk of wire" contacts—Now you can put out the kind of signal your

(as indicated) plus Joymatch Tuners—The complete systems listed below comprise deluxe or standard Joystick & everything else required apart from existing transmitter and/or receiver.

transmitter was designed to produce—yes, even from inside an apartment or home!

A lifetime of experience and antenna "know-how" has gone into the development of this revolutionary "Variable Frequency Antenna" on which World Patents are pending. Uniformly excellent performance on all bands from 160 thru 10 meters. The Joystick's special matching and feeding system insures top efficiency on any frequency. Complete systems are available for s.w.l.'s and mobile, too. Thousands of Joysticks are in use around the world. Flash! Indoor Joystick spans the earth on 3.5 mcs.

ZL4GA reports: I contacted G5WP on 3504 Kcs with INDOOR JOYSTICK and am REALLY AMAZED" (569 BOTH WAYS). W3AZR reports: QSO with W2EQS on 160. W2EQS was 589 on his 160M DIPOLE (the well known Atlantic Spanner!) and 56/79 on an INDOOR JOYSTICK 5' UNDERGROUND IN BASEMENT!!!!!!

SIZE 7'6"
VERTICAL
2-3 METRES

ORDER YOUR JOYSTICK NOW

Full money-back GUARANTEE if you're not completely satisfied.

Still not convinced? Complete the coupon for a detailed brochure and testimonials.

Please ship Joystick system checked below:

- Complete Deluxe Joystick Transmitting System (Shpg. to USA Incl.).....\$24.00
- Same as above, but Standard model\$21.15
- Complete Deluxe Joystick Receiving System (Shpg. to USA Incl.).....\$20.85
- Same as above, but Standard model\$18.00
- Complete Joystick Mobile System (Shpg. to USA Incl.).....\$21.10
- Please send brochures and testimonials.

Name.....Call.....
Address.....
City.....State.....Zip-Code.....

Partridge Electronics, Ltd.

PROSPECT RD. BROADSTAIRS, KENT, ENGLAND

For further information, check number 18, on page 106

18 • CQ • December, 1965


DX stations that cannot obtain *Callbooks* or cannot afford them. I would like to appeal to US hams to send me their outdated or retired *Callbooks*. I, in turn, would offer them to DX stations at no charge, perhaps on a priority basis to clubs and stations in remote parts of the world where the books are not readily available.

If you think this is a worthwhile idea could you help me by appealing to US *CQ* readers to send me their *Callbooks* which they no longer have use for (both US and DX books). I will pass them on to DX stations along with a note informing the recipient of the name, address and call of the donor.

Any comments, suggestions or assistance you might offer will be greatly appreciated.

Mike Grossman, K2JWM
19 Rockledge Road
Hartsdale, New York

Mike, the idea of sending used *Callbooks* to DX stations is certainly a great one, but I've got to dampen your pride a bit by saying that it's not a new thought. For over six years, our own HAM CLINIC doctor, Chuck Schauers, W6QLV (now residing in Luzern, Switzerland) has been soliciting used *Callbooks* for foreign distribution. Others, too, have lent a hand, including K6BX, but Chuck's been at it longest, and is in the best position to channel the books to needy hams. I suggest you drop him a line to see how you can work with him on this worthwhile project. His address is: 4 Lutzelmatt Strasse, Luzern, Switzerland.—K2MGA

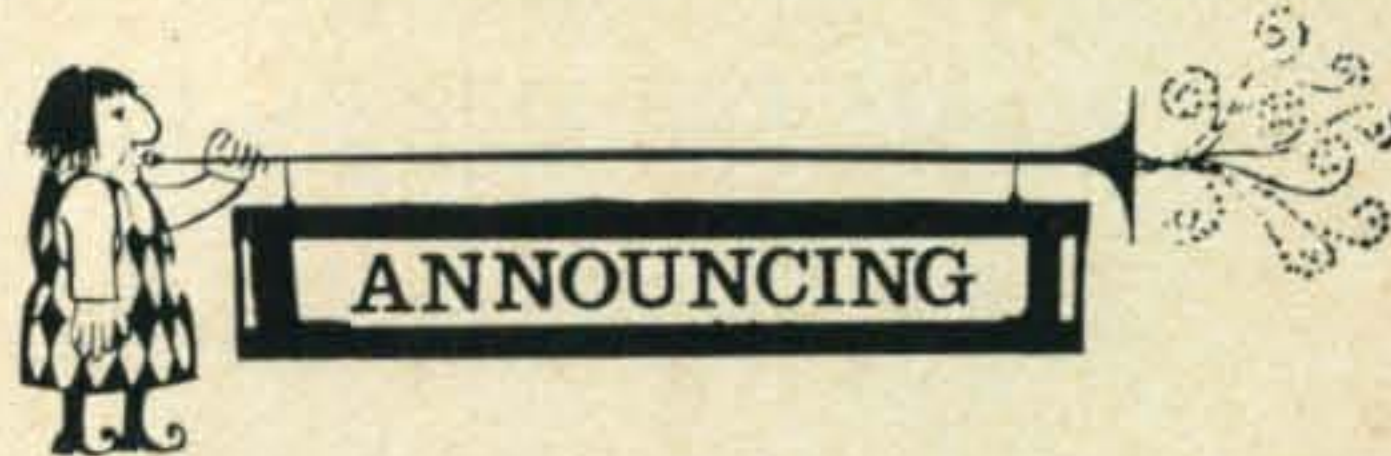

Berkeley, California

CQ ES QST de KPFA is the title of a new program on amateur radio presented each Sunday at 10:15 a.m. on KPFA (FM 94.1 mc). Gene Bergman, WB6IBU prepares the weekly program, which covers all aspects of amateur radio.

If you have had any interesting experiences as a ham operator, are a specialist in a particular category of ham radio (UHF, RTTY, DX, etc.) or would like to make comments or suggestions for the program, send your communication to WB6IBU, c/o KPFA, 2207 Shattuck Ave., Berkeley 4, Calif.

Gene, is a high school social science teacher and devotes his spare time to programming and preparing the weekly show. KPFA is a non-commercial station and derives all its revenue from listener support. Though not an employee of the station, Gene, spends between 8 and 12 hours a week getting the program together. The subjects of the program are geared strictly for the amateur: announcements of radio clubs, speeches recorded at hamfests and conventions, and general information from periodicals with occasional interviews keep the program interesting and timely.

New Rochelle, New York

The Communications Club of New Rochelle will hold its fifth annual dinner and ham get-together on Saturday evening, December 18, 1965 at the Davenport Club in New Rochelle. There will be prizes offered. For reservations (\$6.00 Each) and information contact Henry M. Wymbs, WB2GMN, 100 Joyce Road, Hartsdale, N.Y.

Correction


In the September issue on page 99, W5OMJ is listed as QSL Manager for VP2GL. W5OMJ is not the QSL Manager for VP2GL.

In the Oct. issue on page 55 under "Where You Can Get An APX-6", BC Electronics is listed as selling the unit used, with tubes, for \$17.00. BC Electronics, 2333 S. Michigan Ave., Chicago, notifies us that they only have used units, less tubes for sale at \$7.50 each.

EIMAC

3-400Z triodes power new Henry Radio 2 K linear amplifier


Henry Radio Co.'s new 2 K linear amplifier is sure to become a classic in its field. With an ultimate simplicity of design, it covers the 80, 40, 20, 15 and 10 meter bands for SSB, AM, CW, FM or RTTY. It provides Pi-L plate tank output circuit for maximum attenuation of unwanted harmonic output and resonant cathode input circuit for finest linearity and minimum drive requirement. The best possible performance was demanded of this new linear amplifier. That's why Henry Radio chose two rugged, original design Eimac 3-400Z grounded grid triodes. Designed especially for zero-bias operation, these two Eimac 3-400Z's provide 800 watts of plate dissipation and make possible simplicity of equipment design with no screen or bias power supplies required. For complete information on Eimac zero-bias triodes write Power Grid Manager or contact your local EIMAC distributor. EIMAC—a division of Varian Associates, San Carlos, California.

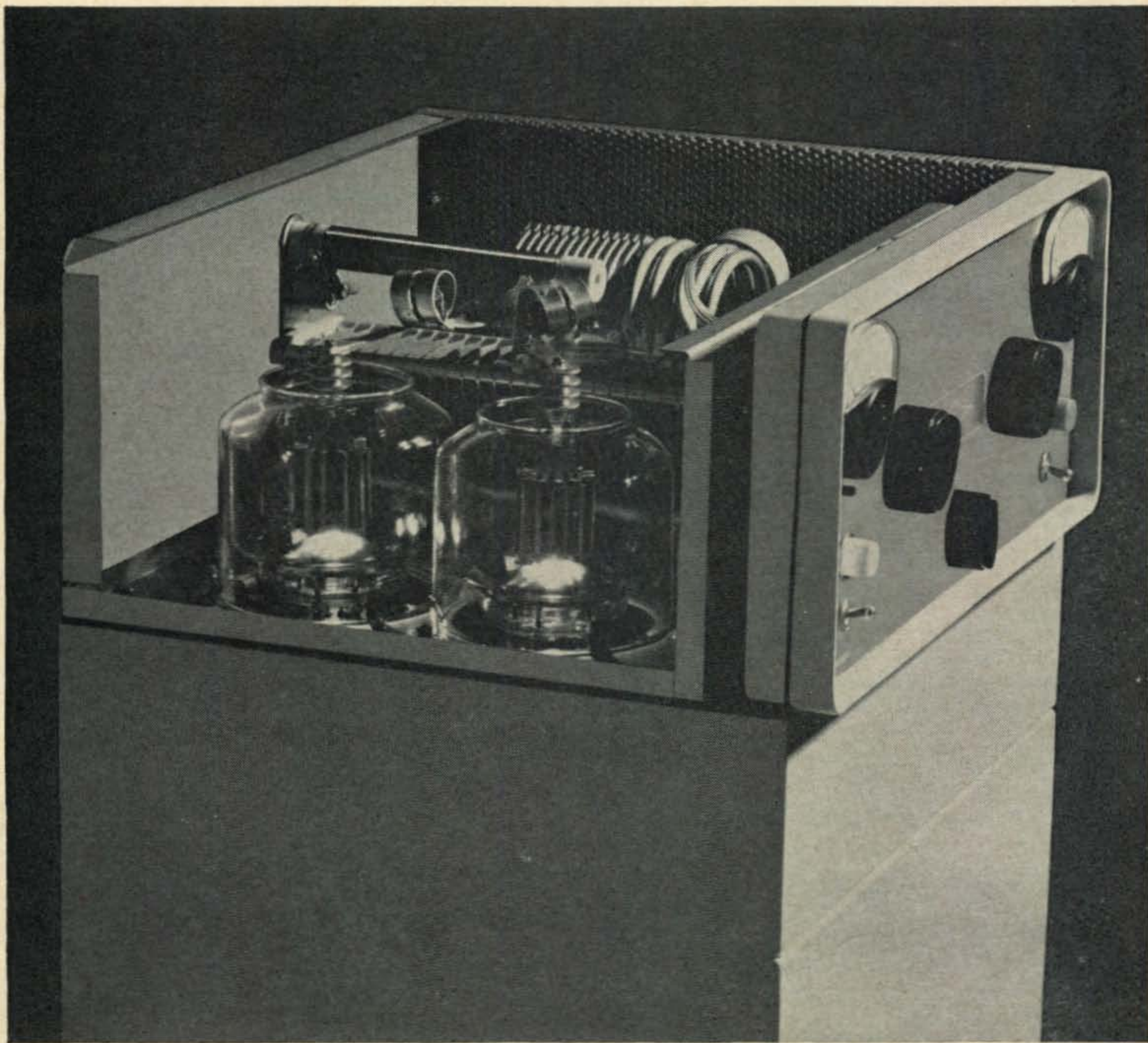

For further information, check number 19, on page 106

MASTER MOBILE'S NEW DART-LINE

SLEEK & SLIM FOLD-OVER ANTENNA & COILS

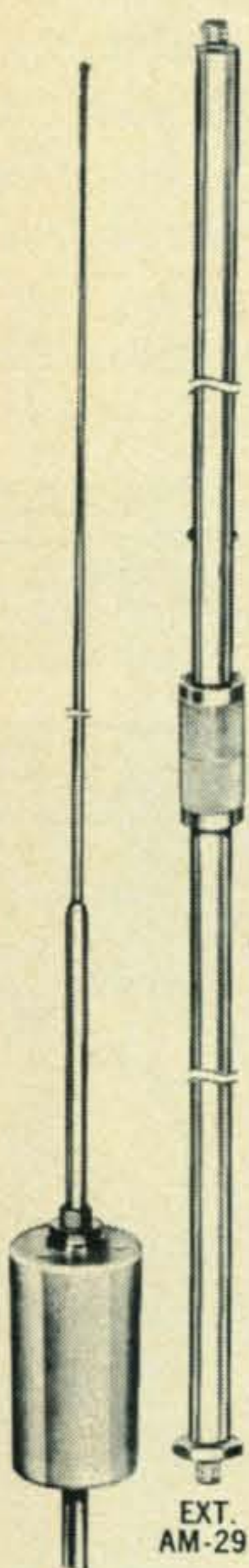


COIL AND WHIP

EXT. AM-29



10 - 15 - 20 - 40 - 80
METERS

New 36" and 48" Stainless Steel Laydown Extension used in conjunction with miniaturized coils, capable of handling 500 Watts AM. Adjustable one-piece whip and coil moves in and out of resonant frequency. Coils are 2 1/8" in dia., lengths range from 2" to 7" depending on desired band operation. Antenna coils designed specifically to handle high power mobile operation while utilizing the small streamlined antenna design normally desired for low powered mobiles. Extension lays over at 18". Extension, coil and whip maximum height 82". Constructed of stainless steel with brass fittings, corrosion resistant, weather-proof. Slim locking sleeve holds a rigid vertical position, extremely convenient in clearing garage doors, car ports and low overhangs. Extension terminates in a 3/8"-24 stud at both ends for additional uses.

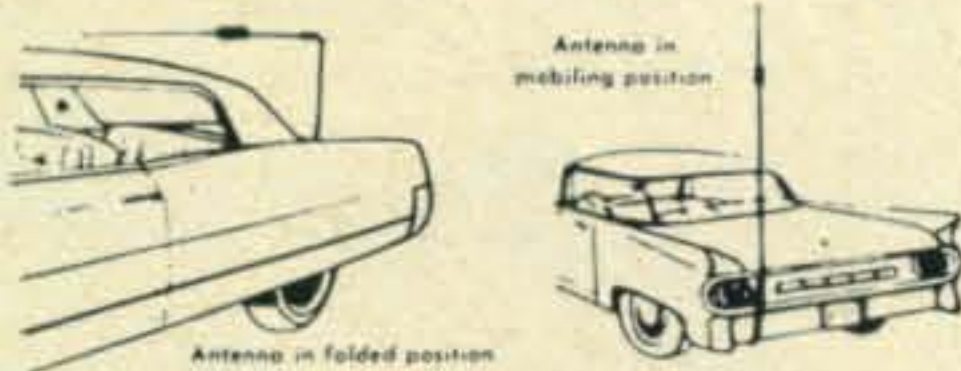

BANDWIDTH RESONANT FREQUENCY

10 Meters	— Approx.	100 to 120 KC
15 Meters	— Approx.	100 to 120 KC
20 Meters	— Approx.	80 to 100 KC
40 Meters	— Approx.	40 to 50 KC
75 Meters	— Approx.	25 to 30 KC

POWER RATING: AM-dc input, 250 Watts - SSB-dc input 500 Watts

AM-29	36" Stain. Steel Laydown Ext. Breaks at 18" (Fender or Deck Mt.)	\$11.95
AM-35	48" Stain. Steel Laydown Ext. Break at 36" (For Bumper Mt.)	14.25
AM-30	80 Meter Coil & Whip	9.95
AM-31	40 Meter Coil & Whip	8.95
AM-32	20 Meter Coil & Whip	7.95
AM-33	15 Meter Coil & Whip	6.95
AM-34	10 Meter Coil & Whip	5.95

DEPT. CQ

AREA CODE 213, 731-2551

Master Mobile Mounts



4125 W. JEFFERSON BOULEVARD
LOS ANGELES, CALIFORNIA 90016



CLUB FORUM

AL SMITH,* WA2TAQ

MOST amateur radio clubs will have completed their elections this month and the newly elected officials will be taking over the reins come January 1st. And . . . most amateur radio clubs will just breeze along with no thought of conducting an installation ceremony of any kind.

This lack of ceremonial splendor in amateur radio is a point the CLUB FORUM will consider this month.

You can go down the line of organizations from local civic groups to world wide veteran and fraternal organizations and you'll find that few do not hold an installation of officers. This swearing in ceremony is an important part of a clubs program and is usually the signal for a big night.

By far the topic mentioned most in the CLUB FORUM mail bag is "how can we keep interest in the club." Also mentioned is the desire for new activities. There's no doubt that fresh ideas are pertinent to club survival. Yet the older activities can still hold member interest if properly conducted.

Many clubs have a problem in finding members who are willing to take on responsibility of leadership. One big reason for this is a lack of incentive (that word again) to take on an office.

If one is expected to do more than the other members of the club then there should be a way to attach the needed prestige to the officers. If there is no air of importance attached to holding office, then your club is missing a good thing.


The officer positions in any club should be coveted rather than shunned. The question now is how to find ways to supply the prestige needed.

To start our newly elected officers off on the prestige trail, what could be better than an installation of officers. Actually there is no standard procedure in our avocation. However there is one ceremony authored by this writer which has appeared in the yearly ARRL club bulletin. This procedure seems to fill the bill and we include it here for your consideration.

Installation Procedure

Installing officer takes over the meeting. For the ceremony he (or she) requests the Sgt. at Arms to escort all newly elected officers to the rostrum with the exception of the President. Officers to be installed face the installing officer who says:

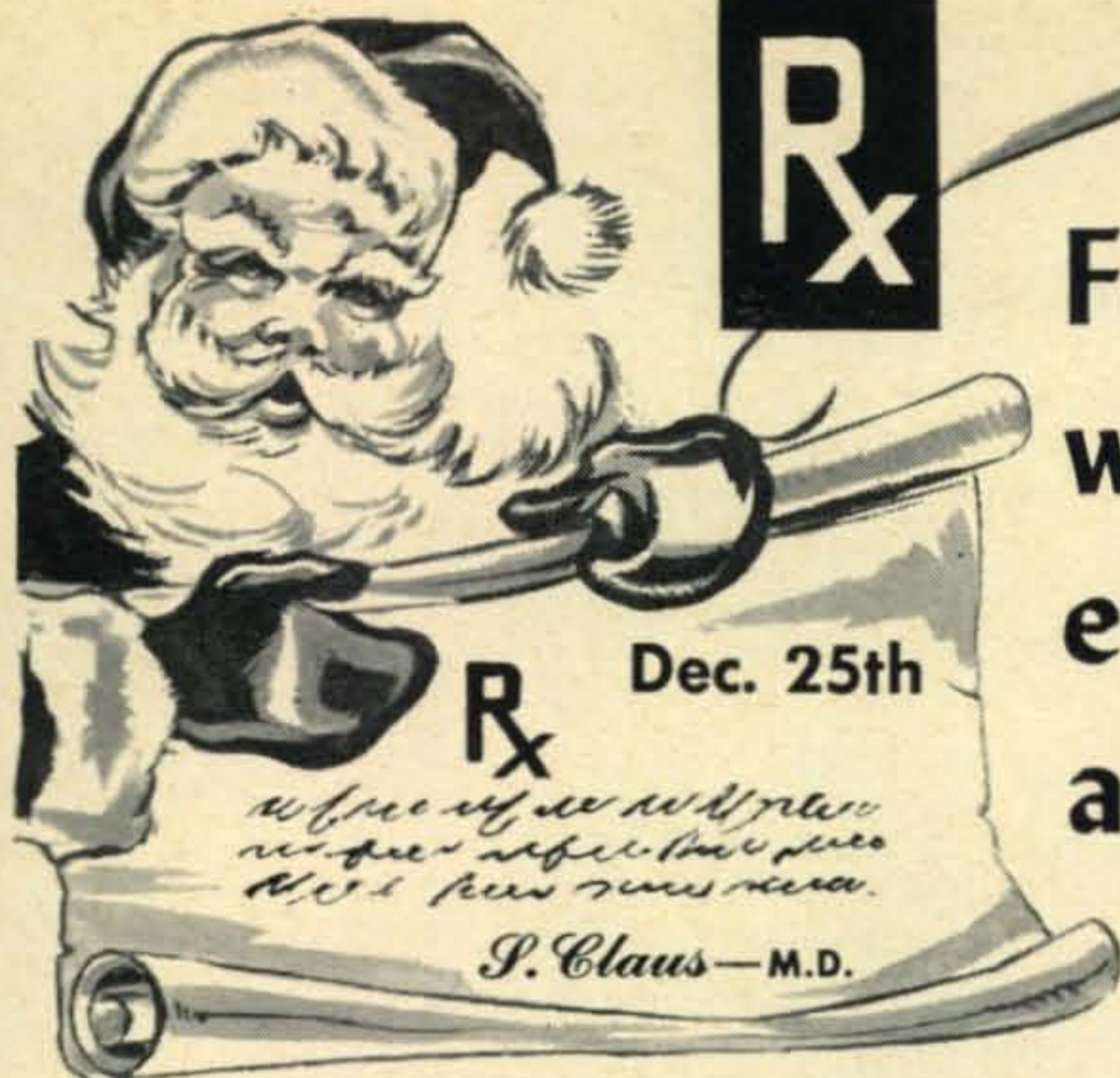*504 Beach 43rd St., Far Rockaway, N.Y. 11691.



Rx

For the ham
who has practically
everything...
add *Waters*

J. Claus - M.D.

He's a wise cookie, old Doc Santa! Figures every ham to be the smart guy he actually is and prescribes a simple "Add Waters" to improve his amateur operating. Could be Santa himself is something of an operator . . . and a good one, too! How else could he know that any piece of "Convenience Engineered" Waters gear would make even the well-equipped ham the happiest ham on the holidays? And long, long after, for that matter!

Waters AUTO- MATCH™

MOBILE ANTENNA

The structurally stronger mobile antenna that puts a stronger signal out — way out! Engineered to last car after car, rig after rig! Operates all bands with only a coil change . . . fits any standard mount.

Mast 370-1	\$12.95
Radiator Tip 370-2	\$ 9.95
Coil 370-75	\$15.95
Coil 370-40	\$14.95
Coil 370-20	\$13.45
Coil 370-15	\$12.75
Coil 370-11	\$11.95
Coil 370-10	\$11.95



Waters CLIPREAMP™

You can give him that increased "talk power" he talks about with the sensational CLIPRE-AMP. Solid state, self-powered and compact it installs in a jiffy in the mike line of either mobile or fixed rig. Great for that added punch when QRM and band conditions are tough.


Model 372 \$21.95 (less batteries)



Waters CODAX™

CODAX — the automatic keyer that puts rhythm-smooth CW at his fingertips. Never anything like it! Feather-touch double paddle is automatically timed for 5 to 50 WPM. Operates block grid or into mike jack for VOX or CW on either sideband. Monitors his signal, too!


Model 361 \$92.50 (less batteries)

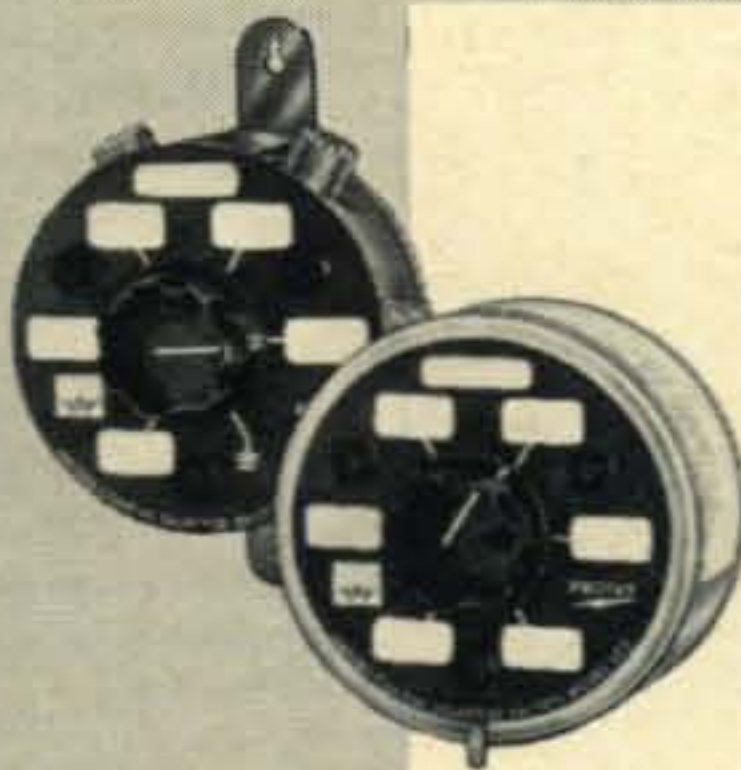

Waters PROTAX™

A must! Brand new Coaxial Antenna Switch that automatically grounds the antenna system when the shack is shut down. Handles a full 1000 watts . . . comes complete with knob, escutcheon plate with erasable marking panels. (mounting bracket on Model 376)

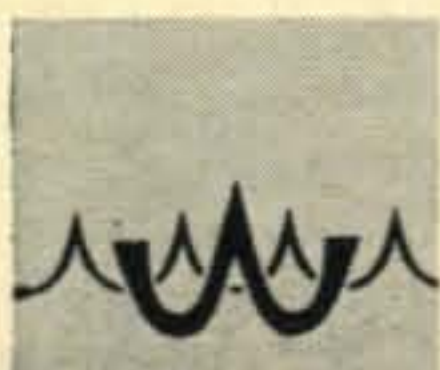Model 375
6-position rear axial connectors \$13.95
Model 376
5-position side radial connectors \$12.50




WATERS

MANUFACTURING INC.
WAYLAND, MASSACHUSETTS

WATERS PRODUCTS ARE SOLD ONLY THROUGH WATERS QUALIFIED DISTRIBUTORS

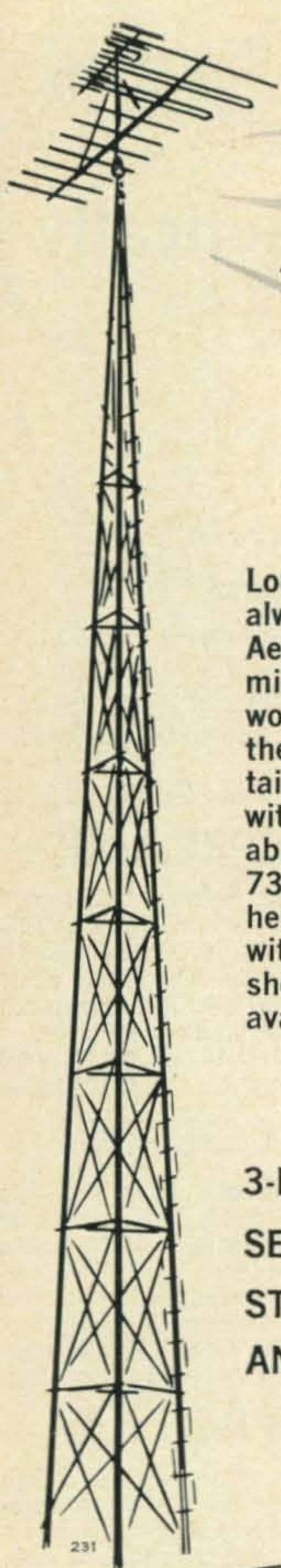For further information, check number 21, on page 106



**DO
YOU
READ ME?**

Loud and clear! That's always the way with Aermotor. Eighty-five mile-an-hour winds won't tip, tilt or topple these towers. They sustain 1500 pound loads without guy wires. Available in 20, 33, 47, 60, 73, 87 and 100 foot heights. Type MI-98 with 2-inch pipe top is shown. Other styles available.

**3-POST
SELF-SUPPORTING
STEEL
ANTENNA TOWERS**



AERMOTOR

Towers

SINCE 1888

BROKEN ARROW, OKLAHOMA 74012

For further information, check number 22, on page 106

22 • CQ • December, 1965

"You have been chosen by your fellow members to lead your club for the coming year. The responsibility of leadership now falls on your shoulders. It is your duty to set the example not only for your fellow club members but to all radio amateurs. This can be done by your faithful attendance at club meetings and activities, and by doing your utmost to support your clubs programs, and as exemplified by your own on the air operating practices. . . . You will now repeat after me, giving your name where I give mine." Installing officer now gives oath of office as follows:

I, _____, BEING DULY ELECTED SOLEMNLY SWEAR TO UPHOLD THE CONSTITUTION AND BY-LAWS OF THE _____ AMATEUR RADIO CLUB, AND THE RULES AND REGULATIONS OF THE FEDERAL COMMUNICATIONS COMMISSION. I WILL DO MY UTMOST TO FURTHER THE PROGRAMS OF THE _____ AMATEUR RADIO CLUB AND PROMISE TO SUPPORT THE CLUB IN ALL ACTIVITIES. I WILL DO ALL POSSIBLE TO KEEP UP THE STANDARDS OF AMATEUR RADIO BY MY OWN OPERATING PRACTICES. I WILL WHEN CALLED FOR ASSIST MY COMMUNITY IN TIME OF NEED.

Following the oath the installing officer proclaims: "I now declare you duly installed." He will then request the group to face the membership and announce: "This is your slate of officers for _____ (year) with your support they will guide your club for the ensuing year."

The installing officer then directs the Sgt. at Arms to seat the installed officers and then requests that the newly elected President be brought before him. The installing officer then repeats the installation ceremony duly installing the club President. Following the oath the President takes over the meeting, makes a short speech or comments, then returns the rostrum to the installing officer for comments. There you have it. You have only to get your group together and make it an enjoyable occasion. Remember that we have few activities in which other than ham members can take part. This is a good chance to invite the XYL and members of the family.

A good recipe for a small installation would possibly be: Take one regular meeting, add a small buffet with soda, coffee and cake. Invite all families, sprinkle a few prominent public officials, add a dias, hold a swearing in ceremony and you have an installation.

Consideration should be given to inviting your ARRL Division Director as installing officer. This will give your club a chance to meet this official and perhaps provide an opportunity for a good question and answer session.

By all means be sure to invite local government officials. This will afford an opportunity to blow amateur radios horn so that others will know of our public service activities. One other very important consideration should be to invite

R-4A
Receiver



T-4X
Transmitter



*May
the joys of
this season
be yours*

along with all the
Drake Ham Gear
that will fit
under your
Christmas Tree!

TR-4
SSB Transceiver



MS-4
Matching Speaker



RV-4
Remote VFO



T-4
"Reciter"




Best Wishes

from all the Radio Amateurs at
R. L. DRAKE COMPANY
MIAMISBURG, OHIO, 45342


**NO MORE
ETCHING, WIRES OR TERMINALS!**
Save time and money with

VEROBOARD

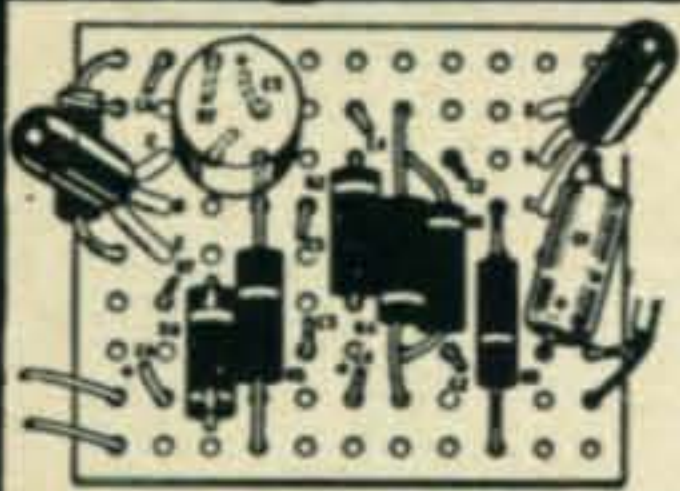**THE ONLY 2 STEP WIRING
BOARD AVAILABLE TODAY**



Step No. 1—Mount components and solder

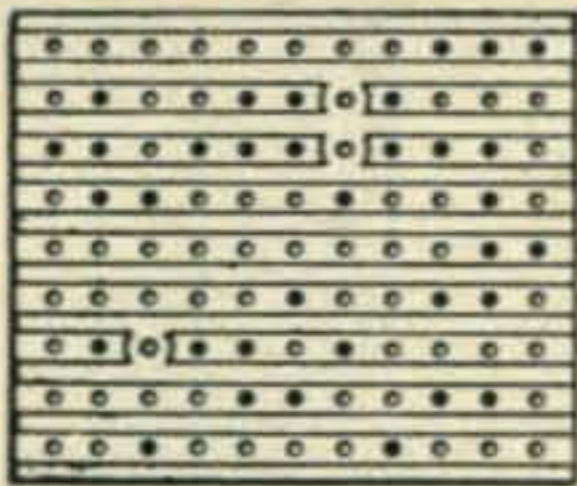

Step No. 2—Break copper strip where required

VEROBOARD KITS

- | | | |
|-------|--|---------|
| PK-5 | 5 Veroboards & 5 projects to build | \$ 1.95 |
| BK-6 | 6 Veroboards & spot face cutter w/inst. | 5.95 |
| VBK-7 | Complete laboratory development kit | 29.95 |

VEROBOARDS

- | | | |
|---------|-------------------------------------|------|
| No. 6-1 | 3.3" x 3.5" with .2 x .2 grid.... | .75 |
| No. 6-2 | 2.5" x 4" with .156 x .1 grid.... | .60 |
| No. 6-3 | 2.5" x 6.9" with .156 x 1 grid | .80 |
| No. 6-4 | 2.5" x 6.9" with .156 x 1 grid.. | .95 |
| No. 3 | 4.8" x 5.8" with .2 x .2 grid | 1.75 |
| No. 20 | 3" x 4.5" with .2 x .1 grid | 1.75 |
| No. 25 | 4.5" x 6.5" with .2 x .1 grid | 2.65 |
| No. 91 | 3.6" x 17" with .156 x .1 grid .. | 4.05 |
| No. 125 | 4.7" x 5.9" with .1 x .1 grid .. | 2.50 |

SPOT FACE CUTTERS

- | | | |
|----------|--------------------------------|------|
| No. 2020 | for .2" x .156" Veroboard | 1.50 |
| No. 2021 | for .1 Veroboard | 2.25 |

VERO ELECTRONICS INC.

48 Allen Blvd., Farmingdale, New York

Please send the following order. I am enclosing check for _____ (N.Y.S. residents add Local sales tax)

_____ Kit No. _____ @ _____

_____ Veroboard No. _____ @ _____

_____ Spot Face Cutters @ _____

Name _____

Address _____

For further information, check number 24, on page 106

a distinguished guest such as the editor of the local paper.

With the holiday season approaching I would now like to extend my very best wishes for an enjoyable holiday to all. And wouldn't it be nice if Santa would leave at least a KWM II under every hams Christmas tree. Merry Christmas and a safe and enjoyable New Year.

73 AI, WA2TAQ

“THEY”

A COUPLE of months ago we mentioned in *A ZERO BIAS* an all-powerful group called “They” upon which the blame for most any dastardly deed is always placed. Any reader having a pet gripe was asked to send it along to us; the best “Why Don't They . . .” would win a one year subscription to *CQ*. We received quite a number of these pet gripes and below are a few which we thought were particularly good.

The free one year sub goes to K7NCP.

Ray Winiecke, K7NCP writes Why don't “They” wait until I get on the air before they begin complaining about TVI?

A month ago I moved my mobile home to a new trailer court. The second week I dug the hole for my tower; the third week the tower was assembled and installed. The fourth week, “They” told me that I was ruining TV reception and causing radio's to buzz. All I have up is the tower. No antenna, no lead-in!

Phyllis McCarthy, WA2PVB, says: Why don't “They” learn to carry on a conversation? I go wild when, after talking for 10 minutes on various subjects, “They” come back and say “Fine Business and back to you” with absolutely no comments on any of my QSO!

Dave Williams, K7HMP wonders: Why don't “They” build more rigs using type “45” and “2A3” tubes so I can use all the spare tubes and batteries I've saved?

“Otts” Beyer, K8CIR (again): Why don't “They” use GMT? Imagine a sked, “Meet you on 14300, 1735 PST Wednesday the 18th. Not sure what this is in GMT but sure you can figure it out.” Or “1645 MST.” That doesn't mean anything to anyone but the mountain people.

“They” should use GMT for all ham logging and activities.


Asks **Lew Clark, WA2TOV**: Why don't “They” dump the contact who always maintains “We put up a new beam,” or “We adjusted the rig.” Instead of “I put up a new beam,” or “I adjusted the rig?” Where do some of these fellows get all the help?

Says **George Maxey, W6BIL**: My pet gripe is the guy who calls CQ DX over and over again without signing his call. How the devil are you supposed to know if *you* are DX for him or not? After a series of CQ DX CQ DX CQ DX for about three minutes he finally lets you in on the secret of *who* he is! Nuts!

I'm in favor of disqualification for any station that calls CQ DX in a DX Contest!


Introducing...


The HEATHKIT® SB-100

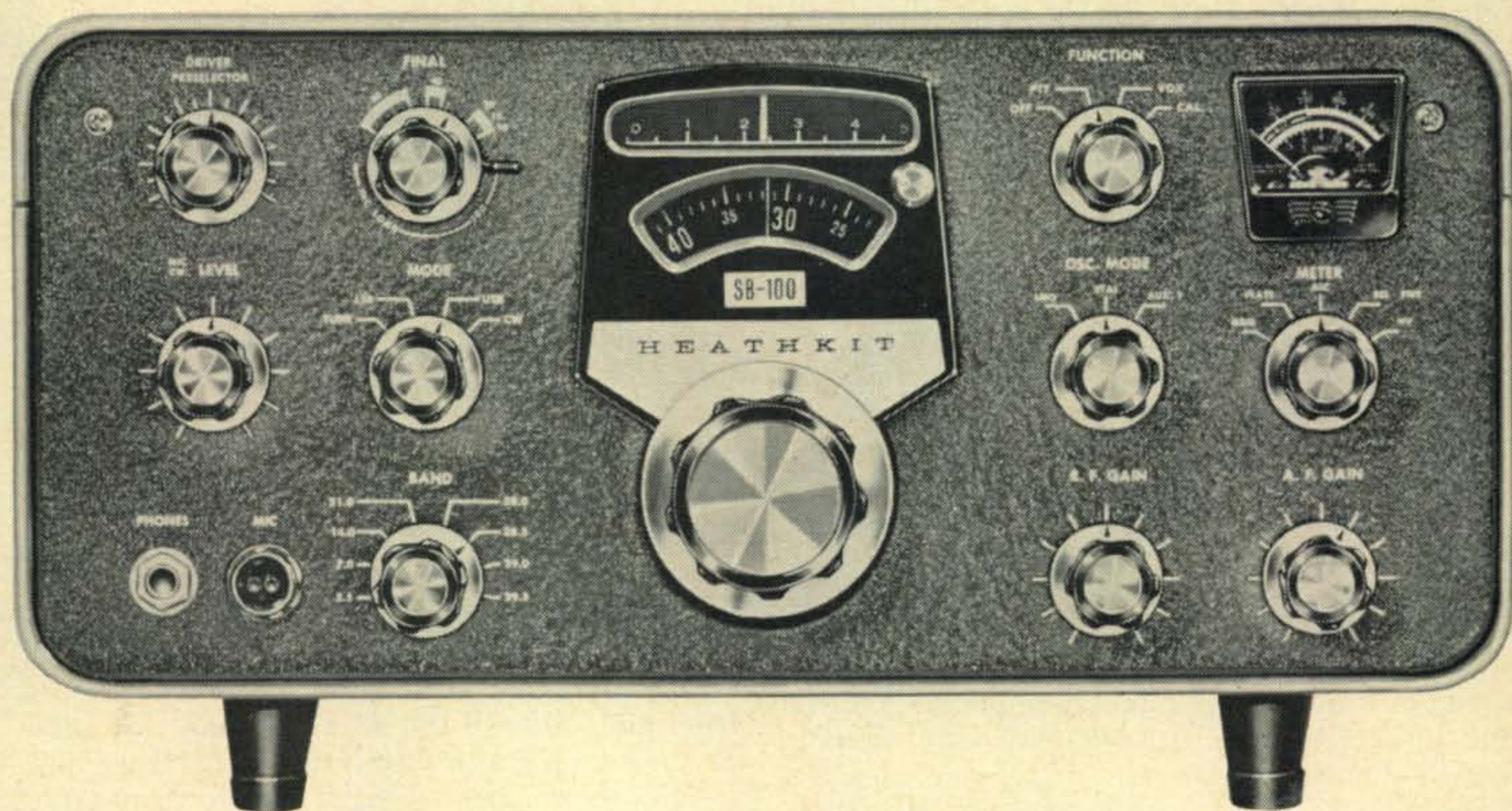

180-Watt, 80-10 Meter SSB Transceiver \$360.00

- Full five band transceive SSB & CW operation, 80-10 meters
- 180 watts P.E.P. SSB-170 watts CW • Switch selectable Upper/Lower sideband/CW operation • Operate PTT & VOX
- VOX-operated CW with built-in sidetone • Can operate crystal control in the transmit mode with variable tuning of receiver or can operate crystal-controlled transceive mode—excellent for net control • Separate offset CW carrier crystal for clear, pure CW note • Triple Action Level Control™ • Built-in 100 kc crystal caibrator • Enclosed relays for quiet, trouble free operation • Heath SB-Series LMO (Linear Master Oscillator) provides truly linear tuning with 1 kc dial calibration—less than 100 cps per hour drift after warm-up—400 cps accuracy • Perfect companion for HA-14 KW Kompact or SB-200 final amplifiers • Fixed station operation with HP-23 power supply—mobile with HP-13 & SBA-100-1 mobile mount for quick plug-in/quick disconnect mobile installation • Fast circuit board assembly • Simple alignment—requires only a VTVM with RF probe, a dummy load and a broadcast receiver

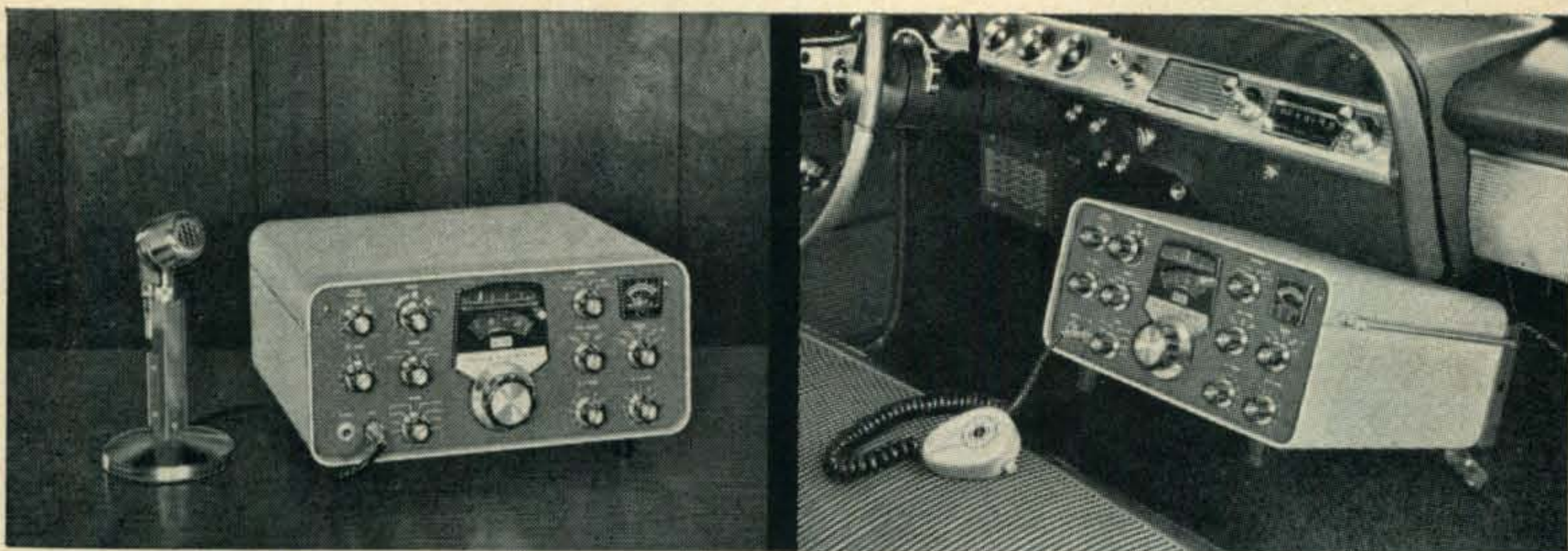If you are considering the purchase of an SSB transceiver, we urge you to read every word on the next two pages before deciding. 



Heathkit SB-100—The SSB Rig You've Been Waiting For

The Newest And The Hottest Of The SB-Series! Here's a complete 80 through 10 meter 180-watt SSB transceiver. It includes all of the high-performance features you've read, heard talked about, or experienced on the already famous Heathkit SB-Series Amateur Radio Equipment . . . plus 5-band coverage with fast, simple band-switching and tune-up . . . alternate "remote" power supplies for fixed or mobile operation . . . new Heathkit Switch-Board™ coil and band-switch assembly . . . and a new ALC control circuit (TALC™) that allows even greater variation in speech level. All this and more in the new SB-100!

Here's Engineering That Sets The Pace For The Industry! The Heath SB-Series crystal filter features a 6 pole lattice filter (6 individual crystals) to produce a superior 2 to 1 shape factor for sharper receiver tuning . . . greater sideband suppression. The filter pass-band is symmetrical . . . for identical characteristics on both upper and lower sideband signals . . . and for optimum SSB reception with steep skirts for adjacent signal rejection. What's more, the entire filter assembly is hermetically sealed to retain its published specifications just as they were when "checked out" at the time of production. Compare these specifications with any other SSB filter on the market! Improved Heathkit Techniques Produce Better Than Factory Assembled Results! The new Heathkit Switch-Board™ coil and bandswitch assembly virtually eliminates the troublesome point-to-point wiring of tuning circuitry . . . eliminates the critical job of "lead dressing" required in "wired" circuitry. Here the assembly procedure is simplified further by a removable switch shaft which enables easy "stacking" of the individual Switch-Boards. Switch-Board construction is a new step forward in achieving electronically stable circuit construction, plus ready accessibility to tuning coils.

Power Consistent With Maximum Versatility. 180 watts P.E.P. is the best transmitter power level for most hams. This power level permits using the right tubes for the job and does not require eliminating useful features to pay for increased power. The SB-100 produces a "bare-


foot" signal comparable to the higher power transceivers and is ideally suited for driving a grounded grid linear for a really big signal without the problems of excessive drive.

TALC™ (Triple Action Level Control) Sets New Standards For Automatic Level Control. Control from three separate circuits is combined in TALC™ to provide greater speech compression . . . allow for even more variation in speech level . . . and boost the performance of the SB-100 still higher.


Operating The SB-100 Is A Pleasure . . . Like Driving A Fine Automobile! Select the band, dial the frequency, peak-up the preselector, and tune. Receiver and transmitter bandswitching is simultaneous. The preselector control peaks up the driver. Final tuning is quick, sure, and positive. And for CW op's who prefer headphone listening, there is a separate headphone level control to adjust the headphone audio level independently of speaker volume. In addition, the transmitter and receiver are always on the same frequency . . . no "leap-frogging" around the frequency when you're working round tables.

Order The SB-100 For The Best Value In SSB Transceivers . . . Regardless! We invite comparison of the *complete* SB-100 specs on the next page with those of any other make SSB transceiver. Also consider circuit design as related to inherent stability, use of quality components and fine mechanical construction, cost of companion power supplies and linear amplifiers, band coverage in view of increasing 10 and 15 meter activity, ease of circuit familiarization with regard to possible maintenance, and resale value. You will agree that the SB-100 is the best investment you can make in amateur radio equipment. (Recommended for hams with previous electronic or kit construction experience.)

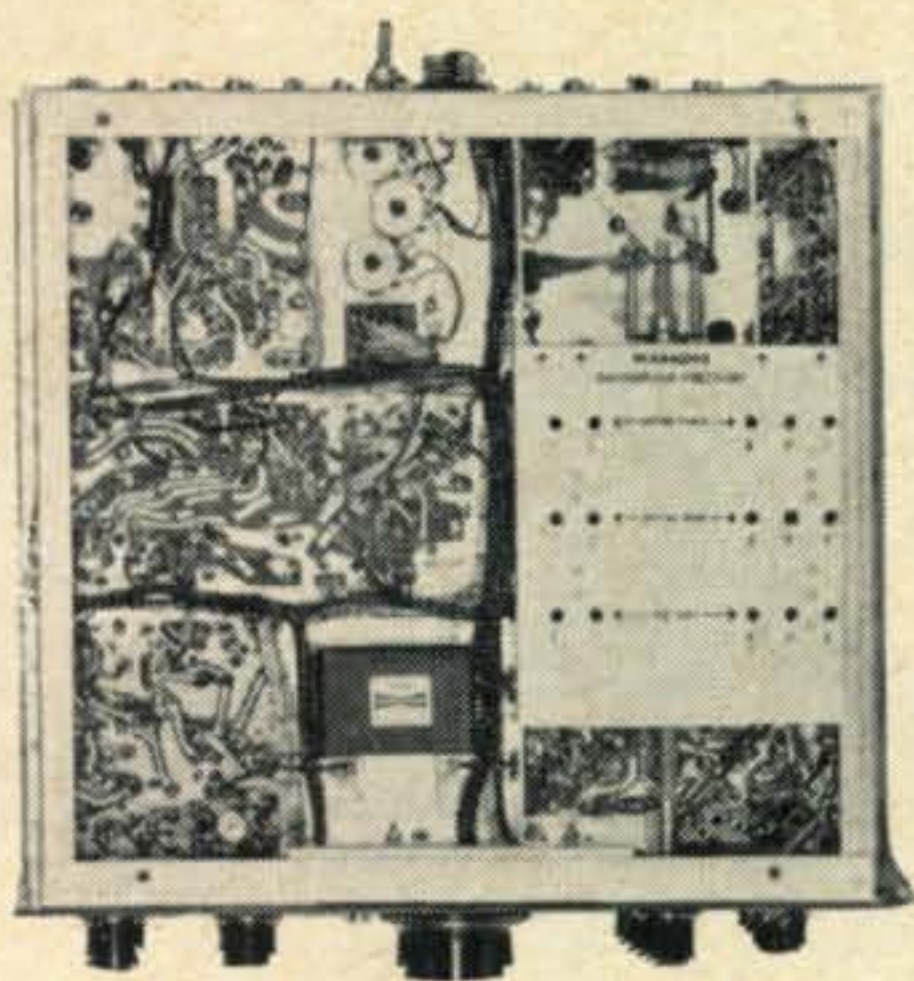Kit SB-100, 23 lbs., \$36 dn., \$31 mo. \$360.00
 SBA-100-1, Mobile Mounting Kit, 6 lbs. \$ 14.95
 GH-12, Mobile PTT Mike, 2 lbs. \$ 6.95
 HDP-21, Communications Microphone, 4 lbs. . . . no money dn., \$5 mo. \$ 29.40
 Kit HP-13, DC Power Supply, 7 lbs. . . . no money dn., \$6 mo. \$ 59.95
 Kit HP-23, AC Power Supply, 19 lbs. . . . no money dn., \$5 mo. \$ 39.95



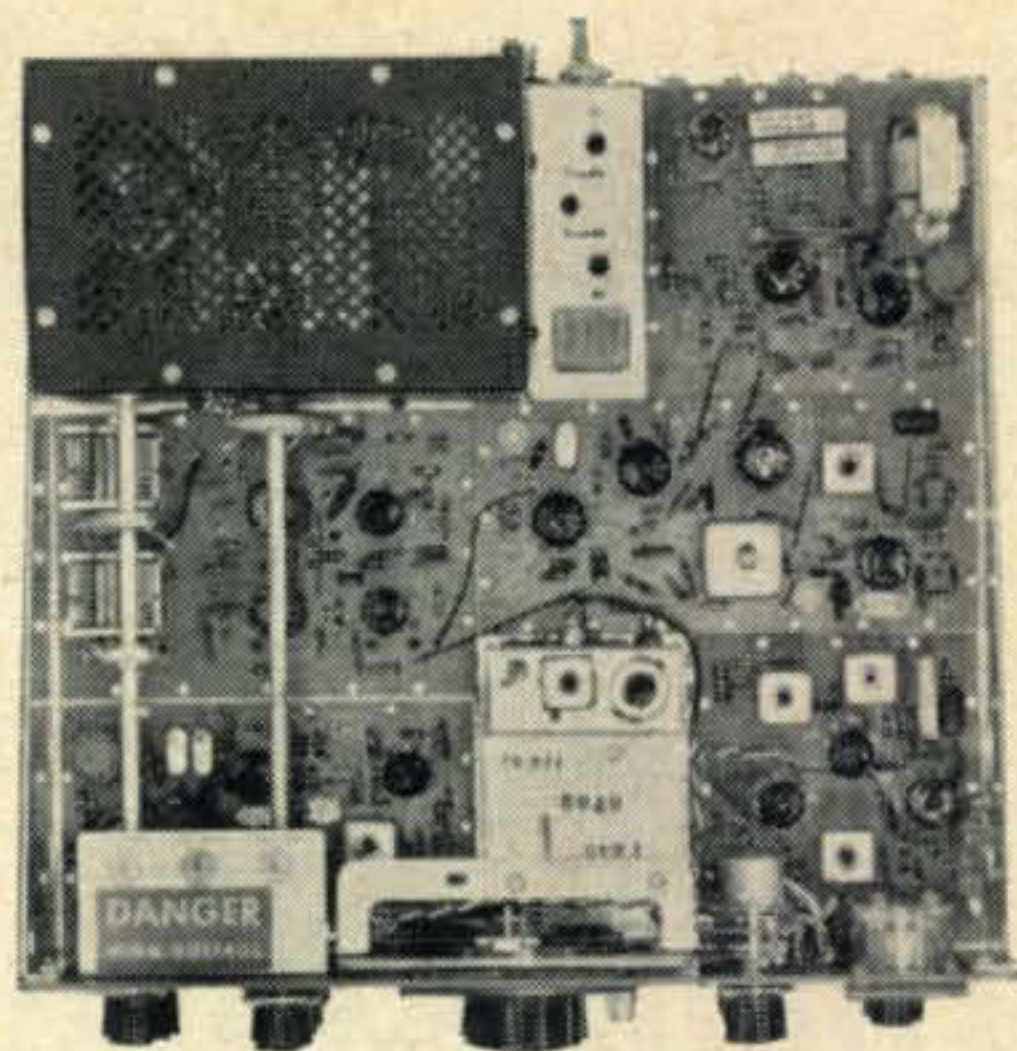Better than factory assembled!—sectionalized circuit board construction, a minimum of point-to-point wiring, the use of pre-assembled wiring harnesses, plus the personal care given to kit assembly assure the quality you demand.



Just how hot can a SSB transceiver be?—Heath SB-Series leads in amateur radio electronics. Modern circuitry, select components, ample shielding, and the rock-stable Heath LMO give the SB-100 pace-setting high performance.

SB-100 SPECIFICATIONS—Receiver section: **Sensitivity:** Less than 1 microvolt for 15 db signal plus noise-to-noise ratio for SSB operation. **SSB selectivity:** 2.1 kc minimum at 6 db down, 5 kc maximum at 60 db down—2:1 nominal shape factor—6:60 db. **Input impedance:** Low impedance for unbalanced coaxial input. **Output impedance:** Unbalanced 8 and 600 ohm speaker, and high impedance headphone. **Power output:** 2 watts with less than 10% distortion. **Spurious response:** Image and IF rejection better than 50 db. Internal spurious signals below equivalent antenna input of 1 microvolt. **Transmitter section: DC power input: SSB:** 180 watts P.E.P. continuous voice. **CW:** 170 watts—50% duty-cycle. **RF power output:** 100 watts on 80 through 15 meters; 80 watts on 10 meters (50 ohm nonreactive load). **Output impedance:** 50 ohms to 75 ohms with less than 2:1 SWR. **Oscillator feedthrough or mixer products:** 55 db below rated output. **Harmonic radiation:** 35 db below rated output. **Transmit-receive operation: SSB:** Push-to-talk or VOX. **CW:** Provided by operating VOX from a keyed tone, using grid-block keying. **CW side-tone:** Internally switched to speaker in CW mode. Approx. 1000 cps tone. **Microphone input impedance:** High impedance. **Carrier suppression:** 50 db down from single-tone output. **Unwanted sideband suppression:** 55 db down from single-tone output at 1000 cps reference. **Third order distortion:** 30 db down from two-tone output. **Noise level:** At least 40 db below single-tone carrier. **RF compression (TALCTM):** 10 db or greater at .1 ma final grid current. **General: Frequency coverage:** 3.5 to 4.0; 7.0 to 7.5; 14.0 to 14.5; 21.1 to 21.5; 28.0 to 28.5; 28.5 to 29.0; 29.0 to 29.5; 29.5 to 30.0 (megacycles). **Frequency stability:** Less than 100 cps per hour after 20 minutes warmup from normal ambient conditions. Less than 100 cps for $\pm 10\%$ line voltage variations. **Modes of operation:** Selectable upper or lower sideband (suppressed carrier) and CW. **Dial accuracy—"resettability":** Within 200 cps on all bands. **Electrical dial accuracy:** Within 400 cps after calibration at nearest 100 kc point. **Dial mechanism backlash:** Less than 50 cps. **Calibration:** 100 kc crystal. **Audio frequency response:** 350 to 2450 cps ± 3 db. **Phone patch impedance:** 8 ohm or 600 ohm receiver output to phone patch; high impedance phone patch input to transmitter. **Front panel controls:** Main (LMO) tuning dial; Driver tuning and Preselector; Final tuning; Final loading; Mic and CW Level Control; Mode switch; Band switch; Function switch; OSC Mode switch; Meter switch; RF Gain control; Audio Gain control. **Internal controls:** VOX Sensitivity; VOX Delay; Anti-VOX; Carrier Null (control and capacitor); Meter Zero control; CW Side-Tone Gain control; Relative Power Meter Adjust control; P.A.—Bias; Phone Vol (headphone volume); Neutralizing. **Rear Apron connections:** CW Key jack; 8 ohm output; 600 ohm output; Phone patch input; ALC input; Power and accessory plug; RF output; Antenna switch; Receiver Antenna. **Power requirements:** 700 to 800 volts at 250 ma; 300 volts at 150 ma;—110 volts at 10 ma; 12 volts at 4.76 amps. **Cabinet dimensions:** 14 $\frac{1}{8}$ " W x 6 $\frac{3}{8}$ " H x 13 $\frac{3}{8}$ " D.

Buy Now—Use This Order Blank

FREE 1966 HEATHKIT CATALOG



See the wide array of Heathkit Amateur Radio Equipment available at tremendous do-it-yourself savings! Everything you need in "mobile" or "fixed" station gear with full descriptions and specifications . . . Send for FREE copy!

Heath Company, Dept. 12-12
Benton Harbor, Michigan 49023



- Please send FREE 1966 Heathkit Catalog.
 Enclosed is \$_____ plus shipping.

Please send model(s) _____

Name _____

Address _____

City _____ State _____ Zip _____

Ship Via:


- Parcel Post Express Collect Freight
 20% Included, C.O.D. Best Way

All prices & specifications subject to change without notice.

AM-160

For further information, check number 27, on page 106

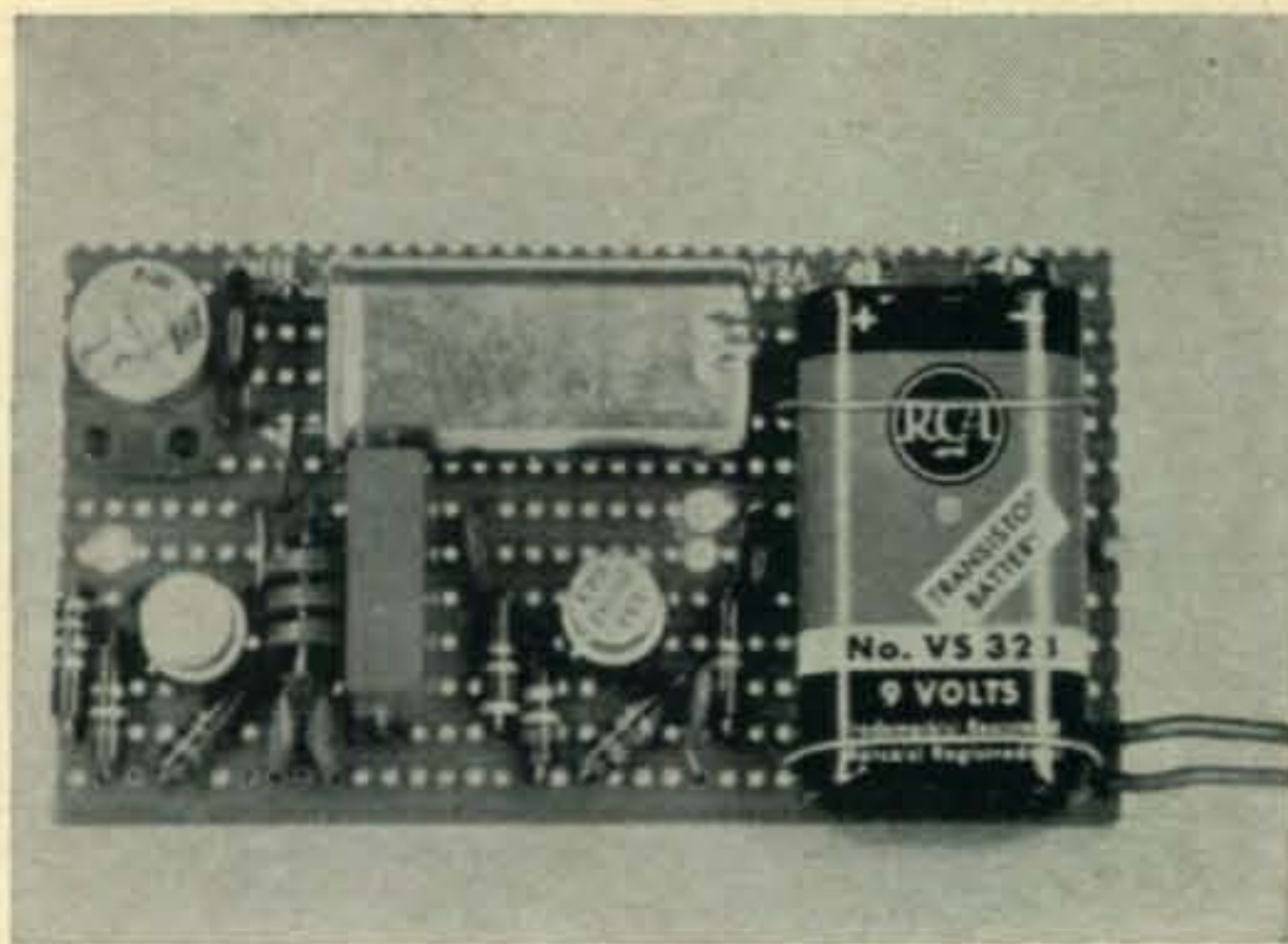The parts for the 100 kc calibrator as mounted on the printed-circuit board. The oscillator is at the left, the harmonic generator at the center and the 100 kc crystal is at top center.



Harmonic-Rich 100 Kc Crystal Calibrator

BY WILFRED M. SCHERER,* W2AEF

THERE are many occasions when a 100 kc crystal calibrator comes in handy, particularly if you're operating near the band edges or if you wish to otherwise check frequency points for receiver, transmitter or v.f.o. calibration, but many receivers, especially those in the transceiver class, are not so equipped. As an accessory, a transistorized calibrator is about the simplest and most convenient type to build and handle. It also lends itself nicely to mobile use or other portable applications in the field, on the bench or in the laboratory not only as a frequency reference, but also as a signal source for various uses.¹

Unlike many solid-state calibrator circuits we've tried out, the one in the unit described here is easy to get going, can be rubbered to exact frequency, is stable and has high output with strong harmonics up to at least 150 mc as evidenced by its S4-5 signals on most of the popular 2-meter transceivers. We've also built

the calibrator in a completely self-contained and handy package, eliminating the breadboard aspect with dangling battery wires as is so often found with most of the models described heretofore.

Our calibrator has two transistors with circuitry as shown at fig. 1. Q_1 is a 100 kc crystal oscillator and Q_2 is a harmonic generator. The oscillator functions in a tuned-collector circuit with feedback to the base through the crystal which can be adjusted to exactly 100 kc with C_1 . A high value collector resistor is used for Q_2 which is then easily driven into saturation by the oscillator to produce an output with a clipped or squared waveform rich in harmonics.

Two output jacks are provided which are connected in parallel in order that the receiver antenna input may at all times be connected to both the operating antenna and the calibrator, thus eliminating the need for interconnecting cables when the calibrator is to be used, or for digging into the receiver to make permanent connections.

In the event the receiver is part of a transceiver

*Technical Director, CQ.

¹For further details see "A Step Attenuator for Receiver and Test Applications" CQ, Oct. '64 page 43.

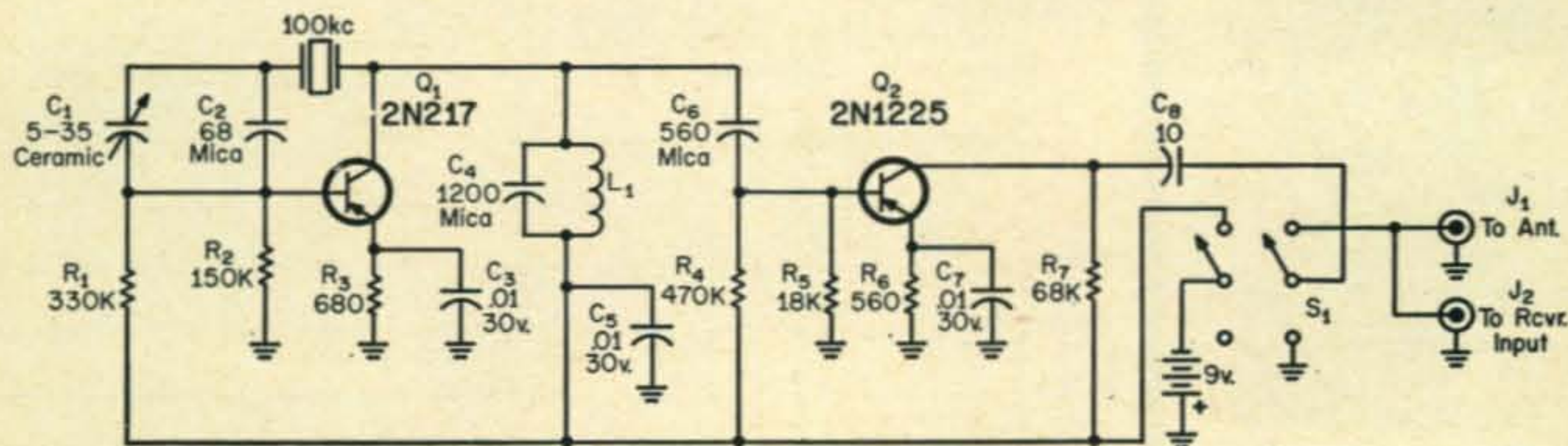


Fig. 1—Circuit diagram for the Harmonic-Rich Calibrator. Specified transistors or their equivalents should be used. Resistors are $\frac{1}{2}$ watt and may vary by $\pm 25\%$. L_1 is 2.5 mh, Millen #J300-2500 sub-miniature iron core r.f. choke.

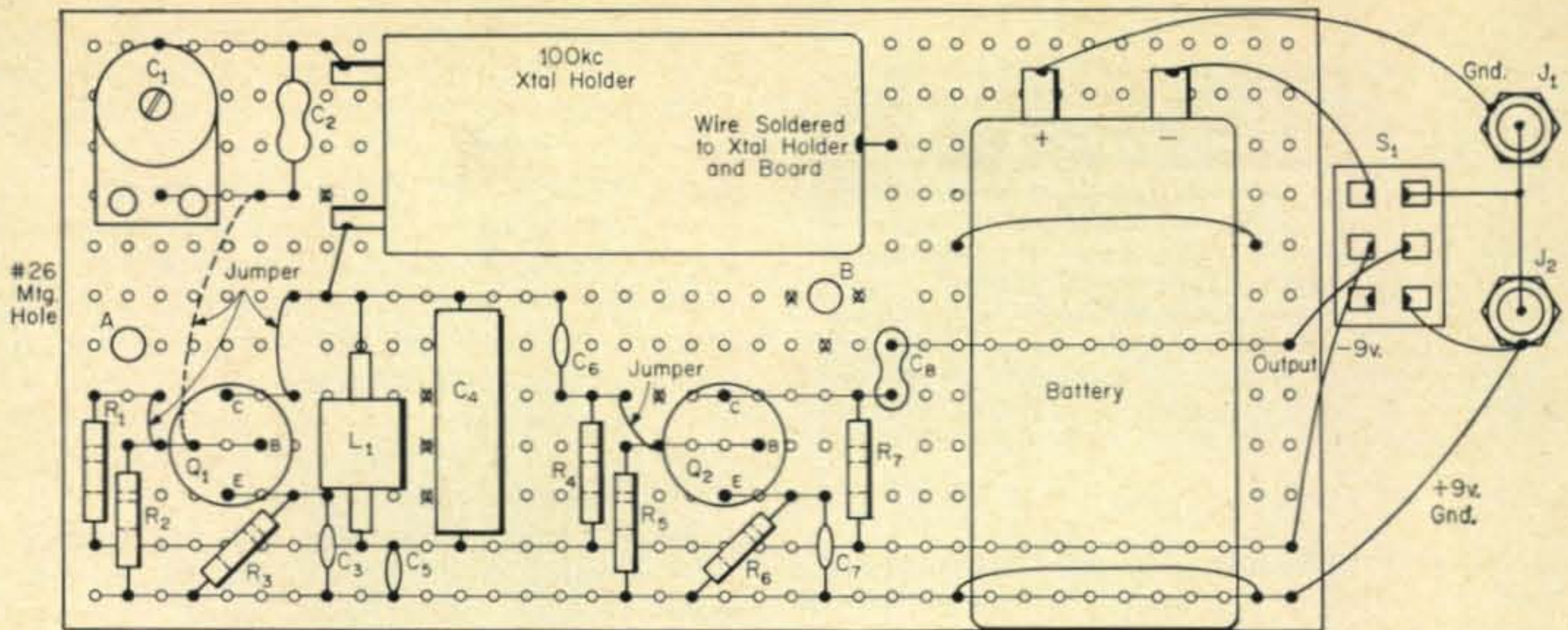


Fig. 2—Placement of calibrator components on the front of the Veroboard. Solid dots indicate soldered connections on the rear. Break in copper strips are made at points marked X. Horizontal lines between holes indicate part of board foils that are actively engaged in the circuit. Holes at A and B should be drilled to size #26 for 6-32 mounting screws. The two jumpers across the battery hold it in place.

where the transmitter output also is applied to the antenna line, Q_2 ordinarily could be damaged by the r.f. power; however, to avoid this possibility, the calibrator output is disconnected from the antenna circuit and is grounded when the battery switch is turned off. Safe operation is realized as long as you remember to shut off the calibrator! If you tend to be a bit absent minded, it is suggested you substitute a momentary contact push-button type switch that must be held on while the calibrator is in use.

Construction

The components for the calibrator are mounted and wired on a printed-circuit board that is installed in a $2\frac{1}{4}'' \times 2\frac{1}{4}'' \times 4''$ Minibox. The type board used is a Veroboard which comes backed with strips of printed-circuit foils that eliminate the need for doing your own etching. Details about these "made-to-order" boards may be found elsewhere in this issue.²

The board should first be cut down to size $2'' \times 3\frac{3}{4}''$.³ This may be easily done by using a pair of diagonal cutters to snip along the rows of holes in the Veroboard where the cutting is required.


Next, drill out the specified holes for the two mounting screws. See fig. 2. After this, place the board centered in the Minibox with about $1/16''$ clearance at the sides so that the cover may slide on properly. Then mark the hole locations on the bottom of the box and drill #26 holes through it accordingly. This will facilitate accurate hole locations for later installation.

Figure 2 shows where the parts are to be mounted and how they are automatically inter-

connected by the foil strips on the Veroboard. The points at which foil-breaks are to be made are also indicated. The transistors may be wired and soldered directly to the circuit; however, the use of transistor sockets will avoid possible damage to the transistors during soldering, and permit convenient interchanging of transistors. The sockets are the G.C. type 16-918 which have terminal pins that are long enough to be inserted through the board holes. They are available at most parts stores.


The 100 kc crystal holder is placed flat on the board and is held in place with connecting leads soldered to the board foils and the crystal-holder terminal pins. A wire soldered to the top of the holder case and the board adds additional support.

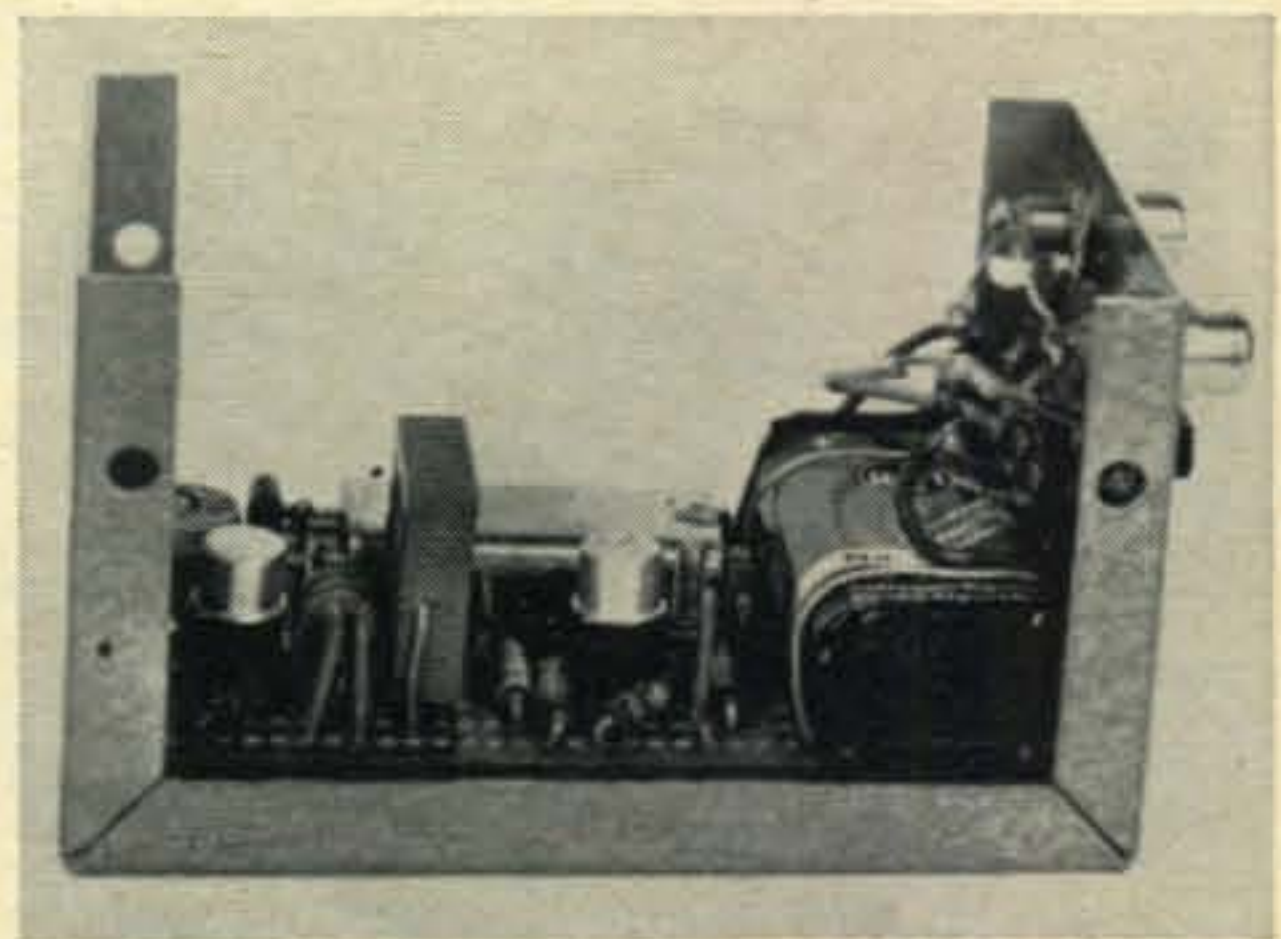Instead of using a hard-to-find battery-holder



The circuit board for the calibrator is mounted in a minibox on $1/4''$ spacers. Not shown, is a heat sink made of a small fuse clip which was later installed on the oscillator transistor to thermally stabilize it when power was applied. The phono jacks are at the top of the right side on which the switch is mounted just above the battery.

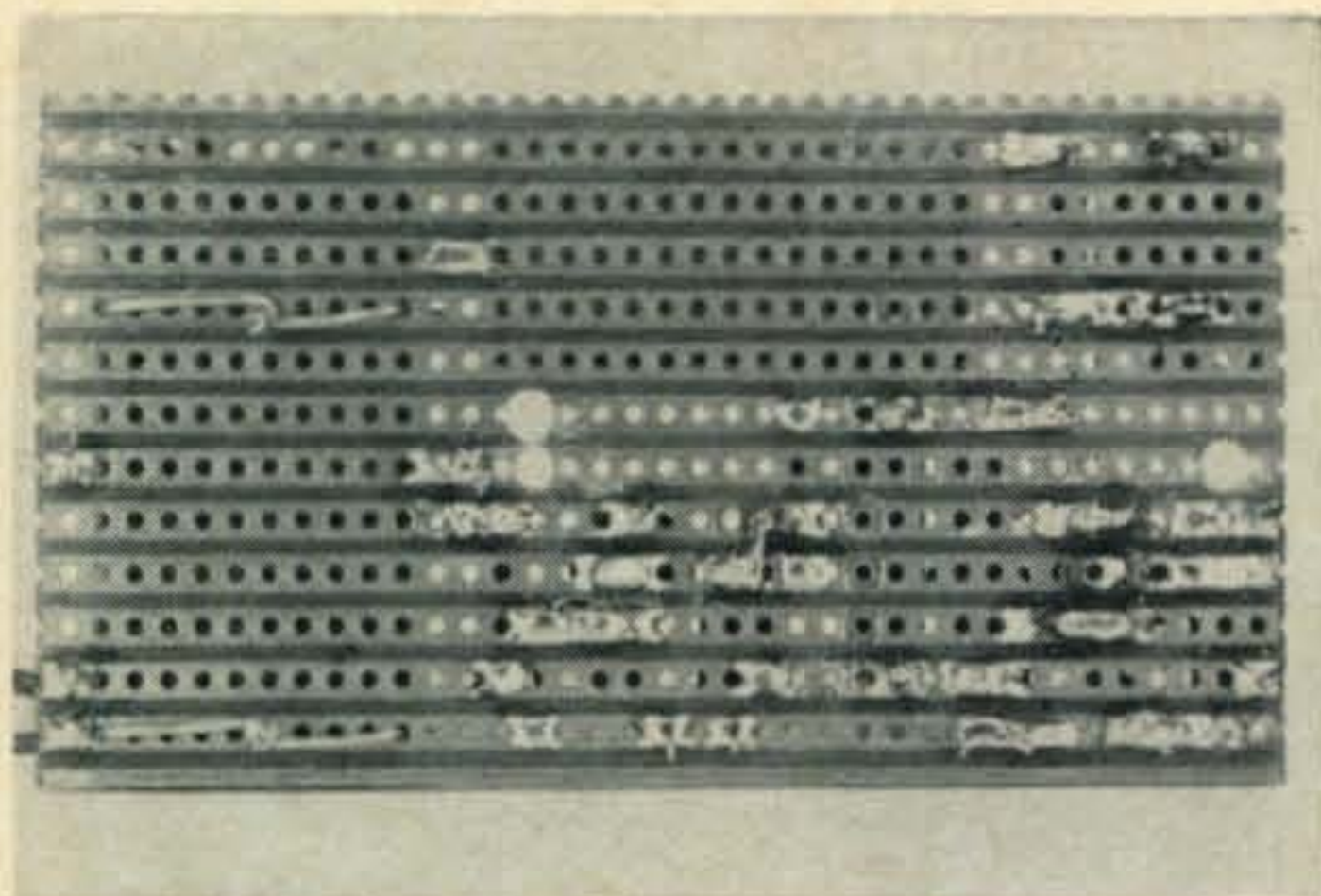²"Circuit Boards—Quick and Easy" page 35 this issue.
³Use 4" board with $.156'' \times .1''$ hole matrix as furnished in Veroboard Kit BK-6.



Rear view of the Veroboard on which the calibrator is built. The component leads that have been inserted through the holes are soldered to the horizontal copper strips (or foils) that are ready-made on the board. Breaks are made in the strips where necessary to isolate circuit elements. Three of the breaks may be seen to the right of center on the 3rd, 4th and 5th strips from the bottom.

clip, the battery is clamped to the board with two wire loops around the battery with their ends pushed through the board holes and twisted together at the back of the board. A snap-on terminal strip is used for connecting leads to the battery.

Capacitor C_1 is held and soldered to the board by its terminal pins that are inserted through the holes. C_2 may be omitted if a 180 mmf miniaturized compression-type trimmer is used for C_1 instead of the type specified. C_1 and C_4 should be temporarily installed until after the unit is working, as explained later. Phono-type jacks for the antenna connections and a d.p.d.t. slide switch are mounted on one end of the box. The center line for the jacks and the switch should be $\frac{3}{8}$ " and 1" respectively from the top of the side as shown in the photo. Also, temporarily make the leads between the antenna jacks, circuit board, switch and battery about 6" long, so the calibrator may be conveniently tested before it is mounted in the box.

Adjustment and Operation

While the circuit board is out of the box with

its temporary-length leads installed, connect the receiver input to the calibrator. With the receiver b.f.o. turned on, switch on the calibrator and tune the receiver for a beat note near any 100 kc point on a low-frequency range. If the signal cannot be heard and assuming that the unit has been correctly wired, chances are that Q_1 is not oscillating, because C_4 is too small or large to properly resonate with the precise inductance of the particular component used for L_1 . The value of C_4 may then have to be changed 100-200 mmf. After the unit is working, permanently install the correct size capacitor for C_4 .

Next, connect an antenna to the other jack on the calibrator, shut off the calibrator and tune in WWV or some other signal whose frequency is known to be an accurate multiple of 100 kc (a BC-221 can be used also). Turn on the calibrator and zero beat it with the signal by adjusting C_1 .⁴ If the crystal cannot be tuned to exact frequency, C_2 is too large or small as can be determined by noting at which end of its range C_1 must be set to approach zero beat. C_2 should then be altered accordingly and until zero beat can be had with C_1 near its mid setting.

The circuit board may now be installed in the box with its leads trimmed down and permanently connected. Fasten the board to the box using 6-32 screws and nuts with $\frac{1}{4}$ " spacers between the board and the box. A fiber washer should be placed on the board-side of each spacer. Make sure that the mounting nuts do not touch the crystal holder or component leads and also see that the edges of the board do not touch the box at any point.


Plastic electrical tape should be attached to the rear side of the battery-terminal clip, or on the inside of the box cover, to prevent shorting of the terminals when the cover is in place. Upon completion, the calibrator should be readjusted to frequency through a $\frac{3}{8}$ " diameter access hole which should be made in the cover before it is installed. ■

⁴If calibrator signal is too strong to produce a good beat, the coupling between the calibrator and the antenna line will have to be reduced.

New Amateur Product

Apollo Engraving Co.

APOLLO Engraving Company has just come out with a new useful idea and we wonder why any one hasn't thought of it before. It is a plastic strip 10" x 12", with your call letters engraved on it. The strip is held to the rear auto windshield by two strong durable suction cups. The item sells for \$3.00, two (one as a gift) for \$5.00. The colors available are black with white letters or red with white letters. For more information write to Apollo Engraving, P. O. Box 81, Brooklyn, N.Y. or circle 64 on page 106.

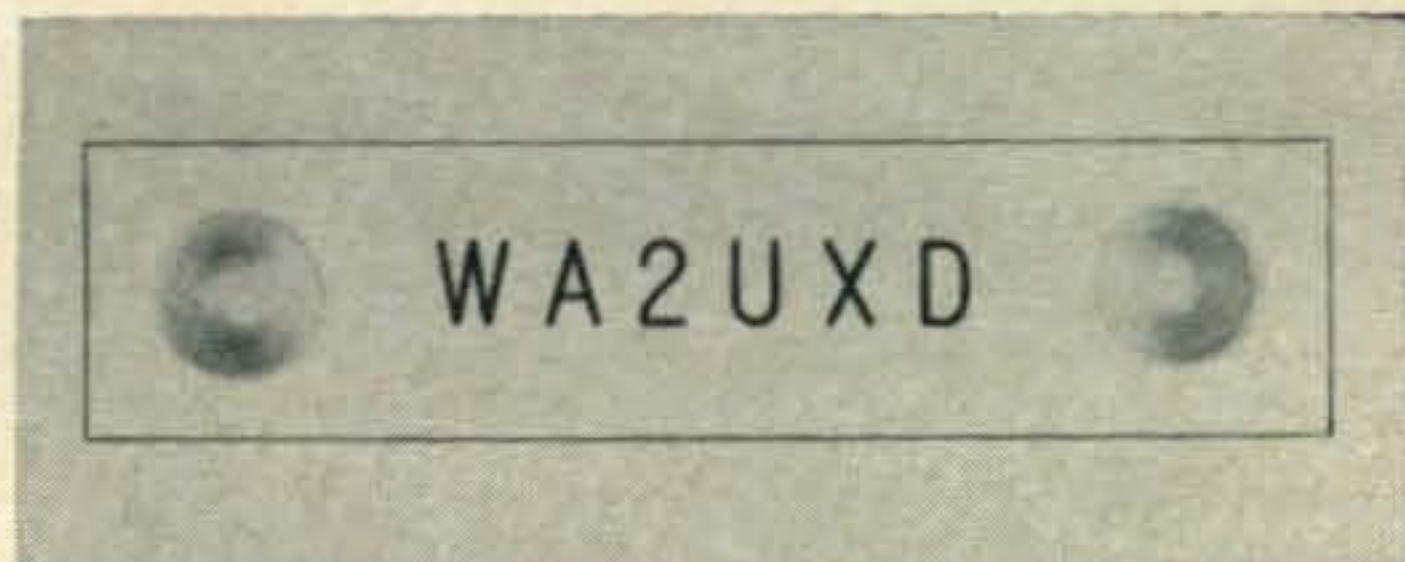

Hum



Reduction!

BY JAMES ASHE,* W2DXH

A simple approach to a common cause of hum in power supplies.

BUILDING a power supply for a high gain audio circuit? Most of us do, sooner or later and sometimes it happens to produce hum!

A rarely mentioned and more rarely tested point of entry for the hum is by way of the power supply filter choke. The properties of this choke are probably far from ideal; its route to the builder's hands may have obscured its ancestry, and anyhow it's well to be a little suspicious of its properties.

'Phone Test

Try the earphone test. Free both leads of the choke, place it and the power transformer at their planned locations. Energize the transformer and see what comes out of the choke by connecting the phones across it. You are probably in for a surprise! Try this for various transformer and choke positions. Discouraging, isn't it?

But wait! Is this the right test? Is the choke in the same sort of electrical circuit it will see in the finished supply?

Figure 1(A) shows a common filter configuration. Figure 1 (B) shows the easy way to do the test, without thinking. In fig. 2 the irrelevant parts of the circuit are omitted. The choke is drawn as a generator supplying a certain hum

voltage, and the two capacitors are drawn as reactances which load the generator. A 26 mf capacitor would have a reactance of about 100 ohms at 60 cycles.

Let's think about fig. 3 for a moment. What does it mean? It means that the hum voltage appears across Z_1 and Z_2 in series. The half appearing across Z_2 is the part seen by the rest of the circuit. That factor of 2 won't make much difference; we're just getting oriented now. The important thing is the magnitude of the load on the choke's hum generator. The magic number is 100 ohms or so.

So when we want to estimate the hum voltage the choke will pick up, we just put a 100 ohm resistor across its leads, and see what voltage it can produce across that load. The result isn't likely to be off by a factor greater than two and if you like large filter capacitors, it will be a good conservative figure.

For example, the following results were taken from a 10 henry choke located 4 inches from a small power transformer, both mounted upright and with their cores in line:

- No load, 100 mv hum voltage.
- 100 ohm resistive load, 2.5 mv hum voltage.
- 24 mf capacitor load, 2 mv hum voltage.

Oh yes—there is one case where all bets are off. That is if L and C resonate at 60 or 120 cycles. ■

*Eli Scientific Co., RD 1, Freeville, New York 13068.

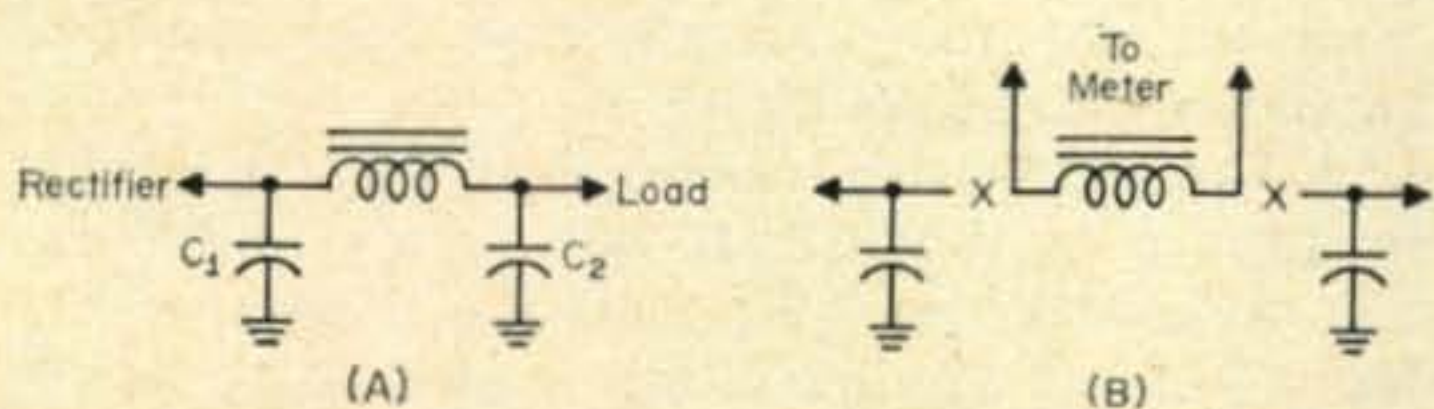


Fig. 1—(A) Basic pi-filter circuit encountered in most power supplies. (B) A simple but inaccurate method of checking the hum voltage pick-up.

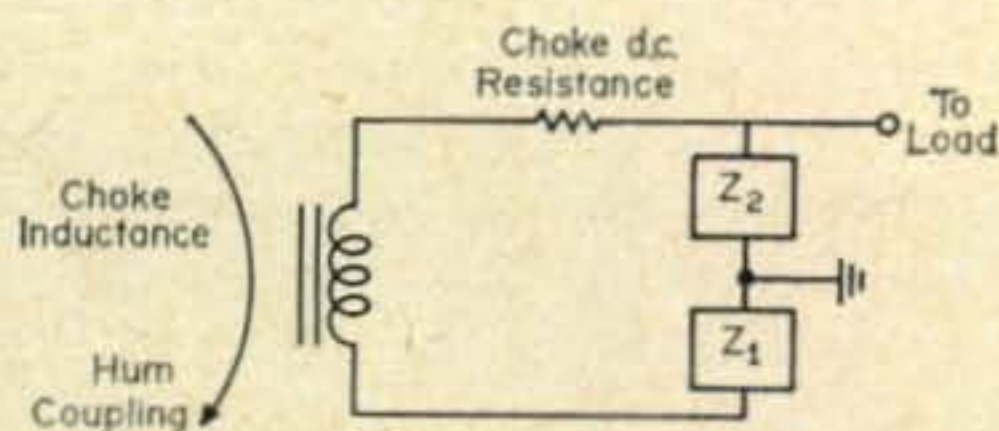


Fig. 2—Equivalent circuit shown above illustrates the choke hum circuit, and shows voltage divider effect of filter capacitors.

OSCAR NOTES

A NUMBER of inquiries have been received concerning the lash-up used for obtaining the oscilloscope displays of OSCAR III's telemetry pulses as shown in the photos on page 56, Sept. '65 CQ.

The trace is that of the r.f. envelope of the signals and may be obtained by sampling the i.f. of a receiver that has an i.f. type noise limiter and applying it to a 5 mc d.c. coupled oscilloscope with a trigger sweep. We used a Hallicrafter's SX-115 receiver which has both an i.f. noise limiter and auxiliary terminals for 50 kc i.f. output. The scope was a Heathkit Model OP-1. In this case, a 100 kc scope could have been used, but with higher i.f.'s a wide-band scope must be used. An i.f. type noise limiter is a necessity, not only for levelling off picked-up noise interference, but also for attenuating noise spikes from the inherent noise of the receiver.

Observations of the r.f. envelope were much more satisfactory than those of demodulated a.f. signals from the detector where a conglomeration of waveforms from various beats made visual observations extremely difficult.

Oscalator Notes

In case you've had some questions about the Oscalator described in the August '65 CQ, here are the answers to a few queries that came up:

Referring to fig. 2 in the original article, the Oscalator track is a sub-satellite track that has been compensated in relation to a rotating earth. If the earth were standing still, the actual arc, starting at 0° W. Long. on the equator, would go through 270° W. Long. at 70° N. Lat. and over to 180° W. Long. on the opposite side of the equator.

The method described for plotting the track should be correct for near-circular orbits having periods up to about 200 minutes. For very high-altitude or longer-period orbits, the determination, for points A, B and C (fig. 2) is slightly different. We hope to cover this in a subsequent article together with data pertaining to elliptical orbits.

For a Southern projection, the easterly and westerly directions on the range scales (fig. 3) should be reversed. Also, the indicated directions are for the great circle route to the 2000-mile limit only. As the range diminishes, the directivity approaches that of the normal compass points. The points do not indicate the *bearings* in *degrees* as related to the angle with the N-S reference.

To illustrate the comments in the 3rd paragraph, 1st column page 58: fig. 4 shows that although the 40th parallel crossing on the N-S

orbit is out of range of Boston (left scale), the orbit otherwise is in range for 12 minutes!

Oscar IV Track

OSCAR IV is expected to be in a near-synchronous equatorial orbit (0° inclination) with a daily eastward progression of about 30°. In this case the sub-satellite track on the Oscalator will follow the equator counterclockwise 30° per 24 hours. The approximate length of time that OSCAR IV will be in or out of range of various latitudes is shown in the table given in the SPACE COMMUNICATIONS column (see page 83). The in-range time will be slightly less for a 30° drift.

It should be noted that the in-range view from various latitudes cannot be determined from the Oscalator. The aforementioned table should be used instead.

As soon as OSCAR IV is launched and the exact orbital parameters are known, we'll gladly send you track data; *provided*, you furnish us with a self-addressed stamped envelope.

Things To Come

Other interesting OSCAR packages that are in the works for future launches are as follows:

A Linear Translator (under construction and test by a group led by Marvin Wahl, K9CHU/6). The translator has an input center frequency of 144.1 mc and an output center frequency of 29.45 mc with a passband of 25 kc. It will also have a 10-meter transmission, and should stimulate further interest in amateur space activity.

AN ARIES/OSCAR (Amateur Radio in Experimental Satellite) satellite is in the design stage under the sponsorship of the San Fernando Valley Radio Club. It is expected to be a 2-meter translator with both v.h.f. and u.h.f. beacons.

A joint project of the Melbourne University Astronautical Society of Australia and the Melbourne University Radio Club, VK3ATM, is a solar end battery powered translator satellite operating in the 144 and 432 mc bands with a proposed 8 channel telemetry system along with a pulse h.f. beacon transmitter.

The Euro-OSCAR translator satellite built by DJ4ZC and others is expected to go in a low-altitude launch sometime in 1966. This package is modeled after the successful translator launched by balloon in Holland.

A 144 mc beacon is being built by a group led by John Fox, WØLER. It will have a 144.05 mc c.w. beacon keyed by a separate telemetry system. A novel telemetry unit is also being developed by Jim Fromke, KØMHC. It consists of a 7 channel binary pulse-code modulation system.
—W2AEF

Using Audio Controlled A.G.C. For Improved Receiver Selectivity

BY JAMES E. TAYLOR,* W2OZH

The use of audio controlled a.g.c. combined with an audio filter can provide superior action and improve the receiver selectivity. How this may be done is described below.

THE "audio hang" a.g.c. circuit developed by Luick¹ appears to be superior to others for communications receiver design. It provides a flat a.g.c. characteristic throughout the normal signal range, eliminates isolation problems, and includes the fast attack and slow release required for proper reception of s.s.b. signals.

For several years, now, I have used this circuit, with a 75A4 receiver, in a manner which permits greater a.g.c. gain and improved effective selectivity of the receiver.

Principles Of Operation

By normal i.f. standards the nominal 3.1 kc mechanical filter has very good skirt selectivity. But, for many years audio filters have been available which display even steeper skirt selectivity characteristics. If such an audio filter is utilized in the audio amplifier of a communications receiver, after the point of origin of the control voltage for audio a.g.c., there can result a "muting" action. This is due to any predominant interfering signal which exists in the frequency range between the selectivity cut-off point of the mechanical filter, and that of the audio filter. However, if the control voltage for the audio a.g.c. is derived from a point *after* the selective

audio filter, this muting effect is eliminated and the speaker volume of the desired signal is not decreased due to the presence of the interfering signal.

Figure 1 shows the block diagram of the conventional audio a.g.c. arrangement as used by Luick. Figure 2 indicates the block diagram of the modification with selectivity derived from the audio filter. Connection (A) permits muting as mentioned above, while connection (B) provides the elimination of this effect.

In fig. 3 typical response characteristics of mechanical and audio filters are shown qualitatively together with an assumed interference situation. Here it is desired that a 1 kc signal be received in the presence of an interfering 3.3 kc signal having twice the amplitude of the former.

Table I indicates, in arbitrary units, the a.g.c. output voltage, the corresponding i.f. gain, and the resulting speaker input voltage for three situations: A, for the conventional arrangement of fig. 1; B, for the same arrangement, except with the audio filter added to restrict output response only; and C, with the audio a.g.c. voltage derived from the audio filter output. Here, for simplicity, linearity has been assumed for all parts of the circuit. It is seen that from situation A, with two units of desired signal in the pres-

*Xerox Corporation, Webster, New York 14580.

¹Luick, G. W., "Improved A.V.C. for Side-Band and C.W.," *QST*, Oct. 1957, p. 46.

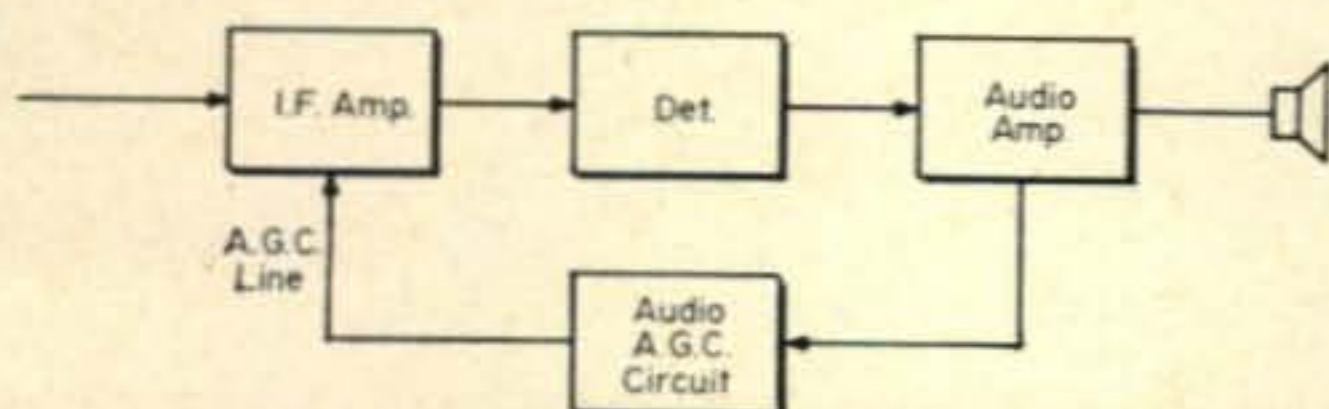


Fig. 1—Block Diagram of the basic a.g.c. circuit.

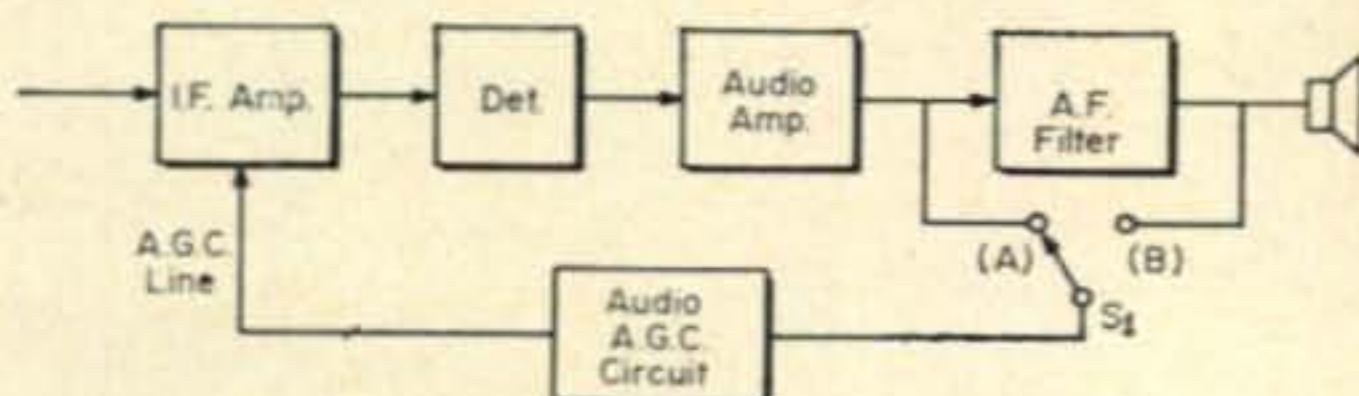


Fig. 2—Block diagram of an audio a.g.c. system using an audio filter for improved performance. Switch S1 permits the filter to be switched out of the a.g.c. loop and in the actual circuit eliminates the filter from the audio circuit also.

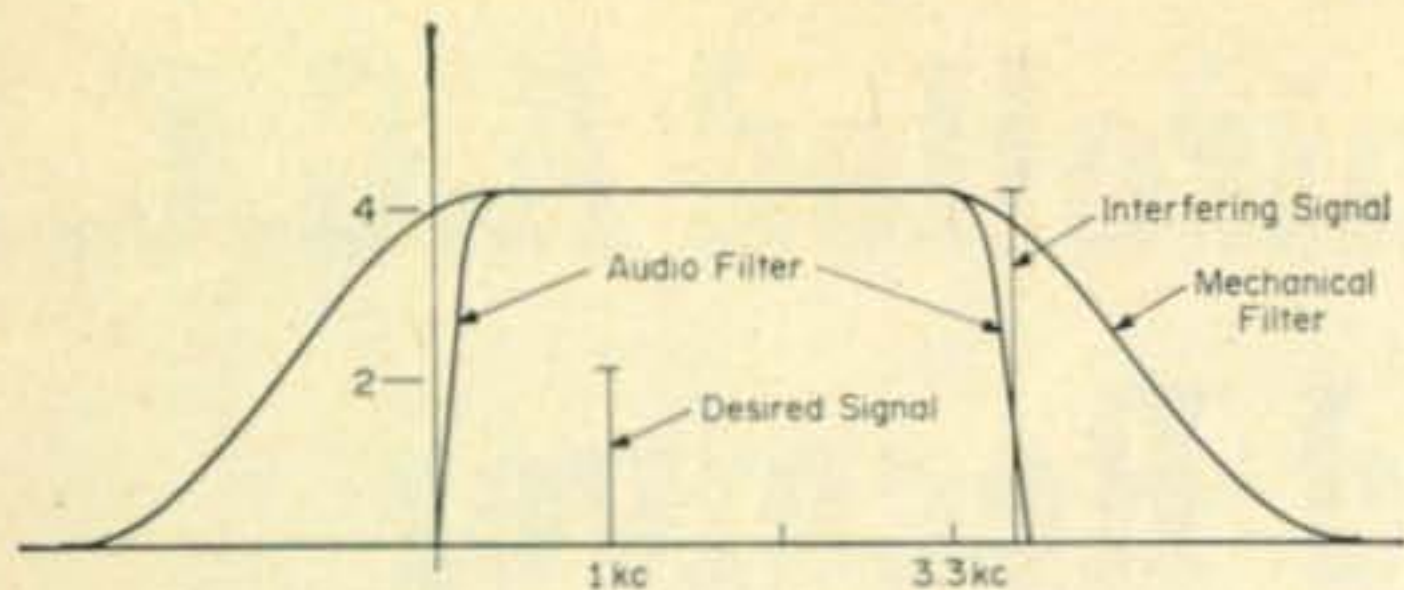


Fig. 3—Shown above are the response characteristics of the receiver with and without the audio filter. The effects upon the desired and undesired signals are described in the text.

ence of four units of interference, the mere introduction of the audio filter, situation B, reduces the interference to one unit. However, the "muting" effect is evident here since the level of the desired signal is only two units. However, in situation C, our improved circuit arrangement produces an output level of desired signal of four units, in the presence of two units of interference. Thus, we see that the signal to interference ratio has been completely transposed from an intolerable 2:4 ratio to a tolerable 4:2 proportion.

Circuitry

The schematic diagram of the circuit used is shown in fig. 4. The basic electronic circuit is that developed by Luick and the audio filter used is the Espy No. 16.296 purchased in the surplus market. This filter was used because it was readily available and it displays the desired flat response with a very steep skirt at about 3 kc. (A filter having even steeper skirts and a much smaller physical size could be used farther back in the audio amplifier, since the Espy unit was designed to operate at a relatively high power output level.) The Espy filter operates at a 500 ohm impedance level and, therefore, a transformer is utilized for matching between the filter and the 4 ohm speaker line.

A second matching transformer is utilized between the speaker line and the input grid of the a.g.c. amplifier. A switch is provided to permit switching the filter in or out without otherwise

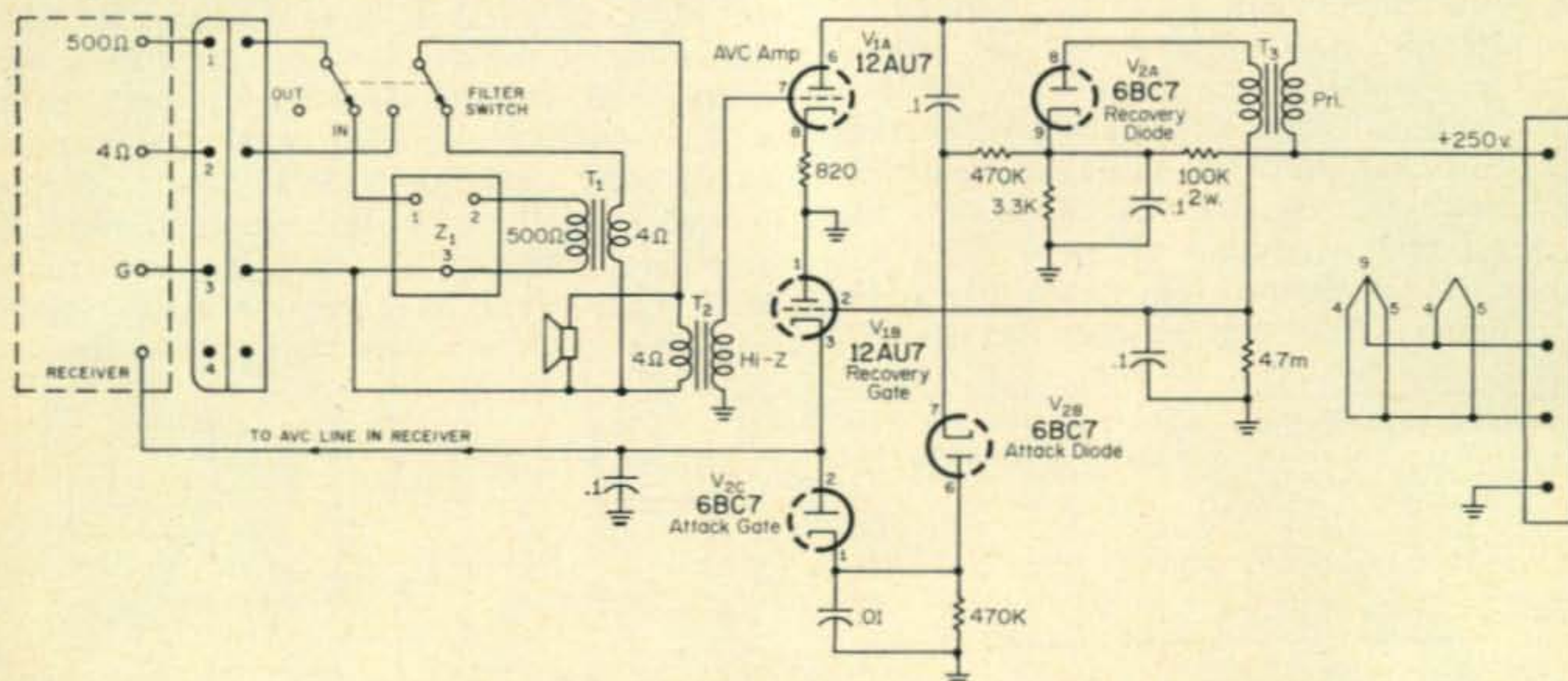


Fig. 4—Circuit of the improved audio a.g.c. circuit. All resistors are 1/2 watt and all capacitors are in mf.

T₁—Universal Output. Stancor A-3841 or equiv.
T₂—Single plate to voice coil. Stancor A-3327 or equiv.
T₃—Single plate to grid. Stancor A-53 or equiv.

Situation	A.G.C. Output	I.F. Gain	Speaker Input	
			Des.	Interf.
A. (fig. 1)	6	1/6	2	4
B. (fig. 2A)	6	1/6	2	1
C. (fig. 2B)	3	1/3	4	2

Table 1—The results of the three situations described in the text are listed in arbitrary units.

disturbing the operation of the circuitry.

Results

The results using this circuit arrangement have been outstanding. The R.F. GAIN control is always operated wide open, at position 10. There is no pumping action regardless of signal strength.

A dramatic change, which results from the use of this circuit arrangement, concerns the effect of the manual AUDIO GAIN control in the receiver. As this control is advanced to the maximum setting there is no noticeable increase in speaker volume, above the comfortable listening level, although the S-meter reading swings higher. The speaker volume for the weakest mobile signals appears to be just as strong as that for the strongest locals. Both I.F. and AUDIO gain controls could readily be removed from the circuit of the receiver, as they are never used!

There is yet another advantage to be gained from the use of the audio a.g.c. circuit. If i.f. derived a.g.c. is used, there is a decrease in gain whenever a strong carrier is tuned to zero beat. This happens when an a.m. signal is tuned in or when the station transmitter is being set on frequency. The use of audio derived a.g.c. eliminates this decrease of gain. Thus, as the transmitter is brought into zero beat there is no audio output and the receiver gain actually increases! This permits the zeroing of the transmitter with much greater accuracy and it is possible actually to "count cycles" as the rig is zeroed on frequency. ■

Z₁—Surplus, Espy # 16.296 audio filter (see text). The homebrew filter described on page 29, April 1964 CQ may be used with no modification.

Circuit Boards— Quick and Easy

BY WILFRED M. SCHERER,* W2AEF

CONVENTIONAL methods of producing printed circuits require a time consuming and usually messy etching process with chemicals. For this reason there probably are many amateurs who steer away from making their own printed-circuit boards. In view of this we think you'll be interested in hearing about a new technique that does away with the fuss and inconveniences ordinarily encountered; in fact, with the XYL's permission, you could even do the work in the comfort of your own living room! The method makes use of Veroboards, a development originated in England.

Unlike the conventional printed-circuit board, the Veroboard already has the circuit strips which instead of being shaped and routed for a specific circuit, merely consist of parallel rows of copper strips which are bonded to a board made of laminated synthetic-resin-bonded paper. The copper strips and boards are punched with evenly spaced holes through which the leads of components may be inserted and then soldered to the strips. The components are thus installed on the circuit board according to the required interconnections afforded by the copper strips. A simple tool is supplied to break the continuity of the strips where connections are not desired.

Other advantages gained by the use of Veroboards is that extensive layout planning is minimized, errors can be easily corrected and modifications to circuitry can usually be made at any

time without discarding an already used board. They should have wide appeal not only for use in home-built gear, but also for commercial and laboratory applications where prototype or even production units are required.

The basic concept and procedure for the Veroboards is shown at fig. 1 using the simple circuit at A; while at B the components are shown as they are mounted on the Veroboard and interconnected with the copper strips. The strips are on the rear of the board with the component leads inserted through the holes from the front of the board. They are soldered to the strips at the holes as indicated by the dark solid dots. Where connections are not required between portions of the circuitry, the copper strips are broken as shown at the points marked X. This is done with the hand tool called a "spot face cutter", or it may be accomplished by drilling or with a penknife. Connections that are required between strips can be made with a wire jumper as shown at Y.

The parts are shown mounted at right angles to the metal strips, but they may also be parallel to the strips as shown by the alternate placement of C_1 (dashed lines), in which case the wire jumper is not needed. Parallel or even diagonal placement, in combination with crosswise-mounted components, often can save space and help compact the layout.

Another arrangement for the same circuitry is shown at C. No breaks in the strips are needed in this particular case. Less horizontal space, but

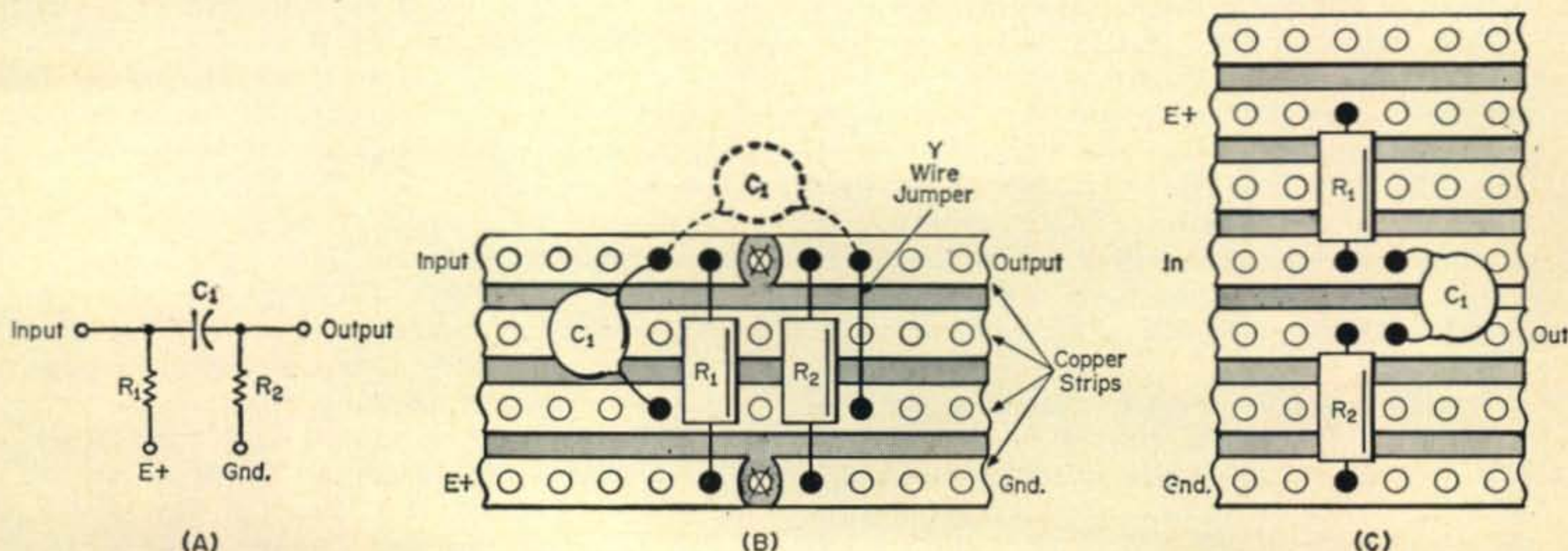


Fig. 1—Basic concept of Veroboard system. Components for circuitry at (A) are shown installed on the Veroboard in two different arrangements at (B) and (C). See text for explanation.

*Technical Director, CQ

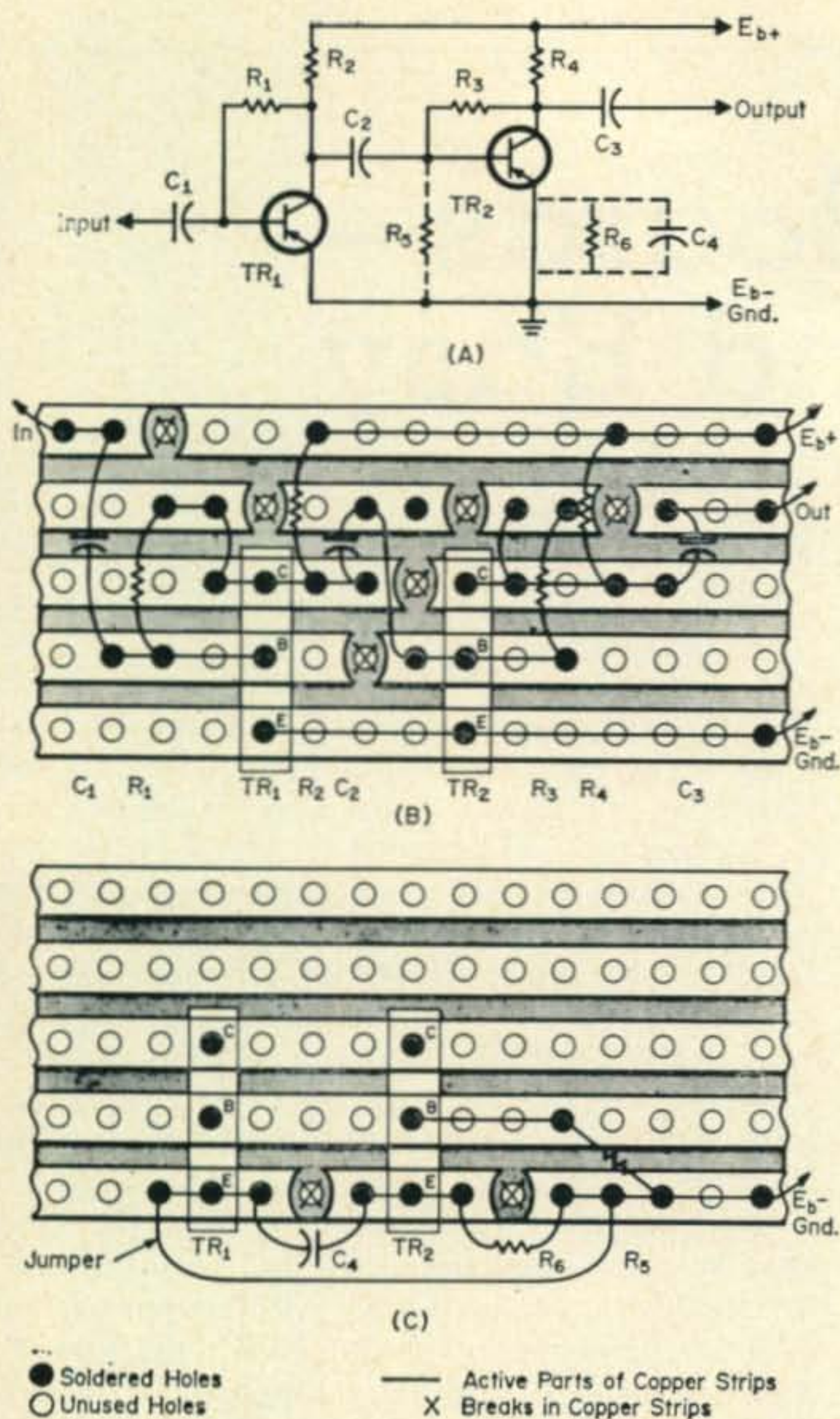


Fig. 2—Circuitry of two-stage transistorized a.f. amplifier (A) as installed on Veroboard at B. At C is shown how circuit modifications (dashed components at A) can be added to the Veroboard.

more vertical space is required on the board; however, as a general rule this layout may be more convenient, running the voltage-supply line on a strip through the center of the board and using the outer strips for the ground busses. Space also may be saved by mounting components vertically in relation to the board itself, in which case they'll stand up "in the air", so to speak. When necessary, the boards easily may be cut down to size by cutting, or they may be drilled for mounting of special components.

Now let us go a bit further and take a look at fig. 2 where the schematic for a simple two-stage transistor a.f. amplifier is shown at A, with the arrangement on the Veroboard at B. Here all the components are placed at right angles to the copper strips. This usually will be the quickest and simplest way of setting up the layout. Note that all the parts are arranged in almost the same sequence as they appear in the schematic.

Now, suppose we wish to rearrange the bias circuitry (R_5) and add emitter bias too (R_6 & R_4). Fig. 2 illustrates how modifications, such as these, can be made to existing circuitry without requiring a new board or a re-etching job which would be the case if conventional printed-circuit board techniques were used. This also

shows how components may be placed parallel to or diagonally across the copper strips.

The Veroboard method also simplifies the planning of the layout which may be done on paper beforehand, since you don't have to figure out just where to route the circuitry to avoid short circuits and to get away from a maze of criss-crossed leads. The circuit runs are already there, so all you have to do is link them with the desired components which are laid out sequentially to follow the required circuit. You then indicate where the breaks are needed to be made in the strips.

When planning the Veroboard layout on paper, you can just simply draw a number of parallel lines on the paper to represent the copper strips and then draw evenly spaced small circles along each line to represent the punched holes. On the other hand, you can obtain Veroboard design sheets which already are drawn to represent the boards and on which the rows of holes are identified numerically and alphabetically for easy identification of individual hole locations. These can be correlated to the actual board during assembly by attaching to the board available adhesive cellulose tapes that are similarly marked with numbers and letters.

To see how you may construct units using the Veroboards, we suggest you refer to page 28 where you'll find a "Veroboarded" 100 kc crystal calibrator you can build yourself. It'll be handy to have around the shack or to use in the car.

The Veroboards are available in various sizes and with different width and spaced copper strips along with a number of different "pitches", or spacing between holes.

More sophisticated type Veroboards also can be had with parallel copper strips on both sides of the board, or with the strips on one side at right angles to those on the opposite side. Other variations have the copper strips gold plated at a tongue on one end, so the board can be plugged into an edge-type connector. This, together with plastic guides in a "Verorack" assembly, allows modular construction using plug-in circuit boards. There are many additional accessories such as special terminal pins, transistor and diode holders, component jigs, etc.

Of special interest to the amateur home-constructor is a low-priced kit consisting of six assorted Veroboards ranging in size from $3\frac{3}{8}'' \times 3\frac{1}{2}''$ to $2\frac{1}{2}'' \times 7''$, a spot face cutter and complete instructions on how to design a layout directly on the boards. This kit is the Model BK-6 which sells for \$5.95.

A more elaborate package is available for the design engineer. It is the Vero Laboratory Development Kit Model VBK-7 which consists of eight assorted Veroboards up to 18" long, a plain Veroboard with a staggered grid of holes and without copper stripping, 500 terminal pins, terminal-pin insertion tool, a spot face cutter, reproducible design sheet and instructions on the Vero-circuit concept. Price is \$29.95.

For further details and catalogue, we suggest you write to Vero Electronics, Inc., 48 Allen Blvd., Farmingdale, N.Y. ■

RTTY From A to Z

BY DURWARD J. TUCKER,* W5VU

Part XVII

The design and construction of a polar relay keyer test set was covered last month. This part covers the operation of this set. The I-193-C polar relay test set was mentioned in Part X and no further mention was made of the set because of its scarcity at the time. Since that time they have been advertised on the surplus market from a number of sources. It is for this reason that it is worthwhile to devote some space to this very important piece of test equipment.

CONSTRUCTION of the test set was discussed last month and it can now be used to measure distortion percentages as outlined below.

Operation Of The Set

The signal output from a square wave generator should be fed into one of the input jacks (J_1 or J_2) of the polar relay keyer test set. The level of the input triggering signal should be set so that the two 6AQ5 keyer tubes are keying properly as indicated by the regular flashing of the NE-51's.

At this point it might be well to call attention to the fact, by way of review, that the 6AQ5 tubes key (*mark*) on the *negative half* (less positive) of the square wave input signal and the positive half of the input wave represents *space*. If this is not clear, review the operation of V_{1A} and V_{1B} in the section on circuit operation.

The vertical input to the scope should be connected to the set through J_6 , with the ground terminal of the scope connected to the sleeve of the plug. This makes it possible to monitor the keying action of the 6AQ5 keyer tubes. The scope should be adjusted so that one cycle can be observed, as in fig. 102. The *mark* and *space* of this signal trace should be equal if the keyer

is in proper adjustment. This assumes that the positive and negative halves of the square wave input signal are equal.

If the *mark* and *space* of the scope trace are uneven, with a proper input signal, it indicates that the keyer set is not in proper adjustment. It is possible that the 6AQ5's are biased beyond plate current cut-off. The grid bias potentiometer should be readjusted while watching the trace on the scope. Any distortion present at this point will be passed on to the polar relay under test, since it is the plate current of the keyer tubes that passes through the signal winding of the polar relay. When no distortion is indicated at this point, one is now ready to check the keying action of the relay output terminals 1, 4 and 5.

Remove the scope monitor plug from J_6 and plug it into J_8 . It may be necessary to readjust the scope to get a trace such as shown in fig. 102. Don't expect the *mark* and *space* trace to be equal unless the polar relay under test happens to be in *perfect* working order. As in the case of the test sets covered earlier, the object is to adjust the polar relay so that the *mark* and *space* on the scope trace are equal.

Amateurs usually use contacts 1 and 4 so that a closing of the contacts represents *mark* and an opening of these contacts represents *space*, with contact number 5 not being used

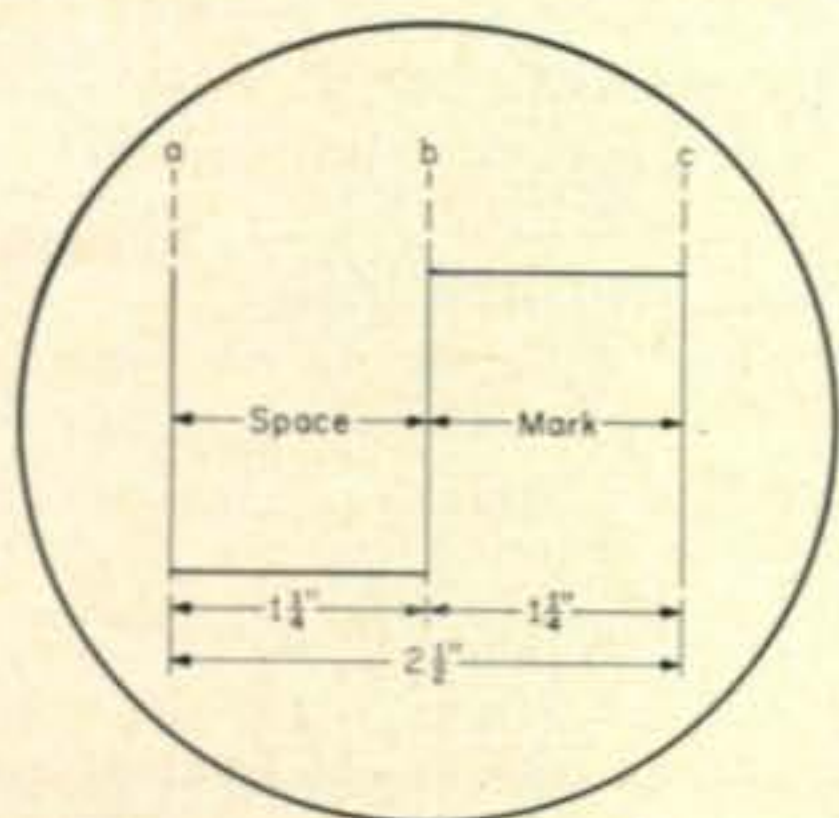


Fig. 102—Scope trace of one cycle of signal in the plate circuit of the keyer tubes.

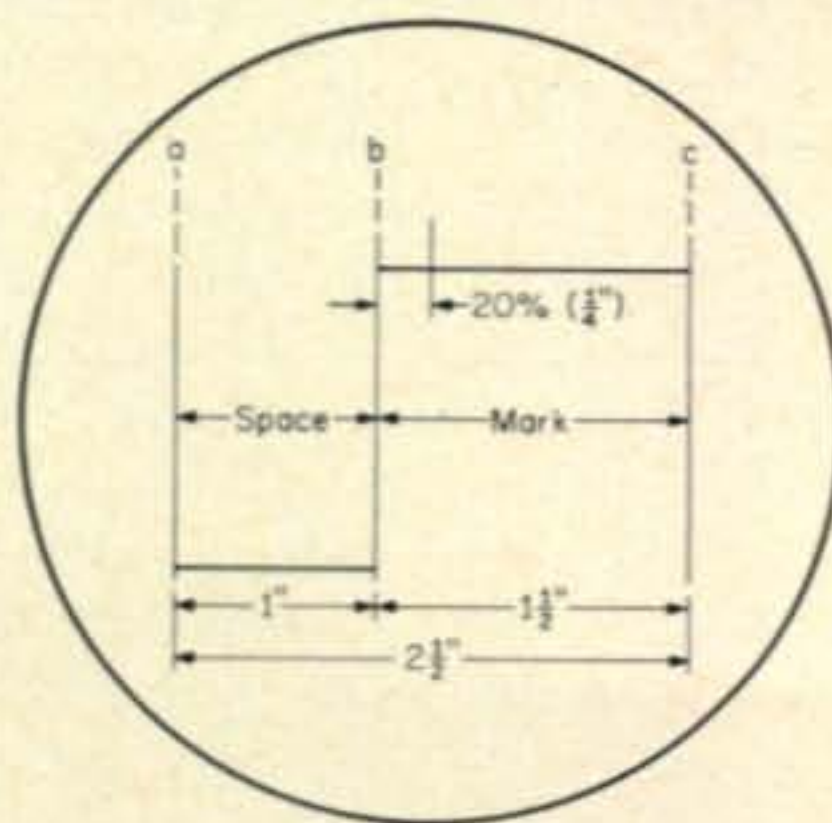


Fig. 103—Scope trace of one cycle of keyed signal, keyed by the polar relay, showing the presence of *mark* distortion. This is indicated by the *mark* trace being longer than the *space*.

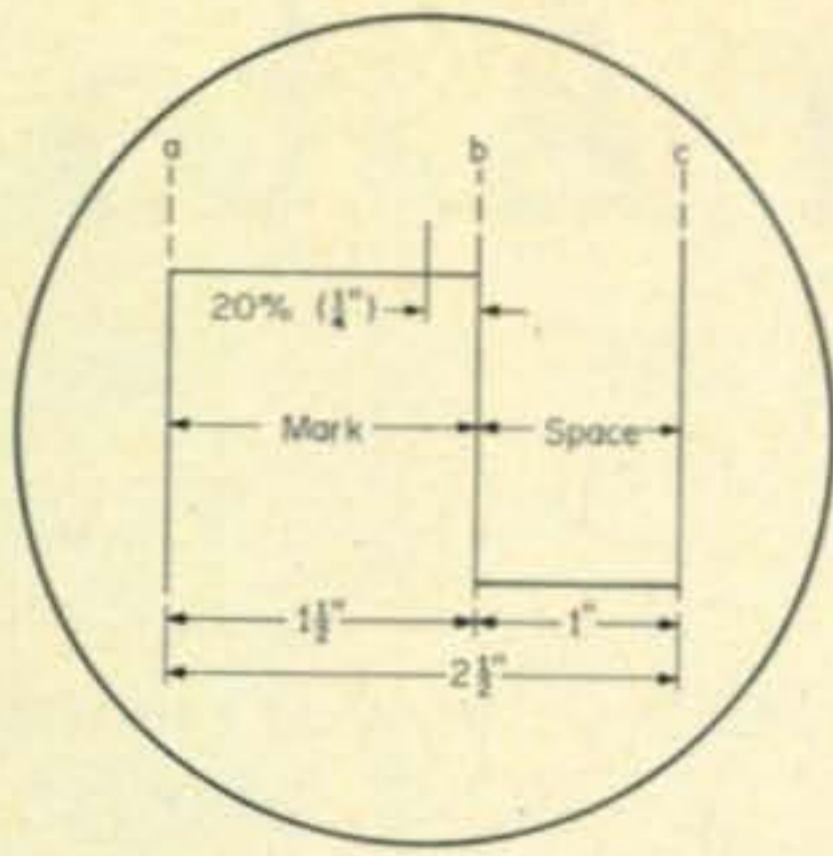


Fig. 104—The same scope trace shown in fig. 105, except the scope is adjusted so that *space* follows, instead of precedes, the *mark* pulse. The scope does not indicate if it is end distortion, as shown here, or bias distortion as shown in fig. 105. This is explained more fully in the text.

except to reverse the action. When the action is reversed, then contact number 4 is not in use. The s.p.d.t. toggle switch on the right side of the front panel marked *s* and *M* is for reversing the action so that contacts 1 and 4 or 1 and 5 may be used. Any relay under test should be checked for each condition by operating this switch.

Determining Distortion Percentage

It will be noted that the measurements in inches of the trace on the scope were given in fig. 102. A special scale with percentages marked thereon could be made up and placed over the face of the scope. However, it was considered that it was as easy to use a small ruler and simple arithmetic to determine the percentage of distortion.

Let us consider that distortion is present in the keying circuit of the polar relay under test, as indicated in the trace of fig. 103. It will be recalled, from a study of RTTY bias and end distortion, that a longer *mark* pulse means a shorter *space* pulse or *vice versa*. The exact amount that one or the other is lengthened is the same amount that the other pulse is shortened.

The trace of one cycle (one *space* and one *mark*) as shown in figs. 102 and 103 was 2½ inches long. In fig. 103 the *space* (*a-b*) was one inch long, whereas the *mark* (*b-c*) pulse was one and one-half inches long. The length of the whole cycle (one *space* and one *mark*) was two and one-half inches. Thus, $2.5/2 = 1\frac{1}{4}$ inches, which represents 100% as the length of the *mark* and *space* if distortion did not exist as shown in fig. 102. The *mark* space was elongated ¼ inch or $0.25/1.25$ or 20%, which indicates 20% mark distortion. The important question is: Is it *bias distortion* indicated by the example of fig. 103, or is it really *end distortion*? The trace on the scope could have been adjusted, just as easily, so that the *mark* pulse came first, as in fig. 104. One must conclude that it takes more sophisticated equipment than this to distinguish between the two. This certainly shouldn't bother the RTTY'er as he shouldn't have a fondness for either. It might satisfy one's curiosity to know if it's bias distortion

or end distortion, but it's far more important to get rid of it, whatever it is!

Other Test Set Uses

In monitoring the trace of a polar relay keying action, one not only is able to observe distortion as above outlined, but other relay faults as well. Contact bounce, dirty contacts, or improperly aligned contacts can also be detected. These show up as a ragged, or discontinuous trace, whiskers on the trace, *etc.*, instead of a smooth, straight line, as shown in figs. 102, 103 and 104. In addition, the test set can also be used in connection with a distortion measuring set (plugged into *J₉* or *J₁₀*) to read the percentage of distortion present.

I-193-C Polar Relay Test Set

The increasing availability of the I-193-C Polar Relay Test Set on the surplus market, from a number of sources, warrants a general discussion of this important piece of test gear for the RTTY'er. The unbelievable prices at which these units are being advertised on the surplus market makes it one of the best surplus buys around. A further incentive for covering this test set is that it is for the testing of the popular polar relays previously discussed. (215-A, 255-A, and D-164816).

Polar relays are so much a part of RTTY that the addition of an I-193-C polar relay test set to one's shack should certainly enhance one's pleasure of RTTY. This test set is a good companion instrument to the polar relay keyer test set just covered. One is used in checking and measuring relay distortion and the other is used as an aid to getting rid of the distortion.


Basically, the test set has three purposes. Probably the most important of these is in the testing and adjusting of polar relays for bias distortion. The second, and possibly the next in importance is in the use of the set for making proper sensitivity adjustments. Lastly, the test set contains a dot-generator circuit. This signal is of inestimable value around any RTTY'er's shack. All of these features will be covered in detail.

Physical Description

The test set was made in three models: I-193-A, I-193-B and I-193-C. We are principally concerned with the I-193-C model. The test set is considered portable as it is mounted in a trunk type carrying case with handles, although it weighs 63 pounds. The test set panel is standard 19 inches wide and drilled for rack mounting. No adapters are required if one desires to remove the set from its portable carrying case and mount it in a standard 19 inch rack or rack cabinet.

Figure 67 gave a general view of this test set. All of the controls, sockets, power connections, *etc.*, are located on the front panel. The test set uses two polar relays which plug into two of the three sockets located in the compartment under the hinged metal lid located at the left edge of

Fig. 105—Schematic of the 20 c.p.s. 1-193-C Test Set oscillator circuit.

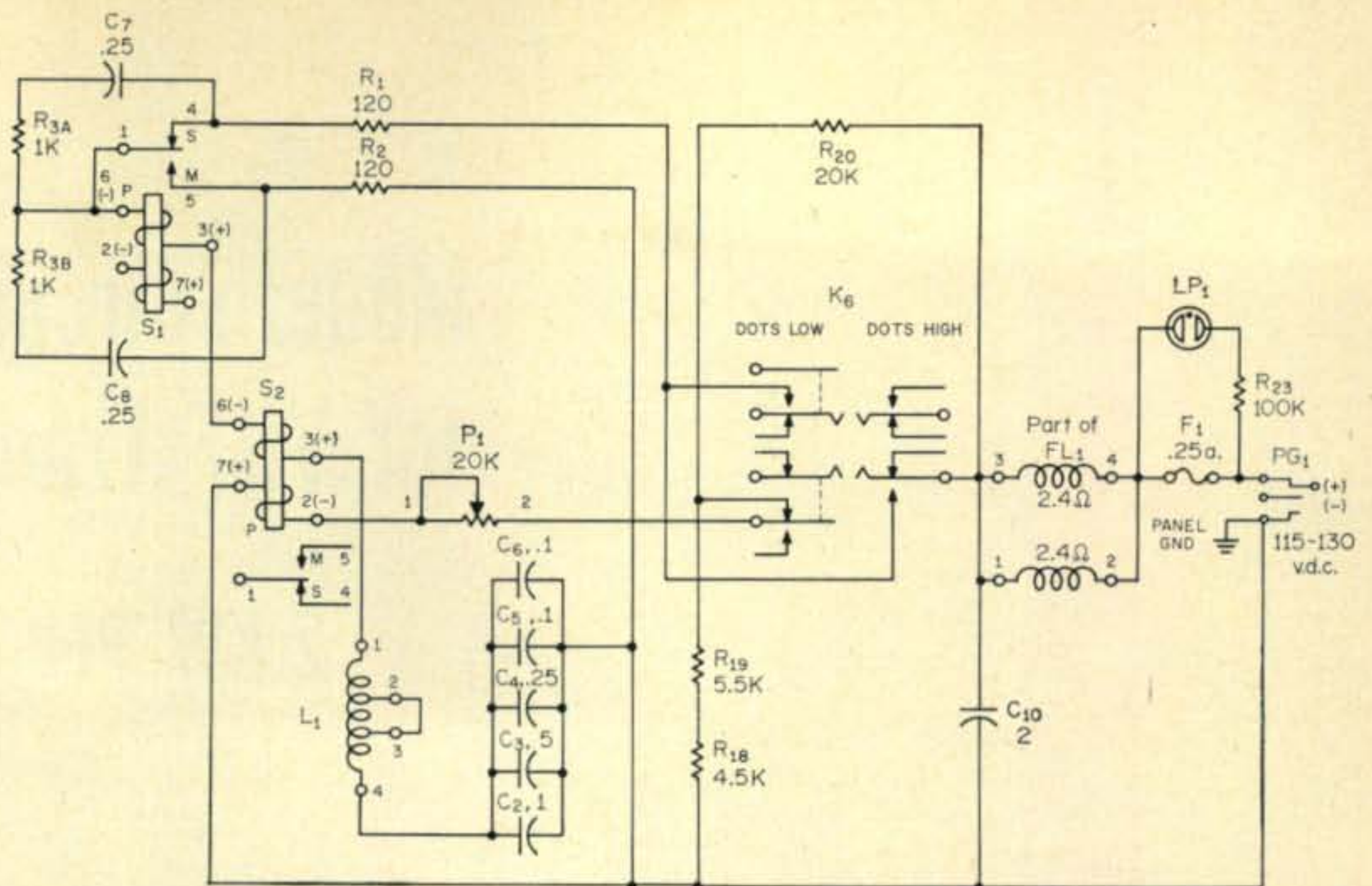

the front panel. The extra socket here is for storing a spare relay. Two spare relays are also supplied with the test set and they are stored by being plugged into two of the three sockets for spare relays. This is located in the compartment under the hinged metal lid located at the right edge of the front panel. These compartments allow space for storing the various cords supplied with the set. A permanent type instruction sheet occupies about two-thirds of the inside surface of the lid. The other inside lid space is taken up with a spare fuse and lamp case, and a rather extensive set of polar relay tools. The thickness gauge contains 12 leaves for thicknesses ranging from 0.002 inch to 0.018 inch. These gauges are used for adjustment of the relay contact gap for armature travel, as previously outlined. The burnisher tool is supplied with six burnisher blades and six wire burnishers that all fit into the fountain pen type barrel handle. This tool is used in cleaning and burnishing relay contacts. The adjusting keys are to be used to adjust relay contact gap and pole-piece

screws. The file is a jewelers type, #6 cut, and should be *used sparingly* to dress relay contacts. The four polar relays and relay maintenance tools alone are worth a considerable portion of the purchase price being asked for these test sets on the surplus market.

Electrical Description

The chief use for the I-193-C Polar Relay Test Set is, as the name implies, to test and aid in the adjustment of polar relays. The primary tests are for bias and for sensitivity of operate-non-operate current values. In addition, the test set may be used as a source of dot signals which are actually equally spaced on-off electrical impulses. This feature was incorporated into the test sets for lining up other teletype or teletypewriter equipment, besides the polar relay. Such a signal may be used to drive the Polar Relay Keyer Test Set, instead of the square wave generator.

[Continued on page 90]


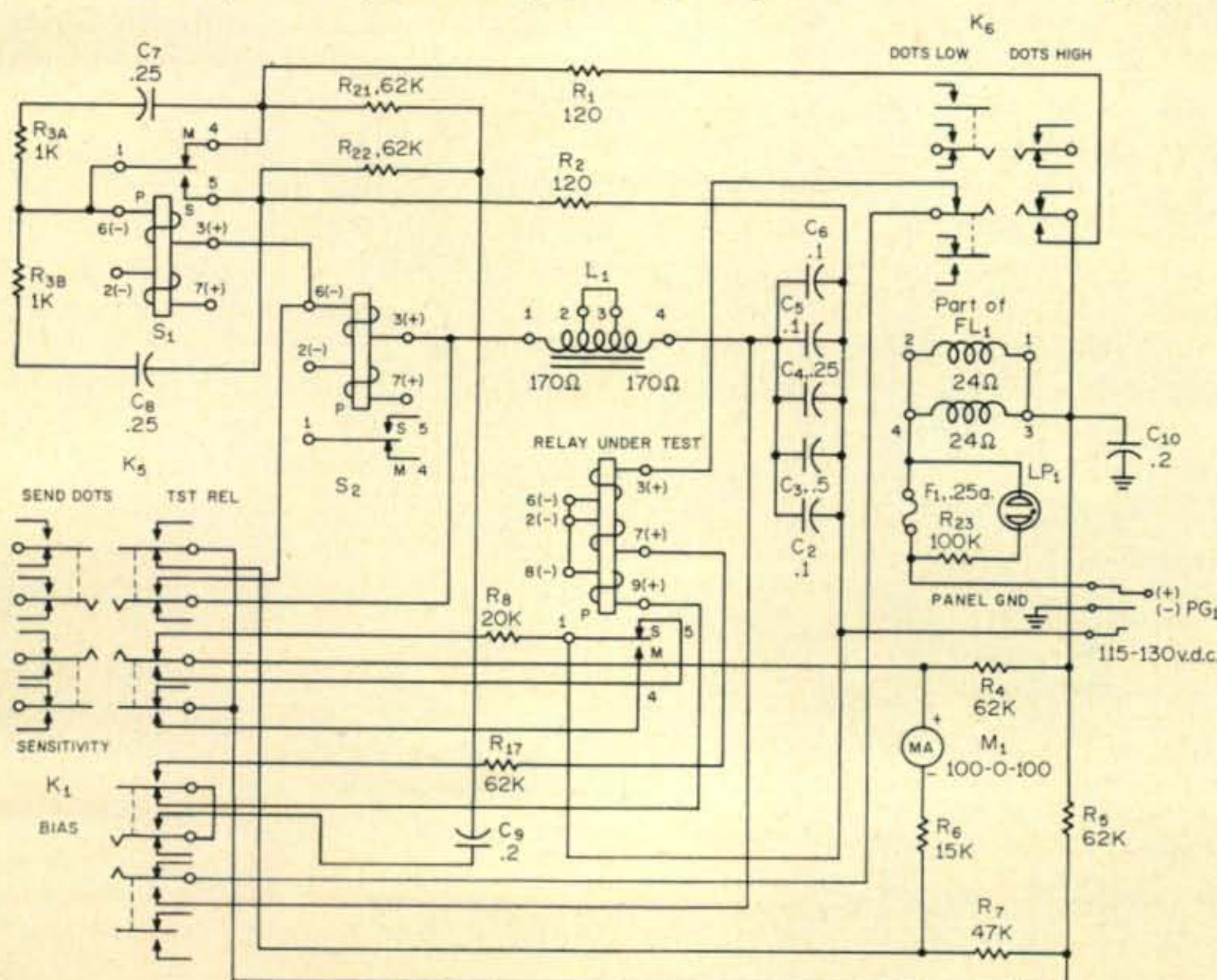


Fig. 106—Schematic diagram of the 1-193-C Test Set circuit for testing bias of a relay under test.

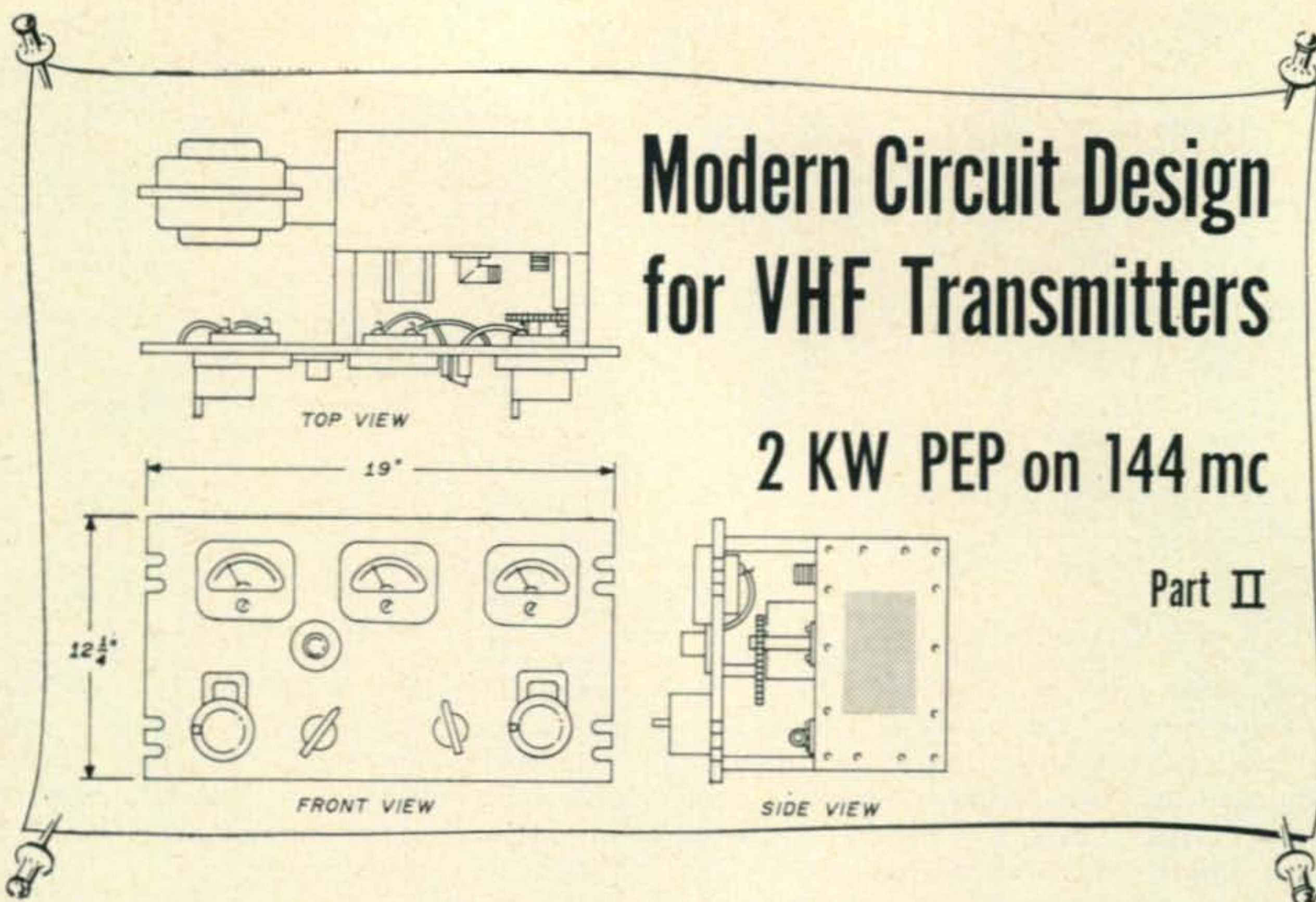

BY H. C. BARBER,* W6GQK; W. I. ORR,† W6SAI; R. RINAUDO,‡ W6KEV AND R. SUTHERLAND,† W6UOV.

Part II of this article describes the construction of a 2 kw p.e.p. linear amplifier that loafs along at the legal amateur power level and requires less than ten watts of drive.

THE serious v.h.f. operator has a need for high power transmitting equipment if he is interested in Oscar IV, meteor scatter, moon bounce or other exotic forms of long-distance v.h.f. communication. In addition, if he contemplates s.s.b. operation, he may be desirous of running the "two kilowatt p.e.p." limit.² Equipment capable of achieving this power level on a reliable basis is scarce in the world of hamdom, although such gear is fairly commonplace in the commercial fields. Many instances exist where commercial gear has been patterned after equipment designed for radio amateur use, so perhaps there is justification for purely amateur gear designed around a proven item of commercial equipment.

This article describes a unique 144 mc high-power linear amplifier, patterned after a 5 kilowatt amplifier that has proven itself in space communication work in the v.h.f. spectrum.

Scaled down to amateur size and power level, and making use of the new Eimac 4CX1000K v.h.f. tetrode, this compact continuous service kilowatt unit combines high power gain, stability and good linearity in a small package. This amplifier design, moreover, may be further scaled down for use at a lower power level, employing a single tube of the 4CX250B family. Requiring no neutralization, and straightforward in adjustment and tune-up, this linear amplifier is an interesting example of up-to-date v.h.f. design techniques. Even though many amateurs may not care to duplicate this unit in its entirety, many of the unique circuits and layout may be well adapted to other v.h.f. equipments.

The previous article³ discussed some of the problems overcome in the design of a high power v.h.f. linear amplifier and the techniques that were employed to solve these problems. This article describes the construction of a 144 mc linear amplifier employing these previously discussed techniques and which is capable of continuous operation at a maximum power level of 2700 watts (p.e.p.). This margin allows a reasonable safety factor at the maximum amateur power input limit and insures that the equipment will not blow up at a crucial moment when an existing DX record is about to be shattered.

The 4CX1000K amplifier employs a half-wave linear plate tank circuit and the grounded screen

*45 Sherwood Court, Millbrae, California.

†Eitel-McCullough Inc., San Carlos, California.

²The F.C.C. definition of the so-called "two kilowatt p.e.p." limit is: "The maximum d.c. plate power input to the radio frequency tube or tubes supplying power to the antenna system of a single-sideband suppressed-carrier transmitter, as indicated by the usual plate voltmeter and plate milliammeter, shall be considered as the "input power" . . . provided the plate meters utilized have a time constant not in excess of approximately 0.25 second, and the linearity of the transmitter has been adjusted to prevent the generation of excessive sidebands. The "input power" shall not exceed one kilowatt on peaks as indicated by the plate meter readings."

³Barber et al., "2 KW PEP on 144 mc," *CQ*, Nov. 1965 page 30.

configuration discussed in the previous article. Overall amplifier efficiency in the Class AB-1 linear mode is unusually high for these frequencies, being of the order of 60 percent or better at a plate potential of 2500 volts. As the practical limit of plate efficiency of a Class AB-1 linear amplifier is no more than 68 percent, it can be seen that tank circuit losses of this unusual design consume only about 8 percent of the output power. Most garden variety v.h.f. tank circuits exhibit losses ranging from 20 to 50 percent.

At a plate potential of 3000 volts the power gain of this linear amplifier is over 22 decibels at the maximum power level, and the peak driving signal power is only 9.5 watts. At a two kilowatt p.e.p. level (3000 volts at 666 ma) the peak driving power is about 6.3 watts. For c.w. or f.m. service at one kilowatt input, the amplifier is capable of 625 watts power output with a driving power of 5.2 watts, and as an a.m. linear amplifier at the one kilowatt input level, a fully modulated 250 watts output may be obtained with only 1.25 watts of drive power.

Thus, in these classes of service, this compact "black box" is capable of better than 22 decibels power gain up to the maximum power level of 2700 p.e.p. on a continuous, 24 hour basis. Cost of all components is less than five hundred dollars, including the tube and socket, so on a



Fig. 8—Front view of a compact two kilowatt p.e.p. linear amplifier for the v.h.f. man. This high power 144 mc linear is suitable for s.s.b., a.m., f.m. or c.w. operation, requiring less than 10 watts drive power to reach the maximum legal amateur power level. The amplifier is mounted behind a standard 12 1/4" relay rack panel. Across the top of the panel (l. to r.) are the plate, grid and screen milliameters, with the grid tuning capacitor (C_2) centered below. At lower left and right are the counter dials for the OUTPUT LOADING control and PLATE TUNING (C_3). Between the counter dials are the grid and screen meter reversing switches. The amplifier enclosure is spaced behind the panel by sections of rectangular aluminum rod and the 4CX1000K mounts in a horizontal position within the enclosure. At the right end of the enclosure are the ventilation holes above the anode of the tube.

watts-per-dollar basis, it is difficult to surpass the high power economy of this modern v.h.f. amplifier package.

Circuit Features

A simplified circuit diagram is shown in fig. 7. The 4CX1000K power tetrode is operated with the screen at d.c. and r.f. ground potential, with the positive terminal of the screen supply grounded and the screen and bias supplies placed "below chassis ground." This is done to eliminate the screen r.f. bypass capacitor in order to achieve maximum intra-stage isolation. Because of the excellent isolation between input and output circuits, neutralization is neither desired nor required.

The plate circuit is composed of a half-wave, shunt-fed, inductor (L_3, L_4) with the tube positioned at the center of the line. The r.f. output loading tap is placed on one segment of the line. Resonance is established at the operating frequency by plate tuning capacitor C_3 , which is a simple two plate assembly with one plate mounted to the anode cooler of the tube.

Two ceramic transmitting capacitors in parallel are used as blocking capacitors for each segment of the plate line inductors. So-called "TV-type" ceramic capacitors should *not* be used, as the circulating tank current is of the order of 40 amperes at maximum power level, and a large portion of this r.f. current flows through the blocking capacitors. The TV capacitors are not rated for such severe operating conditions.

The loaded Q of the plate tank circuit is determined almost entirely by the ratio of plate load impedance to reactance of the output ca-

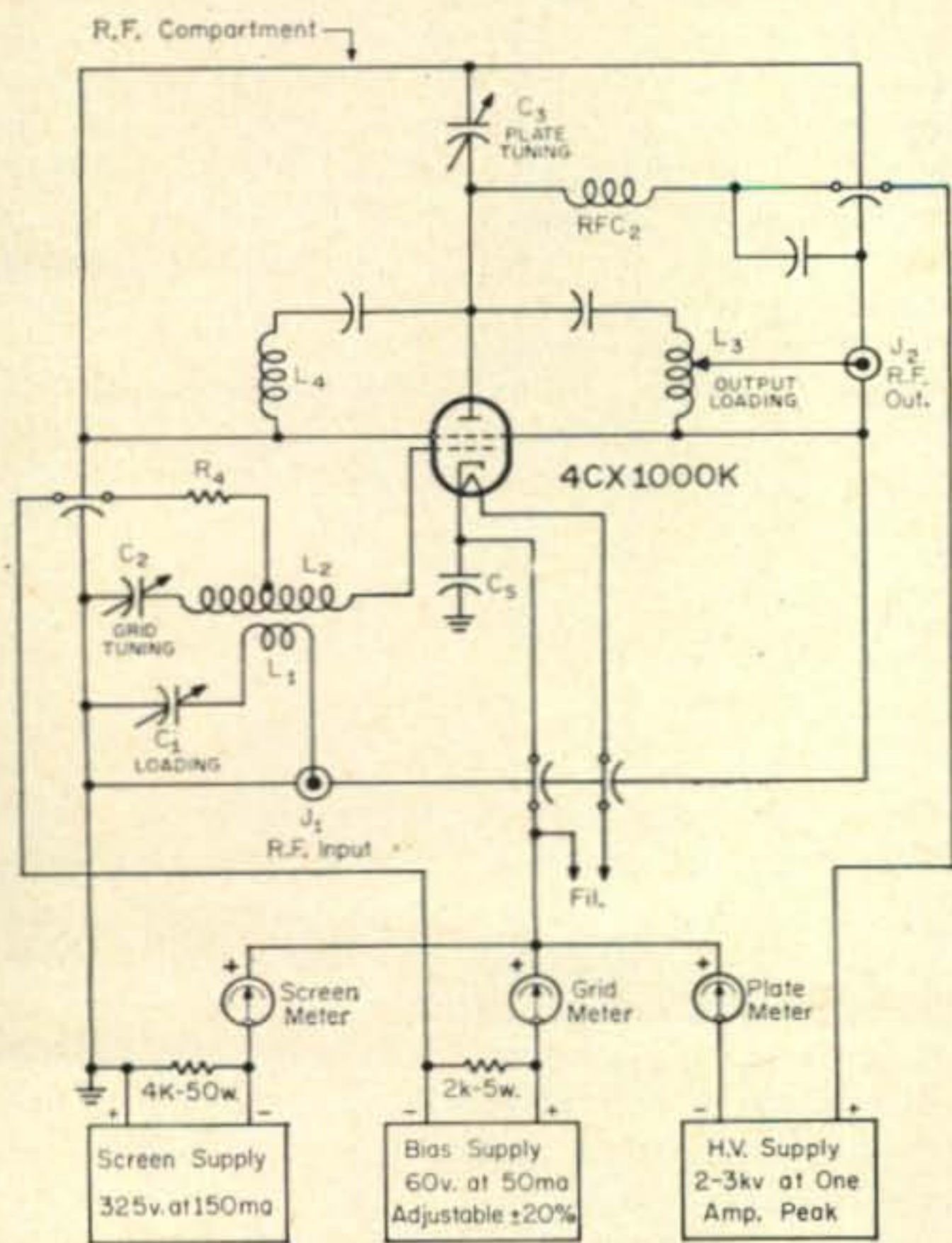


Fig. 7—Simplified schematic of 4CX1000K amplifier. The screen circuit of this v.h.f. amplifier is operated at d.c. and r.f. ground potential with bias and screen supplies placed "below chassis ground". The cathode capacitor (C_s) is an integral part of the Eimac SK-820 socket. Grid circuit components are placed in "r.f. tight" compartment and the special v.h.f. socket prevents intra-stage r.f. currents to flow between plate and grid circuits. The plate tank circuit (L_3, L_4) is a half-wave line with the 4CX1000K placed at the center. All power leads entering the compartments are suitably bypassed to keep the r.f. where it belongs.

capacitance of the tube. This capacitance is a fixed value and the load impedance is determined by the operating conditions imposed by the tube. Loaded Q therefore is relatively inflexible, although higher than normally encountered at lower frequencies. Even so, good tank circuit efficiency can be readily obtained if the unloaded Q is sufficiently high. It is in this case, being approximately 1000. Unloaded circuit Q of this magnitude is difficult to achieve at lower frequencies as the unloaded Q of good coils usually falls below 400. The loaded Q in this instance must be of the order of 10 to 20 to achieve a reasonable degree of tank circuit efficiency.⁴ One disadvantage of high tank circuit Q (usually demanded by high-C v.h.f. tubes) is that a corresponding high value of r.f. circulating current flows. (Restricted bandwidth could also be a disadvantage in some applications). Wide leads having low r.f. resistance are required to carry this current. Ordinary lead solder is *out* as its r.f. resistance is too high, and high temperature silver solder is used for connections in v.h.f. tank circuits operating at power levels in excess of a few hundred watts. Alternatively, the joints may be physically bolted together with brass bolts, provided the r.f. current does not pass through the body of the bolt.

The coaxial output receptacle, J_2 , is a *Type N* fitting, with the flexible strap jumper from the moveable tap on inductor L_3 bolted to the center pin of the fitting. Appreciable current flows through the jumper and a soldered joint at the receptacle has sufficient r.f. resistance at 144 mc to run hot enough to melt the solder at full amplifier input. The older SO-239 style coaxial receptacle is *not* recommended at this point, as the matching PL-259 coaxial plug does not make adequate contact to the shield of the coaxial line, which is only soldered at four points within the plug.

The resonant grid circuit is a half-wave line (L_2), capacitance loaded at one end by grid tuning capacitor C_2 and at the opposite end by the input capacitance of the 4CX1000K. Bias is applied to the tube through the grid line, via isolating resistor R_4 placed at the minimum r.f. voltage point of the circuit. Use of a v.h.f. choke at this point instead of the isolating resistor resulted in a violent 10 mc parasitic oscillation which is entirely absent when the resistor is employed.

The point of minimum r.f. voltage is at the electrical center of the half-wave grid line which happens to fall very close to the socket terminals. The input capacitance of the 4CX1000K is approximately 80 mmf and a simple parallel resonant tank tends to "disappear within the tube" at 144 mc. A half-wave line made up of the tube capacitance and lead inductance permits sufficient tank circuit external to the tube to efficiently couple excitation to the tube. To

⁴Tank circuit efficiency is defined as:

$$\text{Eff} = 100 \frac{Q_u - Q_l}{Q_u}$$

Where Q_u is the unloaded Q , and Q_l is the loaded Q .

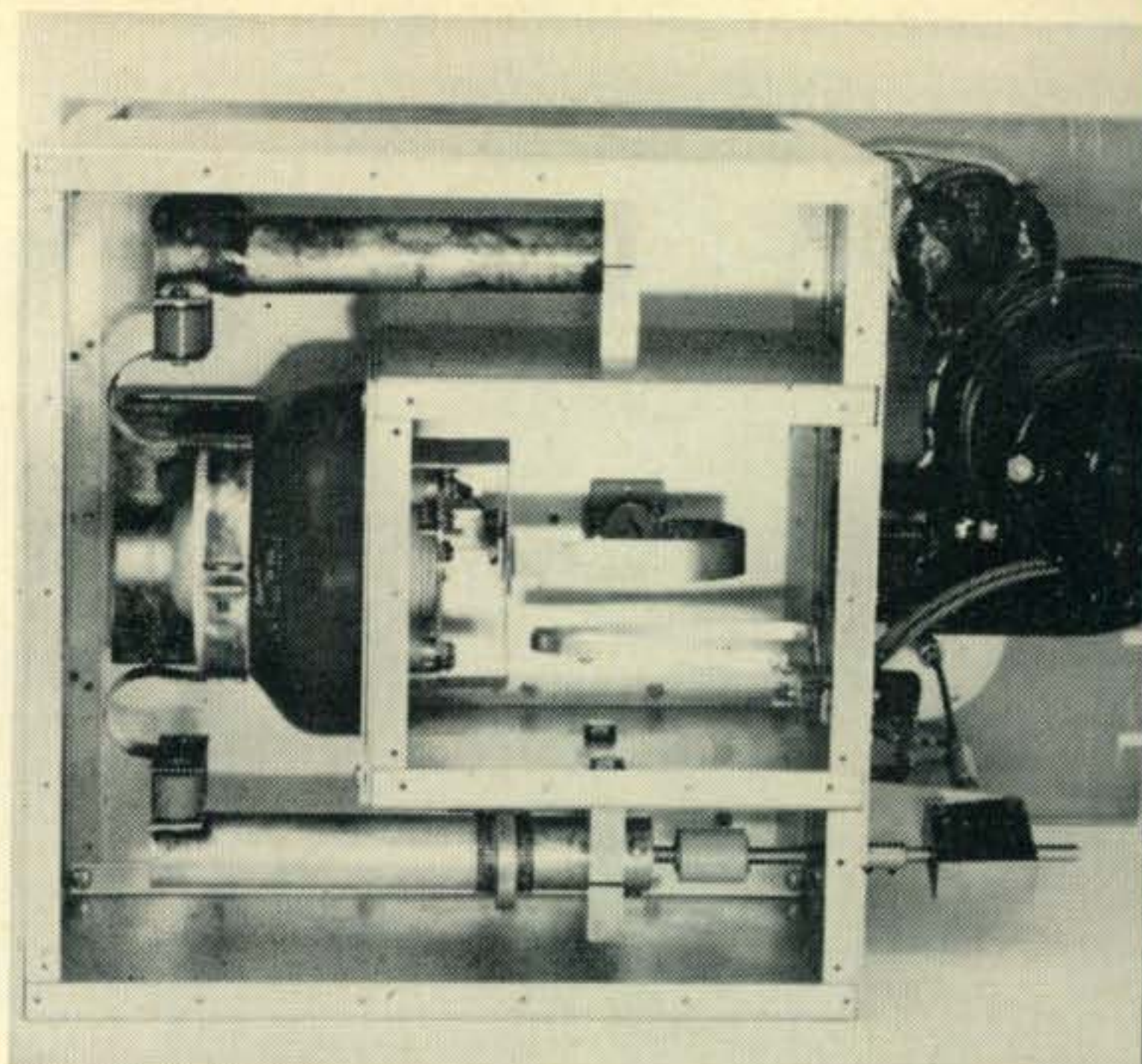


Fig. 9—Interior view of the amplifier enclosure with the rear plate removed. The enclosure normally mounted on its side, is shown in a vertical position. The 4CX1000K, air chimney, and special socket are placed atop the center of the grid compartment, with cooling air passing into the "bottom" of the compartment. The three grid terminals of the 4CX1000K socket are strapped together and the junction is bolted to the U-shaped grid inductor (L_2). The opposite end of L_2 terminates at the GRID TUNING capacitor, C_2 , mounted to the front wall of the compartment. Below the grid assembly at one side is the input link (L_1) with LOADING CAPACITOR, C_1 , mounted to the wall of the compartment. Mounting brackets for the two plate inductors are affixed to the outer side walls of the compartment. The squirrel-cage blower is mounted with a piece of screening across its mouth to restrict r.f. leakage through the vent opening. At the side of the blower is the right-angle drive and flexible shaft for the OUTPUT LOADING adjustment, visible on one anode inductor. The moveable tap is driven via a threaded rotary shaft integral to the plate line.⁵

satisfy this requirement, the grid line is made of copper strap and has an unloaded Q of about 300. Loaded Q is close to this figure as the grid circuit is swamped only by the circuit losses and input conductance of the 4CX1000K. Grid driving power is theoretically zero. In practice a few watts are required to develop the proper voltage at the grid of the tube because of the circuit losses.

Because of the high value of circuit Q and the appreciable capacitance of tuning capacitance C_2 , grid circuit tuning is quite sharp and resonance must be reestablished for frequency excursions of more than a few hundred kilocycles.

Metering and Power Circuits

Separate d.c. milliammeters are used to mon-

⁵A set of blueprints is available at a cost of one dollar which covers, in detail, the various plate circuit components. Write: Amateur Service Dept., Eitel-McCullough, Inc., San Carlos, Calif.

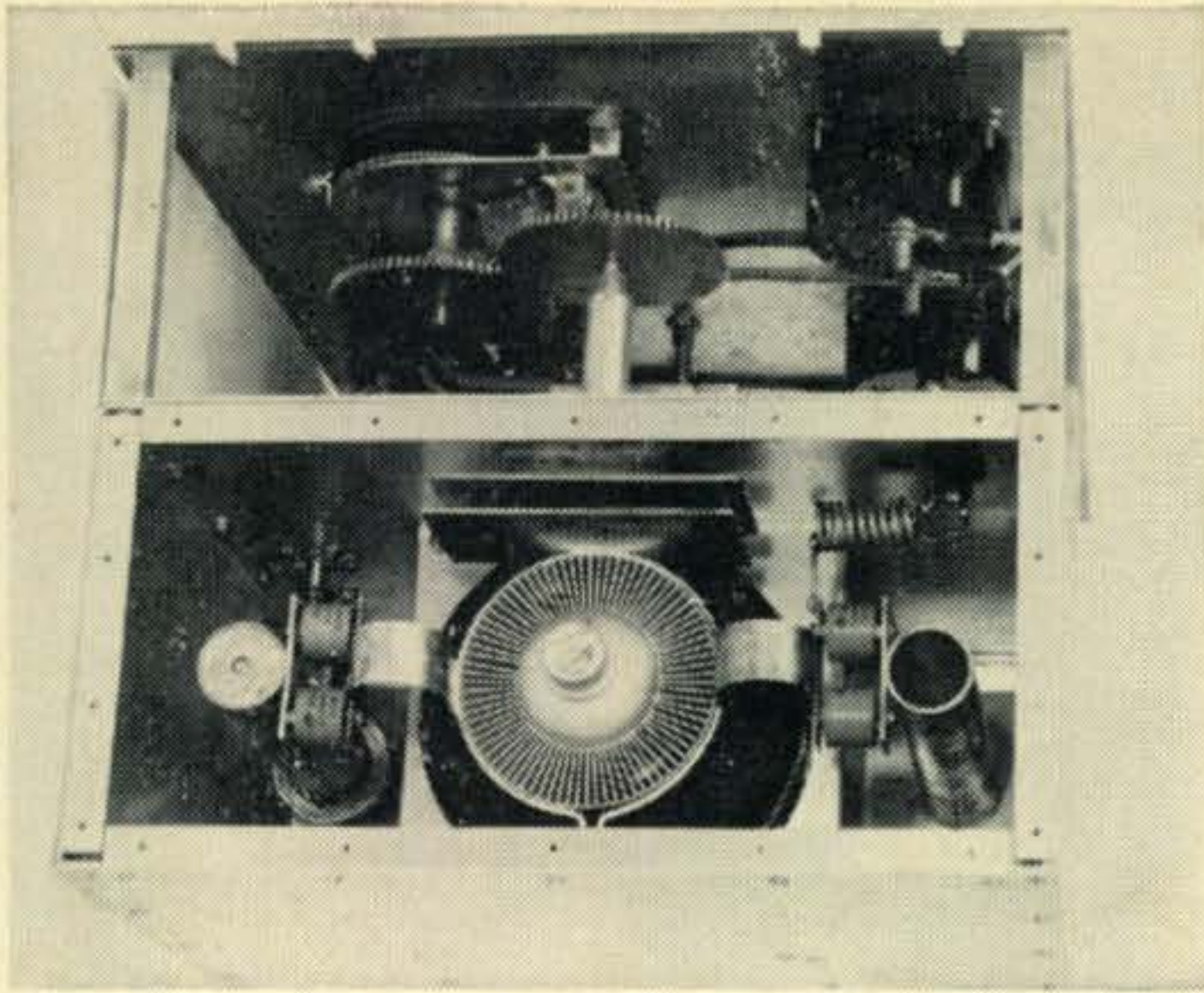


Fig. 10—View into top of plate circuit compartment with the perforated top removed. The PLATE TUNING capacitor (C_3) is immediately in front of the 4CX1000K, driven from the panel-mounted counter dial by two surplus gears. The moveable plate of the capacitor is grounded to the wall of the enclosure by a two-inch wide strap of flashing copper which flexes as the capacitor plate moves closer to the fixed anode plate. The dual plate blocking capacitors are mounted to the sides of the anode strap of the 4CX1000K, and visible at the right is the simple air-wound plate r.f. choke. The bearing of the rotary drive shaft for the OUTPUT LOADING tap is visible at the top of the left plate circuit inductor.

itor grid, screen and plate currents. Normal grid current of the 4CX1000K tetrode is zero in Class AB-1 service; however, small values of current flow during the tune-up process, and grid current excursions up to plus or minus 5 milliamperes may occur. In like fashion, screen current can be either positive or negative in value up to approximately 40 milliamperes or so. Negative current excursions are common in the grid and screen circuits of high gain tetrodes operating in the Class AB-1 mode. To accommodate positive and negative excursions of screen and grid current, zero center meters may be used or a polarity reversing switch can be employed with less expensive positive reading meters. The latter technique is used in this amplifier. Screen and grid metering are accomplished across shunt safety resistors, and rotary meter switches are used in lieu of toggle switches to insure low contact resistance. The safety resistors are placed across the switch arms rather than across the meters so that the circuits are not interrupted during the switching action.

Amplifier Cooling

The 4CX1000K tetrode installed in the SK-820 Air System socket requires an air blast of 25 cubic feet per minute for operation at maximum plate dissipation with inlet air temperatures up to 40 degrees Centigrade. This corresponds to a pressure difference of 0.2 inch of water column. A Dayton #1C-180 blower or Ripley #8472 blower will provide adequate cooling at this level of back pressure. The mouth of the blower is mounted to the under-chassis area as shown in the photograph and r.f. leakage through the

blower air vent is prevented by covering the blower opening with a piece of screening. Cooling air passes from the blower into the grid compartment, through the honeycomb vents in the SK-820 air socket, and is conducted to the tube anode by means of a phenolic hood (Eimac SK-806) that slips over the top of the socket assembly. The air is exhausted from the plate circuit compartment through a perforated area in the enclosure located above the tube. The blower is energized as soon as filament voltage is applied to the tube.

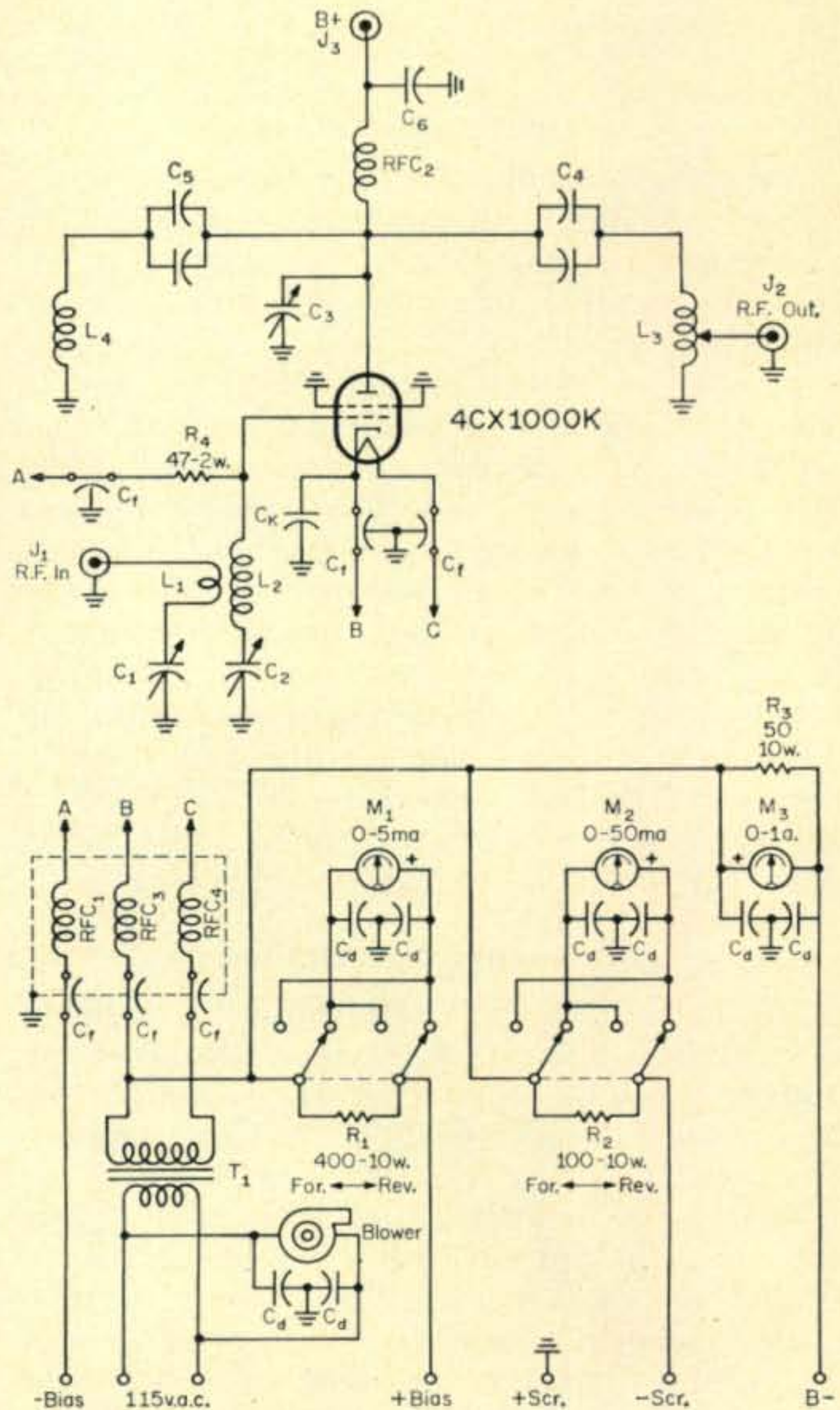


Fig. 11—Circuit of the 2 kw p.e.p. linear amplifier.

- C_1 —20 mmf, Hammarlund HF-20 or equiv.
- C_2 —15 mmf, Hammarlund HF-15X or equiv.
- C_3 —Approx. 3.5 mmf Plate size $2\frac{1}{4}'' \times 4''$, spaced about $\frac{3}{8}''$. See text.
- C_4 — C_5 : Each two 100 mmf, 5kv in parallel. Centralab 850S-100 or equiv.
- C_6 —1000 mmf, 5kv. Centralab 858S-1000 or equiv.
- C_d —1000 mmf disc ceramic, 1.6 kv.
- C_f —1500 mmf ceramic feedthru. Erie 327-X5U-152M or equiv.
- BL₁—25 cubic feet/min. at 0.2" pressure. Dayton #1C-180 or equiv.
- RFC₁—1.8 microhenries, Ohmite Z-144 or equiv.
- RFC₂, RFC₃, RFC₄—9 t. #12, $\frac{1}{2}''$ dia., $1\frac{1}{4}''$ long.
- T₁—6.0 volts at 13 amperes. Stancor P-6463 or equiv.
- J₁—Receptacle, BNC (UG-1094/U).
- J₂—Receptacle, right angle, type N (UG-997A/U).
- J₃—High voltage receptacle, Millen 37001 or equiv.
- S₁, S₂—D.p.d.t. rotary switch, Centralab 1464 or equiv.

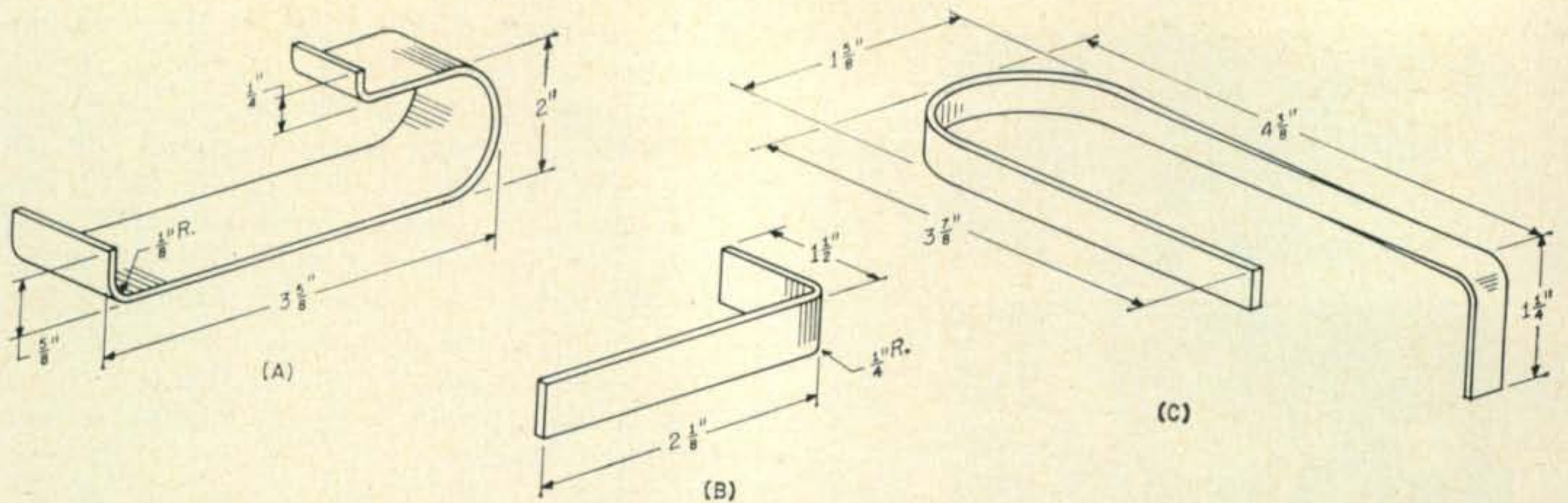


Fig. 12—Structural details for the grid circuit components. (A)— L_2 , $\frac{5}{8}$ " strap, 0.032 material formed to dimensions shown. (B)—Grid connecting strap $\frac{5}{8}$ " wide, 0.064 material, 3 required. (C)—Input link, L_1 , $\frac{1}{4}$ " strap, 0.032 material.

Amplifier Enclosure

The amplifier mounts behind a standard $12\frac{1}{4}$ " relay rack panel, with the 4CX1000K placed in a horizontal position behind the panel (fig. 9). The r.f. enclosure measures 12 inches square and is 6 inches deep. This aluminum enclosure is spaced $4\frac{1}{2}$ inches behind the panel, and in this panel space are located the various meter switches, the meters and counter dials, the filament transformer and a small aluminum box containing the filament and grid isolation networks. The SK-820 air socket is mounted atop the grid compartment box which measures 6 inches wide, 7 inches high and 6 inches deep. The front and back panels of the amplifier enclosure also form the panels of the grid compartment box. As the enclosures are not standard size items, they were made up of 0.062 inches aluminum sheet, formed into simple panels.

Plate Circuit Assembly

The half-wave plate inductor is made up of two $7\frac{1}{2}$ inch lengths of $1\frac{1}{8}$ inch outside diameter copper water pipe (fig. 9). The pipes are clamped to the outer walls of the grid compartment box by means of heavy dural blocks, as shown in the photographs. A special sliding fitting is required on one plate line to allow adjustment of antenna coupling. This fitting consists of a copper ring which slides over the pipe and makes contact to the pipe by virtue of a circular section of flexible "finger stock" which is soldered to the inner circumference of the ring. The ring is driven along the length of the pipe by means of a threaded brass rod internal to the pipe, which is controlled from the front panel through an insulated coupling, a right-angle gear drive and a length of flexible shaft.⁵

The anode collar assembly is shown in fig. 13. It is made up of a circle of $\frac{3}{4}$ -inch wide copper strap to which "ears" have been silver soldered. The ears form mounting brackets for the twin plate blocking capacitors. The stator plate of the variable tuning capacitor (C_3) is also silver soldered to this assembly.

The moveable plate of the tuning capacitor is panel driven by means of a simple bearing that translates rotary motion into thrust (fig. 10). The capacitor plate is prevented from turning by a wide ground strap as shown in fig. 10. To pre-

serve panel symmetry, the capacitor is driven off-center from the counter dial by a set of surplus gears.

Grid Circuit Assembly

Three grid terminals are provided on the SK-820 socket and these are connected in parallel by $\frac{1}{2}$ inch wide lengths of $\frac{5}{8}$ inch wide copper strap silver soldered to the projecting socket terminals. The junction of the three straps is bolted to the grid inductor (L_2), which consists of a single length of copper strap bent into a hairpin which terminates at the stator lugs of the grid tuning capacitor, C_{12} . The composition isolating resistor R_4 is attached to the junction of the straps which is close to the point of minimum r.f. voltage in the grid circuit.

The input coupling loop (L_1) is about an inch away from the grid inductor and consists of a section of $\frac{1}{4}$ inch copper strap formed in a hairpin and connected between the input coaxial receptacle (J_1) and the loading capacitor, C_1 . Aside from the isolating resistor and the two tuned circuits, no other components are mounted within the grid circuit enclosure. Filament and bias leads exit via feedthrough capacitors into a small aluminum box which houses simple r.f. decoupling networks. With a stage gain of over 20 decibels, it is important that no

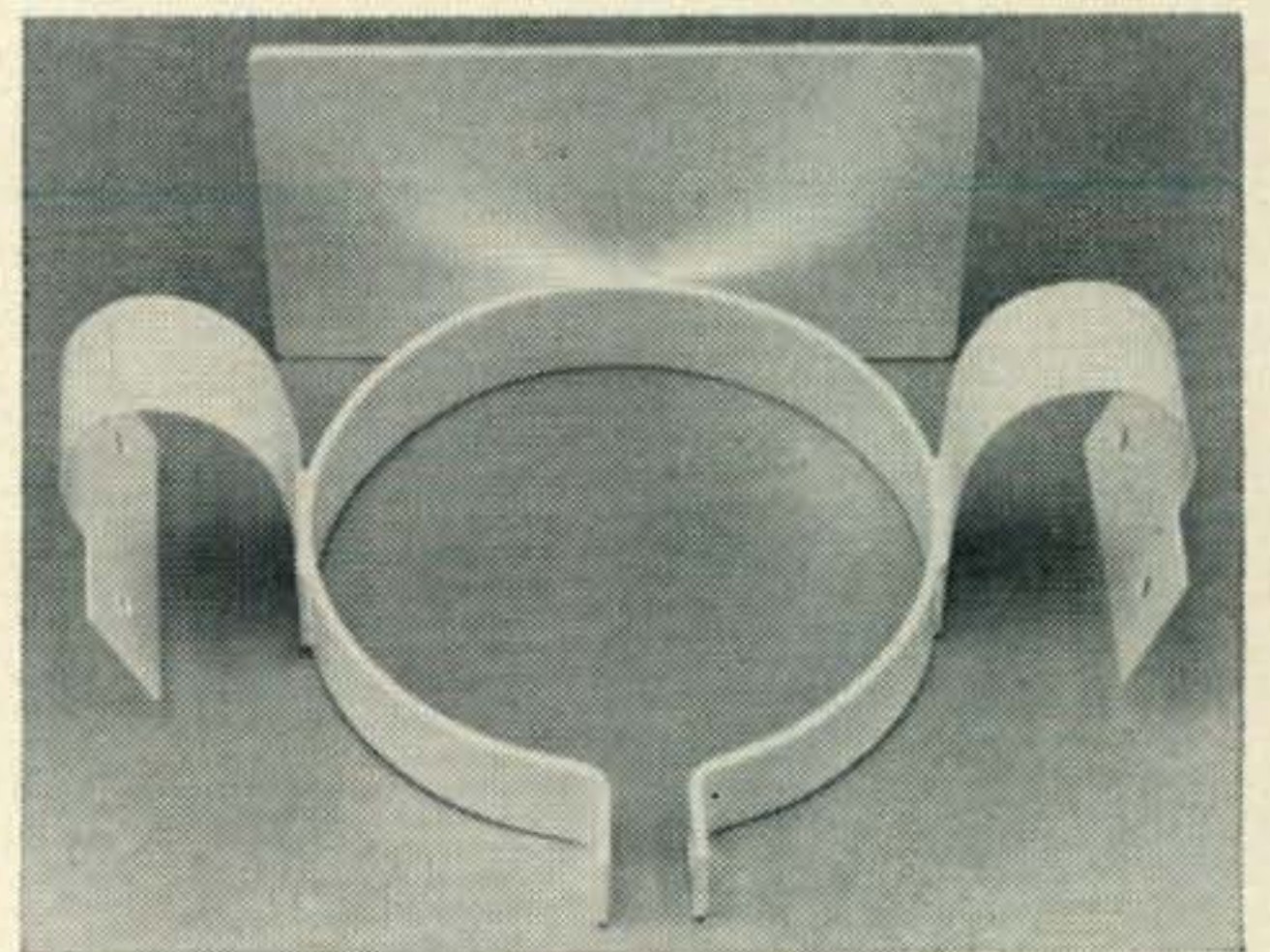


Fig. 13—Anode collar assembly. The anode assembly of the 4CX1000K is made of copper, silver soldered and silver plated. The circular strap encircles the anode cooler of the 4CX1000K and supports one plate of tuning capacitor C_3 and two "ears" which attach to the dual plate blocking capacitors. The capacitor plate measures $2\frac{1}{4}$ " \times 4".

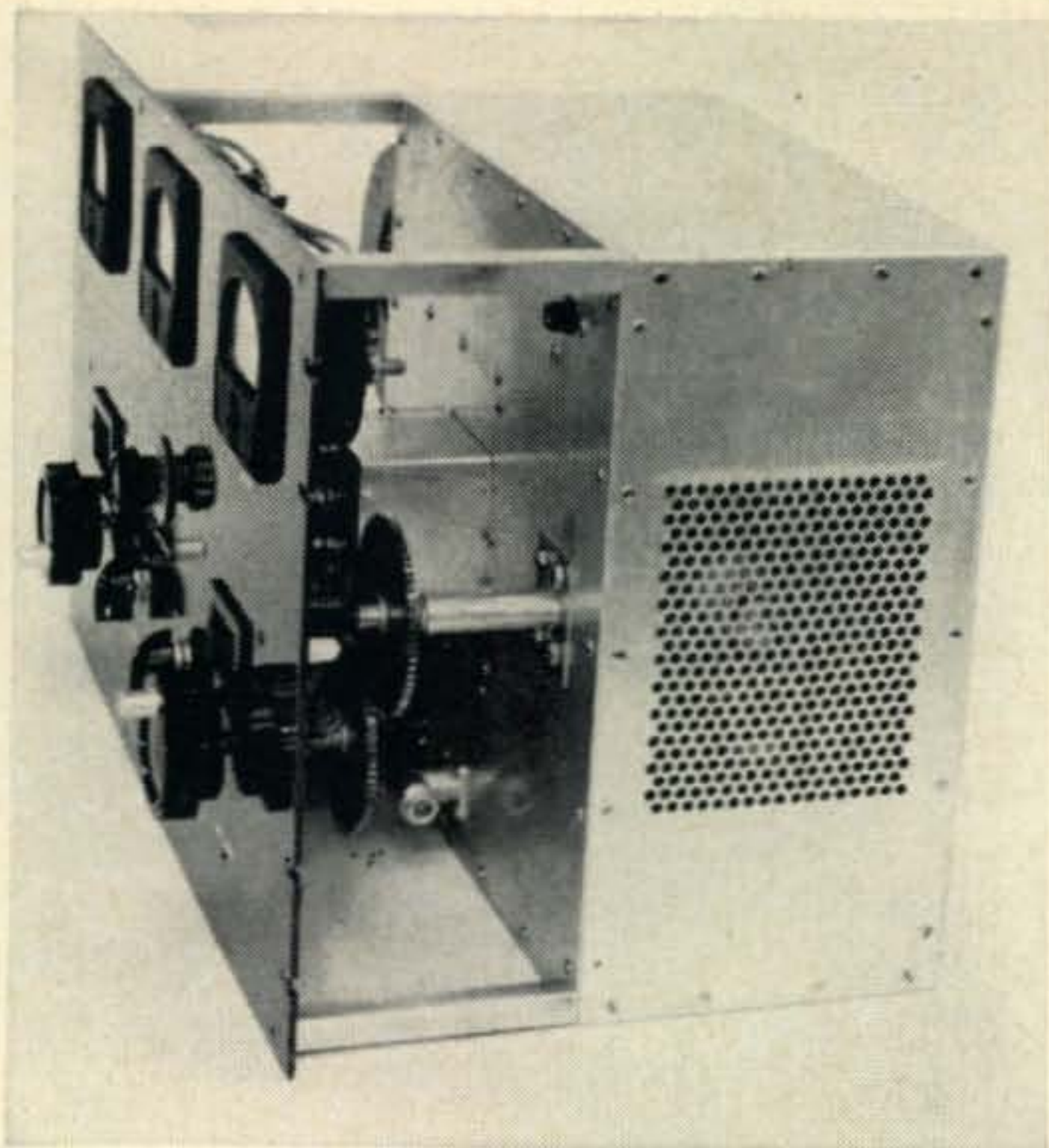


Fig. 14—Oblique view of the v.h.f. amplifier. The r.f. input fitting (J_1), plate circuit gears, and compartment for the power lead filters may be seen in this view. The B plus high voltage connector is located at the top of the enclosure. All meter leads are run in shielded wire, with the shields grounded at each end of the lead and the inner conductor bypassed to the shield with small disc ceramic capacitors at the meter terminals. The end of the plate compartment is perforated to allow exit of cooling air.

r.f. energy be permitted to leak into the grid enclosure. The air inlet at the base of the grid enclosure is covered with screening to reduce r.f. coupling through this opening. In addition, all power leads external to the enclosure are run in shielded braid which is grounded and bypassed at both ends of the lead.

Metering Circuits

Screen, grid and plate circuits are monitored separately by three panel meters. It is useful to observe the ratio of these currents during the tuning process and proper loading can readily be achieved when the operator has sufficient information to adjust the ratio of grid drive to plate impedance. Polarity reversing switches are

incorporated in the grid and screen circuits in order to note negative currents often encountered when tetrodes are operated in the v.h.f. region. Meter circuits are returned to a common cathode point, as shown in fig. 7. The complete metering circuitry is shown in the general schematic, fig. 11.

Plate current is measured in the cathode return circuit to the high voltage power supply. It is necessary, therefore, that the negative terminal of the supply be isolated from ground. Both terminals of the bias supply are isolated from ground as is the negative terminal of the screen supply. The bias supply, in addition, is "hot" to ground.

Power Supplies

As is common with all power tetrodes the screen power supply of the 4CX1000K should be well regulated and the supply "bled" to 70 milliamperes or so. Dangerously high plate currents may flow if the screen power supply exhibits a rising voltage characteristic with negative values of screen current.

Voltage stabilization may be accomplished in several ways: a suitable bleeder resistor may be connected across the screen supply or an electronically regulated supply may be used. It is essential to use a bleeder if a series regulated supply is used, as such a supply exhibits a high input impedance to negative current. A well regulated, choke input supply capable of 150 milliamperes current capacity and bled to 70 ma is probably the best compromise solution.

The rated heater voltage for the 4CX1000K is 6.0 volts (*not* 6.3 volts). Tolerance is plus or minus 5%, but for longest tube life, the voltage should be held between 5.8 and 6.0 volts. The cathode and one side of the heater are internally connected. Heater voltage and blower should be turned on for three minutes before other operating voltages are applied.

Amplifier Tuning and Adjustment

For initial adjustment, a kilowatt dummy load is connected to the amplifier; bias voltage is applied first and set to approximately -60 volts.

[Continued on page 92]

Mode (Class)	Plate Volts	Plate Current (ma)	Plate Input (watts)	Peak Drive Pwr-watts	Power Output (watts)	Max. Grid Current	Max. Screen Current	Grid Bias* (Approx)
AB ¹ (s.s.b.)	2000	883	1766	4.5	915	0	20	-53
AB ¹ (s.s.b.)	2500	800	2000	4.4	1165	0	21	-55
AB ¹ (s.s.b.)	3000	666	2000	6.3	1200	0	18	-56
AB ¹ (a.m.)	2500	400	1000	1.2	250	-0.3	-29	-57
B (c.w.)	2500	400	1000	5.2	625	-2.5	21	-80

*Adjust bias for: Resting plate current of 250 ma for Class AB¹.
 —Resting plate current of 1 ma for Class B.
 —Resting plate current of 200 ma for a.m. linear service.

Fig. 15—Amplifier operating characteristics for the 4CX1000K.

New Amateur Products




Heath SB-110

THE SB-110 is a 180 watt p.e.p. s.s.b. six meter transceiver. It features upper and lower s.s.b. and c.w. operation with p.t.t., v.o.x., and v.o.x. operated c.w. The SB-110 can be operated either v.f.o. transceive; crystal-control transmit, v.f.o. receive; or crystal-control transceive. Frequency stability is less than 100 cps drift per hour after 20 minute warmup. The SB-110 kit weighs 23 lbs. and sells for \$320.00. Power supply not included. For complete specifications and details write to Heath Company, Benton Harbor, Michigan, 49023, or circle 69 on page 106.

"Elements of Radio"

PRENTICE-HALL, INC., New Jersey publishers have recently brought out the new fifth edition of "Elements of Radio" by Marcus and Marcus. Many will recall using this book when first starting out. Through 43 chapters and 672 well-illustrated pages the fundamentals of electronics are brought forth and made clear to both the beginner and more advanced student. It is a worthwhile Xmas gift and invaluable addition to any ham library. The price is \$8.50 at most bookstores. For more information write Prentice-Hall, Inc., Englewood Cliffs, N.J. or circle 70 on page 106.

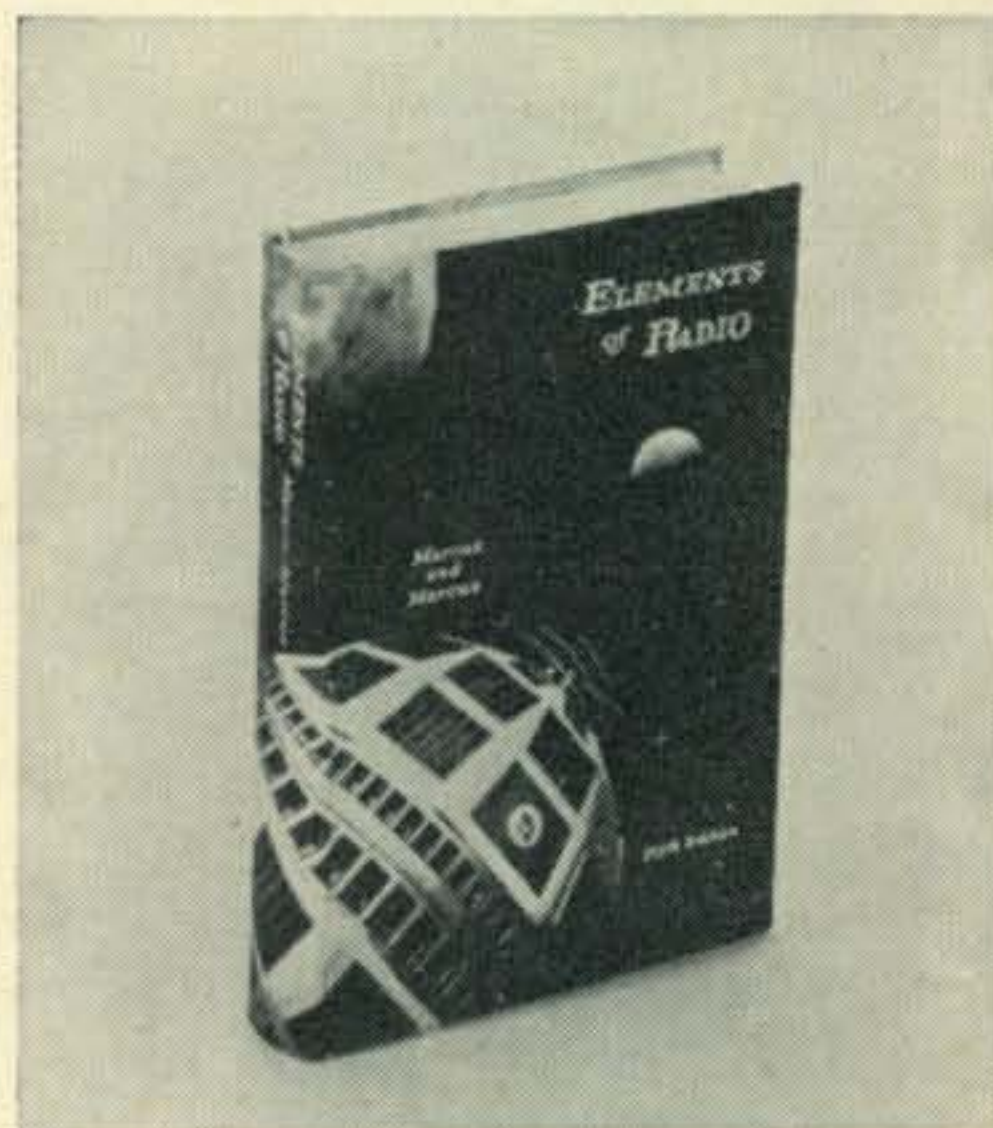


EICO 753 Tri-Band Transceiver

THE EICO 753 covers 20-40-80 meter s.s.b., a.m., and c.w. Input power is 200 watts on s.s.b. and a.m. and 180 watts on c.w. with 110 watts output. Claimed receiver sensitivity is better than one microvolt for 10 db signal to noise ratio. It comes in kit form for \$179.95 and wired at \$299.95, less power supplies and speaker. For more information write to Eico, 131-01 39th Ave., Flushing, New York, 11352, or circle 71 on page 106.

Dexion Do-It-Yourself Steel Angle

RESEMBLING a huge erector set, the Dexion slotted angle components are available from local hardware and lumber yards. With an ordinary wrench and hacksaw and using just nuts and bolts, numerous items can be made for the shack and workshop. Workbench frames, storage shelves, book shelves, operating tables, racks, and other useful things can be made. Dexion is available in two sizes. The standard angle, packaged in bundles of 50 ft., is priced at \$10.50 per package. The heavy duty size is \$12.75. Each package contains 75 nuts and bolts and 20 corner (support) plates. "Idea" pamphlets are offered free with other information by writing to Dexion, Inc. Retail Division, 39-27 59th St., Woodside, New York 11377, or circle 72 on page 106.

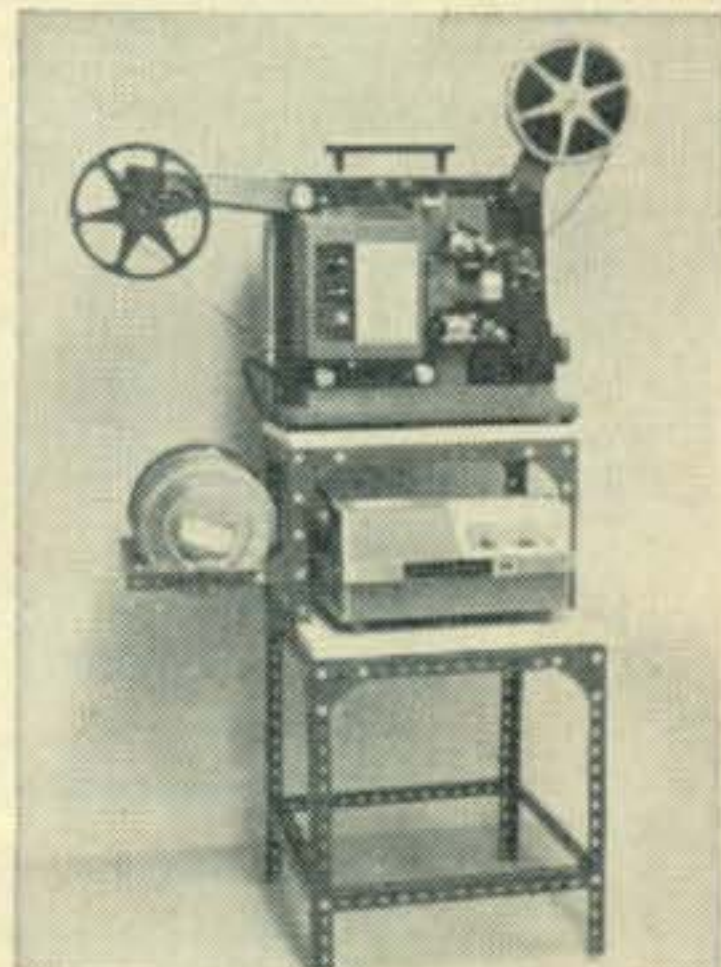

Hallicrafters SR-500 Transceiver


THE SR-500 is a three band (80, 40, and 20) 500 watt p.e.p., s.s.b. and c.w. transceiver. Called the "Tornado," the unit features amplified automatic level control (AALC) and receiver incremental tuning (RIT) which allows the operator to tune the receiver up to 3 kc to either side of the transmitter frequency. The SR-500 sells for \$395.00. Optional equipment includes mobile mounting bracket, a.c. supply, d.c. supply, and v.o.x. adaptor. For further details write to Hallicrafters, 5 Kestner Ave., Chicago, Ill., or circle 73 on page 106.



Estes Engineering Company

INTRODUCTION of the Electro-Shield Alternator Kit is announced by Estes Engineering Company. The kit is designed to eliminate interference from alternator and d.c. generator circuits, permitting long range noise-free operation of all two-way radio systems. It can be used on both gasoline and diesel engines.

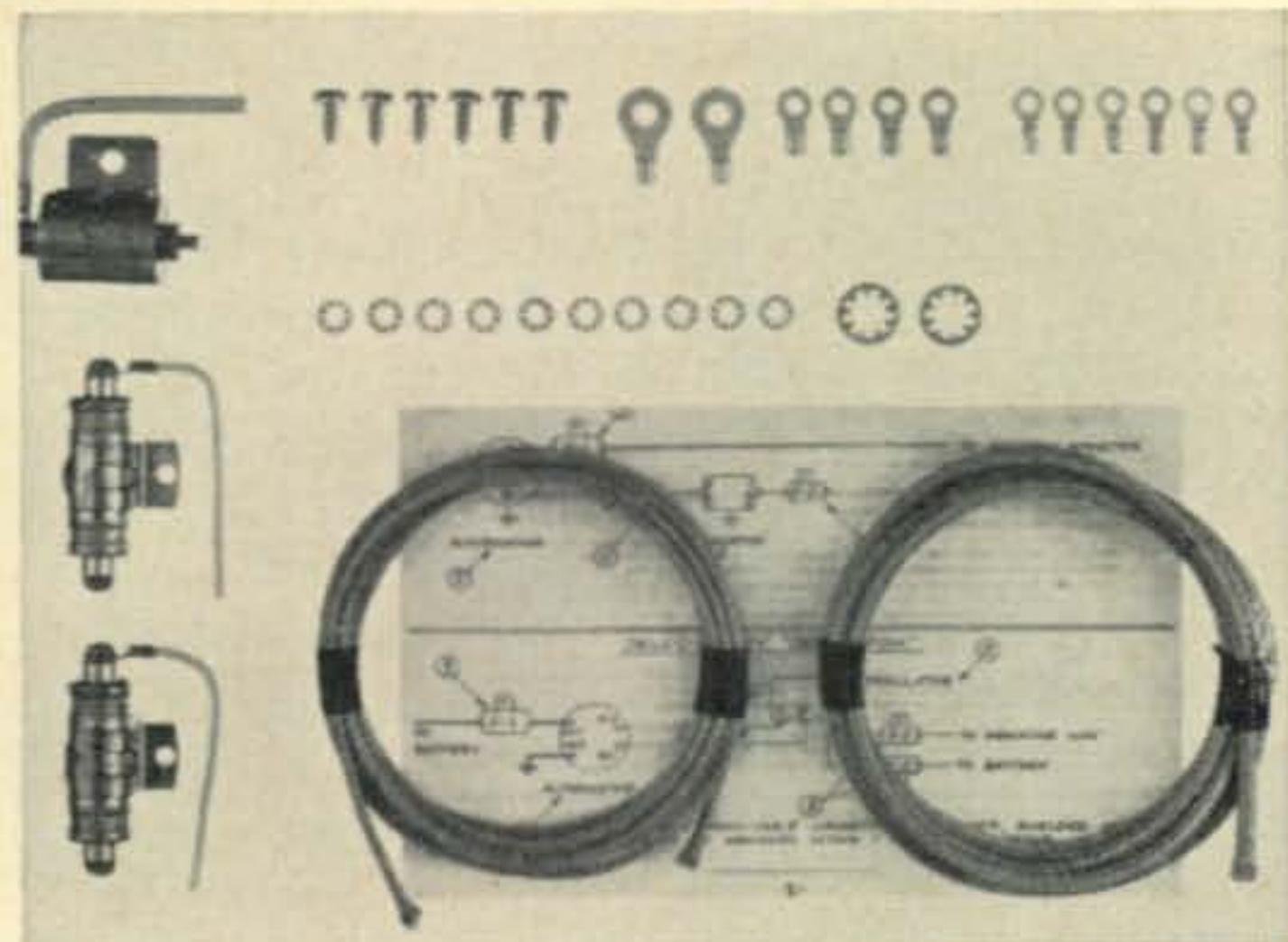The Electro-Shield Alternator Kit includes shielded cables for radiated noise, and 50 amp filters for conducted noise. Circuit diagrams for all popular battery charging circuits are provided. For further details write to Estes Engineering Company, 1639 West 135th St., Gardena, California, 90249, or circle 74 on page 106.



Lafayette HA-650 6 Meter Transceiver

THE model HA-650 is a solid state 6 meter transceiver with 2.5 watt input and 1.5 watt output. It has a push pull modulator, 6 crystal controlled transmit positions and uses standard 8 mc crystals. The receiver is tunable and has a claimed sensitivity of 1.2 uv. A built in mobile power supply (Zener diode), carrying case, shoulder strap, telescoping whip antenna, and batteries are supplied. Fixed station a.c. supply is optional. The price is \$119.95. For more details write to Lafayette Radio, 111 Jericho Turnpike, Syosset, L.I., N.Y. or circle 75 on page 106.



Knight-Kit C-577

THE C-577 is a fully transistorized audio compressor/preamplifier (not a clipper) kit. It serves as a low level preamp for both low and high impedance mikes with minimum distortion and 26 db gain at 1 kc. It has full compression at 3 millivolts input, with an output of 50 millivolts. The kit is priced at \$19.95 and is Allied catalog number 83U816MW. For complete specs, write to Allied Radio, 100 N. Western Ave., Chicago, Ill., or circle 76 on page 106.



Sentry Converters

THE Sentry converter permits the business man or enthusiast to monitor any single frequency between 25 mc and 180 mc, f.m. or a.m. Single switch operation changes normal tuning range and converter. Operated from self contained 9 volt battery. Price is \$37.50. For further literature write to Sentry Manufacturing Co., P.O. Box 12322, Oklahoma City, Okla., or circle 77 on page 106.



אוסקר III*

"Bruno Puts Israel Into Space"

BY URI BERNEAH†, 4X4OC/W6

So reads the headline from the daily newspaper *Ma-Ariv* of Israel, announcing a reported record-breaking QSO between Asia and Europe via OSCAR III satellite. The 950 mile contact was made between 4X4DH, Bruno Bienefeld of Tel-Aviv and LZ1AG of Sofia, Bulgaria. The article reads, in part . . .

"Bruno Bienefeld an engineer from Tel Aviv operates an amateur satellite tracking station in his home and is in communication with other amateur stations around the world.

"While people around the world are wondering about the practical role of the satellites which will eventually bring man to the moon, another kind of satellite orbits the globe. These are the communication satellites used to relay radio, telephone and TV transmissions and in the next few years many "comsats" of this type will be placed in space forming a network which will cover the whole world. The space communication era has begun, but though many "comsats" orbit the globe, there has been no tracking station in the area between the Pacific and the Mediterranean. A pioneer in this field is Bruno Bienefeld, an electrical engineer from Tel Aviv. In his home he operates a private satellite tracking station. With his amateur station he has managed to contact other such tracking stations around the world, and that's how he "put Israel into space".

"How did the radio amateur satellites get into orbit? Even though there are many radio amateurs around the world, they can't build vehicles or boosters to put satellites into orbit. The OSCAR society got in touch with a U.S. missile agency and asked for permission to hitchhike a satellite on one of the boosters. The agency agreed, and three years ago OSCAR I was sent into space.

"The OSCAR satellite was orbited and sent a signal in morse code which meant laughter (HI). Probably the only man in the middle east who heard that "laughter" of OSCAR was Bruno, an enthusiastic radio amateur who looked for new means of communication through space. He managed to receive the OSCAR transmissions which contained telemetry information about the height, speed and many other details, and Bruno's tracking station proved itself.

"Since then, says Bruno, two more satellites were sent up and the telemetric information was received by me". OSCAR III was sent up in March of this year and through Bruno's station, contact was actually established with the European continent." The radio amateur and the satellite will have in the future a very important role in human communication. They are the bridge over all continents," Bruno explains.

"Bruno is a graduate electrical engineer from the *Technion* where he worked for 5 years in cosmic ray research. For 6 years he worked in the Weizman Institution in development of instruments for magnetic field detection. Later, he devoted himself to radio and when the first satellites circled the globe, he tracked and observed them. When Oscar III orbited the earth, he used his amateur station 4X4DH to communicate through OSCAR III to LZ1AG, a radio amateur in Bulgaria. His name was Stanislav, and he and Bruno met each other for the first time through space."

ברונו "הכניס את ישראל לחלל"

האנגינייר התל אביבי בניפולד מבעל ביתו תחנת מעקב על לוויינים וכונן קשר עם תחנות אחרות בעולם

תל אביב, 11 במרץ - ברונו בניפולד, 37 שנים, מהנדס חשמל ב"מטכ"ל, הוא האדם היחיד בישראל שצליח עד כה לתקשר עם לוויין קוסמי. ביום שבת האחרון, 10 במרץ, התקשר בניפולד עם תחנת קשר של לוויין "אוסקר III" ששלח החברות האמריקאיות "אוסקר" ו"אמטור" לתחנתו בביתו בתל אביב. בניפולד, שהיה עד כה מתעניין בלוויינים, התחיל להתעניין בהם לפני שנתיים, כשחברו לוויין "אוסקר I" ו"אוסקר II". בניפולד, שהיה עד כה מתעניין בלוויינים, התחיל להתעניין בהם לפני שנתיים, כשחברו לוויין "אוסקר I" ו"אוסקר II". בניפולד, שהיה עד כה מתעניין בלוויינים, התחיל להתעניין בהם לפני שנתיים, כשחברו לוויין "אוסקר I" ו"אוסקר II".



Oscar makes front page news recently in the Israeli newspaper *Ma-Ariv*. The article reports the successful Oscar III QSO between 4X4DH and LZ1AG.

*OSCAR III (Hebrew).
†Project Oscar, Inc., Foothill College, Los Altos Hills, Calif.

The Transcom SBT-3, Three-band Transistorized s.s.b. Transceiver. The thumb-operated controls, described in the text, are the four horizontal elements on the dark panel near the lower center. The one for p.a. loading is between the upper and lower knobs at the right.



CQ Reviews:

The Transcom SBT-3 Transceiver

BY WILFRED M. SCHERER,* W2AEF

APET peeve of ours is that most of the ham gear designed for mobile operation is just too large to make a neat installation without overcrowding the front quarters of the car or taking up too much leg space, while at the same time allowing accessibility for convenient handling. It was therefore pleasing to find the Transcom SBT-3 three-band s.s.b. transceiver a nicely styled package which takes up only a quarter cubic foot of space, with good performance and economical operation.

Although designed for mobile work, it is also a neat and handy unit for portable, field or fixed station use with many unusual design features included.

The SBT-3 operates at a power input of 165 watts p.e.p. to deliver a p.e.p. output of 90-100 watts; while the receiver has a sensitivity of 0.5 μ v for 10 db S/N ratio. A crystal lattice filter is used in both the receiver and the transmitter for 3 kc selectivity.

Economical mobile operation is obtained by use of transistors throughout, except in the final amplifier where instant-heating type tubes are used (these are the *only* tubes used), the filaments of which are not energized until the mic p.t.t. button is pressed to transmit. Battery drain is thereby held down to a minimum during receiving periods (only 500 ma) and instant receiver/transmit operation is made possible.

Other features of the SBT-3 are: frequency coverage of 3.8-4.0 and 7.2-7.3 mc on lower sideband and 14.2-14.35 mc on upper sideband; frequency stability of 100 c.p.s. or better over any 10-minute period after warmup; fine vernier tuning with one knob revolution covering 5 kc or less; 5 kc dial calibrations; easily adjusted controls using knurled thumb-wheels; carrier

and sideband suppression of 45 and 40 db below maximum output respectively; adjustable pi-network for 30-100 ohm output loads; r.f. compression on transmit; push-to-talk operation; receiver bandwidth of 3 kc at 6 db points; image rejection better than 60 db; 2 watts a.f. output; a.g.c.; a.f. response of 400-2500 c.p.s. \pm 3 db in both receive and transmit. Size is 4 $\frac{3}{8}$ " \times 11 $\frac{3}{8}$ " \times 8 $\frac{3}{4}$ " (H.W.D.) and weight is 10 pounds. Separate external power supplies are required for either 12 v.d.c. or 117 v.a.c. operation. A loudspeaker is built into the a.c. supply. Current drain with 12 v.d.c. is 500 ma on receive, 12-15 a. on transmit.

Circuitry

A number of interesting innovations are included in the SBT-3. The lineup is shown in the block diagram at fig. 1. Starting with the transmitter section, the basic concept is that of generating the s.s.b. signal at 5173.5 kc and heterodyning this with a variable frequency to produce output in the desired amateur band.

The b.f.o. carrier generator feeds a ring-type balanced modulator to which the a.f. from the speech amplifier is fed from a signal splitter, Q_3 . See fig. 2. The s.s.b. output from the modulator then goes through a four-crystal lattice filter, the 2nd and 3rd i.f. stages and thence to the transmitter mixer where the heterodyning takes place with the v.f.o. signals.

For 80 and 20 meter use, the v.f.o. frequency is 4486.25-4586.25 kc. This is doubled to 8973.5-9173.5 kc in the multiplier, Q_{14} , before going to the transmitter mixer. A 13 mc trap eliminates the 3rd harmonic of the v.f.o. when the 20-meter band is in use. On 40 the v.f.o. functions on 4124.5-4158.5 kc which is tripled to 12373.5-12473.5 kc by the multiplier.

Unlike other solid-state gear we've seen so

*Technical Director, CQ.

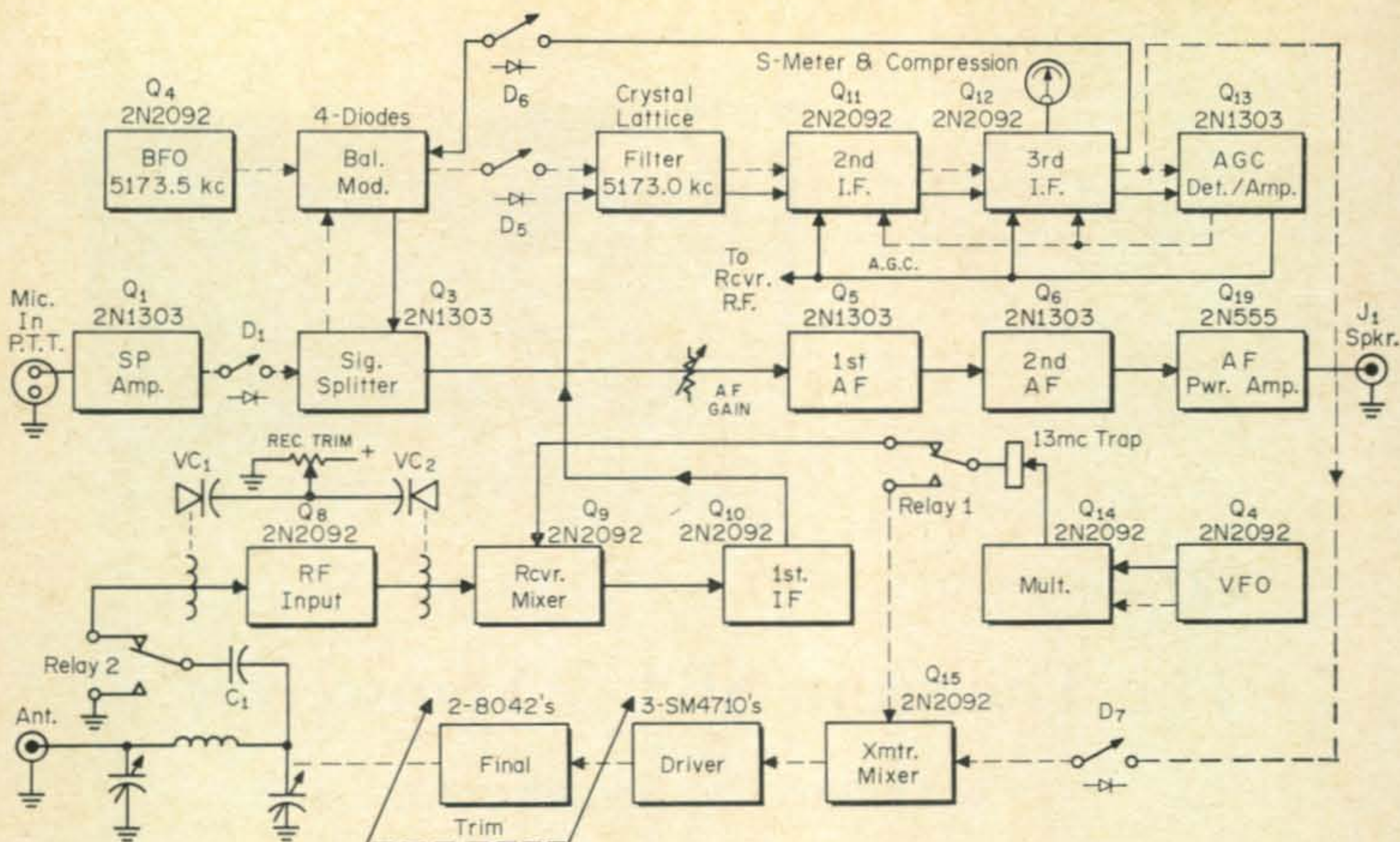


Fig. 1—Block diagram of the Transcom SBT-3 Transceiver.

far, the r.f. driver stage, which follows the mixer, also employs transistors instead of vacuum tubes. Three Motorola SM-4710's are used in a unique circuit wherein the transistors are connected in a cascaded arrangement to provide the required driving voltage for the final p.a. See fig. 3. Excellent stability is exhibited; so much so, that a novel space-saving and inexpensive system can be used that allows gang tuning of the input and output circuits of the driver using a butterfly-type capacitor with one of its stators connected to the input circuit, the other to the output.

The p.a. has two Amperex type 8042 instant-heating tetrode tubes connected in parallel with neutralization and a pi-network output circuit. A toroid-wound tank coil is employed which not only saves space and is highly efficient, but which also minimizes stray r.f. fields around the tank and thus further contributes to the overall stability of the unit.

Separate variable capacitors are used for p.a. tuning and loading in the pi-network. An unusual departure here is that the loading capacitor is a compression-type trimmer which is mounted at the rear of the panel with its adjusting screw in a vertical plane and parallel to the panel. The screw is connected to a metal thumb wheel that protrudes through a horizontal slot in the panel.

Receiver Section

In the receiver the frequency conversions work in reverse order; that is, the incoming signals beat with the v.f.o. signals to produce a 5173.5 kc i.f.

The r.f. stage has a 2N2092 operating as a ground-base amplifier with its collector fed to

the base of a 2N2092 mixer through an impedance-matched transformer. The input signal is obtained from the plate side of the p.a. tank through a small capacitor coupled to a tuned circuit at the emitter of the r.f. transistor, Q₈. Thus there is a double-tuned input arrangement for improved r.f. selectivity.

Varicap diodes (voltage-controlled solid-state variable capacitors) are used instead of the conventional variable capacitors for tuning the input and output circuits of the r.f. stage. Both Vari-caps are "gang tuned" with a potentiometer turned by a thumb-wheel on the panel.

The signal from the r.f. stage goes to the base of the mixer and the heterodyning signal from the v.f.o. is injected at the emitter. The resulting i.f. signal goes to the 1st i.f. amplifier, the 5173.5 kc filter, the 2nd and 3rd i.f.'s and then to the balanced modulator which now functions

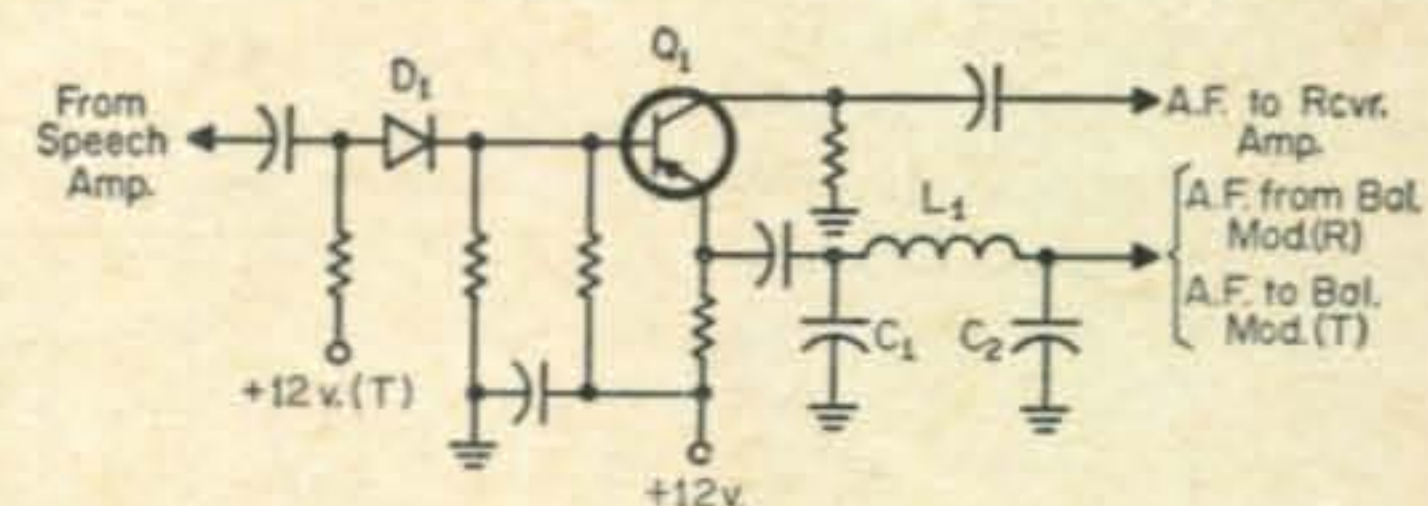


Fig. 2—Signal-splitter circuit used in the SBT-3. It is a bilateral affair through which the a.f. circuits in and out of the balanced modulator are routed and impedance matched. On receive, the a.f. output from the balanced modulator goes to the emitter of Q₁, the collector of which feeds the receiver a.f. amplifier. On transmit, a.f. from the speech amplifier goes to the base of Q₁ via diode switch D₁ and is applied to the modulator from Q₁'s emitter. The emitter impedance matches that of the modulator. L₁, C₁ and C₂ constitute an r.f. filter.

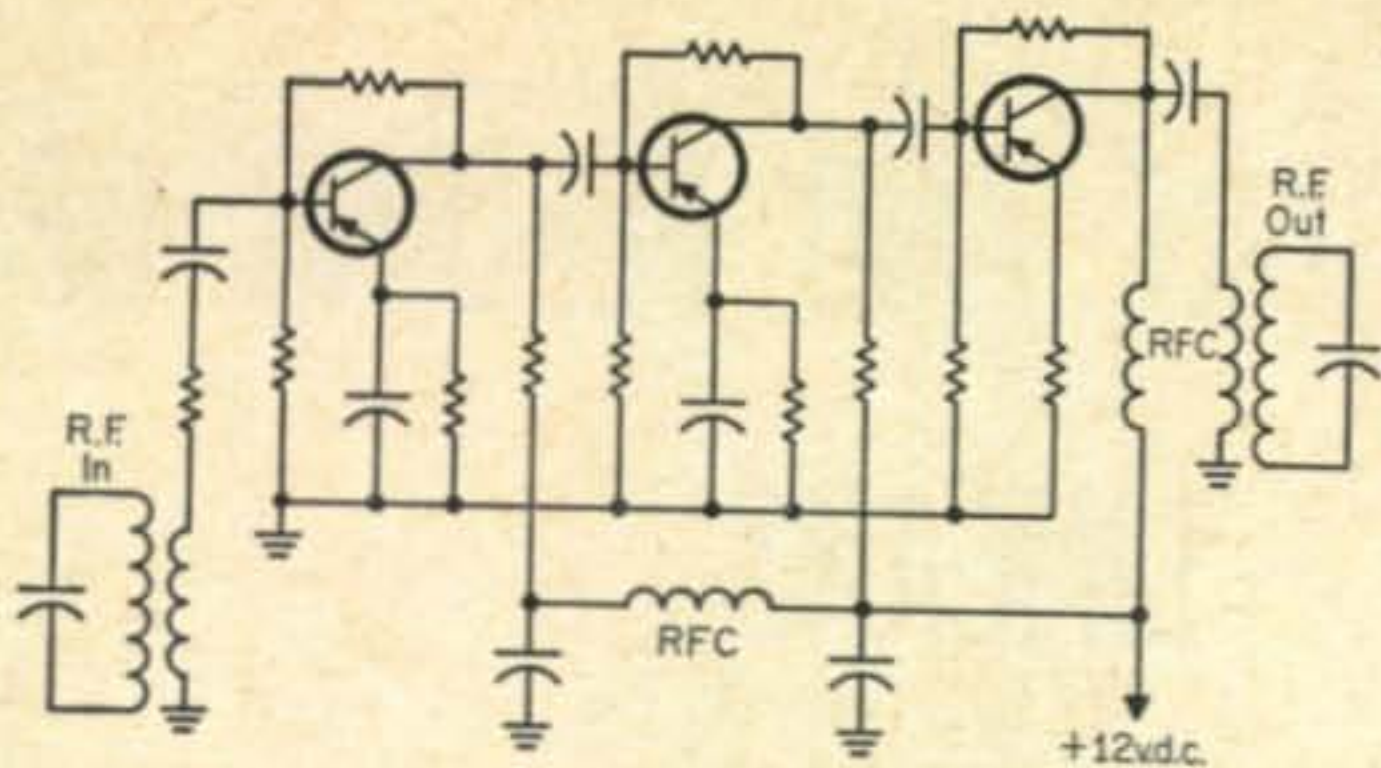


Fig. 3—Circuitry for the driver in the SBT-3. Three transistors are connected in cascade with a configuration which, except for the r.f. chokes and the tuned input and output circuits, is like that of a conventional a.f. amplifier.

as the product detector. See fig. 4.

We were particularly impressed to see this arrangement used, since for many years we've found it a superior method of product detection in our homebuilt gear; and especially since we've run across quite a lot of manufactured gear where the so-called product detector was not acting solely as such, but which at the same time exhibited a considerable degree of envelope detection, resulting in undesirable distortion products.

The a.f. output from the balanced modulator goes to the signal splitter and then to the a.f. amplifier chain consisting of two stages followed by an a.f. power-output amplifier.

A.g.c. is obtained from the a.g.c. detector/amplifier, Q_{13} , which is coupled to the last i.f. stage and the last two i.f.'s. The a.g.c. also acts on the i.f.'s during transmit to provide low-level r.f. compression, a system that does not depend on any final p.a. grid current to produce an a.l.c. voltage.

The S-meter responds to variations in the voltage drop across the emitter resistor of Q_{12} . It also serves as a compression indicator on transmit. When the tuneup position of the SBT-3 is used, the meter is automatically switched to read the plate and screen currents of the p.a. tubes.

Switching

Diode switches are used to transfer the low-level signal circuits from receive to transmit.¹ Two conventional relays are used elsewhere. One switches the v.f.o. multiplier output to the receiver or to the transmitter mixer. It also switches

Top View of the SBT-3. A perforated cage has been removed from the final amplifier in order that the toroid tank coils may be seen at left center. The r.f. driver amplifier is on a circuit board on the right side of the shield next to the p.a. tubes. The bandswitch and the r.f. coils are above the chassis. The b.f.o. is built on a printed-circuit board that is mounted on a baffle (top center) which is firmly supported by a channel bracket. The low-level stages are contained on the board in the right foreground.

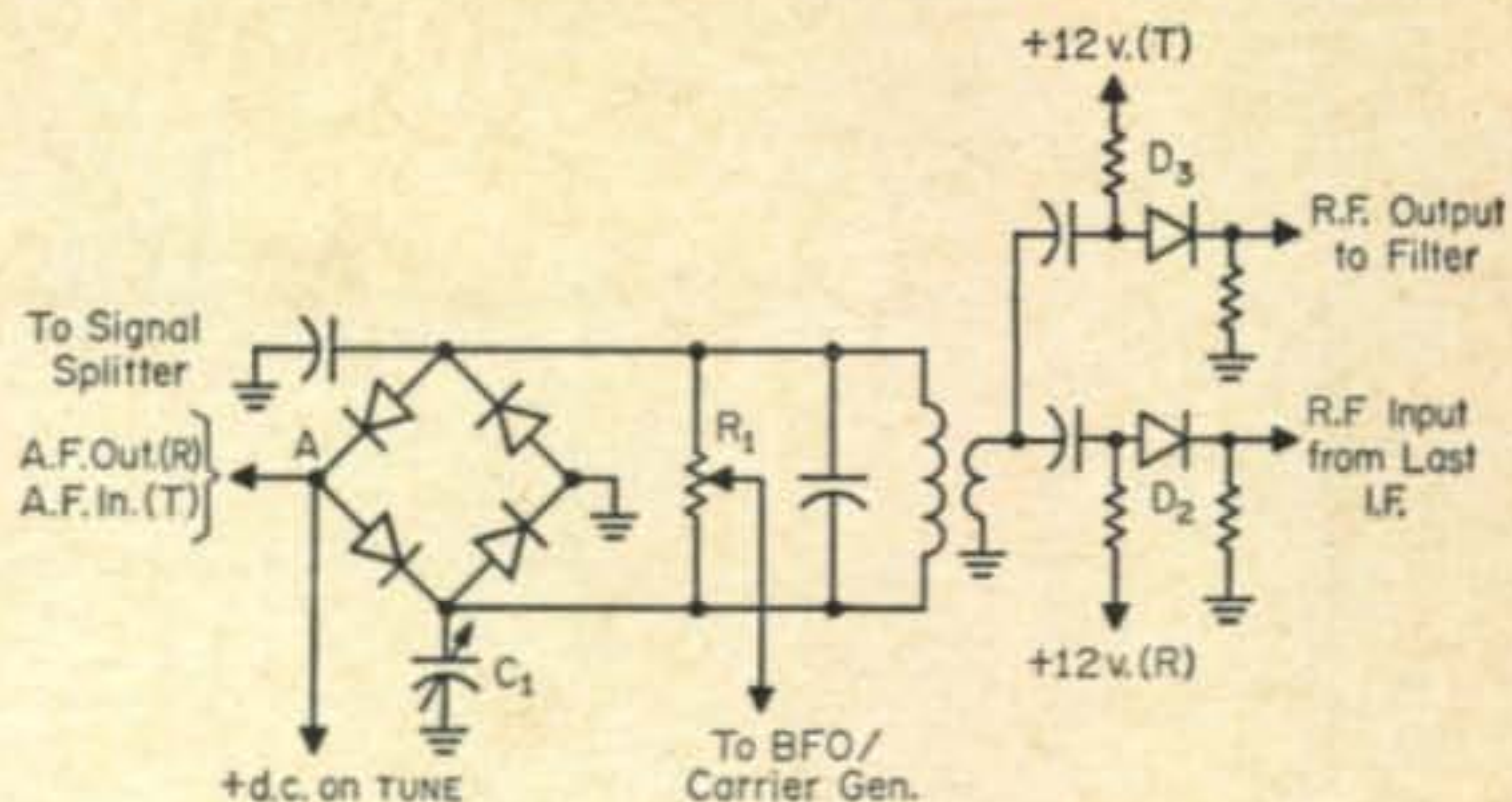



Fig. 4—Balanced modulator/product detector circuitry for the SBT-3. The carrier generator/b.f.o. signal is fed at all times to a ring type modulator using 4 diodes. On receive, r.f. output from the last i.f. goes to the modulator through diode switch D_2 . The demodulated a.f. output from the modulator is obtained at point A. On transmit, the a.f. speech is applied to the modulator at A and the modulated r.f. goes to the lattice filter via diode switch D_3 . The carrier signal is balanced out with R_1 and C_1 . During tuneup, a d.c. voltage is applied at point A to unbalance the modulator and thus supply a carrier.


the supply voltages for the required receiver and transmitter functions. The other relay, during receive, connects C_1 to the r.f. input stage. During transmit, it disconnects C_1 and grounds it. By so doing, any high-power r.f. leakage from the transmitter, that otherwise might take place due to stray capacitance between open relay contacts, is bypassed to ground, and the r.f. transistor is thereby protected against damage.

Due to the physical location of the relay, this method was probably devised to avoid r.f. pickup from r.f. ground currents through the chassis that could occur if the relay were rigged in the conventional manner to ground the input coil instead.

[Continued on page 94]

¹For those not familiar with diode switches, a diode acts as a closed switch when it is conducting, as an open switch when not conducting. Conduction occurs when the diode anode is at a positive potential with respect to the cathode, non-conduction results when the anode is negative in respect to the cathode. The diode switch is operated by applying a d.c. voltage of the correct polarity for the desired switching state.

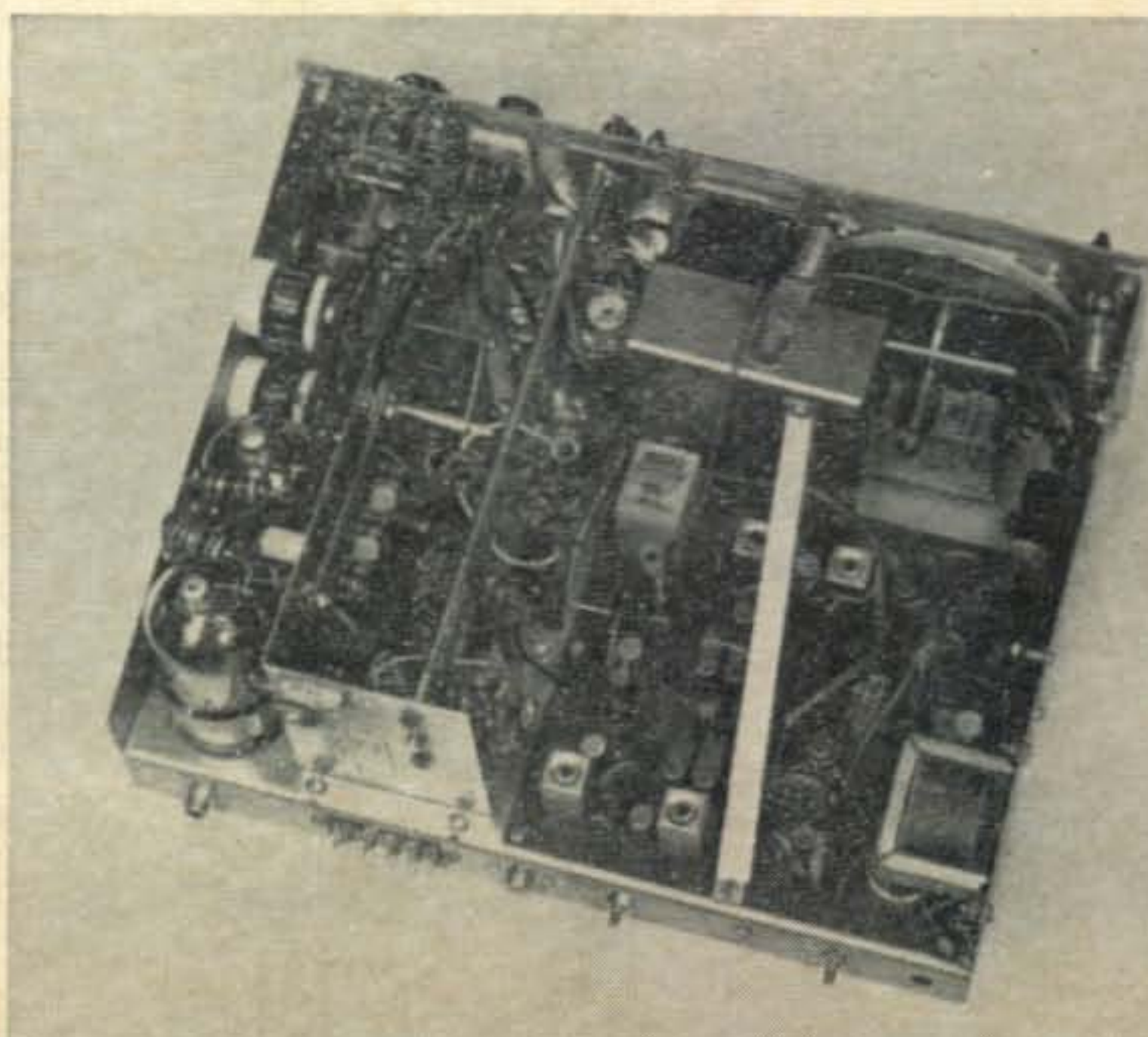

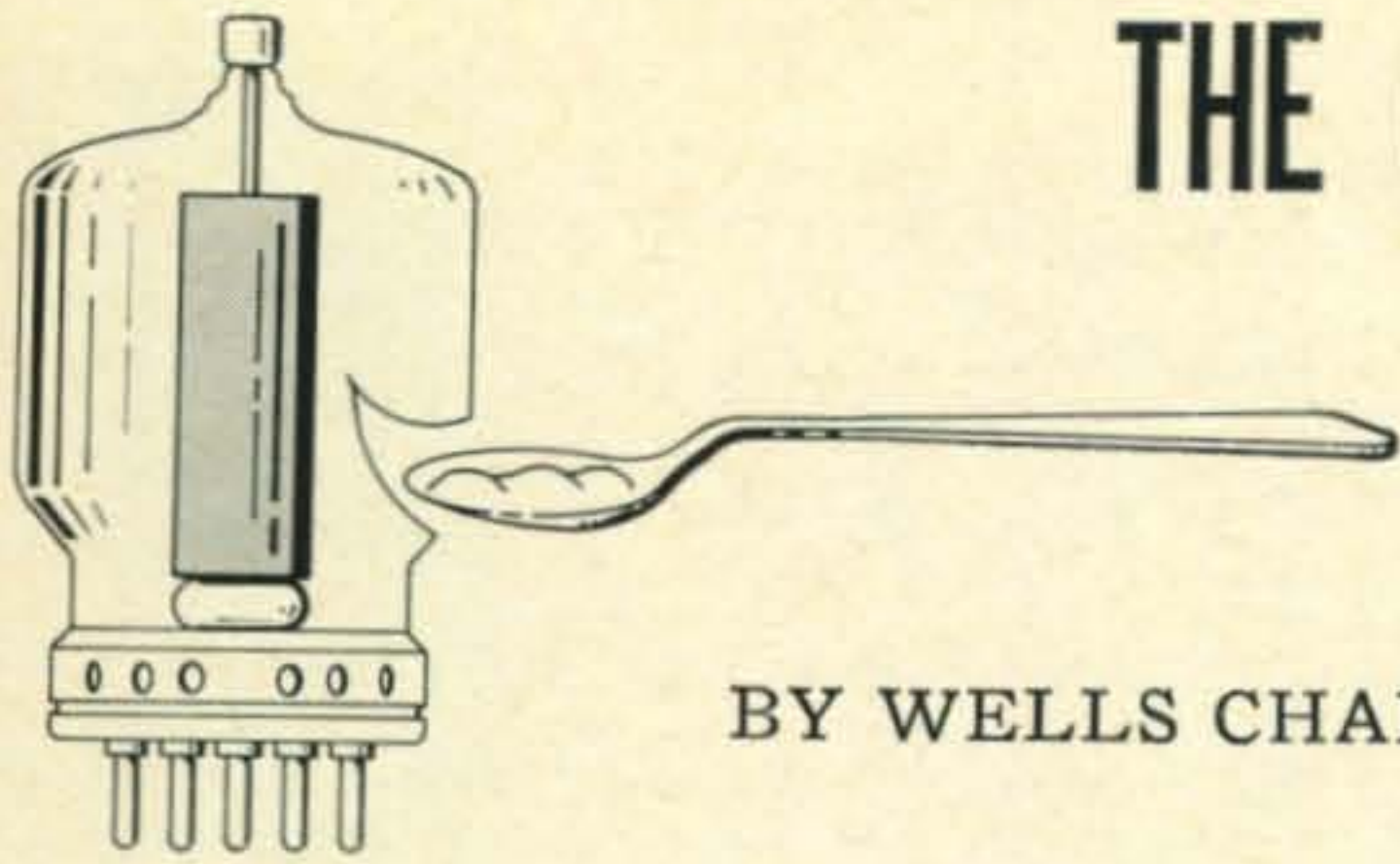

THE CARE AND FEEDING OF LINEARS

BY WELLS CHAPIN,* W2DUD/8

Covered below are several obscure facts about driving and tuning linear amplifiers. Following these simple procedures can improve the quality of your signal on the air.

EVERYONE knows that all you do to get higher power in an economical manner is to hang on an amplifier. However, it is not that simple as some of the problems can be quite sticky. The adjustment, power measurement and calculation, excitation and matching to the exciter can be difficult. In addition, the type of amplifier selected can be important.

Perhaps you do not realize it, you have been using linear amplifiers for some time. The r.f. and a.f. amplifiers in superheterodyne receivers are typical low power linear amplifiers. The IRE dictionary defines a linear amplifier as an amplifier in which the signal output voltage is directly proportional to the signal input voltage. The same source says: a Class B linear amplifier is an amplifier in which the grid bias is approximately equal to the cutoff value so that the plate current is approximately zero when no exciting grid voltage is applied and so the plate current in a specific tube flows for approximately one half of each cycle when an alternating grid voltage is applied. Thus, it is obvious that the input and output signals are very inter-dependent on each other.

There are many advantages besides the power gain when using a high power linear amplifier. The driving power required is lower thus enabling you to use a smaller exciter and its inherent lower harmonic radiation problem. Linears, when used in s.s.b. can approach efficiencies of 70 to 75 per cent. C.w. signals are cleaner and key clicks are eliminated as the keying and shaping are done a lower level.

The type of linear you buy or build is important. The screen grid type of tube requires less excitation and maybe the best if you have a low power exciter in the 10 watt area. However, screen grid amplifiers could give you instability and neutralizing problems. If you have an exciter in the 70 to 100 watt class and you have a linear that uses low excitation you have a

"swamping problem" where you must stabilize and dissipate some of the exciter's energy. Don't be lulled into the trap of buying a 100 watt exciter and plan to back down the audio gain to reduce power as this presents an entirely new set of problems. For example, your carrier suppression and noise level rise and in addition are more difficult to keep in adjustment.

Whether you use a type AB or AB¹ amplifier is not really important. However, if you select zero bias tubes your bias problems are simplified. The problem of having a "stiff" bias supply (a well regulated supply) is eliminated. The grounded grid amplifier should be seriously considered as they are simple, easy to build, most stable and just about fit the average 70 to 100 watt exciter perfectly.

Your experience with Class C amplifiers will have to be forgotten when adjusting and discussing linear amplifiers. Linears are easy to tame but you must remember the driving power, grid current, and plate current dip are quite different than when working with the Class C amplifier.

Power calculation, which can be quite tricky, is not complicated, just a little confusing. You hear the term p.e.p. used on the air and in transmitter specifications. Just what is p.e.p. (peak envelope power)? It is simply the d.c. power input at the peak of the modulation envelope and is limited by the tube plate efficiency. This factor is based on the assumption that the average voice inflection does not exceed the dissipation of the tube. When you read the FCC regulations it doesn't mention the term p.e.p.

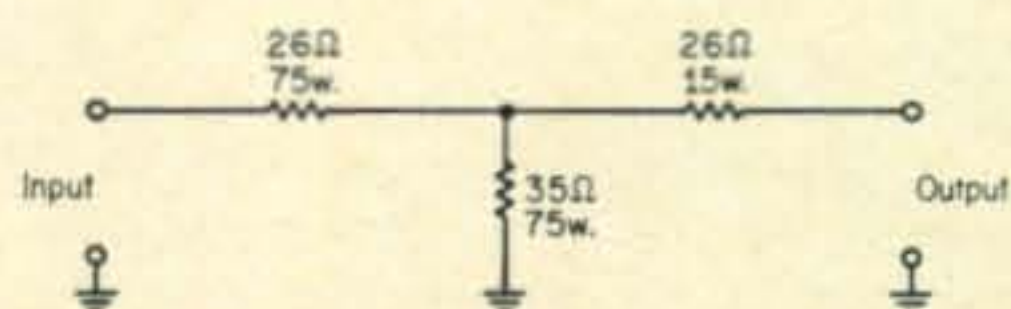


Fig. 1—The T pad circuit can be used to drop the exciter output of 100 watts to 10 watts for a linear and still maintain a proper impedance match.

*2775 Seminole Road, Ann Arbor, Michigan, 48104.

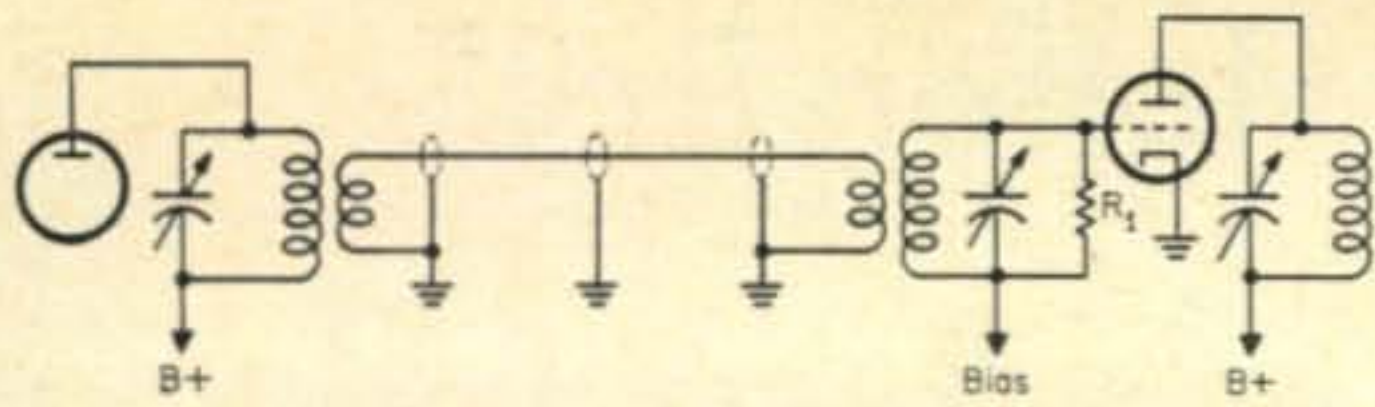


Fig. 2—The exciter output can be swamped by the use of R_1 as explained in the text.

Instead, the FCC regulations say: the legal power input shall be 1 KW d.c. input to the stage or stages delivering power to the antenna. The regulations go on to say: the plate meter used to measure the final plate current shall have a time constant not exceeding 0.25. This time constant is specified because meters are bothered by mechanical inertia. The meter needle just cannot physically follow the rapid excursions of the voice inflections and only shows average. Thus, when you talk up the current on the final amplifier to the point where the peaks don't exceed 500 mils at 2000 volts you are meeting the FCC regulations. (That is if you are not flat topping or creating some other type of distortion.) Even though your d.c. input is not exceeding 1000 watts by meter calculation, your peak envelope power (p.e.p.) is now approximately 2 KW. This p.e.p. is your effective radiated power.

The amount of excitation a linear receives is important. In most exciters you have more power than is necessary to drive the linear and, thus you must find a means to reduce it. To take advantage of the specified carrier suppression (approximately 50 db, average) of your 100 watt exciter you must run the exciter at 100 watts. Anything less will result in poorer carrier suppression. You cannot simply cut back the audio gain control to reduce power. Thus, the only means you have is to use power reducing networks. Naturally, you match the impedance of the power reducing network to the exciter and the final. Most of the equipment today is in the 50 ohm category and has a power output of 100 watts. Those linears that require lower power generally need around 10 watts or so. Therefore, let's consider a T pad

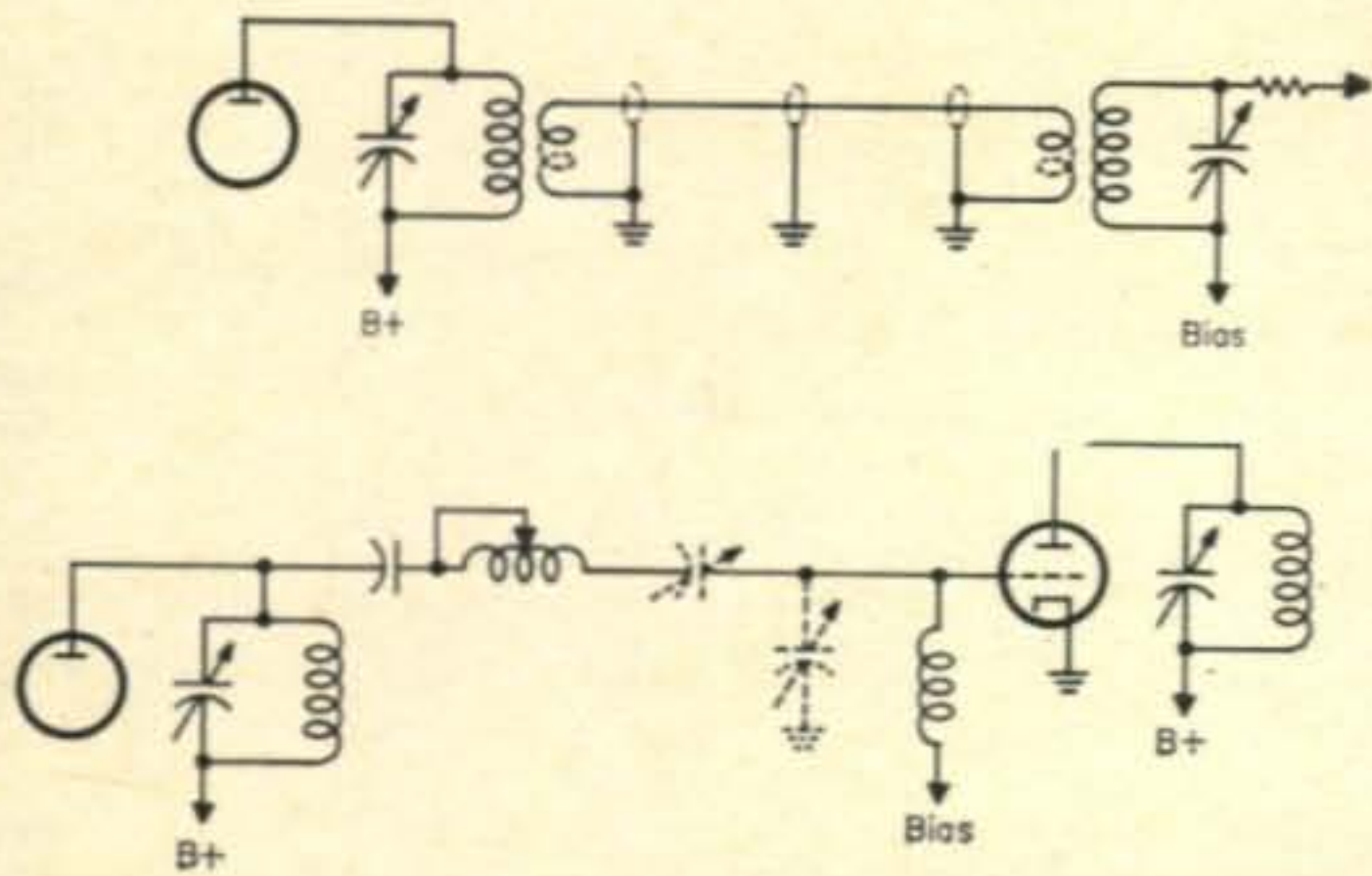


Fig. 3—When coupling the exciter to the linear the s.w.r. on the line must be kept as low as possible. Shown above are two methods of adjustment, one by adjusting the number of turns on the link and the other by tuning with an L-network.

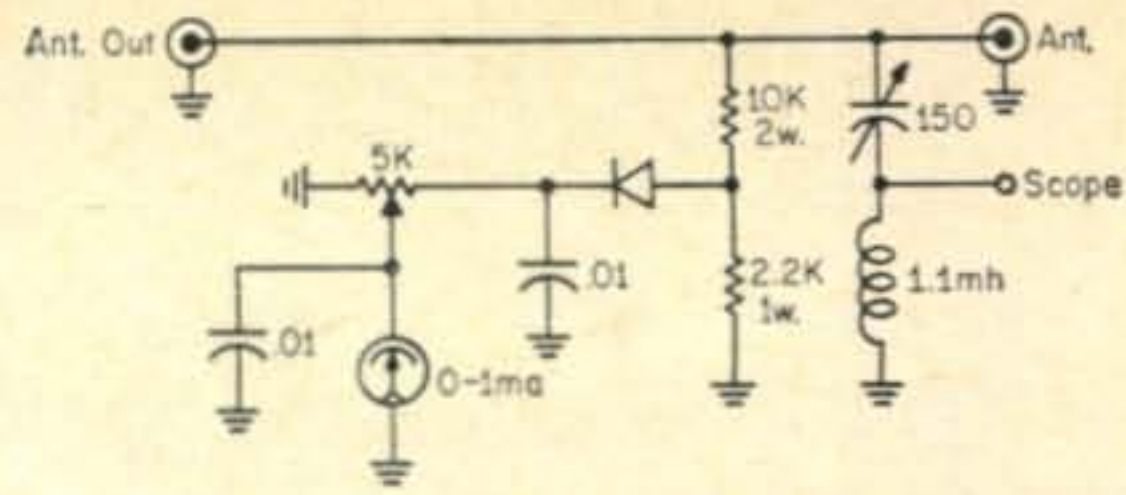


Fig. 4—This output indicator can be connected to the antenna line and it will show relative r.f. output on the 0-1 ma meter. It also provides an attenuated take-off for a scope. This type of tuning aid is almost a must for adjusting linears.

reducing network of about 50 ohms input and output with 100 watts in and 10 watts out. See fig. 1. These figures are not exact but near enough to match and close enough for a cut and try approach. The wattages shown are larger than necessary for safety factors. The resistances should be non-inductive.¹

Another method of varying the load and excitation is "swamping". This is a highly controversial means of obtaining results. Six men will give you six different answers—but all basically will agree that the method works, but all will disagree as to the value of the resistor. This is shown in fig. 2. This resistor, R_1 , should be about 5000 ohms, non-inductive and match the power of your exciter. The best way to approach this method is to cut and try with different sizes of resistors until you achieve the desired results. Use as much swamping as the exciter will stand. This will give you a more nearly constant load.

The object of matching a driver to the amplifier is to load the driver plate circuit so that you obtain the desired excitation without exceeding the plate input of the driver tube. Most drivers have 50 ohms output and generally are connected to the final with 50 ohm coax. Your objective is to make the line between your exciter and final have as low an s.w.r. as possible over as wide a band of frequencies as possible. To keep yourself out of trouble, if you are band switching use as short a line as possible. Several feet can be tolerated at 80 meters but on 10 meters even a short length can cause trouble.

[Continued on page 90]

¹Glanzer, K., "T Pads for R.F. Circuits," *CQ*, July, 1964, P. 31.

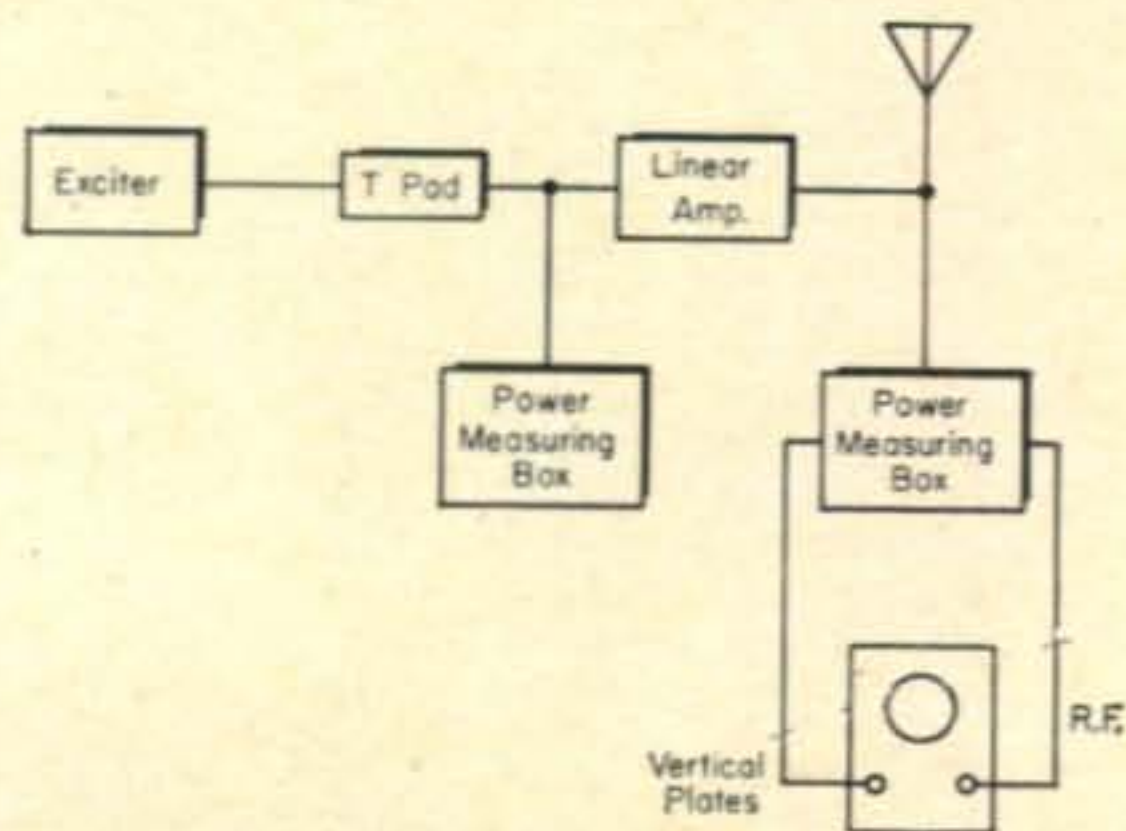


Fig. 5—An ideal monitoring arrangement for the linear is shown above. Power input power output and flat topping checks are made with ease.

CQ Awards Honor Roll

Worked All Zones. The following is a list of the call-letters of top DXers throughout the world who have qualified for the Worked All Zones Award as of October 1, 1965. Calls are listed in alphabetical order by call area and country.

RADIOTELEGRAPH

W1AB	W2BHU	W20GE	W3EPV	W4CKB	W4TFL/1	W5QK	W6DUB	W6KTE	W6RAN	W7AEA	W8AMZ	W8TJM	W9MZP
W1ACB	W2BMK	W20KM	W3EVW	K4CLT	W4TM	W5QKZ	W6DUC	W6KUT	W6RBQ	W7AHX	W8ARH	W8TLL	W9NDA
W1AJG	W2BOK	K20LS	W3EYF	W4COC	K4TWK	W5QN	WA6DUG	W6KYG	W6RDR	W7AIB	W8BHW	W8TMA	W9NLJ
W1AZY	W2BRR	W20TC	W3FYF	K4CTU	W4UXI	W5QVZ	W6DVB	W6KYT	W6REH	W7AJS	W8BOJ	W8TTN	W9NRB
W1BFT	W2BRV	W2PCJ	W3GAU	W4CXA	W4VMS	W5RS	W6DZZ	W6KZL	W6RKP	W7AMX	W8BRA	W8TTS	W9NZZ
W1BGA	K2BU	W2PDB	W3GEN	WA4CXR	W4VPD	W5RU	W6EAK	K6LAE	W6RLN	W7AQB	W8BSH	W8UAS	W90D
W1BGW	W2BVN	W2PEO	W3GHD	W4CYR	W4VYP	K5STL	K6EC	WA6LCK	W6RLP	W7ASG	W8CDT	W8UMR	W90TS
W1BIH	W2BXA	K2PFC	W3GJY	W4CYU	W4WDI	W5TIZ	K6EDE	W6LDA	W6RLQ	W7AUS	W8CED	W8UPN	W90VF
W1BIL	W2BYP	K2PIC	W3GRS	W4CYY	W4YGZ	W5TPC	W6EFM	W6LDD	W6RM	W7BD	W8CLR	K8VDV	W9PIO
W1BLO	K2BZT	K2PKT	W3HHK	W4DHZ	W4YWX	W5URU	W6EFR	W6LEE	K6RTK	W7BE	W8CRI	W8VLK	K9PJN
W1BPW	K2CD	W2PTD	K3HQJ	W4DKP	W4ZYS	W5UX	W6EGB	W6LER	W6RW	W7BGH	W8CQ	W8WBV	W9PQA
W1CKA	W2CNT	W2PTI	W3IMV	W4DLG		K5UYF	W6EHV	W6LGD	K6RWO	W7BPS	W8CUT	W8WT	W9PVA
W1CKU	K2CPR	W2PZI	W3IPO	W4DQH		K5AAP	W5VA	K6EIV	K6LGF	W7BTH	K8CVQ	W8WZ	W9QGR
W1CTW	W2CWK	W2QDY	W3IXN	W4DQS		K5ABW	W5VIR	W6EKZ	W6LGZ	W6SA	W7CAB	W8CWY	K9QIE
W1CUX	W2CFZ	W2QHH	W3IYE	W4EEE		W5ABY	W5WZQ	K6ENL	W6LN	W6SAI	K7CHT	W8DAW	W9QLD
W1CV	W2CZO	K2QHL	W3JKO	W4EJN		K5ADQ		W6ENV	W6LRU	WA6SBO	W7CKY/	W8DEN	W9QIY
W1DGJ	K2DCA	W2QJM	W3JNN	W4EO		W5ADZ	W6AAO	K6ENX	W6LS	W6SC	KL7	W8DFQ	W9ABA
W1DGT	W2DEC	K2QXG	W3JTC	W4EPA		W5AFX	W6ABA	W6EOZ	W6LTX	K6SHJ	W7CMO	W8DHC	W9ABB
W1DHO	W2DEO	W2RA	W3JTK	W4FFV		W5AI	W6ADP	W6EPZ	W6LW	W6SIA	W7CNM	W8DLZ	K9AGB
K1DMG	W2DGW	W2RDD	W3JW	W4FUI		W5ARJ	W6AFI	W6ERS	K6LZI	W6SN	W7CSW	W8DMD	K9ALP
W1DQH	WA2DIG	W2REF	W3JZY	W4FZO		W5AWT	K6AHV	W6ETJ	W6MDK	W6SQP	W7CWE	W8DSZ	K9AVQ
W1EIO	W2DOD	W2RGV	W3KA	W4GD		K5BGB	W6ALQ	K6EVR	W6MEK	W6SR	W7DAA	W8DX	W9RBI
W1EOB	W2DS	W2SAW	W3KBC	W4GRP		K5BGT	W6AM	K6EWL	W6MHB	W6SRF	W7DET	K8DYX	K9BVR
W1EQ	W2DSU	WA2SFP	W3KDF	K4GSS		W5BOS	W6AMA	W6EYC	W6MJB	W6SRU	W7DIS	W8ELL	W9BZB
W1FFO	K2DSW	W2SHC	W3KDP	K4GSU		W5BRR	WA6AMZ	WA6EYP	M6MJY	W6SUQ	W7DJY	W8EVZ	K9CAZ
W1FH	W2EHN	W2SHZ	W3KFQ	W4GXB		W5BUK	W6ANN	W6EYR	W6MLS	K6SXA	W7DL	W8EWS	K9CJL
W1FQA	WA2ELS	W2SSC	W3KPI	W4HA		W5BZT	W6AOA	K6FET	W6MLY	W6SYG	W7DLR	W8EYE	K9CLO
W1FZ	W2EQS	W2SUC	W3KT	K4HFS		WA5CBL	W6AOD	W6FHE	W6MUC	W6TEU	W7DXZ	W8FKE	K9CUI
W1GKJ	W2ESO	WA2TAG	W3KVQ	K4HJJ		W5CE	W6AQP	W6FHW	W6MUF	WA6TGY	W7DZ	W8FRW	K9DNR
W1GKK	W2EXH	W2TP	W3KZQ	W4HUE		W5CEW	W6ATO	W6FLT	W6MUM	W6TI	W7EJD	W8GB	W9DUY
W1GVZ	W2FBS	W2TQC	W3LE	K4HYL		W5CK	W6AUT	W6FOZ	W6MVQ	W6TKX	W7ENW	W8GLK	W9DWQ
W1GYE	K2FC	W2TQR	W3LMA	K4ICK		W5CKY	W6AVM	W6FSJ	WA6MWG	W6TPJ	W7ETK	W8HGW	W9DYG
W1HGT	W2FCQ	W2TVR	W3LMM	W4IFN		W5CYE	K6AYA	WA6FTM	W6MX	K6TQR	W7FB	W8HMI	K9EAB
K1HVV	WB2FMK	W2TWC	W3LMO	K4IIC		W5DA	W6AYZ	W6FUF	W6NGA	W6TS	W7FLD	W8HUD	K9ECO
W1HX	W2FSN	W2TXB	W3LOE	W4IMI		K5DGI	W6BAF	W6FWQ	W6NHA	K6TSY	W7FUL	W8IBX	W9EHW
W1HZ	WB2FSW	W2UFT	W3LUD	W4IUO		W5DML	W6BAM	W6FZL	W6NIF	W6TT	W7FZA	K8IBZ	W9ERU
W1ICP	W2FVI	K2UKQ	W3MFJ	W4JAT		W5DRU	W6BAX	W6GAL	W6NJU	K6TXA	W7GBW	W8ILG	W9ESD
W1IJB	W2FXA	K2UPD	W3MFW	W4JDR		W5EGK	K6BFZ	W6GDJ	W6NKR	W6TXL	K7GCM	K8IQQ	W9ESQ
W1IJO	W2FXN	W2UTH	W3MJF	K4JEY		W5EJT	K6BHM	WA6GFE	W6NNV	W6TZD	W7GDS	W8IQS	W9ETN
W1JDN	W2FZY	W2UVE	W3MSR	W4JII		W5EJV	W6BIF	W6GFE	W6NRQ	W6UCX	W7GHB	W8IRN	W9EU
W1JYH	W2GDX	W2UZF	W3MVQ	W4JIL		W5ENE	W6BIL	WA6GFY	W6NTR	W6UDR	K7GIE	W8JBI	W9EXY
W1KQF	K2GFQ	W2VZ	W3MWC	W4JNE		W5EZE	W6BPD	K6GLC	W6NWI	W6UHA	W7GUI	W8JIN	W9FBI
W1KXU	K2GMO	W2VND	W3NCF	W4JV		W5FFW	K6BPR	WA6GLD	W6NXP	W6UJ	W7GUV	W8JRB	W9FDX
W1LHZ	W2GNQ	W2VUF	W3NKM	K4JVE		W5FNA	W6BSY	K6GMA	W6NZ	W6UNP	W7GXA	W8JRG	W9FID
W1LQ	W2GT	K2VUI	K3NMY	K4KFC		W5FXN	W6BUD	W6GMC	W6OBD	W6UOV	W7HDL	W8JSU	W9FJB
W1LZE	W2GVZ	W2VYX	W3OCU	K4KOY		W5GEL	W6BUO	W6GMF	W6OEG	W6UQQ	W7HIA	K8JWC	W9FKC
K1MLI	W2HMJ	W2WMG	W3OP	W4KWC		W5GNG	W6BUY	W6GPB	W6OES	W6UYW	W7HKT	W8JXY	W9FKH
W1MQV	W2HO	W2WS	W3PGB	K4LNM		W5HDS	W6BVM	W6GRL	WA6OET	W6UZX	W7HXG	K8KAE	W9FVU
W1MV	W2HSZ	W2WZ	W3PN	K4LPW		W5HJA	K6BWX	W6GSL	W6OF	W6VE	W7IWH	W8KBT	W9GDI
W1NHJ	W2HTI	W2YTH	W3QQ	W4LRN		W5IAH	W6BYB	W6GUI	K6OHJ	W6VFR	W7IYA	W8KIA	W9GFF
W1NLM	W2HQL	K2YXY	W3RBF	W4LVV		W5JUH	W6BYH	W6GWW	WA6OHJ	W6VNJ	W7IYW	W8KIT	W9GHK
W1ODW	W2HUV	W2ZGB	W3RBW	W4LYV		K5JZY	W6BZ	W6HDF	W6OMC	W6VSS	W7KTN	W8KMD	W9GIL
W1OJR	WB2HXD	W2ZTV	W3RPG	W4LZF		K5KBH	W6BZE	W6HJT	W6OME	W6VUW	W7KWA	W8KML	W9GRF
W1OOA	K2HXL	W2ZVS	W3RSR	W4MCM		W5KC	W6CAE	K6HOR	W6OMR	K6VVA	W7KWC	W8KPL	W9GXH
W1OOS	W2HZY	W2ZXL	W3RUT	W4ML		K5KES	W6CBE	WA6HRS	W6ONK	W6VVR	W7LBP	W8KSR	W9HCR
W1ORV	W2ICO	W2ZY	W3RZL	W4MR		W5KF	W6CEM	W6HVN	W6ONZ	W6WB	W7LYL	W8KZT	W9HGP
W1OTX	W2IOP		W3SOH	W4MS		W5KLB	WB6CFO	W6HX	K6OPI	W6WGC	W7LZF	W8LOF	K9HOL
W1PFA	W2IRV	W3AEL	W3SWV	W4NBV		W5KUC	W6CG	W6IBD	W6OSU	W6WJM	W7MCT	K8LSG	W9HTY
K1PNL	W2IWC	W3AFM	W3TMZ	W4NJF		W5LBI	W6CGP	W6ID	K6OT	W6WKU	W7MGT	W8LUZ	W9HUZ
W1QJR	W2JAE	W3ALB	W3UXX	W4NNH		W5LCI	W6CHV	W6IDZ	W6OUN	W6WO	W7MX	W8LY	W9IHN
W1QNC	WA2JBV	W3AOH	W3VKD	W4NO		W5LEF	W6CIS	K6IEC	K6OWQ	W6WQT	W7NRB	W8MCC	W9ILW
W1RAN	K2JGG	W3ARK	W3WGH	W4NYF		W5LGG	K6CQM	W6IFW	K6OXU	W6WTH	W7OY	W8MPW	W9INN
K1SHN	W2JT	W3AS	W3WPG	W4OM		W5LGS	W6CTL	W6IPH	W6OYD	W6WWQ	W7PB	W8MTQ	W9IRH
W1TSL	W2JVU	W3AXT	W3WU	K4OMR		K5LIA	W6CTO	W6ISQ	K6OYD	W6WX	W7PHO	W8NBK	W9IU
W1TYQ	K2JYH	W3AYD	W3WV	W4OPM		W5LP	K6CTV	W6ITA	W6PB	W6YK	W7PQE	W8NJC	W9IVZ
W1WDD	K2KCE	W3AYS	W3ZAO	W4PAA		W5LRY	W6CUF	W6JH	W6PBI	W6YMD	W7QGF	K8OHG	W9IWX
W1WLW	W2KED	W3BCY		K4PDV		K5LZO	W6CUL	W6JHV	W6PCS	W6YMH	W7QNI	W8ONA	K9IYW
W1WY	W2KIR	W3BES	W4AAU	W4PLL		W5MBB	W6CUQ	K6JIC	W6PDB	W6YMV	W7QON	K8ONV	W9JIP
W1YYM	W2KJZ	W3BHV	W4AH	W4QCW		W5MCO	K6CWS	W6JK	W6PFD	W6YY	W7QY	W8OYP	K9JJR
W1ZD	W2KUW	W3BQA	W4AIS	K4QIJ		W5MMD	K6CYG	W6JKJ	W6PH	W6YZU	W7RT	W8PHZ	W9JUV
W1ZW	W2LAX	W3CA	W4AIT	W4QT		W5MY	K6CYI	K6JQJ	W6PHF	W6ZCY	W7SGN	W8PQQ	W9KA
W1ZZK	W2LNB	W3CGS	W4AIX	W4RBZ		W5NOT	K6CYO	W6JRY	W6PHN	W6ZEN	W7STC	K8PUU	W9KMN
	W2LPE	W3CPV	K4ASU	K4RDE		W5NUT	W6CYV	W6JZP	W6PKO	K6ZMB	W7UVR	W8QFR	W9KOK
W2AEB	W2LSX	W3DBX	W4AVY	K4RID		W5NW	W6CZQ	W6KBC	W6PLK	W6ZMW	W7UZA	K8QJH	W9KXK
WA2AEI	W2LV	W3DJZ/	K4AW	W4RLS		K50GP	W6DAX	W6KEK	WA6PMK	W6ZMX	W7VY	W8QNW	W9KXZ
W2AGW	K2LWR	BOC	W4AZK	K4RPK		W50GS	W6DBP	W6KEV	K6POC	W6ZUI	W7WVE	W8QQH	W9LIL
W2AQW	W2MES	W3DRD	W4BFR	W4RVW		W50LG	K6DDO	W6KG	W6PQT	W6ZVQ	W7YGN	W8QWI	W9LJU
W2AYJ	W2MUM	W3DWW	W4BJ	K4RZK		W5PIO	W6DFY	K6KII	W6PUY	W6ZZ	W7ZAS	W8QZA	W9LNM
W2AYU	W2NOY	W3DXN	W4BPD	W4SHX		W5PM	W6DI	W6KIQ	W6PZ		W7ZOH	W8RSW	W9LQF
W2AZS	W2NUT	W3ECR	W4BQY	W4SNU		W5PQA	W6DIX	K6KJR	W6QD	W7ABO		W8RQ	W9LSV
W2BAC	W2OBX	W3EFZ	K4BVQ	W4SSU		W5PSB	W6DLN	WA6KNE	W6QDE	W7AC	W8AE	W8SDR	W9MBF
W2BBS	W2OCL	W3EOB	W4BYU	W4SXE		W5PWW	W6DLY	W6KRI	WA6QGW	K7ADL	K8AJK	W8SYC	W9MQK
W2BHM	K20EA	W3EPR	W4BZ	K4SXR		W5PZL	W6DQH	W6KSM	W6QNA	W7ADS	W8AJW	W8SZS	W9MUJ
													K0EUV

W0EWH	DJ1DF	DL3BJ	F3YR	G3IOR	HB9DB	JA3UI	OD5LX	OK1KKJ	PY1HX	SP8HT	VE2BV	VK3JE	ZL1ARY
K0EZH	DJ1JW	DL3BK	F3ZU	G3JAF	HB9DX	JA5AI	OE1BH	OK1KT1	PY2CK	SP8SZ	VE2NV	VK3KB	ZL1AV
W0FFV	DJ1KR	DL3BL	F8BS	G3JHZ	HB9EO	JA5FQ	OE1CD	OK1LM	PY3QX	SP9ADU	VE2WW	VK3NC	ZL1BY
W0FLK	DJ1VP	DL3CM	F8IH	G3JLB	HB9ET	JA6AD	OE1FF	OK1MB	PY4A0	SP9DT	VE2YU	VK3KS	ZL1GX
W0FNN	DJ1VS	DL3DD	F8KJ	G3JUL	HB9EU	JA6AK	OE1FT	OK1MG	PY40D	SP9KJ	VE3BMO	VK3RJ	ZL1HY
W0FRX	DJ2AE	DL3FM	F8TM	G3JZK	HB9GJ	JA6AO	OE1HGW	OK1MP		SP9NH	VE3BMY	VK3RP	ZL1PV
W0FUH	DJ2BO	DL3IE	F8VQ	G3KHE	HB9HZ	JA6MW	OE1RZ	OK1PD	SM1CXE	SP9TA	VE3CFG	VK3TL	ZL1RD
W0GNG	DJ2BW	DL3LB	F8WK	G3KKP	HB9IM	JA7AD	OE3HY	OK1RW	SM2BCS	ST2AR	VE3CIO	VK3XB	ZL2AFZ
W0GUV	DJ2CM	DL3LL	F8XT	G3KZI	HB9J	JA8AA	OE3NH	OK1SV	SM3AF	SV0WP	VE3DEB	VK3YD	ZL2AI
K0GXR	DJ2EO	DL3RK	F9EJ	G3LET	HB9JG	JA8AQ	OE3RE	OK1TW	SM3AGD	SV0WZ	VE3DIF	VK3YL	ZL2CU
K0HGB	DJ2HI	DL3SZ	F9ER	G3LHJ	HB9KB	JA9AA	OE3WB	OK1VB	SM3AKM		VE3DKY	VK4AL	ZL2GX
W0HX	DJ2JE	DL3TG	F9IL	G3LP	HB9KC	JA0AC	OE5JK	OK1WX	SM3AKW	TI2LA	VE3ES	VK4DO	ZL2HP
W0ICQ	DJ2KS	DL3TJ	F9MS	G3LPS	HB9KU	JT1CA	OE5LX	OK1XQ	SM3ATY	TN8AF	VE3EU	VK4EL	ZL3DX
K0IKL	DJ2LK	DL3TW	F9RS	G3OZU	HB9LB		OE8KI	OK1YD	SM3BHT		VE3IR	VK4FJ	ZL3GU
K0KKU	DJ2LM	DL3WV	FA9RW	G3TK	HB9MO	KA2AB	OE8SH	OK1ZL	SM3BIZ	UA1CB	VE3JZ	VK4HR	ZL3IS
W0KOK	DJ2MN	DL3YQ	F9TX	G3VA	HB9MQ	KA2DE	OH1QE	OK2AG	SM3EP	UA1CK	VE3KE	VK4SD	ZL4AW
W0LBB	DJ2RE	DL3ZA	FA8RJ	G3VW	HB9MU	KA2NY	OH1SN	OK2NN	SM4AD	UA1CX	VE3QD	VK4TY	ZL4BO
W0LFY	DJ2SR	DL3ZI	F9BB	G3YF	HB9NL	KG6AL	OH1ST	OK2OV	SM4AEQ	UA1DI	VE3RE	VK5BS	ZL4CK
W0LPA	DJ2VK	DL4BS		G4CP	HB9PA	KG6GD	OH1PI	OK2QR	SM5AHK	UA1KBA	VE3TB	VK5GG	ZP5LS
W0LVA	DJ2WN	DL6DE	G2AGR	G4FN	HB9TL	KH6AUJ	OH1TM	OK2SO	SM5AJR	UA2AO	VE4OX	VK5JS	ZS10U
W0MAF	DJ2YA	DL6EN	G2AJB	G4MJ	HB9TT	KH6AYG	OH2A	OK2UD	SM5AJU	UA2KAA	VE4RO	VK5KO	ZS1RM
W0MCX	DJ2YL	DL6EQ	G2AOL	G4TM	HB9UE	KH6BA	OH2BC	OK3AL	SM5AQB	UA3AN	VE4TJ	VK5MF	ZS2AT
W0MLY	DJ2ZJ	DL6FF	G2BOZ	G5BJ	HB9UL	KH6BLX	OH2BZ	OK3DG	SM5AQV	UA3AW	VE4XO	VK5NQ	ZS2CR
W0NCS	DJ2ZX	DL6GB	G2BVN	G5DV	HB9X	KH6BTX	OH2DP	OK3EA	SM5ARR	UA3BN	VE5JV	VK5QR	ZS2CV
W0NLY	DJ3BB	DL6GP	G2CNO	G5GK	HB9YL	KH6BXU	OH2HK	OK3EE	SM5ATK	UA3CA	VE5KG	VK5RX	ZS2EC
W0NTA	DJ3JZ	DL6MK	G2FFO	G5LP		KH6CD	DH2HW	OK3HM	SM5BC	UA3CT	VE5TK	VK6DX	ZS2RM
W0NUC	DJ3KR	DL6OS	G2FSR	G5MD	I1ALU	KH6CT	OH2LA	OK3IR	SM5BCE	UA3FT	VE5VL	VK6KW	ZS2U
W0OQK	DJ3XK	DL6QW	G2FYT	G5RP	I1AY	KH6CUP	OH2LX	OK3KMS	SM5BEU	UA3FU	VE6AAV	VK6RU	ZS2X
W0OUH	DJ4DN	DL6TW	G2GM	G5VU	I1BNU	KH6DKA	OH2MB	OK3MM	SM5BFE	UA3GM	VE6ABP	VK6SA	ZS4MG
K0PEF	DJ4HR	DL6YK	G2IO	G5YV	I1CHJ	KH6DLD	OH2NB	OK3OM	SM5BGM	UA3HI	VE6AO	VK7CH	ZS6A
W0PGI	DJ4OP	DL7AA	G2LB	G6BS	I1ER	KH6DLF	OH2TM	OK3UL	SM5BIU	UA3KND	VE6BY	VK7LZ	ZS6AJQ
W0PNQ	DJ4SP	DL7AB	G2MI	G6QB	I1FO	KH6DJ	OH2VZ	ON4DM	SM5BPJ	UA4HC	VE6GD	VK9XK	ZS6ATA
W0QDF	DJ4TZ	DL7AD	G2PL	G6RC	I1IF	KH6JQ	OH2XK	ON4FQ	SM5BRO	UA4HP	VE6JR	VO1DX	ZS2U
W0QGI	DJ5IM	DL7AH	G2VD	G6RH	I1IR	KH6KC	OH2YV	ON4FU	SM5BST	UA4IF	VE6MN	VP7NS	ZS2X
W0QVZ	DJ5MX	DL7BK	G2WQ	G6UT	I1KN	KH6LG	OH3NY	ON4IX	SM5BVF	UA4KHA	VE6NX	VQ2GW	ZL2JO
W0QYE	DJ5VQ	DL7CS	G2YS	G6VC	I1NU	KH6MG	OH3OD	ON4JW	SM5BZ	UA4KHW	VE6TP	VQ2W	ZL3AB
K0RAL	DJ8RR	DL7CW	G3AAE	G6VQ	I1SF	KH6MI	OH3PF	ON4LB	SM5CCE	UA4PA	VE6VK	VQ2WR	ZS4MG
W0RBA	DJ9GD	DL7DTB/6	G3AAM	G6XA	I1SM	KH6PM	OH3QC	ON4MN	SM5CO	UA4PW	VE7AHG	VQ4ERR	ZS6A
K0RHO	DJ9HA	DL7EG	G3AGN	G6XL	I1UA	KH6PY	OH3RA	ON4QF	SM5CXF	UA4QA	VE7BW	VR2BZ	ZL4AW
W0SMV	DJ0IK	DL7EN	G3AIM	G6YQ	I1UB	KH6QH	OH3RS	ON4QJ	SM5DW	UA6FD	VE7CE	VS1FZ	ZL4BO
W0SML	DL1AM	DL7HU	G3AIZ	G6ZO	I1XK	KH6VP	OH3SE	ON4QX	SM5EC	UA9CL	VE7CQ	VS1JF	ZL3GU
W0SQO	DL1AU	DL7JA	G3AJP	G8FW	I1ZCT	KL7BHE	OH3TA	ON4SB	SM5KP	UA9CR	VE7GI	VS4RS	ZS2AT
W0SYK	DL1BO	DL8CH	G3ASG	G8GP	I1ZL	KL7MF	OH3TH	ON4TA	SM5KV	UA9DN	VE7HC	VS6AE	ZS2CR
W0TJ	DL1BS	DL8CM	G3ATU	G8IG	I1ZN	KL7PI	OH3TY	ON4TX	SM5KX	UA9DT	VE7JB	VU2AK	ZS2CV
K0UKN	DL1CF	DL9EH	G3AZ	G8IP	IT1AGA	KL7PIV	OH3UO	OY7ML	SM5LL	UA9VB	VE7KC	VU2MD	ZS2EC
W0UOX	DL1DC	DL9KP	G3BHW	G8JM	IT1TAI	KL7PJ	OH3XZ	OZ3GW	SM5LN	UA9WS	VE7KJ		ZS2RM
W0UQV	DL1DX	DL9OH	G3BI	G8JO	IT1ZGY	KL7UM	OH4NS	OZ4H	SM5WI	UA0GF	VE7MD	XE1AE	ZL3IS
W0VAF	DL1EE	DL9PF	G3BKF	G8KP		KP4AQQ	OH5NJ	OZ4RT	SM5WZ	UA0OM	VE7PU	XE1CV	ZS6AJQ
W0VBK	DL1ES	DL9PX	G3CEG	G8KS	JA1AA	KP4KD	OH5NK	OZ5JT	SM5YG	UB5AQ	VE7PV	XE1PJ	ZS6ATA
W0VBQ	DL1FF	DL9RK	G3CSL	G8KU	JA1AB	KP4RK	OH5OP	OZ7BG	SM6AMD	UB5CG	VE7QL	XZ2TH	ZL4CK
W0VKB	DL1FK	DL9TJ	G3CQE	G8PL	JA1AG	KP4YT	OH5OU	OZ7KV	SM6AMF	UB5CI	VE7SB		ZP5LS
K0WQI	DL1FZ	DL9YX	G3DO	G8QZ	JA1BF	KP6AA	OH5PE	OZ7SN	SM6APH	UB5FJ	VE7VC		ZS10U
W0YTL	DL1GU	DL0FT	G3DOG	G8TD	JA1BK	KR6JZ	OH5RH	OZ8SS	SM6CCB	UB5KAB	VE7VO	YO2BU	ZS1RM
W0YTL	DL1GV	DM2AEJ	G3DQC	G8UG	JA1BLC	KR6LJ	OH5TK	OZ9N	SM6VY	UB5KDS	VE7ZK	YO2CD	ZS6CT
W0YXO	DL1HA	DM2AND	G3DQO	GB2SM	JA1BN	KV4AA	OH5UQ		SM7AIA	UB5MZ	VE7ZM	YO3FF	ZS6DW
W0ZYB	DL1HH	DU7SV	G3ESY	GI3AXI	JA1BNK	KW6DF	OH5VF	PA0FAB	SM7ANB	UB5ZV	VE8AW	YO3RD	ZS6EU
	DL1IA		G3EYN	GI3NPP	JA1BRK	KW6DG	OH6AA	PA0FX	SM7CAB	UC2AA	VE8DX	YO8CF	ZS6FN
CE3AG	DL1IB	EA1BC	G3FKM	GI3OQR	JA1BTM		OH6OA	PA0HG	SM7CNA	UC2AD	VE8PB	YU1AG	ZS6IF
CE3AX	DL1IN	EA1GZ	G3FPI	GI4RY	JA1BWA	LA1H	OH6RC	PA0LOU	SM7EH	UC2AR	VE8RG	YU1EH	ZS6IW
CE3DZ	DL1IP	EA2CR	G3FPK	GI6TK	JA1CC	LA1K	OH7OU	PA0LY	SM7ID	UC2CB	VK2ACX	YU1KC	ZS6LW
CE3HL	DL1IT	EA3CY	G3FUR	GM3ASM	JA1CR	LA2B	OH8QA	PA0OI	SM7MS	UD6AM	VK2AM	YU3EA	
CN8BP	DL1KB	EA3KI	G3FXB	GM3CIX	JA1DM	LA3DB	OH9NC	PA0PN	SM7QY	UF6FB	VK2APK	YU3OV	3V8AB
CN8DJ	DL1KS	EA4CR	G3GAD	GM3DHD	JA1FHK	LA3UF	OH9PF	PA0RLF	SM7TQ	UH8BO	VK2DI	YV5AB	
CN8GU	DL1LT	E13R	G3GCD	GM3EST	JA1GC	LA4DD	OH9RD	PA0TAU	SM7TV	UH8DA	VK2HZ	YV5AXQ	
CN8IF	DL1LZ	E14Q	G3GFG	GM3LYS	JA1GV	LA5HE	OK1AEH	PA0VB	SM7YO	UI8AG	VK2JZ	YV5BQF	4X4CJ
CN8JX	DL1ME	E19U	G3GGS	GM5RH	JA1MJ	LA6U	OK1AW	PA0VDV	SP1JV	UP2KNP	VK2NS	YV5FK	4X4FQ
CO2SW	DL1MF	E19Y	G3GSZ	GM6MD	JA2AIR	LA7Y	OK1AWJ	PA0VO	SP2AP	UQ2AN	VK2PV		4X4JN
CR6AI	DL1QT		G3GYH	GW3BNQ	JA2AT	LA7Z	OK1BP	PA0WOR	SP2HL	UQ2AS	VK2QL	ZC1CL	4X4KK
CR6BX	DL1SF	F2BS	G3HCL		JA2BL	LA8LF	OK1CG	PK4DA	SP3DG	UR2AR	VK2RA	ZC4IP	4X4RE
CR7IZ	DL1TA	F2NB	G3HCT	HA1KSA	JA2DN	LU5AQ	OK1CX	PK6HA	SP4JF	UR2BU	VK2XU	ZE3JO	
CR7LU	DL1XS	F2PO	G3HDA	HA5AM	JA2DO	LU6DJX	OK1FF	PY1ADA	SP5AA	UT5AA	VK3AHQ	ZE4JS	5A1TW
CR9AH	DL1YA	F3AT	G3HFJ	HA5BI	JA2JW	LU7AS	OK1FV	PY1AHL	SP5AFL	UW3DR	VK3AX	ZE6JY	5A5TE
CX1BZ	DL1YQ	F3CB	G3HFP	HA5BU	JA2KG	LU8BAJ	OK1GL	PY1AJ	SP6AT		VK3BZ	ZE8JJ	5A5TH
CX1FY	DL1ZM	F3DM	G3HIW	HA5KAG	JA3AA	LU8EN	OK1GT	PY1BG	SP6FZ	VE1EP	VK3CN	ZK1AK	5A5TO
CX2CO	DL2YU	F3FA	G3HLY	HA5KBP	JA3BP	LZ1KPZ	OK1HI	PY1DH	SP6FT	VE1PQ	VK3CX	ZL1AH	
	DL3AO	F3II	G3ID	HA5KFR	JA3DY		OK1JQ	PY1GJ	SP7HX	VE1WL	VK3EK	ZL1AJU	
DJ1BZ	DL3AR	F3YP	G3IMV	HB9AAF	JA3FT	MP4BBE	OK1JX	PY1HQ	SP8CK	VE2AIO	VK3HL	ZL1AMO	9S4AX

RADIOTELEPHONE

W1BAN	WB2FSW	W2WZ	W4NJF	K6CYG	W6USG	W7MGT	K9EAB	W0QUU	DL6EN	G3AIZ	Q13JIM	JA1BWA	OE1FF
W1BHP	W2FXN	W2ZTV	W4OM	W6EKZ	W6VFR	W7PHO	W9EXY	W0QVZ	DL7AA	G3BYM	GI3KVQ	JA6CY	OE2YL
W1BIH	W2GNQ	W2ZX	W4PAA	W6GT	W6VUW	W7UZA	W9ILW	W0TJ	DL7AB	G3DO	GI6TK	JT1CA	OE3NH
W1DGJ	W2HTI		W4PDL	W6GVM	K6VVA	W7ZAS	W9JF	K0UKN	DL7AD	G3FKM	GW3AHN		OK1MB
W1FZ	WA2IZS	W3AYD	W4TDW	W6HYG	W6WWQ		W9NDA	CN8MM	DL7BA	G3FPM		KA2BW	OK2AG
K1IXG	K2JGG	K3COW		W6ITH	W6YK	W8ARH	W9RBI	CX2AX	DL7HU	G3FPQ	HB9DS	KG6AJB	ON4DM
W1ORV	W2JT	W3DJZ/	W5AFX	W6KTE	W6YMV	W8BF	W9UZC	CX2CO	DL9CT	G3FXB	HB9ET	KH6DLF	ON4RC
W1PST	W2MES	W3GHD	W5IYU	K6LAS	W6YY	K8CFU	W9WHM		DL9OH	G3HCT	HB9J	KH6OR	OZ7FG
W1UOP	W2OKM	W3LE	K5JEA	W6MBD	WA6ZIQ	W8CUO	W9YSX	DJ2AA	EA1GH	G3HDA	HB9KU		
W1ZW	WA2RAU	W3LMA	W5JWM	K6MLS		W8CUT	W9S	DJ2VZ	EP2AG	G3HLS	HB9MX	LA5HE	PA0FX
	W2RGV	W3LMA	W5KBU	W6NGA	W7AQB	W8EWS	W0AIW	DJ2YI		G3MVV	HK3LX	LA5LG	PA0HBO
W2APF	WA2SFP	W3NKM	W5KXG	W6OBH	W7AUS	W8IJZ	W0BFB	DJ5LA	F2MO	G3NUG	I1AOF	LA5YE	PA0WWP
W2BOK	WA2TAG	W3WGH	W5LBI	W6QOG	W7AUS	W8JIN	W0CPM	DL1FK	F3DJ	G3NWT	I1RB	LA8LF	PA0ZD
W2BXA	W2TP	W4AZD	K5MDX	W6RCD	W7BPS	W8KIA	K0CTL	DL1IN	F8DC	G6TA	I1RIF	LU1DAB	PY2CK
W2CZF	W2TVR	W4DQH	W5PQA	W6RKP	W7BTH	W8KML	W0JYW	DL1KB	F8SK	G8GP	I1SM	LU4DMG	PY2JU
K2DCA	W2UTH	W4EEE	W5PSB	K6RWO	W7CMO	W8MPW	W0LBB	DL3DW	FA8RJ	G8IG	I1UA	LU6AJ	PY4CB
W2DEC	W2UZF	K4HYL		K6TSY	W7DLR	W8PQQ	W0LIL	DL3EA		G8KS			PZ1AX
WA2ELS	W2VCZ	W4JGO	W6AM	W6TXL	K7GCM	W8WT	W0MAF	DL3LL	G2BOZ	GI3CDF	JA1ACB	MP4BBW	
W2EXH	K2VQQ	W4MS	W6CHV	W6TZD	W7LBP	W8ZET	W0MLY	DL3RK	G3AAE	GI3IVJ	JA1BK	MP4BCC	SM3AZI


SM3BIZ	SM5RY	SP9KJ	UR2BU	VE40X	VE6NX	VE7CE	VE7PU	VK2JZ	VQ4ERR	YV5AB	ZL1ACI	ZL2UW	ZS6VX
SM3EP	SM5TR			VE4XO	VE6SF	VE7GI	VE7SB	VK4FJ		YV5AIP	ZL1AIX	ZL4BO	ZS6YQ
SH5AZU	SM5WJ	UB5UN	VE1WL	VE5JV	VE6TF	VE7HJ	VE7ZM	VK4RQ	XE1AE	YV5AXQ	ZL1HY	ZS5PG	
SM5CO	SP7HX	UC2AA	VE2WY	VE5RU	VE6TP	VE7IT	VE8RG	VK5QR	XE1CV	YV5BBU	ZL1KG	ZS6LW	4X4DK
SM5LL	SP8CK	UQ2AN	VE2YU	VE6BY	VE6VK	VE7MD	VK2AAK	VK6RU	XZ2SY	YV5BQF	ZL2GX	ZS6Q	9K2AZ

ALL SINGLE SIDEBAND

W1AOL	W2EXH	W2WZ	W4MS	W5PQA	K6TSY	W7UZA	W9ILW	DL1AU	G2BVN	JA1DM	OK1MP	UA3CR	VK6RU
W1BAN	WB2FSW	W2ZTV	W4NJF	W5PSB	W6USG	W7ZAS	W9JFJ	DL11FK	G3AIZ	JA2JW	ON4DM	UA3DR	VQ2AT
W1BHP	W2FXN	W2ZX	W4OM	W5QVE	W6VUW		W9JYJ	DL1IN	G3AWZ	JA3UI	ON4QX	UA3FG	VQ4ERR
W1BIH	W2GNQ		W4OPM		K6VVA	WA8AJI	W9QQN	DL1JV	G3DO	JT1CA	OY7ML	UB5KAB	
W1DCE	WA2HOK	W3CGS	W4PAA	W6BAF	W6WWQ	W8ARH	W9SFR	DL1UX	G3FKM		OZ7FG	UR2AR	XE1AE
W1GOX	WA2IZS	W3DJZ	K4PUS	K6CYG	W6YMW	W8BF	W9UZC	DL1VR	G3FPK	KG6AJB			XE1IL
W1ICV	K2JFV	K3COW	W4QCW	W6EKZ	K6YRA	W8BKO	K0BJK	DL3DW	G3HDA	KH6DLF	PA0HBO	VE3BQP	XE2WH
K1IDW	K2JGG	W3GHD	W4RBZ	K6ERV	WA6ZIQ	K8GLH	W0BMQ	DL3IR	G3NMR	KP4CK	PZ1AX	VE4XO	XW8AS
K1IXG	W2JXH	W3JTC	W4SHP	K6EXO	W6ZJY	W8HBI	K0CTL	DL3RK	G3NUG	KP4CL		VE6BY	
K1JMV	W2LV	W3KT	W4SSU	WA6EYP	K6ZXW	W8IJZ	W0CVU	DL5AO	G6LX	KR6HL	SM2BCS	VE6NX	YO3GK
W1LLF	W2MES	W3LMA	K4TJL	W6GT		W8JIN	W0KFA	DL6EN	G8KS	LA5HE	SM3BIZ	VE6TF	
W1OOS	W2PTM	W3MAC	W4VCB/	WA6HOH	W7AQB	W8MPW	W0LBB	DL7HU	G13CDF		SM5IC	VE6TP	
W1ORV	W2QNE	W3NKM	KL7	W6HYG	W7BPS	K8NZD	W0MLY	DL9OH	G13IVJ	LA5LG	SM5LL	VE6VK	ZL1AIX
W1UOP	WA2RAU	K3TPL	W4WDI	W6KTE	W7BTH	W8PQQ	W0NFA	DL9OV	G16TK	LA8LF	SM5MC	VE7CE	ZL2GX
W1YDO	W2RGV	W3WGH	K4WHD	W6LDA	W7CMO	K8CFU	W0QLX		GM3CIX	LU1DAB	SM5UF	VE7GI	ZL3AB
W1ZW	WA2SFP	W3YZI		K6LGF	W7DLR	W8EAP	W0QVZ		GM3JDR		SM6SA	VE7IT	ZL3IA
	WA2TAG	K4AJ	W5AFX	WA6MAZ	W7DQM	W8EWS	K0RAL	E14Q		MP4BBW	SP9FR	VE7MD	ZS5DW
WA2AEI	W2TP	W4ANE	WA5EFL	K6MLS	K7GCM	K8RTW	K0RDP	EP2AG	HB9TL			VE7PU	ZS5JM
W2BXA	W2TVR	K4HEF	W5IYU	W6NWZ	K7HJN	W8TMA	W0TJ		HB9ZY	OD5CT		VE7ZM	ZS6BBP
W2CZF	W2UTH	W4HKJ	K5JEA	W6REH	W7LBP	W8YBZ	K0UKN	F8DC		OE1ME	T12HP	VE8RG	ZS6LW
K2DCA	W2UZF	K4HYL	W5KFT	W6RKP	W7PHO		W0UUV	F8SK	I1AMU	OE1RZ			ZS6YQ
W2DGW	W2VCZ	W4INL	W5KGX	K6RWO	W7QPK	K9EAB			I1RB	OH2HN	UA1CK	VK3AHO	
WA2ELS	W2MWG	W4LZT	W5MMD	K6SOK	W7UPF	W9EXY	DJ3KR	G2BOZ	I1UA	OH2NB	UA3CG	VK4FJ	4X4DK

USA-CA The United States of America Counties Certificate is awarded in six levels for working different numbers of United States counties beginning at the 500 county level. The following list, in alphabetical order, indicates those who have received the USA-CA Certificate and additional endorsements. Complete rules for the Program will be found on page 75, January, 1965 CQ.

3079	K4VOF	K3LXN	W9HUF	K1NWE	WA2WEE	K4GLA	W5BUK	WB6IUH	W8APN	W8WT	K9QBV	W0MCX	LA6CF
K9EAB	K4VRI	K4BAI	W9KA	K100J	WA2WGS	K4GMR	W5CME	W6JNX	K8BHG	W8WUT	K9QGR	K0MLM	LU1DAB
	W5EHY	WA4CLR	W9LKB	W1PLJ	WA2WQU	W4GYP	W5CRF	WA6KHK	WA8BIC	K8YBU	W9QGR	W0MLY	OK2QR
3000	W5NXF	K4ISE	K9LLX	K1QZV	W2YVQ	W4HKJ	K5DGI	WA6KNE	K8BIT	K8YGU	K9QJT	K0ORB/	OK3EA
K8CIR	K5SGJ	W4KA	W9QWM	W1RWP	K2ZKU	W4HOS	W5DJB	WA6MIE	WA8CGZ	K8ZCG	W9QWM	K0VRB	PA0VB
K9EAB	K5SGK	WA4MGC	K9UTI	W1SXX	W3AIZ	K4IEH	W5DQK	WA6MWG/	K8CIR	K8ZNI	K9RFU	W0PLN	PJ3AO/
W0MCX	W6KG	W4UF	W9UX	K1TNB	W3AYS	K4IKF	WA5DUL	KH6FLC	WA8CNN	W9ACU	W9SZR	K0QIX	VE2LP
	K8CIR	K4VOF	K9WSL	W1UOP	K3BNS	K4ISE	W5EHY	W6NAT	W8CSK	WA9AIB	K9UCG	K0QJG	PZ1AX
2500	W8CYB/2	K4VRI	K0DEQ	W1UOT	W3BNU	W4IZR	W5EJT	W6NUQ	W8CXS	WA9AJF	K9UTI	W0QWS	SM5CCE
K4VOF	K8EUX	W4VWW	K0EJW	W1VBR	WA3BQX	K4JIG	W5EMZ	WA6OET	W8CYB/2	K9AMD	W9UX	K0RGU	SM5WI
K5SGJ	WA8EZW	W5EHY	W0GYM	W1VKZ	K3BTT	W4JUJ	W5FPN	W6JW	W8DCD	K9AZX	W9UZC	K0RRO	SM7ID
K5SGK	K8IWI	W5NXF	K0HUU	K1VTM	W3BVL	W4KA	WA5FRN	W6PCA	W8DCH	W9BJH	W9UZS	K0RTH	SP7HX
K8CIR	K8KOM	K5SBN	K0IDV	W1WHQ	W3BWU	WA4KUM/	K5FTH	K6PQY	K8DCR	K9BLX	K9VYL	K0SPH	TG9AD
K8IWI	W8NAN	K5SGJ	K0IHK	W1YPH	W3CDG	W1AFA	WA5HDA	W6QIL	WA8EOH	W9CHD	K9WSL	W0TFQ	TG9SC
K8KOM	W8NXN	K5SGK	W0JWD	W1ZLX	W3DKT	W4KZF	K5IKL	WA6RXM	WA8EOZ	W9CLH	W9WUQ	K0TKQ	VE1AE
WA9AJF	W8UPH	K5UYF	W0KZZ	K1ZND	W3EFY	WN4LSU	W5KKL	WA6RZX	WA8EUC	W9CMC	K9YND	W0VFE	VE3BKL
K9EAB	K8VSL	K6BX	W0MCX	K2BFU	K3FFJ	W4LYV	W5LDH/	K6SXA	K8EUX	WA9CNN	W9YT	K0WEM	VE3CBY
W0JWD	K8YGU	W6KG	K0RTH	K2CJN	K3GEO	WA4MGC	W5LXX	W6UBP	WA8EZW	K9CSL	K9ZXG	K0WEN	VE3CWE
W0MCX	WA9AJF	K6SXA	W0VFE	K2CPR/	K3HNP	K4MPE	W5LEF	K6UHI	W8GDQ	W9CTA	WA0AAD	K0YET	VE3EUH
VE3-9301	W9CMC	W6YC	VE3BKL	W3BXE	W3IMN	K4MSS	K5LWL	WA6UQS	WA8HSB	W9DGA	WA0AQN	CO8JK	VE3EVZ
	K9EAB	K6YMZ	VE3-9301	W2EAF	K3JHG	K4MYO	K5MID	K6UTO/	W8HWX	K9DWG	WA0ARO	CR6CA	VE3LZ
	W9HAS/	W7K0I	VE3-11367	W2EBW	K3JYZ	W4NOK	K5MOF	K7UXN	W8IBX	K9EAB	W0BBS	CR7IZ	VE3RN
2000	K4KWQ	K7NHG	WPE3EBF	W2EMW	W3KDP	WA4PFQ	K5MWV	W6YC	W8IEC	K9EGQ	W0CUC	CT1PK	VE6ABP
K4VOF	W9HUF	K7SQD	WPE9ETT	K2ETC	K3LXN	K4PXY	W5NXF	K6YMZ	K8IQB	WA9FXJ	K0DEQ	DL1IB	VE6ABV
W5EHY	W9LKB	K8CIR		W2ETS	K3PSU	K4RNS	K5OCX	K6YVV	K8IWI	K9GDF	K0DEW	DL1QT	VE6AGE
W5NXF	K9UTI	W8CYB/2	500	W2EWZ	K3QVV	W4SKI	W5ONK	K7AGJ	W8JAQ	W9GFF	WA0DGW	DL9PF	VE6UP
K5SGJ	K9WSL	W8DCD	K1BOM	W2FLD	K3SLP	K4TVE	K5OPT	W7BNV/	K8JIC	W9GML	K0DJC	F9BB	VE7CE
K5SGK	K0EJW	K8EUX	K1CXP/	W2FXA	K3SVI	W4UF/	W5PQA	K7JRE	W8JXY	K9GOE	W0EGC	FG7XL	VE7HJ
K8CIR	W0GYM	WA8EZW	W1BHV	WA2HGL	W3TKQ	W4ZKD	W5PSB	K7CPC	K8KOM	W9HAS/	K0EJW	G2FFO	VK3AHO
WA8EZW	K0HUU	K8IQB	W1DMD	WB2HKZ	K3VSV	K4Vfy	K5RBN	K7CRL	W8KPL	K4KWQ	K0EQF	G3DO	VK3AXK
K8IWI	K0IDV	K8IWI	W1DPJ	WA2IMT	W3YRN	K4VGL	W5RIT	W7GA0/6	K8KPM	W9HAT	K0EQY	G4CP	VK3RJ
K8KOM	W0JWD	K8KOM	W1DWA	W2JMF	K4ADU	K4VOF	K5SBN	W7GBL	W8LAU	W9HGP	W0EXD/5	G6VQ	VK3XB
W8UPH	W0KZZ	W8NAN	W1EIO	W2JWK	WA4AEB	K4VQP	K5SGJ	K7GTK	K8MQB	W9HUF	K0FIK	G8PL	VK7SM
K8VSL	W0MCX	W8NXN	W1EQ	K2KBI	K4AUL	K4VRI	K5SGK	W7JZB	W8NAN	K9IHU	WA0FPU	GB2SM	VP9AK
K8YGU	W0VFE	W8RCJ/	W1FAB	W2KIR	K4BAI	W4VWW	K5SHQ	K7KHA	W8NXN	K9IIQ	K0GIC	GI6TK	XE1AE
WA9AJF	VE3-9301	W1BUS	W1FPS	W2KXL	W4BCB	W4WLM	W5WZQ	W7K0I	K8ODY	W9ILR	W0GNX	HK1QQ	XE1VT
W9CMC		W8RQ	W1GF	WB2LZF/	WA4BMC	W4WSF	K5YWX/0	K7KPM	K8OHS	W9IRH	K0GSV	HK3LX	XE2DS/
K9EAB	1000	K8TNE	W1GKJ	W90IJ	K4BVD	K4WVX/	W5ZBC	K7MPQ	W8OQV	W9IXF	K0GVA	HK3RQ	XE2DPS
K9UTI	K1CXP/	W8UMR	W1HGT	WB2MFX	W4BWR	HR3JP	WA6AJF	K7NHG	K8PFX	W9JCV	W0GWT	HK3VV	YV5ACP
W0JWD	W1BHV	W8UPH	W1HOY	K2MYW	K4CDZ	K4ZA/	WA6ATY	W7NNF	K8QYG	W9JQE	W0GYM	HK7ZT	ZL1TB
W0KZZ	W1FPS	K8VSL	W1HTE	K2PBU	K4CEF	K6ZA	W6BIL	W7NPV	W8RCJ/	W9JWJ	W0HAO	HV1CN	ZL4CK
W0MCX	W1GF	K8VZW	K1IHK	K2PFC	WA4CLR	K4ZCP	K6BX	W70EB	W1BUS	W9KA	W0HSC	I1ER	SWL
W0VFE	W1GKJ	W8WT	K1IJU	WA2PMW	W4CZ/	K4ZNK	K6CJF	K7QXG	W8RQ	K9KCQ	K0HUU	IT1AGA	VE2-8679
VE3-9301	WA2IMT	W8WUT	K1INO	WA2PWI	W1CV	K5ABE	WA6CRN	W7RZY	W8RSW	WA9KHW	W0IDM	KH6BIH	VE3-7554
	W2JWK	K8YGU	K1KCN	WA2QMF	W4DPN	W5AKR	W6DIX	K7SQD	W8SH	W9KSE	K0IDV	KH6BLX	VE3-9301
1500	WB2LZF/	WA9AJF	K1KPS	WA2RMP	WN4EBE	WA5ALB	WA6DWH	W7TDC	K8TBR	W9LKB	K0IHK	KH6DKA	VE3-11367
W1GF	W90IJ	K9AZX	W1KVA	WA2RUB	W4EEE	W5ANE	WA6ECF	W7ULC	K8TNE	K9LLX	W0IJN	KL7MF	W2-6893
W2JWK	K2PBU	W9CMC	K1LBH	WA2SAZ	W4EJP	W5AWT	K6EIE	W7VJI	W8UMR	W9LXW	K0IOZ	KP4CC	WPE2HEA
K3LXN	K2PFC	K9EAB	K1MBM	W2SCP	W4EJQ	K5BQS/	W6ETR	W7WLL	W8UPH	K9MAU	W0IUB	KZ5BX/	WPE3EBF
K4BAI	WA2PWI	W9HAS/	W1MRQ/	W2SNI	K4FF	W5KPO	W6FGJ	W7ZKL	W8VII	K9MMA	K0JPL	W0BXMW5-10353	
K4ISE	WA2QMF	K4KWQ	W1MX	K2UKQ	WA4FJF	WA5BSV	WA6GWM	WA8AJZ	K8VSL	W9NZS	W0JWD	KZ5JW	WPE9ETT
WA4MGC	K3HNP	W9HGP	K1NJE	K2UPD	WA4GAY	K5BTM	K6HOR	W8AL	K8VZW	K9PZD	W0KZZ	LA2MA	W0-10646

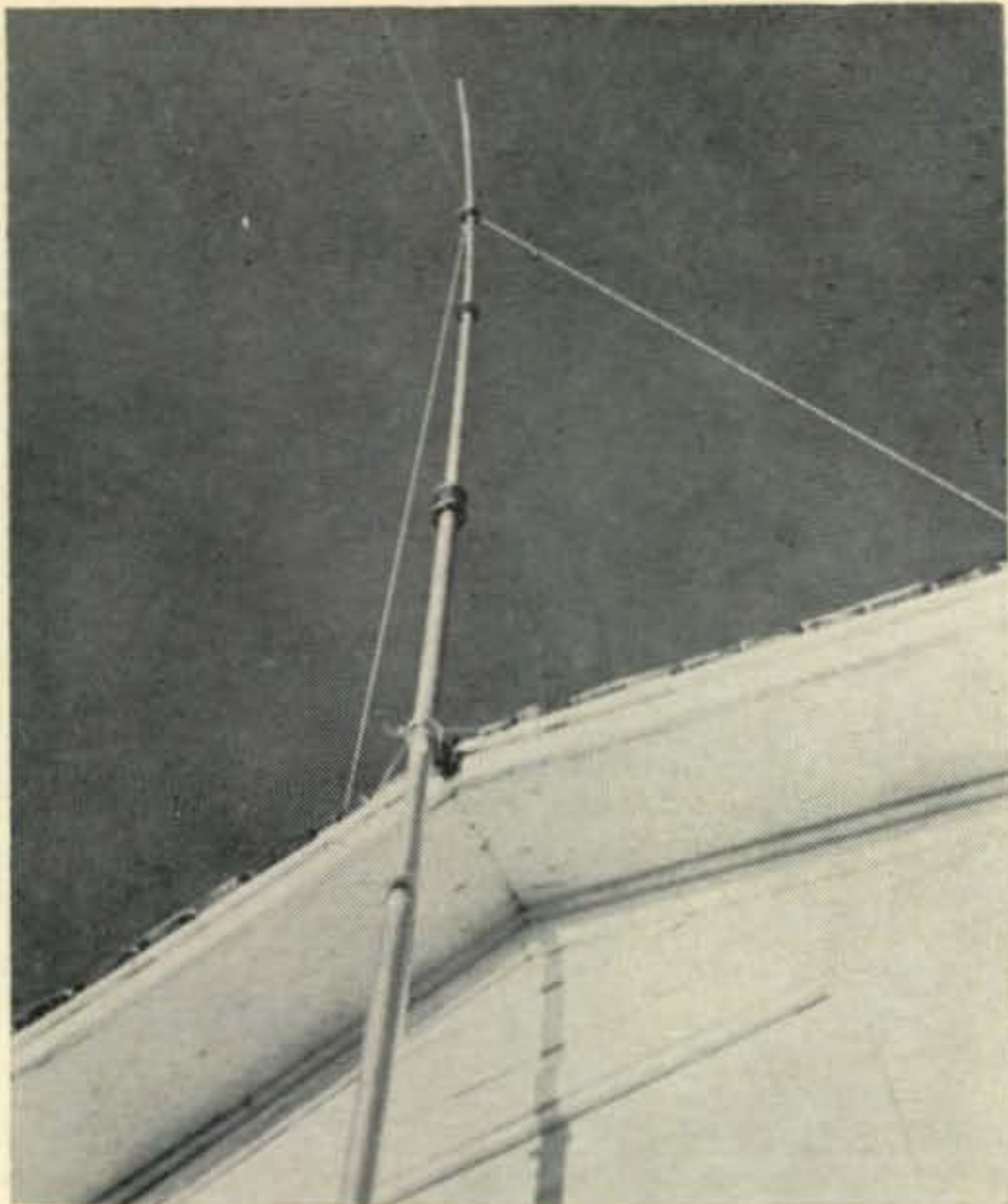

View of the half wave 40 meter vertical antenna. A standoff insulator on the edge of the roof and three nylon ropes provide adequate support.

Construction

Technically the antenna has several good advantages, low angle radiation, easy matching, *etc.* Construction wise we decided on a fifty foot telescoping TV mast, utilizing TV mast extension to complete the necessary 64 feet.

First the mast was placed on the ground and the 64 feet measured correctly. Each section was then marked so that the same measurements would hold true once we stood the assembly in the air. All top sections were pulled completely out, and the bottom two sections were used for adjusting to frequency. Since each section clamps together, we decided to solder a piece of braided wire at each joint to give a good electrical contact.

With the $\frac{1}{2}$ wave vertical antenna, a matching coil and capacitor is needed as the impedance

A HALF WAVELENGTH VERTICAL

BY W. E. LA FARRA,* W5ZCC


This simple vertical is a half wavelength on forty meters and a quarter wavelength on 75 meters. Its construction is simple and inexpensive.

WITH the sunspot cycle past the minimum and on the upswing, we can all look forward to the high bands opening again, but this time is yet several years away. In the meantime we will have to settle for the bands we have. Of course every ham has his own pet band and pet antenna. We have tried most of the antennas: beer can, ground planes, loaded whips, and we're looking for something different. Since we are lazy, live in a small town, and have a limited budget, we had to give up some of our wilder dreams.

What we had in mind was an antenna that would be inexpensive, easy to construct from locally available material, and would perform when it was finished. For some time now we had been dreaming of a half wave vertical antenna especially for forty meter operation, and without the matching network this antenna would then serve as a quarter wave for seventy-five meters. These two bands have good DX openings at this stage of the sunspot cycle. After thinking about the $\frac{1}{2}$ wave vertical for forty, we just had to give it a try.

*P.O.B. 43, McGehee, Arkansas.

Fig. 1(A)—Test set-up used to select the proper tap position on the coil for 52 ohm coax. (B)—Basic construction of a 40 meter half wave vertical antenna. For 7.2 mc the length is 64' 2" ($\lambda/2 = 462/f_{mc}$).

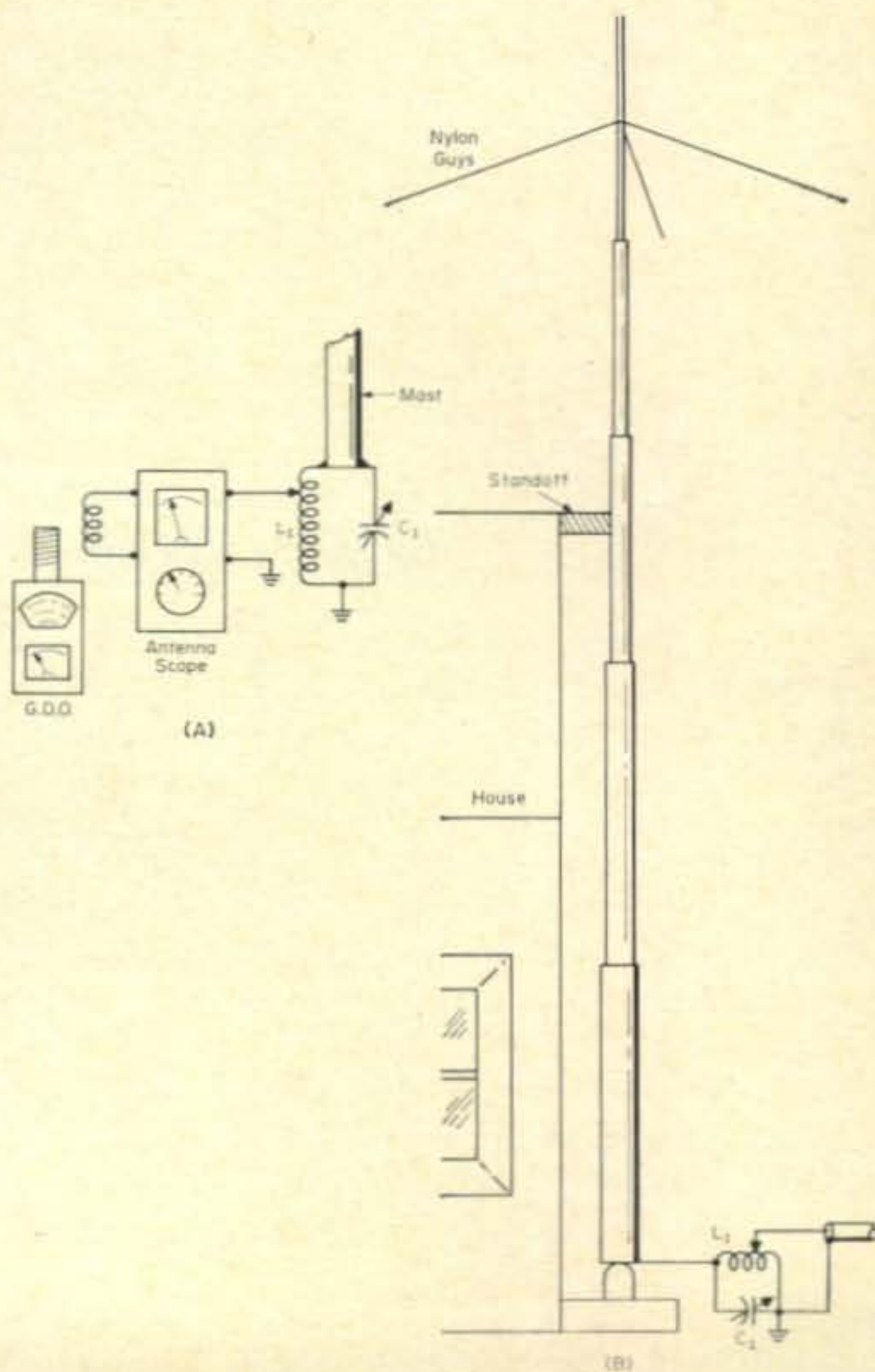



View of the temporary lashup used to match the 40 meter vertical to a 52 ohm coaxial line. The assembly was rebuilt in a plastic refrigerator container for waterproofing. For 75 meter operation the antenna can be fed directly by coax.

at the end of a $\frac{1}{2}$ wave antenna is approximately 2500 ohms. The parallel tuned circuit meets this requirement and allowed us to tap up on the coil to find a 52 ohm matching point for a low v.s.w.r. For 75 meters no tuned circuit is used but a ground system will be needed. Better still, use quarter wave radials extending out from the base. This can be fed directly by 52 ohm coaxial cable. The quarter wave radials for 75 meter operation will also improve the half wave forty meter antenna as it offers an established ground.

Guy wire became a problem. We felt that few were needed since the antenna was supported at the house and didn't offer, in itself, much of a wind catcher nor was it supporting anything. Wire guides are OK if you break them up with insulators every few feet. We decided on using rather heavy nylon fishing net cord. This was not too expensive, 500 feet for \$2.00, and would eliminate the insulating problem.

For the matching coil about anything that will hit the frequency, 7.2 mc, and handle the power will do. We used a 250 mmf variable capacitor from the junk box and an old coil

form. A 250 mmf variable and a 3" length of Air Dux #2004 ($2\frac{1}{2}$ " dia., 4 t.p.i., 5 microhenries) will do very nicely. You can use a neon bulb to resonant this tank if a grid dip meter is not available. This assembly was later placed in a plastic refrigerator box to seal it from moisture.

Tune-up

For test purposes and to allow us to try our set-up we stood the antenna on a board, insulating the bottom with a power company standoff. This standoff had a hole in it, and the mast has a hole in it too. By placing a bolt or nail through the mast hole, with it down over the insulator, you have a nice seat for the antenna. Using a step ladder and adjusting the last two sections, we were able to set the mast to our selected frequency of 7.25 mc.

Utilizing an antenna scope and grid dip meter¹ (fig. 1(A)) we started up from the bottom of the coil until a 52 ohm point was found. If the grid dip meter and antenna scope are not obtainable, these measurements can be made with a standing wave meter which most hams have or can borrow for the short time needed. The idea here is to feed 7.2 mc at low power, into the antenna. Then find the lowest v.s.w.r. by tapping the coil and adjusting the vertical section. Repeat the procedure until the v.s.w.r. is brought down to 1:1.

Results

On the air tests with the antenna has generated lots of excitement. First off, everyone just doesn't have a half wave job, and the result proved that the antenna was performing. On seventy five the antenna does a terrific job of working mobiles in the vicinity. Our cost was less than 20 dollars for our antenna and even if every part has to be purchased, the price shouldn't run over \$25.00. ■

¹Novice, CQ March 1960, p. 70.

Geiser, D. T. "The Instrument Deluxe," CQ, October 1962, p. 47.


New Amateur Product

Seiko Time Corporation

THIS new, 17-jewel, self-winding, automatic calendar watch from Seiko, Official Timer of the 1964 World Olympics for all events, tells the time instantly on five continents simultaneously at just a glance, requires no mental arithmetic or reference to charts. It gives the time in the world's major cities with the same ease as local time, including automatic color indication of whether time is night (black) or day (blue).


The automatic date-calendar has Seiko's patented Instant Reset, allowing the date to be moved instantly back or forward with just a click of the crown, without turning through 24-hour cycles.

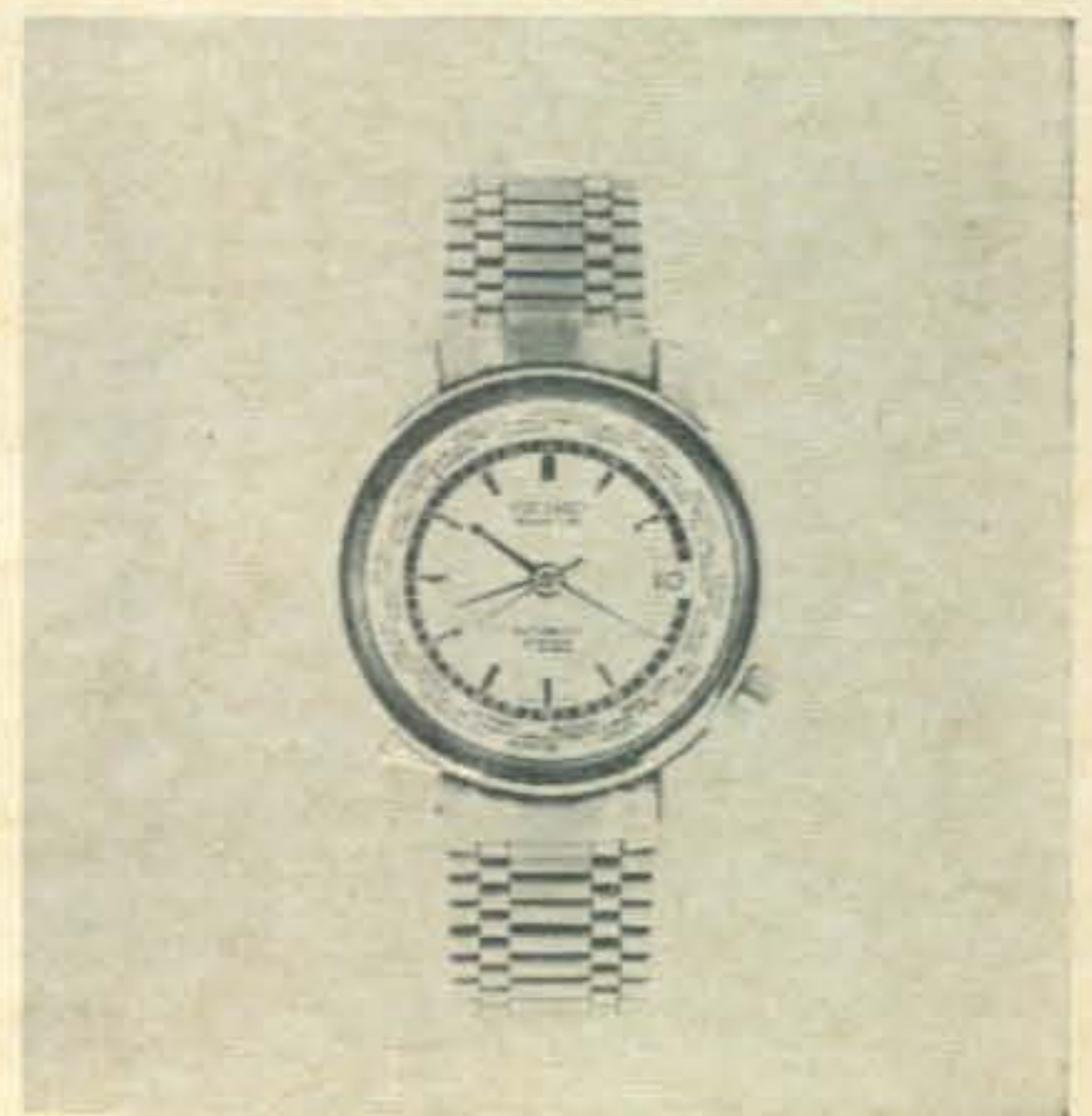Waterproof and shock-resistant, price \$55.00. For further information write to Seiko Time Corporation, 9 Rockefeller Plaza, New York, New York 10020, or circle 65 on page 106.



A Quiet with the

Weekend JET-SET

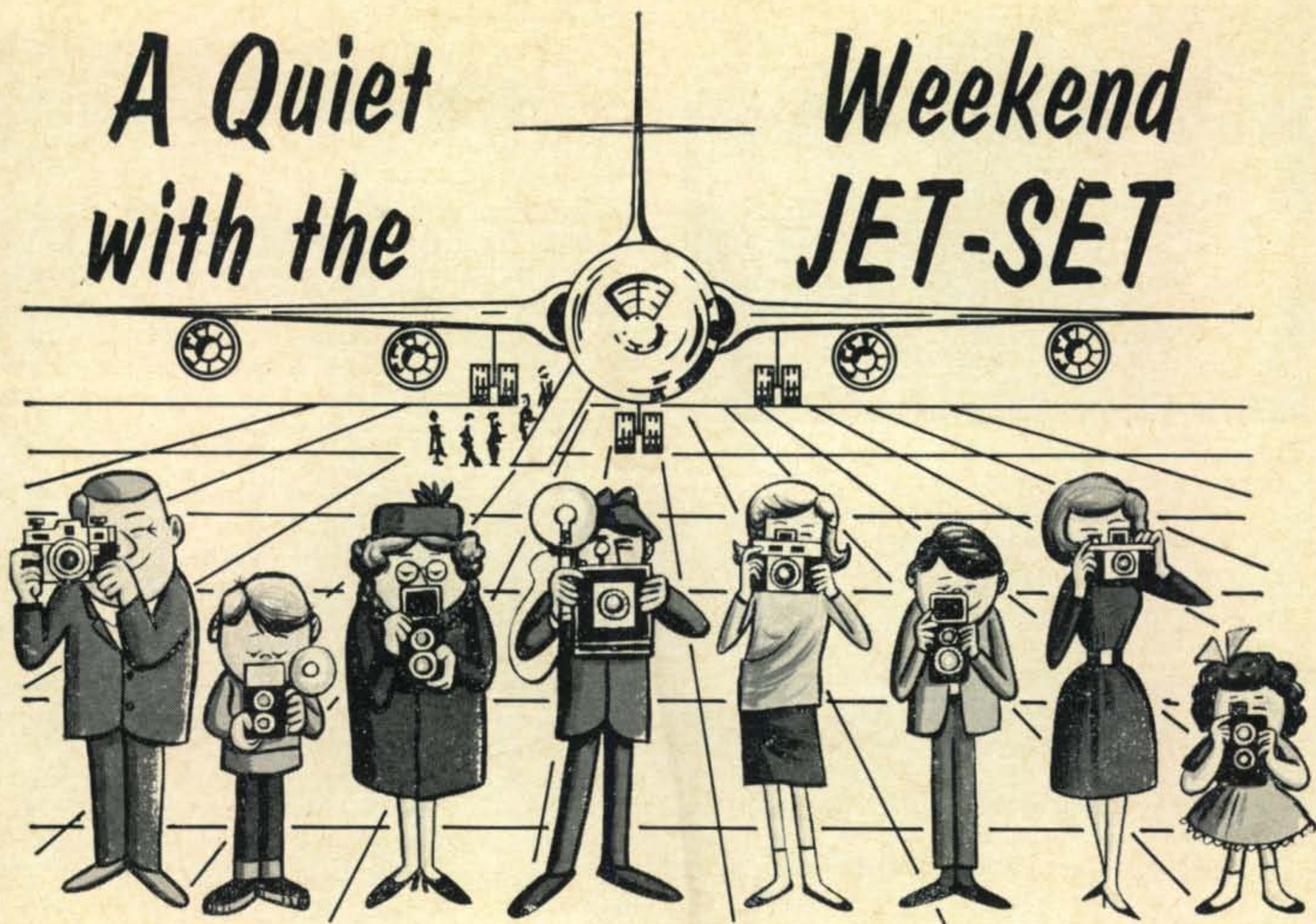

BY SYLVIA MARGOLIS*

So what's a gorgeous doll like you doing in a crummy joint like this?"

Thus graciously did John Gayer, HB9AEQ, Honorary President of the International Amateur Radio Club, greet me when we first met at the Communications Exhibition in London last October.

He had come to pay respects from one to another international amateur radio organization. Ours is the Amateur Radio Mobile Society, whose monthly publication, *Mobile News*, my husband and I edit, and at whose Exhibition booth I was noisily flogging myself to death.

For four, twelve-hour days a deranged few volunteers staff the ARMS booth. Using the entirely new approach that *radio amateurs are human, too*, we sell membership in our unique Society, sell specialist supplies, exchange gossip and information on mobile operation and generally embellish the occasion. Come to the Exhibition, find the noisiest booth and you can buy Me and My Girls a drink!

"If you like doing this kind of thing," said John, "and will pay your own expenses and work for nothing—such a nut we can use. Come to Geneva for our Third Convention in September."

I said yes because it was easier and John is a hell of a nice guy.

It was to be a real, restful vacation, away from the thunder of tiny feet and an ever-loving husband, that break in routine that every doctor would prescribe for every woman, particularly

if she is the wife of G3NMR, the mother of G3UML and of a 10-year-old avid short-wave-listener, too. So there's not much else happens in our home except amateur radio.

Geneva is a fine city, with splendid historical buildings, statues, parks, magnificent shopping, an enchanted lake, the highest fountain in Europe and, invisible most of the time, Europe's highest mountain, Mont Blanc.

Or so they tell me. I saw two buildings in Geneva, both circa 1960. The one with the flags outside is the I.T.U. Building. The one with the Cadillacs and Rolls Royces outside is the Intercontinental Hotel.

From London I travelled night-flight, because it's 50% cheaper and a girl doesn't make much money writing for *CQ*. My husband said he would pay the fare if I brought home one of



Eric, G3IIR, and Bill, W6SAI, explain amateur radio to African delegates.

*95 Collinwood Gardens, Clayhall, Excid, Essex, Eng.



Plenipotentiary delegates are introduced to Harold Megibow, K2HLB, host at the reception given in their honor in Geneva's Intercontinental Hotel on the evening of the first day of the Convention.

the top raffle prizes. Wise guy!

Night-flight brings you in at 3:30 A.M. Yet at 12 noon, bleary but eager, I reported for duty at the I.T.U. Building. I was greeted with joyous cries that should have warned me. John and his staff were still busy with their own I.T.U. work but, goody-goody, here was the first of their voluntary workers walking right into the trap.

To arrange a Convention as ambitious as this involves not only imagination and verve and genius. It means hundreds of hours of sheer, administrative slog. I saw and did enough to convince me of what must already have been done.

They found me some clerical work to keep me occupied and out of the way. When, at 6 P.M., I staggered up off my knees, Vera Jackson, John's super-efficient *British* secretary, the administrative genius behind the Convention, said we must go home early, have a quiet dinner and an early night. Tomorrow would be rather a difficult day. To hell with British understatement. Tomorrow was murder.

We started at 9. For ten hours we handled "Registration." Each arrival had to be welcomed and identified and his documents produced. We explained that he would receive one free raffle ticket, that more were available at 25¢ each, which was a good buy, because the manufacturers had presented an SR-500 and an HX-50A as just two of the prizes. Then he must be docketed, ticketed, indexed, cross-indexed, cossetted, labelled, tabulated, soothed and charmed. All this in four languages and five currencies.

Besides, we had to be able to inform and advise on hotel bookings, bus routes, exchange rates, excise restrictions, licensing regulations (the Swiss P.T.T. issued temporary HBØ licences on the spot), where to buy a sweater, a watch or a camera, which hairdresser would still take bookings, was there a doctor in the house and what would be the local time in Milwaukee. There must be an easier way of spending a Friday.

The first of the Convention's three lavish Receptions, at the Intercontinental Hotel, was attended by a large group of delegates from the I.T.U. Plenipotentiary Conference. They were

transported from Montreux to Geneva in buses loaned by the Swiss P.T.T. The host was K2HLB, Dr. Harold Megibow.

The delegates mingled with the radio amateurs, a splendid token for amateur-professional-diplomatic relations. I wore a "little black" and the gorgeous perfume that dear George Jacobs, W3ASK, had brought me when he visited us in London in March. This was a plushy set-up, all diamonds and mink and Diorama and mohair suits and Corona-Coronas and hand-kissing and Chivas Regal. The women had really gone to town. Nothing flatters an occasion more, nor makes it zing, than women who have taken the trouble to look glamorous.

The place glittered with personalities—John Huntoon, W1LVQ; Stu Meyer, W2GHK; Neal Latorraca, WB2NAD; Emil Savundra, G3SDN; George Pearson, G3AWZ; Dick Van Breen, PAØFX; and the Presidents of several National Societies. As Mr. Gayer's Young Ladies, we were expected to act as hostesses, keep things running smoothly, interpret, circulate, introduce. Afterwards we were taken to dinner by some of the delegates. Any gentleman foolish enough to offer food to the Staff was on a bad deal, for we needed endless calories. I only stopped eating that night because by then, I needed sleep more than food.

Now I had to make a momentous decision. Two cars were available to ferry us home. One was a superb 1935 Bentley, owned by Bill Boyle, VK9WB; the other was John's Mercedes 220SE. Such problems every girl should have.

At 8 A.M. next morning we opened shop at the Intercontinental. The routine was the same, but twice as frantic—the decor more luxurious. Whilst the opening ceremonial was performed by Gerald Gross, W3GG, Secretary-General of the I.T.U., Vera and I watched from the back of the hall, impressed despite ourselves at this complex project which she had designed and I had helped to execute.

Now the first copies arrived from the printer of the IARC's 1965 glossy publication, *Interadio*. Vera gave us the firmest orders.

"Supplies are strictly limited. One each *only*. Tick off the callsign on the list as they take their copy."



Perhaps the most popular section of the reception area—Heinz Oswald, (HB9ZO), a Swiss PTT official from Berne, issues on-the-spot temporary mobile licenses.

At noon they poured all over us and began to snatch the books. No time to check, count or tick—chaos threatened. Then I remembered what we did in England during the War when a shop got a supply of fresh oranges. But how would this extrovert, suave, masculine horde react? I gambled.

"PUT THOSE BOOKS BACK IN THE PILE AT ONCE. PLEASE FORM AN ORDERLY QUEUE!"

I have a very loud and clear voice and the reputation for being a bitch-on-wheels. There was silence. Then quietly, meekly, they shuffled into a beautiful, straight, obedient, patient British queue. Choking with laughter, we issued the books like army boots—callsign, check, tick, hand over the book, next please!

At the Convention Banquet, that night at the Intercontinental, we ate exquisite fresh salmon, roast beef and ice cream. I sat with the Megibow's and Harold ordered a magnum of champagne for his party. It made us feel pampered and immensely witty and also bland enough not to mind about winning nothing in the raffle. The winning tickets were drawn by the youngest child of Emil Savundra, the diminutive Jacquie, in a frothy, pink dress, hopping from one foot to another in her excitement.

The elaborate Convention Program included lectures and seminars on radio frequency allocation, s.s.b., antennas, Moonbounce, OSCAR, operating techniques, DX-peditions, equipment and mobile operation. I had heard from several satisfied customers that the presentations had been playing to standing room only, despite the glorious weather. On Sunday, Dorothy Megibow and I strolled in to the discussion on reciprocal licensing. The number of wives in the audience who were completely engrossed by the program proves what a delicate balance of technology and general interest was attained at Geneva.

Now, if anything were required to justify the very existence of the I.A.R.C. Conventions, it was this extraordinary debate. With over 80 countries present, this was the very first time there had been such an authoritative and open discussion of a most important problem. Bob Booth, W3PS, was Chairman and the way the procedure jell-ed was dramatic and enormously constructive. Representatives of each country reported, under Bob's masterly direction, on the situation in their country—what to do to obtain a temporary licence—or how far negotiations with officialdom had progressed. John Gayer pleaded with holders of temporary licences to abide scrupulously by the regulations of the host country and Bob Booth summed up by saying that we have the momentum at last and we must not let it drop; it is up to the individual to seek out his own authorities and to carry on the good work.

Theatrical people speak of the magic something that can spark a performance, no matter how humble or amateur, when the fourth wall between audience and players dissolves and, in the most unlikely circumstances, you know you



A view of the Council Chamber in the ITU building, scene of the Convention technical panels.

are seeing pure Theater. This happened in Geneva on September 19. It was the most significant episode in the whole happy weekend.

But, after tea—these British customs penetrate everywhere—I had a terrifying experience. John Gayer had asked if I would speak on one of the Panels, about mobile operation. "Don't be ridiculous!" I said, "What do I know about anything—except how to run a better club and magazine than you?"

Onto the rostrum of the august, solemn Council Chamber filed Stu Meyer; Gus Browning, W4BPD; top Dx-er George Pearson, G3-AWZ; Past-President of the RSGB Geoff Stone, G3FZL. All important, famous, informed people, who knew what they were talking about. Then John yelled SYLVIA. "You'll be sorry!" I hissed. I missed his instep with my stiletto heel. I'll get him some time, though.

Very smoothly, Stu Meyer shuffled us into a cabaret act. Petrified, I waited my turn. They'd know me for a phony and walk out. I don't know an 813 from a teapot. To me a crystal lattice filter is costume jewelry and a VR6 a new detergent. I don't believe Ohm's Law. Bleak with misery, I stared out of the window opposite. Then a miracle happened. Later John said he had it all arranged specially for the Convention, all part of the IARC service.

Mont Blanc emerged from the surrounding clouds, which it does about three days a year if you are lucky. There it soared, unbelievably high and lovely and aloof. I looked at the mountain and the mountain looked at me and I thought, "Hell! You were there a million years before us and you'll be there a million years after we've gone! All the little things we fight and worry about—reciprocity, QRM, frequency allocations, commercial intruders—it will all be the same in a million years!"

They tell me I spoke very well. ■

* PLEASE include your *
* ZIP code number on *
* all correspondence. *



A group photo taken at a luncheon given by General Francisco Miliani, YV5GA, at the headquarters of the Venezuelan Air Force during the Awards presentation weekend by the Radio Club de Venezolano. From left to right: Cap. Pablo Miliani A. YV5GU; Armando Diaz, YV5AQO; Carlos Julio Martinez, YV5FI; Napoleon Centeno, YV5BNR; Mayor Francisco R. Marin S., YV4BH/5; General of BGDA, Francisco Miliani A. YV5GA; Frank Anzalone, W1WY; Stuart Meyer, W2GHK; Ricardo Sierra, CX2CO; Eduardo Cabrera, YV5AXU; Enrique Berrizbetia, YV5AGA; Rafael Domingo Moros, YV5AVW; Oscar Oyarzabal, YV5ANF; Arturo Rosales, YV5BNV; Miguel Angel Delgado, YV5AIP. The pictures on the wall show the founders of Venezuelan aviation.

PEOPLE AND PLACES



James J. Lawlor (right), waits for Lance Corporal John A. Palcer (center), of Marine Corps Schools, Quantico, Va., amateur radio station W4PFC to complete his transmission before talking shop. Looking on (left) is Corporal Doug Rundel, noncommissioned officer in charge of the station. Mr. Lawlor, executive secretary of the International Eye Bank, Washington, D.C. Division, visited with the station operators, September 2. It was his first meeting with the two Marines since the station's hook-up with the Eye Bank network. (Official Marine Corps Photo by Sgt. Eugene Bender)



The Wilkinsburg Emergency Radio Net helped 3000 Boy Scouts open an historical hiking trail this summer. The Forbes trail, named after General Forbes, was used in 1758 to march an army to what is now Pittsburgh. John Wright, K3AZP, is shown checking a problem of a patrol of Boy Scouts as they hike the Forbes Trail. The Radio Net was used to relay instructions to the hiking column, which at times was 13 miles long.

These are before and after photos of Dick Buckley's, K1ZBT, antenna and tower. The after photo was taken last Dec. after a storm. The ice was three inches thick on the elements and the tower was frozen solid making it impossible to lower for six days. The drooping elements are forty feet long. This is just a reminder for this Dec., to check weather reports and to winterize antenna installations where possible.





BY URB LE JEUNE,* W2DEC

SSB Honor Roll Notes

The return of Singapore to the list added one country to the standings of the following: K1IXG, W1LLF, W2BXA, W2FXN, K2MGE, W2PTM, W2TP, W2VCZ, W2ZX, W3KT, W3MAC, K4HYL, W4OPM, W4RLS, W4SSU, K4TJL, W5KC, K6CYG, K6LGF, W6RKP, W6UOU, W6USG, W6NWE, W6YMV, W6ZJY, W7BTH, W7DLR, K8ONV, W8PQQ, K8RTW, K9EAB, W0QLX, W0QVZ, DL1IN, G2BVN, G2PL, G3AWZ, G3DO, G3HDA, G3NUG, G8KS, GM3JDR, HB9TL, I1AMU, OZ7FG, PZ1AX, SM5UF, VK4FJ, VK5QR, XE1AE, YV5AFF, and 5Z4ERR. CE0XA moves TI2HP back into first place at 305. Musty, W2TP, stands at 304, thanks to LA5CI, Jan Mayen. G3AWZ added PY2BZD/PY0 Trinidad for 303. I1AMU reached 282 with CR4, FY7, VP8HF, VP8GQ, VQ8BFC and 8Z4. CE0AG, CR4, OH0, TU2, VP2D, YU, 7B1 and 8Z4 pushed Vin, W5KC, onto the Honor Roll.

Guest Editorial by K6TZX

The day of the Extra and First Class license is almost upon us. Certainly incentive licensing will do its part in improving our bands and the quality of the signals contained therein. However, let us not lose sight of the fact that the purpose behind the incentive licensing proposals is to improve the radio amateur and his "image" before the world in general and other users of the radio spectrum in particular. This is of primary importance if we are to retain our bands.

But will merely passing a 20 w.p.m. code test and a "tough" written exam save our bands? I think not—to think that it would, will lead to disaster. It will help, but operation in the public

*Box 35, Hazlet, New Jersey 07730.

SSB HONOR ROLL

TI2HP	305	W1LLF	282	G2BVN	264	OZ7FG	234
W0QVZ	304	W6UOU	282	G3DO	260	W4HUE	231
W2BXA	304	W3KT	282	W4RLS	260	W3DJZ	231
K4TJL	304	I1AMU	282	W6WNE	260	W2PTM	231
W2TP	304	G8KS	280	PJ2AA	258	WA2EOQ	229
G3AWZ	303	W2RGV	279	KP4CL	256	W6ZJY	228
W2ZX	302	K4HYL	277	K6LGF	251	W3FWD	226
5Z4ERR	301	DL1IN	276	W1AOL	250	K1SHN	224
W8PQQ	300	HB9TL	276	W4OM	249	K2JFV	223
K2MGE	297	PZ1AX	275	W4PAA	249	K4JEY	221
W3NKM	296	W4SSU	274	W4NJF	248	W2MJ	215
W2FXN	294	W6RKP	274	GM3JDR	247	SM5UF	209
W4OPM	291	K9EAB	274	XE1AE	247	W0QLX	206
W2VCZ	291	W2LV	271	W7CMO	246	W5KC	206
K1IXG	289	G3NUG	270	YV5AFF	240	K6CYG	204
K8RTW	288	K8ONV	270	W7DLR	239	W6USG	204
WA2IZS	285	G2PL	266	K1JMV	236	K0UKN	202
W3MAC	282	W6YMV	265	W3VSU	235	G3HDA	200

interest is the key. And how do we, as DXers, serve the public interest? Not very well I'm afraid. Here we have the tremendous potential, with our huge beams and our kilowatts, to spread the word to the world that we really are "good guys" not "bad guys". And what do we do? We exchange RST's rather than ideas.

I worked a 16-year-old VE7 on 15 meters several weeks ago and had a nice long chat with him, with a few words of advice on how he could improve the note on his DX-60. His card came the other day with this note, "Our QSO certainly raised my opinion of W6s." The price of this goodwill was only half an hour of my time.

I'm not advocating a long rag chew with every DX station worked but when the band is "dead", work a JA, VK, ZL, UA0 and find out what he does for a living, and let him know what you do (besides work DX, hi). I've worked a JA who's very interested in sports car racing, a UA0 who was surprised to learn that not every W6 runs a KW and that not every house in California has a swimming pool, and a VK school teacher who was surprised to learn that few of our high schools teach calculus.

It only takes an hour or two a week. Your country total may not go up as rapidly but at least it will help to assure that those "countries" will be there a while longer.

When was the last time you had a QSO instead of a qso? (Thanks NCDXC).

Here and There

FR7 Reunion Island: Guy, FR7ZD, can be found at 1230 GMT on Saturdays on 20 meter s.s.b. (Tnx LIDXA).

GC Guernsey: GC8HT, Dick, looking for W/K from 1400 GMT on Wednesdays on 14,242 kc and on Sundays between 1400 and 1500 GMT on or near 14,285 kc. If you want QSLs direct send something to help defray expense, otherwise via bureau. (Tnx WGDXC).

KG6I Marcus: Chuck, KG6IF, on 14,270, at 0200 GMT. Also heard on 14,200 and 14,245. The new quad is putting out fair to good signals to the East Coast and Chuck promises to be on as much as possible. He will be there for about six more months. QSL W6ANB. (Tnx LIDXA).

VK9 Papua Territory: VK9WE 14,035-40 kc 0530-0800 GMT daily and 1200-1300 GMT week-



Jack, 9G1FK, looks like he has the conveniences of home in his Accra, Ghana shack. (Tnx K2DGI).

The following certificates were issued between the period from September 6th, 1965 to and including October 5th, 1965:

CW-PHONE WAZ			682	SM3CJD	Carl Otto Ragne
2207	K2ZKU	Edward Gaudet	683	SM4CHM	Torbjorn Landstrom
2208	OK1DJ	Stanislav Novak	684	VE3CWE	Walter C. Kimball
2209	K1IGO	Robert F. Herrick	685	W5JKJ	Stan Kuhl
2210	VE6ABP	Margaret Tettelaar	686	SM6CMU	Ingemar Olsson
ALL PHONE WAZ			PHONE WPX		
316	OE1NY	Helmuth Nikischer	123	W5NXF	Norman L. Maguire
TWO-WAY SSB WAZ			124	G3MCN	Harry James
342	VE6ABP	Margaret Tettelaar	SSB WPX		
343	W4DLG	Rudolph B. Spivey	218	W5LEF	Willie E. Petty
344	OE1SF	Frank Friedl	100 TWO-WAY SSB		
345	K9LUI	Verna D. Franz	470	GW3NWV	Robert C. Holt
346	OA4PD	Vitaly Franco	471	W7CMO	Norman S. Moberg
CW WPX			200 TWO-WAY SSB		
680	K3GKF	M. F. Nelson	131	G3WW	R. F. G. Thurlow
681	SP6ALL	Seweryn Wojtusiak			

ends when band open. All W/K QSLs go via WA6GLD (Jerry Hagan, 5031 Arroway Avenue, Covina, Calif. 91723) whose QTH is not correct in the *Callbook*. (Tnx WGDXC).

VP5 Grand Turk Island: VP5AR, Tony, will be active for 18 months at present using temporary rig with mobile whip antenna but is awaiting his "S-line" and TA-33 beam. (Tnx WGDXC).

VR6 Pitcairn Island: Tom, VR6TC, active most Mondays on 15 meters at 2200 GMT on 21,250 (a.m.) working W's on 21,300 then 21,255. Also 21,065 c.w. QSL W4TAJ.

4W1 Yemen: 4W1G and 4W1I QSLs are now being handled by Harry Charvat, K9BPO, 207 Mandel Lane, Prospect Heights, Illinois, who has the logs from both these stations and is now having cards printed. Harry requests s.a.s.e. and GMT. He will probably be handling QSLs for other 4W1 stations as they are activated. (Tnx K2MGW).

ET Ethiopia: The following letter is from Jim, the new president of ET3USA. "I am very happy to announce that Kagnew Station Amateur Radio Club, ET3USA, will be using a special call sign 9F3USA for the entire month of December. I would like to take time out now to give my thanks to K7UCH, W7TDK and K1QHP/FL8-AK as our QSL managers. They have done a job which mere words cannot describe.

"I am very sorry to say that one of our best members has left our club, Albert L. Kemmesies, K1QHP/FL8AK. When he arrived here over a year ago, our club was barely making a go of things. After his arrival, he took over as President and has made the club what it is today—a well-organized, world wide known club which can now hold its head up with pride of a job well done, knowing when Al leaves here that he has left something better behind and a part of himself.

"Now that I have taken over the job as President, I will continue to carry out along in his footsteps. If I can do just half the job Al has done, this club will remain among the top in

the world, with a QSL program which is hard to beat.

"Now to change the subject a little bit. I have had many people ask how come they don't hear ET3USA on 80, 75 and 10 meters. Well, I guess one of the reasons is the lack of antennas. The other being very poor band conditions here. I for one would like to see these bands being used because I know there are many hams looking for rare DX stations on these bands and I will do my best to see that ET3USA will be among these DX stations on 80, 75 and 10 meters.

"Also, at this time I would like to say that if there are any hams who would like a special schedule with ET3USA to feel free to write me or any of the other operators at any time on this matter or any other matter. All the members of the club are willing and able to set up any kind of QSO with you. I would like to mention that we do not have any equipment for 6 and 2 meters. The address for the club is ET3USA, OP: Jim, APO, New York 09843.

"Another thing I would like to bring up is the discourtesy which some hams have shown us in the past. Any ham who causes us needless QRM, for example, calling on frequency during a QSO, or anything along that line will have his call taken and posted next to the equipment, and at no time in the future will a QSO be made with that operator. This may sound mean or harsh, but the way I look at it, that one LID has caused us to lose five or more QSOs with other hams who had the courtesy to wait.

"In closing I would like to say that I will try my best to be the ideal ham by bringing good DX from Ethiopia and that the WPX hunters will not be disappointed with our new prefixes of 9E3 and 9F3."

160 Meter DX Tests

The annual trans-Atlantic and World-Wide DX Tests on 160 meters will be held as follows: Dec. 5 and 19; Jan. 2 and 16; Feb. 6 and 20.



Radio Club Venezolano Award

A special series of 160 meter tests will be held also, for "First Timers" as follows:

Europe and Africa—Dec. 19 and Feb. 6.

W/VE/North America—Jan. 9 and Mar. 7.

All those in these areas who have previously worked 160 meter DX will please QRT and let the boys who have never worked real DX on 160 enjoy a clear field, without QRM from the "big boys" and regulars. See last month's column for full details.

DX Awards

Korean Amateur Radio League

The Korean Amateur Radio League has established the HM Award (HMA) and All Seoul Award (ASA), available to any licensed amateur. The HMA is issued in five classes for Korean contacts as follows: HMA-K—Five HM's; HMA-O—Ten HM's; HMA-R—Twenty HM's; HMA-E—Thirty HM's; HMA-A—50 HM's.

The ASA requires 9 confirmed QSO's with HM stations in all 9 districts of Seoul, the capital city of South Korea. The 9 districts and their Korea Districts Number (KDN) appear on HM QSL's issued after May 1, 1965 and are as follows:

A-11 Chongrokoo	A-16 Seodaemoonkoo
A-12 Choongkoo	A-17 Mapokoo
A-13 Seongdongkoo	A-18 Yongsankoo
A-14 Dongdaemoonkoo	A-19 Yongdungpokoo
A-15 Seongbookkoo	

All contacts must have been made after July 1, 1959 with any HM station with the following exceptions: 1—Ex-HL9TA (now HM0HQ) in 1959 and 1960 counts



The presentation of the winner's trophy during the first "Foxhunt" ever held in Hong Kong. Left to right VS6BJ and VS6FF winning team, VS6FO and VS6FJ winners up and VS6DS chairman.



Joe, LU9DM, is very active on all bands from this neat station.

as HM0HQ. 2—HM0HL operated by HL9 in 1964 is not effective.

Any single band and/or single mode operation will be noted on the certificate on request. A minimum report of R3 T8 is required. QSL's or GCR and full log data with 10 IRC's should be sent to: KARL, Central Box 162, Seoul, Korea.

Radio Club Venezolano

Two new awards are available to amateurs working 200 countries (DX-200 Award) or 300 countries (DX-300 Award). Endorsements are available for the DX-200 for 225, 250 and 275 countries. ARRL Countries list is used, and the certificates are issued in three classes: 1. General (mixed); 2. All Phone; and 3. 2 Way SSB Only.

Submit ARRL form "CD-11" indicating your country total or indicate issue and page in QST showing your country total. This only applies for classes 1 and 2 above.

For class 3, 2 Way SSB, submit the equivalent form (or photocopy) issued by CQ or indicate issue and page in CQ showing your 2 X SSB total.

In the absence of either of the above, all QSL's must be sent accompanied by list in order of prefix giving full log data. Include sufficient postage for Registered Mail return of cards.

Fee for DX-200 and DX-300 is \$1.00 or 10 IRC's. Compliance with all license restrictions and rules of good sportsmanship are mandatory. Applications should be sent to: Radio Club Venezolano, Comision de DX, P.O. Box 2285, Caracas, Venezuela, S.A.

QTHs and QSL Managers

BY4SK	via W4ECI.
CR7BJ	Box 1, Milange, Mozambique.
DJ0AA	via G2DHV.
DJ0LJ	via G2DHV.
DL5AC	via K8UZA.
EA3OT	via WB6BSJ 1597 Minerva Ave., Anaheim, Calif.
HC6GM	Box 374, Latacunga, Ecuador.
HL9KT	via K8UZA.
HM9AP	via K6ZDL.
KA2AC	via K8UZA.
KG4AA	via W4ORT.
KG6IF	via W6ANB.
KW6EJ	via W2CTN.
MIAC	via K8UZA.
ON5ZQ	via G2DHV.
ON8IR	via G2DHV.
PA9DHV	via G2DHV.
PY2BZD/PY0	W/VE via K2HLB. Others via Box 19094, Sao Paulo, Brazil.
PZ1BK	Box 160, Paramaribo, Surinam.
VP2MN	via W6FET.
VP2SJ	via VE4OX.
VP3MU	via W2FKQ.
VP5AR	via WA8GUA.
VR4CR	Box 619, Honiara, Solomon Islands.
W9WNV/8F3	via W4ECI.
ZC4MO	Club Station, RAF, Troodos, Cyprus.
3A2CK	via G2DHV.
5VZ8CM	via W1YDO.
9A1AC	via K8UZA.

73, Urb



Contest Calendar

BY FRANK ANZALONE,* W1WY

Calendar of Events

November	27-28	CQ WW DX C.W.
December	4-5	OK DX C.W.
December	4-5	New England Party
January	8-9	ARRL VHF SS
January	8-10	Arkansas Party
January	15-16	ARRL CD C.W.
January	22-23	ARRL CD Phone
January	29-30	Louisiana Party
January	29-30	CQ WW 160 DX

OK DX C.W.

Starts: 0000 GMT Sunday, December 5

Ends: 2400 GMT Sunday, December 5

This is a world wide type contest, each contact counts 1 point, but 3 points if it's with a Czech station. The multiplier is determined by the number of prefixes worked. (CQ WPX list)

Certificates are awarded for contest activity and also for the "100 OK" (worked 100 Czech stations) and the "S6S" (worked all continents).

Complete rules in last month's CALENDAR.

Logs go to: Central Radio Club, Post Box 69, Prague 1, Czechoslovakia. Mailing deadline is January 15, 1966.

New England QSO Party

Three operating periods. (EST)

7:00 to 11:00 p.m. Saturday, December 4

7:00 to 11:00 a.m. Sunday, December 5

7:00 to 11:00 p.m. Sunday, December 5

This announcement was received too late to give complete details but rules are same as last year and can be found in the December 1964 issue.

Operation is restricted to stations in New England only.

Logs go to: Connecticut Wireless Ass'n. c/o Pete Chamalian, WIBGD, 111 Buena Vista Road, West Hartford, Conn. 06107. Mailing deadline is January 11, 1966.

Arkansas QSO Party

Starts: 2200 GMT Saturday, January 8

Ends: 0400 GMT Monday, January 10

Complete rules and operating frequencies in next month's CALENDAR.

CQ WW 160 DX

Starts: 0200 GMT Saturday, January 29.

9 p.m. EST Friday, January 28.

Ends: 1400 GMT Sunday, January 30.

9 a.m. EST Sunday, January 30.

It doesn't seem 7 years ago that yours truly got together with Charlie O'Brien, W2EQS and got this "Little Gem" going on 160. But here

we are going into our 7th year and the participation is steadily going up, 1,374 by actual count last year, with 270 logs from 26 countries. Charlie our Contest Chairman has done a wonderful job in making this the "biggest little contest in the world." (See the August issue for a full report on the last one.)

Since the top scores were pretty evenly divided as to U.S. areas and countries, we are leaving the rules alone.

1. This is a c.w. contest *only*. (No c.w. to phone or cross band contacts allowed.)

2. For W/VE/VO stations: Contacts with other W/VE/VO stations, 2 points per QSO. Contacts with all other countries, 10 points per QSO.

3. For all other countries: 2 points per QSO with stations in the same country, 5 points per QSO with stations in other countries; except for contacts with W/VE/VO stations, which will count 10 points.

4. For all stations: A multiplier of one (1) for each state, Canadian province or foreign country worked.

5. Final score: Total QSO points multiplied by the total multiplier.

6. Exchange: RST report plus a progressive contact number starting with 001 for the first contact, followed by your state or province. (It will not be necessary for DX stations to send their country, that's quite obvious.) (i.e.: W1BB/1 579001 Mass.)

7. Disqualifications: Violation of the rules and regulations pertaining to amateur radio in the country of the contestant, or the rules of this contest, or unsportsmanship conduct, or taking credit for duplicate contacts in excess of 3 percent of the total number of contacts made, will be deemed sufficient cause for disqualification.



You can thank Barbara Plomitello for your 1964 certificate. "Bobbie" typed over 700 odd certificates for our last World Wide DX Contest.

*14 Sherwood Road, Stamford, Conn. 06905.

CALENDAR OF EVENTS — SPRING 1966

<i>Established Dates¹</i>		<i>Suggested Dates</i>	
		<i>International²</i>	<i>Domestic³</i>
January	8-9	ARRL VHF SS	—
January	8-9	—	—
*Arkansas Party			
January	15-16	ARRL CD C.W.	—
January	22-23	ARRL CD Phone	—
January	29-30	CQ WW 160 DX	—
February	5-6	—	REF C.W.
February	12-13	ARRL DX Phone	—
February	12-13	—	—
*N.Y.C.-L.I. Party			
February	19-20	QCWA Party	—
February	19-20	YL/OM Phone	—
February	26-27	ARRL DX C.W.	—
March	5-6	YL/OM C.W.	REF Phone
March	12-13	ARRL DX Phone	—
March	19-20	RSGB BERU	—
March	26-27	ARRL DX C.W.	—
April	2-3	—	SP DX C.W.
April	9-10	(EASTER)	—
April	16-17	CQWW DX SSB	—
April	16-17	ARRL CD C.W.	—
April	23-24	ARRL CD Phone	PACC CW/Phone
April 30-May 1	1	CQ Spring VHF	*Helvetia 22
May	7-8	—	USSR DX
May	14-15	—	OZ CCA C.W.
May	21-22	—	Bermuda Party
May	21-22	—	*YL Int. SSB
May	28-29	—	OZ CCA Phone
June	4-5	CHC/FHC/HTH Party	—
June	4-5	National Field Day	—
June	11-12	ARRL VHF Party	Bermuda Party
June	18-19	—	—
June	25-26	ARRL Field Day	—
July	2-3	Venezuelan Contest	—

Hawaii and Alaska will be considered as "foreign countries" for QSO and multiplier credit. The District of Columbia counts same as Maryland. And don't forget, VE1 is divided into three provinces, Nova Scotia, New Brunswick and Prince Edward Island.

Certificates to the Top station in each State, Canadian province and foreign country. If participation warrants 2nd and 3rd place awards may be made.

Log sheets and United States Operating Regulations for 160 may be obtained from CQ upon request. A large s.a.s.e. please.

Mailing deadline for your logs is Feb. 28th and they go to: CQ, Att: 160 Contest, 14 Vandeventer Ave., Port Washington, L.I., N.Y.

Louisiana QSO Party

Starts: 1400 GMT Saturday, January 29.

Ends: 2200 GMT Sunday, January 30.

This is the first annual Louisiana QSO Party sponsored by the Lafayette Amateur Radio Club.

Use all bands and modes, c.w. and phone, a.m. and s.s.b. being classified as phone.

Exchange: QSO number, RS/RST and QTH. Parishes for Louisiana stations, state, provinces and country for all others.

Scoring: Each contact counts 1 point. The same station can be worked and counted for QSO points on each band and each mode. Louisiana stations can also work in-state stations for QSO points.

¹The established dates above are those that have already been officially announced or established by previous activity in past years.

²The International suggested dates are based on previous years and with some slight changes to avoid past conflicts.

³Most of the State Parties also follow previous dates. Trying to avoid other activities is a rather difficult problem.

*Activities that have already been announced.

Final Score: Total QSO points multiplied by number of different Louisiana parishes worked. Louisiana stations will use states, Canadian provinces and countries as their multiplier.

Frequencies: Suggested spots are: 3600, 3910, 7100, 7230, 14100, 14300, 21100, 21400, 28100 and 28700 kc.

Log Data: Date/time in GMT, station worked exchange sent and received, band, mode and score.

Awards: Certificates to the Top score in each State, call area in Canada and each country. In Louisiana certificates will be issued to the 1st, 2nd and 3rd place winners. (Note: A minimum score of 50 points is required to be eligible for an award.)

Logs must be postmarked no later than February 28th and they go to: Louisiana QSO Party, c/o Bill Allen, W5NQR, 155 Karen Drive, Lafayette, Louisiana, 70503.

Editor's Notes

At this writing we are anticipating the coming World Wide DX Contest. And by the time you read this they will probably be all over and once again we on the committee will have months of hard work ahead of us. By the way requests for log forms have been rolling in this one promises to be the biggest year yet. Anticipating this mountainous task we are adding two additional members to our working committee, Fred Capossela, W2IWC and Andrew Bodony, WB2CKS. Freddie is an avid contest man with years of experience behind him, Andy not only has years of experience but is also an authority on European contest procedures. Both should be of great assistance to us and perhaps lighten the load a bit this year.

[Continued on page 96]



Propagation

BY GEORGE JACOBS,* W3ASK

SOME 10 meter DX openings are forecast for December, generally to southern and tropical areas, during the daylight hours. Good 15 meter DX openings are expected to most areas of the world during the daylight hours, with signals often exceptionally strong. Twenty meters is expected to open for DX shortly after sunrise, and remain open to one area of the world or another through the daylight hours and into the early evening. When propagation conditions are better than normal, 20 meters is likely to remain open to southern and tropical areas during the hours of darkness as well.

With static levels at seasonally low values in the northern hemisphere, and the hours of darkness at a maximum, a considerable improvement in DX propagation conditions is predicted for 40, 80 and 160 meters during December. Forty meters is expected to open for DX during the early afternoon hours, and remain open to one area of the world or another during the hours of darkness and the early daylight hours. Frequent 80 meter openings are forecast to many areas of the world during the hours of darkness. Some DX openings are also expected on 160 meters during the hours of darkness, with signals peaking when it is dark at one end of a path, and sunset or sunrise at the other.

160 Meter Tests

The following information has been received from W1BB concerning the annual 160 meter trans-Atlantic and Worldwide DX Tests:

"Again, reminiscent and symbolic of the first pioneering trans-Atlantic radio crossings by Marconi, Deloy, Schnell, Reinartz and Godley between 1901 and 1924, and continuing a yearly operating activity on 160 meters established in 1932 and held every year since (except during World War II), the Annual Trans-Atlantic and Worldwide "Top-Band" DX Tests will be held between 0500-0730 GMT on the following Sundays: December 5 and 19, January 2 and 15, and February 6 and 20. During these Test periods, special efforts will be made to establish new records on 160 meters. W/VE stations should call "CQ DX Test" the first five minutes of the hour, and alternate periods thereafter, listening between periods. DX stations should call "CQ DX Test" during the 2nd, 4th, 6th, etc. five minute period, listening between periods.

*11307 Clara Street, Silver Spring, Md. 20902.

LAST MINUTE FORECAST

Day-to-Day Conditions and Quality for December

Days	Forecast Rating & Quality			
	(4)	(3)	(2)	(1)
Above Normal: 3, 13-14, 28-29	A	A-B	B-C	C
Normal: 1-2, 4-6, 11-12, 15, 17-18, 21, 25-27, 30-31	A-B	B-C	C-D	D-E
Below Normal: 7, 9-10, 16, 19-20, 22, 24	C	C-D	D	E
Disturbed: 8, 23	D	D-E	E	E

HOW TO USE THESE CHARTS

The following is an explanation of the symbols shown above, and instructions for the use of the CQ propagation predictions:

1—Enter Propagation Charts on following pages under appropriate band and distance or geographical area columns. Read predicted times of band openings at intersection of both columns.

2—Following each predicted time of band opening is a forecast rating which indicates the relative number of days the band is expected to open during each month of the forecast period. The higher the rating, the more frequent the opening, as follows: (4) band open more than 22 days each month; (3) between 14 and 22 days; (2) between 8 and 13 days; (1) less than 7 days.

3—With the forecast rating noted above, start with the numbers in parentheses at the top of the "Last Minute Forecast" appearing above. Read down the table for a day-to-day forecast of propagation conditions in terms of Above Normal (WWV rating higher than 6); Normal (WWV rating 5-6); Below Normal (WWV rating 4); Disturbed (WWV rating reception conditions (signal quality, noise and less than 4). The letter symbols (A-E) describe fading levels) expected for each day of the month and have the following meanings: A—excellent opening with strong, steady signals; B—good opening, moderately strong signals, little fading and noise; C—fair opening, signals fluctuating between moderately strong and weak; D—poor opening, signals generally weak and considerable fading and noise; E—poor opening, or none at all.

4—This month's DX Propagation Charts are based upon a transmitter power of 250 watts c.w.; 500 watts s.s.b., or 1000 watts d.s.b. into a dipole antenna a quarter-wave above ground on 160 and 80 meters, a half-wave above ground on 40 and 20 meters, and a wave-length above ground on 15 and 10 meters. For each 10 db gain above these reference levels, reception quality shown in the "Last Minute Forecast" will improve by one level; for each 10 db loss, reception will become poorer by one level.

5—Local Standard Time for these predictions is based on the 24-hour system.

6—The Eastern USA chart can be used in the 1, 2, 3, 4, 8, KP4, KG4 and KV4 amateur call areas; The Central USA Chart in the 5, 9 and 0 areas, and the Western USA Chart in the 6 and 7 areas. The Charts are valid through Dec. 31, 1965, and are prepared from basic propaganda data published monthly by the Central Radio Propagation Laboratory of the National Bureau of Standards, Boulder, Colorado.

As far as possible, stations participating in the Test transmissions should use the following frequency plan; Eastern W and VE stations, 1800-1825 kc; western W and VE stations, 1975-2000 kc; European stations, 1825-1830 kc; VK and ZL stations, 1800-1860 kc; Japanese stations, 1880 kc; African stations 1800-1825 kc. These Trans-Atlantic Tests are exciting, and all radio amateurs are reminded to be alert for unusual DX openings *anywhere* over paths that are in total darkness, or when it is dark on one end of the path, and sunset or sunrise at the other. Remember, these Tests are not contests! They are conducted for pleasure in an unusual operating

activity, without competition, and to develop some propagation information, which may make a worthwhile contribution to the art of radio. W/VE stations should send their Test reports directly to W1BB after each Test period. W1BB's QTH is Stewart S. Perry, 36 Pleasant Street, Winthrop, Mass. British stations should send their reports to G6QB, "Tommy" Thomas, DX Editor *SWM*, 49 Winchelsea Lane, Hastings, Sussex, England. Other DX stations can send their reports to either W1BB or G6QB."

V.h.f. Ionospheric Openings

There is a tendency for sporadic-E propagation to reach a minor seasonal peak during December (the major peak occurs during the early summer months). This may result in some short-skip openings on 10 and 6 meters, between distances of approximately 800 and 1400 miles. An interesting letter has been received from Pat Dyer, WA5IYX, who, as a senior in High School, is conducting a sporadic-E research program. Pat would like to hear from other radio amateurs who may be interested in participating in this program. His QTH is 279 Lark Avenue, San Antonio, Texas 78228.

A major meteor shower, the Geminids, should take place during the second week of December. Short-skip v.h.f. openings may be possible for distances up to approximately 1000 miles during

this period as a result of ionization produced by the meteors as they enter the earth's atmosphere.

V.h.f. ionospheric openings over several hundred miles are also likely to occur during auroral displays. Such displays often occur during periods of ionospheric storminess. Check the "Last Minute Forecast" appearing at the beginning of this column for those days that are expected to be "disturbed" or "below normal".

Sunspot Cycle

The Zurich Observatory reports a monthly average sunspot number of 16.3 for September, 1965. This results in a smoothed running number of 12.7, centered on March, 1965. The sunspot cycle is rising very slowly from the minimum value of 9.7, which occurred during October, 1964. A smoothed sunspot number of 25 is predicted for December, 1965.

This month's column contains DX *Propagation Charts* for December, 1965 and January, 1966. Short-Skip *Charts* for December appeared in last month's column.

The Editor of this column would like to take this opportunity to extend the warmest of wishes to readers of this column for a Merry Christmas and a very Happy New Year.

73, George, W3ASK

CQ DX PROPAGATION CHARTS DECEMBER 1965 & JANUARY 1966

Time Zone: EST (24-hour Time)
EASTERN USA TO:

	10/15 Meters	20 Meters	40 Meters	80/160 Meters
Western & Central Europe & North Africa	08-12 (1)* 07-08 (1) 08-09 (3) 09-11 (4) 11-13 (2) 13-15 (1)	06-07 (1) 07-08 (2) 08-09 (3) 09-12 (4) 12-13 (3) 13-15 (2) 15-17 (1)	15-17 (1) 17-18 (2) 18-23 (3) 23-01 (2) 01-03 (1) 03-04 (2) 04-05 (1)	18-20 (1) 20-23 (2) 23-03 (3) 03-04 (1) 20-00 (1)† 00-02 (2)† 02-03 (1)†
Northern Europe & Eastern USSR	07-08 (1) 08-10 (2) 10-13 (1)	06-07 (1) 07-08 (2) 08-10 (3) 10-11 (2) 11-15 (1)	17-03 (1)	19-02 (1) 21-01 (1)†
West & Central Africa	08-10 (1)* 10-12 (2)* 12-13 (1)* 07-08 (1) 08-11 (2) 11-12 (3) 12-14 (4) 14-15 (2) 15-16 (1)	01-03 (1) 06-07 (1) 07-09 (2) 09-12 (1) 12-14 (2) 14-16 (4) 16-17 (2) 17-18 (1)	18-19 (1) 19-22 (2) 22-01 (1)	20-02 (1) 21-00 (1)†
South Africa	08-10 (1)* 10-12 (2)* 12-15 (1)* 07-10 (1) 10-12 (2) 12-14 (3) 14-15 (2) 15-17 (1)	01-03 (1) 07-13 (1) 13-14 (2) 14-17 (3) 17-18 (2) 18-20 (1)	18-19 (1) 19-21 (2) 21-00 (1)	19-22 (1) 19-22 (1)†
Eastern Mediterranean & East Africa	08-11 (1)* 07-08 (1) 08-10 (2) 10-13 (1)	00-03 (1) 07-09 (1) 09-11 (2) 11-13 (3) 13-14 (2) 14-16 (1)	18-19 (1) 19-21 (2) 21-00 (1)	20-23 (1) 19-22 (1)†

*Predicted 10 meter openings, all others in column are 15 meter openings.

†Predicted 160 meter openings, all others in column are 80 meter openings.

Central Asia	08-10 (1) 17-19 (1)	06-07 (1) 07-09 (2) 09-10 (1) 18-21 (1)	06-08 (1) 19-22 (1)	Nil
South-east Asia	08-11 (1) 17-19 (1)	06-07 (1) 07-09 (2) 09-12 (1) 18-21 (1)	06-08 (1) 17-20 (1)	Nil
Far East	17-18 (1) 18-19 (2) 19-20 (1)	06-07 (1) 07-09 (2) 09-11 (1) 16-18 (1) 18-19 (2) 19-21 (1)	05-08 (1)	05-07 (1)
Guam & Pacific Islands	13-14 (1)* 14-15 (2)* 15-17 (1)* 11-14 (1) 14-15 (2) 15-16 (3) 16-17 (2) 17-19 (1)	05-07 (1) 07-09 (3) 09-11 (2) 11-18 (1) 18-20 (2) 20-22 (1)	01-02 (1) 02-04 (2) 04-07 (3) 07-08 (2) 08-09 (1)	04-05 (1) 05-07 (2) 07-08 (1) 04-07 (1)†
Australasia & New Zealand	15-17 (1)* 09-12 (1) 15-16 (1) 16-18 (2) 18-21 (1)	06-07 (1) 07-10 (2) 10-13 (1) 13-15 (2) 15-18 (1) 18-20 (2) 20-22 (1)	04-06 (1) 06-08 (2) 08-09 (1)	05-08 (1) 05-07 (1)†
Northern & Central South America	08-10 (1)* 10-12 (2)* 12-14 (3)* 14-15 (2)* 15-16 (1)* 07-08 (1) 08-09 (2) 09-11 (3) 11-14 (2) 14-16 (4) 16-18 (2) 18-20 (1)	06-07 (2) 07-08 (3) 08-09 (4) 09-11 (3) 11-15 (2) 15-17 (3) 17-19 (4) 19-20 (3) 20-22 (2) 22-00 (1) 00-03 (2) 03-06 (1)	18-20 (1) 20-22 (2) 22-00 (3) 00-04 (2) 04-07 (1)	19-21 (1) 21-02 (2) 02-05 (1) 21-04 (1)†
Southern Brazil, Argentina, Chile & Uruguay	08-12 (1)* 12-16 (2)* 16-18 (1)* 07-08 (1) 08-14 (2) 14-16 (4) 16-17 (3) 17-18 (2) 18-20 (1)	01-06 (1) 06-07 (2) 07-09 (3) 09-10 (2) 10-14 (1) 14-15 (2) 15-17 (3) 17-19 (4) 19-21 (3) 21-01 (2)	19-21 (1) 21-03 (2) 03-07 (1)	21-05 (1) 02-04 (1)†

Mc-Murdo Sound, Antarctica	08-11 (1) *	06-07 (1)	22-00 (1)	Nil
	07-08 (1)	07-09 (2)	00-02 (2)	
	08-10 (2)	09-12 (1)	02-06 (1)	
	10-14 (1)	15-17 (1)		
	14-16 (2)	17-19 (2)		
	16-19 (1)	19-21 (3)		
	21-23 (2)			
	23-03 (1)			

Mc-Murdo Sound, Antarctica	08-11 (1) *	06-07 (1)	22-00 (1)	Nil
	07-08 (1)	07-09 (2)	00-02 (2)	
	08-10 (2)	09-12 (1)	02-06 (1)	
	10-14 (1)	15-17 (1)		
	14-16 (2)	17-19 (2)		
	16-19 (1)	19-21 (3)		
	21-23 (2)			
	23-03 (1)			

Time Zones: CST and MST (24-hour Time)

CENTRAL USA To:

Time Zone: PST (24-hour Time)

WESTERN USA To:

	10/15 Meters	20 Meters	40 Meters	80/160 Meters
Western & Central Europe & North Africa	09-11 (1) * 07-09 (1) 09-11 (3) 11-14 (1)	07-08 (1) 08-10 (2) 10-12 (3) 12-14 (2) 14-16 (1)	15-17 (1) 17-23 (2) 23-03 (1)	17-19 (1) 19-21 (2) 21-02 (1) 20-01 (1) †
Northern Europe & European USSR	07-09 (1) 09-10 (2) 10-12 (1)	07-08 (1) 08-10 (2) 10-13 (1)	18-01 (1)	20-00 (1) 21-23 (1) †
East & West Africa	08-10 (1) * 10-12 (2) * 12-13 (1) * 07-09 (1) 09-11 (2) 11-13 (3) 13-14 (2) 14-15 (1)	06-07 (1) 07-09 (2) 09-11 (1) 11-13 (2) 13-16 (3) 16-17 (2) 17-19 (1) 22-02 (1)	18-19 (1) 19-21 (2) 21-23 (1)	19-21 (1)
Central & South Africa	08-10 (1) * 10-13 (2) * 13-16 (1) * 07-10 (1) 10-12 (2) 12-14 (3) 14-16 (2) 16-18 (1)	08-12 (1) 12-14 (2) 14-17 (3) 17-18 (2) 18-21 (1)	18-20 (1) 20-22 (2) 22-00 (1)	19-22 (1)
Eastern Mediterranean	07-08 (1) 08-10 (2) 10-11 (1)	22-02 (1) 07-10 (1) 10-12 (2) 12-15 (1)	18-23 (1)	20-22 (1)
Central Asia	07-10 (1) 19-21 (1)	06-07 (1) 07-09 (2) 09-10 (1) 19-21 (1)	06-08 (1) 19-21 (1)	Nil
Southeast Asia	09-12 (1) 17-20 (1)	06-07 (1) 07-09 (2) 09-12 (1) 17-20 (1)	06-08 (1) 17-19 (1)	Nil
Far East	16-17 (1) 17-19 (2) 19-20 (1)	06-07 (1) 07-09 (2) 09-11 (1) 15-17 (1) 17-19 (2) 19-21 (1)	03-09 (1)	04-07 (1)
Pacific Islands & New Zealand	12-14 (1) * 14-16 (2) * 16-18 (1) * 10-13 (1) 13-14 (2) 14-16 (3) 16-18 (2) 18-19 (1)	06-07 (1) 07-09 (3) 09-11 (2) 11-15 (1) 15-17 (2) 17-19 (3) 19-20 (2) 20-21 (1)	22-00 (1) 00-02 (2) 02-06 (3) 06-07 (2) 07-09 (1)	22-00 (1) 00-02 (2) 02-06 (3) 06-07 (2) 07-09 (1) 03-07 (1) †
Australasia	14-15 (1) * 15-16 (2) * 16-17 (1) * 08-14 (1) 14-18 (2) 18-20 (1)	06-07 (1) 07-11 (2) 11-19 (1) 19-21 (2) 21-22 (1)	01-03 (1) 03-07 (3) 07-08 (2) 08-09 (1)	03-05 (1) 05-07 (2) 07-08 (1) 04-07 (1) †
Northern & Central South America	08-10 (1) * 10-14 (3) * 14-15 (2) * 15-16 (1) * 07-08 (1) 08-09 (2) 09-13 (3) 13-16 (4) 16-17 (2) 17-19 (1)	06-07 (2) 07-11 (3) 11-14 (2) 14-16 (3) 16-18 (4) 18-19 (3) 19-21 (2) 21-00 (1) 00-02 (2) 07-06 (1)	18-20 (1) 20-22 (2) 22-01 (3) 01-03 (2) 03-06 (1)	19-21 (1) 21-02 (2) 02-05 (1) 23-04 (1) †
Southern Brazil, Argentina, Chile & Uruguay	08-11 (1) * 11-15 (2) * 15-17 (1) * 07-08 (1) 08-13 (2) 13-15 (4) 15-16 (3) 16-17 (2) 17-19 (1)	06-07 (2) 07-09 (3) 09-10 (2) 10-14 (1) 14-15 (2) 15-16 (3) 16-18 (4) 18-21 (3) 21-23 (2) 23-06 (1)	19-21 (1) 21-02 (2) 02-06 (1)	21-05 (1) 01-03 (1) †

	10/15 Meters	20 Meters	40 Meters	80/160 Meters
Western & Central Europe & North Africa	07-09 (1) * 06-07 (1) 07-09 (2) 09-11 (1)	05-07 (1) 07-10 (2) 10-13 (1) 21-23 (1)	16-18 (1) 18-22 (2) 22-00 (1)	18-23 (1) 19-22 (1) †
Northern Europe & European USSR	07-09 (1)	06-08 (1) 08-10 (2) 10-13 (1)	17-00 (1)	19-23 (1)
Eastern Mediterranean & East Africa	07-09 (1)	06-07 (1) 07-09 (2) 09-11 (1)	18-22 (1)	Nil
West & Central Africa	09-13 (1) * 07-09 (1) 09-10 (2) 10-12 (3) 12-13 (2) 13-14 (1)	06-10 (1) 10-13 (2) 13-16 (3) 16-18 (2) 18-19 (1)	18-22 (1)	19-21 (1)
South Africa	08-13 (1) * 06-08 (1) 08-10 (2) 10-12 (3) 12-14 (2) 14-16 (1)	09-11 (1) 11-13 (2) 13-15 (3) 15-17 (2) 17-19 (1) 00-02 (1)	18-21 (1)	18-20 (1)
Central Asia	08-10 (1) 17-19 (1)	06-07 (1) 07-09 (2) 09-11 (1) 17-19 (1) 19-20 (2) 20-21 (1)	05-07 (1) 18-20 (1)	Nil
Southeast Asia	15-18 (1) * 09-11 (1) 15-16 (1) 16-18 (2) 18-19 (1)	07-09 (1) 09-11 (2) 11-17 (1) 17-19 (2) 19-20 (1)	01-04 (1) 04-07 (2) 07-09 (1)	04-07 (1)
Far East	14-17 (1) * 13-15 (1) 15-17 (2) 17-19 (1)	08-10 (1) 13-14 (1) 14-17 (3) 17-19 (2) 19-20 (1)	22-00 (1) 00-06 (3) 06-08 (2) 08-10 (1)	00-01 (1) 01-05 (2) 05-08 (1) 01-06 (1) †
Pacific Islands & New Zealand	12-15 (1) * 15-17 (2) * 17-18 (1) * 09-12 (1) 12-14 (2) 14-16 (4) 16-18 (2) 18-20 (1)	07-08 (1) 08-10 (2) 10-15 (1) 15-16 (2) 16-18 (4) 18-19 (2) 19-21 (1)	20-22 (1) 22-00 (2) 00-05 (3) 05-07 (2) 07-09 (1)	00-03 (1) 03-06 (2) 06-08 (1) 03-06 (1) †
Australasia	12-14 (1) * 14-16 (2) * 16-17 (1) * 08-10 (1) 10-12 (2) 12-15 (1) 15-17 (3) 17-18 (2) 18-19 (1)	07-08 (1) 08-10 (3) 10-12 (2) 12-17 (1) 17-18 (2) 18-20 (3) 20-21 (2) 21-22 (1)	01-03 (1) 03-05 (2) 05-07 (3) 07-09 (1)	03-05 (1) 05-06 (2) 06-08 (1) 04-07 (1) †
Northern & Central South America	08-10 (1) * 10-12 (3) * 12-14 (2) * 14-16 (1) * 06-08 (1) 08-10 (2) 10-12 (3) 12-14 (4) 14-15 (3) 15-16 (2) 16-18 (1)	05-07 (2) 07-09 (3) 09-14 (2) 14-15 (3) 15-17 (4) 17-18 (3) 18-20 (2) 20-05 (1)	18-20 (1) 20-00 (3) 00-02 (2) 02-04 (1)	20-22 (1) 22-01 (2) 01-03 (1) 22-01 (1) †

*Predicted 10 meter openings, all others in column are 15 meter openings.

†Predicted 160 meter openings, all others in column are 80 meter openings.

[Continued on page 96]

two-way contact about 15 minutes after setup of the 5900 mc gear on F2, and then changed modes to rebreak the record on F3. Will Jensby, WA6BQO, assisted at the Copernicus peak end." *In all, quite a day for v.h.f.!*

Syracuse Report


Things looked dark for a time, but we (K2UYH) did finally make it to the Syracuse V.H.F. Roundup! Fred, WA2FSQ, our co-driver, came down with a cold at the last moment. Due to the resultant last-minute confusion we did not leave until 6:00 a.m. the next day (Saturday), which meant a 5-hour trip up and a 5-hour trip back—all on the same day. Sunday had already been reserved for work. The Roundup, however, we can assure you, was well worth the effort.

Shortly after receiving local directions from W1OOP (who was also mobile enroute to the gathering) we arrived at our destination, the Three Rivers Inn. Immediately we began trading ideas with the fellows there. In my opinion these talk sessions are the most rewarding aspect of any v.h.f. conclave. The chance to talk face-to-face and hear other amateur's plans and ideas is invaluable.

Syracuse attracts the "tops in v.h.f. radio." Practically every moonbounce enthusiast on the east side of the Mississippi was present. We spent a considerable amount of time talking with Tom Sly, K2QRX. Tom is one of the few stations in this country seriously working with two meter moonbounce. Using an array consisting of 4 ten-element yagis, Tom has received his own echoes, and has just recently started maintaining skeds with W6DNG. Though moonbounce is marginal on two meters, we expect that Tom will succeed due both to the precision and practicability of the way he is approaching the project. We tried to persuade him to use the weak-signal detection system we have been experimenting, with which supplies gain by integration and applies a modified Dicke system (used in radio astronomy) for gain stability. Use of such a system should take two meter moonbounce out of the realm of the "marginal."



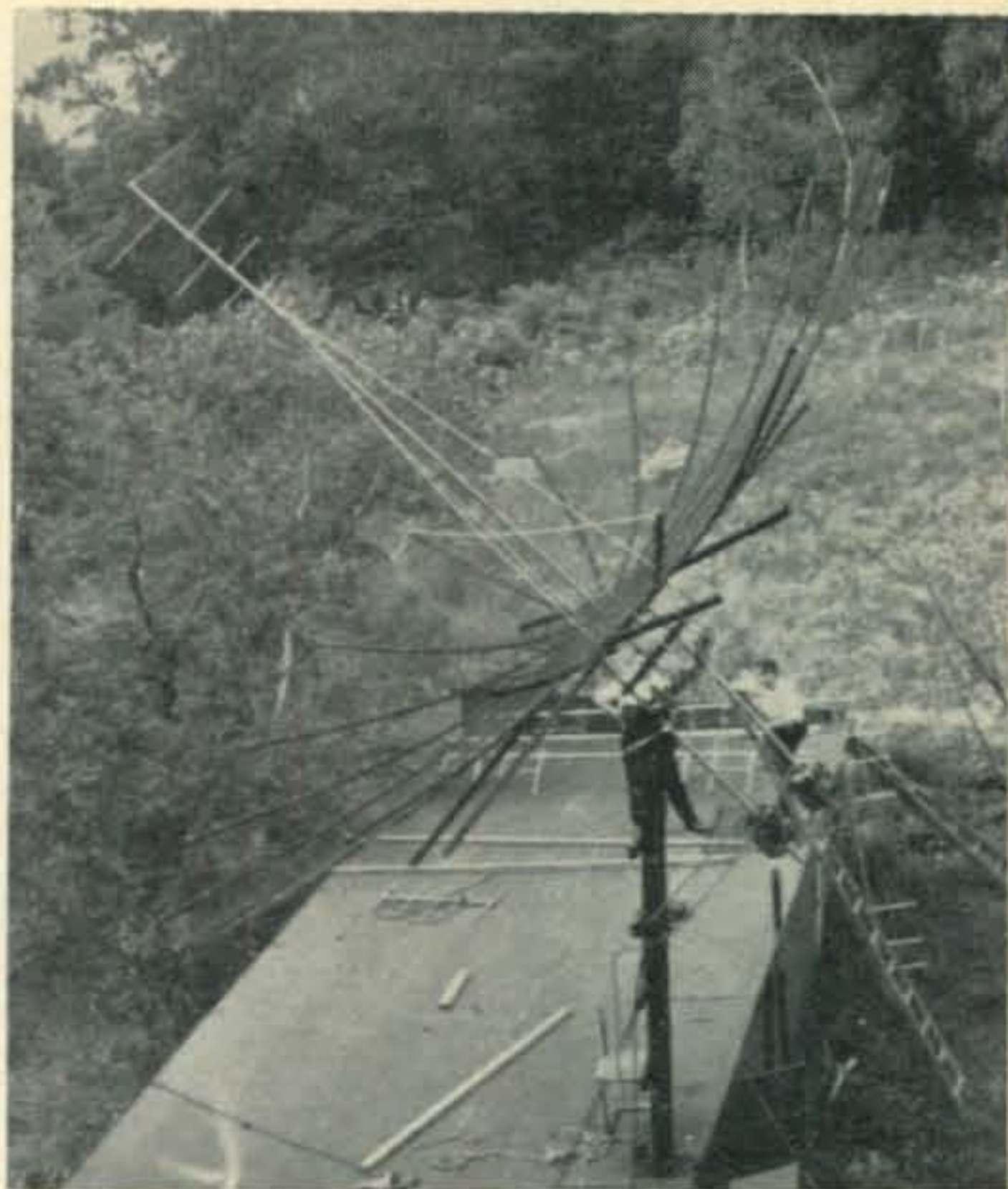You'd be excited too if you were hearing HB9RG & G3LTF on 432. Bottom to top, behold WA6MGZ, W6CBE, K6HCP and an interested observer operating WA6LET on Sept. 25.




Visitor inspects K2UYH's new moonbounce dish at Oak Ridge, N.J.

Technical Program

The first speaker, whom we nearly missed by being engrossed in our conversation with K2QRX, was Fred Collins, W1FRR. Fred spoke about the fantastic advances being made by solid-state devices on the v.h.f.-u.h.f. scene. Much of his talk was concerned with varactor multipliers—a device with which Fred is intimately connected by his work for Microwave Associates, Inc. Of particular interest was a 432-to-1296 mc varactor tripler using lumped components (no cavities). We obtained a schematic of the unit and Fred promised to send pictures. So you can expect construction information on this device next month. Fred also mentioned that Microwave Associates is still supplying varactors "for hams only" at a price of 10 dollars.

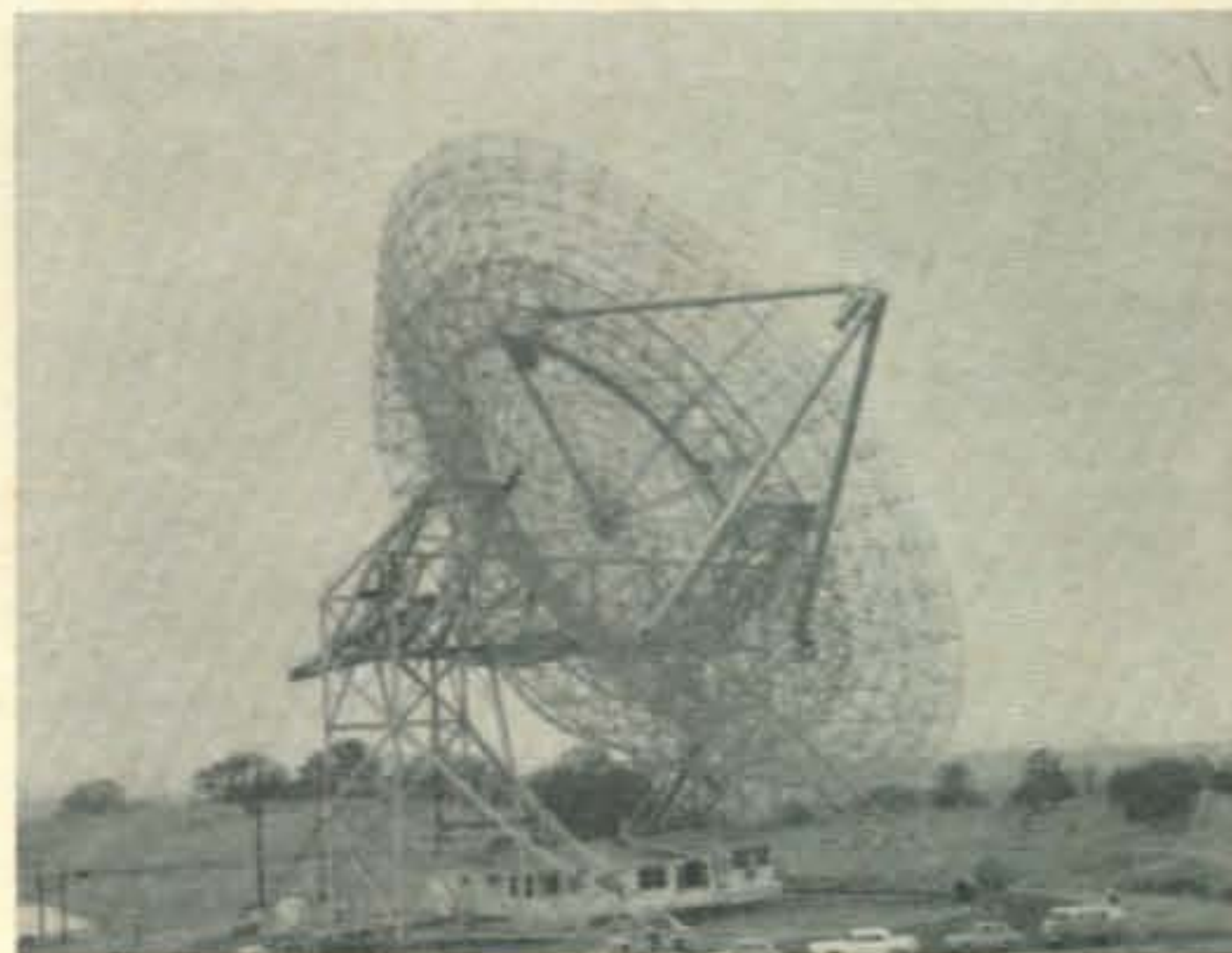The next speaker on the roster was Henry Cross, W1OOP, a close friend of both W1FZJ and KP4BPZ and a moonbounce expert in his



Here's the monster responsible for the big 432 moon-bouncing affair on Sept. 25. It is Stanford Research Institute's 150' tiltable parabolic, into which WA6LET rammed 1000 watts. Europe on 3/4 meters?!



Here's Fred Collins, W1FRR, delivering his "Solid State & VHF" presentation at Syracuse on Oct. 2nd. (Photo by K2AVA).

own right. Henry described the 1000 foot dish at Arecibo and gave the inside story of its operation for amateur purposes. One point he mentioned which jarred us was the fact that when the multi-megawatt transmitters at Arecibo are used on the moon, not only is it possible to hear one echo, but a second (the signal bounced off the moon, off the earth, and off the moon again) can also be received . . . *that* is what we call a signal! At the end of his talk, Henry played tapes made at Arecibo during the 432 mc moonbounce tests of July 3 and 24 of this year.

Project Oscar

The final speaker was Nick Marshall, W6OLO, who gave an excellent talk on the history of Project Oscar supplemented by color slides. It might interest you that the idea of Project Oscar was born on the pages of *CQ* in an article by Don Stoner, W6TNS, who for a time acted as v.h.f. columnist.

The Evening

Before the banquet we spent most of our time talking with Vic, W3SDZ, so much so that we were nearly late for the dinner. Vic had tapes of his 432 mc moonbounce contacts with KP4BPZ and WA6LET and supplied us with much information on his own moonbounce efforts. After the meal, awards were presented to the highest scoring multi-operator stations in the nation and Western New York section for the June ARRL V.H.F. Contest. (W1MHL and W2WEB won the awards respectively.) Next, the door prizes were awarded. (I believe that Fred, W1FRR, took First Prize—How is that for luck?) Finally came the floor show which was said to be first rate. However, considering the distance ahead of us and the rigours of the day, we decided to leave early. As it was, we did not arrive home before the wee hours of the morning.

Hope to see more of you at Syracuse next year.

On The WA6LET Tests

Victor Michael, W3SDZ, Milton, Pa: "The WA6LET tests have proved that the 'honeymoon is over' or moonbounce is difficult with amateur techniques even if you have a 150 foot dish. A total of seven different stations made it although

VHF DX RECORDS

The following represent the greatest confirmed distance records established by amateurs for two-way communications.

- 50 Mc**
12,000 m.: LU3EX-JA6FR, March 24, 1956.
- 144 Mc**
5250 m.: OH1NL-W6DNG,* April 11, 1964.
- 220 Mc**
2540 m.: W6NLZ-KH6UK, June 22, 1959.
- 420 Mc**
5092 m.: KH6UK-W1BU,* July 31, 1964.
- 1215 Mc**
5092 m.: KH6UK-W1BU*, Aug. 9, 1962.
- 2300 Mc**
170 m.: W1EHF/1-W2BVU/1, July 1963.
- 3300 Mc**
190 m.: W6IFE/6-W6VIX/6, June 9, 1956.
- 5650 Mc**
120 m.: WB6JZY-WA6KKK, Sept. 25, 1965.
- 10,000 Mc**
265 m.: W7JIP/7-W7LHL/7, July 31, 1960.
- Above 30,000 Mc**
500 feet: W6NSV/6-K6YYF/6, July 17, 1957.

*moonbounce communications.

11 calls were used for contacts. It seems that troubles were part of the problem at Stanford. I talked with the crew by telephone during and after the tests, and they are not sure they were tracking the moon accurately during the test. I know their signal improved a good bit from the time I worked them at 1500 GMT until the signal was strongest at about 1900 GMT to about 1945 GMT when they signed off.

"I think this again points up the fact that for celestial tracking an el-az type of mount is most difficult to use. It requires a computer to get even technical tracking. With my polar mounted antenna, I was able to run the dish ahead in our angle and check sun noise to be sure the antenna was aiming properly. For instance, the crew in California were concerned that they were having problems with refraction of the signal through the atmosphere. Whether or not this is a problem I don't know (I've been told it isn't) but having the sun to check on solves the problem.

"We had excellent tracking on Sat. In fact, we ran some tests (quick echo) and were pleasantly surprised to find our own echoes coming back. They are not loud, but I do have them on tape.

"The reason I didn't continue the echo tests on Sat. was that we blew a screen bypass in the final amplifier and shorted out one tube when we really tried to push the final amplifier up.

"Speaking of the new final, it works real well. We are developing 62% efficiency at 600 watts output. For the California tests we were running about 450 watts out to be sure everything would hold up. We have been able to measure as much as 1100 watts output from the amplifier with everything running wide open. It is using 8122's (RCA) in push-pull with half-wave lines.

"I'm not satisfied that I'm getting the maximum results I may eventually be able to get
[Continued on page 98]



HAM CLINIC

CHARLES J. SCHAUERS,* W6QLV



THE task of trying to keep up with the state of the radio-electronics art is not an easy one today—even for those of us who make a lot of effort to do so. It seems that something new is always followed shortly by something newer. Today's grand technical achievement often turns out to be tomorrow's "old hat"—but modern day technical progress is frequently measured in very small "units" or "spurts." Some of the most spectacular breakthroughs are not always as widely publicized as they should be.

One of the most outstanding accomplishments during this century (as far as amateur radio is concerned) was the rocketing into orbit of the OSCAR series of communications satellites. OSCAR (Orbital Satellite Carrying Amateur Radio) was no "stunt." As more OSCAR shots follow, each will contribute still more to the stature of amateur radio and the wider use of the uncluttered v.h.f., u.h.f. and even s.h.f. bands.

As sure as the sun sets and rises, one of these days a ham *anywhere* will be able to talk to another ham *anywhere* via amateur repeater satellites.

The new OSCARS in "stationary" orbit will be sophisticated jobs and even employ the multiplex techniques which permit hundreds, lo, even thousands of channels to be made available for communication. Of course, the h.f. bands will continue to be used but most hams will use the v.h.f./u.h.f. satellites.

Can't you imagine a number of ultra-modern, long-lived OSCARS in orbit? I can!

You know, the day will surely come when it will be possible to service communications satellites via interplanetary spacecraft. Far-fetched? Not at all!

As time goes on, newer power supply systems will be available and so will v.h.f./u.h.f. high power transistors. There is really nothing to prevent the establishment of a complete system of amateur communications satellites except money. Actually, if you get right down to it, 99% of the world's active hams would no doubt contribute enough money to get up the first 3 or 4 satellites. Of course the job is a big one but not so big that it cannot be done.

What we actually need in the world today is an international amateur radio organization which will be accepted by all countries and even

have a seat within the International Telecommunications Union! Amateur radio is important enough for this.

This organization would act for *all* national radio organizations on frequency allocations and other matters.

Let us hope we all see the day when we have satellites for amateur radio communications purposes in orbit and also an international organization to take care of the *world's* ham requirements.

More on s.w. Broadcasting

My piece in the August 1965 issue of *CQ* on shortwave broadcasting resulted in my receiving exactly 28 letters. All of these letters defended s.w. broadcasting, but many writers lost the point of my little essay. The point again is: we have too many s.w.b.c. stations! These stations *are not all* needed. Nations of the world should be limited (according to location, population and resources) to the number of stations to effectively give the world-wide coverage they seek. True, s.w. broadcasts are not all propaganda and have much news and cultural value. Also, the educational aspects of shortwave broadcasting should not be overlooked for as was pointed out to me by a reader from Venezuela, a large number of people do learn languages by listening to s.w. broadcasts, as well as many other subjects.

I wrote in my August piece that I felt that developing nations should develop their own internal communications requirements before spending a lot of money on s.w. broadcast stations which would be of doubtful value in the crowded s.w. bands as they are today.

I would hate to think that I was responsible for the installation of an expensive s.w. broadcast station when my country's overseas telephone services were either non-existent or were very inefficient.

The argument that more h.f. band space must be made available to make room for more s.w.b.c. stations is nonsense—especially when there may be some thought of chasing the hams off the few kilocycles they have. I feel that a country that encourages amateur radio operation has a great asset in technically trained people that they would not have otherwise. If amateur radio development is curtailed then a country suffers technically. The largest countries in the world encourage ham radio (especially the USA and the USSR) for they realize that the citizens who train themselves and practice the amateur radio art are more than just "hobbyists." No country in its "right mind" would prevent development of its own technical resources by curtailing a radio service (the amateur radio service) without doing harm to itself.

Show me a country with a lot of hams and I will show you a nation that has good internal as well as external communications!

I rest my case.

Questions

Integrated Circuits (IC)—"What role do you think integrated circuits (IC's) will play in the

*c/o *CQ*, 14 Vanderventer Ave., Port Washington, L.I., N. Y.

did with a special bracket I made) and when I hooked it up to the matching network also supplied by Partridge, I was able with my KWM-2 to work Europe without the difficulty I had before. However, there is a question I'd like to ask and it is this: I am planning to buy a Henry 2K final, do you think this antenna will handle the power?

The Henry 2K final is a high efficiency linear amplifier and the reports I have received on it are absolutely excellent. It does put out the maximum power allowed by FCC regulations but the tests I have made here (in Switzerland with the help of HB9ACN) indicate that the antenna is *under-rated*—especially if it is used as an outdoor antenna. With the Joystick you have the advantage of the feeder radiating as well as the main "stick." If you are up high enough, the antenna will operate (especially on 15 and 20 meters) as well as a well-known 3 element beam with which we compared it. The tests were *operational* not "theoretical." We found that if we could hear 'em we could work 'em . . . and in most cases with 100 watts input! If you operate the Joystick as suggested by the manufacturer and have a good ground ("earthing" to the Englishman) it is hard to beat the Joystick as a simple, easily installed and non-complicated antenna, even if you have a suite in the Empire State building. I like it.

HB9XBC—"I understand that the Swiss PTT granted mobile licenses for three days to attendees to the IARC convention this year. As you were a panelist did you have a call and what was it? By the way, how was *the* convention?"

The convention was great! Thanks to the PTT I did operate mobile from HB9AEQ's mobile. My call was HB9XBC. The International Amateur Radio Club is a great organization! If you do not belong to the IARC, drop a letter to the Secretary, IARC Geneva 20, Switzerland for an application blank. Gosh, we had a lot of fun!

KWM-2 Power Supply Modification—Thanks to Doug Horner, W0HUF of Collins Radio Co. here is some information that will be of interest to KWM-2 owners. He says: "the KWM-2 will operate with the 516F-2, 516F-1, MP-1, 516E-1, 516E-2, and the PM-2 power supplies. It is only the latter power supply which underwent modification to increase the momentary supply voltage limits." The modification bulletin for the PM-2 is available by writing Collins and directing your inquiry to Doug. Ask for Bulletin No. 1 for PM-2.

Second Mixer Revision for 75A-4—A few of the earlier manufactured 75A-4's passed d.c. through the mechanical filter. This was not harmful, but should one of the pins or coils become grounded, the mechanical filter often was destroyed. There apparently are a few 75A-4's that have not been modified to prevent this. So if you have a 75A-4 and are interested in the modification, write Doug and ask him for the bulletin titled as is this paragraph. Thanks so much Doug! We know

that those interested will write to you. Aside: you know, it is a *nice* thought to know that a large manufacturer of precision equipment is interested in keeping their customers posted.

1625 GG Amplifier—"I'd like to build a linear amplifier using 1625 tubes and be able to drive it with 20 watts or so. Any issues of *CQ* have information on this?"

Yes. Try the September 1960 issue for the article "A 1625 GG Linear Amplifier." Reprints of the article (as for any other available article) are obtainable from the Editor, *CQ* for \$1.00. (Do *not* send your article reprint orders to HAM CLINIC!)

BC-779 Ultimate Conversion—"In what issue of *CQ* did an article on the BC-779 appear which covered a lot of modifications?"

Try the April 1961 issue of *CQ*. Other articles on the BC-779 appeared in the Sept. 1958, Oct. 1952, May 1948 issues.

Thirty

We extend our Christmas season's greetings to all of our readers, manufacture service managers who have assisted us to assist you in solving some of your knotty technical problems and to fellow hams all over the world. May 1966 be a year of peace and progression for amateur radio.

73 and 75 Chuck & Elfriede.

BY THE WAY . . .



Where else would this mobile amateur radio rally be held—but Wolfsburg, Germany, home of the Volkswagen. Seen entering the town is a caravan of mobile stations from all over Germany. In the distance (upper left side of photo) can be seen the Volkswagen plant.



NOVICE

WALTER G. BURDINE,* W8ZCV

I HAVE always advocated that the new amateur build his first station and get it working; he will be much better for the experience. Many are just a little afraid to try changing anything from the parts list. The value of most components can be changed as much as 25 percent in value without adversely affecting the operation or the circuit. Indeed the ratings are sometimes + or - 20 percent of the value indicated by the color code. Resistors with larger wattage ratings can always be used if you have the space. This is sometimes considered an advantage to the operation of the set. The value of resistance can be obtained by paralleling or series connecting resistors using ohms law to arrive at your value. Resistors of lower wattage rating should never be used except in an emergency, then they should be replaced with the correct replacement value as soon as possible.

Replacing open or shorted capacitors should present no problem if the correct replacement is available. Always check any resistor in the circuit bypassed by a shorted capacitor, they have usually been overloaded when the capacitor shorted. This can easily be spotted by discoloration of the resistor due to the additional load placed upon the resistor by the shorted capacitor. Always check the resistor in the circuit with an ohmmeter to see if it has changed value. The capacitor should be replaced with one of the same or larger voltage rating and the capacity rating can be anything near the value used in the original equipment. Connecting capacitors in series or parallel can solve unusual values of capacitance. Use the handbook to help you remember the formulas for building the right capacity, if you use them often you won't need the handbook after a while.

Replacing transformers can be a task but with a little ingenuity and careful planning many transmitters can be repaired to make that schedule on time. If you have a homebrew station you can use almost any available unit that will fit in the space. A better way is to disconnect the transformer leads and wire a cable into the circuit and plug in a power supply as shown in last month's column. This can furnish power for your station until you can get a replacement unit for a permanent repair. I usually build my power supply as a separate unit for ease of replacement when necessity arises. Filament transformers for high powered finals are usually placed near the

tubes to reduce the voltage drop in the filament leads to the tube. High voltage can be built on another chassis to conserve space for the final tubes.

In an emergency some 400 cycle power transformers can be pressed into service as a modulation transformer. Filament transformers can be used as output transformer for emergency repair. These are tricks that have kept many hams on the air during emergency operations. They work even if they aren't the best way to do the job.

Repairing coils and inductances can be more tricky than any other part of the transmitter or receiver. Changing any parameter of the coil will change its frequency coverage. Coils can be repaired but read the handbook carefully before attempting repair or replacement of coils in frequency determining circuits.

Learn to use your handbook correctly. Know where to find the formulas. Learn how to read the tube charts and evaluate the physical and electrical parameters of the tubes. Keep your magazines for future reference, read them and learn to understand their information, someone took a long time to write that information. You will one day be able to help the newcomer.

Letters to the Editor

Please read this letter carefully and you will see that we are still trying to help the newcomer and why we sometimes use the parts and methods to keep the constructional cost down to the bone. This letter from Leon Johnson, WNØDWV, P.O. Box 146, Holland, Missouri.

"Hello Walt: I'm finally getting around to writing about the modest station here. I hope it will be of interest to someone.

"The rig consists of a Lafayette HE-80 receiver and a homebrew transmitter. The transmitter is a 6L6 oscillator running about 10 watts. I got 99 percent of the parts from old television sets. Three cheers for old TV sets and for cake pans, the poor man's radio chassis. I spend most of my time on 7.158, 7.167 and 7.183. I am working 15 meters and have worked Miami. I'm planning a beam for 15 with wire elements supported by fishing poles as my dipole doesn't work so well on 15.

"I received my ticket in February, it was dated January 5 so I lost one month there and it took another month to get the transmitter working. I owe a lot to Bob Cox, K5KMK and Jack White whose call I have forgotten. They gave me the code and theory course in Blytheville, Arkansas YMCA. I know of three who took the test and I'm sure they passed and all should have their tickets.

"I must heap praise on the crew at CQ. You do a great job, I think the Novice section is the greatest. The main thing about CQ that I like is the construction articles, they are easy to build. I wish you would have more articles on amplifiers, transmitters, receivers and equipment built from old television sets. I have many of them laying around and almost anyone wanting a license has one or two, or can get them cheap enough, to build their station. This would help us to save money and get on the air. I'm only 17 and a senior in high school. We teens aren't too rich you know. I think you could give some layout ideas for the rank beginner, because there's a difference between the schematic and the physical layout. For someone who isn't experienced that presents quite a problem. It's the little things that you "old timers" take for granted that bothers us dopy little Novices. I believe that too many newcomers have been led to believe that you must have a fancy high powered rig to do anything. Actually I've learned that with a few parts you can build a rig that will give as much pleasure as the commercially built rigs. I can work about anything that I can hear, with my QRP 10

*R.F.D. 3, Waynesville, Ohio 45068.

watt rig. I've had many ask me what I had in the final when I gave my power, they didn't believe me. I have worked California with a 569 and Oregon with a 569 but I hope to change that on 15 meters. I hope to go v.h.f. some day using surplus gear as that seems the cheapest way. I also would like to go ATV but guess by the time I get there it will be as crowded as the 40 meters is now.

"I would like skeds with the Western and Northeastern states for my WAS, I have 29 for 35 states, all on 40 meters. Either my receiver, antenna or something else isn't as good as it should be or something because I don't hear those rare and exotic calls that I read about in *CQ*. I always tune across the Novice and General bands and listen but I just don't hear them. I may be crazy but I'm in favor of some sort of incentive licensing even though it will deprive me of some privileges. I also think the new amateur should do some homebrew work. I hope to have at least 90 percent of my station homebrew or converted surplus.

"I'll send a picture of the shack someday. Keep up the good work of explaining circuits and giving us simple circuits that we can build. BCNU es 73. Leon."

Thanks, Leon, I am planning a complete station built around surplus TV set parts. This will have something for all classes of licenses and will be for all bands. I now have the TV sets and am working out some of the designs and it will be for many modes of communications but must wait until this winter until I can have a little more time. Thanks for the nice letter and be looking for me on the bands. I plan to get on the low frequencies this week. The antenna is up and the transmitter is ready except for the relay and switching arrangement. See you there.

I have received many letters of late along this same line that shows someone is thinking along the same lines that have been worrying me.

"Dear Walt: What in the world has happened to ham radio? Or, maybe I should say, what IS happening to ham radio?"

"Wat! my RST only 579 Standby OM, let me retune my final. By the way OM wat rcvr u using? Guess the old band is going sour. Will say 73, 73 before you lose me.

"I built myself a nice little 20 watt 40 meter rig the other day. After three days carefully tuning the band and calling CQ, I worked a station in Ohio. He said I was the lowest power he had ever worked.

"I can remember when a pair of 807s was king of the band. If you ran more than ten watts on two meters you were in the elite class.

"Remember when you wrote Santa Claus for a new 6L6 or a tuning condenser? Now it's Dear Santa, please bring me a new KW linear and a low-pass filter.

"Remember when you wrote a penny post card for a parts catalog? Now it's a nickel for an *equipment* catalog.

"Well, Walt my electric typewriter is getting warm so I better turn it off. See you on two meters when I get my new transceiver. My 522 blew a button by-pass so I am QRT. Sincerely, John."

This letter from John M. Risinger, W5ATT/2, 15 Bayview Lane, Flanders, L.I., New York, leads me



The neat novice station of Dale Darnall, WN8PUZ, 20 North Locust Street, Buckhannon, West Virginia should work lots of DX. Here he is studying for the general class license. Watch for him on the air.



James R. Hill, K6OZL is hearing lots of novice signals aboard ship many miles East of Madagascar Island. He will still be listening for you and hoping for reciprocal licensing in his part of the world. Thanks Jim.

down the lane of nostalgia (built my first radio in 1925). It is a good thing to remember yet few of us would trade our present for the past. That was part of the growing pains. The hams that build their own equipment are the ones contributing to the development of the new equipment and that is what causes the change. The fellow with money is always ready to pay somebody else to do his equipment over or build new gear. I guess this is part of the general scheme of things. Few lead, many follow, take your choice.

Just to add a little foreign flavor to the column this month I will print a letter from Kaj Stridell, SM5DAD, Box 2080, Norrkopings 2, Sweden.

"Dear Walt: I just want to take the opportunity to QSO you, too, as I am sending an envelope to the *CQ* magazine.

"I am and am not a novice, depending on how you look at it, but I love reading your column, for I feel I never get too old to learn: you always put gems of hints in your text.

"I want to stress a point which some ham (in Portugal, I think it was) wrote to you about some years ago. That is the fact that your magazine is being eagerly waited for each month all over the world. And in most parts of the world you *cannot* easily obtain U.S. made components, or if you can they cost several times what they would cost if made in the constructor's own country. Last week I had to pay \$2.65 for a TR switch to the Heathkit HW-30. I could have bought a European made one for 50¢ if I had not been in such a hurry. So please state in every description, the values along with the part numbers of the components used in all construction articles. DO PLEASE for we few foreigners that buy your magazine. I know that this is being done mostly in *CQ* but sometimes it is forgotten. This also applies to transistors, I know we have European (and Japanese) equivalents to most US types.

"Something I have been missing is a description on how to build a 6 VOLT transistorized power pack. I have seen plenty of information for 12 volt systems but I would like to know how to build a transformer for 6 volts from junk box parts and wind my own transformer.

"There is one other thing I would like to ask. Ham radio has more or less become a world wide fraternity where most of us can make ourselves more or less understood by using some sort of English language. The English language is very difficult for many peoples. Can you tell me how many amateurs there are who frequently use the international language, Esperanto? If you could find out and put it in a column later this year, put me at the top.

"73 and thanks for all your past and future nice articles. Kaj Stridell, SM5DAD."

This brings up many interesting angles to the hobby of amateur radio and I think this might solve the lingual difficulties if we either learn Esperanto and/or

[Continued on page 98]



the
USA-CA
PROGRAM

BY ED HOPPER,* W2GT

AN interesting story about County Hunting from the other side of the Atlantic, but first here is the data on USA-CA Awards issued. USA-CA-1500 Awards went to Fred, W1GF and Bob, K9WSL. W1GF also received all A-1 endorsement for his USA-CA-500 Award. "Jeep", W8RCJ/W1BUS earned USA-CA-1000 as did Bruce, WPE3EBF. Bruce is the 10th s.w.l. to receive a USA-CA Award but #1 from the 3rd district, and he is the 3rd s.w.l. to receive a USA-CA-1000 Award. Frank, WA6KHK received a USA-CA-500 Award endorsed all A-1 and Bruce, WP3EBF received a USA-CA-500 Award endorsed all 7 mc s.s.b. USA-CA-500 Awards, endorsed Mixed, went to Ronald, K1VTM, Carl, W1ZLX, David, K1ZND, Bill, K3LSP, Bob, K7QXG, David, W0EGC and to Rundy, K4ZA/K6ZA who has been doing a fine job of giving out some rare counties with his mobile operations. He was a tremendous help to Cliff, K9EAB our #1 USA-3079-CA holder. Rundy is also well known to the DX fraternity for his operations from many rare DX countries.

County Chasing From Czechoslovakia

By courtesy of "K.D.", W6DIX/7, here are some excerpts from a letter from Jindra, OK1CG to W2NWM, translation by W2NWM.

"My friend OK1SV is unhappy because he is no longer able to ham into the wee hours of the morning and sleep only four hours as before. As for myself, I haven't been on the air during night time for some five years now; not even in the evening, for I couldn't sleep then without taking a sleeping pill. That is why I embarked,

*103 Whittman St., Rochelle Park, New Jersey, 07662.

**SPECIAL USA-CA HONOR ROLL
TOP TWENTY-FIVE
COUNTY HUNTERS**

3079	K5SGJ	W5EHY
K9EAB	K5SGK	WA8EZW
3045	W0JWD	K8VSL
W0MCX	VE3-9301	K8YGU
3037	K8KOM	W9CMC
K8CIR	2410	W5NXF
2800	W0VFE	1905
WA9AJF	2335	W2JWK
2780	W8UPH	1877
K8IWI	2050	W9HAS/6
2515	K3LXN	1780
W0KZZ	2000	K4BAI
2500	K9UTI	1726
K4VOF		K0HUU

USA-CA HONOR ROLL

ALL 3079	1000	K1VTM	523
K9EAB	1	WA6KHK	524
	W8RCJ/W1BUS	K3SLP	525
	WPE3EBF	K1ZND	526
		W0EGC	527
1500		K7QXG	528
K9WSL	40	WPE3EBF	529
W1GF	41	K4ZA/K6ZA	530
	W1ZLX		

with all my remaining energy, on this Worked All California Counties project. W6's come in here usually between 5 and 8 A.M.; they used to, that is, before this sun-spot misery set in.

"I have accomplished the impossible, I made it, but eight years of concentrated effort, hundreds of airmail letters for skeds, thousands of listening hours, seem almost out of proportion. I am no diploma hunter, even though I am CHC 758, Hi. I was, so to speak, forced into that by WA6ATY who kept offering to arrange everything, including taking care of the expenses. He merely wanted me to send him the list of my diplomas, barely sufficient to make me eligible for membership. I kept ignoring the WACC, just as a lot of others. But one day I surveyed my W6 QSLs with the thought that, having that many of them, perhaps there wouldn't be too many missing counties after all. I was very surprised, when, talking to W6 hams, I learned that in twenty years only 59 California stations had qualified for that diploma, and only one non-Californian, W3FYS, and that the diploma was virtually unattainable for Europeans.


"It was then that I resolved to do a piece of work for the good name of the "OK" prefix. It was to be at the same time the "Swan Song" of my amateur career.

"Well, I succeeded, it was hard work, one of my greatest rewards was the write-up in *QST*. In my own country our *Amaterske Radio* glossed over it in just a few words.

"However, the long effort of working for the WACC was the most enjoyable period of my entire amateur activity; except, perhaps, for the days of my very beginnings. Once again I experienced moments of excitement and tension, met true ham spirit, sacrifice, comradeship, and a great love for the common cause. Long live



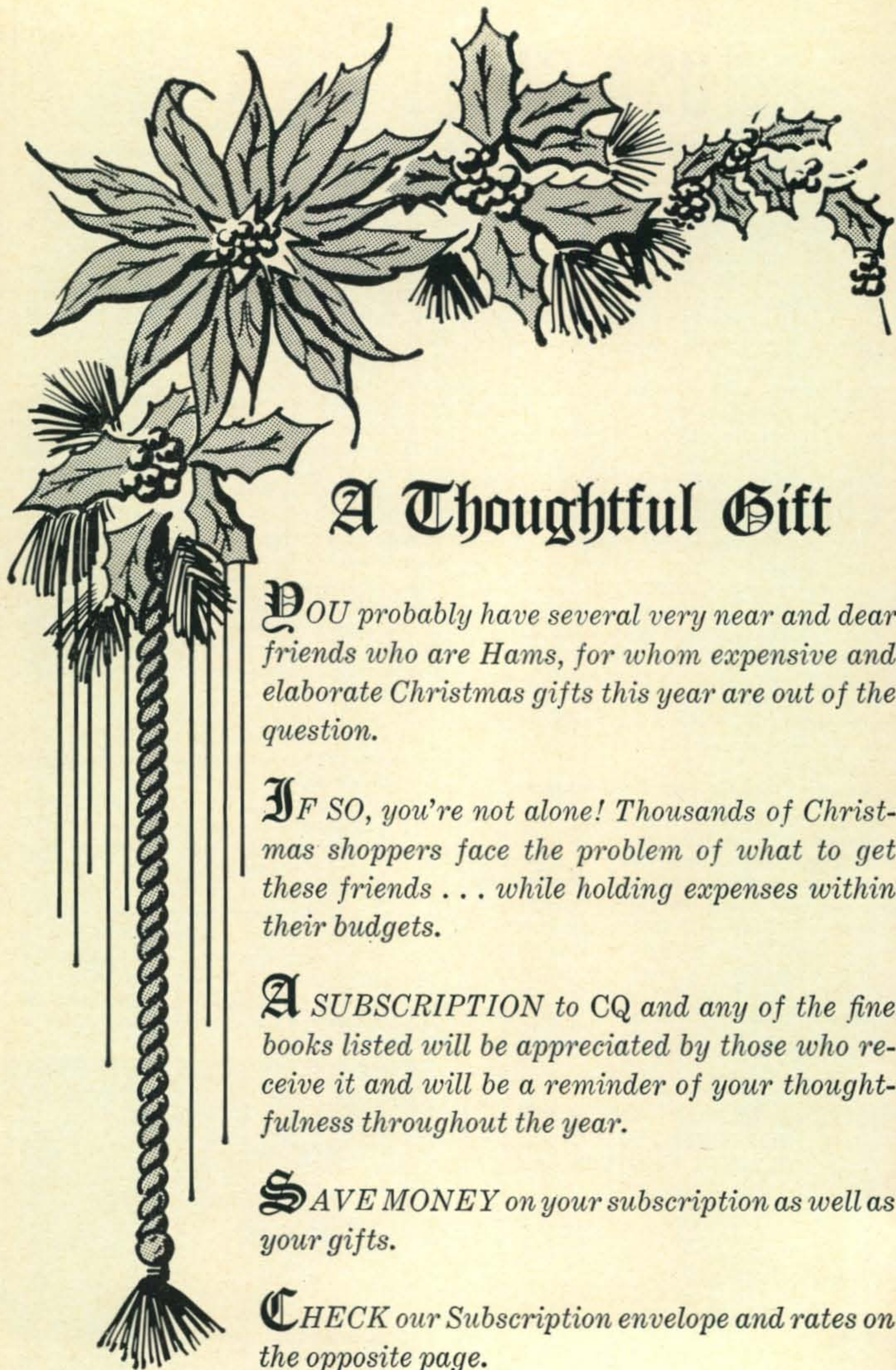"K.D.", W6DIX/7, who, since the death of his wife in 1961, has been traveling Colorado, New Mexico, Arizona, Utah and Nevada.



A Thoughtful Gift

YOU probably have several very near and dear friends who are Hams, for whom expensive and elaborate Christmas gifts this year are out of the question.

IF SO, you're not alone! Thousands of Christmas shoppers face the problem of what to get these friends . . . while holding expenses within their budgets.


A SUBSCRIPTION to CQ and any of the fine books listed will be appreciated by those who receive it and will be a reminder of your thoughtfulness throughout the year.

SAVE MONEY on your subscription as well as your gifts.

CHECK our Subscription envelope and rates on the opposite page.



WORKED ALL CORNHUSKERS

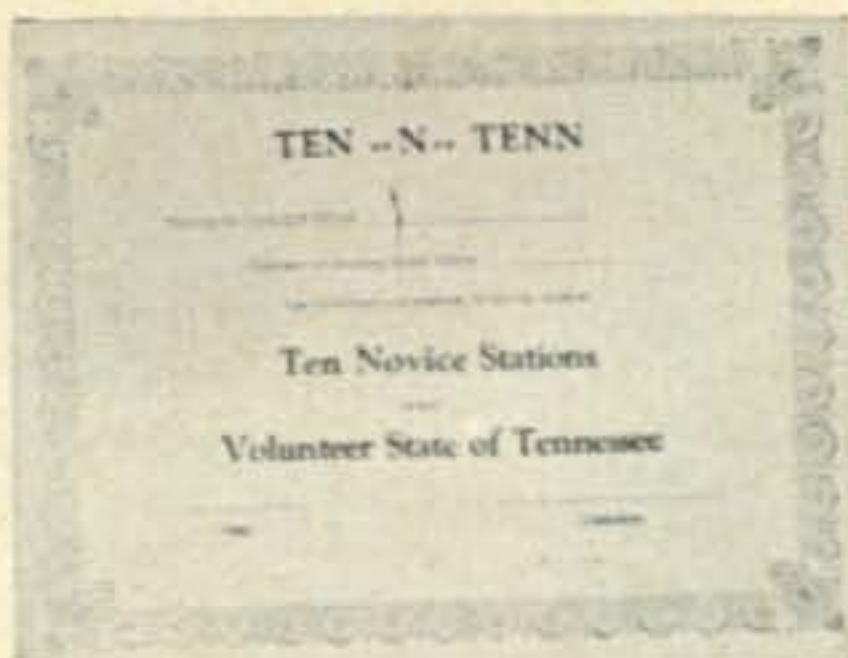

TEN-N-TENN AWARD



WORKED ALL JACKSON AWARD

the amateurs of California! Just for my sake they would travel to amateur-forsaken counties high in the mountains, even in wintertime; always kept their schedules and followed my progress. They kept me informed about planned expeditions into the mountains, and would arrange for me schedules with other counties. But I owe my greatest gratitude to W6DIX, who with his gear makes a yearly round-trip through all the difficult counties, thus putting them on the map. His XYL used to accompany him. Aside from the frequent QSOs, we also maintained correspondence. One day, however, the unexpected news of his wife's death left me stunned and virtually incapable of replying. His planned round-trip for the year was canceled, I was aware of his great sorrow. He wrote that he was off the air, not able to do anything, nevertheless he considered it his duty to inform me about the situation so I wouldn't keep the schedules in vain, I need not say more.

I could go on and on, even the final moments of my WACC effort were highly dramatic. Now all I needed was one last county—Plumas—and the conditions were getting worse every year. I began giving up hope of ever completing the job, but then, after a long interval, W6BIL called me again and asked how far I had progressed with the WACC. I explained my situation to him, but as he was replying the band suddenly changed and he faded out. All I gathered was that he was suggesting some sort of schedule to me. At that moment I again saw a ray of hope. We exchanged letters and he offered to make a trip to Plumas County on a Saturday and should conditions be unfavorable, we would try again the following week. He also told me that a very active YL, K6ENL, had married and had moved to Plumas County. W6BIL was going to visit her there but didn't think she would be on the air yet.

Well, the conditions were hopeless! It was

nerve-wracking. Later on I could merely hear some very weak W6 working him, but I could not hear W6BIL. In spite of all that, I continued watching the band every day. Then all of a sudden, on Tuesday, on a band that was practically dead, on 14,075 kc., there was a very faint station calling me, although I had not been transmitting, yes, calling me slowly and for a long time—I knew it could only be Plumas; but oh my nerves! Yes, it was K6ENL alright, readability 5 both ways but she was S4 and I was S6—neither of us could believe our ears. She was using only 120 watts and poor antenna and was unable to hear any other Europeans. She could hardly have realized how terribly important it was to this unknown ham who she did not know and would never meet.

I was overjoyed, my gratitude to W6BIL was immense. However, because of my poor English, I was incapable of expressing it adequately. I suffered literal physical pain as I was writing my letters of thanks to all. And, of course, it had to be a woman too, to furnish, in the twelfth hour, my last county. All this, and much more, would I have liked to write, through the medium of *CQ* and *QST*, to all amateurs of California in recognition of their wonderful spirit. However, even if I had been able to write it, it would have hardly rated publication." (*Editor—So we Ws think we have it tough—Hi . . . And here is the story in CQ, even if a little late. . .*)

Letters

JOE, W2JWK, writes: "Many of the boys on the net have expressed their delight at the prompt manner in which you issue the county certificates and their endorsements. Count me as a solid booster of *CQ's* county hunting venture.

Please remind the boys to check into the net on 7223 as activity has slackened and thus many of the mobiles are not checking into the net with new counties. I devote as much time as possible at net control, but sometimes after a ten or fifteen minute QRZ, nothing shows up. Perhaps with the advent of the fall season,



NEW ENGLAND CHC CHAPTER #32 AWARD



HILLBILLY AWARD



AMATEUR RADIO COMMUNICATIONS AWARD



Car and trailer of W6DIX/7 at Tonopah, Nevada.

the boys will take to their operating chairs more frequently. Once again my sincere thanks Ed for your zeal and promptness. Keep up the good work, 73."

ED, W9HAS/6, writes: "I have been inactive lately since I have been in the Air Force, but I do keep up with the USA-CA Program and the County Hunters through your column in *CQ*. I hope to become active again in the near future and try to pick up some of these western counties I could not get from the home QTH. Your efforts and interest in the county hunter program are much appreciated."

CARL, W0KZZ, writes: "I am in the process of completing my book for the 2500 endorsement to my USA-CA Award, my confirmed counties stand at 2515."

"Keep up the very fine work of your *CQ* USA-CA Program column. We sure do enjoy it and it is the first thing we turn to when we open each new issue."

BOB, VE3ELL, writes: "Enjoy your column very much and have turned into an award hunter. I am retired and have complete knowledge of Canada and wish to volunteer my services to anyone who needs help on pin-pointing Canadian points in regards their counties. I would appreciate a self-addressed envelope (US stamps I can not use).

"Why oh why do the various organizations take so long with their awards? I have waited up to 2 months for some of them." (*Editor—May I suggest you send Bob an IRC to cover postage or a Canadian stamp? Write to him, Bob Lightfoot, VE3ELL, Box 352, Malton, Ontario, Canada.*)

LOUIS, K8IWI, writes: "Just a note to tell you how much I enjoy your monthly column in *CQ*. I always get a lot of pleasure from reading all the names and calls of the different hams who have earned USA-CA Awards."

"I am still busily engaged in county hunting but they come slow as I have gone quite high but I only run low power and have no beam."

Best regards Ed, and keep up the good work."

BOB, K9WSL, writes: "We enjoy your monthly column a great deal. Our county hunting is mostly a mobile operation and has made us many friends, both on and off the air. As a group, these people are FB, as I'm sure you realize."

"Tnx for your leadership and 73."

RALPH, WA0JNF, writes: "I have been enjoying your column this year and have been sort of a county hunter since I received my Novice license a little over a year ago. During this time I have been happy to give many county hunters a QSO with Vernon County Missouri on 40 and 20 c.w."

"I will sked anyone needing Vernon county on 80, 40 or 20 c.w. or on 75 or 40 fone."

"I would like to know just how rare is Vernon County and Delaware County in Oklahoma as I have a cousin there who could help. Perhaps I can also help if hunters would let me know of hard to get counties in South West Missouri and South East Kansas."

Write to WA0JNF, Ralph Porkorny, Box 406, Nevada, Missouri 64772.

Awards

Worked All Cornhuskers: The Lincoln Amateur Radio

Club, Inc., of Lincoln, Nebraska wishes to announce the creation of this new VHF certificate to help put Lincoln, Nebraska on the v.h.f. map. Rules are as follows:

- DX 6 meters—10 contacts with Lincoln amateurs.
- 2 meters— 6 contacts with Lincoln amateurs.
- Local 6 meters—15 contacts with Lincoln amateurs.
- 2 meters— 9 contacts with Lincoln amateurs.

No charge is made for the certificate, QSLs are not required. The certificate is retroactive to 1 January, 1965. Send list of stations worked to: Custodian, Cornhusker Award, Bernie J. Sasek, W0YOY, 3030 Shirley Court, Lincoln, Nebraska 68507.

Ten-N-Tenn Award: Sponsored by *The Tennessee Ham* to encourage contacts with Novice operator in the state of Tennessee. Any station may obtain this award by working and confirming contacts with 10 Novice stations in Tennessee. Send copy of log data verified by two others with sample of your QSL card to *The Tennessee Ham*, 612 Hogan Road, Nashville, Tennessee 37220. There is no charge but a large s.a.s.e. would be appreciated.

The New England CHC Chapter #32 Award is awarded for working members of the New England Chapter #32. Five classes: Class E for working 15 members; D for 30; C for 50; B for 75 and A for working 100 members. Elected officers count double if worked in year of office. GCR List and \$1.00 or 10 IRCs (DX) to Awards Chairman CHC Chapter #32. Henry Trepanier, K1PMJ, 31 Tame Buck Road, Wolcott, Connecticut 06716. TCR and MER apply. Send s.a.s.e. for membership list.

Hillbilly Award: This Honoray Hillbilly Radio Certificate sponsored by the Southwest Missouri Amateur Radio Club has been improved and the rules changed a little to make it available to more of a cross-section of hams. Work 5 Springfield, Missouri stations including one active club member station. No date limit. Send log information (QSL cards not required) and 50¢ to Hillbilly Award, SMARC, P. O. Box 291, Springfield, Missouri 65801. Present members are W0's AH, AIP, BPD, BVG, CGJ, CXF, CZD, FGS, FNN, FXU, HUI, ICW, IWT, KWZ, NHO, RZV, SZT, TE, VJC, WRQ, YWS. K0's BWE, HUU, IKZ (Honorary full member at K.C., Mo.), JPJ, KYM, LLJ, MXK, ZZH. WA0's BDS, DSK, FKI, GVH, GVJ, HWJ, IIK, JLL, JYX, KFQ, LPS, LRT. WN0's MAN, MAO.

Worked All Jackson Award, is sponsored by the Jackson Amateur Radio Club of Jackson, Mississippi and is awarded when the following conditions are met: Establish two way communications with stations in Jackson area as follows: For stations within continental U.S.—5 Jackson stations. For all others—1 Jackson station. Contacts must be made after 1 January, 1965. Send log data and \$1.00 to Custodian, Worked All Jackson Award, Ross Hutchinson, 270 Lea Circle, Jackson, Mississippi 39204. If desired, special note will be made of all SSB, CW or AM, as well as all on one band.

Amateur Radio Communications Award, is issued without cost by the CRES Amateur Radio & Electronics Club (Franklin County Civil Defense Affiliate) of Columbus, Ohio. Issued for QSOs with ten club members, QSLs are required. Since they have more than seventy licensed members plus a club station (WA8JVV), operators have an excellent opportunity of achieving this certificate and winning additional endorsements for each additional ten non-duplicate QSLs. Write to CRES Amateur Radio & Electronics Club, 6200 East Broad Street, Columbus, Ohio 43213.

Hope Santa Claus remembers each and every one of you and that you have all your wishes fulfilled, such as lots of new Awards and Certificates, much new equipment and needed QSLs, and how was your year?

73, Ed., W2GT

Fight BIRTH DEFECTS

Join MARCH OF DIMES



BY GEORGE JACOBS,* W3ASK


THE latest word from Project OSCAR Headquarters in Sunnyvale, Calif. is that OSCAR IV has a chance of being orbited some time in December. A deadline of November 15 has been set by NASA for delivery of the satellite package to launch officials, and an interesting race is on. At this writing, two satellites are being prepared for launching, by two different groups: The Project OSCAR Association is nearing completion of its 2-beacon package with output on 144 and 432 mc, with an outside chance that a 1296 mc beacon may also be aboard.

A second group, the Thompson-Ramo-Woolridge Radio Club also in southern California (including W6NLZ, K6OPZ and K8RVM/6) is also nearing completion of a rather exotic repeater-type package. The competition is keen, but friendly, and whichever package can be delivered by the deadline will be orbited as OSCAR IV.

Near-Synchronous Orbit

Present information indicates that OSCAR IV will be placed in a near-synchronous orbit over the equator, at an altitude of 18,200 nautical miles (21,000 statute miles) giving a view angle of 162° on the earth. That is, an area encompassing 162° of the earth's circumference at the equator, and nearly from pole-to-pole, will be within range of OSCAR IV.

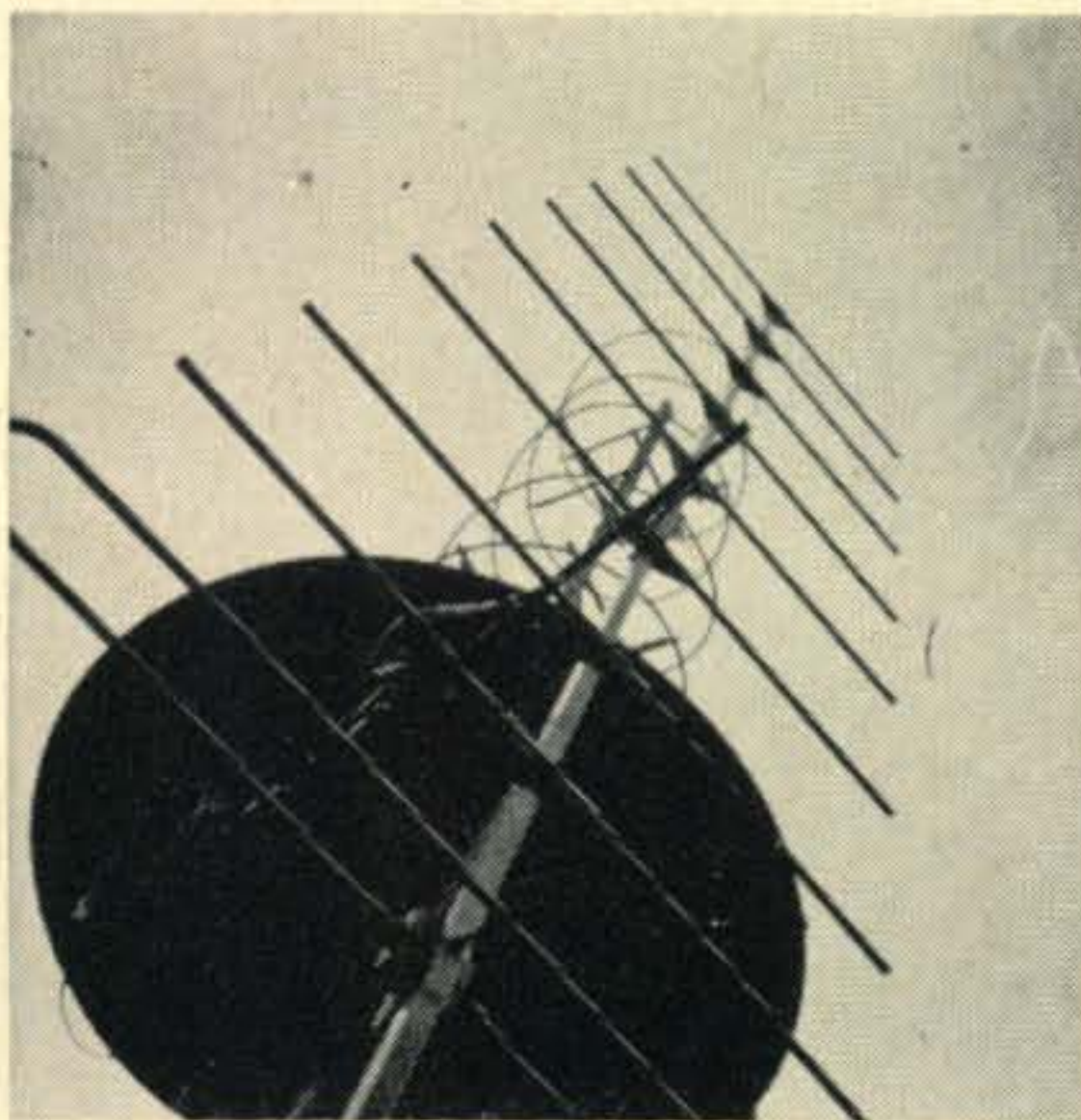*11307 Clara Street, Silver Springs, Md. 20902.



In Bonn, Germany, space-listener M. Dieter Oslender has copied signals from almost every satellite launched to date. Shown above are his parabolic, helical, and Yagi antennas that he plans to use for copying the OSCAR-4 satellite.

Table I—
Predicted OSCAR IV Visibility

Observer's Lat. (deg.)	Θ (deg.)	In Range		Out of Range	
		Hrs.	Min.	Hrs.	Min.
0	81.0	136	19	166	43
10	80.8	136	5	166	57
20	80.4	135	22	167	40
30	79.4	133	41	169	41
40	78.8	131	43	169	19
50	75.9	127	52	175	10
60	71.8	120	55	182	7
65	68.1	112	39	190	23
70	62.8	105	46	197	16
75	52.8	88	55	214	7
80	25.7	43	22	259	40
81	< 1.0		< 1	303	1

To use table: Find the difference between the observer's longitude and that of the satellite. If this difference is equal to or less than Θ for the observers latitude, the satellite is within range. If the observer's longitude is greater than the satellites, the satellite is East of the observer; if it is less, the Satellite is West. The times indicate the duration of range between aquisition and fadeout at the indicated latitude.

The position of the satellite, relative to a given point at the equator, will move Eastward at a rate of 27½° per day, giving a ham at the equator over 5 solid days of OSCAR coverage out of every 13 days! Nearly one half the surface area of the earth will be within range at all time!

The length of time the satellite will be visible decreases with increasing latitude; that is, the closer you are to the North or South Pole, the shorter will be the "view period." Table I shows the degrees and total hours of visibility for various latitudes, assuming an orbit of 18,200 nautical miles (21,000 statute miles) above the earth.

The Two Satellite Packages

The Project OSCAR satellite will be rather routine in its operation, with beacons on 144.05 and 432.15 mc transmitting the usual OSCAR HI telemetry. Time will dictate whether the 1296.45 mc beacon will be aboard. The TRW Radio Club's package, however, incorporates a number of techniques which are new to the OSCAR program.

The TRW translator will receive signals over a 10 kc bandwidth centered on 144.1 mc, and re-transmit them over a 10 kc segment centered on 431.8 mc with an output power of 3 watts.

To facilitate satellite tracking and ground equipment adjustment, a c.w. beacon will transmit through the repeater every 10 minutes for twelve seconds. The familiar OSCAR HI will then be transmitted for four seconds for identification purposes *only*, (no telemetry), and the "10+4" cycle will then repeat, giving a total beacon on-time of 32 seconds. The beacon frequency will be 432 mc.

The satellite will be tetrahedral in shape, (four



The display model of the first OSCAR satellite is still drawing considerable attention. Here the satellite is shown on exhibit recently in Cleveland, Ohio, where large crowds viewed it with amazement. (Photo by Damon).

sides), and will be solar powered.

Monitor W1AW for launch details, late orbit information, and information about which package has become OSCAR IV. Should OSCAR IV fail to orbit properly, the next opportunity for a piggyback launch will probably come some time in March, 1966.


Mariner-4 Shut Down

The radio-telemetry circuit between MARINER-4 and Earth was temporarily shut down by NASA on October 1, as the spacecraft's orbit around the sun carried it out of useful range. Since it was launched on November 28, 1964, MARINER-4 had transmitted to Earth nearly 50 million engineering and scientific measurements on the environment of interplanetary space and in the vicinity of Mars. It flew within 6200 miles of Mars on July 14, recording the first close-up pictures of the planet's surface.

The telemetry circuit was closed by a signal transmitted from a 100 kw transmitter at Gold-



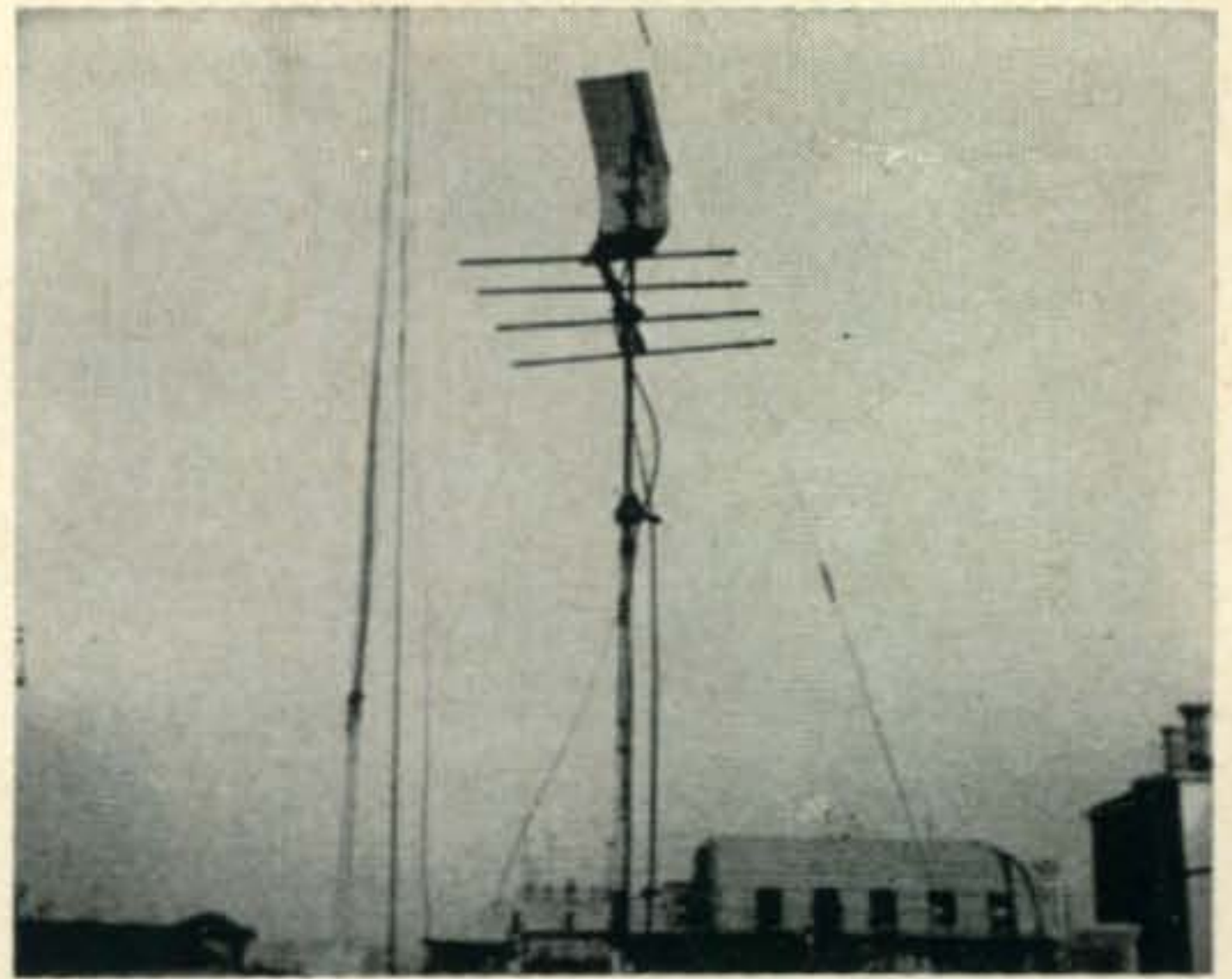Here's the man who put Spain on the space communications map. Ing. J. M. Cordova-Barreda, EA4AO of Madrid is shown at his home-built v.h.f. station used for OSCAR and meteor-scatter communications. EA4AO is anxiously awaiting the launch of OSCAR-4.



Radio pioneer Dr. Ing. Mario Santangeli, I1ER, of Milan, Italy, is standing by to copy OSCAR-4's signals. Above are Mario's 1290 mc corner-reflector and 432 mc Yagi.

stone, California, and beamed at the spacecraft nearly 191 million miles away. The signal switched the spacecraft's transmitter from the high-gain directional antenna used for telemetry transmission, to the omni-directional antenna which can be used only for tracking information.

The switch-over is only a temporary shut-down of the telemetry circuit between MARINER-4 and Earth. By mid-1967, the spacecraft's orbit around the Sun will again bring it close enough to Earth to attempt to resume telemetry contact, if the equipment aboard MARINER-4 is still operative.

G5RV Trophy

The G5RV trophy is a new award to be presented annually by the Radio Society of Great Britain to the British radio amateur who has contributed the most to amateur radio communications.

The first recipient of the G5RV trophy is Bill Browning, G2AOX, for his contributions in preparing information on orbital predictions for the OSCAR-3 satellite, and the sound technical advice and information freely given by him which enabled many radio amateurs to participate actively in the experiment.

The handsome trophy will be awarded to G2AOX at the RSGB's Annual General Meeting to be held in London on December 17. The congratulations of this column are also extended to G2AOX.

Bulletin

It has just been reported that an extremely large, unidentified, nearly spherical payload, led by eight smaller objects, has been sighted on a peculiar polar orbit, having a perigee at chimney-top level. Monitoring by radio amateurs and space-listeners in all areas of the world disclose odd-sounding transmissions over a wide range of frequencies, which are believed to be emanating from the larger object. The signals appear to be fully modulated by a husky, jovial voice, proclaiming, "Peace On Earth, Goodwill to Men—Merry Christmas to all, and to all a good night." 73, George, W3ASK



BYRON H. KRETZMAN,* W2JTP

RTTY Operating Frequencies

Nets centered on frequencies given; operation usually ± 10 kc on h.f.

80 meters	3620 kc
40 meters	7040 kc
40 meters (narrow shift)	7140 kc
20 meters	14,090 kc
15 meters	21,090 kc
6 meters	52.60 mc
2 meters	146.70 mc

AUTOMATIC-frequency-control (a.f.c.) for radioteletype reception is a very nice feature as it compensates, up to a point, for the *other* fellow's drift. It is an electronic method of varying the b.f.o. in the receiver in such a manner that it will maintain the *mark* tone within close enough tolerance to enable the converter, or terminal unit (TU), to make solid copy. The action can be so adjusted that control of the signal will be kept until the signal or the receiver drifts to the edge of the useful band-pass of the channel filters in the TU. (We are speaking in terms of an audio-type of TU, most common in usage.)

Modification of the station communications receiver is required, or at the minimum a connection to its i.f. amplifier. A completely "out-board" adapter must then be constructed, such as the one shown on page 157 of the *New RTTY Handbook*. Those of us who do not hesitate to dig into our receivers can just add a silicon diode, connected to act as a variable capacitive reactance, across the b.f.o. Figure 1 shows the simplicity of the hook-up. Of course the error-correcting voltage must come from some kind of discriminator that samples the *mark* tone.

The AN/FGC-1, Part VI Automatic Frequency Control

Most surplus AN/FGC-1 terminal units (RTTY Column, *CQ*, July '65) contain an a.f.c. panel which puts out the required error-correcting voltage for control of a reactance device connected across the receiver b.f.o. The old Press Wireless AN/FRR-3 and Wilcox CW-3D receivers contained a reactance tube for use with the a.f.c. panel of the AN/FGC-1. In these days

of solid-state devices, a silicon diode is used to perform the same function.

Figure 2 shows a simplified schematic diagram of the a.f.c. circuit. This circuit keeps the *mark* frequency within ± 50 cycles of its proper value of 2125 cycles. If this frequency deviates from 2125, a d.c. voltage appears in the output; which, when applied to the receiver reactance device, causes a compensating change in the b.f.o. frequency in the receiver(s). The *mark* frequency passes through the 2125 cycle filter to the control grid of tube V_2 where it is amplified. It is further amplified in tube V_3 . The output of V_3 contains two branches. In one branch a portion of the output passes through a 0.1 mf capacitor and a resistor network which impresses one-half of the output voltage on the plates of dual-diode V_4 . The plates of V_4 are biased about -23 volts by means of the 130-volt supply acting through a resistor network. If the peak voltage of the a.c. output of tube V_3 exceeds about 46 volts, tube V_4 conducts and pulses of current pass to ground through V_4 . As in similar a.v.c. circuits, the resulting current through the resistor network which is connected between the plates of V_4 and ground impresses a negative potential on the grid of V_2 thereby reducing its gain. Thus V_4 and its associated circuit acts as an automatic volume control and maintains the output of V_3 substantially constant with a peak voltage somewhat greater than 46 volts. A negative voltage is impressed upon the control grid of V_1 by the a.v.c. circuit, which is twice the value impressed on V_2 . When V_3 has its normal output, this potential is sufficient to cut off V_1 .

Should the radio frequency signal be so far from normal that the *mark* frequency falls outside of the 1600-2500 cycle pass band of the 2125 cycle filter, the high impedance of the filter then reduces the strength of the signal and prevents operation of the a.f.c. circuit. It is therefore necessary to by-pass the filter in order to develop an a.f.c. voltage. This is the function of V_1 .

When the *mark* falls outside of the filter pass-band, the output voltage of V_3 drops below its normal 46 volts and the bias to V_1 decreases,

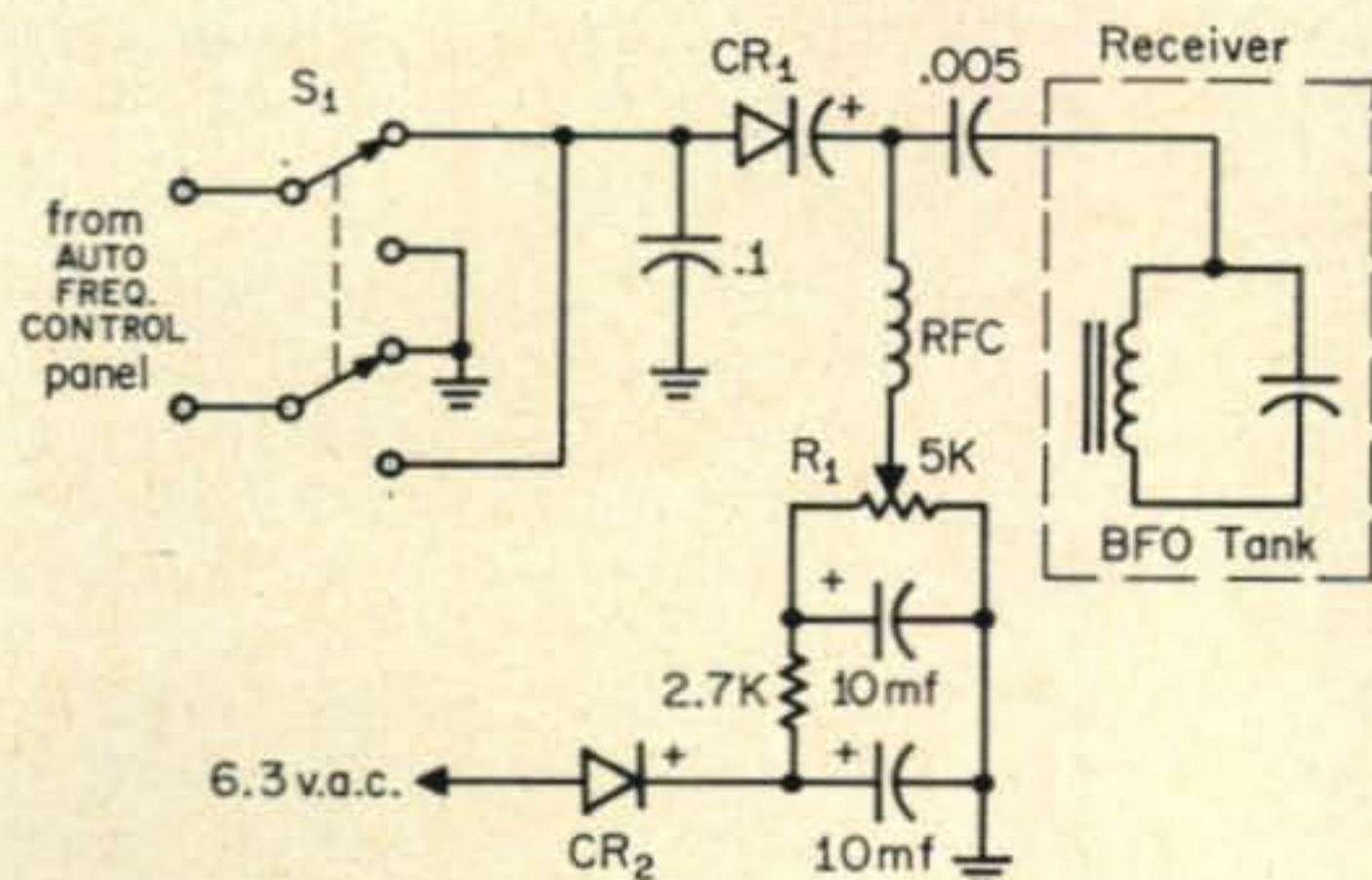


Fig. 1—Silicon diode reactance shift circuit. S_1 is a reversal switch. CR_1 is an International Rectifier Type 6.8SC20 Semicap, and CR_2 can be almost any type of diode. Adjust R_1 until a 1-volt d.c. input results in a 1000-cycle shift in the b.f.o. frequency.

*431 Woodbury Road, Huntington, N. Y. 11743.

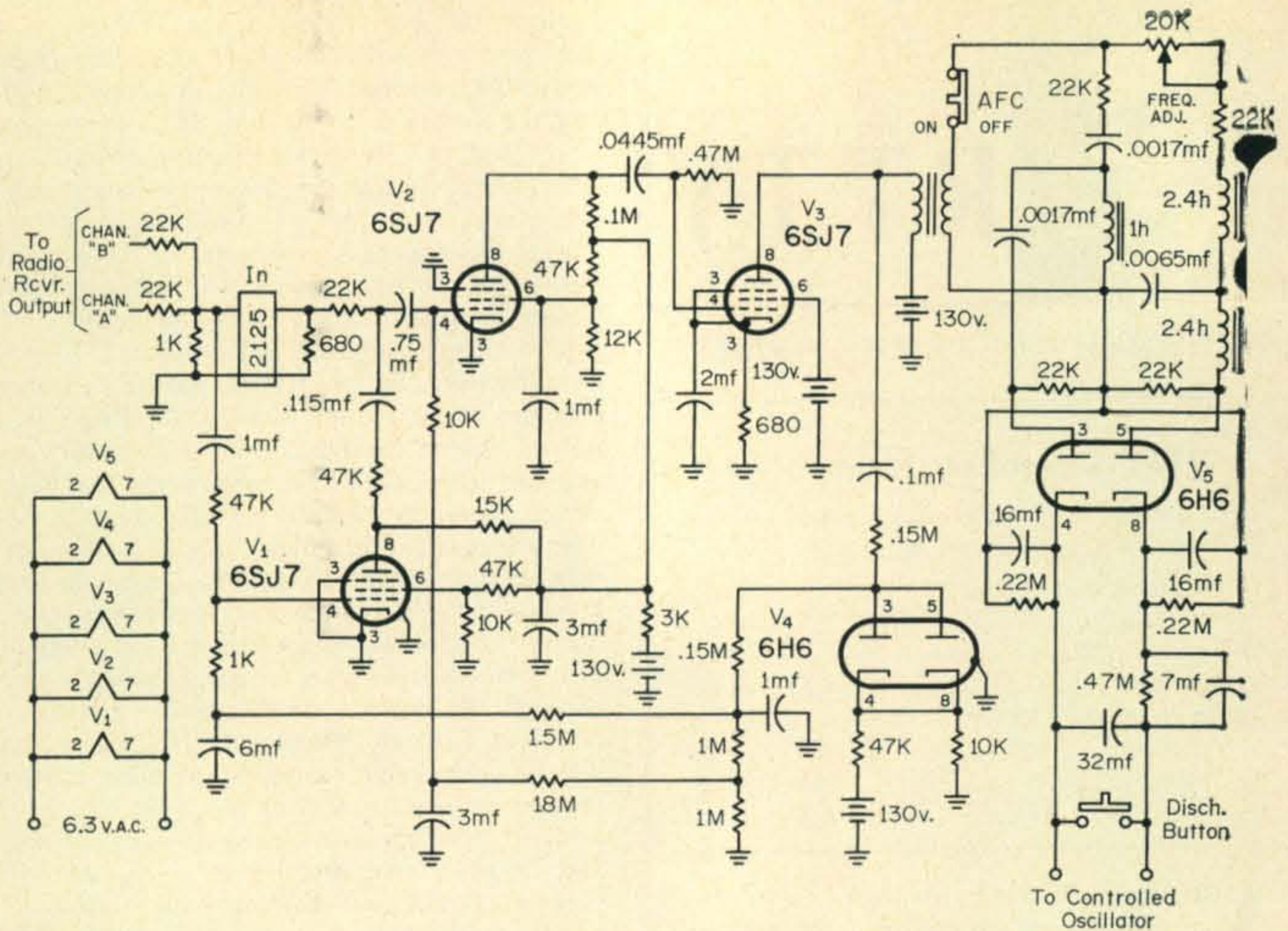


Fig. 2—Simplified schematic of automatic frequency control circuit.


allowing it to become operative. V_1 then becomes a by-pass for the filter and permits the developing of an a.f.c. voltage. This voltage acts continuously to bring the *mark* within the filter pass-band. When this is accomplished, V_1 is again disabled by the development of normal a.v.c. bias. The loss through V_1 when that stage is active is actually greater than the loss through the filter, so that the a.v.c. bias developed when the by-pass path is operative is less than normal and is not sufficient to disable V_1 until the *mark* comes within the pass-band of the filter. The time required to discharge the R-C circuit supplying a.v.c. bias to V_1 is about 10 seconds. This means that if a *sudden* frequency change in the order of several hundred cycles or more occurs during normal operation, approximately 10 seconds must elapse before the a.f.c. can restore the tuning.

The other output of V_3 is fed to a high-pass and a low-pass filter in parallel, which act as a discriminator. These filters are adjusted by the FREQ ADJ knob to have the same losses at 2125 cycles. The outputs of the two filters are rectified in V_5 . When the frequency is 2125 cycles, equal currents pass through the two diodes, so that no voltage exists across the output terminals. If the frequency is lower than 2125, it passes through the upper filter to the upper diode, whereas the lower filter allows little or no current in the lower diode. Thus the upper output terminal is positive in respect to the lower terminal. Similarly, if the frequency is higher than 2125, the lower terminal is positive with respect


to the upper. Since the latter is usually grounded (in the receiver), the upper terminal in this case is negative with respect to ground.

The error-correcting voltage is about ± 1 volt for a frequency departure of ± 40 cycles from 2125. The receiver reactance device in the original receivers was set up so that a control voltage of 1 volt caused a 1000 cycle change in the b.f.o. frequency, therefore the control voltage tends to increase to a value much greater than -1 volt. But, as it increases, the b.f.o. changes frequency in the direction to *decrease* the output frequency. When the control voltage reaches -1 volt, the output frequency will have decreased 1000 cycles, establishing equilibrium; and so the controlled frequency will remain 2165 cycles (2125 plus the 40 necessary to make a 1000-cycle correction).

[Continued on page 100]

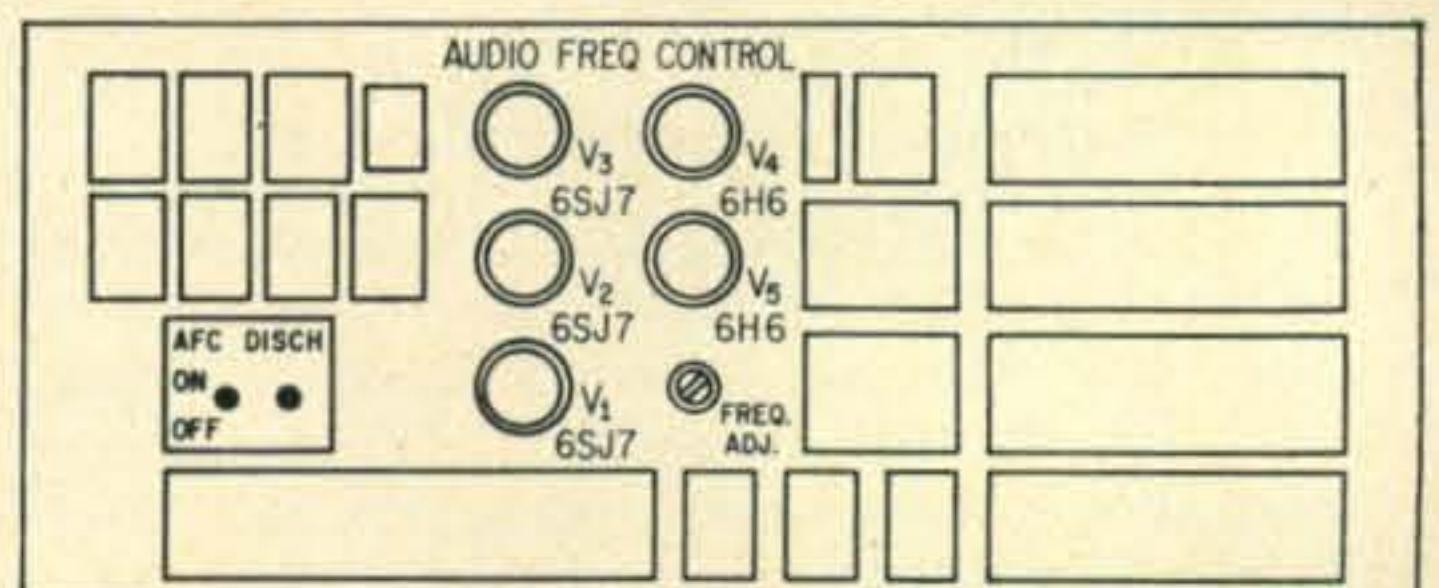

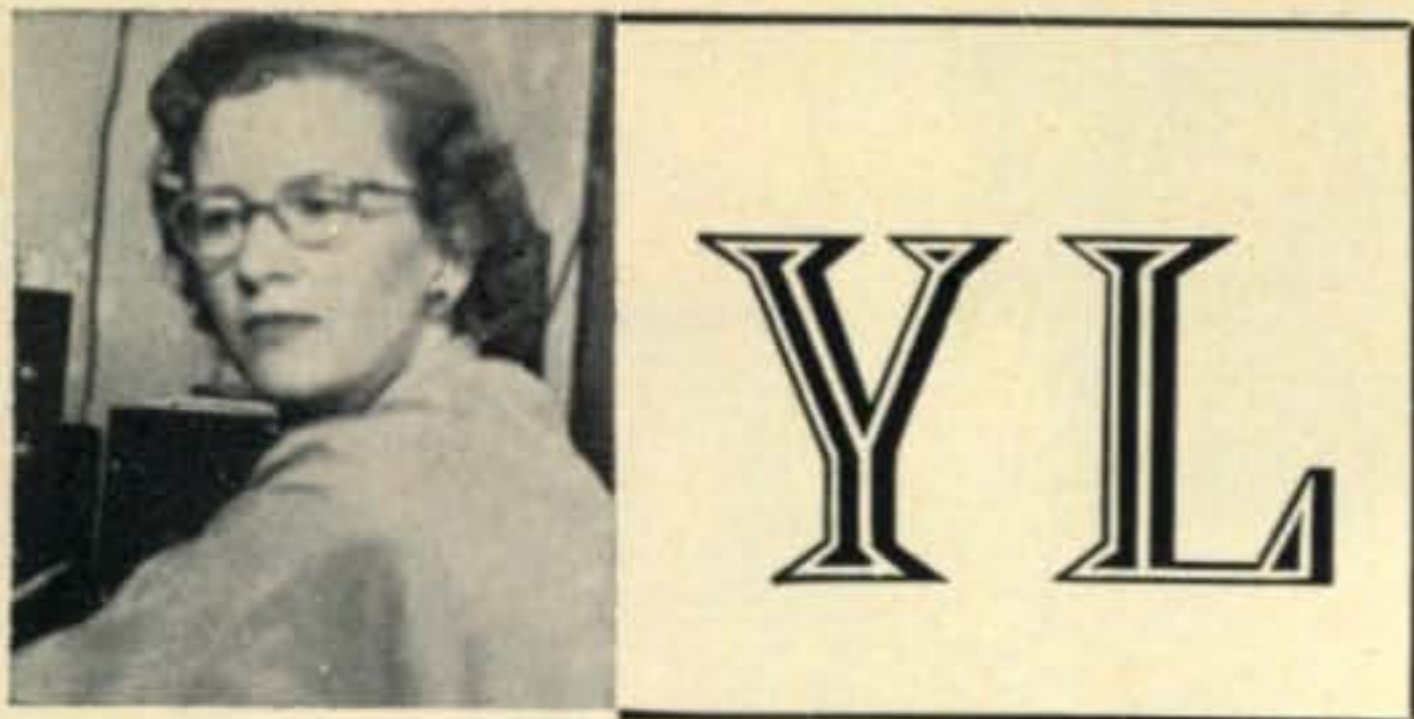Front view of the Automatic Frequency Control panel as it is installed in the AN/FGC-1, usually at the top of the rack, just under the bay terminal strips and fuse storage panel.



LOUISA B. SANDO,* W5RZJ

By vote of amateurs in the State of Idaho, W7GGV, Helen Maillet, of Pocatello, has been chosen "Idaho Ham of the Year" in recognition of her public service work, which has continued ever since she became licensed in 1956. As reported in October *CQ*, Helen served as Asst. Dir. of Communications for the Senior Girl Scout Roundup at Farragut, using call K7GS. Emergency work has included handling traffic during the Yellowstone earthquake in Aug. '59 and the eastern Idaho floods in '62 to '64.

For the past eight years W7GGV has been Radio Officer for District One (eastern Idaho), coordinating traffic from District to State and District to County. She is a faithful check-in on the Daily CD, Third Emergency and FARM nets and has been net mgr. and NCS of the latter. Helen served as SCM from '59 through '63. She is active in YL nets, is secretary of the LCLYL net, and was 7th D/C for YLRL in '61. Helen holds 55 certificates, is a member of CHC and custodian of Chap. 33/73 "Eyewink" membership certificate.

W7GGV may be found on 80 through 10 meters and she also operates a Heath 2-er for local CD work. Gear includes a Viking II and SX 101 and she has a Swan 400 for s.s.b. Antennas include a Hornet tri-band beam, dipoles for 40 and 80 and a 2-meter ground plane. OM is "Pop," K7CXP, and they have one daughter.

Congratulations, Helen, on this well-deserved honor! According to *Ham Hill News*, which announced Helen's selection, a bronze cup goes with the tribute.

*4417 Eleventh St., N.W., Albuquerque, New Mexico 87107.



KØZSQ, Val Eldridge, net mgr. of the Colorado Weather Net.

Colorado Wx Net

Tnx to Kayla, WØHJL, for sending us a copy of the FB feature article in *The Denver Post's* "Empire Magazine" for July 11, '65, describing ham participation in the Colorado Weather Net. Started some ten years ago by Bob, WØNVU, after the Purgatoire River flooded Trinidad, it has grown from 10 members to 45, and is in operation six days a week. Wx instruments are read about 6 a.m. and between 6:30 and 7:30 the information is passed on the net to WAØBAD, WAØBXR, KØZSQ or WØZFU who phone it to the Wx Bureau at the Denver Airport. Here reports are sent via teletype to area radio & TV stations and on AP wires. Weather patterns are made at the Bureau using reports from areas where there are no official weather stations, and small planes especially depend on the reports of the net.

YLs mentioned in the article were Val, KØZSQ, at Commerce City, who is net manager, and Ann, WØWZN, at Palmer Lake. When the disastrous storm and flooding hit Palmer Lake in June, Ann and her jr. YL, Charline, immediately contacted Civil Defense Hq. in Denver and Colorado Springs, and the Air Force Academy sent equipment and personnel to assist the 300 motorists stranded on the highway. The YLs remained at their mobile rig for 8 hours until land-line communications were restored, and worked another 16 hours to relay message re the safety of Palmer Lake residents.

Ann got into ham radio via her son Norman, who became KØDNP in '59. When he left for college she got tired of dusting the unused rig so got her own license. A year ago Charline, a sophomore and science major at Southern Colo. State College at Pueblo, got her call, WAØLDU. Ann joined the wx net in '60 and since then has transmitted about 1500 wx reports.


Val, KØZSQ, licensed five years ago, started checking into the Wx Net in '62. Besides being net mgr. she is NCS two days a week. Val holds sectional, regional and area net certificates for Colorado Hi Noon Net, Twelfth Region and Pacific Area. She prefers c.w.—holds 25 CPC—



Members of BAYLARC at the San Mateo County Fair operating WA6YBE (County Civilian Defense station) on Aug. 8, '65. In 12 hours the YLs handled 86 pieces of traffic and explained the use of ham radio in CD operation. L. to r., K6USC, WA6OGK, WA6PKP, WA6PJJ, WB6GID, K6HIW, WA6ALK, W6BDE.

POWERMAKER

300 Watts
for
\$49.95

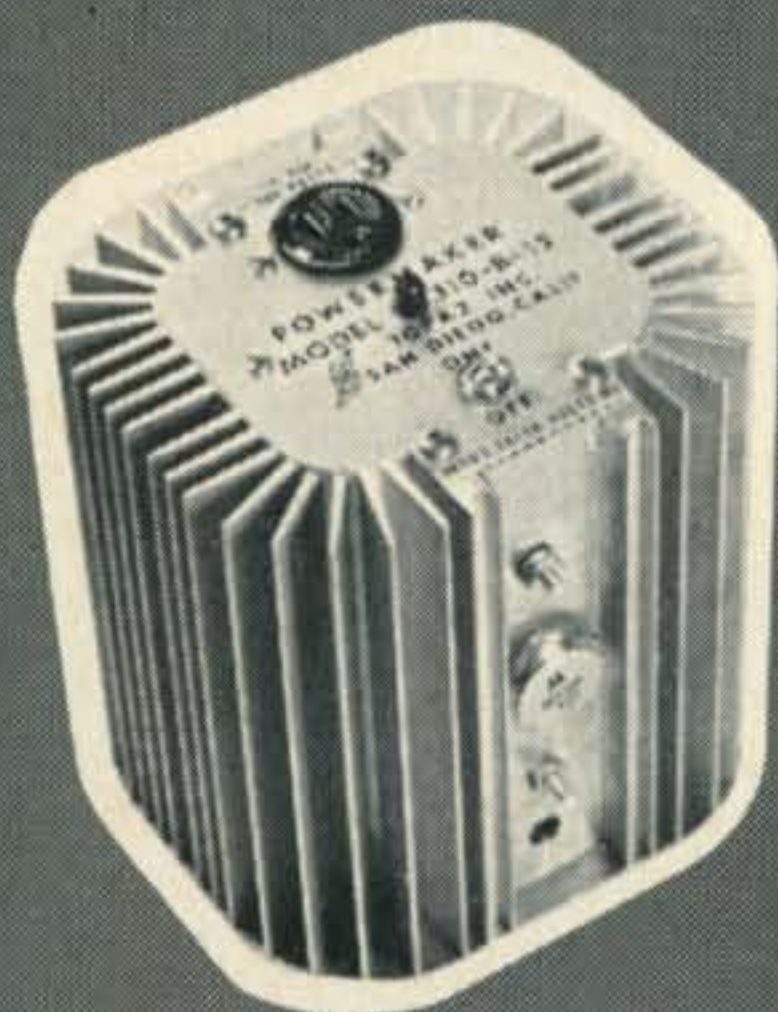

Changes 12
Volt Battery
Power to 60
Cycle AC Power

All Transistorized—Light, Compact, Rugged—Easily Installed

Runs T.V., Lights, Recorders, Public Address,
Tools, etc. In Your Auto, Trailer, Camper or Boat

Order From Your Dealer or Direct From Manufacturer
Shipping in U.S.A. \$2.50 Calif. Res. Add \$2.00 Tax



TOPAZ INCORPORATED

3800 HOUSTON STREET
SAN DIEGO, CALIF. 92110

For further information, check number 53, on page 106

EASY TO LEARN CODE

It is easy and pleasant to learn or increase speed the modern way—with an Instructograph Code Teacher. Excellent for the beginner or advanced student. A quick, practical and dependable method. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready, no QRM. Beats having someone send to you.



ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for full particulars and convenient rental plans.

INSTRUCTOGRAPH COMPANY

4711 SHERIDAN RD., CHICAGO 40, ILL.
4700 Crenshaw Blvd., Los Angeles 43, Calif.

For further information, check number 54, on page 106

"HOW TO MAKE MONEY IN Mobile Radio Maintenance"

AUTHORITATIVE GUIDEBOOK
ABOUT THE BOOM IN TWO-WAY MOBILE-RADIO.
GIVES FACTS, FIGURES, PAY RATES.
WRITE TODAY!

FREE



LAMPKIN LABORATORIES, INC. Electronic Div. BRADENTON, FLA.

NOW! A SSB TRIBAND TCVR KIT FOR ONLY \$179.95



NEW **EICO** 753
IN STOCK AT
HENRY RADIO

211 North Main Street

Butler, Missouri



WØWZN, Ann Meck, (right) with her daughter Charline, WAØLDU, handled emergency traffic at Palmer Lake following the disastrous floods in Colorado in June.

and enjoys building as well as operating. She has second radiophone license and is studying for first.

Val also holds RACES license and helps her OM on his C.D. programs as State Radio Officer. His call is KØDCW and his Dad's is KØPGQ. Val's oldest son is WAØGCM and her younger one is interested, and both boys hold commercial tickets. Top of the list of Val's other hobbies are her four grandchildren!

Other YLs checking into the Colo. Wx Net include WØVLS, Eleanor, and KØLCZ, Hazel.

1965 Midwest YL Convention

Members of LARK (Ladies Amateur Radio Klub) are sponsoring the 1966 Midwest YL Convention, with W9SJR, Bernice, as chairman. It will be held May 13-15, 1966 at the Flying Carpet Motor Inn at Rosemont, Ill. Registration is \$2 to April 1; thereafter \$2.50. Tickets available from K9TRP, Diane Price, 6123 N. Rockwell, Chicago, Ill. 60645.

Here and There

LARK elected these officers for '65-'66: Pres. K9IWR; V.P., K9EMP; secy, K9FHM; treas., WA9CCP; P/C, K9ZWV; Novice Rep., WA9ABG; editor of *Pinfeathers*, K9TGK.

Recently elected officers for WAYLARC: Pres., W3RXJ, Irene; V.P., W3CDQ, Liz; secy, WN4VLI, Brooke; treas., W3UTR, Meg; exec. member, W3UXU, Betty; rep. to Foundation for Amateur Radio, K4LMB, Ethel.

Calling "CQ YL" . . .

It's getting toward that "gift-giving time" again. Why not tell your OM you'd like a copy of "CQ YL" (or give *him* a copy), or get one for a friend or DX pal? "CQ YL" is the one and only book about the YLs. With the addition of several supplements in the years since it was published, the book is up to date through 1965 YLRL officers, and the addition of two entire new chapters brings it current through all the YLRL Conventions held to date. Order copies from W5RZJ (QTH at head of column); price \$3, postage paid.

Happy Holidays and all best wishes for 1966!

33—W5RZJ

A gift from **HARVEY**... no finer way to say Merry Christmas!




ELECTRO-VOICE MICROPHONES MODEL 676: Dynamic Cardioid with revolutionary backbone—cancels sound from back of mike. **\$60.00 net**


MODEL 600E: Mobile dynamic mike shaped for comfort. Ideal for SSB and AM transmission. **\$23.40 net**



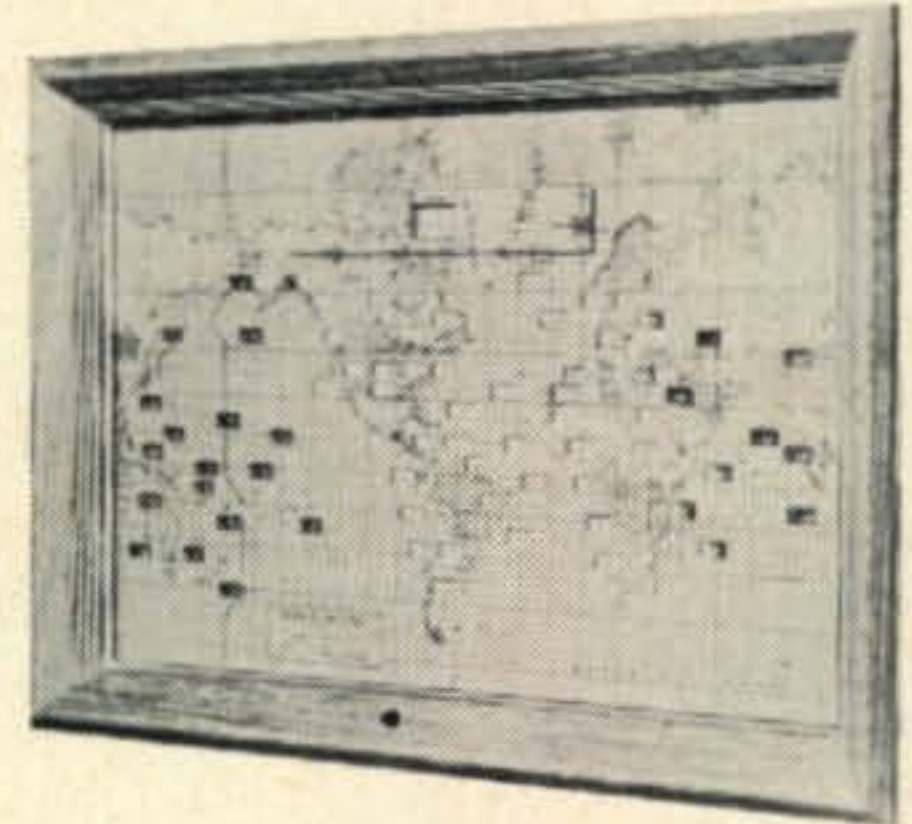
SUPEREX MODEL AP-S HEADPHONES Extra-high sensitivity for weak signals and hard-to-read stations; 600-ohm or 4-ohm impedance. Crisp reproduction, free of distortion. **\$24.95**



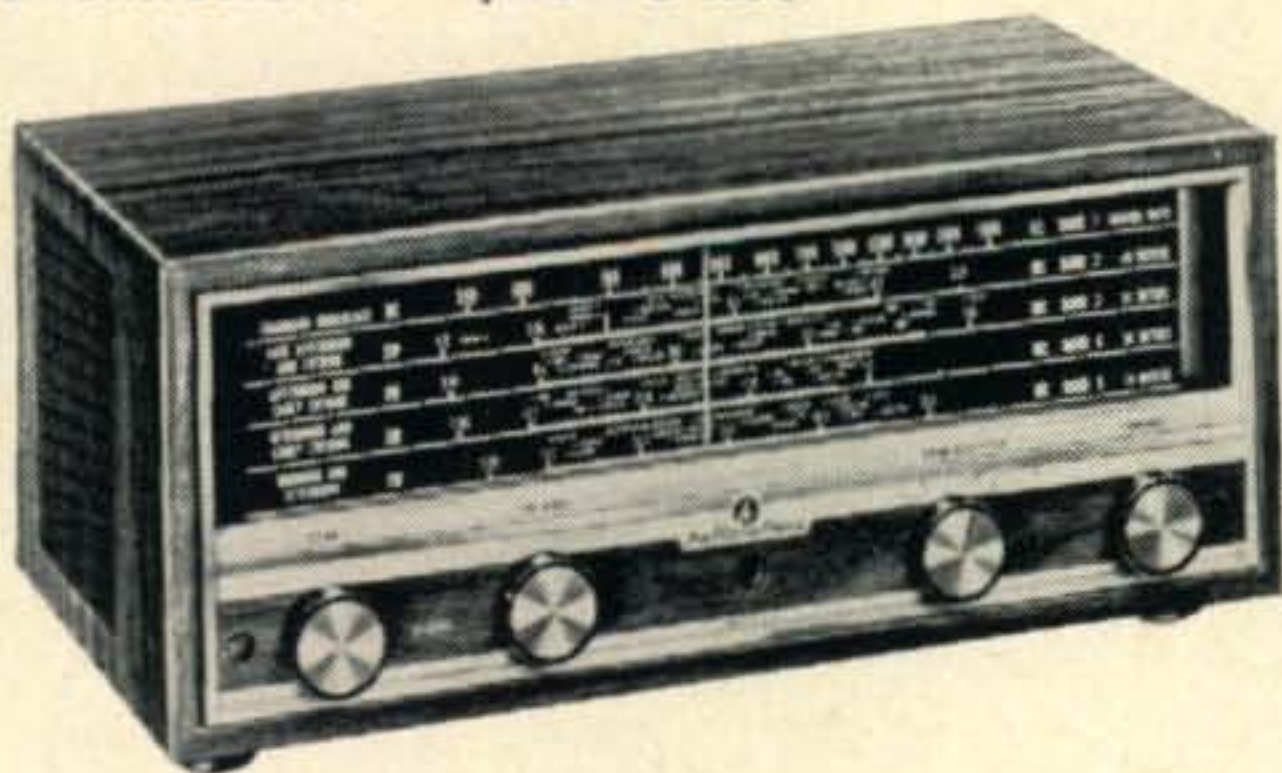WORLD TIME ELECTRIC WALL CLOCK Useful full-color map clock of the world with continuous correct Standard Time in 70 different cities and in every time zone. **\$49.95**



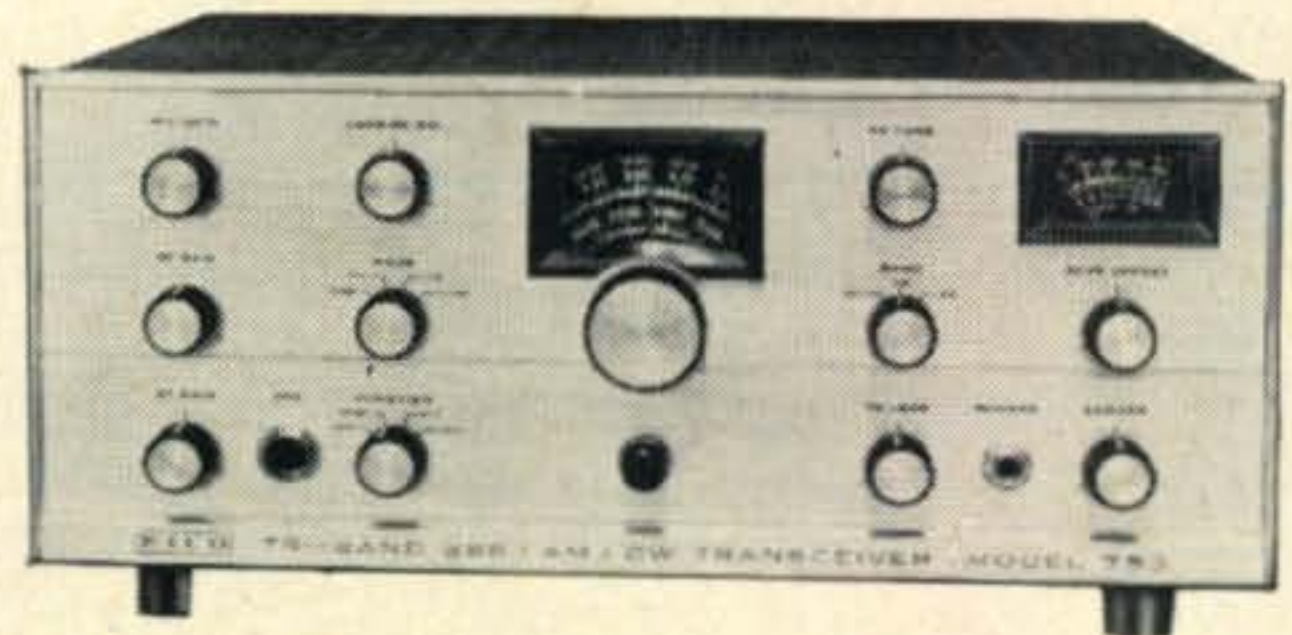HALLICRAFTERS S-200 "LEGIONNAIRE" 5-band short wave receiver offering foreign broadcast in 4 segments plus standard broadcast. Sensational new S-P-R-E-A-D tuning for effortless, hairline tuning. **\$59.95**



EICO TRI BAND SSB/AM/CW TRANSCEIVER KIT Eico presents the finest sideband rig kit available. High level dynamic ALC. Automatic carrier level adjustment on CW & AW. 180 watts on all modes. Receiver offset tuning. **\$179.95**

What to give a ham is answered in many ways at Harvey Radio — New York's leading ham center. Here you'll find all famous national brands of amateur radio equipment, parts and accessories — ideal for Christmas giving. Our experienced staff — all qualified hams themselves — will help you in making the right selection to fit your gift specifications. Backed by over 38 years in sales and service of ham equipment, we guarantee satisfaction and performance on everything you buy. Remember, if a ham is on your gift list, there is no finer way to say Merry Christmas than with a gift from Harvey's.

— Elliot Berelson, WA2HDP



HARVEY RADIO CO., INC. OUR **38TH** YEAR

103 W. 43rd St. / N.Y., N.Y. 10036 / (212) JU 2-1500
60 Crossways Park West / Syosset, L.I., N.Y. 11797 / (516) WA 1-8700
(Subsidiary) Federal Electronics, Inc. / Vestal Parkway, Vestal, N.Y. / (607) Pioneer 8-8211

For further information, check number 40, on page 106

Feeding Linears [from page 53]

The usual tricks of changing link turns and adding a capacitor in series or parallel in cut and try method as shown in fig. 3 will solve your problem.

Adjusting the linear is the real key to success and will try your ingenuity. You will really have to forget your old class C experience and try a new bag of tricks. The ordinary ham isn't the proud possessor of a scope so he has to do the job without one. To do a really good job, one should use a scope. One thing that really is a must, is some sort of output power measuring device², because in your tune-up you will find that the highest input current doesn't necessarily mean highest output. Figure 4 shows such a device that can be hung on the antenna. Notice that there is a power dividing network to reduce the output voltage for use on the vertical plates of a scope.

Another necessary gadget is a dummy load. There are several good loads on the market at reasonable prices. However, the old light bulbs still do a pretty good job.

If you have no scope and cannot borrow one, then proceed as follows: Tune up the exciter for proper excitation to the final. You can hang your handy dandy power measuring device on this unit too if you desire. (See fig. 5.) Now put the power output measuring device on the final and adjust coupling to feedline. Be sure the final amplifier tuning is set for maximum output at proper plate dissipation at resonance. If the coupling is increased, the d.c. input goes up but the output remains constant or even decreases. The point of maximum output for maximum input current is the proper adjustment for the linear amplifier. Now that you have reached this point, you must check to see if your amplifier flat-tops. This means you have exceeded the dissipation of the tube and hence, any output above this is just lost power. In addition this produces thumping or shot type interference on the band. There is a simple way to check for this condition; vary the amount of carrier insertion from your exciter (note the power output meter) until you reach a point where more carrier insertion gives you no rise in plate current and power output. This is really the proper adjustment. Listen on your receiver (without antenna) and get checks on the air. If OK, you are in business.

Scoping

If you are the proud possessor of a scope, use the set-up in fig. 5. The correct way to adjust a linear amplifier is with a scope and a two tone oscillator. Anyone who owns a scope we will assume knows how to operate it. The adjustments of your transmitter are not any more difficult than without a scope—and as a matter of fact, the procedure you follow is exactly the same. All the scope does for you is to show you how you are adjusted and enables you to

²Chapin, W., "The Transmitter Tune-Up Box," *CQ*, November 1964, P. 47.

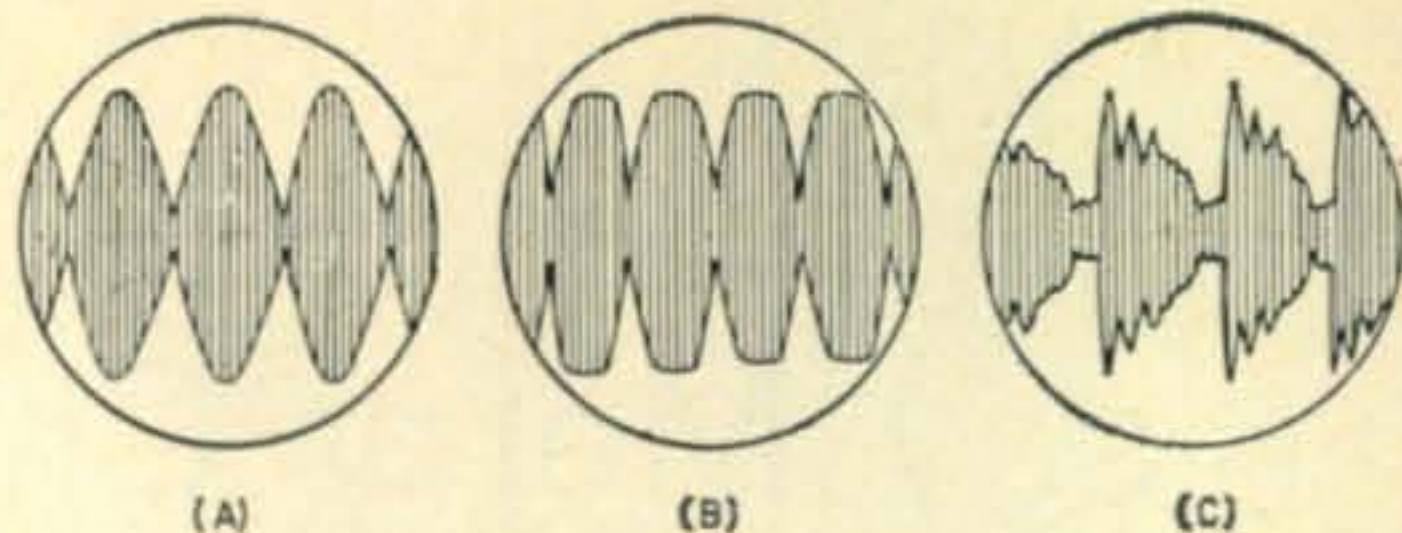


Fig. 6—Various two tone test patterns show linear amplifier performance clearly. (A) shows a proper two tone test pattern. (B) indicates flat topping while (C) might be a typical voice pattern.

see what adjustments do to clarify the problem. A two-tone test is useful in checking the linearity of the transmitter. Figure 6A is a properly adjusted two-tone test pattern and 6B shows flat topping or distortion. If you use some sort of audio compression, you will be able to see the benefits by using it on voice—removing and checking results. Where you have several linear amplifiers, you may have to back up from the final to check on problem areas. Figures 6B and C are typical patterns. Other patterns will show other problems such as parasitics, etc.

Linear amplifiers are very useful beasts when properly used and tamed. They are easy to abuse—and once you have yours adjusted, you will have to operate it carefully to avoid fouling up the bands with broad signals and shot type interference. ■

RTTY A-Z [from page 39]

a power supply. The simplest thing to do is use one's local loop power source, since the set requires a maximum of about 25 ma. The test set contains six basic electrical circuits. It will be recalled that, at 60 w.p.m. and a baud rate of 45.45, a signal of approximately 23 c.p.s. is created. One of the circuits, (fig. 105) is an oscillator that produces a 20 c.p.s. signal. The circuit used two W.E. type 255-A polar relays, S_1 and S_2 , to accomplish this. These are the two relays located in the left hand compartment. Naturally, these two relays must be in proper adjustment in order for the oscillator circuit to function properly. There is an oscillator circuit that produces a 10 c.p.s. signal which is similar to that of fig. 105.


The schematic diagram of the test set circuit for determining the bias of a relay under test is shown in fig. 106.

The Oscillator Circuit

The 20 cycle oscillator circuit is shown in fig. 105. The frequency of the circuit is determined from the series-resonate circuit composed of inductor L_1 and the bank of capacitors C_2 , C_3 , C_4 , C_5 and C_6 . This resonant circuit is shock excited from the action of polar relays S_1 and S_2 .

Polar relays S_1 and S_2 , in fig. 105, must be operating properly before the test set can be used to test other polar relays, or as a source of alternating current signals. This can prove to be a sticky problem unless one has two properly adjusted Western Electric Type 255-A relays to

Meet the NEW PR Z-9C Crystal

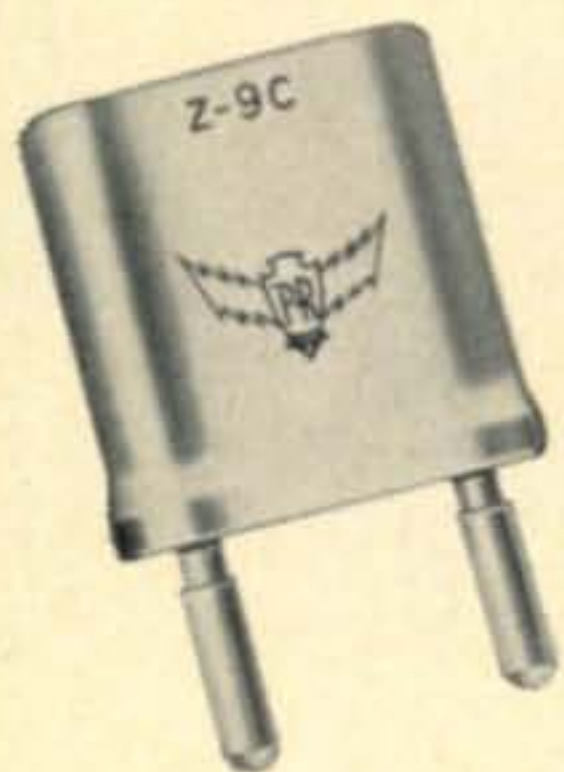

This sleek new model makes an instant hit everywhere. Smaller in size, saves space. Hermetically sealed. Stable, long-lasting, stands up under maximum crystal currents. High activity and power output.

PR Z-9C—AMATEUR TYPE—FUNDAMENTAL. Pin spacing, .486"; pin diameter, .093"; height above pins, 3/4"; width, 3/4"; depth, 5/16". Calibrated with a load of 32 mmfd. Frequency ranges in Kcs.: 1750 to 2000 (160M); 3500 to 4000 (80M); 7000 to 7425 (40M); 8000 to 8222 (2M); and 8334 to 9000 (6M).

Calibrated ± 500 cycles . . . \$2.95 Net


EVERY PR CRYSTAL IS UNCONDITIONALLY GUARANTEED

PETERSEN RADIO CO., INC. 2800 WEST BROADWAY
COUNCIL BLUFFS, IOWA

For further information, check number 49, on page 106

New SOLID STATE DEVICES

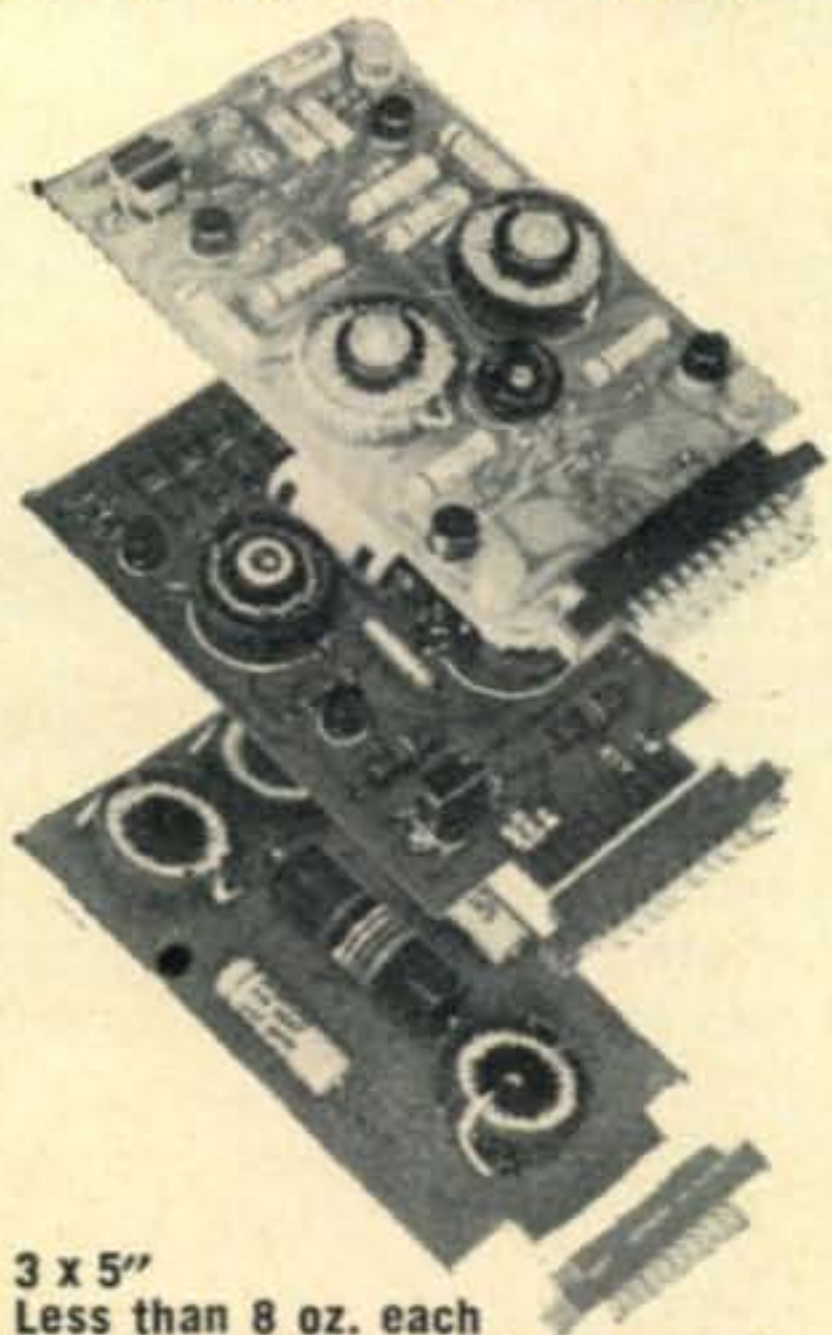FOR RECEPTION AND TRANSMISSION OF RTTY SIGNALS



3 x 5"
Less than 8 oz. each
Complete with matching connectors
postpaid USA

W2JAV DEMODULATOR Completely solid state radio teleprinter demodulator employing seven transistors and four diodes. Input impedance is 600 ohms and can be driven from a communications receiver or an AFSK. Will operate with input signal less than 50mv. Unit requires external polar relay and a 8 to 9 Vdc supply @ 50ma. W/instructions. **KIT \$19.95**

W2JAV AFSK UNIT Completely solid state unit employing two transistors and three diodes. Uses standard 850 CPS shift. Other shifts available. Adjustable output level from 0 to better than 200 mv terminated in 600 ohms. Oscillator is Zener diode regulated and accuracy is $\pm 1\%$ or better. Requires 8 to 9 Vdc @ 5-10 ma. **ASSEMBLED AND TESTED \$24.95**

W2JAV BAND PASS FILTER This unit will pass the band of frequencies from 2kc to 3 kc with little or no attenuation. It will severely attenuate those frequencies falling outside the pass band. When properly terminated in 600 ohms, the response is flat (within 1db) over the pass band. **ASSEMBLED AND TESTED \$7.50**

Tele Type Sync Motors, excellent condition **\$7.50***

*Shipping wt. 20 lbs., please include sufficient postage

The W2JAV Demodulator is also available factory assembled, tested and guaranteed. **\$29.95** Also printed circuit board only with schematic diagram, **\$2.95**. Sorry AFSK and Band Pass Filter are not available in kit form.

ESSCO

ELECTRONIC SURPLUS SALES CO.
"RTTY Specialists"
324 Arch Street, Camden, N.J. 08102

Phone: (609)
365-6171

For further information, check number 50, on page 106

**HANDS FREE
"STM MOBILER"
"SHOULDER TALK"**



FOOT SWITCH OR VOX CONTROLLED

- "no encumbering earphones"
- "Beamed AUDIO"
- "Controlled Magnetic Mike"
- PLUGS INTO SWAN - NATIONAL - COLLINS HALLICRAFTER - DRAKE - GALAXY - TRANS-COM ETC.

AMATEUR NET \$29.95

(foot switch and harness optional)

ORDER FROM YOUR DEALER OR:

**MARCO ELECTRONIC
PRODUCTS, INC.**

Box 158, Sonoma, Calif. • Phone 707-996-7722

For further information, check number 35, on page 106

ALL BAND TRAP ANTENNA!



Reduces interference and Noise on All Makes Short Wave Receivers. Makes World Wide Reception Stronger. Clearer on All Bands!

For ALL Amateur Transmitters. Guaranteed for 600 Watts AM 1200SSB Pi-Net or Link Feed. Light, Neat, Weatherproof.

Complete as shown total length 102 ft. with 96 ft. of 72ohm balanced twinline. Hi-impact molded resonant traps. (Wt. 3 oz. 1" x 5" long). You just tune to desired band for beamlike results. Excellent for ALL world-wide short-wave receivers and amateur transmitters. For NOVICE AND ALL CLASS AMATEURS! NO EXTRA TUNERS OR GADGETS NEEDED! Eliminates 5 separate antennas with excellent performance guaranteed. Inconspicuous for Fussy Neighborhoods! NO HAYWIRE HOUSE APPEARANCE! EASY INSTALLATION! Complete Instructions. 75-40-20-15-10 meter bands. Complete\$15.95
40-20-15-10 meter. 54-ft. (best for swl's). Complete\$14.95

SEND ONLY \$3.00 (cash, ck., mo) and pay postman balance COD plus postage on arrival or send full price for postpaid delivery. Free information on other all band antennas. 160-6 meters. etc. Available only from

WESTERN RADIO • AC-12 • Kearney, Nebraska

RTTY From A to Z [from page 90]

start with. The test set is equipped with a 100-0-100 milliammeter, as shown in fig. 67. This meter should vibrate near its zero position, making equal excursions to either side of this point when switch K_6 is put in the respective "dots high" and "dots low" positions. This is an indication that polar relays S_1 and S_2 are in proper adjustment. If none of one's relays can pass this test, then one must be able to borrow two properly adjusted relays or face the task of first properly adjusting two relays without the use of the test set. One might be inclined to ask at this point, "If this can be done, then what is

the point of obtaining an I-193-C Test Set in the first place?" Actually, the test set would be of some value under such circumstances, since one could plug in the relay, which is being adjusted, in socket S_1 or S_2 from time to time as it is being adjusted in order to check its operation. One should probably find or properly adjust a relay for socket S_1 first. The set may be used as a source of a.c. to test other RTTY gear after relays S_1 and S_2 are functioning properly.

I-193-C Test Set Summary

There are numerous individual circuits in the I-193-C Test Set manual, such as the circuits shown in figs. 105 and 106. Space does not permit the reproduction of all of those circuits here, nor does space permit a further discussion of their functions. As previously mentioned, one of the important functions of the test set is in the determination and adjustment of polar relay sensitivity. This and the other functions are adequately covered with numerous circuits and pictures in the 98 page manual.

It is hoped that the data given here has given the reader sufficient information to realize the value of this test set to any RTTY shack. The subject of distortion, some of its causes, methods and devices used in connection with its measurement have been covered. Next month the author will cover an RTTY distortion measuring set that is commercially available at a price that many amateur RTTY'ers can well afford.

[To be continued]

2 KW on 2 [from page 45]

Screen and plate potentials are applied *simultaneously* and the grid bias is adjusted for a resting plate current of 250 milliamperes. A small amount of r.f. drive is applied to the amplifier and the grid and plate circuits brought to resonance. The link loading capacitor C_1 is adjusted for lowest s.w.r. on the coaxial line from the driver. Driving power is slowly increased, while dipping and loading the plate tank circuit. Plate loading and grid drive are juggled until the desired parameters outlined in the "Amplifier Operating Characteristics" (fig. 15) are achieved. Grid and screen currents are sensitive indicators of amplifier operation,⁶ and these, together with some form of r.f. output meter, will permit the operator to quickly adjust the amplifier for optimum operating parameters. For best linearity, the amplifier should be slightly overcoupled to the antenna so that the r.f. power output drops about two percent from maximum value at the point of proper loading. Under the two kilowatt p.e.p. rating, the amplifier will deliver 1200 watts to the antenna circuit, with a power gain of over 22 decibels. Intermodulation distortion products are low and the signal, when driven by a clean s.s.b. exciter is a pleasure to listen to. Neutralization, of course, is not required and the amplifier tunes up "just like on the d.c. bands." ■

⁶Meacham, D., "Understanding Tetrode Screen Current," *QST*, July 1961, p. 26.

CQ TECHNICAL BOOKS



CQ ANTHOLOGY I

We've looked back through the years 1945-1952 and assembled all in one place the articles that have made a lasting stir. The issues containing most of these articles have long ago been sold out and are unavailable.



ANTENNA ROUNDUP

A common denominator for all ham stations is the antenna. Here at last is the cream of antenna information packed into a 160 page book. Forty-seven information-packed articles that will dispel much of the mystery surrounding antennas.



CQ ANTHOLOGY II

Top favorite CQ articles from 1952 to 1959 . . . including some you may have missed . . . compiled into one new information-packed book! No more need to try to locate sold out back copies of CQ. This Anthology includes past articles of lasting interest to every amateur radio enthusiast. Over 250 pages of text. Over 75 different articles. A definite Must for your shack!



SIDEBAND HANDBOOK

Written by Don Stoner, W6TNS, who was almost one full year in the preparation of this terrific volume. This is **not a technical book**. It explains sideband, showing you how to get along with it . . . how to keep your rig working right . . . how to know when it isn't . . . and lots of how to build-it stuff gadgets, receiving adaptors, exciters, amplifiers.



VHF FOR THE RADIO AMATEUR

If you are, or are planning to be a VHF operator, you can't afford to be without this dynamic new handbook written especially for you. Filled from cover to cover with all new and original construction material presented so you can understand it. Written by Frank C. Jones, W6AJF, nationally acclaimed for his VHF pioneering.



SURPLUS SCHEMATICS

This is a book literally loaded with schematics for all the currently popular pieces of surplus gear. Most amateurs are well aware of the problems encountered in purchasing seemingly inexpensive surplus units, only to find that no schematic diagram is available. Trying to figure out the circuitry cold turkey can be many-times more difficult than the most involved puzzle, and purchasing a single instruction book can run as high as \$3.50.

CQ LICENSE GUIDE

212 pages of everything the Amateur must have to get his license and progress toward the general class ticket. Plus many additional pages of vital information for the ham operator.



THE NEW RTTY HANDBOOK

A treasury of vital and "hard to get" information. Loaded with equipment schematics, adjustment procedures, etc. A valuable asset to both the beginning and the experienced RTTY'er. Special section in getting started, all written by Byron Kretzman, a well known authority in the field. First printing sold out. Second printing on hand.



MOBILE HANDBOOK

This new Mobile Handbook by Bill Orr, W6SAI, has been getting raves from top experienced mobile operators. Written for advanced, as well as beginning mobile operators, much of this information cannot be found anywhere else. This is NOT a collection of reprints.



COWAN PUBLISHING CORP. Book Div.

14 Vanderventer Avenue
Port Washington, L.I., N.Y. 11050

CQ ANTHOLOGY I	\$2.00	<input type="checkbox"/>
CQ ANTHOLOGY II	3.00	<input type="checkbox"/>
ANTENNA ROUNDUP	3.00	<input type="checkbox"/>
SIDEBAND HANDBOOK	3.00	<input type="checkbox"/>
VHF FOR THE RADIO AMATEUR	3.50	<input type="checkbox"/>
SURPLUS SCHEMATICS	2.50	<input type="checkbox"/>
CQ LICENSE GUIDE	2.50	<input type="checkbox"/>
"NEW RTTY HANDBOOK"	3.95	<input type="checkbox"/>
MOBILE HANDBOOK	2.95	<input type="checkbox"/>
ELECTRONIC CIRCUITS HANDBOOK	3.00	<input type="checkbox"/>
SHOP & SHACK SHORTCUTS	3.95	<input type="checkbox"/>
SURPLUS CONVERSION HANDBOOK	3.00	<input type="checkbox"/>
UNLIGHTED GLOBE	19.95	<input type="checkbox"/>
ATLAS	15.00	<input type="checkbox"/>
CODE RECORD	3.50	<input type="checkbox"/>
REGULAR LOG SHEETS (100)	1.00	<input type="checkbox"/>
SSB LOG SHEETS (100)	1.00	<input type="checkbox"/>
HAM'S INTERPRETER	1.50	<input type="checkbox"/>
TVI HANDBOOK	1.75	<input type="checkbox"/>
BINDER—YEAR WANTED	4.00	<input type="checkbox"/>
DX ZONE MAP	3.00	<input type="checkbox"/>
DIODE SOURCE BOOK	2.50	<input type="checkbox"/>
USA-CA RECORD BOOK	1.25	<input type="checkbox"/>

*New York City and State residents must add sales tax applicable to your area.

SIRS: My check (money order) for \$ _____ is enclosed. Please send the following items to:

Name _____

Address _____

City _____ Zone _____ State _____

Seasons
Greetings
from
the
HUSTLER
Folks

NEW-TRONICS CORPORATION
"the home of originals"
3455 Vega Ave., Cleveland, Ohio 44113

For further information, check number 33, on page 106

HW 12-22-32 owners
Complete triband transceiver
conversion plans. p.p. \$10.00
(*New Tribander Manual 32 Pages)

Send to:
Tribander

Box 18, Queens Village Station, Jamaica, New York, 11429

QCWA

Quarter Century Wireless Association, Inc.

Licensed amateurs who held an amateur license 25
or more years ago are eligible for membership.

Entry Fee \$3.00 3 Years Dues \$5.00

Applications may be obtained from
A. J. Gironda, W2JE, Executive Secretary
1417 Stonybrook Avenue, Mamaroneck, N.Y.

LEARN CODE

**QUALIFY
FOR
EXTRA
CLASS
LICENSE**

Rentals
Available



Model A as illustrated.

\$4950

Model B identical to model A except
contains no tone source or speaker.

\$3950

AUTOMATIC TELEGRAPH KEYS CORPORATION
275 Madison Avenue, New York 10016

For further information, check number 34, on page 106

**CQ Reviews the Transcom SBT-3
Transceiver [from page 51]**

Construction

The construction, workmanship and layout must be seen to really be appreciated. All stages, except the final, are assembled and wired on printed-circuit boards which are those made to Mil Specs of glass-epoxy rather than the cheaper and less desirable synthetic-resin boards ordinarily used. All soldering on the boards has been neatly done by hand and there is no maze of tangled wires from the breakouts of the interconnecting wiring harness.

Another Mil Spec procedure we've not seen in ham gear is that the leads for the small glass diodes are looped once before they are inserted in the circuit board. This relieves strain on the glass bodies of the diodes and leaves additional lead length for dissipating heat during soldering. The loops also offer a convenient place for attaching a heat sink, such as a pair of long-nose pliers or tweezers, when soldering is being done.


Like the RECEIVER TRIM (preselector tune) and the LOAD control, the r.f., a.f. and mic gain controls are adjusted by thumb-wheels. Numerals appear on the face of each wheel for reference settings. Other controls have conventional knobs. If the carrier null should require readjustment at any time, it may be done with a screw driver through an access hole without removing the cabinet.

The v.f.o. dial is calibrated in 5 kc steps and is driven with a pinch drive that provides a very slow tuning rate of 40 knob revolutions to cover each band. On 80 and 20 one turn of the knob covers about 5 kc, on 40 it tunes about 2.5 kc per turn. The dial window has two hairlines; one is used for l.s.b. on 80 and 40, the other for u.s.b. on 20 meters. One thing that is lacking however, is a means for setting the hairline or the v.f.o. frequency for calibration purposes.

Phono-type jacks are used for the antenna and the speaker connections on the rear apron. A mic jack on the panel accommodates a 3-way phone plug (PL-068). The power-cable connector has split-forked prongs for positive and secure contact. The case has mounting feet for tilt-up positioning at fixed locations and a gimbal bracket is available for mobile installation.

Power Supply

Two types of power supplies are available; one for mobile use from a 12 v.d.c. *negative-ground* source; the other for fixed use with 117 v.a.c. and which has a built-in speaker and a console cabinet. With 12 v.d.c. operation only the Transcom d.c. power supply should be used because of the special filament voltage needed for the p.a. tubes. The size of the d.c. supply is only 4" x 6³/₄" x 6³/₄", making it feasible to mount behind the dash. The speaker in the a.c. supply is 4" x 6" and there is a relay with contacts for actuating a linear amplifier. Size of this unit is 4⁷/₈" x 7" x 8³/₄" (H.W.D.)

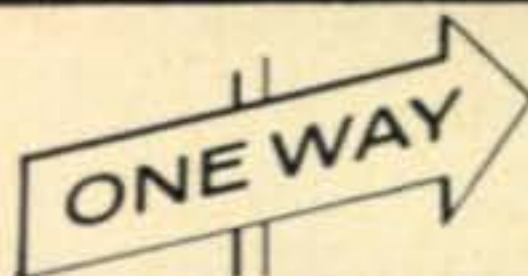

— to GREATER Efficiency!

NEW C-P BROADBAND **SUPER STATIONMASTER**[®] BASE STATION ANTENNA

Soon to be announced—the new, higher-performance broadband antenna by C-P. Communication Products Company, Marlboro, New Jersey—Tel. (201) 462-1880

DIVISION OF PHELPS DODGE ELECTRONIC PRODUCTS CORPORATION

For further information, check number 51, on page 106

NOW! A SSB TRIBAND TCVR KIT FOR ONLY \$179.95



NEW **EICO** 753

IN STOCK AT
ELECTRONICS, INC.

227 North Santa Fe

Salina, Kansas 67401

EUREKA!! TV CAMERA KITS, \$16.95 UP

Enjoy the fun of building your own "live" TV camera. Most of the components can be found right in your own junkbox. We furnish only the hard-to-locate parts and easy-to-follow construction plans. 6 different kits to choose from, including printed circuit models. Plans also available separately for \$3.00—refundable with later kit order.

Send 10c for comprehensive catalogue.

Box 396-C, ATV RESEARCH, South Sioux City, Nebr. 68776

EQUIPMENT WANTED • HIGHEST PRICES EVER!

TURN YOUR SURPLUS GEAR INTO READY CASH. WE ARE READY TO BUY NOW ANY OF THE ITEMS LISTED BELOW. CALL COLLECT NOW CY 9-0300 AND GET OUR HIGH BID. WE PAY "CASH-ON-THE-BARREL," AS WELL AS SHIPPING CHARGES.

NAVY: "TED" TRANSMITTERS, AN/SPN-5, 7, 11, 18 RADAR Raytheon 1400, 1, 2, 1500 (Pathfinder Radar) AN/URA-8B, AN/SPA-4, 8, 9

AN/GRC: 3, 4, 5, 6, 7, 8, 9, 10, 19, 26, 46, RT-66, 67, 68, 70, AM-65/GR, T-368C/URT, PP-109/GR, RT-196/PRC-6, PP-112/GR, RT-174/PRC-8, R-108/GR, RT-175/PRC-9, R-109/GR, RT-176/PRC-10, R-110/GR, T-217A/GRC-27, T-195/GR, R-278B/GRC-27, R-125/GR, MD-129A/GRC-27, T-235/GRC-10, SB-22/PT

AN/TRC-24: T-302A ΔB-332, R-417B, MK-133, PP-685A, MK-122, AM-912, ME-82, AM-913, 4, 5, J-532, AT-414, AM-682/TCC-3, TA-219/L

COMMERCIAL AIRCRAFT COMMUNICATONS:

COLLINS: 17L-4, 7, 51X-2, 3, 618s, t, 479S-3, 479T-2, 1882, 3, 4, 578D-1, 578X-1, WP-101, 618M-1, 51R-3, 6, 51V-2, 3, 4

ARC: R-30A, C-59A, RT-11A, (21A), C-67E, R-38A, T-27A, C-100A, T-25C, R-35A, R-34A, R-31A, L-11, IN-12, IN-13, & Test Gear.

INDICATORS: ID-250, 1, ID-387, ID-257, ID-307, ID-351, ID-1103, ID-637, ID-310, ETC.

ALL COLLINS IND. & CONTROLS

TEST EQUIPMENT, AN/URM-25, AN/URM-26, SG-1A/ARN, AN/URM-80, AN/URM-81, SG-2A/GRM, AN/URM-32, AN/ARM-8, SG-13/ARN, AN/URM-48, AN/ARM-25, AN/ARM-22, AN/ARM-65, AN/ARM-5, SG-66/ARM, AN/USM-26, AN/UPM-98, AN/UPM-99, AN/UPM-4A, MD-83A, AN/USM-16, AN/URM-43, AN/APM-66, AN/APM-68, TS-723/U, TS-757, AN/UPM-32, TV-7/U, TV-2/U, AN/PRM-10, ME-11/U, AN/ARM-51, TS-710, TS-330, TS-683, TS-382, TS-621, AN/URM-52, TS-510A, AN/URM-44, AN/PSM-6B, AN/URM-7, AN/TRM-3, SG-24/TRM, ME-6/U, AN/URM-14, AN/GPM-15, ME-30A/U, AN/USM-24, AN/USM-50, IP-111/ART-26, TS-407B, TS-403B, TS-186D, TS-505D, TS-537, SG-12A/U, ETC. WE ALSO BUY ALL H-P, BOONTON, ARC, MEASUREMENTS, TEKTRONICS, GR, PRD, FXR RFL, NARDA BIRD, BALLANTINE, ALFRED, ETC.

RECEIVERS: AN/APR-9, 13, 14, R-388/URR, R-388A, R-390, R-390A, R-391, R-392, R-274, R-220, SP-600JX, 51J-2, 3, 4, 51S-1, ETC.

AIRCRAFT EQUIPMENT: AN/ARC-34, 44, 38, 52, 58, 27, 73, 84, ETC., AN/ARN-14, 21, 59, 67, AN/APN-70, 81, 84, 22, AN/APS-20E, 81, 100, AND ALL RELATED ITEMS SUCH AS INDICATORS, RECEIVERS, IF STRIPS, ETC.

MISC.: 5HG SYNCHROS, 2K25 KLYSTRONS, 2K56 KLYSTRONS, VA-220C, D, E, VB-16A VIBRATORS, MEAS. 80 & 80 R, C-654B/APR CONTROL BOXES, TN-131/APR TUNING UNITS

**SPACE ELECTRONICS CO. • 4178 PARK AVENUE • CY 9-0300
BRONX, NEW YORK 10457**

For further information, check number 52, on page 106

NEW callbook

**HOT OFF
THE
PRESS!**



**Over 60% of listings
changed in only a year!**

- Great Circle Bearings
- Great Circle Charts
- Prefixes by Countries
- "Q" and "Z" Signals
- World Time Chart
- Int'l. Postal Rates

United States Listings... \$5.00
DX Listings..... 3.25

See your favorite dealer or order direct (add 25¢ for mailing)

RADIO AMATEURS REFERENCE LIBRARY OF MAPS — ORDER YOUR SET TODAY!



WORLD PREFIX MAP—Full color, 42" x 29", shows prefixes on each country... DX zones, time zones, cities, cross referenced tables.....postpaid \$1.00

RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD—from the center of the United States! Full color, 29" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles. postpaid \$1.00

UNITED STATES MAP—All 50 States with call areas, prefixes, DX and time zones, FCC frequency allocation chart. Plus interesting information on all 50 States. full color, 29" x 17".....postpaid 50¢

WORLD ATLAS—Only Atlas compiled for amateurs. Polar projection, six continents, prefixes on each country... full color, 16 pages.....postpaid \$1.50

Complete reference library of maps—set of 4 as listed above.....postpaid \$2.50

See your favorite dealer or order direct.

**WRITE FOR
FREE
BROCHURE!**

RADIO AMATEUR
callbook INC.
Dept. C, 4844 W. Fullerton Ave.
Chicago, Ill. 60639

Performance

The performance of the Transcom SBT-3 measured up to the given specifications. In addition, on receive the relative gain between each band was found to be within 2 db. A.g.c. figure-of-merit was 6 db a.f. output rise with an 80 db increase of r.f. input signal (10-100,000 μ v). On transmit, two-tone tests indicated excellent linearity.

Operationally the rig tunes up easily and quickly without any fuss. There appears to be no hesitancy when the p.a. tube filaments go on for transmit. The mic gain is ample and no matter how loud you yell into the mic, there is no flattopping caused by the p.a. itself. As with any a.l.c. system, the degree of compression can be overdone, so it must be handled discreetly, in which case on-the-air reports indicate a nice sounding signal.

On receive the a.f. quality is excellent and sounds very clean. The a.g.c. operates very smoothly without annoying pumping and the recovery following a transmission is instantaneous to the ear. The v.f.o. tuning is velvet smooth and the slow tuning is ideal for mobile work. There is some noticeable parallax between the hairline and the dial calibration markers, and the numerals for the 40-meter band are a little too high in the dial window for easy recognition in mobile use. However, after you get accustomed to it, it is not bothersome.

What we like most about the SBT-3 is that it requires little space, particularly in our compact car.

The Transcom SBT-3 Transceiver is priced at \$299.50. The SBA-3 a.c. power supply in console case with speaker is \$99.50. The SBD-3A mobile power supply is \$99.50. Mobile mounting kit costs \$3.50. The manufacturer is Transcom Electronics, Inc., 375 Hale Ave., Escondido, California 92025. —W2AEF

Contest Calendar [from page 67]

Once again we make the request of all of you who did any operating in our contest, to please send in your log, your few contacts might be the ones we need in our cross-checking. And don't underestimate your efforts, you might be a surprise winner.

The Christmas holiday season will soon be upon us, may yours be a very happy one, and may the New Year bring loads of new DX.

73 for now, Frank, W1WY

Propagation [from page 70]

South- ern	08-10 (1)* 10-14 (2)*	06-07 (2) 07-09 (3)	20-22 (1) 22-01 (2)	22-06 (1) 00-02 (1)†
Brazil, Argentina, Chile & Uru- guay	14-16 (1)* 06-07 (1) 07-12 (2) 12-14 (4) 14-15 (3) 15-17 (2) 17-18 (1)	09-10 (2) 10-14 (1) 14-16 (2) 16-18 (4) 18-19 (3) 19-22 (2) 22-06 (1)	01-04 (1)	
Mc- Murdo Sound, Antarc- tica	09-11 (1)* 06-07 (1) 07-10 (2) 10-14 (1) 14-16 (2) 16-19 (1)	06-07 (1) 07-09 (2) 09-12 (1) 16-18 (1) 18-19 (2) 19-21 (3) 21-23 (2) 23-03 (1)	21-00 (1) 00-02 (2) 02-05 (1)	Nil

THINK SMALL...



PERFORM BIG



GO GONSET Sidewinder 2 Mtr.

Here's coverage of the entire 2 meter band in four, one megacycle segments, operation on SSB, AM, or CW, and all packaged in a sharp little chassis only 9" wide, 5" high and 7 $\frac{1}{16}$ " deep.

The Gonset Sidewinder 2 meter transceiver is so compact that it's ideal for mobile as well as fixed station application. Separate 117 VAC and 12 V DC solid state power supplies snap on to the rear of chassis, or may be remotely positioned to simplify installation.

And look at some of the features Gonset builds in to provide top performance: complete push-to-talk operation, full 20 watts P.E.P. input, crystal lattice filtering, vernier tuning, transistors at primary stages, stabilized VFO and high-sensitivity reception.

SPECIFICATIONS *

Frequency Range	143.975 to 148.025 MC
Modes of Operation	AM, SSB, CW
Carrier Suppression	50 db
Sensitivity	0.5 μ v for 10 db $\frac{S+N}{N}$
Selectivity	3.1 KC crystal bandpass filter
Output impedance	50 ohms
Audio Output	2.5 watts into 3.2 ohms
Antenna Input Impedance	50 ohms unbalanced

NEW* - from GONSET

- Two new power amplifiers—model 903A for 2-meter, model 913A for 6-meter
- The GSB-201 Linear Amplifier—provides 2000 watts PEP(SSB) for 10 to 80 meter operation
- Gonset Sidewinder 6-meter SSB-AM-CW Transceiver with all the features of the 2-meter.

* Complete descriptions and specifications on all Gonset equipment is yours for the asking. Write to Dept. 73-7.

© 1965 GONSET, INC.

For further information, check number 31, on page 106



GONSET, INC.

A Subsidiary of *ESV* Ling Altec, Inc.

1515 South Manchester Avenue, Anaheim, California

BIG CATALOG

World's "BEST BUYS" in GOV'T. SURPLUS Electronic Equipment

TRANSFORMERS:

SECONDARY:	PRIMARY:	NO.:	PRICE:
4800 VCT 1.7 A	220 V 50-60 eye	5214	\$39.95
2000 VCT 500 MA	115 V 60 eye	5204	16.95
1600 VCT 400 MA	115 V 60 eye	8894	8.95
500 VCT 60 MA		8894	
840 VCT 255 MA	115 V 60 eye	223959	7.95
12.6 VCT 13 A / 5 V 4 A		223959	
2.5 V 10A	120 V 60 eye	9611.144	2.95
5.7 V 21.8 A	115 V 60 eye	7469149	6.95
6.6 V 10 A	115 V 60 eye	9T35Y158	2.95
12.8 VCT 20 A	120 V 60 eye	1043	8.95
24 VCT 6 A	115 V 60 eye	3992	4.95
36 V 12 A	115 V 60 eye	CON442	8.95
SOLA CONSTANT VOLTAGE Pri.: 190-250 V 60 eye.			
Sec.: 115 V 2000 VA		30M811	75.00

Prices F.O.B., Lima, O.; 25% Deposit on C.O.D.s; Minimum Order \$5.00. For CATALOG, send 25c (coins or stamps) & receive 50c credit on your order! Address Dept. CQ.

FAIR RADIO SALES
P.O. Box 1105 • LIMA, OHIO • 45802

Signal Lack "Punch"?

The model CPR Speech Compressor TRIPLES your average SSB output power; boosts your average AM modulation from 25% to 75%.

- NEW low noise circuits
- Uses internal battery
- Compression level switch
- For high and low impedance microphones
- Attack time .15 seconds; release time 1 to 3 seconds
- ONLY \$14.95



NOW AVAILABLE with PL68 or PL51 output for PTT circuit; input connectors supplied\$16.25

ALL FULLY WARRANTED . . . MONEY BACK GUARANTEE
Send for full description of our product line.

COMMUNICATION COMPONENTS COMPANY
P. O. Box 8721 Dept B Orlando, Florida 32806

For further information, check number 55, on page 106

SUB CARRIER DETECTOR



Add programs of commercial-free music thru your FM tuner. Detector, self-powered, plugs into multiplex output of tuner or easily wired into discriminator and permits reception of famous background music programs now transmitted as hidden programs on the FM broadcast band from coast to coast. Use with ANY FM tuner.

WIRED UNIT \$75.00
KIT, with pretuned coils, no alignment necessary \$49.50
crystal-controlled receivers available

MUSIC ASSOCIATED
65 Glenwood Road
Upper Montclair, New Jersey
phone 744-3387 area code 201

For further information, check number 56, on page 106

DX - - DX - - DX - - DX

SHORT PATH QSL-ing

New!! A Directory to help with your QSL-ing. Subscribe now to the "QSL Manager's Directory." Over 1000 QSL managers listed. Only \$2.00 per year (\$3.00 foreign) with FREE additions and corrections every three months. Send order to:

BOOKBINDER PUBLISHING CO.
DEPT. C, P.O. BOX 54222, TERMINAL ANNEX
LOS ANGELES, CALIF. 90054
(Sorry no CODs. Founder W6GSV.)

For further information, check number 57, on page 106

VHF [from page 73]

with the present antenna, but the echoes are now about 2 to 3 db out of the noise in a 60 cycle filter using the paramp with about 450 watts output from the transmitter. I can get slightly less feedline loss; I still think the feed for the dish can be improved for a couple of more db and the transmitter can put out more power. I also think I might be able to improve the receiver front-end a bit." Vic's letter goes on at great length. Shame we don't have space to run all of it.

METEOR SHOWER DATA

Night Showers

Quadrantids	Jan. 1-4
Lyrids	April 19-23
Aquarids	May 1-6
Aquarids	July 26-31
Perseids	Aug. 10-14
Giacobinids	Oct. 9
Orionids	Oct. 18-23
Leonids	Nov. 14-18
Geminids	Dec. 10-14

Daylight Showers

Cetids	May 19-21
Perseids	June 4-6
Arietids	June 8
Taurids	June 30-July 2

NOTE: Year-to-year variation is negligible, making this data chart an accurate two meter shower DX reference for any year.

Thirty

For co-columnist K2ZSQ, this month's report marks my 61st VHF column for CQ and 14th in direct collaboration with K2UYH. Through the years we have grown with CQ and more recently with, Al Katz, developed a column that is perhaps more balanced and comprehensive than ever. Your support of our efforts has been increasingly encouraging over these years, and we both wish to take this opportunity to say a heart-felt thank you.

Next month we will outline an entirely new v.h.f. program for 1966, a program that we feel will offer something for everyone, including many new awards and advance contest info.

For now, let us wish you a most Merry Christmas. (Two meter men must catch the Geminids & Arietids showers to insure a happy New Year).

73, Bob, K2ZSQ and Allen, K2UYH

Novice [from page 78]

English it would add much to our enjoyment of our hobby. I think that learning an International language will do much to further the cause of world peace. We must be able to understand our neighbor if we are to really get along with him. Kaj, all of the construction articles that I write will have all electrical values as part of the parts list, this I pledge for all of the nice letters that I have received from the peoples of other lands. I DO appreciate your many letters.

Not all of our letters praise the column as does the above, once in a while I'm wrong. Witness this letter

Give "him" or "her"
THE ALL-SEASON

Gift

GREATEST VALUES EVER OFFERED



INCOMPARABLE

telrex
BEAMS

Also: Rotator-Selsyn-Indicator Systems, Inverted-V-Kits, "Baluns," Towers, "Bertha" Masts, 12-Conductor Control Cable and Co-ax. Send for PL66.

ANTENNAS

SINCE
1921

COMMUNICATION SYSTEMS
telrex LABORATORIES

ASBURY PARK, NEW JERSEY 07712, U. S. A.

For further information, check number 36, on page 106

NOW! A SSB TRIBAND TCVR KIT FOR ONLY \$179.95



NEW **ETCO** 753
IN STOCK AT
AMATEUR RADIO
EQUIPMENT CO.

1203 East Douglas


Wichita, Kansas 67201

TELEPLEX teaches CODE

TELEPLEX performs no miracles. It just seems miraculous when compared to any other method. Get the facts. Don't waste your time and money. Write today for descriptive literature. It's free and interesting.

TELEPLEX CO. • 739 Kazmer Court • Modesto, Calif.

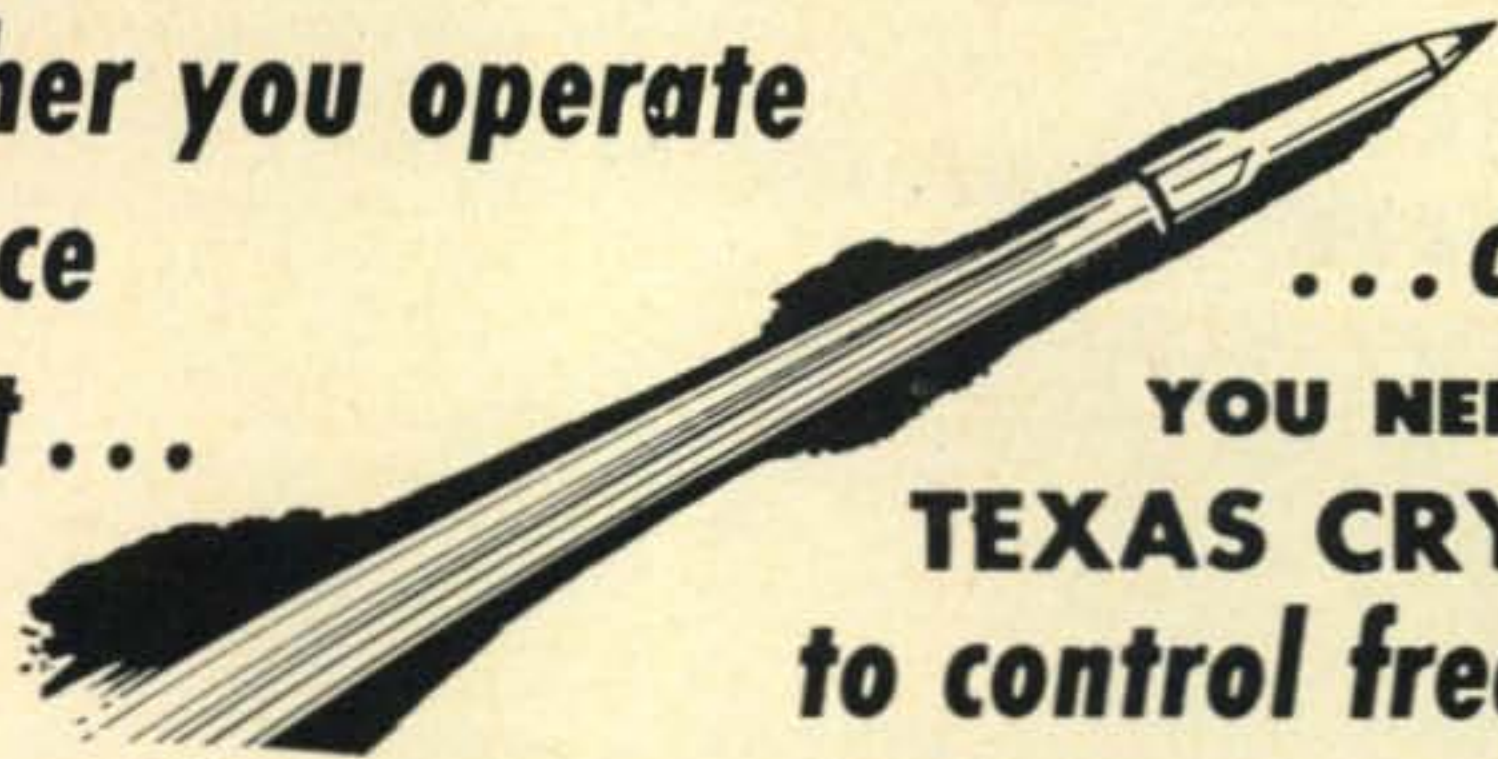**whether you operate
a space
rocket ...**



... or a radio rig ...

**YOU NEED
TEXAS CRYSTALS
to control frequency!**



Why TEXAS CRYSTALS? Simply because you can be sure of their doing the job perfectly, just as they have in numerous space projects. And, TEXAS CRYSTALS are unconditionally guaranteed! Regardless of your crystal needs — CB, amateur, commercial 2-way, low frequency, marine, aircraft, etc. — see your parts dealer for TEXAS CRYSTALS.

If your dealer can't supply your needs, send his name with your request for catalog to our plant nearest you.

- CB • AMATEUR
- COMMERCIAL
- RADIO CONTROL
- MILITARY
- MINIATURE
- LOW FREQUENCY
- AIRCRAFT

TEXAS  **CRYSTALS**

A Division of Whitehall Electronics Corp.

1000 Crystal Drive
Fort Myers, Florida 33901
Phone 813 — WE 6-2109

4117 W. Jefferson Blvd.
Los Angeles, California 90016
Phone 213 — 731-2258

For further information, check number 37, on page 106

CUT HOLES FAST



GREENLEE CHASSIS PUNCHES

Make accurate, finished holes in 1½ minutes or less in metal, hard rubber and plastics. No tedious sawing or filing—a few turns of the wrench does the job. All standard sizes . . . round, square, key, or "D" shapes for sockets, switches, meters, etc. At your electronic parts dealer. Literature on request

GREENLEE TOOL CO. 
2028 Columbia Ave., Rockford, Illinois

For further information, check number 58, on page 106

FREE ALL NEW

1966 HAM/CB CATALOG

SEE WRL'S EX-
CLUSIVE HAM/CB
GEAR!

TUBES, PARTS,
ETC., AT LOW-
LOW PRICES.

SELECTED GOOD
BUYS ON RADIOS,
RECORDERS, ETC.

SPECIAL PUR-
CHASES FOR
ELECTRONIC
BUILDERS

MOST COMPLETE
AMATEUR EQUIP-
MENT LISTINGS
EVER COMPILED

BUY ANYTHING
ON OUR EASY-
PURCHASE CRED-
IT PLAN

GET
YOURS
TODAY

WORLD RADIO LABORATORIES

3415 WEST BROADWAY, COUNCIL BLUFFS, IOWA 51504

Rush me your Free 1966 Catalog

Name _____

Address _____

City _____

State _____

Zip _____

For further information, check number 59, on page 106

100 • CQ • December, 1965

sent by Joe Picior, WB2GYP, 181 Monroe Street, Franklin Square, L.I., New York. It was addressed to the Editor and forwarded to me.

"Editor CQ: I appreciate your nice NOVICE column (n). (Reading it helped me get started.) But how about helping them right? Please check solid state power supply diode polarities in the general purpose power supply in the September '65 issue (vol 21 #9) page 89. Thanks best 73's Joe.

P.S. I read your magazine every month and keep up the v.h.f. gear."

Thanks, Joe, for the information. You are right, the drawing of the diodes are reversed but the marking is correct as shown. Check this in your copy and reverse the drawing of the diodes but leave the + sign as shown. I always go back to the original copy and draw any corrections and reference the correct copy in the article. I checked my power supply and it is correct so I lost no diodes. By the way, I also have a power supply just like this except I use a bridge and get twice the voltage and use the center-tap for the 325 volts for the exciter. This for a unit that uses a linear final. Tell you more about that later. I'm glad you read the column, Joe. Like I said, we all make mistakes, Thanks again.

Help Wanted

If you have problems with getting a license or getting the rig to go let me try to get someone nearby to help you. Now, no one can get you a license except yourself, but maybe you can use some personal advice or help. Write, Walter G. Burdine, W8ZCV, Waynesville, Ohio, and give us the information.

Those needing help now are: Earl Jones, Jr. GB.73 524 Ringo, Mexico, Missouri 65265 needs help with code and theory from a local ham.

Ronnie R. Abbott, R.F.D. #3, North Vassalboro, Maine is a handicapped aspirant that could use some help from a local and possibly the loan or donation of some used equipment to set up a station. Locals have a chance to do their Boy Scout deed of the year.

My good friend, Lawrence "Pelly" Morris, WA9INV, Box 184, RR#1, Lawrenceburg, Indiana would like to obtain by any means legal, a book on the Clegg Interceptor "A". He says that with a book he might be able to put in a better signal but for about 75 miles he seems to consistently put in an S-9 signal here.

To those who get this magazine within the next two months let me be the first to wish you all the best of seasons greetings and may you have the best year of your ham radio life this new year. Just remember, give a little of yourself and time to help make someone else happy and you will be happier for the deed. Merry Christmas and Happy New Year.

73. Walt, W8ZCV

RTTY [from page 86]

The a.f.c. circuit will tune the receiver in 1 or 2 seconds. If, however, the frequency should suddenly be changed several hundred cycles, it would take about 10 seconds for the receiver to be retuned, because the delay circuit associated with V_1 must discharge before this tube can become active. A steady *space* lasting about 5 seconds can be sent without causing the b.f.o. to depart excessively from the correct value. If this signal is prolonged to about 10 seconds, the b.f.o. tuning is changed so that this *space* becomes approximately 2125 cycles. It will then require a steady *mark* of 10 or more seconds for the correct tuning to be re-established.

The AN/FGC-1 a.f.c. circuit is connected to both channels A and B at the radio receiver audio outputs. A knob, marked AFC, is provided on the a.f.c. panel so that the circuit may be made inoperative by turning it to OFF. The DISCH button is provided to short circuit the output momentarily when testing, in order to

save the time which would otherwise be needed to discharge the 32 mf capacitor in the output circuit.

On the Bauds

W1LZB of Braintree, Mass., is on 80 with a Model 19, a 32v-3 running 165 watts, and an NC-183. Oldtimer W1BGW of Boston, Mass., is on 7140 kc Sunday mornings with narrow shift. W1SNN of Framingham, Mass., uses a Boehme Model 5C converter with his 51J-4. K1MQK of Waterbury, Conn., uses a Model 15 with a GSB-100 and an NC-300.

W2YEQ of Babylon, L.I., uses a 75S-3 and a Model 19 with an HT-32 driving a pair of 813's. W2NQW of Port Jervis, N.Y., runs 100 watts to an 811 and has Model 14 printer and TD. W2TAP of New York City works 20. Atlantic Surplus Sales, 250 Columbia Street, N.Y., 11231, has Teletype manuals in stock. W2QFR of New Rochelle, N.Y., makes the required 14 copies (for comments to the FCC) on his Model 28, using an endless tape loop. W2JGE operates 80 from W2GDU in Freeport, L.I., using a KWM-2. W2JBZ of Spring Valley, N.Y., is on 80 as is K2DON of Staten Island, N.Y.

Oldtimer W3CRO of Springfield, Pa., runs a KW to a 4-1000A on 80, and has a new pair of SP-600JX receivers for diversity reception; and, a new Model 28ASR to go with his old Model 26 and Model 14's. W3AZR of Telford, Pa., is building the Twin City TU. K3UNX of Camden, Del., was on 146.32 with a TDQ transmitter (a.m.). K3OJX of King-of-Prussia, Pa., uses tape on 80. K3MIU of Bedford, Pa., is also on 80. W3UQX of Allentown, Pa., runs 400 watts on 80 and has Models 15 and 19. WA4TPS of St. Petersburg, Fla., and W5SKU of New Orleans, La., both work 20 meters.

W7PBV of Boulder City, Nev., reports the following Nevada stations with Model 15 machines: WA7ARZ, WA7BEU, W7CTK, K7DNE, W7HQS, K7NYU, W7PRM, K7PYF, K7RKH, K7ZOK, and W7PBV.

W8TGT of New Martinsville, (WETZ), W. Va., has some Model 28 printers and TD's for sale. K8RFU of New Philadelphia, Ohio, uses a W2JAV tube TU with switchable filters for 850, 340, and 170 cycle shift; and a Marauder on 80, 40, 20, 15, and 10 meters. Charlie reports increased activity on 29,050 kc. (*We would like to hear from the rest of the groups in Ohio, N.Y., and N.C. reported using this frequency for f.s.k.*) K8CPC of Rochester, Mich., has problems with his WE J86205J loop supply (*Who can help?*)

W9GFS of Evansville, Ind., uses a Model 14 strip printer on 80. Phil started in with a Model 12 in 1953. WA9CGW of Jacksonville, Ill., has a Model 15 and is looking for a schematic of his Boehme 5C converter. W0LFH of Algona, Iowa, is using the late W0BP's AN/FGC-1 in diversity. The W0BP Net (Minnesota) meets on 7140 kc with narrow shift Sunday mornings.

DX printed from 20 meters at W2JTP during late August: FG7XX, Guadeloupe Island; I1WT, Firenze, Italy; G2HIO, England.

Comments

Our mail bag has contained many nice letters of appreciation for this series of RTTY Columns on the AN/FGC-1. Naturally, a unit of this magnitude could not be covered in a regular magazine article, even if in two parts. So, knowing that there were quite a few units of this type kicking around, simply because no manual was available (or because it was so big!), we decided to pass along our information and experience in the form of a series of RTTY Columns. Having one in actual operation for several years at W2JTP was a great help, too.

All that remains to be covered is the power supply, and perhaps a short run-down on the line-up procedure. So, stay with us, and if you have the opportunity (and the room!), grab one and enjoy this phase of RTTY.

A Very Merry Christmas, Byron, W2JTP

THREE BANDS 200 WATTS



FOR THE HW12, 22 or 32 TRANS- CEIVER with a new idea from DYNALAB . . .

—with DYNALAB'S Sensational New Three Band Conversion Kit for the HW12, 22, or 32 Transceivers.

A few hours of construction and color coded wiring result in a three-band unit for the "HW" transceiver. A turn of the band-switch produces the same circuitry of all three transceivers.

Here are the results:

- Coverage: 14.2-14.35, 7.2-7.35, 3.85-4.0 Mc. (Full 75 meter coverage with THW12)
- Operation: LSB on 75 and 40 USB on 20
- Power Input: 200 watts PEP
- Calibration: 2 Kc on original dial
- Stability: 200 cps after 20 min. warm-up under normal ambient conditions
- All other specifications remain the same

FEATURES AND HIGHLIGHTS

- ★ Well laid out assembly modeled after the famous Heath manual
- ★ 90-day parts guaranteed and replacement warranty
- ★ Free technical assistance and factory repair service at minimal charge
- ★ Highest quality components throughout

PRICE **\$49.95** Ppd USA proper

ELSEWHERE, ADD \$1.50 FOR SHIPPING

HW12 owners order kit model THW12

HW22 owners order kit model THW22

HW32 owners order kit model THW32



For further information see "Recent Equipment" on page 54 of October QST, or write:

DYNALAB COMPANY

215-28 Spencer Ave. Queens Village, N.Y. 11427

For further information, check number 60, on page 106

December, 1965 • CQ • 101

Announcing

HOTEL SAHARA'S

1ST ANNUAL SAROC

Sahara Amateur Radio Operator's Convention

January 7, 8, 9, 1966

at Hotel **SAHARA** Las Vegas Nevada

Exciting Entertainment...

Congo Room
LISA MINNELLI

Casbar Theatre
LOUIS PRIMA

Luxurious Accommodations...

1,000 beautiful rooms with a special SAROC ROOM RATE OF ONLY \$10 single or double, plus tax (Jan. 5-10).

Special Prize for Advance Registration

Registration fee of \$8.50 includes:

Welcome cocktail upon arrival for Sahara guests.

Two cocktail parties.

Midnight show and drinks in the famed Congo Room.

Sunday SAHARA HUNT Breakfast in the Congo Room.

Complimentary gift from Hotel Sahara.

MARS luncheon... ALSO Special ladies' day program... technical talks... manufacturers' exhibits...

Master of Ceremonies Ray E. Meyers (W6MLZ).

(Deadline for advance reservations, Dec. 31, 1965)

Make Reservations Now!

MAIL COUPON TO JOHN ROMERO
HOTEL SAHARA • LAS VEGAS, NEVADA

NAME _____ CALL _____

ADDRESS _____

Arr. date and time _____ Lgth of stay _____

Accommodations desired (check one)

single double twin

Registration fee of \$8.50 enclosed.

(Please make checks payable to SAROC,
HOTEL SAHARA)



For further information, check number 41, on page 106

102 • CQ • December, 1965

Ham Shop

Advertising Rates: Non-commercial ads 10¢ per word including abbreviations and addresses. Commercial and organization ads, 35¢ per word. **Minimum Charge \$1.00.** No ad will be printed unless accompanied by full remittance. **Closing Date:** The 10th day of the second month preceding date of publication.

Because the advertisers and equipment contained in Ham Shop have not been investigated, the publishers of CQ cannot vouch for the merchandise listed therein.

Direct All Correspondence & Copy to: muriel e. mark, c/o CQ Ham Shop, 14 Vanderventer Ave., Port Washington, L.I., N.Y. 11050.

QSL's Samples—SASE. Moyers, 846 Rising Sun, Telford, RD #1 Pa.

QSL's??? Samples 25¢. Deluxe 35¢ (refunded). Sackers, W8DED, Holland, Michigan.

QSLs. Samples, Dime. Print Shop, Corwith, Iowa.

EMBOSSSED QSL Cards. Free Samples. Ace Printing Service, 3298 Fulton Road, Cleveland, Ohio 44109.

"GOLDEN CALL" QSLs, samples 10¢. Samco, Box 203-G Wynant-skill, N. Y. 12198.

PICTURE of yourself, home, equipment etc. on QSL cards made from your photograph. 250—\$7.50 or 1000—\$14.00 postpaid. Samples free. Write Picture Cards, 129 Copeland, La Crosse, Wis.

CREATIVE QSL CARDS free, new catalog and samples. Personal attention given. Wilkins Creative Printing. P.O. Box 787-2, Atascadero, California.

QSL CARDS \$2.50 per 100 in three colors. Samples and catalog free. Garth, Box 51C, Jutland, New Jersey.

QSL CARDS. As low as \$2.50 per 100. Samples free. Radio Press, Box 24C, Pittstown, New Jersey.

QSL's 3-color glossy. 100 \$4.50. Rutgers Vari-typing Service. Free Samples, Thomas Street, Riegel Ridge, Milford, N.J.

QSLs Samples 25¢. Rubber Stamps; Name Call, Address, \$1.55. Harry Sims, 3227 Missouri Avenue, St. Louis, Mo. 63118.

QSL's... 18 samples 10¢... Filmcrafters... Martins Ferry, Ohio.

QSL's WSL's XYL-OM's (Sample assortment approximately 93/4¢) covering designing, planning, printing, arranging, mailing eye-catching comic, sedate, fantabulous, DX-attracting, Protopay, Snazzy, unparagoned cards. (Wow!) Rogers, K0AAB, 961 Arcade St., St. Paul 6, Minn.

QSL's BROWNIE—W3CJI . . . 3111 Lehigh, Allentown, Pa. Samples 10¢ with catalogue 25¢.

QSL's CB, WPE Samples 10¢ Nicholas & Son Printery P.O. Box 11184, Phoenix, Arizona 85017.

QSL CARDS—100 3-color, glossy \$3.00. World globe in silver; report form on reverse side; Free samples. RUSPRINT, Box 7575 Kansas City, Missouri, 64116.

HUNDRED QSL's: \$1. Samples, dime. Meininger, Jesup, Iowa.

QSL's—Ham and CB, related products. Free Samples. April Sign Co. 56290 Van Dyke, Washington, Michigan.

QSLs. Large Selection, including photos, rainbows, glossy stocks, cuts, etc. Fast Service. Samples, dime. Ray, K7HLR, Box 1176 Twin Falls, Idaho, 83301.

QSLs \$2.00 per 100 postpaid. Free sample. Hobby Print Shop, Umatilla, Fla. 32784.

QSL—Special—100 two color—\$1.65. Quality. Free samples. Kan-uck, Box 461, Dayton, Ohio.

DON'T Buy QSL cards until you see my free samples. Bolles, Box 9363, Austin, Texas.

ELECTRONIC CHASSIS PUNCHING and drilling service, Panels cut, etc. Build that magazine article! Send chassis or request estimate. Hole (16ths) diameters to 1/2", 5¢; to 1 1/2", 25¢; to 4", 50¢; sq., 5¢ perimeter inch in aluminum to 3/16. Steel 20 ga. add 50%. Mark sizes and centers, allow clearances. Payment with material, minimum \$2.00, under 2 lbs returned postpaid. Metalwerk, P.O. Box 1372, Cedar Rapids, Iowa 52401.

ELIMINATE Mobile Vibrator Noise. Revolutionary device outmodes noise-creating vibrator. Completely transistorized unit plugs directly into vibrator socket. No moving parts. Same size as vibrator. 12 Volts. Not a kit. Comes completely wired ready to use. For negative ground only. State make and model of transceiver. \$11.95 PPD. \$5.00 deposit on all C.O.D. orders. Tel-Trol Systems, 2180 Bronx Park East, Bronx, N. Y.

PRINTED CIRCUIT BOARDS Hams, Experiments. Many different projects. Catalog 10¢ P/M Electronics, Box 6288 Seattle, Washington 98188.

WANTED—Laboratory test equipment. Electronicraft, Box 13, Binghamton, N.Y. 13902.

YOUR CALL in NEON. Your call letters or name in neon gas filled tubing. Lights up from R.F. when you're on the air. \$1.00. ADIA-BATIC ENTERPRIZES, Box 151, Albany, California.

WHOLESALE ELECTRONICS, Resistors 3¢, Multimeters \$9.95, speakers 49¢, electrolytics 10¢. Hundreds of items. Catalog 25¢. Refundable. ROYAL Box 2591, El Cajon, California 92021.

ATTENTION HAMS! We buy, sell ham gear. Repair and alignment facilities available. Hold Advanced and First phone. Used Gear always reconditioned. Money back guarantee. KitKraft Company, P.O. Box 406—Canal St. Station, New York N.Y. 10013.

CASH, SONY TRANSISTOR TV's etc. swapped for G-R, H-P, L & N, etc. Equipment, special tubes, manuals, military electronics. Engineering Associates, 436 Patterson Road, Dayton, Ohio. 45419.

HIGHLY EFFECTIVE HOME STUDY REVIEW for FCC commercial phone exam preparation. Free literature. COOK'S SCHOOL OF ELECTRONICS. Box 747, Riverhead, New York 11902.

CRYSTAL BARGAINS. Free list. Nat Stinnette, W4AYV, Umatilla, Fla. 32784.

FINE NEW BOOK—4000 words German-English for Hams and SWL's. Send \$1.25 or 11 IRCs for your copy to Christian Zangerl, OE9CZI, Dornbirn, Nachbeurstrasse 28, Austria.

FREE! Giant bargain catalog on transistors, diodes rectifiers, components; Poly Paks, P.O. Box 942P, Lynnfield, Mass.

THIS COMPANY is looking for Ham & CB cartoon artists and ideas. \$10.00 per idea IF ACCEPTED. For information, write AMBRU PRODUCTIONS, 10 Burbank Street, Yonkers, New York 10710.

Technical Manuals—lowest prices USA, teletypewriters, receivers, transmitters, text equipment and etc. Large lists. Send 10¢ coin-stamps. Quaker Electronics, Hunlock Creek, Pa.

CRAZY . . . NOT QUITE. LET'S DEAL. . . . We want to become Nevada's largest ham store! Look! . . . Swan, Transcom, Galaxy, Hallicrafter, Hammarlund. . . . No honest deal refused. Write: Sierra Electronics, P.O. Box 212/ Sparks, Nevada.

WANTED—An APR-14, 13 receivers. SG-13, H-p4, SG-1, SG-2, MD-83, 479 Collins, in any condition. T-368-C xmtrs. R-390, 390A, R-388, 389, 391. Receivers. RT-66 thru 70 Rt units RT/77-GRC-9, GRC-10, GRC-19. RCA, Bendix, Collins Aircraft Radio and Radar Equip. Hewlett Packard, General Radio, Tektronix, etc., Test Equipment. GRC, PRC, GRR, TCC, ARC, sets ARM, PRM, URM, UPM, URM, SG Test sets any and all types. You name it. Call E. Charol, Tech Systems Corp., 42 W. 15th Street. N. Y. 11. N. Y. CH 2-1949 Collect.

CRYSTALS—LOW FREQUENCY 16.00000kc HC-17U hermetically sealed holder, only \$2.50 each postpaid. No charge matched pairs. Also 700,000 other crystals in stock—lists available. Quaker Electronics, Hunlock Creek, Pa.

CRYSTALS, Transformers, pyranol condensers, etc., top quality surplus. Write for Bulletin No. 865. R & M Electronics, Box 5234, Knoxville, Tennessee 37918.

DISTRIBUTOR WANTED. No Competition. To service and set up new accounts in exclusive territory. Investment secured by fast moving inventory of amazing plastic coating used on all types of surfaces interior or exterior. Eliminates waxing when applied to any type of floor. Eliminates all painting when applied to wood, metal or concrete surfaces. Minimum Investment—\$500/Maximum Investment \$12,000. For details write or call: Phone-314 AX-1-1500, PENGUIN PLASTICS CORP., 3411 North Lindberg Blvd., St. Ann, Missouri 63074.

FOR SALE Complete instructions including 28 page booklet and 22" x 36" schematic for converting the ART-13 transmitter to a.m. and s.s.b. Satisfaction guaranteed. \$2.50. Sam Appleton, 501 No. Maxwell St., Tullia, Texas.

RTTY GEAR for sale. Write for list—issued monthly. 88 or 44 Mhy toroids. Five for \$1.75, postpaid. Elliott Buchanan W-6-VPC—1067 Mandana Blvd., Oakland, California 94610.

WANTED: Many Types Military or Commercial Surplus. . . . Airborne, Ground, Try the Big Boys then write or call, collect, AREA 703-650-5480. Give us YOUR price. We pay case and freight. . . . Dun Bradstreet rated. RITCO, P.O.B. 156, Annandale, Virginia 22003.

MANUALS, for surplus electronics. List 10¢. W31HD, 4905 Roanne Drive, Washington, DC 20021.

GLOBAL WRIST WATCHES, features 24-hr. World Time Conversion. Free brochure. (Mention "CQ") NORDLUND, 7635 West Irving Park, Chicago, Illinois 60634.


TOOOOBBES, TRANSMITTING—SPECIAL PURPOSE—New boxed. Guaranteed. 6CW4 — \$1.40; 6146 — \$2.55; 417A — \$3.95; 826 — \$6.00; 6360—\$3.45 . . . Free Catalog. . . . VANBAR Dist., Box 444Y, Stirling, N.J. 07980

CLOSEOUT discontinued full size beams, new 7/8" and 1" aluminum; three element twenty meter, \$22; Two element, \$16; Three element 15 meter, \$16; two element, \$12; Express Collect Shipment. GOTHAM, 1805 Purdy, Dept. CQ, Miami Beach, Fla.

WRL BLUE BOOK PRICES SAVE MONEY ON QUALITY USED GEAR. Take 10% without trades. G76—\$179.00; "Sidewinder 2m"—\$299.00; 62S1—\$650.00; 32V1—\$149.00; Apache—\$149.00; Valiant—\$199.00; HT-38—\$269.00; SB-400—\$299.00; Invader 200 — \$285.00; 200V — \$499.00; HT-41 — \$229.00; Loudenboomer — \$299.50; Pro 600 JX—\$199.00; SX101A—\$219.00; SS1R—\$545.00; HO-10—\$55.00; and hundreds more. FREE LIST: LEO, WØGFQ, Box 919, Council Bluffs, Iowa.

GIANT 20th Anniversary Catalog. TV Cameras and Electronic Equipment. Free copy. Denson Electronics, Rockville, Conn.

DOW-KEY DK78 SERIES

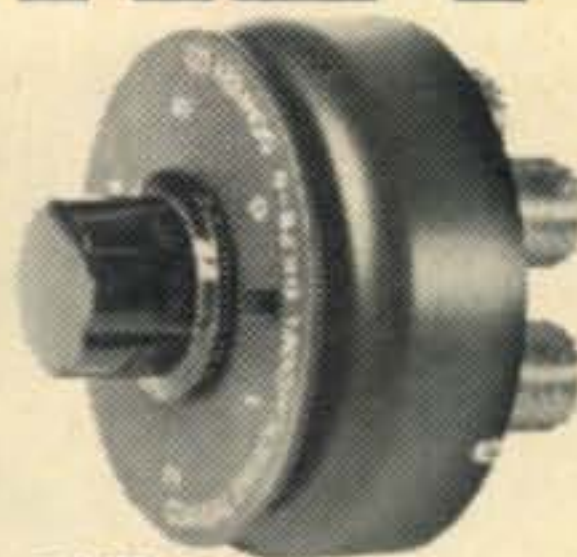

DK78-6

NEW MANUAL COAXIAL SWITCHES . .


(Not Wafer Switches)

New manual DK78 series coaxial switches with excellent r.f. characteristics (not wafer switches). r.f. rating, 1 kw. 50 ohm impedance. VSWR less than 1.05:1 at 150 mc. Isolation greater than 50 db @ 500 mc. and greater than 80 db @ 30 mc. With dial plate and knob. Wt. 10 oz. Size: 3" dia. x 1 1/4" deep.

- DK78-2, single pole, double throw \$12.75
- DK78-3, single pole, three throw \$12.75
- DK78-6, single pole, six throw -- \$15.75
- DK78-T, transfer-crossover switch \$15.75

Available with types BNC, TNC, N and C Coaxial Connectors at slightly higher costs.

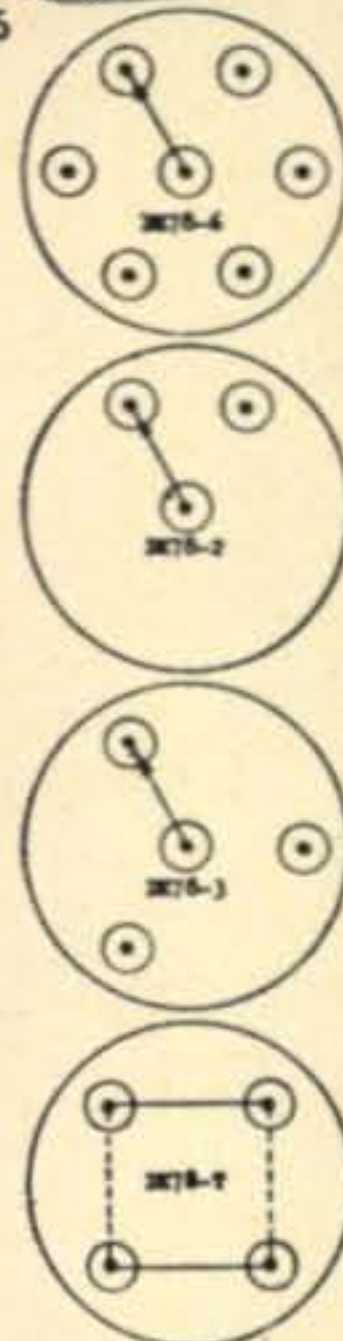Products at your dealer or write:
DOW-KEY COMPANY
Thief River Falls, Minnesota



For further information, check number 42, on page 106

FREE GIANT NEW CATALOG

BURSTEIN-APPLEBEE CO.

Dept. CQ, 1012 McGee, Kansas City, Mo. 64106

Rush me FREE 1966 B-A Catalog.

Name

Address


City..... State.....

Please be sure to show your Zip No.....

SEND FOR IT TODAY

FREE

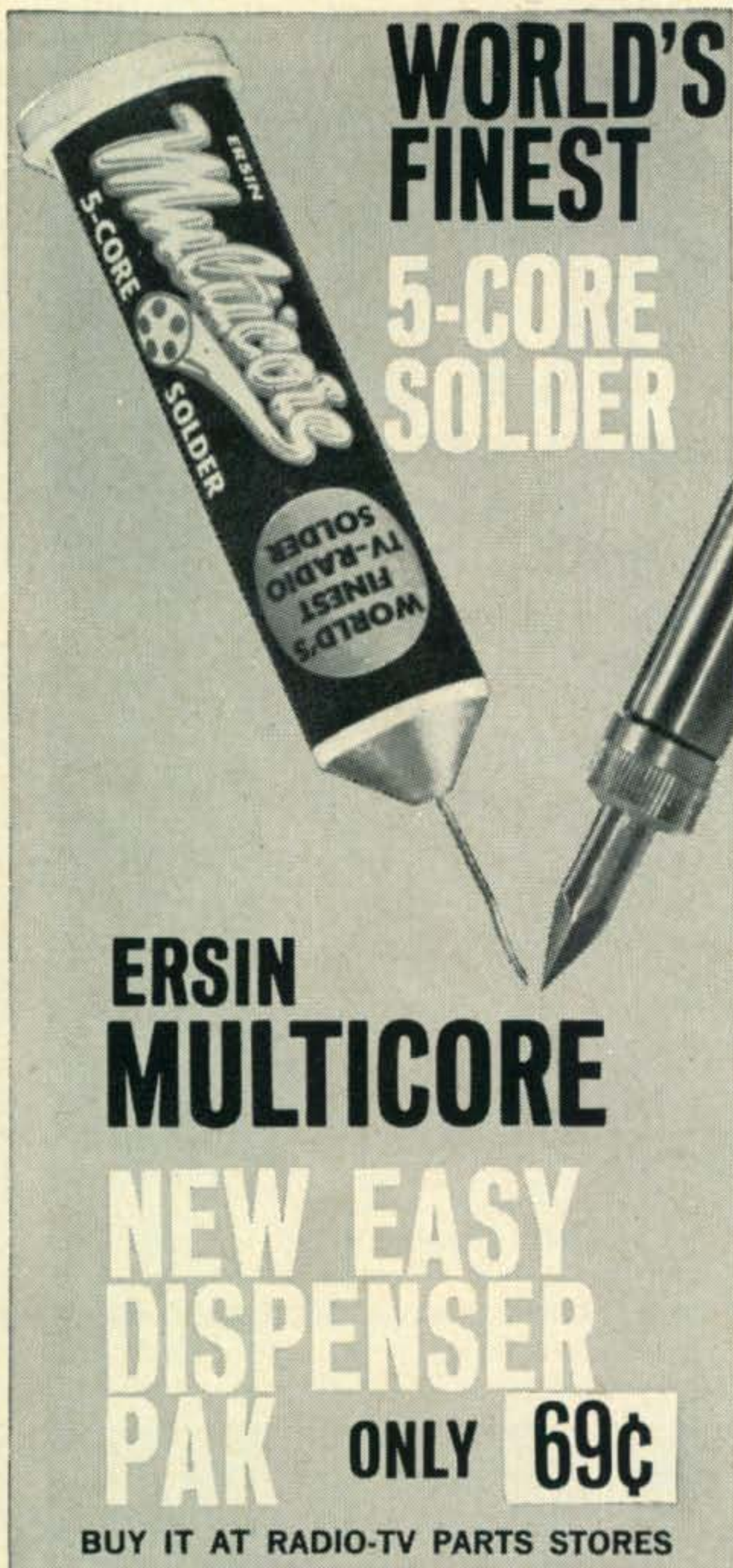For further information, check number 43, on page 106



**WORLD'S
FINEST
5-CORE
SOLDER**

**ERSIN
MULTICORE
NEW EASY
DISPENSER
PAK ONLY 69¢**

BUY IT AT RADIO-TV PARTS STORES

MULTICORE SALES CORP., WESTBURY, N.Y. 11591
For further information, check number 44, on page 106

CALL-IDENT TYMETER®

10-MINUTE STATION
CALL REMINDER

#124

22.50

Plus
applicable
taxes



10-minute repeating timer buzzes warning to sign in your call letters. Walnut or ebony plastic case. H4", W7³/₄", D4". Wt. 3 lbs. 110V, 60 cy. 1 year guarantee.

At Your Dealer, or WRITE TO

TYMETER ELECTRONICS

PENNWOOD NUMECHRON CO.
7249 FRANKSTOWN AVE., PITTSBURGH 8, PA.

For further information, check number 45, on page 106

SELL: Elimac 4x250B tubes. Guaranteed good. \$6.50 each, \$10.00 pair. Prepaid in U.S.A. Send check or money order. Everett Stidham, Jr., W5JLQ, 722 South 30th, Muskogee, Oklahoma.

INTERESTING OFFERS GALORE in the new "Equipment Exchange—Ham Trader"! Rush \$1 for next 12 issues. Brand, WA9MBJ, Sycamore, Illinois.

Need any band coils fitting HRO-7 and components or unit for ART-13 AC power supply. G. Evans, W4WVS, 803 Rosselle St., Jacksonville, Fla.

WANTED: A few RK-65 or 304 TL xmitting tubes for high-power final and spares. Write card stating quantity condition and price. All replies answered. John Mayes, W4VJA, Route 13, Knoxville, Tenn. 37918.

STAMP COLLECTORS: Will swap stamps (your choice) for amateur and military radio equipment, supplies, tech manuals, etc. John Reilly, 35-19 167th Street, Flushing, New York 11358.

LEARN CODE the V method, money back trial, guided sending, records, tapes, write. Page Electronics Institute 90037.

COLLINS 75A-4 OWNERS: Don't trade up! Investigate our conversion that makes the 75A-4 a real dream. W2VCZ-30 Pitcairn Ave., Ho-Ho-Kus, N.J. 201-652-8494.

Wanted: Complete set, preferably bound volumes, CQ for 1945 through 1963. Must be in excellent condition. Write Charles Miller, W4AXV, 2875th GEEIA Squadron, Box 460, APO San Francisco 96323.

"S & H" GREEN STAMPS. Needed for Missionary Ham Station. Have your friends help too. Father Jude, WA2YNO, St. Paul's Abbey, Newton, New Jersey 07860.

JOIN OUR AMATEUR THRIFT CLUB. Pay cash and save. Write for details. Joe Dimare, Box 20672 Dallas, Texas 75220.

REMOTE CONTROL UNIT, brand new \$5.00. Postpaid. (Cost Navy \$125.00) MDC, 923 W. Schiller, Phila. 40.

ANTENNA tuning unit, brand new \$3.00 postpaid (cost Navy \$85.00). MDC, 923 W. Schiller, Phila. 40, Pa.

IMPORTANT INFORMATION

for ALL HAM SHOP ADVERTISERS!

Beginning with the January 1966 issue of CQ, the ad rate for COMMERCIAL ADVERTISERS will be increased to 35¢ per word! No advertising will be accepted unless accompanied by full payment—Payment to be computed on a per word basis, all abbreviations, numerals in sequence, to be considered as individual words in cost computation. Copy must be received prior to 10th of second month preceding issue in which advertising is to appear.

Checks and/or money orders are to be payable to CQ Ham Shop, and all correspondence in connection with Ham Shop should be directed to: Muriel E. Mark, c/o CQ Magazine 14 Vanderverter Avenue, Port Washington, L.I. N.Y. 11050.

WANTED—QSTs for private collection. 1920-Jan. 1917-Oct., Nov., Dec., 1916-Feb., May, June, July. K2EEK, CQ Magazine, 14 Vanderverter Ave., Port Washington, L.I., N.Y., 11050.

MERRY XMAS and A HAPPY NEW YEAR from WØCVU. On the air since 1913. Still a wonderful hobby through these fifty years.

PICTORIAL STUDY in Amateur Radio. Free Details. Dwight Cross KØCZU, 1212 Lynch St., St. Louis, Mo. 63118.

RTTY CHANNEL FILTERS, octal mounted, specify frequency \$3.00 each. Toroids 88mh, uncased, 5 for \$2.50. WA6JGI, 3232 Selby Avenue, Los Angeles, California 90034.

MOBILE TRANSISTOR POWER Supply Parts. Transformers and Partial Kits. Unequaled prices. Send stamp for information. C. F. Grice, 13114 Indian Creek Road, Houston 24, Texas.

PRINTED CIRCUIT Materials. Three sample pieces and details. One Dollar. Betty Lou Nolin, 35 Arbor Drive, New Hartford, N.Y. 13413.

CRYSTALS, Transformers, Pyranol condensers, etc., top quality surplus. Write for Bulletin No. 865. R & M Electronics, Box 5234, Knoxville, Tennessee 37918.

NEED ANY BAND coils fitting HRO-7 and components or unit for ART-13 AC Power Supply. G. Evans, W4WVS, 803 Rosselle St., Jacksonville, Fla.

ATTENTION—FOREIGN HAMS—DX Clubs. Make extra money for ham equipment by selling me used stamp mixtures which you gather. Send for details. Bob Murphy, Box 57732, Webster, Texas, 77598.

SELL: R390A receiver, excellent condition with manual. \$600.00. Larson, 330 No. Saltair Avenue, Los Angeles, California 90049.

COLLINS 51J-3 R388URR, perfect, \$400.00. NCL-2000 perfect, 5 hours time \$550.00. Prefer local. Will ship W7WRS, 4200 Lorna Place, Las Vegas, Nevada.

HQ-129X in gud condx wid spkr. \$75. Pratt Inst. Radio Club W2NOD. Tel: 212 SH 5-1248.

COLLINS KW-1 DELUXE TRANSMITTER. 1,000 watts AM or CW. Would make a fine SSB linear. \$1400.00 or make offer. George F. Norton, W4EEE, Georgia University Station, Athens, Georgia.

SELL: Brand New EICO Triband SSB transceiver wired and tested \$200. Central Electronics 600 L Linear Amplifier \$175. Gerald Williamson, K4LXT, P.O. Box 203, Williamston, N.C., Phone 792-2446.

COLLINS 75S-3B, 32S-3, 516F-2 ac supply, late serial number. Less than 5 hours time \$1,200.00 Firm. Perfect. TH6DX Beam, new in carton \$100. Send money order or certified check. Wm. Edgar Lyons, Sr., 4200 Lorna Place, Las Vegas, Nevada.

PERFECT CONDITION Heathkit HR10 receiver with crystal calibrator and speaker \$65. Heathkit 6M transceiver HW-29A \$35. Hy-Gain 6M Halo, HH-6 \$9.00. All equipment in excellent working condition. You pay shipping. Scantlebury, K8WDK, 319½ S.E. 6th, Hillsboro, Oregon.

COLLINS 32S-1, 75S1, 516F-2 with speaker. Immaculate, without a scratch. Guaranteed in perfect condition. \$750 firm. K5BZW, 2098B Falcon Place, Kirtland AFB, N.M. 87118.

MOBILE Palco 80-10 rig, 12VDC p.s. \$45; Match Box \$10; NCX 12 VDC mobile p.s. \$65; Heath Stereo tuner \$65; matching Amp \$55; Sony stereo recorder \$125; Asst. mikes, etc. \$15. W9TGH, 720-B Kensington, Indpls, Ind. 46226.

WANTED: 3-Phase Delta plate transformer, Primary 220V; Secondary, 3 Phase Wye, 1 A, Approx 1300 V each leg of Wye; or three 1 phase transformers—same specifications. Also need smaller 220 V transformers. E. E. Hanson, K7PDT, 3127 So. 2800 E., S.L.C. Utah.

CHRISTIAN Ham Fellowship now being organized among Christian hams for fellowship, tract ministry, missionary efforts among hams. Christian Ham Call book \$1 donation. Write Christian Ham Fellowship, P.O. Box 218, Holland, Michigan.

National NCX-3; NCX-A, almost new, never mobile, \$325. Mint HRO-60T with 4 coils, \$275. K9ZNZ, 1135 Bohland, Bellwood, Illinois 60104.

I NEED, AND WILL PAY Top Price for a TUSKA receiver for my antique radio collection. Same also applies to GREBE, PARAGON, KENNEDY, CLAPP-EASTHAM and similar material. Worcester, R.D. 1, Frankfort, N.Y.

THIS COULD BE THE BEST DX ANTENNA YOU WILL EVER OWN!



COMPLETE KIT PRICE CONTENTS

- 8 FIBERGLASS Arms Specially reinforced at butt and element intercept points
- 2 Quad Arm "X" Mounts
- Boom to Mast "T" Mount
- 1 Instruction Manual

\$59.95

WRITE FOR BROCHURE TODAY

U. S. FIBERGLASS CO.
5101 N.W. 36 Ave. MIAMI, FLA. 33142

For further information, check number 46, on page 106

THESE OM'S
HAVE RECENTLY
SWITCHED TO A

SHURE 444 MIC

K1KDL
W1MAN
WA2OKO
WA3AKW
WA4EVX
WA4FKW
WA4VJI
WA4VWJ
K5ZFP
WA6ZOL

K7ZUR
WA8HAX
K9FXW
W9KOE
WA9HQJ
WA9JNS
WA9KZI
WA9LXX
WA9NKN
KØPS.I



*... notice their improvement
in intelligibility
and added punch?*

Shure Brothers, Inc.,
222 Hartrey Avenue, Evanston, Ill.

For further information, check number 32, on page 106

NOW! A SSB TRIBAND TCVR KIT FOR ONLY \$179.95



NEW EICO 753
IN STOCK AT
M. N. DUFFY & CO.
Detroit, Michigan

2040 Grand River



LOOK! A NEW ELECTRONICS SLIDE RULE WITH COMPLETE INSTRUCTION COURSE

Professional 10" all-metal Electronics Slide Rule. Designed specifically for technicians, engineers, students, hobbyists. Has special scales not found on any other rule. Enables you to solve electronics problems quickly, accurately. Made to our rigid specs by Pickett, Inc. Slide Rule plus four lesson AUTO-PROGRAMMED Instruction Course with grading service, and top-grain leather carrying case . . . a \$50 value for less than \$20! Send coupon for FREE booklet. Cleveland Institute of Electronics, Dept. CQ-109, 1776 E. 17th St., Cleveland, Ohio 44114.

SEND COUPON FOR FREE BOOKLET

Cleveland Institute of Electronics

1776 E. 17th St., Dept. CQ-109
Cleveland, Ohio 44114



Please send FREE Electronics Slide Rule Booklet. SPECIAL BONUS: Mail coupon promptly and get FREE Pocket Electronics Data Guide, too!

GET THIS FREE!

NAME _____ (Please Print)

ADDRESS _____ COUNTY _____

CITY _____ STATE _____ ZIP _____

A leader in Electronics Training . . . since 1934

For further information, check number 47, on page 106

STOP TVI COMPLAINTS

Justify your existence join our Club or any Club and start your own local Emergency Net—FREE information and Bulletins sent to all our REC Club members. Mail \$3.00 for your Membership and you will receive this Exterior Styrene Plate FREE Postpaid in the U. S. or Canada. (\$1.50 for each Extra Plate.)

MAIL BOX • DOOR • CAR • SHACK • ETC.

SIZE 4½" X 10½"



Enclose \$3.00 for your Membership Bulletins and Styrene Plate Post Paid

CHECK MONEY ORDER BILLS (fold in paper)

REC Club

7918 Sunset Blvd. • Los Angeles, California 90046

Name _____ Call _____

Address _____

City _____ State _____

For further information, check number 39, on page 106

-READER SERVICE-

NAME _____ CALL _____

(Please Print)

ADDRESS _____

CITY _____

STATE _____ ZIP CODE _____

Please send me more information on your ads in the Dec. 1965 CQ keyed as follows:


1	2	3	4	5	6	7	8	9	10	11	12
13	14	15	16	17	18	19	20	21	22	23	24
25	26	27	28	29	30	31	32	33	34	35	36
37	38	39	40	41	42	43	44	45	46	47	48
49	50	51	52	53	54	55	56	57	58	59	60
61	62	63	64	65	66	67	68	69	70	71	72
73	74	75	76	77	Total Inquiries						<input type="checkbox"/>

Void after Dec. 28, 1965

CQ MAGAZINE, Dept. RS

14 Vanderventer Ave.

Port Washington, L. I., N. Y. 11050

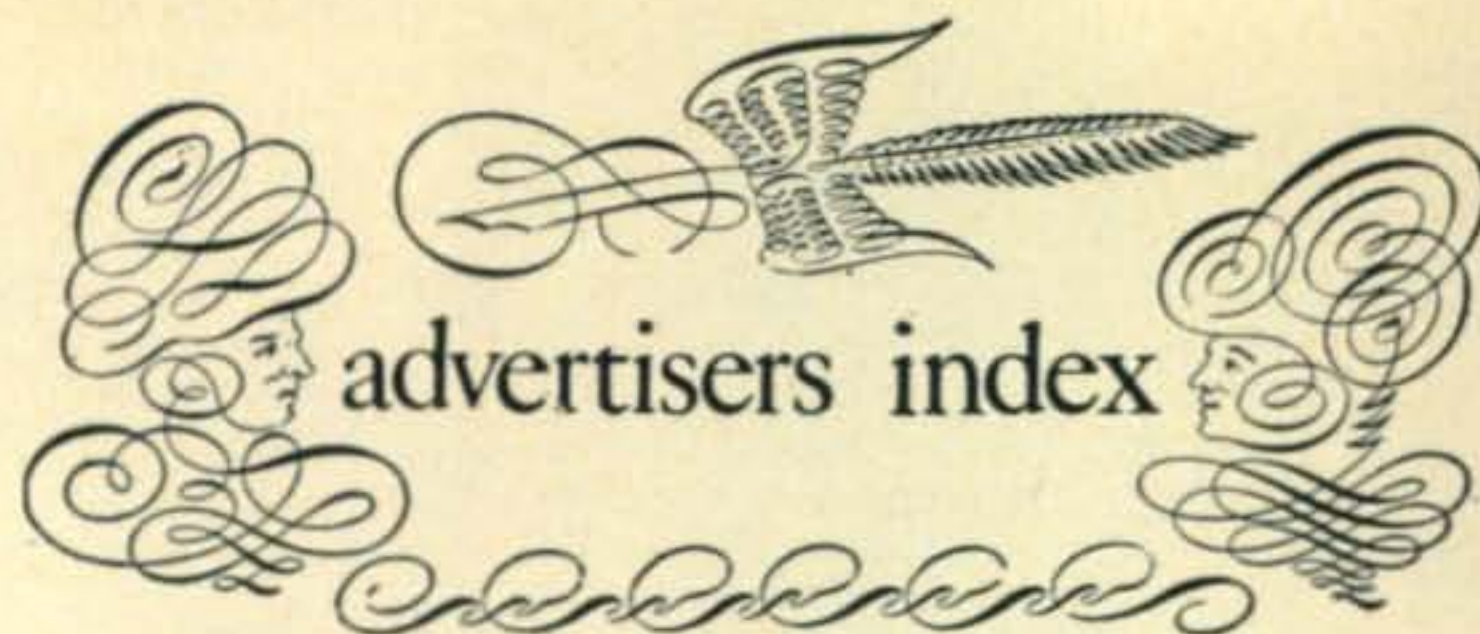


Aermotor	22
Allied Radio	108
Amateur Radio Equipment Co.	99
Amperex Electronic Corporation	4, 5
Astatic Corporation	13
ATV Research	95
Automatic Telegraph Keyer Corporation	94
Bookbinder Publishing Co.	98
Burstein-Applebee Co.	103
Cleveland Institute of Electronics	105
Collins Radio	Cover II
Communication Components Company	97
Communication Products Company	95
Dow Key Co.	103
Drake, R. L. Company	23
Duffy, M. N. & Co.	105
Dynalab Company	101
EICO Electronic Instrument Co., Inc.	6
Eitel-McCullough, Inc.	19
Electronics, Inc.	95
Electronic Surplus Sales	91
Electro-Voice Inc.	1
Fair Radio Sales	97
Finney Company, The	14
Gonset, Inc.	97
Greenlee Tool Co.	100
Hallicrafters	2
Harvey Radio Co., Inc.	89
Heath Company	25, 26, 27
Henry Radio	88
Hotel Sahara	102
Instructograph Company	88
International Crystal Mfg. Co., Inc.	11
Lampkin Laboratories, Inc.	88
Marco Products Co.	92
Mark Products	16
Master Mobile Mounts	20
Millen, James Mfg. Co., Inc.	10
Multicore Sales Corp.	104
Music Associated	98
National Radio Company, Inc.	Cover III
New-Tronics Corporation	94
Partridge Electronics, Ltd.	18
Pennwood Numechron Co.	104
Petersen Radio Company, Inc.	91
Quarter Century Wireless Association, Inc.	94
Radio Amateur Callbook Inc.	96
RCA Electronic Components and Devices	Cover IV
REC Club	106
R.F. Communications	17
Rohn Manufacturing Co.	12
Shure Brothers, Inc.	105
Sideband Engineers	15
Space Electronics	95
Subscription, CQ	80, Insert
Swan Electronics Corp.	8, 9
Technical Library	93
Teleplex Co.	99
Telrex Laboratories	99
Texas Crystals	99
Topaz, Inc.	88
Tribander	94
U. S. Fiberglass Co.	105
Vero Electronics Inc.	24
Waters Manufacturing, Inc.	21
Western Radio	92
WRL World Radio Laboratories, Inc.	100, 107

BREAK

THROUGH

\$450⁰⁰
 Includes Separate
POWER SUPPLY

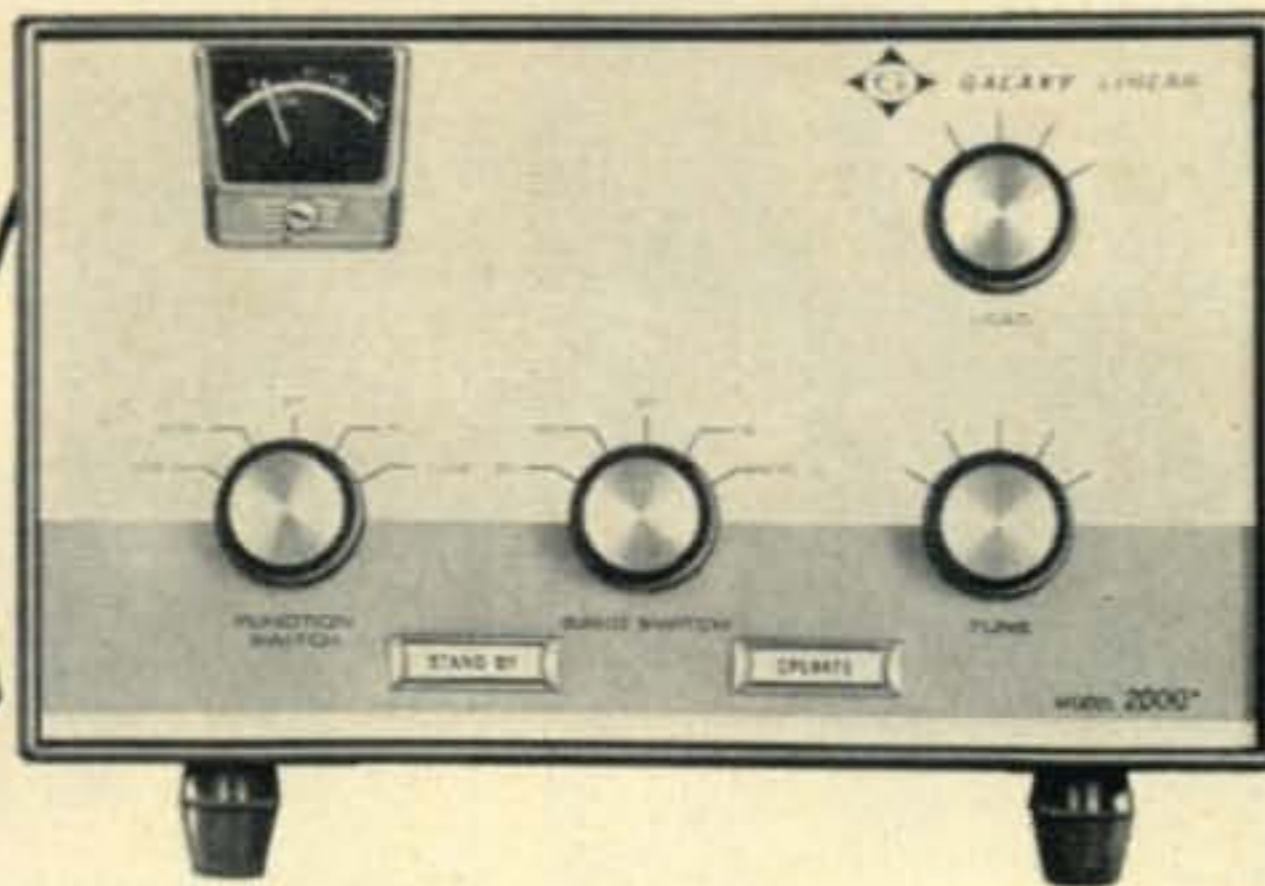

**MORE
 "TALK POWER"
 PER DOLLAR
 Than Ever Before!!**

**WRITE US NOW
 FOR KING SIZE TRADE-INS ON
 YOUR PRESENT GEAR!**

**NOW FOR THE FIRST TIME
 2KW+ TABLE TOP LINEAR FOR UNDER \$500.00
 GUARANTEED! 2KW+ PEP SSB INPUT and 1200
 WATTS PEP OUTPUT, ALL BANDS 80
 THROUGH 10 METERS.**

EXCLUSIVE GALAXY LINEAR FEATURES

- * *Revolutionary new circuit.* Sustains Hi-Efficiency 10-80 Meters.
- * *Most compact 2KW Linear ever made.* R.F. unit just 6" x 10¹/₄" x 11¹/₄". Same as Galaxy III and V.
- * *NEW ALS! (Automatic Linearity System)* An improvement over conventional ALC.
- * *MOST TALK-POWER EVER* in this small size.
- * *Operates AB₁* at all times.
- * *Built-in antenna switching relays.*

MORE OUTSTANDING FEATURES

- * *INPUT: 2,000 Watts PEP-SSB, 1,000 Watts-CW, 1,000 Watts-RTTY.*
- * Complete tube replacement cost under \$30.00.
- * Uses ten 6HF5's in new, efficient design.
- * Full Power from any 100-200 watt output exciter.
- * Tubes fan cooled for longer life.
- * SIMPLIFIED, reduced power tune-up.
- * One knob bandswitching, 80 through 10 meters.
- * High efficiency PI-NET, matches 40/90 Ohms impedance.
- * Built-in, adjustable low-pass filter.
- * 3rd order distortion - 30DB.
- * 115/230 VAC power supply.
- * Shipping weight (Linear and Supply) Approx. 55 lbs.

POWER SUPPLY

Heavy duty power supply has 115/230 VAC primary, conservative 2KW CCS rating with grain-oriented silicon steel core, solid state rectifiers. All cables supplied. Power supply can be placed under desk for operating convenience. Protected by attractive cover.



**GET
 YOUR
 FREE
 '66 CATALOG**

WRL

**WORLD RADIO
 LABORATORIES**

3415 West Broadway
 Council Bluffs, Iowa 51504


- Send information on Linear Amplifier.
- Send quote on separate sheet.
- Send new catalog.

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

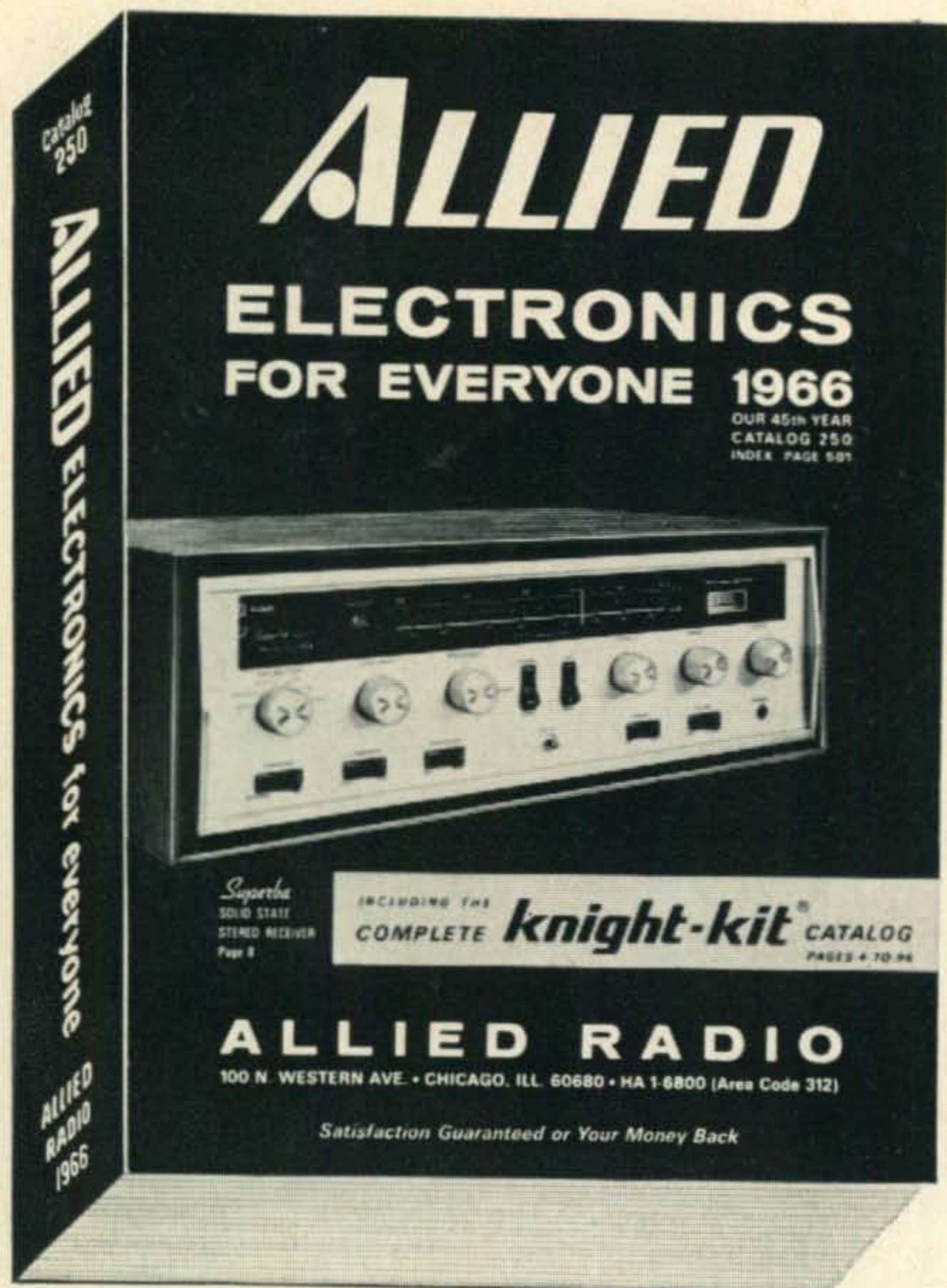For further information, check number 38, on page 106



FREE

send today for
your 508-page

ALLIED


1966 CATALOG



the catalog every ham uses biggest selection, biggest savings

It's your one dependable source for everything in station gear, for everything in electronics. You know, too, you can rely on our staff of over 100 licensed hams to give you the kind of ham-to-ham help you want—in *every* way. Get the 1966 Allied Catalog now—it's invaluable for your shack.

FREE send for it!

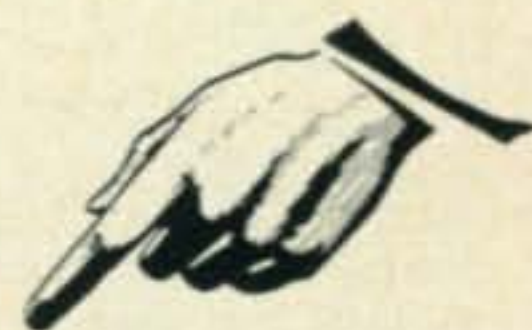

get every Ham buying
advantage—plus
top dollar for trade-ins



EASY TERMS, TOO
Use the Allied Credit Fund
Plan—over 24 months to pay.

ALLIED RADIO
serving the Amateur for 45 years

ALLIED RADIO, Dept. 12-M
100 N. Western Ave., Chicago, Ill. 60680

Send FREE 1966 Allied Catalog.

Name _____
PLEASE PRINT

Address _____

City _____ State _____ Zip _____

For further information, check number 48, on page 106

Index to CQ Vol. 21-1965

AERIALS, ANTENNAS, TOWERS, TRANSMISSION LINES

Antenna Section (Scherer, W2AEF)	49, Jan.
Antenna Zoning; How It Works (Stoffel, WA2JTT)	52, Feb.
Coaxial Cable, How To Select (Camillo, K1RBO/9)	32, May
Coax Dummy Load for 200 Mc and Up, A (Lee, W6VAT)	35, Apr.
Four Square for Six Antenna, A (Daughtrey, K2EEM)	29, July
G4ZU X Beam for 20, The (Schultz, W2EEY/DJØBV)	26, June
Half Wavelength Vertical, A (La Farra, W5ZCC)	57, Dec.
Homebrew Slot Antenna, The (Baldwin, K4ZQR)	26, Feb.
Long Wire Antenna Tuner (NOVICE)	77, June
Perfect Dummy Load, The (Fransen, VE6TW)	50, Nov.
Performing Pulley, The (Fox, W8PZX)	38, June
Portable Beam for Six Meters, A (Lumachi, WB2CQM)	45, Sept.
"Throw Away" Beam, The (Jablin, W2QPQ)	63, Aug.
Tracking A Power Pole (Fuller, W2FZJ)	39, Sept.
"V" Beam Antenna, A (Lumachi, WB2CQM)	30, Aug.

AUDIO AMPLIFIERS—MODULATION

Inverted DSB On Two Meters With The SCR-522 Transmitter (Warden, W4PGI)	45, Feb.
Need An Audio Oscillator (Scherer, W2AEF)	47, Jan.
Simple Improvement For The ART/13 Speech Amplifier, A (Greenberg, W2EEJ)	28, Jan.
Waters Model 359 Compreamp, CQ Reviews: The (Scherer, W2AEF)	43, Feb.

COMMERCIAL EQUIPMENT

Antenna Section (Scherer, W2AEF)	49, Jan.
Clegg Apollo Six Linear, CQ Reviews: The	59, Sept.
Clegg 22'er, CQ Reviews: The	62, June
Dow-Key DK78 Switches, CQ Reviews: The	52, Mar.
Galaxy V Transceiver, CQ Reviews: The	63, July
Hallicrafters 2 and 6 Meter Transceivers, CQ Reviews: The	41, Aug.
Heathkit HO-13 Ham-Scan, CQ Reviews: The	57, Sept.
Justin Mobiltrans 40, CQ Reviews: The	40, May
Lafayette HA-350 Receiver, CQ Reviews: The	60, Feb.
Lafayette Mechanical Filter, CQ Reviews: The	43, Mar.
National HRO-500 Receiver, CQ Reviews: The	51, Nov.
National NCL-2000 Linear Power Amplifier, CQ Reviews: The	60, Jan.
New Components By Millen Mfg.	55, June
Transcom, CQ Reviews: The	49, Dec.
Tunaverter, CQ Reviews: The	58, Nov.
Vero Boards (Scherer, W2AEF)	35, Dec.
Waters Codax Automatic Keyer, CQ Reviews: The	48, July
Waters Compreamp, CQ Reviews: The	43, Feb.

COMMERCIAL EQUIPMENT MODIFIED

Collins KWM-2 On RTTY (RTTY)	88, Apr.
C.W. Monitor For Grid-Block Keyed Transceiver, A (D'Onofrio, W2PRO & Stark, K2OAW)	62, Apr.
Drake 2B, Adding Silicons to the (Fox, W8PZX)	65, June
EICO 772 On Ten, Putting The (Beck, K2QMM)	32, Apr.
Hallicrafters HT-32, Modifying The (Fox, W8PZX)	65, Feb.
Hammarlund Super Pro, A Product Detector For The (Sarovan, W6JPU)	34, July
Heath DX-60 Key Clicks (Sharp, W6DMY)	51, Sept.
Heath Twoer, Souping Up The (Brown, W6HPH)	35, Mar.
Knight T-150 As A SSB Linear, The (Hughes, VE2AUB/W5)	42, May
Planetary Drive, Add A (Lowenstein, W2HWH)	30, Mar.

S.S.B. Transmitters, F.S.K. For (Combs)	36, Feb.
Tubeless Product Detector, The (Brown, W6HPH)	41, Mar.
Volkswagen V.H.F. Mobile (Currell, K6UHZ)	45, Mar.
75A-4 SSB, Improvement The (Agrelus, K6SHA)	53, June
75A-4/HT-32 Transceiver, A (Spencer, W4HDX)	30, Apr.

CONTESTS—OPERATING

CQ 6th Annual 1965 160 Meter C.W. Contest, Results of the (O'Brien, W2EQS)	32, Aug.
CQ Spring 1965 V.H.F. Contest, Announcing the New Results	41, Apr. 42, Nov.
CQ Summer 1964 V.H.F. Contest, Results (Brown, K2ZSQ)	39, Jan.
CQ World Wide SSB Contest, Announcing The	47, Mar.
CQ 1964 World Wide DX C.W. Contest Claimed High Scores Results	74, Feb. 52, July
CQ 1964 World Wide DX Phone Contest Claimed High Scores Results	71, Jan. 56, June
CQ 1965 World Wide DX Contest, Rules	31, Sept.
CQ 12 Hour V.H.F. Contest, Announcing the Results 1964 French Contest (CONTEST CALENDAR)	61, July 71, Jan.
United States of America Counties Award Rules and Program, The	75, Jan.
WAZ and USA-CA Awards Honor Roll	54, Dec.
YL-OM 1965 Annual Contest, Rules Results	90, Jan. 91, July
YLRL 25th Anniversary Party Results (YL)	92, Feb.
YLRL 26th Anniversary Party Rules (YL)	94, Sept.

DX & DXPEDITIONS

Eyeball in the Far East (Weese, K6AJG)	47, Sept.
Lord Howe Holiday (Hall, VK2AGH)	36, Apr.
St. Helena Sojourn (Smillie, G3PEU/ZD7BW)	33, Feb.

HAM CLINIC

January, Page 84

NCX-3 Suggestions and Operational Hints
Reverse, Linear and Audio Tapers
SR-150 Intermittent
Transistorized Speech Clipper
Using 572-B Tubes as Replacements for 811A Tubes

February, Page 86

DX Transceiver Operation
DX-40 to 6 Meters
Power and Modulation Conversion Hints
Printed Circuit Boards
Product Detector With A.G.C.
Vertical Antenna Matching

March, Page 65

Comanche V.F.O. Intermittent
DX-40 Intermittent
DX-100 Rectifier Replacement
Heath OP-1 Scope Trouble
Seneca Drive
Shawnee Squelch Action
SR-150 R.F. Gain Control
Using the SB-10 SSB Adapter
32S Improved C.W. Operation
32S Vox Relay Time Constant Control

April, Page 82

Adding Additional Bands To Transceivers
Cross Modulation Attenuator
Drake 2-A Noise Limiter
NCX-3 Keying Monitor
Semiconductor Coding
SR-150 Pi Network
Transistor For Linear Operation
Voided Warranties

May, Page 73

ASB-5 Radar Receiver to 420 MC
 HQ-170 Calibrator
 HX-20 With 6146B
 KWM-2 On A.M.
 NCX-3 S Meter
 SX-117 Noise Limiter
 Texas Crystals 100 Kc Calibrator
 Transfilters in Oscillator Circuits
 Using Zener Diodes

June, Page 72

CR-88 Receiver Modifications
 HT-40 Mk-1 Questions
 Interference From a TV Set
 NCX-3 Power Increase
 Spotting Switch For The T-60
 SSB Ring Demodulator
 Using Clevite Transfilters
 Warm-Up Drift in Low Priced Receivers

July, Page 82

Adding a T Notch Filter to the BC-453
 Attenuating V.F.O. Signal Output In A Mixer
 Buying Hints
 Buying Used Receivers and Transmitters
 Counterfeit Transistors
 Interpreting Ads
 Making Baluns
 Photo-Stamps for QSL's
 Q Multiplier for High I.F.'s
 Schematic Drawing

August, Page 75

Coil Equivalents
 Converter Power Supply
 HT-32 and HT-32A Modification
 HT-33A Linear Modifications
 Improving GG 813 Operation
 KWM-2A Mike Gain Law
 SB-300 Noise Limiter

September, Page 83

Code Practice Oscillator
 Converter for 432 Mc
 Field Strength Meter
 GSB-201 Linear Modification
 HT-37 Vox Trouble
 KWM-2 Power Supply Modifications
 Miniature Scope Tube
 Oscillator Filament Transformer
 SB-300 60 Cycle Hum
 SR-150 V.R. Tube Replacement
 Super-Pro Power Supply
 Vertical Antenna Radials
 Viking KW Rectifiers
 1 Mc Schmitt Trigger
 3-1000Z Linear
 Gonset 903A and 913A 2M & 6M Linears

October, Page 73

A. F. Signal Generator
 All-Band Selectro-Booster
 Barefoot vs. High Power
 CB Set Conversion
 Peak and Peak-to-Peak Probe
 SB-400 L.S.B. Operation
 Silicon Diode Replacements
 Transceiver Hum
 U.H.F. Power Amplifier Tube
 Zener Diode Noise

November, Page 85

BC-610 to S.S.B.
 Galaxy III and V Operational Hints
 Increasing Dipole Gain on 144 MCS
 Nickel-Cadmium Batteries
 Reciprocal Operations
 SR-150 Lower Sideband Operation
 Transmission Impedance Line Matching
 500-1000 Cycle Tracing Oscillator
 7360 Sheet Beam Tube Stability

December, Page 74

HW-32 Final Modification
 Integrated Circuits
 Joystick
 KWM-2 Power Supply Modification
 Second Mixer Revision for 75A-4
 1625 GG Amplifier

KEYING, BREAK-IN AND CONTROL CIRCUITS

Automatic CQ Sender, An (Schultz, W2EEY/DJ0BV)	48, June
Automatic Station Identification with a Surplus Keyer (Kanda, K0MHU)	50, May
C. W. Monitor For Grid-Block Keyed Transceivers, A (D'Onofrio, W2PRO & Stark, K2OAW)	62, Apr.
DX-60 Key Clicks (Sharp, W6DMY)	51, Sept.
Keying Relay And Monitor (Marriner, W6BLZ)	45, Oct.
Self Powered C. W. Monitor (Wrench, W0MQB)	36, Aug.
Touch-Key Additions (Jackson, VE3QQ)	59, Feb.
Vox Key, The (Horst, W9CUX)	29, Jan.

LEGAL

Antenna Zoning; How It Works (Stoffel, WA2JTT)	52, Feb.
Conducting The Novice Exam (NOVICE)	75, Mar.
FCC Docket 15928: How Do You React? (Pyle, W7OE)	37, July
Important Tower Case Precedent Set In New York (Froude, WA2TEQ)	8, Sept.
Reciprocal Licensing in Great Britain (Jacobs, W3ASK)	90, May
RM-499 FCC Denial and New Proposed Rule Making	8, May
Victory for W0JRQ Antenna Trial (Sando, W5RZJ)	41, May
WA2RAU vs. City Hall In Tower Case (Caposella, Jr. W2IWC)	59, Nov.

MISCELLANEOUS: GENERAL

Amateur Ingenuity (Marriner, W6BLZ)	64, Oct.
Clean Up Your Shack! (Pyle, W7OE)	43, Apr.
Conducting The Novice Exam (NOVICE)	75, Mar.
Cortlandt Street Story, The	30, Oct.
CPR Award, The (Joachin, OK1WI)	57, Mar.
Cranium Queries—Counties Gram	34, Apr.
Cranium Queries—Crossword Puzzle	52, May
Developing A DX Voice (Heisseluft)	51, Apr.
Early DX (Marriner, W6BLZ)	62, Sept.
G Stroke T—Television (Miller, W9NTP)	33, Sept.
Geneva A Go-Go	63, Sept.
Grebe Story, The (Gray, W8JDV)	36, May
HI8XL Provides Communication During Dominican Crisis	87, Sept.
Kitcraft (Beck, W2CE)	62, Aug.
Laser Dangers (Bloom, W0HJL)	38, Sept.
Learn By Mistakes (Adler, K8IKA)	48, May
Near Disaster, A (Marriner, W6BLZ)	64, Feb.
Origin of "Wireless Telegraphy," The (Marriner, W6BLZ)	28, July
Quiet Weekend In London, A (Margolis)	49, Sept.
Quiet Weekend With the Jet Set, A (Margolis)	59, Dec.
Radio Inspector—1920 Style, The (Marriner, W6BLZ)	60, Aug.
Story of Collins Radio, A (Marriner, W6BLZ)	48, Aug.
Story of Communication, The (Marriner, W6BLZ)	45, June
Teaching Morse Code or Why Johnny Can't Reach 13 W.P.M. (Gleit, WB6FJS)	22, Mar.
"Ultimate" QTH, The (Fisher, W2MXJ)	39, July
UN Amateur Radio Club, The (Ellis)	54, Feb.
Who Is Durward Tucker?	51, Apr.
Who Says 160 Is Dead? (O'Brien, W2EQS)	61, May
Writing For CQ? (Higgins)	31, Jan.
YL Net Listing (YL)	94, Nov.

MISCELLANEOUS: TECHNICAL

Care And Feeding of Linear Amplifiers, The (Chapin, W2DUD)	52, Dec.
Coaxial Cable, How To Select (Camillo, K1RBO/9)	32, May
Common Ground, The (Brickey, W7QAG)	49, Mar.
Designing High Power R.F. Attenuators (Marriner, W6BLZ)	49, Feb.
Dimple Those Shields (Jackson, VE3QQ)	26, Aug.
Homebrew Dial For Slug Tuned VFO's, A (Lowenstein, W2HWH)	63, Nov.
Ideal Mobile, The (Jacobs, WA0AIY)	44, Aug.
Quieting Ignition Systems (Glanzer, K7GCO)	32, Feb.
Rack Cabinet Door Holder (Ives)	40, Oct.

R. F. Filtered Lamps (Dezettel, W9SFW)	54, Mar.
Slug Tuned Coils (Baldwin, K4ZQR)	38, Apr.
Some Notes On The International Quiet Sun Year (Hearsum, W8LUZ)	36, June
Ten Minute Minder, The (Ouellette, VE3DSF)	60, May
"Third" Method—Is It Worthwhile? The (Johnson, ZL2AMJ)	49, June
Varactor Harmonic Generators (LaHiff, W2IVT)	65, Aug.
Varactor Multipliers for V.H.F. (Thorpe)	44, Jan.
Watch Those Filaments (Marriner, W6BLZ)	62, Nov.
Why Two Switches When One Will Do? (Tellefsen, W7SMC/6)	50, July
\$10.00 Phone Patch, The (Klappenberger, K3KWX)	34, June

POWER SUPPLIES

General Purpose Power Supply (NOVICE)	88, Sept.
Improving Power Supply Regulation (Glanzer, K7GCO)	28, Mar.
Isolated A. C. Control Center, An (Lee, W6VAT)	57, Nov.
Silicon Diodes and Common Sense (Gunther, W6THN)	53, Sept.
Surplus Power Transformers (Orr, W6SAI)	46, Oct.

RADIOTELETYPE

AN/FGC-1 Terminal Unit (RTTY)	88, July; 90, Aug.; 91, Sept.; 87, Oct.; 92, Nov.
Automatic Station Identification With A Surplus Keyer (Kanda, K0MHU)	50, May
Autostart Discussion (RTTY)	89, Jan.; 79, Feb.; 87, Mar.
Close Look At Transistorized RTTY, A (Hill Jr. & Hill III)	66, Nov.
F.S.K. For S.S.B. Transmitters (Combs)	36, Feb.
KWM-2 On RTTY (RTTY)	88, Apr.
Modifying the TH-5/TG Terminal Unit (May, W5AJG)	44, Apr.
RTTY From A to Z (Tucker, W5VU)	
Part VI, Receivers for RTTY, AFSK	24, Jan.
Part VII, The Converter	55, Feb.
Part VIII, The W2PAT and W2JAV Converters	31, Mar.
Part IX, Polar Relay Construction	46, Apr.
Part X, Polar Relay Adjustment	63, May
Part XI, Modern Polar Relay Replacements	39, June
Part XII, Distortion in Relays	43, July
Part XIII, Eliminating Distortion	50, Aug.
Part XIV, Unusual Circuits in RTTY	65, Sept.
Part XV, Schmitt Trigger Circuit	49, Oct.
Part XVI, Polar Relay Test Set	37, Nov.
Part XVII, Polar Relay Test Set Operation	37, Dec.
RTTY Tuning Indicator and Squelch, An (Combs)	25, Mar.

RECEIVERS AND RECEIVING

Adding Silicons to the Drake 2B (Fox, W8PZX)	65, June
AN/APR-4Y Receiver, The	33, Oct.
ARC-Port On 40 Meters, The (Marriner, W6BLZ)	41, Oct.
Command Sets (White)	34, Oct.
Crystal Controlled Command Sets (White)	43, Oct.
Improving The 75A-4 On SSB (Agrelus, K6SHA)	53, June
Modifying The BC-652A Receiver (Taylor, K9ALD)	39, Oct.
Modifying the R-390/URR (Dell, W0AXQ)	37, Jan.
Preamp for 2 Meter F.M., A (Kretzman, W2JTP)	26, Sept.
Product Detector for the Super Pro, A (Saroyan, W6JPU)	34, July
Putting the APX-6 on 1215 mc (Brown, K2ZSQ & Katz, K2UYH)	
Part I	53, Oct.
Part II	46, Nov.
Putting the R-19/TRC-1 on 6 Meters (Oberto, K4GRY)	33, July
Putting the URC-4 on 50-144-220 (Brigham, W3TFA)	26, Oct.
QRM Killer, A (The Shelbytron) (Shelby, W6RIS)	30, Sept.
Replacing R. F. Amplifier Tubes (Frankart, WB6BLA)	48, Mar.
Second Generation No-Clobber Converter for 2 M. (Thompson)	55, Mar.
Simple BFO, A (NOVICE)	77, May
Simple 432 MC Paramp, A (Jones, W6AJF)	37, Aug.

Simple-Gen Receiver, The (Marriner, W6BLZ)	29, Feb.
Souping Up The Twoer (Brown, W6HPH)	35, Mar.
Three Transistor 6 Meter Converter, A (Tartas, W2YKT)	45, May
Transistorized 6 Meter Converter by K5DOR (VHF)	73, Mar.
Tubeless Product Detector, The (Brown, W6HPH)	41, Mar.
Using Audio Controlled A.G.C. for Improved Receiver Selectivity (Taylor, W2OZH)	33, Dec.
W4HJZ Two Meter Converter, The (Ehardt, W4HJZ)	29, June
75A-4/HT-32 Transceiver, A (Spencer, W4HDX)	30, Apr.
432 Mc Preamp by WA2FSQ (VHF)	82, Nov.

SPACE COMMUNICATIONS

Early OSCAR IV Information (Space)	83, Dec.
Expected Launchings (SPACE)	77, Feb.
HI OSCAR De WA2WEB (Dunkerley, Jr., WA2INB)	40, July
K2IEJ and K9AAJ QSO Via OSCAR III	56, May
Late OSCAR News	51, July
Oscalator, The (Scherer, W2AEF)	54, Aug.
OSCAR Notes (Scherer, W2AEF)	32, Dec.
OSCAR III, An Active Communication Satellite For Radio Amateurs, Part II (Jacobs, W3ASK)	38, Feb.
OSCAR III Telemetry Data (SPACE)	68, Mar.
Transmitting Satellites (SPACE)	78, Feb.; 90, Nov.
We Made It Into Space! (SPACE) (Jacobs, W3ASK)	53, May
W5LFL To Join Astronauts! (Orr, W6SAI)	7, Aug.

SURPLUS

AN/APR-4Y Receiver, The	33, Oct.
ARC-Port On 40 Meters, The (Marriner, W6BLZ)	41, Oct.
Command Sets (White)	34, Oct.
Crystal Controlled Command Sets (White)	43, Oct.
Grinding Surplus Crystals (Sherrard, K9VHA)	52, Oct.
Improved LM Accuracy (Hopper, W1MEG)	38, Oct.
Inverted DSB On Two Meters With the SCR-522 Transmitter (Warden, W4PGI)	45, Feb.
Modifying the R-390A/URR (Dell, W0AXQ)	37, Jan.
Modifying the TH-5/TG Terminal Unit (May, W5AJG)	44, Apr.
Putting the APX-6 on 1215 Mc (Brown, K2ZSQ & Katz, K2UYH)	
Part I	53, Oct.
Part II	46, Nov.
Putting the R-19/TRC-1 On 6 Meters (Oberto, K4GRY)	33, July
Putting the URC-4 on 50-144-220 (Brigham, W3TFA)	26, Oct.
Simple Improvement for the ART/13 Speech Amplifier, A (Greenberg, W2EEJ)	28, Jan.
Surplus Power Transformers (Orr, W6SAI)	46, Oct.
Test Unit for the T23/ARC-5, A (Fortner, W9FYM)	42, Jan.

TEST EQUIPMENT

Direct Reading Capacity Meter, A (Erdman, W8VWX)	35, Nov.
Harmonic Rich 100 Kc Crystal Calibrator (Scherer, W2AEF)	28, Dec.
High Gain Field Strength Meter (Smith, WA4DXP)	48, Jan.
Homebrew Your Meter Scales (Erland, K0GBT)	49, Nov.
Improved LM Accuracy (Hopper, W1MEG)	38, Oct.
Measuring The Frequency Response of S.S.B. Transmitters (Dezettel, W9SFW)	61, Nov.
Mixer Spurious Frequency Analysis (Lee, W6VAT)	42, Sept.
Need An Audio Oscillator? (Scherer, W2AEF)	47, Jan.
Poor Man's Frequency Sinder, The (Wennerberger, WA4PXR)	45, Apr.
RTTY Tuning Indicator and Squelch, An (Combs)	25, Mar.
Sugar Coated Metering (De Maw, W8HHS)	37, Sept.
Test Unit for the T23/ARC-5, A (Fortner, W9FYM)	42, Jan.
Transmitter Tune-Up Meter (NOVICE)	76, May

TRANSMITTING

ARC-Port On 40 Meters, The (Marriner, W6BLZ)	41, Oct.
Care and Feeding of Linear Amplifiers (Chapin, W2DUD)	52, Dec.

C. W. Monitor For Grid-Block Keyed Transceivers, A (D'Onofrio, W2PRO & Stark, K2OAW)	62, Apr.
Designing High Power R. F. Attenuators (Marriner, W6BLZ)	49, Feb.
DX-60 Key Clicks (Sharp, W6DMY)	51, Sept.
F.S.K. For S.S.B. Transmitters (Combs)	36, Feb.
Inverted DSB On Two Meters With The SCR-522 Transmitted (Warden, W4PGI)	45, Feb.
Kilowatt Plate Tank Coil (Adler, K8IKA)	28, Feb.
Knight T-150 As A SSB Linear, The (Hughes, VE2AUB/W5)	42, May
KSSB-2 Sideband Exciter, The (Schofield, W1RIL)	26, July
Low Cost 440 MC Video Transmitter (VHF)	83, Feb.
Measuring The Frequency Response of S.S.B. Transmitters (Dezettel, W9SFW)	61, Nov.
Mixer Spurious Frequency Analysis (Lee, W6VAT)	42, Sept.
Modern Circuit Design for VHF Transmitters (Barber, W6GQK; Orr, W6SAI; Rinaudo, W6KEV; Sutherland, W6UOV)	
Part I	30, Nov.
Part II	40, Dec.
Need A VFO (Hart, W5QJR)	24, Feb.
Peanut Whistle, The (Wright, K4WWY)	59, Aug.
Putting the APX-6 On 1215 mc (Brown, K2ZSQ & Katz, K2UYH)	
Part I	53, Oct.
Part II	46, Nov.
Putting the EICO 772 On Ten (Beck, K2QMM)	32, Apr.
Putting The URC-4 On 50-144-220 (Brigham, W3TFA)	26, Oct.
Simple Improvement for the ART/13 Speech Amplifier, A (Greenberg, W2EEJ)	28, Jan.
Simplest, Cheapest, Smallest Rig, The (Ralston, WA9GRK)	32, July
Six Meter S.S.B. Transmitter, A (Johnson, WØURQ)	26, May
Souping Up The Twoer (Brown, W6HPH)	35, Mar.
"Third" Method—Is It Worthwhile?, The (Johnson, ZL2AMJ)	49, June
Triodes For Linear Amplifiers (Orr, W6SAI)	32, Jan.
TVI-Proof 21 Mc Exciter, A (Shoots, W6BMM/2)	40, Nov.
Varactor Harmonic Generators (LaHiff, W2IVT)	65, Aug.
Varactor Multipliers for V.H.F. (Thorpe)	44, Jan.
V.H.F./U.H.F. Output Circuitry (De Maw, W8HHS)	39, Mar.
16 Watt Rock Crusher, The (Alexander, W6IEL)	22, Jan.
75A-4/HT-32 Transceiver, A (Spencer, W4HDX)	30, Apr.
144 Mc to 432 Mc Varactor Tripler (VHF)	71, May

V.H.F. and U.H.F.

Coax Dummy Load for 200 Mc and Up, A (Lee, W6VAT)	35, Apr.
Four Square For Six Antenna, A (Daughtrey, K2EEM)	29, July
High Power VHF/UHF Dummy Loads (LaHiff, W2IVT)	35, July
Inverted DSB On Two Meters With the SCR-522 Transmitter (Warden, W4PGI)	45, Feb.
Low Cost 440 Mc Video Transmitter (VHF)	83, Feb.
Modern Circuit Design for VHF Transmitters, (Barber, W6GQK; Orr, W6SAI; Rinaudo, W6KEV; Sutherland, W6UOV)	
Part I	30, Nov.
Part II	40, Dec.
Portable Beam for Six Meters, A (Lumachi, WB2CQM)	45, Sept.
Preamp for 2 Meter F.M., A (Kretzman, W2JTP)	26, Sept.
Putting the APX-6 on 1215 Mc (Brown, K2ZSQ & Katz, K2UYH)	
Part I	53, Oct.
Part II	46, Nov.
Putting the R-19/TRC-1 On 6 Meters (Oberto, K4GRY)	33, July
Putting the URC-4 On 50-144-220 (Brigham, W3TFA)	26, Oct.
Second Generation No-Clobber Converter for 2 M. (Thompson)	55, Mar.
Simple 432 Mc Paramp, A (Jones, W6AJF)	37, Aug.
Six Meter S.S.B. Transmitter, A (Johnson, WØURQ)	26, May
Souping Up the Twoer (Brown, W6HPH)	35, Mar.
Three Transistor 6 Meter Converter, A (Tartas, W2YKT)	45, May
Transistorized 6 Meter Converter by K5DOR (VHF)	73, Mar.
Varactor Harmonic Generators (LaHiff, W2IVT)	65, Aug.
Varactor Multipliers for V.H.F. (Thorpe)	44, Jan.
V.H.F./U.H.F. Output Circuitry (De Maw, W8HHS)	39, Mar.
Volkswagen V.H.F. Mobile (Currell, K6UHZ)	45, Mar.
W4HJZ Two Meter Converter, The (Ehardt, W4HJZ)	29, June
144 Mc to 432 Mc Varactor Tripler (VHF)	71, May
432 Mc Preamp by WA2FSQ (VHF)	82, Nov.

got a match?

Definitely not. It's a cold fact that no competitive linear amplifier compares with National's NCL-2000—regardless of price. Take the time to look at the chart below and plug

in the specs of *any* amplifier next to those of the '2000 — not a single competitive unit in the maximum power classification offers even half the features of the NCL-2000:



FEATURE	NCL-2000	COMPETITION
POWER	Entire equipment I.C.A.S. rated for full 1000 watt average, 2000 watt peak input; output tubes and all RF components rated for C.C.S. operation. Power input and efficiency identical on all bands — 80 through 10 meters.	
SIZE	Completely self-contained, including power supply, in desk-top cabinet (dimensions only 7 ⁵ / ₈ " H, 16 ¹ / ₄ " W, 12 ³ / ₄ " D).	
DRIVE REQUIREMENTS	Adjustable passive grid input and use of high power ceramic tetrodes in final permits drive to full output with exciters delivering as little as 20 watts or as much as 200 watts.	
METERING	Separate rear-illuminated precision D'Arsonval plate and multi-meters for simultaneous measurements.	
ALC	ALC output to exciter for maximum talk-power with greatest linearity.	
SAFETY AND PROTECTIVE DEVICES	Fuses, time delay and plate current overload relays, plate power lid interlock and automatic HV mechanical shorting bar.	
CLASS OF OPERATION	Grid-regulated AB ₂ permits easiest tune-up, low drive power for maximum exciter linearity, and protection from destructive peak currents.	
EASE OF TUNE-UP	Internal dummy load in grid circuit makes adjustment of exciter into amplifier possible without turning on NCL-2000 and without radiating a signal.	
STYLING	Award-winning design matches NCX-5 transceiver and complements any equipment.	
GUARANTEE	National's exclusive One-Year Warranty.	
PRICE	Only \$685.00.	

The NCL-2000 is a rock-crusher of a rig built to *commercial* standards. That's why you get I.C.A.S.-rated maximum legal power in a one-piece desk-top package, and why you get ALC and drive power compatibility with high quality exciters. It's why you get two

precision meters, and sensible protection afforded by proper safety devices. Match the NCL-2000 with all the others before you buy — then see your National dealer for easy terms and trade-in deals.



NATIONAL RADIO COMPANY, INC.

37 Washington Street, Melrose, Mass. 02176 • World Wide Export Sales: Auriema International Group, 85 Broad St., N.Y.C.

For further information, check number 3 on page 106.



66* in '66

**Most sincere wishes for health, happiness + good cheer on this Christmas Day.*



RCA Electronic Components and Devices, Harrison, N.J.

*Message Sixty-Six (66) listed in ARRL Log Book.