

75 cents

hrc

focus
on
communications
technology . . .


ham radio

magazine

APRIL 1972

this month

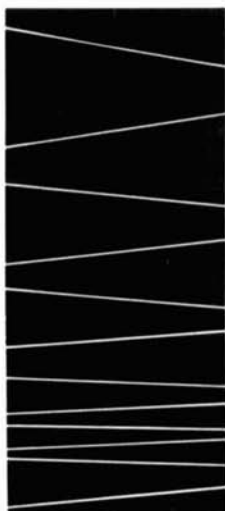- ssb two-tone tester 11
- tuning toroidal inductors 24
- direct-conversion receivers 32
- digital station accessory 36
- audio-actuated squelch 52



FM

TWO-METER

TRANSMITTER

Hallicrafters' Single Sideband/CW communications comes in many forms, backed by over 38 years of radio engineering experience and service to hams.



Hallicrafters' communications equipment has a world-wide reputation for high quality and reliability with hundreds of thousands of sets in every-day use by ham operators on every continent.

Hallicrafters' line features the latest state-of-the-art advances in amateur communications equipment with such exclusive features as receiver incremental tuning, amplified automatic level control, integral 2KW exciter/linear, P.A. tube balancing, amplifier cooling system, unique low-noise receiver circuitry, outstanding signal clarity and many other built-in features.

Dollar for dollar, Hallicrafters' Single Sideband/CW equipment gives you the best engineered package of built-in features, power and performance you can buy. All-American made, and supported with extensive service and parts inventory.

In other words, if you want the best, you should be talking with a Hallicrafters. Your local Hallicrafters distributor is ready to talk to you too. The Hallicrafters Co., 600 Hicks Road, Rolling Meadows, Ill., 60008 U.S.A. Phone: 312/259-9600. A Subsidiary of Northrop Corporation

**You should be
talking with a
Hallicrafters.**

CONSIDERABLY SPECIAL CONSIDERING THE SPECS

NEW 2 METER FM TRANSCEIVER Model SRC-146



Frequency	143-149 MHz (2MHz spread)
Number of channels.....	5
Supplied with 146.94 simplex, 146.34/.94 (same plug in crystals as SR-C826M)	
R.F. Output.....	1 watt minimum
Sensitivity.....	better than 0.4 uv/20 DB Q.S.
Audio output.....	500 mw
Meter	monitors battery voltage on Tx, S Meter on Rx
Current drain	400 maTx, 15 maRx SBY
Size.....	.8 $\frac{3}{8}$ " high x 3" wide, x 1 $\frac{5}{8}$ " deep
Weight	24 oz., less batteries

Options: external mic, or mic-speaker, stubby flexible antenna, desk top charger, leather case.

\$279⁰⁰
Suggested
Amateur
Net Price



Consider the new VHF-FM hand held Transceiver by Standard Communications Corp., with exclusive Astropoint design. For complete specifications and the name of your nearest dealer, write:

STANDARD COMMUNICATIONS CORP.

639 North Marine Avenue, Wilmington, California 90744, (213) 775-6284

Only an MC-4 can "top" a Drake TR-4

the optimum Sideband Transceiver



(Sometimes even
the MC-4 ends up
on the bottom . . .)



Adding an MC-4 Mobile Console, with its excellent wattmeter and built-in speaker, is the only way to improve a Drake TR-4.

BUILT-IN TR-4 FEATURES

- Full Frequency Coverage on all amateur bands 10 through 80 meters. No additional crystals required.
- 300 Watts PEP input on SSB.
- Shifted-Carrier CW 260 watts input
- Upper and Lower Sideband all bands.
- Controlled-Carrier Screen Modulator for AM
- VOX or PTT
- Output Impedance Adjustable with pi-net.
- Two Special 9 MHz Crystal Filters for sideband selection.
- 1 kHz Dial Accuracy.
- 100 kHz Crystal Calibrator
- Price \$599.95 Amateur Net

ACCESSORIES

MC-4 Mobile Console (shown in photos above)	\$ 69.00
MMK-3 Mobile Mounting Kit	\$ 6.95
AC-4 115/230 VAC 50/60 Hz Power Supply	\$ 99.95
DC-4 12 VDC Solid State Power Supply	\$125.00
34PNB Noise Blanker	\$100.00

TR-4 SPECIFICATIONS: • **Frequency Coverage:** Full coverage on all amateur bands 10 thru 80 meters, in seven 600 kHz ranges: 3.5 to 4.1 MHz, 7.0 to 7.6 MHz, 13.9 to 14.5 MHz, 21 to 21.6 MHz, 28 to 28.6 MHz, 28.5 to 29.1 MHz, 29.1 to 29.7 MHz. • **Solid State VFO:** Has linear permeability tuning. Tunes 4.9 to 5.5 MHz for all ranges. • **Dial Calibration:** 10 kHz divisions on main tuning dial and 1 kHz divisions on the tuning knob skirt. • **Frequency Stability:** High stability solid state VFO tunes same range on all bands. Drift is less than 100 cycles after warm-up, and less than 100 cycles for plus or minus 10% line voltage change. • **Modes of Operation:** SSB Upper and Lower Sideband, CW and AM. • **Misc:** 20 tubes including voltage regulator; two transistors; 8 diodes; 100 kHz crystal calibrator built in; Dimensions: 5 1/2" high, 10 1/4" wide, 14 3/8" deep. Weight: 16 lbs. . . . **TRANSMITTER:** • **Single Sideband:** 300 watts P.E.P. input power, VOX or PTT. Two special 9 MHz crystal filters provide upper or lower sideband selection on any band, without the necessity of shifting oscillators. • **CW:** Power input 260 watts. Carrier is shifted approximately 1000 cycles into one sideband, and mixer and driver are keyed. Grid block keying is free from chirps and clicks. Automatic transmit/receive switching when key is operated. CW sidetone oscillator for monitoring. • **AM:** Controlled carrier AM screen modulator is built-in. 260 watts P.E.P. input. Low carrier power increases 6 times to 50 watts output at maximum modulation. This system is compatible with SSB linears, VOX or PTT. Diode detector used for receiving on this mode. Product Detector can be used by switching manually. . . . **RECEIVER:** • **Sensitivity:** Less than 1/2 microvolt for 10 dB S/N • **I. F. Selectivity:** 2.1 kHz at 6 dB, 3.6 kHz at 60 dB. • **Antenna Input:** Nominal 50 ohms. • **Audio Response:** 400 to 2500 cycles at 6 dB. • **Audio Output Power:** 2 watts. • **Impedance:** 4 ohms.

MC-4 SPECIFICATIONS: • **Frequency Coverage:** 1.8-54 MHz • **Line Impedance:** 50 Ohm resistive • **Accuracy:** ± (5% of reading +3 watts) • **Power Capability:** 300 watts forward or reflected • **Controls:** Front panel 2-position switch selects forward or reflected power • **Speaker:** 3" x 5" oval, 2.98 ounce ceramic mag.

R. L. DRAKE COMPANY

540 Richard St. Miamisburg, Ohio 45342



DRAKE

Phone: (513) 866-2421

Telex: 288-017

April, 1972
volume 5, number 4



ham
radio
magazine

staff

James R. Fisk, W1DTY
editor

Douglas S. Stivison, WA1KWJ
assistant editor

Nicholas D. Skeer, K1PSR
vhf editor

J. Jay O'Brien, W6GDO
fm editor

Alfred Wilson, W6N1F
James A. Harvey, WA6IAK
associate editors

Curt J. Witt
art director

Wayne T. Pierce, K3SUK
cover

T. H. Tenney, Jr. W1NLB
publisher

Hilda M. Wetherbee
advertising manager

offices

Greenville, New Hampshire 03048
Telephone: 603-878-1441

ham radio magazine is
published monthly by
Communications Technology, Inc
Greenville, New Hampshire 03048

Subscription rates, world wide
one year, \$6.00, three years, \$12.00
Second class postage
paid at Greenville, N. H. 03048
and at additional mailing offices

Foreign subscription agents
United Kingdom
Radio Society of Great Britain
35 Doughty Street, London WC1, England

All European countries
Eskil Persson, SM5CJP, Frotunagrand 1
19400 Upplands Vasby, Sweden

African continent
Holland Radio, 143 Greenway
Greenside, Johannesburg
Republic of South Africa


Copyright 1972 by
Communications Technology, Inc
Title registered at U. S. Patent Office
Printed by Wellesley Press, Inc
Wellesley, Massachusetts 02181, USA

ham radio is available to the blind
and physically handicapped on magnetic tape
from Science for the Blind
221 Rock Hill Road, Bala Cynwyd
Pennsylvania 19440
Microfilm copies of current
and back issues are available
from University Microfilms
Ann Arbor, Michigan 48103

Postmaster: Please send form 3579 to
ham radio magazine, Greenville
New Hampshire 03048

contents

- 6 two-meter fm transmitter**
Ronald M. Vaceluks, W9SEK
- 11 ssb two-tone test oscillator**
Henry D. Olson, W6GXN
- 16 frequency-measuring oscillator**
Russell C. Alexander, W6IEL
- 20 21-MHz preamplifier**
Courtney Hall, WA5SNZ
- 24 tuning toroidal inductors**
Galen K. Shubert, WA0JYK
- 28 nostalgia with a vengeance**
Irving M. Gottlieb, W6HDM
- 32 direct-conversion selectivity improvements**
Vladimir N. Gercke, K6B1J
- 36 digital station accessory**
E. H. Conklin, K6KA
- 52 audio-actuated squelch**
Gene F. Greneker III, K4MOG
- 58 digital integrated circuits**
Edward M. Noll, W3FQJ
- 64 beam antenna headings**
Irvin M. Hoff, W6FFC
- 4 a second look**
- 110 advertisers index**
- 58 circuits and techniques**
- 72 comments**
- 99 flea market**
- 68 ham notebook**
- 74 new products**
- 110 reader service**

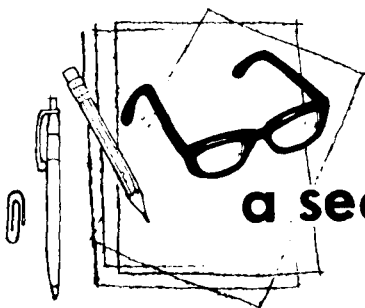

a second look

by Jim
fisk

Early this month a team of scientists from the Signetics Research and Development Department in Sunnyvale, California announced completion of a revolutionary new instrument that promises to transform every field of human endeavor, from radio communications to theology. Led by bio-electronics expert Dr. Ulfias Stopgapski, famous for his theory of positive retrogression, the team unveiled the instrument, called the *omphalometer*, on the first of April.

"The instrument is the ultimate outgrowth," Dr. Stopgapski said, "of my theory of retrogression. I first conceived the idea while assisting my good friend, Professor Ottmar Heissluft, catalog some Tibetan relics in Stanford University's Museum of Anthropology. We were cataloging what were reputed to be dried parts of the anatomy of the Yeti, the so-called Abominable Snowman of the Himalaya. These were actually dried navels. I noticed that no two were alike, and this led me to launch a small investigation of my own, involving several volunteers from the Life Sciences Department. Sure enough, all the navels were different."

By using the omphalometer (the name comes from *omphalo*, meaning navel, with the suffix *meter*, or "means for measuring") an operator can perform *omphaloskepsis*. This later technique is, in Dr. Stopgapski's words, "Mediation while gazing at the navel, as practiced by some mystics. This is the first electronic instrument in the world by which the American public can become mystics and omphaloskeptics at home. Monasteries and prolonged meditation are now obsolete."

After sample markets in the United States are tested, the instruments will be

exported to the Far East where the demand is expected to be enormous. It may also play a vital role in the Vietnamization Program, although details are reported to be classified.

With the latest scientific evidence showing that palmistry has some validity, the medical world is hailing the omphalometer as a significant new means of prognosis, for it establishes the pattern of the navel's convolutions and thus indicates the future course of a disease. In fact, a patient's *omphalospectograms* can be compared by computer with thousands of others to predict future events and future illnesses. To convert a standard omphalometer to medical use the operator merely attaches an *OmPhallus Probe* to the patient's navel.

Nor is medicine the only application for the versatile omphalometer. One security officer, speaking for the members of his profession, stated that the instrument will soon be installed at all plants that have won contracts from the Government. "It's a natural," he said, "No two belly-buttons are alike, and you know what that can mean to the surveillance and detection people. Why, heck, we'd do away with ID badges. All the employee would have to do would be to show his navel to an *OmphaloScanner*, and the door would open electronically, click-shoosh, at least if he didn't have anything to hide."

Jim Fisk, W1DTY
editor

My thanks to Roy Twitty, public relations manager of Signetics Corporation, for providing this bit of nonsense, which combines equal parts of St. Patrick's Day blarney and April Foolery.

AMATEUR ELECTRONIC SUPPLY

is the Best Place to purchase your new

DRAKE gear for the following reasons

- Performance
- Versatility
- Resale Value



TR-22



ML-2F



R-4B



2C



TR-4

ML-2F "Marker Luxury" 2m FM	\$329.95
TR-22 Portable 2m FM Transceiver	199.95
AA-22 Rec/Xmtr Amplifier - 12vdc	149.95
MMK-22 Mobile Mount	6.95
Extra crystals for ML-2F, TR-22 - each	5.00
DRS-1 Digitally Synthesized Receiver	2195.00
2C Receiver	255.00
2AC Calibrator for 2C	18.75
2CS Speaker for 2C	22.00
2CQ Speaker/Q-multiplier for 2C	39.95
2NB Noise Blanker for 2C	26.95
R-4B Receiver	475.00
MS-4 Speaker for TR-4/6, R-4B	22.00
TR-4 Transceiver 80-10 Meters	599.95
34PNB Noise Blanker (plug-in)	100.00
RV-4 Remote VFO for TR-4	110.00
FF-1 Crystal Control adaptor	46.95
TR-6 Transceiver - with noise blanker	650.00
RV-6 Remote VFO for TR-6	110.00
AM Plug-in Filter for TR-6	35.00
CW Plug-in Filter for TR-6	35.00
LSB Plug-in Filter for TR-6	35.00
AC-4 AC supply for TR-4/6, T-4XB	99.95
DC-4 12vdc Supply for TR-4/6	125.00
MMK-3 Mobile Mounting kit for TR-4/6	6.95
MC-4 Mobile Console for TR-3/4/6	69.00
2NT CW Transmitter	164.00
T-4XB SSB Transmitter	495.00
L-4B Linear Amplifier	825.00
MN-4 Antenna Match Network	99.00
MN-2000 Antenna Match Network	195.00
W-4 RF Wattmeter (2-30Mc)	61.95
WV-4 RF Wattmeter (20-200Mc)	73.50
C-4 Station Control Console	299.95
TC-6 6m Transmitting Converter	250.00
TC-2 2m Transmitting Converter	300.00
SC-2 Receiving Converter for 2m	76.00
SC-6 Receiving Converter for 6m	71.00
CPS-1 Power Supply for SC-2, SC-6	19.75
SCC-1 VHF Crystal Calibrator	26.95
CC-1 Converter Console	26.95
TV-300HP High-Pass Filter	4.95
TV-1000LP Low-Pass Filter	18.75
LN-4 Line Filter 120v 5 amp	8.00
729SRD Microphone with plug	17.00
SPR-4 Programmable Receiver	495.00
5NB Noise Blanker	65.00
DC-PC DC Power Cord	5.00
TA-4 Transceive Adaptor	15.00
SCC-4 Crystal Calibrator	20.00
RY-4 Teletype Adaptor	10.00
CRYSTAL KITS FOR SPR-4	
Aeronautical Overseas - 7 crystals	32.00
Amateur Bands - 6 crystals	27.00
Citizens Band - one crystal	5.00
Marine Bands - 11 crystals	49.00
MARS - 5 crystals	22.00
Teletype Commercial - 4 crystals	18.00
Time & Freq. Std., WWV - 5 crystals	22.00
Tropical Broadcast - 3 crystals	13.50

- TOP TRADES for your good clean equipment
- STAY-ON-THE-AIR PLAN - Enables you to keep your trade-ins until your new gear arrives - Lose no operating time!
- PERSONAL SERVICE from fellow hams who understand your problems.
- SAME DAY SERVICE on most Orders and Inquiries from our Centrally Located Modern Facilities
- Top Notch Service Department
- LARGE COMPLETE STOCK means Fast Deliveries. United Parcel Service available to most parts of the country. - UPS Blue label (AIR) to the West Coast.
- LOW LOW 1% Monthly Service Charge (ONLY 12% per annum) on GECC Revolving Charge Plan. Only 10% Down Plus LOW Monthly Payments - For Example: \$10 a month finances up to \$300, \$20 up to \$610. Write for complete information and credit application.

If you purchase any of the new Merchandise listed below at the Regular Price and Without a Trade-In, you may take the "Bonus" Credit indicated below toward the purchase of other merchandise (such as power supplies, antennas, towers, microphones, crystals, linears, accessories, etc.).

2NT Transmitter	\$10 Bonus	TR-4 Transceiver	\$50 Bonus
2C Receiver	\$20 Bonus	TR-6 Transceiver	\$60 Bonus
SPR-4 Receiver	\$40 Bonus	L-4B Linear	\$80 Bonus
R-4B Receiver	\$40 Bonus	ML-2 2M FM Xcvr	\$30 Bonus
T-4XB Transmitter	\$40 Bonus	TR-22 2M FM Xcvr	\$10 Bonus

SIX EZ-WAYS TO PURCHASE

1. CASH
2. C.O.D. (20% DEPOSIT)
3. MASTER CHARGE
4. BANK AMERICARD
5. AMERICAN EXPRESS
6. GECC REVOLVING CHARGE



Order Today
Direct from this Ad



Ray Grenier, K9KHW
Mgr. Mail Order Sales

TO: AMATEUR ELECTRONIC SUPPLY
4828 W. Fond du Lac Ave, Milwaukee, Wis. 53216

I am interested in the following new equipment:

I have the following to trade: (what's your deal?)

Ship me:

I Enclose \$ _____; I will pay balance (if any):
 COD (20% Deposit) GECC Revolving Charge Plan
 Master Charge* BankAmericard American Express

Account Number: _____

Expiration DATE _____ *Master Charge Interbank number _____ (4 digits)

Name: _____

Address: _____

City & State: _____

Send used gear list Send Drake literature

AMATEUR ELECTRONIC SUPPLY

4828 West Fond du Lac Ave. Milwaukee, Wis. 53216

Phone (414) 442-4200

HOURS: Mon & Fri 9-9; Tues, Wed & Thurs 9-5:30; Sat 9-3

CLEVELAND Area Hams may wish to visit our Branch store located at: 17929 Euclid Ave., Cleveland, Ohio, Ph. 486-7330, Pete Smith, Mgr. ALL Mail Orders and Inquiries should be sent to our Milwaukee store.



two meter fm transmitter

Reliability, economy
and proven design
characterize
this five-watt
fm transmitter

Ron Vaceluke, W9SEK, 17 West 540 Hillcrest, Wood Dale, Illinois 60191

In the September, 1970 issue of *ham radio*, Joe Price, WA9CGZ, and I described a 2-meter fm receiver and promised a companion transmitter. This is it! Our goals were similar to those laid down for our receiver: it had to give good performance without costing a fortune to build. Power output had to be adequate not only for repeater use but for point-to-point work as well. This meant that a power output of about 4 to 6 watts was desirable, without the use of vswr protection circuitry.

swr considerations

The lack of vswr protection may raise a few eyebrows, but let's consider this for a while. In the "good old days" when tubes were still being used, vswr protection was never thought of in a ham rig. No one in his right mind would operate his rig without an antenna connected

RMV Electronics, Box 283, Wood Dale, Illinois 60191 can supply a complete parts kit and assembly manual for this transmitter for \$59.95 plus \$1.40 postage. RMV also can supply just the printed-circuit board, coil forms and assembly manual for \$14.50, postage paid. The ferrite beads mentioned in the text are also available, nine for \$1.00, postage paid, from the same source. Illinois residents should add the 5% sales tax.

because the tube in the final amplifier would blush red before turning white hot and melting. Then the operator would blush and . . .

Of course, a tube was more forgiving; it could take more abuse before failing than could most transistors. A high *vswr* is not only rough on the transmitter but is also an indication that something is not performing properly, which usually amounts to poor efficiency. This results in having to run more power output to make up for losses in a poor antenna system. The cheapest way to improve not only transmitter output efficiency, but receiver sensitivity as well, is to use a good antenna with a low *vswr*. This, of course, holds true for any rig, on any band.

Occasionally things go wrong and damaging conditions can crop up (or *off* when the car wash chops the antenna from the car) which place the final amplifier in jeopardy. Most commercial rigs have *vswr* protection circuits built in because of economic necessity. After all, it's far better to install an inexpensive rf power transistor and its attendant protection devices than to invest in a good unprotected rf power transistor. The only problem with this is that protection circuits often fail at times when they are needed the most.

The transistor used in our design is made by Fairchild Microwave and Optoelectronics, part number MSA8508. This device was chosen after testing less expensive devices which would blow when the load was removed or the antenna jack was shorted. The MSA8508 withstood this test as well as *vswr* from unity to infinity.

crystal oscillator

The crystal oscillator was next in line for a shakedown. I felt that an oscillator that could be switched remotely would be more desirable than one which had to have its crystal switch placed right at the transmitter board. Early attempts at switching the crystals with diodes did not work out very well because of the diodes'


change of junction capacitance and resistance with change in temperature. Commercial two-way radio equipment has always used a separate oscillator for each frequency, and it's easy to see why. This, then, was our choice also; four channels would be a good start and could be added to, if desired. If maximum stability is desired, use a good quality crystal manufactured by a reputable firm. Buying poor grade crystals is false economy. We recommend the 0.0005% temperature and frequency tolerance; crystals will vary widely from unit to unit even though they are made by the same manufacturer.

circuit description

Each oscillator has its emitter lead brought out to a terminal which is grounded for operation and left open if not used. A diode is included in each emitter lead to provide isolation and prevent false operation if other voltages are present on the frequency-selector switch contacts. The output of each oscillator is connected to the input of a buffer amplifier, Q1, which is slightly forward biased.

Following the buffer is an MPF102 fet phase modulator, Q2. This has both the rf and audio applied to its gate input and produces a phase-modulated signal at the output. A slight amount of a-m is also produced but is removed by the following stages. Transistors Q3 thru Q6 are all frequency doublers which multiply the 9-MHz signal sixteen times to the resultant 144-MHz signal which is applied to Q7 for further amplification. The outputs of Q4, Q5 and Q6 are all double-tuned to reduce the passage of undesired frequencies which are usually present.

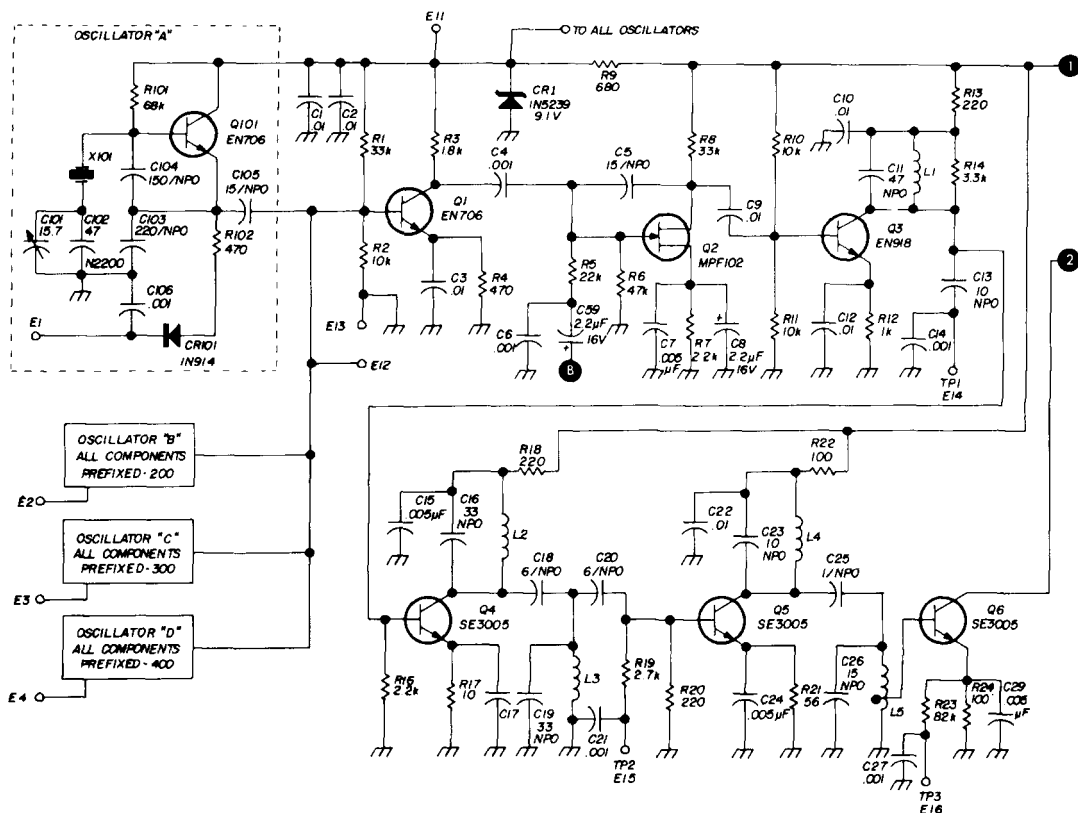Transistor Q7 is a straight-through amplifier and uses a Motorola 2N4427. I emphasize the manufacturer of this device because I found that transistors carrying the same number by a different manufacturer could not produce the output required while the Motorola units did. This conclusion was not reached on



C32, C48, C54,
C101, C201, C301, C401
1.9-15.7 pF variable

C37
8-60 pF variable

C43
7-100 pF variable

C44
37-250 pF variable

L1
21 2/3 turns no. slug tuned. This and all other coils have an inner diameter of 0.215 inches.

fig. 1. Schematic of the two-meter fm transmitter.


the basis of one rig but of many that have been built. A HEP S3001 is also a good choice for Q7.

The rfc's in the base leads of Q7 and Q8 consist of a 10-ohm resistor and two ferrite beads. The rfc in the base lead of a power-amplifier stage can be the cause of many headaches to someone trying to get one of these devices to work. A choke with a high Q can cause the stage to be highly unstable, while a very low-Q choke will begin to shunt some of the drive and therefore, be wasteful. I found the present value by cut-and-try. The final amplifier, Q8, produces approximately 5- to 6-watts output which can be connected to an antenna or a power amplifier.

Use a 50- μ A meter or vom for metering. Test point TP6 uses a capacitive divider and diode rectifier to indicate relative rf output. All other test points except TP3 measure the developed base bias of the stage being checked; TP3 measures the emitter voltage of Q6.

audio stages

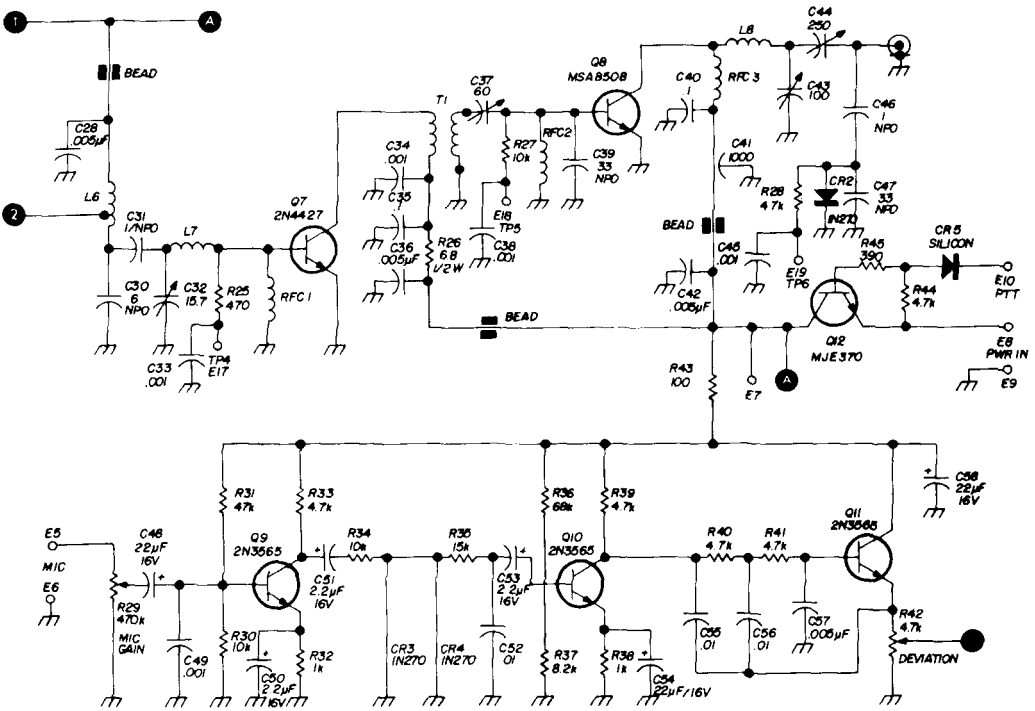Transistors Q9 thru Q11 amplify the low output from the microphone to the level necessary for the modulator stage. The input is designed for a dynamic microphone. Two controls are provided in the audio stages. R42 is the deviation control which, when set at maximum, will give about 10-kHz deviation. The microphone gain control, R29, is used to



- L2, L3 7 1/3 turns no. 24, slug tuned
- L4 7 1/3 turns no. 22, slug tuned
- L5 7 1/3 turns no. 22, slug tuned, tapped at 1 2/3 turns
- L6 4 2/3 turns no. 20, air wound
- L7 7 turns no. 20, air wound

- L8 2 turns no. 18, air wound
- RFC1, RFC2 2 ferrite beads and a 10 ohm, 1/2 watt resistor
- RFC3 5 3/4 turns no. 20, air wound
- T1 5 1/2 turns no. 20, primary, 1 1/2 turns no. 20, secondary interwound with primary

compensate for the output level of the different type microphones that may be used with the rig. Do not use R29 for deviation adjustment because you want as much audio as can be tolerated by Q9. This is because the semilog clipping action of diodes CR3 and CR4 depend upon a strong audio signal being delivered to them. If the output of the microphone, compressor or RTTY afsk generator is very high, Q9 will be driven to the point of distortion; R29 should be set just below this point.

Transistor Q12 switches power on during transmit and off during receive. Normally the transistor is not conducting — it's like a switch that is open. However, when the cathode of diode CR5

is grounded, Q12 will conduct, and the switch is closed. Power is distributed to all circuits through a liberal amount of decoupling circuits. These decoupling circuits are highly recommended to minimize stray coupling through the power distribution circuitry. Part of the decoupling scheme used on Q6, Q7 and Q8 is ferrite beads; they perform this function well at these frequencies.

Power for the oscillators is derived from zener diode CR1 and limiting resistor R9, providing regulated 9.1 volts. Voltage to the transmitter should be kept between 12 and 15 volts. Five-watts output will be easily obtained at 13.6 volts; this is the average voltage found on an automobile battery that is being

charged with a running automobile engine.

The transmitter is built on a 3 x 7-inch double-sided G-10 printed-circuit board. The top surface is used as the ground with all remaining conductor paths on the bottom. Most of the resistors are mounted vertically to save space. If PC-board construction is not desired it can be built on perforated board, but be certain to allow a wide ground path for best results.

Heat sink Q7 with a finned dissipator and bolt Q8 to a piece of $2\frac{3}{4} \times 2\frac{1}{2} \times 1/8$ -inch aluminum. Heat conduction of these devices to their respective heat sinks is enhanced by the use of Wakefield no. 122 thermal compound which is recommended over the usual silicone grease commonly used a few years ago.

tuneup

Initial tuneup is done in three steps. Power is left off Q7 and Q8 while all remaining stages are tuned. Install a crystal in oscillator A and ground lead E1. Apply +13 volts to lead E8 and -13 volts to any convenient ground point. Measure the voltage at the collector of switching transistor Q12 (point E7) and observe no—or very little (0.1 to 0.2 volts)—voltage. Momentarily ground lead E10 and the voltage out of Q12 should be around 12.5 volts. If the voltage is much lower than this, remove the ground from lead E10 and remove all power from the rig before trying to find out what's wrong. Assuming, however, that the proper voltage is available from Q12, tuneup can begin.

Note that all test points except TP3 produce negative current. Connect a 50- μ A meter to TP1 and tune L1 for maximum. Tune L2 and L3 for a maximum reading at TP2 and L4 and L5 for a maximum reading at TP3. Connect the meter to TP4 and tune L6 and C30 for a maximum reading (considerably lower than the readings obtained at the previous test points).

Proceed by connecting power to Q7 and metering the base circuit of Q8 at

TP5. Tune C37 for a maximum reading; this should be about 25 μ A or more. If everything has functioned well up to this point, the final amplifier, Q8, can now get the smoke test. Connect the output to a load which will present a low vswr at 144 MHz. If a wattmeter is available, connect it to the output circuit. If a wattmeter is not used, connect a meter to TP6. Apply power to all stages and tune C43 and C44 for maximum; power output will be between 6 and 7 watts. Now reduce the output power to 5 watts by using C43 and C44.


You reduce power because it is better to run the output stage a little cooler than to push for maximum with its higher collector current. The value of collector current will vary under changes of vswr, and some values of vswr can drive the collector current close to the transistor's absolute maximum rating. By backing off on the power output/collector current slightly, the current will never reach this high limit even with a high vswr. It may be wise to meter TP6 continuously when using the rig to ensure proper operation because a high vswr will give a higher reading at this point than is normally obtained under low vswr conditions. Although the final transistor can operate under these adverse conditions, efficiency is poor, and it should be adjusted for maximum performance.

Speaking of performance, always use an antenna which has been cut to frequency by means of an swr bridge and not just by the antenna manufacturer's cutting chart. In the case of mobile installations especially, the location of the antenna can cause the required antenna length to vary quite a bit compared to what the cutting chart shows. If at all possible, use a gain antenna rather than a ground plane or a short whip. An antenna with 3-dB gain is the same as doubling your power into a unity-gain device.

reference

1. Ronald Vaceluke, W9SEK, and Joseph Price, WA9CGZ, "An FM Receiver for Two Meters," *ham radio*, September, 1970, page 22.

ham radio

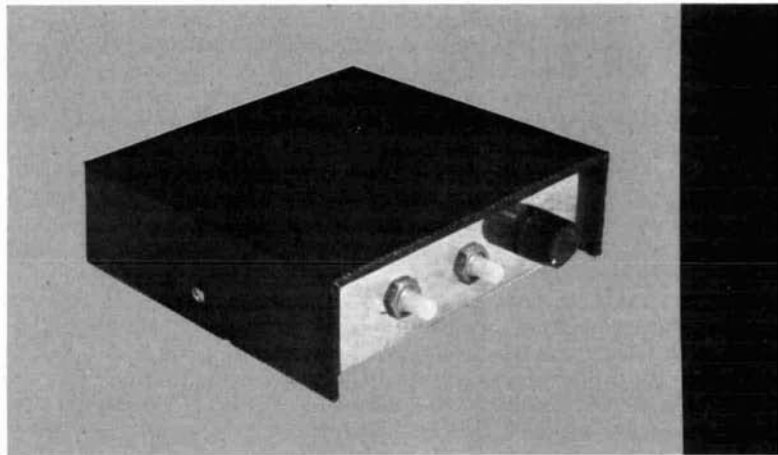

low-distortion two-tone oscillator for ssb testing

A handy piece
of test equipment
featuring excellent
spectral purity

Hank Olson, W6GXN, Box 339, Menlo Park, California 94025

A good sine-wave oscillator is an asset to any ham shack or electronic service bench. For adjustment of single-sideband equipment, one oscillator is a necessity, and two such are very helpful at times. Since most ham shacks are lucky to have even one audio test oscillator, two-tone testing is a rare luxury.

Here is a dual Wien Bridge oscillator that produces 800 Hz and 2000 Hz (both frequencies within the normal voice-frequency range) of good purity for ssb testing. I took advantage of some of the new inexpensive operational amplifier ICs which provide large blocks of gain and ease of application. IC op amps are also used as active low-pass filters to provide optional harmonic reduction of each of the two tones generated. An etched circuit-board layout is provided and laid out so that you can build a simple two-tone generator and combiner with two ICs.*

You can also add one or two stages of

*A printed-circuit board and a complete parts kit for this unit are available from Southwest Technical Products, 219 West Rhapsody, San Antonio, Texas 78216.

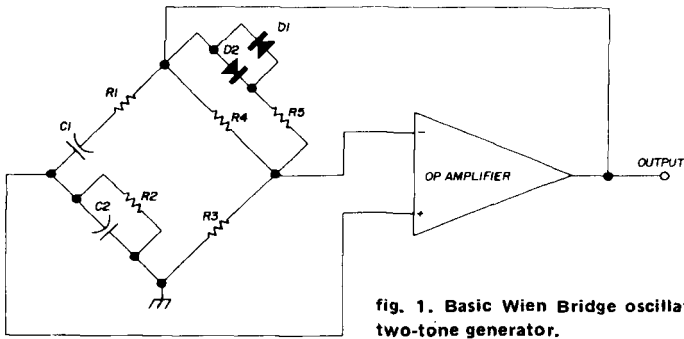


fig. 1. Basic Wien Bridge oscillator used in the two-tone generator.

low-pass active filtering after each oscillator, for successively purer output. The full-blown circuit with two stages of low-pass active filtering following each oscillator provides a two-tone output

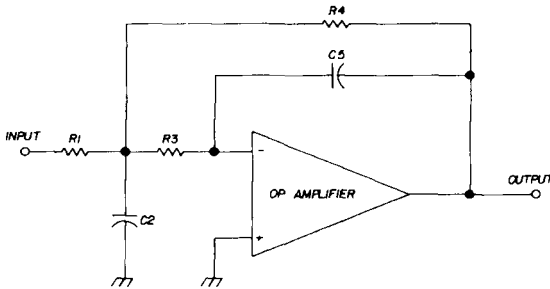


fig. 2. Basic active R-C low-pass filter used in the two-tone generator.

with all other components (harmonics of 800 Hz and 2000 Hz) down more than 70 dB.

The basic Wien Bridge oscillator circuit used in the two-tone oscillator is shown in fig. 1.¹ Note that this variation is different from the classic Wien Bridge oscillator using a lamp as the nonlinear resistance element in the R3 position. In the original lamp version the lamp decreases the gain of the loop by increasing resistance with increasing oscillation amplitude. The diodes used as a nonlinear resistance in fig. 1, however, decrease effective resistance with increasing amplitude; so they are placed in the upper leg of the negative-feedback half of the bridge. Like most Wien Bridge oscillators, the frequency of

oscillation is $1/2\pi R1C1R2C2$. Unlike most Wien Bridge oscillators, however, there is no feedback time constant (usually provided by a lamp or thermistor thermal time constant). The back-to-back diodes operate essentially instantaneously to control amplitude, but since they conduct nearly symmetrically and have a large resistance in series with them, nonlinearity is not too severe. The result of the nonlinearity introduced by the back-to-back diodes is that odd harmonics are larger than ordinarily present in a Wien Bridge oscillator. However, the nonlinearity is not all bad as it helps to increase the stability of the oscillator.²

If you are content with a two-tone spectrum that has all harmonics down 40 dB or more, the circuit may consist of only U1 and U4. That is, the circuit is simply the two Wien Bridge oscillators and an operational adder. However, if you want better spectral purity of each of the two tones, follow each oscillator with one or two sections of active low-pass filtering to attenuate harmonics. The

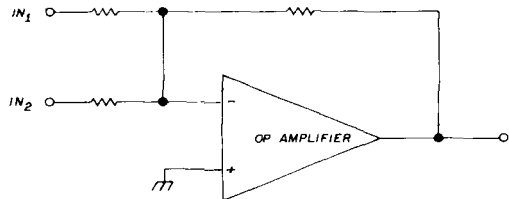


fig. 3. Basic operational adder used in the two-tone oscillator.

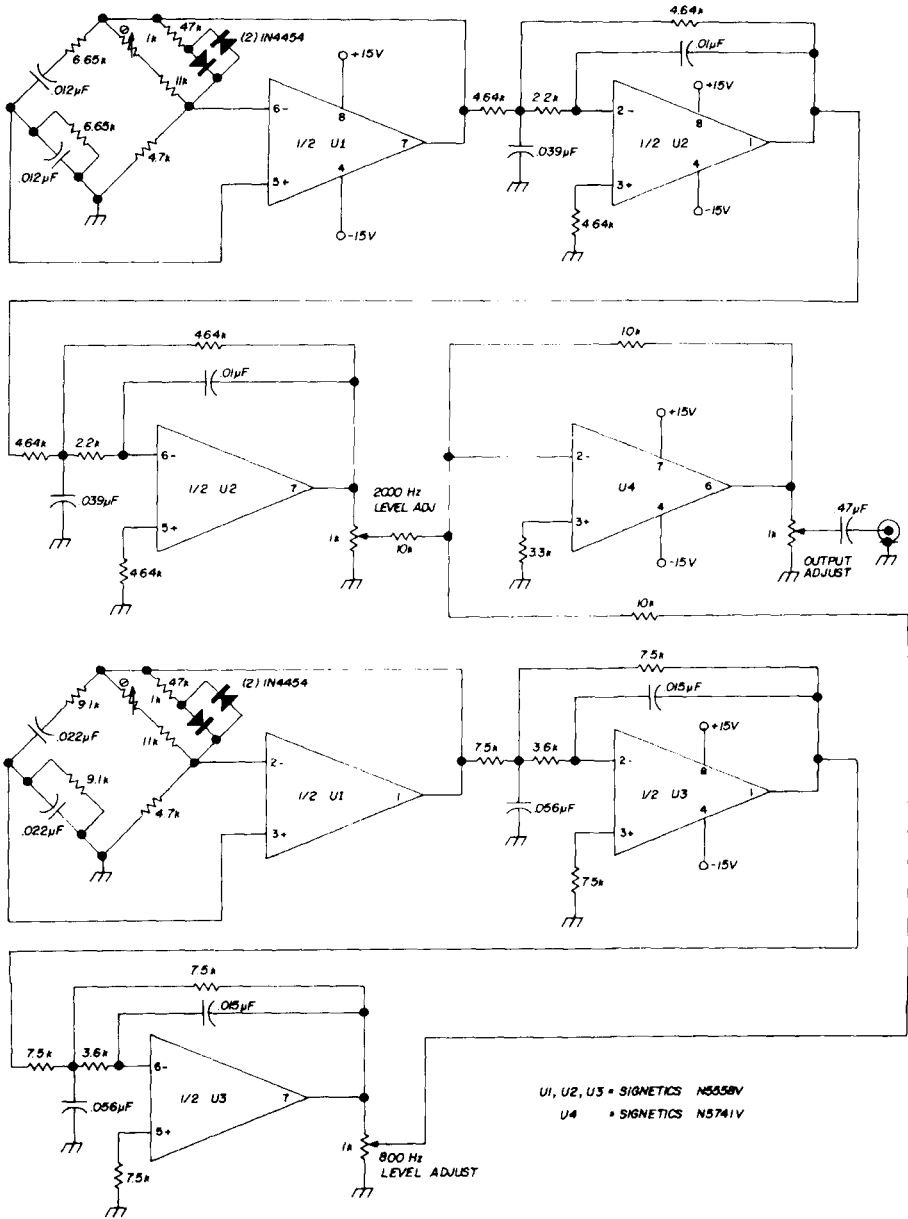


fig. 4. Complete circuit of two Wien Bridge oscillators, two sections of active low-pass filtering for each oscillator and the operational adder.

harmonics of the 800 Hz oscillator are more troublesome, of course, since the second, third, and fourth all fall in what is generally considered to be the audio-frequency range: 300 to 3300 Hz. Depending on your application, the low-pass

filter following the 2000-Hz oscillator may or may not be necessary. In any case, because of the way that the circuit board is laid out, the low-pass filters may be left out entirely, one section may follow each oscillator, or two sections

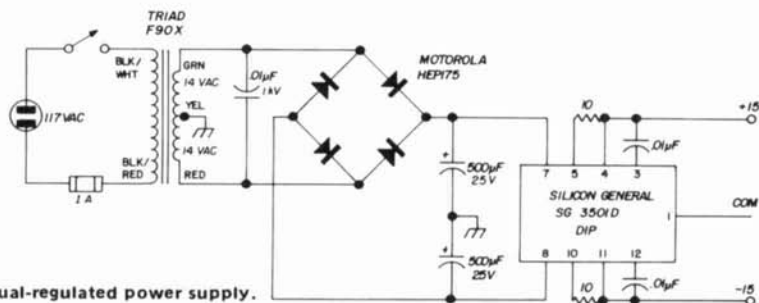


fig. 5. IC dual-regulated power supply.


may follow either or both oscillators.

The low-pass filters, like the Wien Bridge oscillators, utilize IC op amps and R-C elements to accomplish frequency-selective functions. These R-C active low-pass filters are quite stable, easily calculated, and have the advantage of providing gain if desired.³ The basic active low-pass filter is shown in fig. 2. There are three Rs and two Cs that completely determine the gain and cutoff frequency of this filter. The ratio of R1 and R4 determines the *gain* of the filter (1 in our particular example), but you must not get the impression that varying R1 and/or R4 will affect *only* gain. R1 and R4 also affect the filter frequency cutoff. The cutoff frequency of the filter that follows the 800 Hz oscillator is set at 1000 Hz, and the one that follows the 2000 Hz

oscillator is designed for 2500 Hz. Each *section* of active low-pass filter affords a roll-off of 12 dB per octave.

The operational adder (fig. 3) provides a way of combining (or adding) the two tones with virtually no interaction between oscillators. Such an adder is quite often called a mixer in the audio world; but I prefer to call it an adder, because it actually algebraically *adds* the two inputs. Since the summing point (the inverting input to the op amp) appears to be a virtual ground, each oscillator (or oscillator followed by a filter) sees 10k to ground. This fact, that there is a virtual ground at the very point where the signals are connected together, assures that the two oscillators cannot affect each other. Since the operational adder is a very linear device, it does not cause mixing (why I choose not to call it an audio mixer), and no detectable cross-products are produced. If this adder were non-linear, of course, we should expect to see all sorts of spurious frequencies such as $2000 - 800 = 1200$ Hz, $2000 - (2 \times 800) = 400$ Hz, and so on. The exact spectrum of spuri would depend on the nature of the nonlinearity.

Fig. 4 shows the complete circuit with two Wien Bridge oscillators, two sections of active low-pass filtering for each oscillator, and the operational adder. At this writing, only Signetics is making available the half dual-inline package N558V, used as the dual op amp. However, both National Semiconductor and Motorola are soon to offer their own equivalents; the Motorola equivalent is to be called an MC1458CP1. The half dual

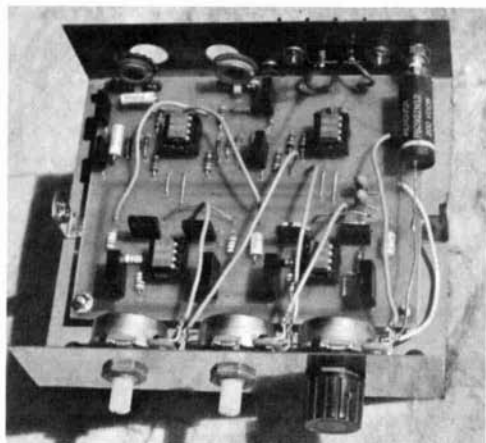

Inside view of the test oscillator shows parts placement.

inline packaged "741" (Signetics N5741V in fig. 4) is also made by Texas Instruments, Motorola National Semiconductor, Fairchild and others. Each of these second-source companies has their own particular (similar) number for the IC. For example, the Motorola number is MC1741CP1.

Note that there are five controls in the circuit. There is a negative feedback control on each oscillator circuit, used to set the amplitude of oscillation. These controls should be adjusted to give about 12 V p-p output from each oscillator (a setting giving too low an output will increase the percentages of harmonics). Since the negative feedback controls are only set once, they are board-mounted screwdriver-adjust trimmer pots. The other three controls—used to set the amplitude of each tone and combined output level—are mounted off the board.

Since the two-tone test generator requires ± 15 V at 20 mA, it may be powered by a group of series-wired batteries. Four Burgess F4BP and two Burgess F2BP types are more than adequate. It is a good idea to use a dpst switch with this battery pack so the +15 V and -15 V are applied at one time. An IC dual-regulated supply may also be used. Such a supply is shown in fig. 6. The Silicon General SG3501 is used here for both + and - regulation. This IC is only offered by Silicon General at this writing, but is soon to be second-sourced by Motorola.

Measurements of harmonic content (and to check for possible cross-products) were made using a General Radio 1900A wave analyzer, which has a dynamic range of 80 dB.

references

1. R. Botos, "Breadboard Techniques for Low Frequency Integrated Circuit Feedback Amplifiers," Motorola Application Note AN271, October, 1966.
2. B. Oliver, "The Effect of μ -Circuit Non-Linearity on the Amplitude Stability of RC Oscillators," *Hewlett Packard Journal*, April-June, 1960.
3. "Handbook of Operational Amplifier Active R-C Networks," Burr-Brown, Tucson, Arizona.

ham radio

• LEADERS IN COMPACT ANTENNAS •

MAXIMUM EFFICIENCY/MINIMUM SIZE


FOR APARTMENTS • SUBURBAN HOMES

Marine and Portable Operation
Packaged for APO and FPO Shipping

ALL MODELS COMPLETELY WEATHERPROOFED

NEW

B-24 + RK-3 COMBINATION

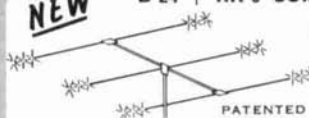


3 ELEMENTS
10-15-20
METERS

Bands	10-15-20 Meters
Power Rating	1400 Watts P. E. P.
Total Boom Length	11'
Turning Radius	7'-10"
Total Weight	23 lbs.
Single Feed Line	52 ohm
SWR at Resonance	1.5 to 1.0 max.

B-24 + RK-3 Combination Net \$94.95

RK-3 Reflector Kit (only) Net \$36.95

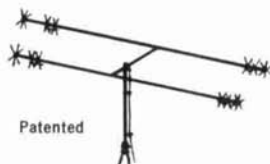The features of the popular B-24 plus the new RK-3 reflector kit make a unique 3 element combination. Choose the combination or add the RK-3 to your present B-24 and enjoy the improved gain and front to back.



Patented

Bands	6-10-15-20 Meters
Power Rating	1400 Watts P. E. P.
El. Length	11'
Turn. Radius	7'
Total Weight	13 lbs.
Single Feed Line	52 ohm
SWR at Resonance	1.5 to 1.0 max.

6-10-15-20 METERS

The time proven B-24 4-Band antenna combines maximum efficiency and compact design to provide an excellent antenna where space is a factor. New end loading for maximum radiation efficiency. No center loading.

Model B-24
Net \$62.95

MULTIBAND COAXIAL ANTENNA for 6-10-15-20 METERS

Needs no ground plane radials. Full electrical $\frac{1}{2}$ wave on each band. Excellent quality construction. Mount with inexpensive TV hardware. Patented.

Power Rating	1400 Watts P. E. P.
Total Weight	6 lbs.
Height	11'
Single Feed Line	52 ohm
SWR at Resonance	1.5 to 1.0 max.


Model C4 Net \$36.95

See our entire line at your nearby distributor or write the factory for further information and literature.

Mini-Products, Inc.

Call 814 - 454-2171

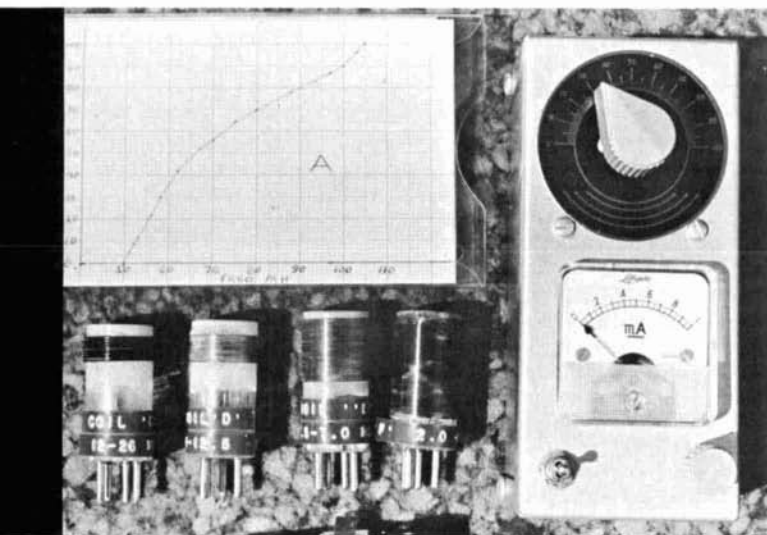1001 W. 18th Street - Erie, Pennsylvania 16502



frequency measuring oscillator

Looking for a small,
self powered gdo?

This design
offers a
forward-reading meter
and full coverage
between 2-100 MHz

One of the most useful testing devices is the grid-dip oscillator. This instrument has evolved through many stages of development from tube-types to modern solid-state models known as gate-dip oscillators or tunnel dippers. One of the advantages of the later designs is user convenience — no need for primary power, which can be a problem when climbing a tower to make antenna adjustments.

frequency-measuring oscillator

Here's a still later development in solid-state gdos, but with a new (and more nearly correct) title and a different mode of indication. Instead of a dip in meter indication, the fmo meter swings forward with alacrity, which makes for easier observance of resonance.

The circuit is shown in **fig. 1**. Transistor Q1 is in a Colpitts oscillator circuit. The oscillator is followed by Q2, Q3; a high-gain dc amplifier of the Darlington configuration. Connections and polarities are such that meter movement is in the

R. C. Alexander, W6EL7, Route 3, Box 502, Sequim, Washington

forward direction when the circuit to be tested is near or at resonance.

construction

The fmo can be housed in a 2¼ x 2¼ x 5-inch utility box. If you

underside of the board to reduce capacitance effects. All other wiring is installed on top of the circuit board. Install the transistors upside down, with leads facing up, and bend the leads toward their respective soldering pins, which may be

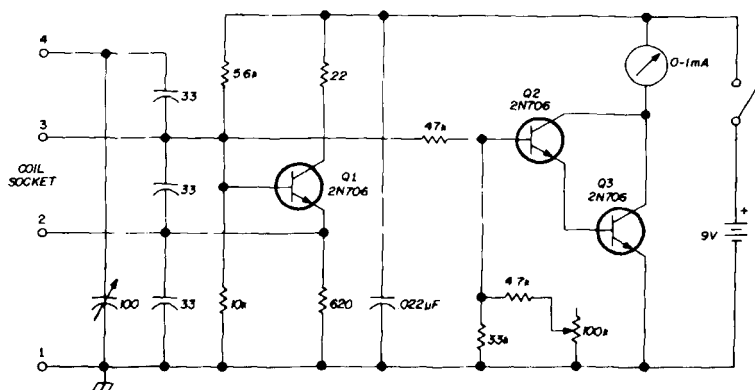


fig. 1. Schematic of the frequency-measuring oscillator. Circuit features forward-reading meter and full coverage from 2 to 100 MHz.

desire this shirt-pocket size, the switch and pot should be of the miniature variety such as used in small transistor broadcast sets. For those wishing to duplicate the instrument shown, a parts list (table 1) and coil data (fig. 2) are provided. A full-scale layout drawing (fig. 3) is also shown.

A 2 x 3½-inch circuit board holds the parts. Three of the circuit wires (shown dotted in fig. 3) are installed on the

small brass push-through connectors or standoffs. Holes 1 and 2 in fig. 3 are for mounting screws (see photo).

tuned circuit

The superior performance of the fmo at all frequencies is due primarily to the coil-capacitor arrangement, in which feedback and bandsread are obtained automatically. Except for coils A and B, each coil has a series-parallel capacitor arrange-

table 1. Parts list for the frequency-measuring oscillator.

qty	description	
1	aluminum mini-box, 2¼ x 2¼ x 5"	3
1	2" 0-100 dial-plate	33-pF miniature glass or ceramic capacitors
1	pointer knob, 1"; modify if needed	1
1	small knob for pot control	.022-µF (or .02) mylar or paper miniature capacitors
1	perfboard piece, 1/16 x 3¼ x 1-7/8"	1
2	3/8 x 1¼" mounting pillars, poly or steatite	0-100 pF variable capacitor, Hammarlund MAPC-100-B or equivalent, with ¼" shaft
1	miniature 0-1 dc milliammeter, 1½" mounting-hole size	7
1	miniature pot, ½" diameter, 0-100k	¼ watt resistors, one each 22, 620, 4700, 5600, 10k, 33k, 47k
1	miniature spst toggle switch	3
1	battery mounting strap	transistors, 2N706, npn silicon
1	miniature 5-pin socket, Amphenol 78S-5S, with retainer ring. Modify per instructions	7
		miniature capacitors for coils, mylar or ceramic, three 100 pF, two 240 pF, two 470 pF
		4
		coil forms, Amphenol 24-5H, 5-pin. Miscellaneous wire, solder, and flea clips for terminals

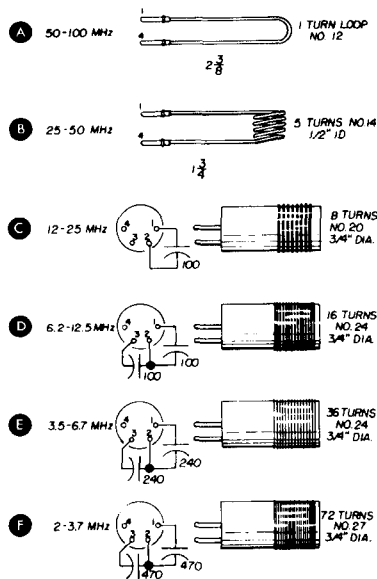


fig. 2. Coil-construction data. Pin 5 is removed from the four low-frequency coils and used for plug-in support of coils A and B.

ment, which provides the bandspread feature described.

Wind a few extra turns on coils E and F so wire can be removed if necessary to


bring the circuit within the desired frequency range. This modification may be necessary as the small fixed capacitors will be within 10-20% of their marked values, and adjustment of the tuned circuit is made by removing coil turns. A light coat of Q dope should be applied to the coils. Final calibration (described below) is done after the coil dope is completely dry.

coils and sockets


The coil forms and sockets are modified by removing pin 5 of each form and the center shield of the socket. (These pin numbers are not used; the number sequence is shown in fig. 2.) The removed pins are used to support coils A and B in the socket.

When constructing the low-frequency coils, install the padding capacitors well down inside the coils, keeping the leads short. The lead from pin 4 goes to the top end of the coil; this is to minimize desoldering problems when removing turns from the top of the coil for calibration.


Keep all leads as short as possible

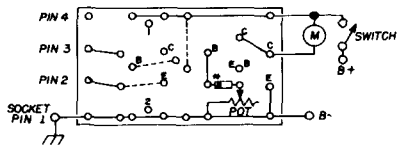


A

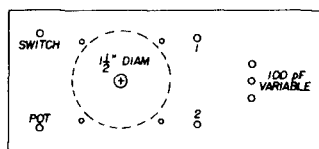

B

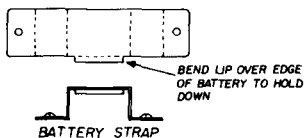

C

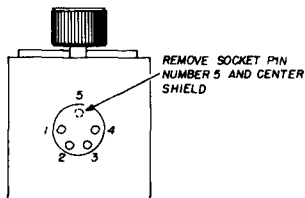

END VIEW

D

fig. 3. Full-scale layout drawings. (A) and (B) are templates for the circuit board and enclosure top. Holes E, B, C are for transistor leads. Component marked with asterisk is the 4.7k resistor in fig. 1, which was added after unit was built. Holes 1 and 2 are for mounting polystyrene pillars. Lower edge of knob (D) must be sawed off so set screw will reach capacitor shaft. Note that the numbers molded on the socket are not used. Three small holes in (B) are used to hold the dial in place.

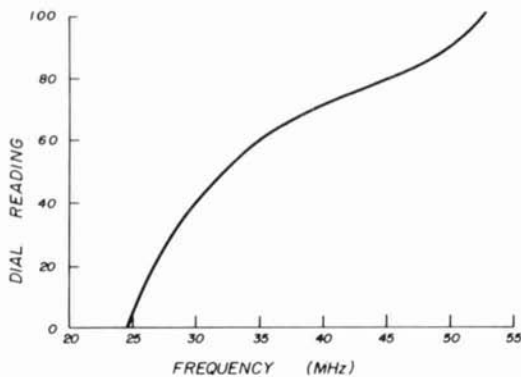


fig. 4. Typical calibration curve. Data is for coil B, 25-50 MHz.

between coil socket, variable capacitor, and the circuit board. Place a solder lug under *each* mounting screw for the variable capacitor, and run a wire from these lugs to pin 1 of the coil socket. Wire a short lead directly from pin 1 of the socket to the end of the ground wire (B-) along the edge of the circuit board nearest the coil socket.

Care should be used when soldering leads and capacitors into the coil forms as the material softens when excessive heat is applied. A heat sink, such as a pair of long-nose pliers with a rubber band


damping action is suitable. A 0-1 mA meter is adequate; a more sensitive meter costs more and provides no added advantage.

calibration


The instrument should be calibrated against a receiver of known accuracy. Plot the calibration curves with at least 20 data points for each coil range. Fig. 4 is a calibration chart for the 25- to 50-MHz range. Accuracy will be only as good as the data source and the care used in calibration.

operation

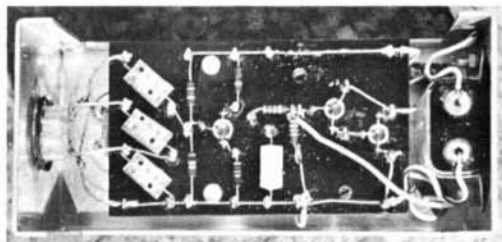The fmo is used in the same way as the earlier gdos; that is, when the circuit or



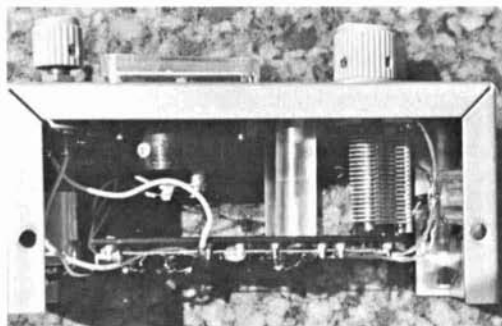Wiring on component side of circuit board.



Side view of completed instrument. Objects to left of tuning capacitor are polystyrene support pillars.

around the handle, should be used when soldering heat-sensitive components. This also applies to transistors.

An inexpensive milliammeter with low

coil being measured and the fmo are tuned to or near the same frequency, the meter will swing forward. It will not dip as in a gdo. The pot is first adjusted to take the meter slightly off zero, the sensor coil is brought close to the coil or circuit under measurement, and the fmo knob is turned until a sharp forward meter indication is obtained. The fmo is then backed off. The smallest amount of coupling that will give a meter indication should be used.

The frequency-measuring oscillator is a versatile instrument. In addition to checking resonance of coils, antennas and other tuned circuits, it may be used as a CW signal source for circuit alignment. It's also useful for measuring inductance and capacitance within the range of component values used at rf.

ham radio

emitter-tuned preamplifier for 21 MHz

A simple and stable
two-transistor project
to improve
receiver performance
on the 21-MHz band

Courtney Hall, WA5SNZ, 7716 La Verdura Drive, Dallas, Texas 75240

Some of the commercial receiving gear I have owned has shown a pronounced need for more gain at 21 MHz. Measurements at my station show that the antenna noise at 21 MHz is 25 to 30 decibels less than at 7 MHz. The term antenna noise is used here to include all noise received by the antenna, whether it is atmospheric noise, galactic noise, man-made noise or whatever. Antenna noise is the increase in noise heard when the antenna is connected to the receiver. It is not intended that very strong local sources of man-made noise be included in this definition, but only those which appear randomly.

If the antenna noise cannot be heard, then many low-level signals cannot be heard either. Receiver gain should be sufficient to hear antenna noise, and a preamp connected between the antenna and the receiver is one way to bring the gain up.

In my case, a circuit was required which would be stable, have 25- to 30-decibels gain, bandwidth of about 300 kHz (I operate CW only), reasonable noise figure and adequate cross modulation and intermodulation performance.

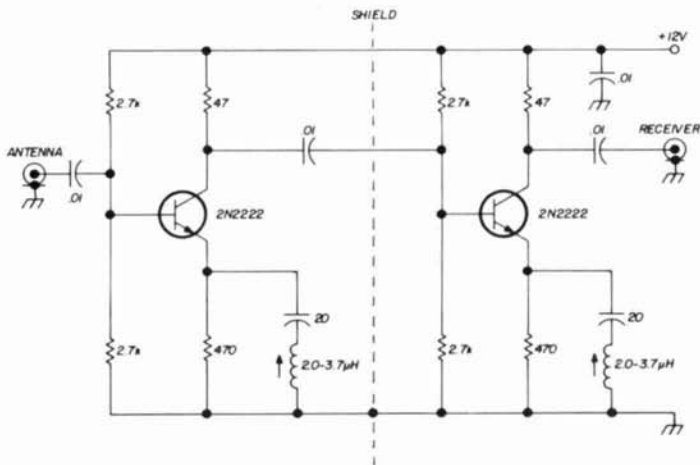


fig. 1. Schematic of the 21 MHz emitter-tuned preamplifier.

The first circuit I experimented with was a simple fet common-source amplifier, unneutralized, with parallel tuned circuits in the gate and drain leads. Stability was a severe problem, and the circuit was more likely to oscillate than amplify.

I decided on an emitter-tuned amplifier similar to one described by Chow and Paynter¹ would be worth a try. My version of the circuit is rather different from theirs because of the difference of intended application.

theory


The voltage gain of a common-emitter transistor amplifier stage is roughly equal to the load seen by the collector divided by the impedance in the emitter circuit. The intrinsic emitter resistance of the transistor must be included as part of the emitter circuit impedance when estimating gain. Its value is:

$$r_e = \frac{26}{I_E \text{ (ma)}}$$

To keep r_e small so that gain will be high, each transistor is operated at about 10 mA emitter current; this results in r_e being about 2.6 ohms.

Fig. 1 is a schematic of the 21-MHz

emitter-tuned preamp. Tuned amplification is achieved because the series-tuned emitter circuits present low emitter circuit impedances at resonance and high emitter circuit impedances outside the passband. The coils I used had an unloaded Q of about 120 at 21 MHz, and the 20-pF capacitors were duramica. Impedance of the series-tuned circuits at resonance should be about 3 ohms. Total emitter impedance, including intrinsic emitter resistance, should be about 5.6

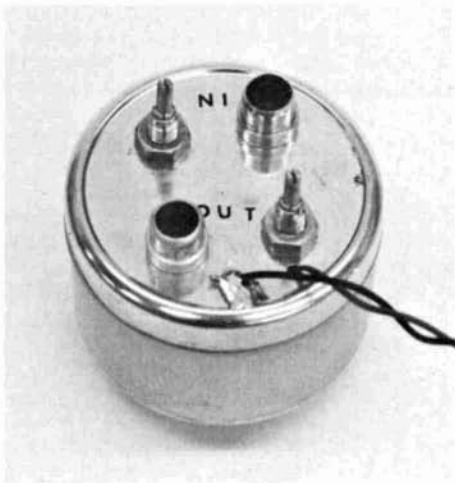

Complete preamp is built in a can; hookup wire brings in power; phono jacks connect to receiver and antenna.

ohms. The collector resistor of each transistor is 47 ohms; if a 50-ohm load is paralleled with this resistor, the collector will see an equivalent load of about 25 ohms. Thus the voltage gain should be $25/5.6 \cong 4.5$ or about 13 dB. Two stages would then have a gain of 26 dB. Measured gain of the two-stage amplifier was 27 dB, indicating the above estimate was reasonably close.



All wiring is done on the can's lid without the use of tie points.

The 3-dB bandwidth is determined by the Q of the series-tuned circuits. Intrinsic emitter resistance must be included as part of the series-tuned circuit, but the 470-ohm resistor has negligible effect at resonance. With r_e included in the series-tuned circuit, Q is 66, giving a bandwidth of about 300 kHz. This was verified by measurement. Two stages decrease the bandwidth to about 200 kHz.

Input impedance to the base of each transistor was not measured, but since estimated gain and measured gain agree so closely, this impedance is assumed to be in the range of 50 to 100 ohms.

Outside the passband, the series-tuned circuits become large impedances, and the emitter resistance approaches a limit of 470 ohms, resulting in a gain-per-stage of 0.05 to -26 dB. This means -52 dB outside the passband for two stages. The floor of the response curve should be 79 dB below the peak amplification, but it is probably not this good due to stray leakage paths.

At first glance, this amplifier circuit may appear to have poor noise figure as well as poor cross-modulation and intermodulation performance. Measurements of this type were not made, however, no operational shortcomings were detected. The noise output of the receiver dropped 20 dB or more when the antenna was replaced with a 50-ohm resistor, indicating internal amplifier noise was well below the noise received by the antenna.

construction

The amplifier was built in a small steel can 2 inches in diameter by 1-3/8-inches high. All parts are mounted on the lid of the can as shown in the photograph. A brass shield, soldered to the lid, separates the two amplifier stages; holes are drilled through the shield to pass the interstage coupling lead and the 12 volt lead. Components are soldered together without tiepoints, and are supported by their leads. This results in compact construction and short leads. Hookup wire feeds in the power supply voltage, and phono connectors are used for input and output. The coil slugs should be adjusted for maximum receiver output at the center of the frequency range to be used.

conclusion

This amplifier is simple, easy to build and relatively fool-proof. Current drain is rather high, but stability is excellent. The emitter-tuned amplifier offers a quick and easy way to obtain rf or i-f gain. It may be used at other frequencies by using appropriate series-tuned circuits, but gain and bandwidth will be a function of Q . Less gain is to be expected at higher frequencies due to decreasing transistor h_{fe} .

reference

1. "A Handbook of Selected Semiconductor Circuits," NObsr 73231, prepared by Transistor Applications, Inc. for the Bureau of Ships, Department of the Navy, circuit 4-7, pages 4-33 and 4-34. For sale by the Superintendent of Documents, U. S. Government Printing Office, Washington, D. C.

ham radio


the most powerful signals under the sun!



Hy-gain

400 ROTO-BRAKE

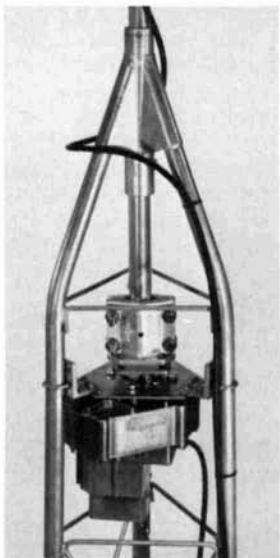Up to 10 Times the mechanical and braking capability of any rotator on the market!



- Handles large beams and stacked arrays with ease
- Delivers over 4,000 IN/LBS of starting and rotating torque
- Gear train protected by husky cast aluminum housing
- Solenoid operator brake adjusted to slip at 5,000 IN/LBS to prevent damage
- Extra heavy duty machined steel gears for maximum strength
- Handsome control unit features sweep pointer over choice of three great circle maps or compass rose
- Select desired position and rotator's logic circuit brings into desired position
- Capacitor start for high torque
- Operates off 110VAC 60 cycle power source
- No blind spots—moves 380°
- Antenna automatically moves to position when control is activated
- Heavy duty mast clamp takes up to 3" O.D. mast
- Mounts to standard tower plate with min. of 10" tower leg spacing
- Mounting kits available for poles or small towers
- Universal tower mount available
- Temperature range—30° F to 120° F
- Permanently lubricated
- Requires one 5 wire cable
- Cable available from Hy-Gain 412

Buy a 400 ROTO-BRAKE from the best distributor under the sun—the one who stocks Hy-Gain!

Model No. 400

Suggested retail price **\$189.95**

HY-GAIN ELECTRONICS CORPORATION

P. O. Box 5407-WD, Lincoln, Nebraska 68505

tuning toroidal inductors

Professional tips
on using
simple test equipment
and ingenuity
to measure and tune
toroidal inductors

Toroidal inductors have been praised as the ultimate inductor for miniaturized equipment. Their usefulness extends from audio to vhf with power levels from sub-microwatt to several hundred watts. The magnetic field of the toroid is closed, and, for this reason, it is somewhat self-shielding and will operate well under crowded conditions.¹ This closed magnetic field also means that a grid-dip oscillator is going to be worthless because there is not enough flux leakage from the toroid to permit coupling. Put the grid-dipper on the shelf. It is time to develop some practical methods and procedures to tune those toroids.

equipment

You will need a signal source with a low distortion sine wave because it will give a better indication at resonance. A distorted waveform can be restored to a clean sine wave with a parallel tuned

circuit to ground. Hewlett-Packard makes some beautiful signal generators but don't overlook the following possibilities:

1. Heathkit, Eico, and other budget-priced equipment.
2. Military and commercial surplus.
3. Homebrew oscillators.
4. The station transmitter (in spot mode or swamped).
5. A vfo.
6. Receiver audio (beat bfo against crystal calibrator).
7. Electronic organ.

A meter will be required mostly for use as a null detector. The possibilities for meters are a bit more limited but consider:

1. Any vtvm.
2. A diode and a sensitive dc meter.
3. A vom.
4. A receiver with an S meter.
5. An oscilloscope.

The problem of measuring frequency is a little more difficult. The dial calibration of some generators is adequate for some applications. More high-quality digital frequency meters are being found in ham shacks now for several reasons. Heathkit has a very reasonably priced counter kit, but possibly even more important to the ham is the switch that industry is making toward the new integrated-circuit counters. This has made available numerous low-frequency tube-type counters that still perform quite well. Counters are not the only

G. K. Shubert, WAØJYK, 1308 Leeview Drive, Olathe, Kansas 66061

answer. Anything from a crystal calibrator to an electronic organ or a pitch pipe can be used to find the frequency.

equipment connections

Any of the five equipment setups may be used to tune any coil and capacitor. However, there are some preferences. It is generally best to tune the circuit as a parallel circuit if it is to be used in the equipment in parallel resonance, and best to tune in series if it is to be used in series resonance. An exception to this rule is at

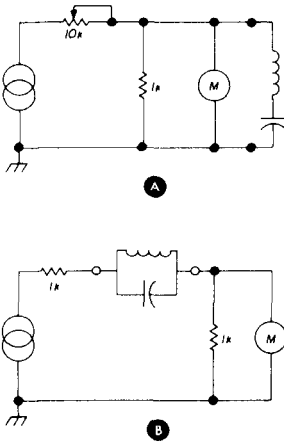


fig. 1. Test setups for determining resonant frequency of an L/C circuit using toroids. Both circuits will show a voltage minimum at resonance. A is series resonant and B is parallel resonant.

frequencies above about 2 MHz where it is desirable to tune *all* circuits in parallel to minimize the effects of lead lengths, even if the actual final circuit is series resonant.

Use a low signal level; ten millivolts is a good level, but unfortunately, most inexpensive vtvm's will not indicate a level this low. If a good high-impedance vtvm is available but lacks the ten millivolt sensitivity, then **fig. 2** is the hookup to use with a volt or two at the peak reading.

It should be noted that the hookup of **fig. 2** indicates a peak or maximum voltage at resonance while **fig. 1A** and **fig. 1B** both indicate nulls or voltage minimums.

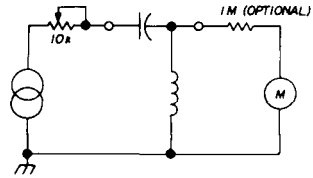


fig. 2. Setup for use with a high impedance vtvm lacking 10-mV sensitivity. The voltage will peak at resonance (usually 1 to 2 volts).

Fig. 3 requires an oscilloscope, but may be used with generators that have high harmonic distortion or noise in the output. This is a phase-shift method of tuning, and, if a good scope is available, this method is very accurate. Off-resonance frequencies cause an ellipse to be displayed which closes to a straight line at resonance. Distorted signals may be used, but the straight line at resonance will not be perfect.

Small coils and low-frequency coils require low test levels, but as physical size and frequency increase, the core is less likely to saturate, and higher test levels may be used. The cause and effect of saturation is too complex to detail here.² A good test to determine if the level is too high is to decrease the level to half or lower and check the resonance again. There should be no change in the resonant frequency. This test may be used to allow higher test levels on larger cores or at higher frequencies.

tuning to frequency

It is easy to get the inductance of a toroid in the ballpark by winding the turns determined by:

$$\text{turns} = 1000 \sqrt{L_{\text{mh}}/A_l}$$

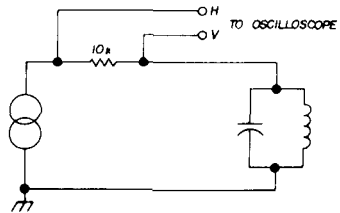


fig. 3. Accurate test setup uses an oscilloscope and the phase-shift principle. This setup can be used with signal generators with distortion and noise in their output.

L_{mh} = wanted inductance in millihenries.
 A_1 = millihenries per thousand turns on the core. (If A_1 is given in microhenries per hundred simply move the decimal one place to the left.) A_1 is sometimes stamped on the core but, most often, must be obtained from the manufacturer's data sheets.

Any one or a combination of the following methods may be used to fine tune the toroidal inductor:

1. Adding or subtracting turns. It is helpful to figure the hertz per turn or turns per hertz and compute the total turns to be adjusted. Raiding the wife's sewing basket for a crochet hook will accelerate turns removal. Obviously, if the coil has very few turns this method is not accurate enough.

2. All the remaining methods are variations of the variable capacitor method. The variable capacitor may be all or only a small portion of the total tuning capacity. Of course, true variable capacitors of the rotor/stator or piston type with dielectrics of air, ceramic, glass or quartz as well as the multi-plate compression mica types work very nicely; they are fine if you don't mind spending a mint just to tune a circuit.

3. The most economical variable capacitor on record is two pieces of magnet wire tightly twisted together and then trimmed to the desired capacitance — commonly known by old-timers as a gimmick. Number 22 or 23 heavy insulated magnet wire is a good choice and yields from 1 to 5 pF per inch depending on how tightly it is twisted. Trim off a fraction of an inch at a time to raise the resonant frequency of the circuit; if too much is trimmed off simply twist the remaining wire a little tighter.

4. Disc-ceramic capacitors may be ground off with a small sanding disc or grinding wheel. Disc capacitors can be reduced in value by 50 percent with no deterioration in performance. Just

be certain that the grinding action takes place longitudinally to the plates. In other words, don't smear any metal across the dielectric between the plates. Disc ceramic capacitors offer several advantages in this application. The entire circuit capacitance can be in the single disc capacitor. The disc can be a negative temperature coefficient type which

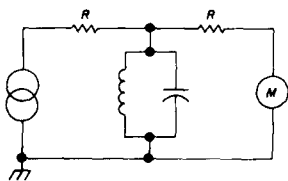


fig. 4. Circuit for determining Q. Make the two resistors as large as possible.

will compensate for temperature drift in the inductor. Large capacitances are physically very small in the low voltage, high temperature coefficient capacitors. Once the circuit is tuned the exposed capacitor edge should be coated with melted wax or polystyrene (Q-dope).

5. Spreading or compressing the turns of the coil will vary the turn-to-turn capacitance and change the resonant frequency slightly. This method is actually cheating and is mentioned only as a quick-cure method involving some risk. A toroidal inductor has a closed field only if it is perfectly symmetrical and any intentional distortion of the winding will cause flux leakage to the chassis, other inductors and other circuits. The best practice is to preserve symmetry. The start and finish of the winding upset the symmetry enough but are necessary evils.

Q measurement

Some of the equipment used to tune the toroidal inductors can provide information about the quality factor or Q of the coils.³ Use the setup in fig. 4 with nearly maximum output from the signal

generator and the largest possible values for the resistors. It is very important to not load the Q with a low-impedance generator or meter. If loading from the meter or generator cannot be avoided, it is still practical to make Q comparison tests to evaluate inductors. Adjust the frequency for a peak reading on the meter. Here again a low voltage level is preferred. Tune up in frequency until the voltage is 0.707 of the original reading. Record this frequency as F_h . Now tune the generator down in frequency until the level is again 0.707 of the peak voltage and record this frequency as F_l . These are the 3-dB down points, or half-power points. The formula that closely approximates Q from the 3-dB points except for Qs less than 10 is:

$$Q = \frac{\frac{1}{2}(F_h + F_l)}{(F_h - F_l)}$$

The tips in the preceding paragraphs are by no means limited to the tuning of toroids, but, since toroidal cores are not adjustable, some of these methods must be used. All of the methods are used daily in commercial practice, and are all practical. There have been so-called adjustable toroids available, but the adjustment was at only one point on the core which upset the symmetry and caused flux leakage and stray-coupling problems. It is also possible to grind notches in the core material of a coil with few turns and, if done at many different points around the core, a high degree of symmetry can be maintained. Core grinding is tedious and seldom used commercially.

references

1. Hank Olson, W6GXN, "How to Use Ferrite and Powdered-iron for Inductors," *ham radio*, April, 1971, pages 15-27.
2. "Ferroxcube Magnetic Design Manual, Bulletin 550," Ferroxcube Corp., Saugerties, New York, January, 1971.
3. *Reference Data for Radio Engineers*, International Telephone and Telegraph Corp., New York, New York, 1968.

ham radio

UNIVERSAL Aluminum Towers are GREAT!

* Strong * Lightweight * Easy to assemble * Rust-Free (less maintenance) * Self-Supporting Models are available from 30-90 feet with a choice of wind loads to meet your specific needs. Write us for literature. Shown here is a Model 18-50 (18 sq. ft. wind load -50 ft. high) installed at Ted Willett's house (W9NHE), our Print Shop Manager. AMATEUR ELECTRONIC SUPPLY can recommend the proper UNIVERSAL TOWER to fit your particular needs.

AMATEUR ELECTRONIC SUPPLY

4828 West Fond du Lac Ave. Milwaukee, Wis. 53216

Phone (414) 442-4200

nostalgia

with a vengeance

A blonde,
a kilowatt and
a memory —

It was during spring-cleaning of the attic under dire forebodings from my wife that it happened. For it was thusly, while investigating a pile of boxes situated in a long undisturbed corner, that I discovered the bottles. Antiquated bottles they were; mellow in their peaceful hibernation with thick coatings of dust.

Envisioning a sweet rendezvous with cherished brew of Ohmar's squeezings, I deftly brushed away the dust. Alas, the bottles were devoid of the coveted spirits! In fact, the bottles, though of ancient vintage, were quite empty except for the insolently protruding gizzards of primitive electron tubes. Closer inspection revealed enumerations such as 211E, 210 and 250.

Tempus fugit and shades of hades, how time flies! (In the manner of greased lightning, OM.) Shutting my eyes to black out the eerie illumination, sweet reminis-

cence conveyed me, dream-like, to days of yore. Ah, sweet days of yore. . .

In the wee small hours of a misty morning, I deposited the belle of the senior class on her doorstep and bestowed the usual prolonged kiss in the usual tender fashion. Then, not being overly-desirous of a QSO with her OM, I leaped into the waiting Essex.

With effervescent gusto I coaxed the last rpm from the protesting connecting rods. Soon, I was home with my first and true love, the 80-meter Hartley with one 211E, three 210s and two 250s coordinating more-or-less in parallel.

I reached up and yanked the handle of the main switch. Fondly, I beheld the glowing filaments. (Brother, you too would glow with double voltage on your filaments.) Trembling with anticipation of a hot DX contact, I appraised the performance of the rig in the usual professional manner.

I pressed the key for a few brief moments. A 500-cycle roar of defiance shattered the ether. The motor-generator tugged in agony at the half-inch bolts which secured it to the four-by-four support, then resigned to its torment by dropping speed. The lights in my room dimmed by an amount deemed proper.

I picked up a pair of binoculars and observed the light bulb in my neighbor's garage, some fifty yards due South. The intensity of its glow indicated healthy antenna radiation. I released the key just as the filament of one of the 250's became visible through the plate. Feeling

Irv Gottlieb, W6HDM, 931 Olive, Menlo Park, California 94025

well rewarded for my efforts, I turned my attention to the receiver.

The receiver, though completed only ten days previously and not completely de-bugged, had already revealed itself as a signal snatcher *sui generis*. It was, in fact, the reception of a VK from Australia that motivated the DX quest about to take place.

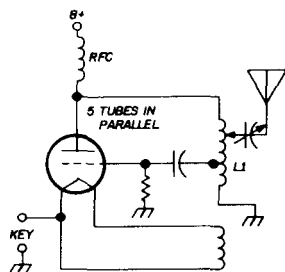


fig. 1. Salient features of the transmitter. Abundant harmonic generation assured a response on some band. L1 is copper-tubing tank from a Hoyt automatic water heater. Plate voltage was 1200V on spaces, 1000V on dots and 850V on dashes.

The design, my own, consisted of a regenerative rf stage, regen detector in a reflex arrangement which re-squirted the signal back into the rf stage, which now functioned as an audio amplifier. This was followed by two stages of conventional audio amplification, or *almost* so.

The slight departure from the "run of the mill" involved the use of Model T spark coils as inter-stage transformers. The tubes, chosen after much deliberation were 201As.

I placed the 8000-ohm Baldwin phones over my noggin and turned on the receiver. It was, verily, full with the joy of life. As I advanced the various controls, a terrific fringe howl sallied forth from the cans and reverberated within my tortured head like a freight train stalled in a tunnel! Quickly, I jerked the phones off and backed down the regen controls, lest the OM burst into the shack with an R9 lecture about the need of sleep for growing boys, etc. Swearing with R9 fervor, albeit in hushed breath, I resolved to be more careful with those very, very critical knobs.

Using the utmost caution to maintain regeneration just on the threshold of oscillation, I searched the endless kilocycles for a voice lost in the wilderness. It wasn't long in forthcoming. Somewhere in the depths of Boltzman's constant, all but buried in the crackle of shot noise, shot capacitors, thermal agitation and ionized soldering paste, I heard it . . . yes I heard it, a weak CQ!

Carefully, ever so carefully, I advanced the you-know-which controls. Now, a tiny bit more, a shadow here, an Angstrom there. The results were no less than magical. The signal, except when fading obliterated it entirely, now was R3 in any ham's lingo. Only thing was, the fading was somehow mysteriously synchronized with the announcement of the station's identity.

Carefully, ever so carefully, I trimmed the other controls with my left hand, while my right maintained vigilance with the detector regen control. Waiting in suspended animation for the final station identification, I arose from my chair. I leaned over the receiver to provide the nth degree of trimming by means of body capacity. A bead of perspiration dripped from my brow and landed dangerously close to the grid terminal of the detector tube. I blew the saline droplet away from the socket.

Then it happened . . . I caught the call just before he signed off. It was none other than the VK recently logged! Shades of hades, could I work him?

I laid the earphones on the operating table and promptly went to work with the home-spun bug. This was constructed from materials distinctly out of the ordinary, among which were the innards of a Pocket Ben, ignition breaker points and a segment of corset stave donated by the belle of the senior class. Between the bug and raucous note, I was certain my signals had that spark of personality needed to attract the attention of DX ops.

For the first minute or so, my sending fist trembled and threatened to freeze. However, the bug gave unselfishly of its

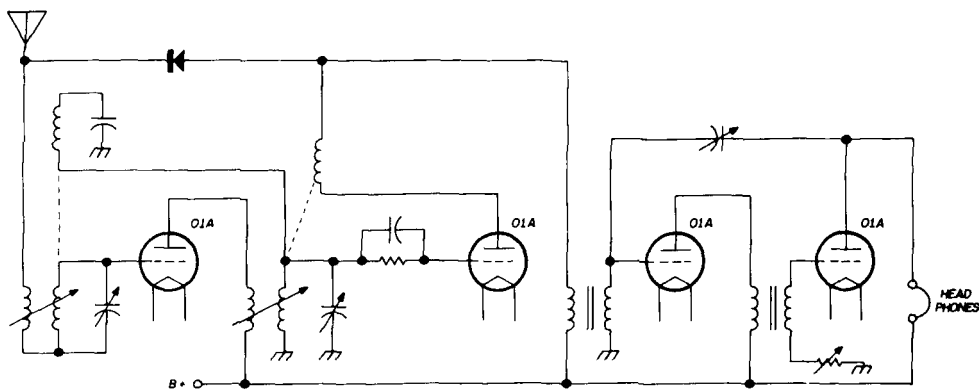


fig. 2. Schematic depicting general idea of the receiver. This set is regenerative to the nth degree; it should not be confused with workable schemes.

dots and I soon regained poise. I settled down to a fifteen minute grind of three VK calls interspaced by two of my own.

The dit-dahs were now oozing with the solid self confidence that I pounded into them. My enthusiasm mounted until I could scarcely contain myself. Finally, I repeated my call eleven times and culminated with a stately 'RK'!

I climbed into the phones and listened. Amidst the playful electrons, I heard *nothing*, absolutely *nothing*. Ever so carefully, I applied torque, one part physical, nine parts psychic, to the detector regeneration knob. The impending fringe howl was lurking in the infinitesimal depths of perception, intent upon springing out at me, tiger-like. Precariously but nonetheless skillfully, I held it at bay.

Within the innermost realm of consciousness, I became aware of minute fluctuations in the background noise having the characteristics of dots and dashes. I copied it mentally: "sure gld to wrk the West coast OM. Ur sig FB here in Melbourne. Pse give my report..." The signal faided out but I could sense he was signing over.

I prepared to acknowledge his message. So intoxicated was I with the prospect of bettering my previous DX record by some seven thousand miles that I had to deliberately pause a few seconds before tickling the bug.

Then, *boom*, like a bolt of lightning did the terrible catastrophe strike! The phones, still on my head, became the forerunners of the present day dynamic speaker. Unmerciful decibels assailed by burning ears. Between the jack-hammer thumps, the fringe howl lashed out with tongues of sonic flame.

I tore the phones from my head and threw them on the table. The thumps were saying, "VK3- de W6- tnx for fb rept. Ur coming in QSA 5, R6." "R6! Shades of hades," I muttered to myself, "All he has is a superhet with no regeneration and he has the gall to call a signal R6 which I can just barely pick up."

W6- resided in the high-falutin section of town because his OM was well heeled, the owner of a chain of shoe stores. W6 attended private school, owned a brand new Model A Ford and had a 5-kW rig full of store-bought components. What with all this, he now runs away with my DX station!


So what? Did I begrudge his monied pop? Was I envious of his classy rig? Did I resent his swiping my VK? Shades of hades, *no*. After all, it was I who was the steady of the belle of the senior class! But OM, that is another story altogether... anyhow she's mighty anxious that I get this attic cleaned up, pronto!

ham radio

Savoy

High Accuracy Crystals

For over 30 years

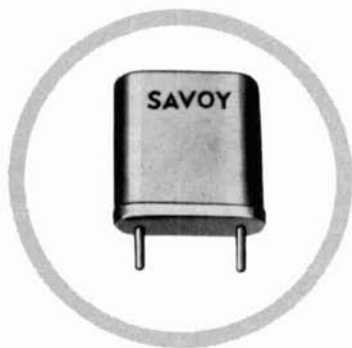

TYPE 900 A



TYPE 901

Either Type

RECEIVER — \$3.95

TRANSMITTER — \$4.95

Post paid in U.S.

Specify crystal type, make and model of set, and desired frequency.

For amateur FM, fixed, mobile, and repeater use on 144 Mhz band.

Regency, Varitronics, Standard, Drake, Gladding, Tempo, Swan, and most others.



Savoy Electronics, Inc.

P.O. Box 7127 - Fort Lauderdale, Florida - 33304

Tel: 305-566-8416 or 305-947-1191



improved selectivity for direct-conversion receivers

The subject
of these mods
is the Ten-Tec RX10 —
however,
they may be applied
to any
direct-conversion receiver
with good results

About fifty years have elapsed since radio amateurs replaced their one- and two-tube regenerative receivers with the superheterodyne circuit. Progress has been spectacular . . . Or has it?

It is now possible to build a receiver for the high-frequency bands that performs as well as or better than the superhet without the problems caused by i-f amplifiers, such as images and spurious oscillations. The improved circuit is based on the old synchrodyne detection method and is known as direct conversion. It has been described in earlier issues of *ham radio*.^{1, 2} A direct-conversion receiver available commercially is the RX10.* Reviews of the RX10 have appeared in *ham radio* and elsewhere.^{3, 4}

To improve the selectivity of my RX10 I developed the front-end modifications described here, which are adaptable to other direct-conversion circuits as well.

Selectivity is provided by a sharp audio filter preceding the audio amplifier and the high Q of the input tank circuit. The high Q is developed by regeneration; when regeneration is removed selectivity will be about equal to that of a galena crystal set.

*Manufactured by Ten-Tec, Inc., Sevierville, Tenn. 37862.

Vladimir N. Gercke, K6BJJ

Fig. 1 shows five diode-detector circuits and their respective selectivity curves:

A. Crystal or tube detector with no tuned circuit.

E. Same as D, but with extremely low L/C ratio.

As shown in fig. 1, the culprit is dimension A, which is the portion of the

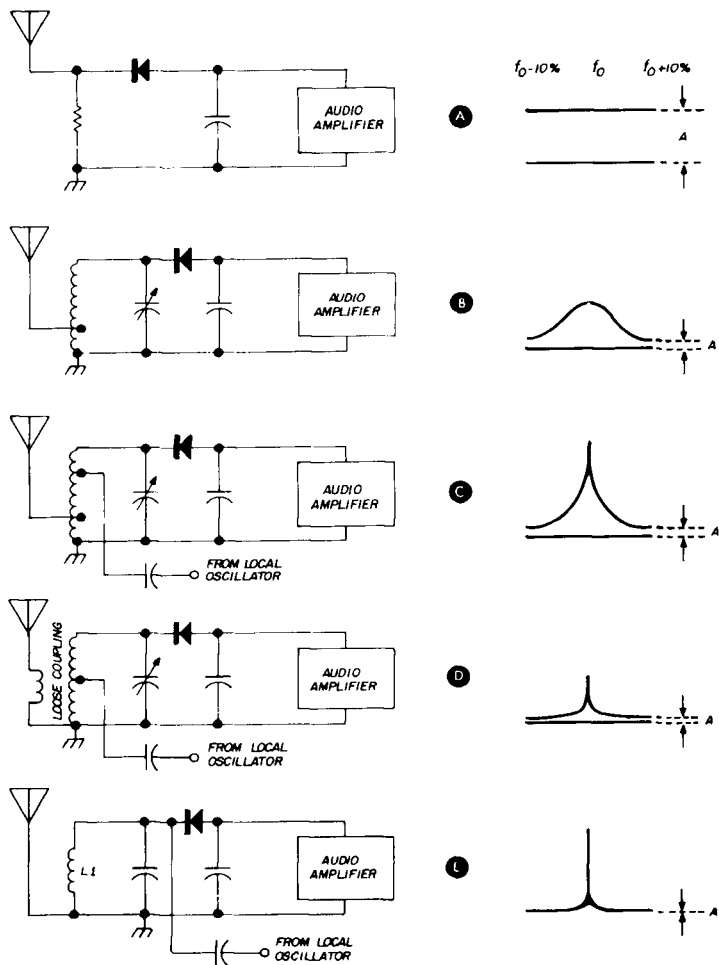


fig. 1. Five diode-detector circuits and their respective selectivity curves. Circuits C, D and E are direct-conversion types. Bias and audio filters have been omitted for clarity.

B. Same as A with added tank circuit.

C. Same as B with injected local-oscillator voltage.

D. Same as C with very loose coupling to the antenna.

response curve that levels off and continues indefinitely above and below f_0 , the frequency of interest.

Loose coupling, as in fig. 1D, will decrease dimension A almost to zero; but most of the signal is lost. An audio

system with extremely high gain will be needed to restore the signal.

RX10 modifications

The circuit of **fig. 1E** seemed to be the solution to the selectivity problem. The

which can otherwise defeat the purpose of the circuit.

All my experiments were made with the Ten-Tec RX10 receiver. The front end was modified according to **fig. 2**, a partial schematic of the unit. The value of

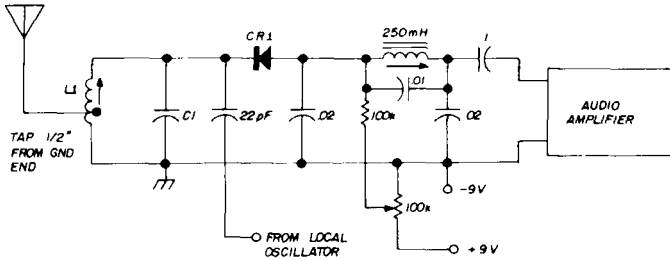


fig. 2. Modified front end of the RX-10. L1 is 2 turns no. 12 solid copper wire, 5/8-inch diameter; C1 is 1400 pF, 4400 pF and 13500 pF for 14, 7 and 3.8 MHz, respectively. CR1 is any hf or vhf diode or a transistor E-B or C-B junction chosen for minimum noise (varies to 10 dB among units with the same 1N or 2N prefix.)

tank coil was made with two turns of heavy wire, and the tap for the antenna was 1/2 inch from the ground end. All signals below f_0 are returned to ground, and all signals above f_0 are blocked by the enormous value of C1 (13,500 pF for 80 meters). C1 consists of several silver micas in parallel to reduce lead inductance,

L1 is a compromise; it's too large for 20 meters and too small for 80 meters. One turn for L1 and 2,400 pF for C1 would be better for the 20-meter band.


conclusion

The selectivity of a tuned circuit is a function of its Q, the ratio of reactance to resistance at the resonant frequency. The excellent selectivity of the modified RX10 front end is due to the high Q obtained by decreasing the L/C ratio and by decreasing circuit resistance with large-diameter wire in the tank coil.

Perhaps we've been on the wrong track by climbing the vertical wall of the superhet for 50 years. Maybe we should go back and see if there's a path, or freeway, around that wall.


references

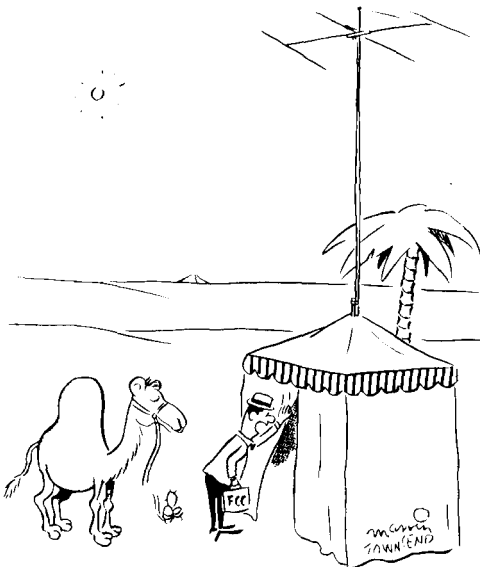1. Richard S. Taylor, W1DAX, "CW Transceiver Operation with Transmit-Receiver Offset," *ham radio*, September, 1970, p. 56.
2. Rick Littlefield, K1BQT/6, "The Sideband Minutener," *ham radio*, October, 1970, p. 16.
3. Skip Tenney, W1NLB, "Ten-Tec RX10 Communications Receiver," *ham radio*, July, 1971, p. 63.
4. Morgan W. Godwin, W4WFL/1, "Ten-Tec Model RX10 Communications Receiver," *QST*, July, 1971, p. 44.



"Sir, are you aware that you are interfering with television reception in this area?"

ham radio

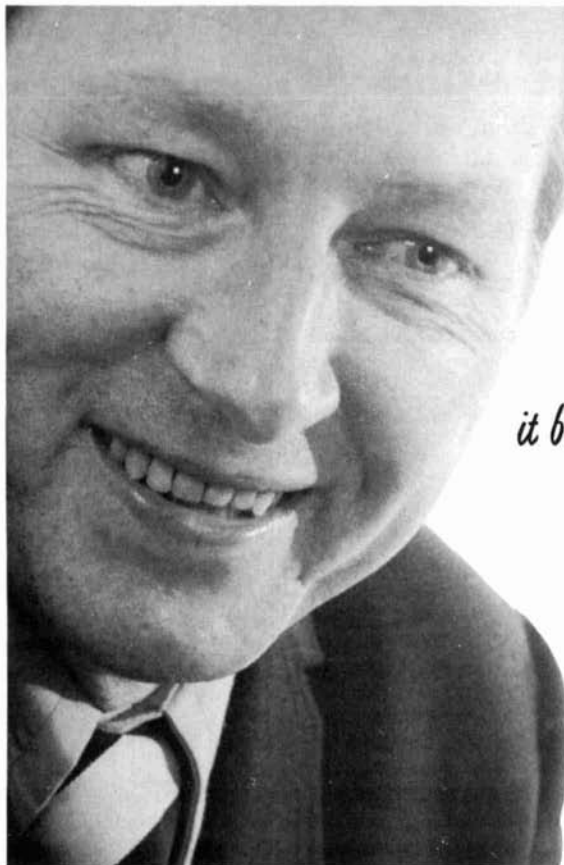

*"I guarantee,
that if you're not
100% satisfied with your
new Swan FM 1210-A
transceiver, you can send
it back to me for a full refund."*

George, W60GM

(G. W. McGinley, executive vice president
and general manager, Swan Electronics)



Now 144 channel combinations, for 2-meter FM, are possible with Swan's new FM 1210-A transceiver. You can avoid crowded frequencies and virtually eliminate unwanted QRM. Independent switching for transmit and receive tuning, coupled with a capacity for 12 transmit and 12 receive crystals, gives you a wide choice of channels from 144 to 148 mc.

Regardless of its price, no other 2-meter transceiver has better selectivity than the Swan FM 1210-A. You can count on Swan's 16.9 mc crystal lattice filter to substantially increase the rejection of adjacent channel interference.

More. No other 2-meter transceiver has a crystal oven for superior $\pm .001\%$ frequency stability in environments ranging from -30° to $+50^\circ$ C. And, every crystal has its own trimmer capacitor for exact frequency adjustment.

Another exclusive: Every Swan FM 1210-A comes with a heavy-duty, pedestal type, AC power supply as part of the deal. For a compact base station, efficiency and performance, you can't beat the new Swan FM 1210-A.

\$329

plus shipping
(Calif. residents
add sales tax)

*Package includes: Dynamic
microphone, antenna connector
plug, spare tubes and lamps, AC
power supply, DC power cord,
and mobile mounting bracket.*

**As little as \$10 per month on Swan's new
Revolving Credit Service:**

\$26 down, \$10 mo. on unpaid balance. Annual percentage rate is 18%. (BankAmericard and Master Charge accepted)

 **SWAN**
ELECTRONICS
A Subsidiary of Cubic Corporation

305 Airport Road; Oceanside, California 92054
(714) 757-7525

**SEE THE NEW SWAN 1972 SPRING CATALOG
FOR LIST OF FM 1210-A SPECIFICATIONS.**

Mail to: **SWAN ELECTRONICS, Dept. H**
305 Airport Road;
Oceanside, CA 92054

Please send me the following:

- Model FM 1210-A (Full payment enclosed)
 Model FM 1210-A (Charge my account # _____)
 Swan's 1972 Spring Catalog
 Swan's Revolving Credit Service Application

Name _____ Call _____

Address _____

City _____

State _____ Zip _____

14205

digital station accessory

Concluding
construction details,
including the
input amplifier,
and counting circuits
for direct
frequency read-out
of your receiver
or transmitter

My first counter, fortunately, used the relatively slow Fairchild DTL 9093 dual flip-flops. Two of these and a gate can divide by ten, with no input circuitry, from low audio rates up to 2.2 MHz. For many digital dial read-out purposes, however, these will not do for the first decade or so. Higher-speed TTL units are comparable in price, but take more care in driving the first FF to make them toggle (and produce a divided output).

Later, the decade dividers became available at reasonable prices. The ones tried here — the Sylvania SM90 which has no counter outputs and the 7490 made by Texas Instruments, National Semiconductor, Philco, Motorola and others — all toggled directly at low audio rates as well as at rf. In normal use these are up-counters; although with decimal read-outs like the Nixie, down-counting can be arranged by inverting the wiring.

Data sheets indicate a maximum frequency of 10 MHz, minimum, and 18 MHz, typical, for the 7490. My tests showed that some ICs toggled to a maximum of 30 to 41 MHz without an input amplifier, and much higher with certain amplifier circuits. Care must be taken to bypass the plus V_{CC} to prevent spikes from causing a miscount which can occur when noise or hum is present. Some types of input circuitry require relatively high input at low audio frequencies. Careful design of input circuitry for proper wave shape and signal level may be required to toggle the ICs from low audio frequencies up to extreme frequencies.

For most purposes a selected SN7490N decade can start the count string, following a satisfactory count gate. Tests on the low-cost SN7400N quadruple two-input gates indicated that a few operated above 110 MHz. One high-speed SN74H00N went to 45 MHz.

The JK flip-flops, such as the Sylvania SF7473N, were somewhat variable when tested on audio and rf. Several went to 33

E. H. Conklin, K6KA, Box 1, La Canada, California 91011

or 34 MHz, but others did not. Therefore, if one of these units is used in the first counting position, selection is desirable.

Fully programmable up/down counters can be preset readily to start at any number so that division can be by any number. Most interest has been in decade operation, such as is provided by the SN74192N synchronous, programmable up/down decade counter. Input clock frequency typically can be 32 MHz. Power dissipation is greater than the 7490 decade counter.


The 74192, when used as the initial count FF, requires a count gate. Note that down-counters may be needed in only some decades. That is, if a receiver dial reads only to 0.1 kHz, and a one-second counting gate is used, the units and tens decade counters can be 7490 up-counters because they do not affect the read-out. Furthermore, the MHz counter also can use 7490 up-counters if they do not affect the read-out.

fier can be very strict if the digital station accessory is to be used for many purposes. It should be possible to obtain suitable drive for the first count IC, U16, with any input from about a tenth of a volt, to 25 volts or more. The impedance should be high so it does not significantly disturb the circuit to which it is attached. It should require no tuning or adjustment; it should respond to frequencies from below five hertz up to 50 MHz or so. Also, it should drive the first count IC reliably.

Although the 7490 decades will respond over such a frequency range, it is not always convenient to connect the IC directly to the circuit. This has resulted in a great deal of experimentation, and some of the more difficult problems were solved while resting in the middle of the night!

The basic circuit started with the seven-transistor amplifier used in the new 80-MHz Heath SM-105A counter. This

fig. 1. Input amplifier. See text regarding bypass of R9 and variations in resistor values. Q1 is Heath (T1) 417-251 at \$2.25; Q2 is Heath 417-260, 80c; Q3 is Heath 417-125, 65c. Noise generation somewhere ahead of Q1's input gate was minimized by connecting 30 pF from final output to ground.

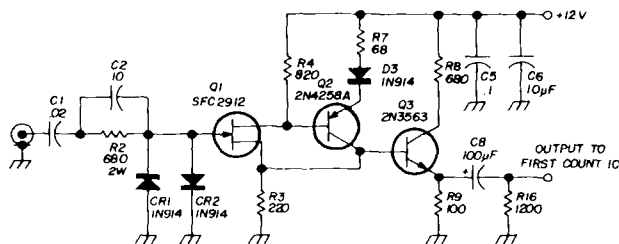

Dc wired information from a band-switch can be provided to the megahertz read-outs without any counter, latch or decoder/driver for MHz information. Of course, this works best on amateur band equipment, but MHz read-out probably would be eliminated on all-wave receivers where 30 switch positions may not be tolerated anyhow. To clarify this, note that the down-count is a frequency division just like an up-count. The only difference is the direction of the BCD count going to the read-out display.

input amplifier

The requirements for the input ampli-

circuit was found to be sensitive as to selection of voltage, components and part values. The substitution of the 2N5485/MPS107 jfet, an inexpensive plastic device, proved to be subject to problems. Some of these problems did not affect another amplifier of similar design which used the metal-cased SFC2912 (Heath 417-251, \$2.25), the case of which can be grounded. Somewhat improved performance may be obtained by further variation of resistor values from those shown in fig. 1, but the values shown do work.

Using a large output-coupling capacitor, and a variable sink resistor across the

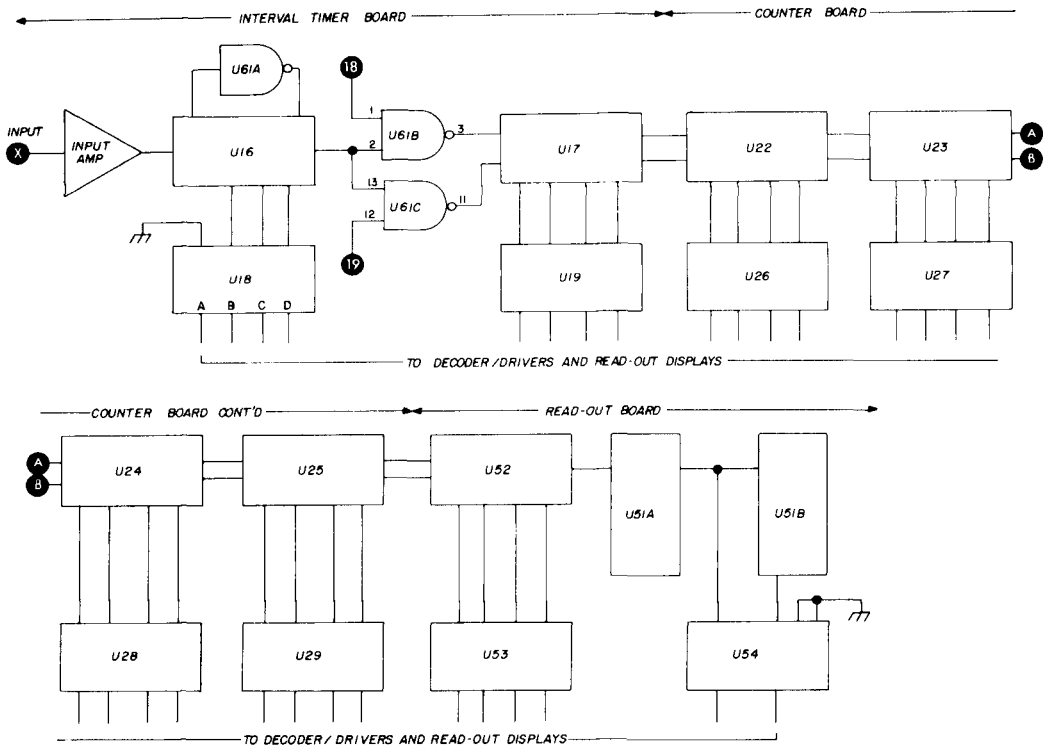


fig. 2. Flow chart for counter ICs. Circle are plugs.

following IC, this amplifier successfully drove a selected 7490 FF to 65 MHz. When the capacitor and a fixed sink resistor were installed permanently with shortened leads, there was some sacrifice in performance, but results were still adequate. The first IC, the A section of a TC7490E,* followed by a 74H00 gate, toggled accurately to 52 MHz when R9 in the amplifier was by-passed with several microfarads. A Philco 7490 counted to 34 MHz.

A 15- μ F capacitor temporarily installed across R9 increased amplifier output and produced a square wave. However, when the leads were shortened and the fixed resistor substituted, the capacitor was omitted to prevent possible injection of noise which might result in miscounting; later, I found that toggling of the first IC on audio frequencies was

being affected by spikes on the 5-volt power supply line. No further attempt was made to readjust the value of R16, the IC input sink resistor, for maximum frequency; counting from below 4 hertz up to nearly 50 MHz seemed adequate.

The input amplifier occupies about one square inch of the upper rear corner of the IT-board, and does not interfere with the mounting of the DIP ICs on that portion of the board which carries the V_{CC} and ground busses. Also, it leaves space for the end-mounting of steering diodes for multiple programs for the up/down counters. The top edge buss had been opened for use as a plus 12-volt V_{CC} buss for the input amplifier (connected to Plug-Y). The remainder of the edge buss remains at ground potential, plug-Z.

count chain

Vector sockets were provided for the count gate, U61A, and the first two count ICs, U16 and U17, shown in the

*Available from Solid State Sales, Box 74, Somerville, Massachusetts 02143.

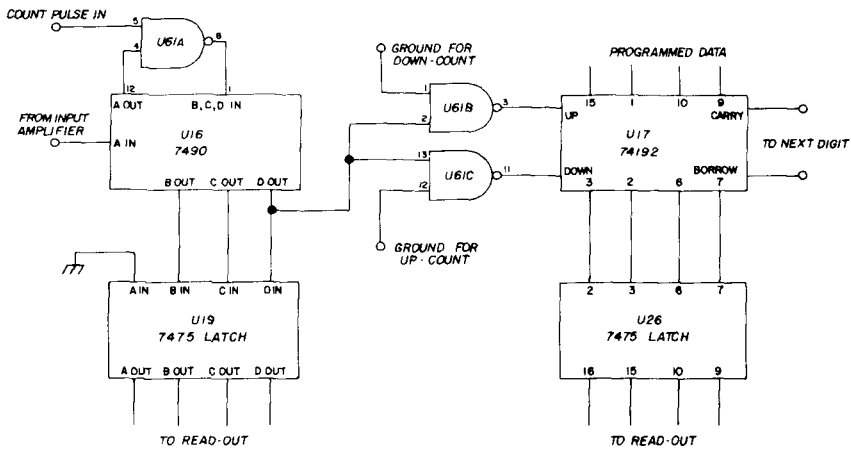


fig. 3. Flow chart for input gates and first two counter decades.

block diagram, fig. 2. These facilitate testing individual ICs and selecting the most satisfactory one for these critical positions.

Ordinarily, the input signal passes first through a count gate which controls the time during which the count is made, and the output drives the first FF. However, this resulted in some limitations (later found to be associated with noise spikes on the power supply) which were readily overcome by an unusual course. The A section of a selected 7490 decade up-counting divider, U16, was driven directly by the amplifier; this was followed by the count gate U61A which drove the BCD section of the 7490 (see fig. 3). This odd arrangement allows the A section to continue to count; the effect on the read-out is eliminated by tying the U18 latch input to V_{cc} or ground, whichever tends to correct the normal one-count error due to the relative phase of the time-base gating and input wave. At most, it will produce an error on one hertz in the count.

If part of the same gate is used for coincidence-gating, such as was done in U61D, there will be some interaction in the outputs of all gates in the same IC, even when V_{cc} is adequately by-passed to ground. Although this possibility should be kept in mind it did not cause any trouble in my unit.

Following the A section of U16, up and down gates U61B and C were installed for later use with the 74192 up/down counters. If 7490s are used these gates should be omitted.

The 7490 up-counting decade FFs may be used for U17, U22, U23, U24 and U25. These will be satisfactory for normal counting functions and for counting the synthesized operating frequency.^{1, 2, 3}

The outputs of the counting decades are connected to the numbered D inputs of their respective 7475 memory latches, U20, U21, U26 through U29, U53 and U54. For use with MSD047 or SN7447N decoder/drivers and Minitron read-outs, the latch Q outputs are wired to the decoder/drivers on the read-out board.

Note that the V_{cc} switching scheme permits wiring the count latches on the IC-board to the AND gates which control clock information (but capacitors must be installed across V_{cc} switching contacts to keep the clock from advancing). Note that the final two decades are on the read-out board. The last of these is a dual JK FF which is adequate for a count of four; it repeats if the frequency is 40 MHz or above.

The general wiring of the 7490 ICs is much the same as described last month, except that it is necessary to reset all of the count decades after the end of the

count and after the transfer pulse, to display the count, and be ready for the next period. This means that there never is a grounded R_0 reset input in the count

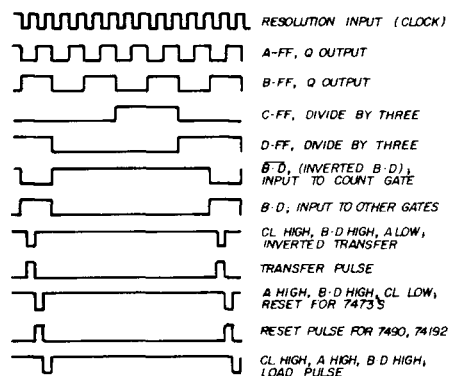


fig. 4. Pulses from resolution input, through divider U20 and U21, and selection of coincidence gating to generate the necessary pulses.

chain. However, one R9 input on each IC should be grounded.

gating

The gating system follows the general plan described by Kenneth Macleish, W7TX.² However, there are many ways to accomplish this.

By charting the divide-by-two and divide-by-three square waves at the end of the time-base chain, fig. 4, it is easy to select gating inputs that will provide a one-second count period (or decimal fraction). After this, there must be a short off-period containing a transfer (memory latch) pulse and a reset pulse. For 74192 up/down counters, there also must be a load pulse which transfers the programmed frequency correction into a presetting of the 74192 counters from information at their data inputs. These pulses can be produced simply by coincidence gating. Connecting the gates to the correct square-wave output produces the desired pulses at the right times.

Although this method is widely used there may be a small error in having reset pulses begin or end with the finish or start of the count period. This is because

the propagation time through an IC may not be the same as the time required for resetting it. Therefore, the positioning of these pulses in the noncounting period has been selected differently.

Also, the divide-by-twelve SN7493N, used by W7TX as a final time-base divider, was replaced by two 7473 dual JK flip-flops. One of these could have been the 16-pin SN7476N, which is available at surplus prices. This has a common clock for the two FFs so, generally, it may be used where that is satisfactory, including the divide-by-three circuits in the time and clock sections. The 7476 is provided with separate clear and preset pins which are useful for counting days and months which start with "1".

Fig. 4 shows the pulses in the final time-base divider, using the two 7473s. The entire gating schematic is in fig. 5. Note that the Q and not-Q outputs are useful to avoid the requirement of a reversing NAND gate.

The load function in the 74192 up/down counters must be eliminated, or the load data be zero, in every case for unprogrammed counting of some unknown frequency. This can be done in several ways, including running the load signal out to a switch and back again. Fig. 7 includes gate U60D, otherwise unused, which can be used with another NAND gate (or both can be replaced with one AND gate) to give one-wire control over a program loaded into the up/down counters.

Some resets, such as that for the 7473s, go to ground to reset. Others, like the 7490 and 74102, must go to a logic high. Because there is a fan-out limit of eight to ten in DTL and TTL gates, the reset signal for the 7473s is wired out to other boards on plug-D. NAND gates U62C, U70C and U80A invert the reset signal on those boards as necessary for 7490 and 74192 ICs.

Each memory latch presents a load of four FFs to the transfer pulse. Thus, only two 7475s are being driven by one gate section. An inverted transfer pulse is wired out to other boards, then inverted by NAND gates U62D, U70D and U80B.

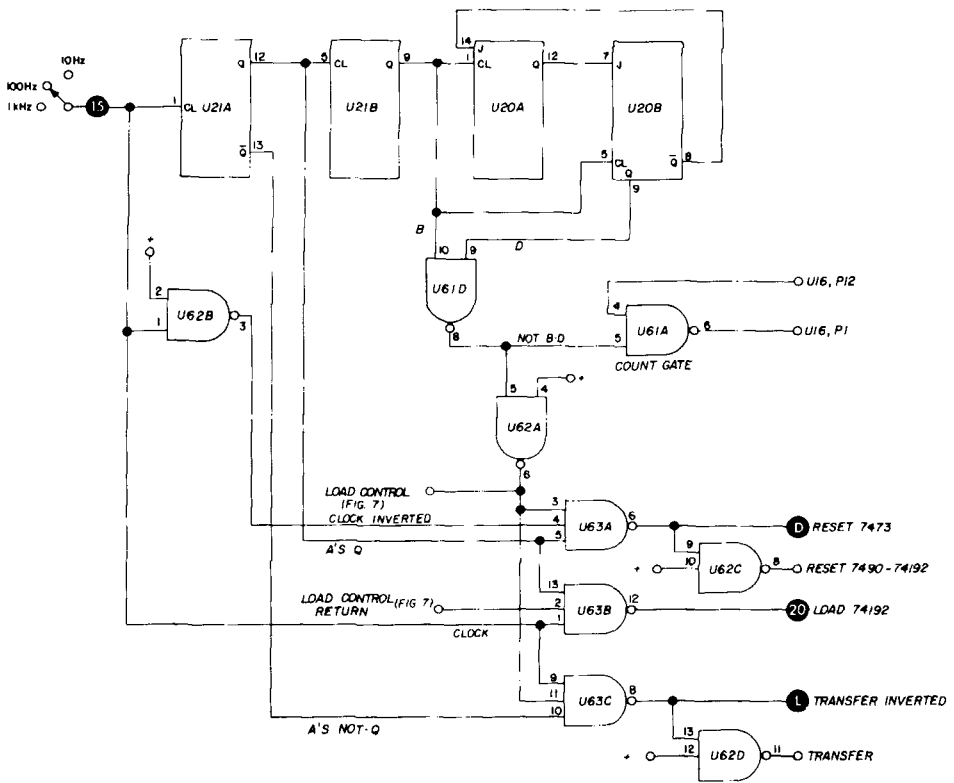


fig. 5. Detailed flow chart from resolution to generation of pulses, with pin designations. See fig. 7 for single-line load control using two NAND gates or one AND gate.

Three "resolutions" are provided at plugs 12, 13 and 14. The one-second gating counts units of hertz; the one-tenth-second gating counts tens of hertz; and the one-hundredth-second period produces hundreds of hertz. For some fast-tuning applications the shorter count periods are useful. Also, during CW and RTTY keying, the short periods will occasionally produce a stable read-out, while others will be short-counted due to keying during the gate-open time. This occurs in the "signal mode" of the synthesis method, but not in the vfo count method that will be described later.

When up/down counting is used with the loading of a correction, it would be complicated to change the programmed loading for more than one counting period. Therefore, only one resolution is suggested: Whenever the switches inject a

programmed correction which is satisfactory to the operator.

The different pulses can be seen on a scope but it is somewhat of a problem to identify where each one occurs in the non-counting period. In case of trouble, try disconnecting one source of these pulses and study what happens. When the coincidence gating plan is worked out and followed, however, everything turns out right. Nevertheless, keep in mind that a reset pulse before a transfer pulse will give a read-out of exactly nothing. A reset pulse after a load pulse in the 74192 will clear the load. This could be useful in preventing the loading function, if properly planned.

testing

It is possible to feed the input amplifier with 60 Hz from the ac line, an audio

oscillator, a grid-dip oscillator or a tap from the timing chain to test the count chain. A scope together with ac and dc inputs to meters can also be used. The dc assumes a medium value except that it is lower in the D output of decades due to the duty cycle in the divide-by-five section. The scope distinguishes between true stable counting and added noise counts. A low-C probe for the scope and an rf probe for the meter are necessary at high frequencies. However, the scope can often be put at the end of a decade or two to show what is going on at high rf inputs. Above 20 MHz or so, there does not seem to be much of a square wave anywhere.

digital dials

W7TX has covered the method of synthesizing the original transmitting or receiving frequency by heterodyne mixers. In this method, the three frequencies in the Collins S-Line are mixed in a manner that results in up-counting the synthesized operating frequency itself.

In general, this method is accurate, although you can expect one small difference: When in the transceive mode, the transmitter is on a slightly different frequency if the bfo is not on the same frequency in the two units — due either to the receiver's variable bfo or to the fact that the two bfo crystals may not be on exactly the same frequency. This would show up if the counter were switched from the receiver to the transmitter.

In some types of reception, the count accuracy depends upon zero beat. This is satisfactory with ssb, but involves some possible error on CW unless some means of limiting the error is employed. In correspondence W7TX pointed out that sufficient bfo signal leaks into the i-f so a scope on the i-f output would indicate when there is zero beat between the signal and the bfo. Also, the "signal mode" by which the i-f signal itself is counted, rather than the bfo, is often preferred by the user.

When the signal is keyed, the counting in the signal mode may be a longer period

than the dashes, thus giving many short counts unless the key is held down. This happens particularly in the high resolution (long counting period). On the other hand, while the read-out will often stand still in the lowest resolution (short counting periods) the decimal point then is moved over so that the frequency is not measured as accurately.

If an oscillator, such as the exciter's CW calibrator, is placed in zero beat with the signal, or to one side of frequency-shift keying, accurate information on frequency and shift can be obtained.

Somewhat more design work may be required for using the synthesis method in some receivers³ such as those where the heterodyning process changes on different bands. In some others, such as the Racal,⁴ it may prove to be almost impossible to filter the resultant desired frequency from all its components.

It has been mentioned in the Motorola application note that the MC1496 and μ A796 double-balanced mixers can operate as frequency doublers by introducing the same signal at both input ports. Such a device might provide a convenient way to multiply oscillator frequencies to separate several receiver or exciter oscillators.

The CA3001 amplifiers are covered by an RCA data sheet, File No. 122, and an application note, ICAN-5038. Although many of the circuits shown require a negative as well as a positive power supply, the small negative current can frequently be obtained from the same power supply.

The cost of the CA3001 is higher than that of the MC1550. The CA3001 differs from several competing types due to the incorporation of emitter-followers. These permit cascading stages with similar connections. Useful gain can be obtained beyond 30 MHz although the design goal was 20 MHz in a broadband amplifier.

Tests of the low-cost MC1550 provided negative gain when I attempted to cascade two of them. Motorola Application Note AN-299 discusses this, and proposes that the second of a two-stage video amplifier be operated as a com-

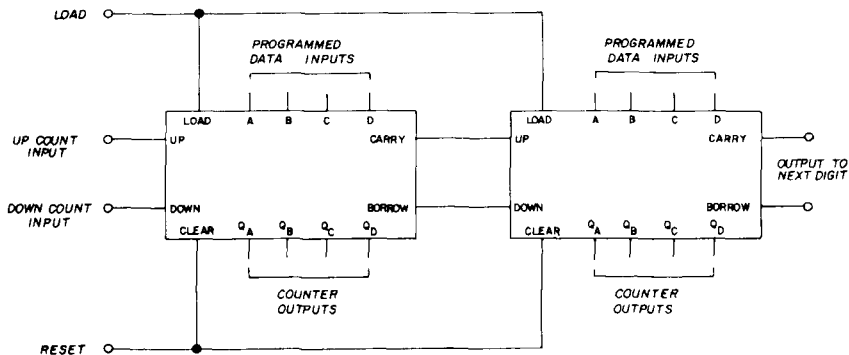


fig. 6. Method for using serial up/down counters, type 74192.

mon-collector, common-base amplifier. This permits direct capacitive coupling between stages.

Both of these devices can provide symmetrical limiting, thus tending to square up the waveform when the low input requirements are exceeded slightly.

Another matter should be kept in mind when recreating the original operating frequency. The recreated original frequency should not create interference to the receiver. Also, the transmitter output should not cause troubles in the counter.

In arranging the switching in the station digital accessory, provision was made for use of the synthesis method, and also for putting a vfo signal through a tuned circuit and separate amplifier before connecting it to the counter input amplifier. In practice, however, the Racal and Collins receivers produced adequate voltage directly at the counter amplifier without the use of a tuned circuit or special amplifier. However, such an amplifier should increase the isolation between the receiver and the counter, which would be desirable.

up/down counting

One goal for the digital station accessory was to provide for a direct vfo count with programmed frequency corrections. In that way, the dial of essentially any receiver or exciter can be replaced with a digital electronic counter. One means to do this is with the 74192 up/down

counter.* Like the 7490 decade, it takes a plus voltage to reset. It has two inputs and outputs, one input to be driven while the other is held at a logic high. It has four binary-coded decimal inputs for pre-setting when a load terminal receives a logic low pulse. These BCD inputs, when not connected, will assume a logic high, so they must be grounded if a load pulse is not to transfer the BCD inputs to the internal decade counter. It is shown in fig. 6. As stated, the up/down counter actually is a frequency divider like the 7490 and programs always go high, but only the BCD read-out is down-counting.

The digital accessory, as now built, continues to use the A section of a 7490 before the count gate, to obtain suitable performance, followed by the BCD section (see fig. 3). This means that the units read-out will actually be up-counted, never down-counted. However, if the units figure is required, all is not lost. It is necessary only to subtract it from zero for the actual frequency. For example, say that a frequency shows as 14,200.794. Subtract the ending 4 from 790, and the actual frequency is 14,200.786. This is subject to the plus or minus one-count error of the count gating and the A section of the first decade.

Also, only five up/down counters are

*Although not advertised at a comparable price, the one-line-input and up/down control is available in the SN74190N. The programmable SN74196N decade is also useful, but it is an up-counter only.

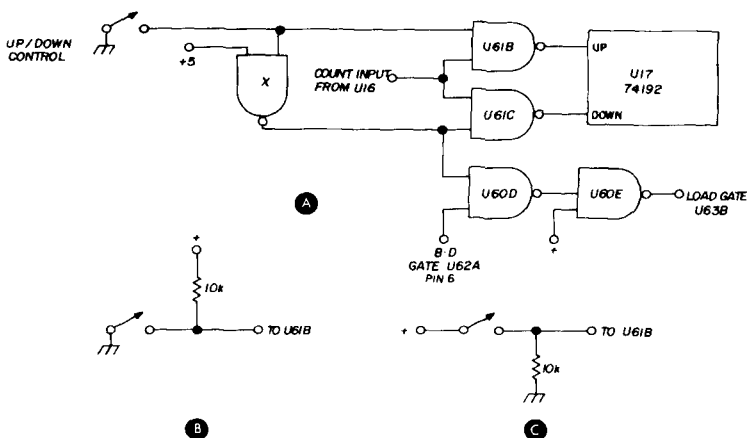


fig. 7. (A) Proposed method of single-line control of up and down count, with automatic elimination of load pulse for up-counting, if desired. Note that U60D can be fed from a switch as a single-line control. (B) Method of forcing gate inputs high if they do not assume a high level. (C) Method of using a switch on positive instead of negative power if desired for switching convenience.

used. One reason is that it is not usually feasible to count the megahertz in vfo counters, although arrangements could be made for a dc-switched display of megahertz. The carry from the sixth read-out to the seventh and eighth, therefore, will be up-counted. It is convenient to cut them off.

Ordinarily, the seventh decade could be driven by the D output from the last up/down counter. However, if it is driven from the carry output of the up/down counter, then the seventh and eighth read-outs will operate only on up-counting, but not on down-counting, which is desirable. This fits the specific application for the Racal receiver, and may fit others as well because the vfo itself does not indicate the band involved.

When tapping signals from the receiver oscillator or mixer, take care to avoid noise, birdies or transmitter pickup on the lead. RG-62A/U coax has been recommended for its lower capacitance than RG-58B and RG-174. For testing purposes, a Vector Voltage and Current Test Adapter can be inserted under the desired tube. It permits attaching a resistor in series with the coaxial cable. The resistor frequently can be as large as 5k to 7k. The coax feeds the counter's input amplifier through a selector switch. Should the

signal not be sufficient, presumably a CA3001 or MC1550 IC video amplifier, possibly with a tuned circuit, could be inserted.

If the one-second display is not too far behind the tuning dial rotation rate, it is the most satisfactory resolution. Next would be the 10-Hz resolution, producing a one-tenth second count; this takes one less up/down counter, but removes all doubt as to the nearness of the indicated frequency to the 0.1-kHz read-out. In any event, you may make switching provisions to remove V_{CC} or ground from the decoder/drivers and read-outs beyond the effective count digits for the application involved, should they show up and be disturbing to the accurate reading of the dial.

Usually there are several ways to do the switching and control. The up/down counters must have plus V_{CC} on the unused up or down input. One way to do this is to have two gates, one for up-input and one for down-input, so arranged that a ground on the control-line second input of a gate will make that one's output go high (see fig. 3). This requires two control lines and, sometimes, more than minimum switch facilities.

A single control line, either for V_{CC} or ground, probably can be devised. One

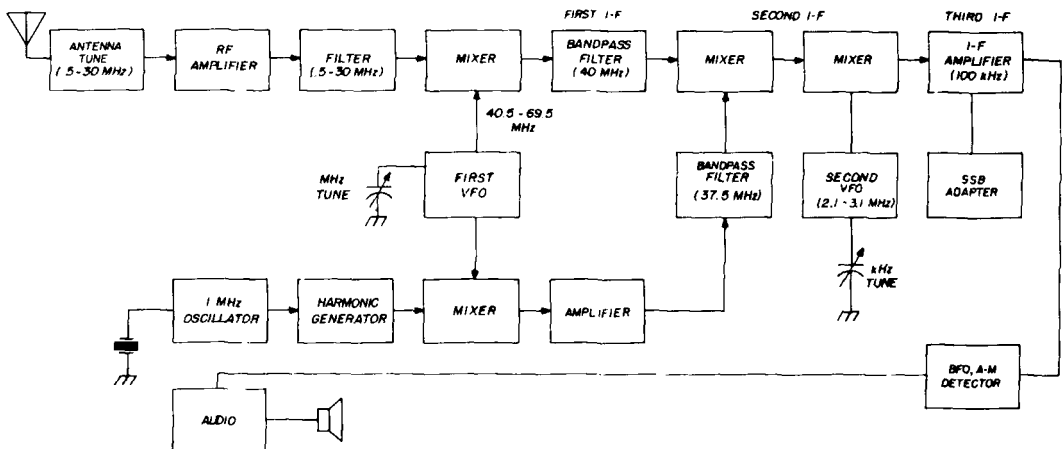


fig. 8. Block diagram of the Racal RA-17C.

way is to place a NAND inverting gate between the second inputs of the two up and down counting gates as shown in fig. 7. If a gate input does not assume an adequate positive potential when left open, a 10k resistor can be provided so that one control line can handle either ground or V_{CC} to switch between up and down counting. One of these may permit using the same switch contacts as already are serving another purpose, such as changing the programmed loading for several bands.

At my station only up-counting is required when not using a programmed error correction, and only down-counting when loading a program. These are suitable for Collins equipment (which can be through a mixing unit) and the Racal (on a direct vfo down-count). The elimination of the loading pulse can be accomplished automatically with a suitable AND gate in series with it, or two NAND gates which will reverse twice.

There are other ways of applying a gate to minimize the number of control lines and switch poles. One way is to use a 4-input load gate at U63B. Another is shown in fig. 7.

It is convenient to use the AND gate or some left-over NAND gates to cut off any one of the coincidence gate inputs to U63B that select the position of the load pulse. One consideration is to feed only a

logic low to a following NAND gate to cut it off — a logic high will wash out the input pulses and feed the following gate with a logic high so it is not cut off.

programming

Let's say that we wish to down-count a vfo, and to have the counting start at a programmed frequency which will correct for all other oscillators and errors in the receiver. This is not difficult.

After a long warm-up, set the receiver dial exactly in zero beat at the zero end of the dial, with WWV or a harmonic of the digital station accessory's crystal calibrator after careful adjustment to WWV. Then, in the up-count position, determine the reading. This becomes the amount to preset into the up/down counters. Each digit should be converted to its binary equivalent, and the ABCD inputs of the 74192 ICs grounded except where they are to be at a logic high as required for the binary equivalent for that digit. Do this for each digit.

Example: The Racal receiver covers the entire 30-MHz range, with or without a tuned input circuit, and beats it with an unstabilized oscillator in the 40 to 70 MHz range. This vfo also feeds a mixer which mixes harmonics of a 1-MHz crystal, passes the mixed result through a 37.5-MHz band-pass amplifier and back to the signal stream. There, a mixer

preceded by a 40-MHz bandpass filter mixes the 37.5-MHz signal to produce a 2- to 3-MHz second i-f (see fig. 8).

Since the unstabilized oscillator is injected and removed (at another harmonic of the 1-MHz crystal) the second i-f signals have crystal accuracy. At this point, a 2.1- to 3.1-MHz vfo tunes the signal, and is counted, before it produces a 100-kHz IF. This, in the RA-17C at least, is mixed with an 82-kHz oscillator fitted with a fine-tuning dial, passes through L/C sideband filters in the 18-kHz range and is detected.

The thing to remember here is that the 2.1- to 3.1-MHz vfo covers a 1-MHz band and contains an error of at least the 100-kHz of the following i-f.

Set the dial at zero (vfo output, 3.1 MHz). Using one-second gating, count the vfo frequency. We can discard the megahertz figure because it will be beyond the first six digits and will not appear on the display, but we must program the 100,000-Hz i-f error and any other little errors lying around. This is done quite simply — by grounding every ABCD data input to the up/down counters except the A input to the sixth decade (fifth up/down counter in this case). This means that the six digits after a reset and load will read 100,000 *before* counting.

Now, for one second, this is down-counted (disregarding the 3 MHz which will not show), and the 3.1 MHz signal reduces the 6-digit reading to 000,000 Hz. This is what we want.

At the 2.1 MHz end of the dial the down-counting would fall 1 MHz short and leave it at 1,000,000 Hz. But, again, the 1 MHz is not indicated. All frequencies between the vfo ends are shown to the Hertz.

If the vfo to be counted has an increasing output frequency with its dial settings, then a slightly different procedure is used. Loading the program results in the same upward indication. But, we need a program below zero, for up-counting. Therefore, turn the vfo to the low-frequency end of the dial, set it carefully to zero beat with WWV or a calibrator harmonic, and count the frequency. This

count must be subtracted from zero, and the result wired into the program.

Again, let's take an example based on a fictitious reversal of the Racal dial used in the down-count example above. Assume that zero frequency produces a 2.1-MHz vfo output, while the 1000-kHz higher end of the dial produces a 3.1-MHz output. Assume that the count at the low end is actually 2100 kHz. Here again, it would be desirable not to indicate megahertz through counting spill-over into the seventh and eighth decades. So, we have 100,000 to program. We subtract this from zero; the answer is 900,000 (to six figures). In the sixth count decade — in this case the fifth up/down counter — the A and D inputs should be left open or connected to a logic high, and all other inputs should be grounded.

Let's examine the results. The oscillator is at 2.1 MHz, so it starts up-counting at 900,000. The first 100,000 Hz brings it to an even 1 MHz, and the next 2 MHz brings it to a total of 3 MHz. But we decided not to indicate the MHz reading by a counting means, so the read-out is 000,000 Hz. Similarly, at the high-frequency end, the 900,000 programmed figure is raised by 3.1 MHz to a total of 4 MHz, and again it reads 000,000 Hz, inasmuch as we do not indicate the 4 MHz.

The Racal's fine-tuning control on the stable 82-kHz oscillator makes it possible to use the 100,000 program in every case, and then to adjust the zero setting on WWV with the fine tuning, which holds for every band.

To avoid errors due to the Racal's 1-MHz crystal being slightly off frequency, remove the 1-MHz crystal and feed the oscillator with 1-MHz obtained from the counter's 1-MHz test output, plug 5 of the input and time-base board as shown in fig. 2, last month.

Soldering does the job when only one band is to be programmed (30 bands in the Racal). In many receivers, however, five or more bands, involving different errors, may be present.

The bandswitch on the digital station accessory can be set to the same band as

table 1. Plug assignments common to two or more boards.

plug	to	purpose
D	RO-C-IT	reset 7473
E/J	reserved	program
K	BS3e	program
L	all	transfer invert
M	RO-C	count in/out
NPRS	IT-RO	tens BCD
TUVW	IT-RO	units BCD
Y	power	+12 V _{CC}
4/7	RO-C	100k BCD
8/11	RO-C	10k BCD
12/15	RO-C	1k BCD
16/19	RO-C	100-Hz BCD
20	IT-C	load 74192
21	IT-C	carry/up
22	IT-C	borrow/down

the receiver or transceiver. This switch can provide a pole for selection of up or down counting, provision of the load pulse and selection of the correct program for the band. Instead of soldering the programmed inputs in place, all programs should be counted for several bands, and written down. Then, convert these to binary-coded decimal for each digit. Add the values of the A, B, C and D outputs (1, 2, 4 and 8) to convert.

If all bands require a particular input pin to be at a logic high, that pin is left open. If all bands require a particular data input to be at a logic low, the pin must be grounded. But many inputs will have to be high on some bands, and low on others. For those bands on which a specific input must be grounded, this can be done through a steering diode (they can be mounted perpendicular to the *Plugbord* in nearby unused holes) for each affected band, with anode to the pin and cathode to the bandswitch contact. Then, when the bandswitch is turned to a particular band, it will ground all diodes connected to that contact.

For a particular five-band equipment, as many as four diodes (such as surplus silicon small-signal diodes) may be necessary to connect a particular input pin to the switch contacts for several bands. In the equipment described, with five up/down counters, each with four inputs, as many as fifteen diodes could connect to a single band-switch contact. On the aver-

age, however, somewhat less than half of this number may be necessary for the required programs. Five board plugs, E through J, have been reserved to ground the program input pins.

If the same bandswitch contacts are to be used for grounding some other circuit, such as up/down control, a steering diode may be required in this additional line to prevent the assumed logic high on the input pins from affecting others.

For ultimate cycle-accuracy, much of the above depends upon determination of zero beat. Sometimes, particularly with high-fidelity earphones or a loudspeaker, this can be done by ear. W3FQJ has described how to use a scope to show zero beat when connected to the i-f.⁵ Another way is to use a separate audio oscillator, and adjust WWV and the vfo under test to the same audio beat, and then correct for the indicated offset oscillator frequency. A source of this audio signal is the 1-kHz output from the time-base chain of ICs, preferably through a stopping capacitor or high value resistance. When WWV or any other signal is in phase with this 1-kHz signal on the scope, the vfo is exactly 1 kHz off zero beat, and the read-out can be corrected mentally.

wiring

The time-base wiring was described last month. The remaining wiring for the input amplifier, resolution, gating, control and count decades can follow the accompanying figures and tables. These are based upon separate up/down controls, and taking the load-pulse control line out to a switch. Methods of reducing the plug and switch requirements for these have already been discussed. Addi-

table 2. Additional plug assignments for the input and time-base board.

plug	to	purpose
12	RS4b	1 kHz
13	RS4c	100 Hz
14	RS4d	10 Hz
15	RS4f	resolution
18	BS2c/j	up count
19	BS2b	down count
X	MS4a	rf in
M	BS3a	load control

table 3. Additional plug assignments for the read-out board.

plug	to	purpose
X	RS2b	decimal U32
21	RS2c	decimal U33
22	RS2d	decimal U34

tional plug assignments are given in tables 1, 2 and 3.

Connect all V_{cc} pins to the V_{cc} supply. Bring a NAND gate input, if unused, to V_{cc} . Bring all ground pins to the ground bus. In the final divider and the gating, follow fig. 5. Proceed with the detailed board connections listed in table 4 for the input and time-base board. Note that +5-V buss for both plug-A and plug-B, on each side of the broken foil, must be connected to their proper plugs.

The count-board connections are given in table 5. Make similar connections from decade dividers to memory latches in each decade. The latch outputs can be connected more easily to the AND gates from the timer FFs than directly to the indicated plugs. However, there are three places where there is no time output from the time FFs to the plugs due to minutes and hours being less than 100. With counters being fed V_{cc} through plug-A only when counting, and the AND gates receiving +5V from plug-W only when time is displayed, the outputs can operate in parallel as indicated.

The read-out board connections appear in table 6. Connections for eliminating leading-edge zeros have been discussed; other connections involving the decoder/drivers and the read-out units are the same for each digit. Note, however, that the two unused inputs to the final memory latch should be grounded (or the same inputs to the decoder/drivers should be grounded) to prevent arbitrary activation of the final read-out above the digit 3. It will be recalled that plug-B is used for +5 volts to the middle four digits for use as a digital clock, and the two digits at each end receive their +5 volts from plug-A.

Switch wiring, using a new 4-pole, 11-position bandswitch for controlling

band, up/down count, loading and load pulse is tabulated in table 7. No specific assignments are given as yet to the plugs for the mixer board, which has not yet been wired and tested with the shielded Weeductors and the MC1550 amplifier. Should anything of unusual interest develop in its construction, supplementary material will be published in *ham radio*.

To minimize the chance for switching that might step up the digital clock, a filter capacitor was added from the +5-volt switchable power supply to ground. Also, several 10- μ F capacitors (or larger) were put across the resolution switch contacts to ground whenever they in-

table 4. Connections on the input and time-base board.

from	to	purpose
Plug-X	amp input	rf in
Plug-A	V_{cc} bus	+ count
U16p14	amp out	count in
U16p2	V_{cc}	unused
U16p3	U62Cp8	reset
U16p7	ground	R9
U16p12	U61Ap4	A out
U16p1	U61Ap6	BCD in
U16p9	U18p3	B out
U16p8	U18p6	C out
U16p11	U18p7	D out
U18p16	Plug-T	A out
U18p15	Plug-U	B out
U18p10	Plug-V	C out
U18p9	Plug-W	D out
U18p2	ground	A in
U61Bp1	Plug-18	up
U61Bp3	U17p5	up
U61Bp2	U61p11	D out
U61Bp2	U61Cp12	D out
U61Cp13	Plug-19	down
U61Cp11	U17p4	down
U17p14	U16p3	reset
U17p11	U63Bp12	load
U17p13	Plug-22	borrow
U17p12	Plug-21	carry
U17p3	U19p2	A out
U17p2	U19p3	B out
U17p7	U19p6	C out
U17p6	U19p7	D out
U17p7	Plug-N	A out
U19p16	Plug-P	B out
U19p10	Plug-R	C out
U19p9	Plug-S	D out
U62Dp12	V_{cc}	transfer
U62Dp13	U63Cp8	transfer
U62Dp11	U19p4/13	transfer
U19p4	U18p4/13	transfer
Plug-Y	+12 bus	amplifier V_{cc}

table 5. Connections on the count board. See text regarding similar connection to each decade.

from	to	purpose
Plug-A	V _{cc} bus	+ count
Plug-21	U22p5	up
Plug-22	U22-4	down
Plug-D	U70Cp13	reset
U70Cp11	U22p14	reset
U22p14	U23p14	reset
U23p14	U24p14	reset
U24p14	U25p14	reset
U70Cp12	V _{cc}	unused
Plug-L	U70Bp4	transfer
U70Bp4	U70Op10	transfer
U70Bp5	V _{cc}	unused
U70Op6	U22p4/13	transfer
U22p4	U23p4/13	transfer
U70Op9	V _{cc}	unused
U70Op8	U24p4/13	transfer
U24p4	U25p4/13	transfer
Plug-20	U22p11	load
U22p11	U23p11	load
U23p11	U24p11	load
U24p11	U25p11	load
U22p13	U23p4	borrow
U22p12	U23p5	carry
U23p13	U24p4	borrow
U23p12	U24p5	carry
U24p13	U25p4	borrow
U24p12	U25p5	carry
U25p12	Plug-M	count out
U22p3	U26p2	A out
U22p2	U26p3	B out
U22p6	U26p6	C out
U22p7	U26p7	D out
U26p16	Plug-16	A out
U26p15	Plug-17	B out
U26p10	Plug-18	C out
U26p9	Plug-19	D out
U27p9	Plug-15	D out
U29p10	Plug-6	C out
U29p9	Plug-7	D out

involved breaking the +5-volt supply to the AND gates on the count board, breaking the supply to the time decoders and read-outs and breaking the +5-volt supply for counting.

potpourri

The possibility of rf interference to the counter has been mentioned. A completely closed cabinet or chassis might be useful, but may not be effective unless the 117-volt ac supply and other leads from the unit were suitably treated. In the presence of substantial capacity on input and output circuits, and IC count

input and output circuits do not always toggle properly.

Interference from the counter was reduced materially by placing a 0.02- μ F capacitor directly across the input of each LM309K and LM336 voltage regulator. Interference was also reduced by reversing the power plug — which suggests that a statically shielded power transformer might be useful. There was also some leakage of 1-MHz harmonic output, modulated nearby by 1 kHz, which did not occur in the earlier counter which used a double switch to prevent leak of the calibrator signal to the receiving antenna.

Shielding is needed to avoid addition of receiver birdies and other noise into a counted oscillator. This is more likely to occur with the direct up/down counting method (unless an IC amplifier reduces it)

table 6. Connections on the read-out board.

lug	to	purpose
V _{cc}	Plug-A	+5 volts
ground	Plug-Z	-5 volts
Plug-M	U52p14	7490 in
U52p12	U52p1	A-BCD
U52p11	U51Ap1	count
U51Ap12	U51Bp5	count
Plug-D	U80Ap1	reset
U80Ap1	U51Ap2	reset
U51Ap2	U51Bp6	reset
U80Ap2	V _{cc}	unused
U80Ap3	U52p2	reset
Plug-L	U80Bp4	transfer
U80Bp6	U53p4	transfer
U53p4	U53p13	transfer
U53p13	U54p4	transfer
U54p4	U54p13	transfer
U52p12	U53p2	A out
U52p9	U53p3	B out
U52p8	U53p6	C out
U52p11	U53p7	D out
U51Ap12	U54p2	A out
U51Bp9	U54p3	B out
U54p6	ground	no C
U54p7	ground	no D
U53p16	U45p7	A in
U53p15	U45p1	B in
U53p10	U45p2	C in
U53p9	U45p6	D in
U51Ap12	U46p2	A in
U51Bp9	U46p3	B in
Plug-K	U35p9	decimal
Plug-22	U34p9	decimal
Plug-21	U33p9	decimal
Plug-X	U32p9	decimal

table 7. Wiring connections for the mode switch and bandswitch, including provision for synthesized mixing board and five-band programmed correction.

lug	to	purpose
MS1a	M plug	hf mixer
MS1b	phono	transmitter hf
MS1c	phono	receiver hf
MS1d	MS1c	receiver hf
MS2a	M plug	vf mixer
MS2b	phono	transmitter vf
MS2c	phono	receiver vf
MS2d	MS2c	receiver vf
MS3a	M plug	bf/lf mixer
MS3b	phono	transmitter bf
MS3c	phono	receiver bf
MS3d	phono	receiver i-f
MS4a	IT plug-X	rf in
MS4b	M plug	amplifier out
MS4c	MS4b	amplifier out
MS4d	MS4c	amplifier out
MS4e	phono	Racal vfo
MS4f	phono	counter
BS1a	M plug	mixer out
BS1b	M plug	2 - 3 MHz
BS1c	M plug	3.5 MHz
BS1d	M plug	5 MHz
BS1e	M plug	7 MHz
BS1f	M plug	10 MHz
BS1g	M plug	14 MHz
BS1h	M plug	21 MHz
BS1i	M plug	28 MHz
BS2a	ground	control
BS2b	IT plug-19	down count
BS2c/j	IT plug-18	up count
BS3a	IT plug-M	load control
BS3b	open	load
BS3c/j	ground	no load
BS4a	IT plug-K	program
BS4b/j	reserve	load

than with the synthesis of the operating frequency by the mixer method.

Since building the unit and writing this article, I have found that the power input to the LM309K regulator that most required the 0.02- μ F capacitor across the input had a substantial saw-tooth wave. This mostly was eliminated in the regulator but there were still some small spikes in the output. These may have been caused by the input waveform, or may have come down from the counter, though synchronous with 60-Hz power.

In any event, while the spikes did no harm when counting rf, they occasionally caused irregular counts at audio frequencies. In fact, I suspect that this noise

is responsible for the problem described above in gating the very first FF of the counter, which led to the unusual gating circuitry. Also, it appears to place a limit on how much coaxial cable capacitance can be present on the interval-timer board, to the switch, to the phono plug and beyond the chassis to the receiver. While RG-62A/U cable reduces capacitance, so does the length of the cable. This will be investigated further, with a view to putting the count gate ahead of the A section of the first count decade.

If the bypass capacitors do not eliminate the tendency of switching spikes occasionally to step up the digital clock, to consideration can be given to using a shorting-type switch. If the AND gates cause a spike in the V_{CC} line when it is switched on and off the AND gates, then these gates can be controlled with an input line while leaving the V_{CC} on them.

conclusion

There have been many tests, experiments, substitutions, and the like, in the construction of this unit. However, the results have been worthwhile, making a pleasant addition to operating the station. The unit has been a help in Official Observer and Intruder Watch work, particularly in the ease with which accurate frequencies and fsk shifts can be determined. As stated initially, the facility with which digital IC equipment can be built makes them particularly adaptable for homebrew and self-designed items in the amateur station.


references

1. Kenneth Macleish, W1EO, "A Frequency Counter for the Amateur Station," *QST*, October, 1970, page 15.
2. Kenneth Macleish, W7TX, Henry O. Pattison, W7EFV, Roy C. Hejhall, K7QWR, "The Rec/Counter," *QST*, May, 1971, page 11.
3. Kenneth Macleish, W7TX, Henry O. Pattison, W7EFV, "More on the Rec/Counter" (Technical Correspondence), *QST*, June, 1971, page 38.
4. Douglas A. Blakeslee, W1KLLK, "The Racal RA-71," *QST*, October, 1965, page 52.
5. Edward M. Noll, W3FQJ, "Amateur Applications for WWV." *ham radio*, January, 1972, page 53.

ham radio

Everything you always wanted in keyers and QRP equipment.

■ POWER-MITES

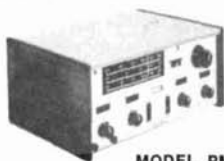

MODEL PM2B

MODEL PM2B. Popular two watt CW transceiver. Operates on 80-40-20 meters. Side-tone. Lantern battery or 12 VDC power source. Size 10 $\frac{3}{8}$ " W X 4 $\frac{1}{2}$ " H X 6 $\frac{1}{2}$ " D. Weight 2 $\frac{3}{4}$ lbs.

Price \$64.95.

MODEL PM3A. Advanced 5 watt CW transceiver. Operates on 40-20 meters. Side-tone. Push pull final. Pi Network. Break-in keying. Size 10 $\frac{3}{8}$ " W X 4 $\frac{1}{2}$ " H X 6 $\frac{1}{2}$ " D. Weight 3 lbs.

Price \$79.95.

■ ANTENNA TUNER

MODEL AC5. Matches 52 ohm output of Power-Mites to open wire on random length antennas. Maximum power 10 watts. Size 4" W X 2" H X 4" D. Weight 1 lb. 4 oz.

Price \$8.95.

■ SWR BRIDGE



AC4

MODEL AC4. Favorite for QRP. Measures from $\frac{1}{4}$ watt to 200 watts. Size 4" W X 2" H X 4" D. Weight 1 lb. 4 oz.

Price \$14.95.

■ SIGNALIZER



S20

MODEL S20. Complete audio and speaker system for receivers/transceivers. Plugs into headphone jack. Provides maximum AGC to keep all signals constant level. Front panel headphone jack. Size 8 $\frac{1}{4}$ " W X 4 $\frac{1}{2}$ " H X 6 $\frac{1}{2}$ " D. Weight 3 $\frac{1}{2}$ lbs.

Price \$39.95.

MODEL S30. Similar to S20 but has built in FR4 CW filter; switchable. Size 8 $\frac{1}{4}$ " W X 4 $\frac{1}{2}$ " H X 6 $\frac{1}{2}$ " D. Weight 4 lbs.

Price \$49.95.

Argonaut



The Argonaut is for every ham. A transceiver that operates on an AC pack or lantern battery. Covers Amateur bands 80-10, SSB and CW.

Completely solid state. Permeability tuning. Less than 100 Hz drift. $\frac{1}{2}$ uv sensitivity. 9 MHz crystal filter. 2.5 kHz bandwidth. 1.7 shape factor. Amateur bands 3-30 MHz. AGC. Speaker, SWR bridge, S-meter built-in. Instant CW break-in. Side-tone. Plug-in circuit boards. Selects normal side band, reversible. One control tune-up. 50-75 ohm push-pull output. Direct frequency read out.

Argonaut price	\$288.00
Power supply	\$24.95
Microphone	\$17.00

■ KEYERS AND KEYSER PADDLES



KR40

MODEL KR40. Squeeze keyer. Iambic sequence. Full memories. Variable weighting. With dual paddles. Speeds from 6-60 wpm. 115 volt AC operation. Side tone. Size 4 $\frac{3}{4}$ " W X 2 $\frac{1}{2}$ " H X 8" D. Weight 4 lbs.

Price \$89.95.

MODEL KR20. Keyer. Self-completing. On/off weighting. With dual paddles. Speed 6-60 wpm. Monitor side tone. 115 V AC operation. Size 4 $\frac{3}{4}$ " W X 2 $\frac{1}{2}$ " H X 8" D. Weight 4 lbs.

Price \$59.95.



KR5

MODEL KR5. Keyer. Self-completing. Optimum weighting. Single paddle. Speed 6-60 wpm. Operates from 6 or 12 volts DC. Size 4" W X 2" H X 6" D. Weight 1 lb. 6 oz.

Price \$34.95.

MODEL KR1. Paddles as used in KR40 and KR20. Mounted in formed aluminum case. Size 4 $\frac{1}{4}$ " W X 2" H X 6" D. Weight 1 lb.

Price \$18.95.

MODEL KR2. Paddle as used in KR5. Mounted in formed aluminum case. Size 4 $\frac{1}{4}$ " W X 2" H X 6" D. Weight 1 $\frac{1}{2}$ lbs.

Price \$12.95.

Ask your TEN-TEC dealer to show you our complete line. If there is no dealer in your area, send your order direct. Include \$2.00 shipping for each Argonaut, all other items shipped postpaid.



Dept. W-2

TEN-TEC, INC.

Highway 411 East □ Sevierville, Tennessee 37862

audio-actuated in-line squelch... the squelcher

A new twist
to an old idea
that can be added
to any receiver
in one evening
without
major modification

While the **avc-operated squelch** has been around a long time, there's something to be said for the audio-actuated in-line squelch, and the Squelcher is the last word in in-line squelch circuits! Traditionally, the squelch circuit has been used to silence receivers during inactive periods. The Squelcher has other important functions other than receiver muting during periods of inactivity. For example, the Squelcher makes possible clear channel operation even in 20 dB of noise, if the received signal is at least 5 dB above

the noise level. There will be some noise under the received signal, but the ear, an amplitude-type detector, hears the audio output of the receiver go from a zero level during the squelched period to a maximum during transmission; the effect is to create an auditory illusion. The desired received signal seems much stronger than it actually is. In short, the Squelcher can mask a great deal of background noise between words and sentences that contributes to operator fatigue during long operating periods.

The Squelcher is basically an audio-actuated switch that closes a set of relay contacts in series with the speaker each time the receiver output exceeds a pre-set level. As long as the audio level stays above the pre-set threshold, the relay stays closed, keeping the speaker connected to the receiver output. However, when the receiver output falls below the pre-set level, and after a time delay determined by the time constant of a capacitor (C3), the relay contacts open and silence the speaker.

While most squelch circuits rely on a change in avc voltage to achieve squelch action, the Squelcher operates on the change in the audio output of the receiver. The addition of the agc squelch circuit to an existing receiver can be a custom project with as many variations in circuitry as there are different makes of receivers. The Squelcher, on the other hand, can be added to any existing

Gene F. Greneker, K4MOG, 2546 Wilson Woods Drive, Decatur, Georgia 30033

receiver with an output impedance of 4 or 8 ohms and will achieve the same results.

theory

The Squelcher consists of an internal rectifier bridge that converts 6.3 Vac to dc to operate an amplifier stage and a relay driver stage. Diodes CR1, CR2, CR3 and CR4 comprise a standard full-wave bridge rectifier whose output is filtered by capacitor C4. Resistor R6 serves to limit the current flowing through zener diode (CR7) to a bias point that allows the zener to regulate the voltage to 8.2 volts regardless of load.

Transformer T1's primary is connected directly across the receiver output. During periods when the threshold is too low to allow the receiver output to be switched to the speaker, T1 presents a constant 8-ohm load to the receiver. When the output rises to a level sufficient to switch in the speaker, the low-impedance input of T1 keeps the reference level to the amplifier fairly constant regardless of the additional speaker load.

The secondary of T1 is fed into the high side of the potentiometer (R7) which serves as the squelch or threshold-level control. Capacitor C1 passes the ac component into the 2N2925 amplifier stage, which amplifies both positive and negative peaks in linear fashion. The output of the transistor amplifier stage (Q1) is coupled through C2 to a negative peak clipper (CR1) and a half wave rectifier (CR2) whose output is averaged

by capacitor C3. The value of C3 determines the time constant or hold-in time of the relay driver circuit. For shorter hold times, decrease the value of C3. The voltage stored by C3 is applied to the base of transistor Q2 through resistor R5. When the voltage applied to the base of Q2 reaches a sufficient level to cause conduction, relay K1 closes, connecting the speaker to the receiver.

Switch S1 is mounted on the threshold potentiometer. In the off position, S1 shorts the open contacts of K1 connecting the speaker directly to the output of the receiver, taking the squelch circuit completely out of the circuit. This action also opens the 6.3 Vac input line, disconnecting the Squelcher from the power supply.


construction

The parts layout is not critical. However, for ease in assembly, it may be best to make your own printed-circuit board or to purchase the ready-made board.* If you use the pc board, parts should be mounted as shown in the photograph, with the exception of capacitor C4 and potentiometer 1 — these will be mounted later. When all the other parts have been mounted, check to insure all leads were clipped close to the foil on the pc board.


Mount the potentiometer first. The three leads of the potentiometer are designed to be soldered directly to the board. Solder the three leads of the potentiometer to the foil side of the board and trim any excess leads. Make sure the potentiometer is *flush against the component side of the board*, or the board may crack during final tightening of the mounting nuts. Next, solder 1½-inch pieces of wire to the switch portion of the potentiometer.

When installing capacitor C4, be care-

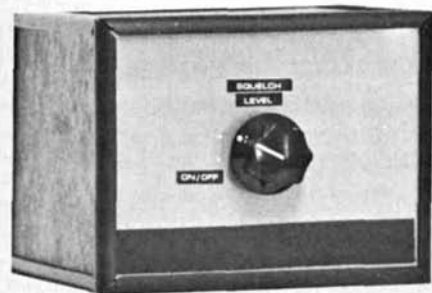*All components, including cut and drilled printed-circuit board, pre-drilled Eico Flexi-Cab cabinet, and the input transformer are available for \$19.95 from H & L Electronics, Box 9707, Atlanta, Georgia 30319. The printed-circuit board alone is \$2.95, and the transformer is \$1.00 from H & L.



Front view of the Squelcher.

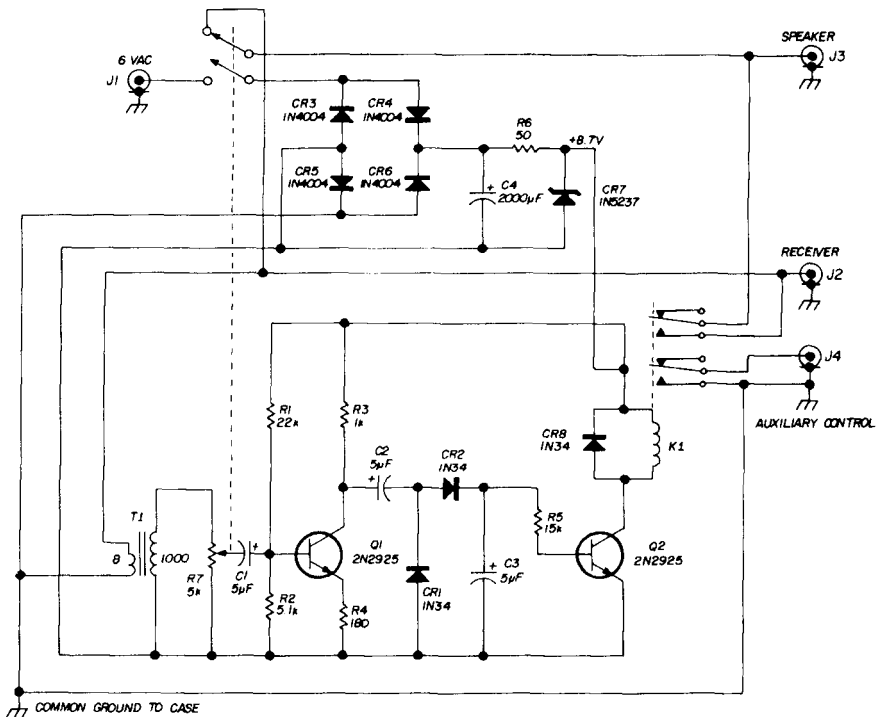

K1 dpdt reed relay, 12 Vdc coil (Allied Control RF-2A)

R7 5k, 1/2 W potentiometer with S1 attached (Clarostat A42-5000K-6140 with type 21 switch attached)

fig. 1. Schematic diagram of the Squelcher. All capacitors are rated at 25 Vdc, all resistors are half watt.

S1 two, spst switches, one on and one off per throw (Clarostat type 21 switch attached to R7)

ful to observe the correct polarity. The positive lead goes to the relay side of the board.


When mounting the potentiometer and pc board inside a cabinet, use two lock nuts as spacers to prevent the cabinet from shorting the foil side of the printed circuit. I housed my Squelcher in a 4 1/4 x 3 3/4-inch box with the potentiometer mounted in a 7/16-inch hole in the center of the front panel. Construction is completed with the wiring from the pc board to four phono jacks mounted on the back panel. These jacks provide for all interconnections between the Squelcher and the rest of your station.

installation

Two pairs of wires must be brought

out of the receiver. Find a pilot light or other source of 6.3 Vac and attach the leads to a phono plug to mate with J1. Be certain to connect the ground side of the plug to a good receiver ground. If your receiver filaments are 12 volts, change R6 to 330 ohms.

Next, the output leads that normally go to the speaker should be connected to a phono plug to mate with J2. The station speaker should be connected to J3 through another mating phono plug. I recommend using shielded cable for these connections to insure a good common ground throughout and to minimize hum pickup. Through J4, you can connect any other unit which you want to control with the normally open contacts of the relay.

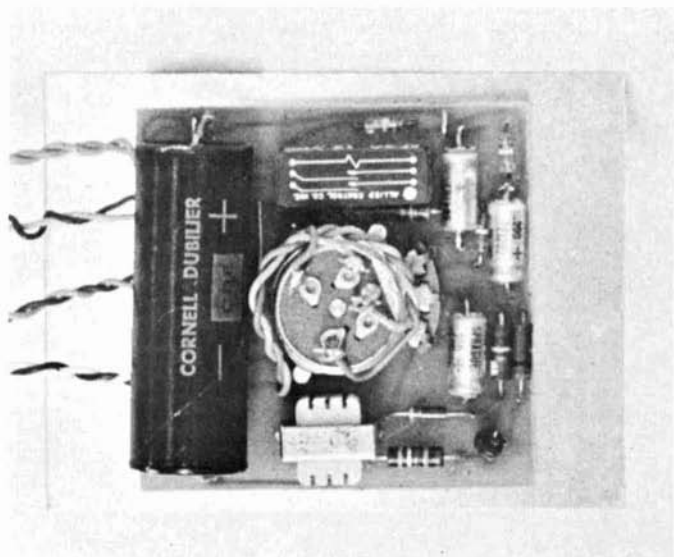

The pc board wiring. The potentiometer must be mounted flush against the printed-circuit board.

With the Squelcher connected to your receiver and speaker turn the receiver on. Assuming there is no problem, turn the volume up to a point just above the level that is usually considered comfortable.

Next, turn the Squelcher threshold control clockwise just past the point where the switch clicks on. Tune to a quiet frequency and advance the threshold control until the speaker becomes silent. At this point the receiver is squelched. Tune across the band until a signal shows on the S meter, simultaneously the audio should be heard in the speaker. By varying the setting of the threshold control, the minimum level required to break the squelch can be controlled quite accurately.

additional hints

Receivers having agc circuits with a dynamic range of 30 or 40 dB will cause some problems with the Squelcher unless the rf gain control is turned down to a point where the agc action is not noticeable. Otherwise, a signal reading S-9 on the S meter will have the same relative audio output level as a 40 dB over 9 signal. Since the Squelcher detects audio rather than signal level, the audio must be relative to signal strength. Therefore, by

setting the receiver audio output for a comfortable level and retarding the rf gain control, the Squelcher will operate dependably.

The optional contacts of the relay will find numerous uses. By changing capacitor C3 to a lower value the reed relay can be driven by moderate to fast CW. By connecting the spare contacts of K1 to a code practice oscillator it is possible to obtain QRM-free copy on strong CW signals, by keying the oscillator in repeater fashion. No doubt, other uses have already come to mind.

After some playing around with the Squelcher, it will be noticed that extremely fine levels in signal change can be detected. As a bonus, operator fatigue will decrease due to squelched noise and interference during lulls in the contact.

Because the Squelcher is somewhat audio-level dependent, it will take a few minutes to determine the proper balance between the receiver audio and rf gain controls. Once these are set, the squelch level will be determined by the threshold control. With time, the Squelcher will become an interference rejection tool for your receiver equal to the Q multiplier, crystal filter and noise limiter.

ham radio



1

6

7

8

9

10

Is your amateur station a serviced station?



When signal/one engineers set out to design the most advanced ham rig ever, they knew they were getting into trouble. Because they wanted to build a rig that incorporated every feature the serious amateur would want. They knew that would take a lot of circuitry and a lot of innovation. With that comes bugs. And they had their share of them. We're not ashamed to tell you some of the earlier models literally went up in smoke. But . . . live and learn. We went back in and got the bugs out. What we've ended up with is the world's most sophisticated rig. And it works! Fantastically so.

Ah . . . you're thinking that anything so complicated is someday going to need service. And we know that, too. That's why we maintain a factory-only service center. With fast turn-around time, and the job's always done right, with original factory replacement parts.


You pay \$2,195 for the CX7A. It's worth it, as you'll discover when you see it at your signal/one dealer's. It serves every purpose an amateur could dream of. Including reliability. And service you can count on.

Features:

1. Instant band change without tuneup.
2. Instantaneous digital frequency readout.
3. IF shift control.
4. Built-in pre-IF noise blander.
5. All popular modes of operation.
6. Transceiver-plus-receiver operation.
7. Hang AGC levels out wide swings in signal strength.
8. All ham bands from 160 through 10 meters.
9. RF envelope clipping provides matchless talk power.
0. Metering of all critical functions.

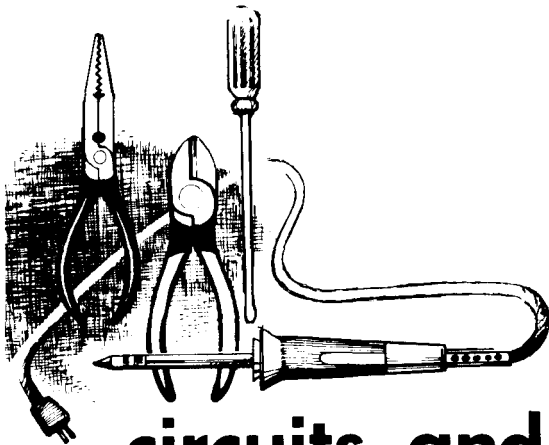 **signal/one**

a subsidiary of
Computer Measurements, Inc.
1645 West 135th Street
Gardena, California 90249
Phone: (213) 532-9752



circuits and techniques

ed noll, W3FQJ

digital integrated circuits

One of the exciting side effects of computer technology has been the involvement of a different mathematical form in electronic circuit design and application. The versatility of the true-false (1,0) concept is phenomenal.

Last month we considered inverter, OR, AND, NAND and NOR logic functions and circuits. The basic Boolean expressions for these functions are:

OR	$A+B$
AND	$A \cdot B$
NAND	$\overline{A \cdot B}$
NOR	$\overline{A+B}$

There are quite a number of Boolean theorems and relations. One of the most important is known as the DeMorgan theorem. In practice this theorem proves the validity of a very common form of digital integrated circuit known as the

NAND gate. This one type of integrated circuit includes NAND, AND and OR functions. Furthermore, some typical negative-logic NAND gates can also be operated as positive-logic NOR gates. Thus a single digital IC can provide a number of logic functions.

Recall the NAND circuit symbol and truth chart, fig. 1. When both A and B are true, the output is false. However the signal is logically inverted as indicated by the line above the expression in the NAND function equation:

$$X = \overline{A \cdot B}$$

The NAND function can also be written:

$$X = \overline{A} + \overline{B}$$

It is DeMorgan's theorem that equates these two relations.

$$X = \overline{A \cdot B} = \overline{\overline{\overline{A} + \overline{B}}}$$

There are several ways of proving DeMorgan's theorem. Perhaps the most

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

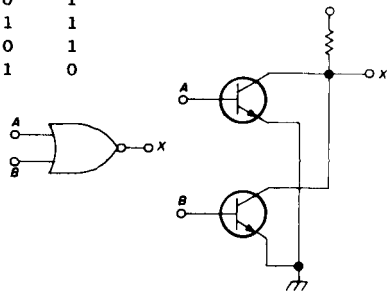


fig. 1. Basic NAND function using negative logic.

obvious uses the truth tables in **fig. 1**. First we set down the truth table of an OR function. However, the relationship we are trying to prove indicates that the A and B terms have been logically inverted as per the second truth chart. Next set down the truth chart for the NAND function. Note that the output values are identical and therefore:

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

You can go a step further and invert the logic of the output of the NAND circuit, **fig. 2**. The fourth chart shows this inversion. Note that the output expression now contains double lines above A and B. These indicate that the signals have been inverted twice. This restores the original logic just as any signal twice inverted is returned to the original polarity. Most important, note that the output of the inversion corresponds to the out-

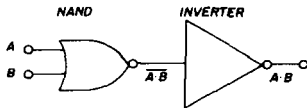


fig. 2. NAND to AND inversion.

put of an AND circuit. It is readily understandable how a single digital IC can be constructed to include a variety of logic possibilities.

A NOR gate, like a NAND gate, can also provide the AND and OR functions. The addition of an inverter (NOT circuit), permits an OR output. The first truth chart of **table 2** is that of an AND function. An inversion of its logic produces the logic of chart 2. Note that the output is the same as that of a NOR function circuit, chart 3. This proves the validity of the DeMorgan theorem and the following equality can be stated:

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

If the output of a NOR circuit is followed with an inverter, you obtain the results shown in the fourth chart. Note that this corresponds to the output of an OR truth chart.

table 1. Validity of DeMorgan's theorem and inversion of NAND to AND function.

OR			OR INVERTED		
A	B	A+B	A	B	A+B
0	0	0	1	1	1
0	1	1	1	0	1
1	0	1	0	1	1
1	1	1	0	0	0
(1)			(2)		

NAND			NAND INVERTED		
A	B	A·B	A·B	A·B	A·B
0	0	1	1		0
0	1	1	1	inverted	AND out
1	0	1	1		0
1	1	0	0		1
A·B = A+B (3)			A·B = A+B (4)		

In fact, suitable circuits based on the truths of the various Boolean theorems can permit a variety of logic functions. You can use the circuit of **fig. 3** as an example. Basically, it is a NAND configuration. Base biasing (resistors R1, R2 and R3) is such that the transistor conducts when logic 1 (positive logic) voltage is applied to both inputs. Under this condition the output will be logic 0. When logic 0 voltage is applied to both inputs or to either input, the transistor is turned off, producing logic 1 voltage at the output. Tied in with a follow-up

table 2. Validity of DeMorgan's theorem and inversion to OR function.

AND			AND INVERTED		
A	B	A·B	A	B	A·B
0	0	0	1	1	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	1	0	0	0
(1)			(2)		

NOR			NOR INVERTED		
A	B	A+B	A+B	A+B	A+B
0	0	1	1		0 OR
0	1	0	0	inverted	1 out
1	0	0	0		1
1	1	0	0		1
A+B = A·B (3)			A+B = A+B (4)		

inverter (NOT circuit), the arrangement can be made to operate as an AND circuit.

The same circuit functions as a NOR gate by changing the polarization of the

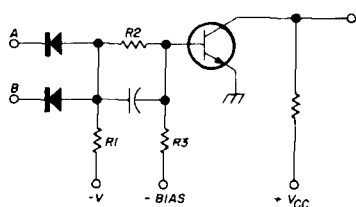


fig. 3. Basic NAND gate.

input diodes and changing the bias level established by the base voltage-divider resistors. In this case, when either or both inputs are at logic 1 voltage, the transistor is turned on to produce a 0 logic output. With both inputs at logic 0, the output is logic 1 because the transistor remains cut off. A follow-up inverter is used to establish an OR function operation.

standard integrated circuits

Digital integrated circuits are found in a number of standardized configurations. The transistor-transistor logic combinations, abbreviated TTL or T^2L , are very common. A basic circuit, fig. 4, is a pair of direct-coupled transistors. The input transistor has a dual-emitter, a separate one for each input gate. This circuit operates as a NAND gate.

When logic 0 voltage is present on either or both input gates, the corresponding emitter-base diodes are forward biased. However, no significant collector current exists because of the reverse biasing of the base-emitter of transistor Q2. Stated another way, the saturation current of transistor Q1 is not high enough to forward bias transistor Q2. Therefore transistor Q2 output is logic 1 (positive logic).

The emitter-base diodes of Q1 are shut off when logic 1 voltage is applied to both. In so doing, the collector junction is forward biased. Base current magnitude and direction in Q1 is now such that the

base of transistor Q2 is forward biased. Transistor Q2 is now turned on and the collector voltage drops to the 0 logic level.

A complete diagram of an integrated circuit NAND gate is shown in fig. 5. It is referred to as a dual 4-input positive NAND gate. Note that two circuits similar to that of fig. 4 are included in the chip. There are four NOR input gates instead of two. A more elaborate output circuit is included to provide higher output to low-impedance loads and to obtain the capability of driving up to 30 loads (high fanout).

I mentioned previously that the AND function can be obtained by the addition of an inverter after the NAND gate. It should also be mentioned that a NOR function can be obtained by cascading two NAND gates. By including multiple gates on an IC chip, any number of common and special logic functions can be established by appropriate external wiring.

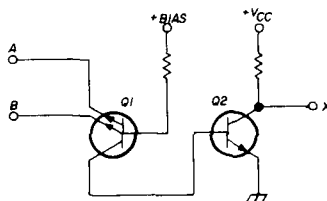


fig. 4. Basic TTL NAND gate.

The diode-transistor logic (DTL) is also common and similar to the TTL ICs. The DTLs are not as adaptable to complex functions and do not have the speed and capability of driving low-impedance loads as the TTLs. The input NOR switches are diodes, fig. 6. They are followed by an inverter stage. When both inputs are at logic 1 positive voltage, the diodes are reverse biased. The series or offset diode, however, is forward biased. Current holds the transistor in saturation and its low collector voltage corresponds to logic 0.

The application of logic 0 to any one

or both of the input diodes results in conduction, dropping the voltage at the anode of the series diode to a level that

tor-transistor logic (RCTL) types.

An increasingly popular family is the emitter-coupled logic (ECL) digital ICs.

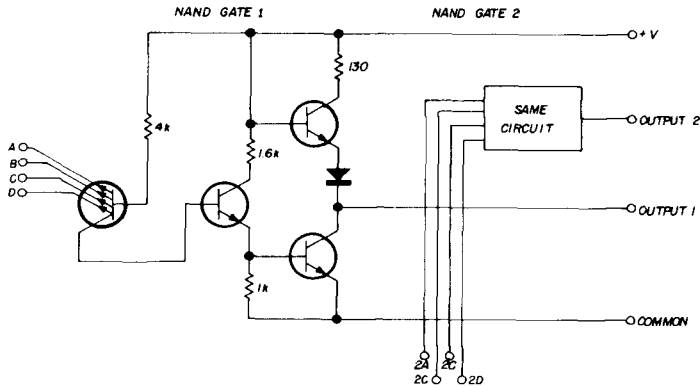


fig. 5. Dual 4-input positive NAND gate (Texas Instruments SN7420).

reduces the base current of the transistor to cutoff. Therefore, positive logic 1 output voltage is present at the collector.

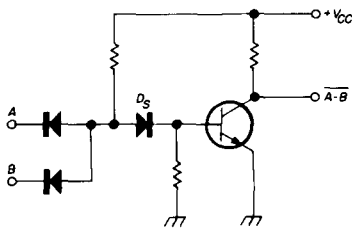


fig. 6. Basic DTL NAND circuit.

A similar family with higher supply voltages and greater power dissipation are known as the high-threshold logic (HTL) group.

Some of the very first IC types were resistor-transistor logic (RTL), fig. 7. This is a basic NOR circuit. These circuits are limited in switching speed and fanout capability. Though economical and adaptable to numerous applications, they have relatively poor noise immunity. Capacitors across the input resistors convert circuits to higher-speed resistor-capaci-

These provide the highest speed of all and include such favorable characteristics as low output impedance, high fanout and acceptable noise immunity. The high speed of operation is a result of limited voltage swing in a manner of operation similar to linear types and the non-saturated operation of transistors. These types perform up into the hundreds of megahertz.

In a typical NOR circuit, fig. 8, the emitters connect to a common emitter resistor. This connection prevents saturated operation. Transistor Q4 is used to set the threshold voltage at the input. A

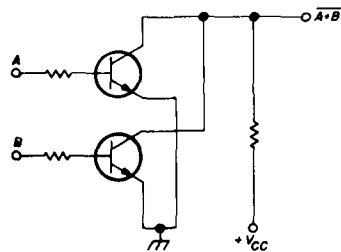


fig. 7. Basic RTL NOR circuit.

succeeding follow-up emitter follower insures low output impedance and good fanout.

The use of metal-oxide semiconductor field-effect transistors (mosfets) in digital integrated circuits adapts them to elaborate, multi-stage and highly-repetitive

No doubt many other hams use similar setups.

It occurred to me that the receiver vfo should be capable of serving as a tunable

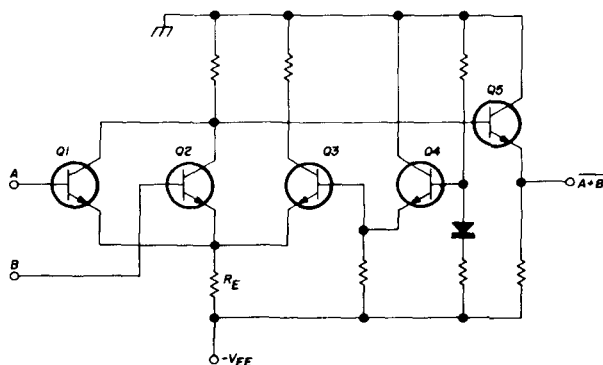


fig. 8. Basic ECL NOR gate.

operations. Complex logic circuits can be incorporated into tiny chips. In a basic NAND circuit, fig. 9, negative voltage establishes logic 1 at the input, and both input gates conduct. The output voltage switches to the logic 0 value. When either or both of the input gates are set to 0 logic voltage, there is an open in the source circuit of the output mosfet and the output is at logic 1 level.

schedule

The digital IC series will be interrupted next month but will resume the following month with discussions of flip-flops and frequency counters. Instructions will be given on how to set up a small experiment board so you can watch them operate on an oscilloscope and hear them on your receiver. Next month's column will be devoted to antennas to complement *ham radio's* popular antenna issue.

available vfo signal

Here is part of a note from James W. Harrison, Jr., WB4TEX: "... I use a Heath SB300 and SB400 cabled up for transceiver. Under this arrangement, the receiver feeds its 5- to 5.5-MHz vfo output into the transmitter for frequency selecting, both for receive and transmit.

oscillator for a QRP transmitter, if such a transmitter included a proper mixer. It appears to me that such an arrangement would make a dandy QRP transceiver setup. I should imagine there are numerous integrated-circuit units capable of handling these functions as part of a QRP CW transmitter . . ."

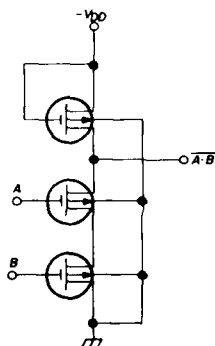


fig. 9. Basic mosfet NAND gate.

Here is a challenge for some of you QRP buffs. Is this not a good opportunity to come up with a vfo-controlled multi-band QRP transmitter that you can operate transceive with your big receiver? Thank you, Jim.

ham radio



The crowd pleaser

Working portable is never more enjoyable than when you're working with Yaesu's incomparable FT-101. It's a 30-pound power package, with 260 watts PEP SSB, 180 watts CW and 80 watts AM input power. Plus 0.3 microvolts receiving sensitivity, with a 10 db signal-to noise ratio.

The FT-101 includes a noise blander. And built-in 117 VAC, 12 VDC power supplies. As well as built-in VOX, 25 KHz and 100 KHz calibrators, the WWV 10 MHz band and a high-Q permeability tuned RF stage. Plus a ± 5 KHz clarifier.

The FT-101 is all solid-state, except for finals and driver. It's equally at home

in your shack or on a mountain-top. Or on a Sunday afternoon outing.

We'll be glad to send you a detailed brochure on the FT-101. Or, for only \$559.95, we'll send you the rig.

You'll have a crowd pleaser on your hands. Including the crowd of hams out there who'll copy you loud and clear.



SPECTRONICS WEST

Dept. Q, 1491 E. 28th, Signal Hill, Ca. 90806 / (213) 426-2593

SPECTRONICS EAST

Dept. Q, Box 1457, Stow, Ohio 44224 / (216) 923-4567

Please send detailed information on all Yaesu products.

Enclosed find \$ _____

Please send model(s) _____

Name _____

Address _____

City _____ State _____ Zip _____

All prices F.O.B. Signal Hill, Ca.

Master Charge and BankAmericard accepted. "H4"

beam antenna headings

An inexpensive
guide to accurate
antenna beaming
for within
the United States
and around
the world

Have you ever wondered what direction your beam *really* should be turned to work that elusive station? Have you ever been in a 3-way contact and wondered what heading would catch the other stations on some decent compromise heading? Information is available for beam headings from the central part of the U. S. A. (usually Chicago), and at times from other major cities. This may not help you to any reasonable extent, and the information is pretty much

worthless for knowing where to set the antenna for stations here in the U. S. A.

I have wanted accurate beam heading information as much as anybody else, and went so far as to laboriously plot a number of representative cities throughout the U. S. A. on an aeronautical chart. This was quite helpful, and I used the list frequently. I am only a few miles from San Francisco, so the list of foreign beam headings published in the *Foreign Callbook* for that city worked well for me.

While developing a computer-controlled program for aeronautical inertial navigation systems, I decided to use that information to provide a supplementary beam heading program. This is now available, and comes in two lists — the first has 90 domestic cities at well-known places in the United States, the second list has 309 entries of various foreign countries and 10 U. S. cities representing each call district. Thus the program would be useful to stations outside the United States.

The program lists the true heading, magnetic heading, distance in kilometers and distance in statute miles. It thus helps give some indication if the long path is really that much further or not. It is useful to know just how far the other station really is, as it helps give an additional feeling of knowing a little more about the person you are talking with. To further help locate the station, the continent to which it is assigned is listed. If the country is fairly large or has

Irvin M. Hoff, W6FFC, 12130 Foothill Lane, Los Altos Hills, California 94022

a best-known city, that is listed also.

Even at a normal computer terminal speed, it takes one hour to print the entire listing of domestic cities and foreign countries. As most computer time costs \$20 per hour, there is no way the typical amateur could normally afford to pay for such a customized and accurate print-out. However, I made arrangements to use a high-speed printer, and I have written a fully automatic program. This service is offered to anybody interested for \$2 per copy plus 25c postage and handling. Since this would give exact headings from your exact location, this should be of unusual benefit to those interested at a price small enough any amateur could afford. Certainly no profit will be made on this, but so much time has already gone into writing the program and inserting all the data needed, it seemed a shame not to make this information generally available.

I can insert latitude and longitude just

as accurately as you can supply it. I already have information on some 30,000 countries, states, cities and towns in the world, but I can just as easily insert the exact coordinates of your very home, if you take the time to find out what they are.

Here is the information I need to put into the computer for your particular printout:

1. Latitude (degrees, minutes, seconds).
2. Longitude (degrees, minutes, seconds).
3. Variation in degrees and whether East or West.
4. What name you wish to appear for location.

You will note from the example for Greenville, the name "From: Greenville, New Hampshire" appears at the top of each page. In my case, I use the coordinates of my house (off the deed to the

FROM: GREENVILLE, NEW HAMPSHIRE					
LOCATION	DEG. TRUE	DEG. MAGNETIC	DIST. STAT.	DIST. KILOMTR.	DIST. NAUT.
45. MONT., GREAT FALLS	292	308	1902	3062	1652
46. N.CAR., ASHEVILLE	229	245	802	1290	696
47. N.DAK., BISMARCK	289	305	1415	2278	1229
48. N.DAK., FARGO	289	305	1228	1976	1066
49. N.J., NEWARK	211	227	239	385	208
50. N.J., TRENTON	213	229	286	460	248
51. N.MEX., ALBUQUERQUE	264	280	1938	3118	1682
52. N.Y., ALBANY	235	251	125	201	109
53. N.Y., BUFFALO	263	279	358	576	311
54. N.Y., NEW YORK CITY	208	224	239	384	207
55. N.Y., ROCHESTER	265	281	291	468	252
56. NEBR., OMAHA	271	287	1236	1989	1073
57. NEV., LAS VEGAS	272	288	2326	3743	2020
58. NEV., RENO	78	94	2657	4276	2307
59. OHIO, CINCINNATI	248	264	729	1172	633
60. OHIO, CLEVELAND	256	272	525	845	456
61. OHIO, COLUMBUS	250	266	630	1013	547
62. OHIO, TOLEDO	261	277	613	987	533
63. OKLA., OKLAHOMA CITY	256	272	1476	2375	1282
64. ONT., OTTAWA	303	319	224	361	195
65. ONT., TORONTO	272	288	378	608	328
66. ORE., PORTLAND	291	307	2509	4037	2178
67. PA., HARRISBURG	229	245	352	567	306
68. PA., PHILADELPHIA	215	231	311	501	270

fig. 1. An excerpt from the U. S. antenna headings chart plotted on the HAM RADIO magazine office in Greenville, New Hampshire. Antennas can be accurately oriented with an ordinary compass by the magnetic degrees heading.

FROM: GREENVILLE, NEW HAMPSHIRE

B E A M H E A D I N G S A N D D I S T A N C E S

CALL	LOCATION	DEG. TRUE	DEG. MAGNETIC	DIST. STAT.	DIST. KILMTR.
1. 3A	MONTE CARLO, MONACO (E)	60	76	3808	6128
2. 3VB	TUNIS, TUNISIA (AF)	65	81	4183	6732
3. 3W8	SAIGON, VIETNAM (A)	2	18	8670	13953
4. 4S7	COLOMBO, CEYLON (A)	34	50	8513	13700
5. 4U1	UN, GENEVA, SWITZERLAND (E)	58	74	3662	5893
6. 4U8	UN, TURIN, ITALY (E)	59	75	3759	6050
7. 4W1	SANA, YEMEN (A)	61	77	6676	10744
8. 4X4	TEL AVIV, ISRAEL (A)	56	72	5454	8777
9. 4Z4	TEL AVIV, ISRAEL (A)	56	72	5454	8777
10. 5A	TRIPOLI, LIBYA (AF)	68	84	4471	7195
11. 5B4	NICOSIA, CYPRUS (A)	54	70	5245	8441
12. 5H3	DAR ES SALAAM, TANZANIA (AF)	80	96	7598	12227

fig. 2. An excerpt from the DX beam heading chart.

house, by the way) and so on mine it says: "From: Hoff House, California." I could have said "From: Los Altos Hills, California" just as easily.

You can find your latitude, longitude and magnetic variation from your property deed (the local city hall can look it up for you), from the county surveyor who has records of all this information, or there are several other things you can do. If you are reasonably close at all to any airport or commercial radio or tv transmitter, they always know exactly what the latitude and longitude are plus the magnetic variation in that area.

You can estimate from a road map your location with respect to that landmark. If all else fails, give the name of your community, and if it is less than 10,000 population, give the name of some larger nearby community with your approximate distance and direction from there. Again, I can provide you with information just as accurate as you give me to work with.

This should give you all the information you need to get your personalized beam heading printout. Include a self-addressed stamped envelope if you ask any questions that need to be answered, as the computer is located in Texas and

all the actual printouts will be mailed from there. Also, I may find this service is too overwhelming to continue, or too expensive to offer for this nominal fee, and may wish to return your money. In any event it shall only be possible to crank out 15-20 of these in one evening, probably, so be patient on getting your copy.

If ordering, provide the following:

1. Latitude.
2. Longitude.
3. Magnetic variation (if you can't find this, I know already for anywhere in the USA to the closest 1°).
4. Name of location you wish to appear.
5. SASE for possible return of money.
6. Include \$2 for the printout plus 25c mailing.
7. If sending from outside the United States, mailing costs would be for 2.5 ounces.

Mail to: Irvin M. Hoff

Attn: Beam

12130 Foothill Lane

Los Altos Hills, Calif. 94022

ham radio

The voice of



is heard around the world



Here's why Thunderbirds outperform all other tri-banders:



- **Thunderbird's "Hy-Q" traps** provide separate traps for each band. "Hy-Q" traps are electronically tuned at the factory to perform better at any frequency in the band—either phone or CW. **And** you can tune the antenna, using charts supplied in the manual, to **substantially** outperform any other antennas made.
- **Thunderbird's superior construction** includes a new, cast aluminum, tilt-head universal boom-to-mast bracket that accommodates masts from 1¼" x 2½". Allows easy tilting for installation, maintenance and tuning and provides mast feed-thru for beam stacking.
Taper swaged, slotted tubing on all elements allows easy adjustment and readjustment. Taper swaged to permit larger diameter tubing where it counts! And less wind loading. Full circumference compression clamps are mechanically and electrically superior to self-tapping metal screws.
- **Thunderbird's exclusive Beta Match** achieves balanced input, optimum matching on all 3 bands and provides DC ground to eliminate precipitation static.
- 25 db front-to-back ratio.
- SWR less than 1.5 to 1 on all bands.
- 24-foot boom... none longer in the industry.
- Extra heavy gauge, machine formed, element to boom brackets, with plastic sleeves used only for insulation. Bracket design allows full mechanical support.
- Interlaced, optimum spaced elements for higher gain and better pattern control.
- 3 active elements on 20 and 15 meters. 4 active elements on 10 meters.

New 6-Element Super Thunderbird
Model 389
Suggested retail price, \$179.95

Fabulous 3-Element Thunderbird, Jr.
Model 221
Suggested retail price, \$99.95


Improved 3-Element Thunderbird
Model 388
Suggested retail price, \$144.95

Popular 2-Element Thunderbird
Model 390
Suggested retail price, \$99.95

Buy one today at your favorite Hy-Gain distributor!

HY-GAIN ELECTRONICS CORPORATION

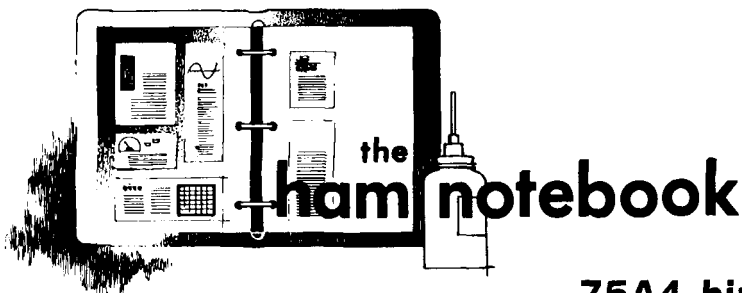P. O. Box 5407-WD, Lincoln, Nebraska 68505



ic power

Too often, when radio amateurs start experimenting with IC packages we stop thinking like amateurs and start thinking by the book. A case in point was my own experience with a dual two-input gate which was used to build a Schmidt trigger. Briefly this is a circuit which will take almost any waveform provided it is above the needed trigger level and convert it into a form which can be used to trigger flip-flops.

The circuit was put together with an input voltage of about three volts, the output on the scope was a very nice square wave. Trying to trigger a series of flip-flops with this output was sheer frustration. Everything was wired properly, the supply voltage was on the money, but the flip-flop triggering was erratic. I finally decided to think like an amateur and measured the *output* of the Schmidt trigger and found that it was about 0.4 volts. I then powered the trigger with my variable voltage supply and found that at six volts dc applied to the IC, the output rose to 0.65 volts and the flip-flops triggered reliably. This circuit has been working very nicely for some months now with six volts, not the 3.6 as recommended. There have been no signs of failing or blowing up. Don't be afraid to think like an amateur!

A. S. Joffe, W3KBM

75A4 hints

To increase the amplitude of the 100 kHz markers on the 75A4, directly substitute a 6BZ6 in place of V1, the 6BA6 calibrator oscillator tube. If a further increase is desired, the oscillator 1-pF coupling capacitor, C5, can be replaced by a 10-pF silver-mica capacitor. The combination of the foregoing will result in a 20-dB calibration signal increase, as read on the S-meter, on the 14 MHz band. This was without any apparent degradation of the frequency stability as read on a General Radio model 1192 frequency counter.

For the convenience of having a front-panel ground of the antenna input circuit for testing, simply bend in the tip of the outside plate on the stator of the antenna trim capacitor, C18. This will short the antenna terminal to ground as the rotor passes over this one point. It means, however, that the trimming capacitor must be rotated from the opposite direction while in use. Full 360° rotation is no longer possible, but this loss is more than justified by the convenience.

M. H. Gonsior, W6VFR

wet basement alarm

Having always been concerned about plumbing leaks in my basement hamshack, I finally whipped up a combination water alarm and shut-off circuit for my well pump. Sensors placed strategically around the basement (near the well pump, washing machine and hot water heater) trigger Q1 into conduction

when a water leak is detected. Q2 is then cut off, releasing the relay which breaks the line to the well pump, preventing the basement from being turned into a swimming pool. When Q2's collector voltage rises, Q1 is latched on via the 470k feedback resistor until the circuit is manually reset. At the same time, Q3 is

actually more than enough to operate the relay.

I found that small pieces of pc board worked well as sensors. I used pieces about 1/2-inch wide and 2-inches long, double sided, with one lead connected to each side.

Al Donkin, W2EMF

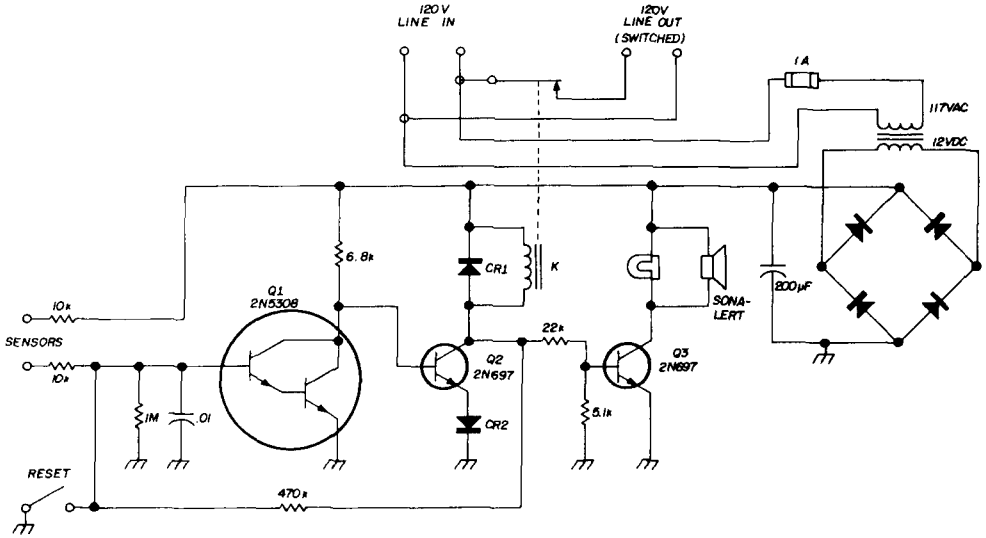


fig. 1. Schematic of the wet basement alarm. The relay is a Magnecraft 88DX3 and the alarm is a Mallory SonaLert.

turned on, sounding the alarm and illuminating an alarm lamp.

Although my installation controls a well pump, a solenoid in the water main supply could be used by the city dweller. Variations on this circuit design may be made to suit the builder's junk box, but a few cautions should be observed. Q1 (2N5308) is a dual transistor internally connected as a Darlington circuit, resulting in high current gain which produces a sensitivity in excess of one megohm for the sensor. The .01-µF capacitor and 10k resistors at the sensor inputs serve as an rf filter to prevent my transmitter from energizing the alarm. The relay I chose is a model with heavy duty (50 A) contacts and a 24-Vdc coil. The power supply produces about 22 volts under load,

s-line spinner knob

S-Line users will find that a small amount of weight added to the receiver tuning knob will materially increase the ease of tuning because of the added inertia of the system. This may be easily accomplished in several ways.

Apply RTV or any other adhesive mixed (such as bathtub caulking) with lead shot, or similar material, to the cavity in the knob. If you put too much weight in the knob, you can remove it with a hobby knife. Alternatively, a metal insert may be fitted into the cavity. For those wishing to splurge, Collins will supply a weighted spinner tuning knob. The part number is 547-1824-003, and the price is ten dollars.

M. H. Gonsior, W6VFR

logic monitor

I call this unit the logic monitor, and it is capable of monitoring logic circuits for dc levels (zero or one logic state) or detecting either positive or negative going pulses. The unit is very simple to make, requiring only a few simple parts and two inexpensive integrated circuits.

The circuit consists basically of an inverter operating into two mono-stable multivibrators. The first monostable operates for positive-going signals and the second one operates for negative-going signals. In detecting negative-going signals, the first monostable acts as an inverter only. Each monostable will operate for its own particular pulse polarity for the length of time set by the R-C time constant of each stage. The time constant of each stage is designed to be long enough to allow the indicator lamp to turn on when a pulse is detected. As the frequency is increased the lamp will glow, but at a reduced brightness.

The logic monitor is invaluable in checking out digital projects, particularly if you do not possess an oscilloscope. This little unit will make short work of checking out a digital keyer, counter or voltmeter. It can determine if flip-flops are toggling or if gates, switching or shift registers are shifting. It is even capable of detecting pulses which many oscilloscopes can not. This is possible since the monitor is designed using medium speed

logic classified as DTL — diode transistor logic — which is capable of faster operation than average oscilloscopes.

I believe the logic monitor is a very worthwhile investment. It can be built as a logic probe by installing the unit in a length of tubular plastic or it may simply be contained in a small aluminum box. The unit is designed for five volts and should not be used for logic levels greater than this.

The indicator lamp can be any five-volt lamp which draws 50 mA or less. The monostables are designed using a MC844 which enables the second monostable to also act as a lamp driver, thus reducing the necessity for an additional transistor.

W. L. McGehee, WA5SAF

vectorbord tool

Reader's of W6CMQ's article in the August, 1971 *ham radio* might be interested in a commercial tool to accomplish a similar task. Designed for isolating terminal points from a surrounding copper-clad surface, Vector offers two tools to do the job. W6CMQ gave many applications for the technique, and Vector points out another — use of inexpensive un-insulated push-in terminals rather than the more expensive insulated standoffs.

The Vector tools are intended for cutting rings through the copper surrounding a prepunched hole. Two sizes are available, the model P116 for 1/4-inch diameter circles and the P116A for 3/16-inch diameter circles. They sell for \$2.32 and \$2.48, respectively. Unlike W6CMQ's version, these commercial tools have a centering pin which limits their use to prepunched or drilled boards. However, to use them with inexpensive, surplus copper-clad board, you would simply have to first drill a small pilot hole for the tool.

The Vector Pad Cutter Tools are available through the Allied catalog and are made to fit most common electric drill chucks.

Douglas Stivison, WA1KWJ

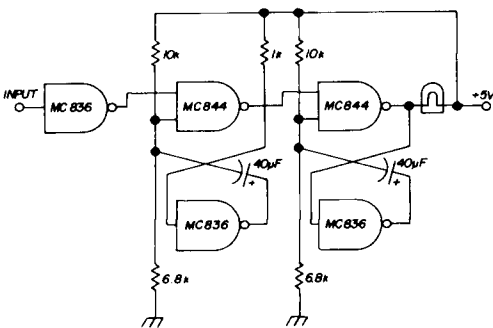


fig. 2. The 844 is a dual 4-input expander with all unused inputs tied to 5 volts with the exception of the expander input.

SBE

feature after feature after feature

Been denying yourself all that great fun so many other amateurs are having with their rock-solid, through-the-repeater contacts?

Delay no longer! Hasten to your SBE dealer. Verify that the brilliant new **SB-144** has more channels---greater power output ---starts your enjoyment **now** by including three sets of crystals on popular repeater frequencies and a high quality, SBE exclusive dynamic microphone **without extra charge**. Add a sizzling, double-conversion receiver and a combo "S" and output meter with big **lighted** scale that also saves your battery by showing when the transceiver is ON.

Confirm the price then make the deal. Lose no time in securing this book-size beauty under your dash with the tilttable mounting bracket supplied. Then, **power on!** ENJOY!

SB-144 2 meter FM TRANSCEIVER



10 WATTS
OUTPUT
ALL
SOLID STATE



12
CHANNELS.
BACK LIGHTED
NUMBERS



SUPPLIED
WITH
3 SETS OF
CRYSTALS



LARGE
SCALE METER,
COMBO,
"S"/OUTPUT




SUPPLIED
WITH
DYNAMIC
MIC.

239⁹⁵

SBE

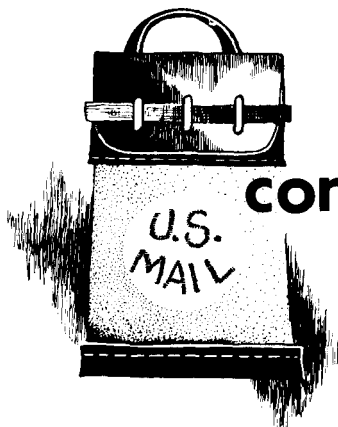LINEAR
SYSTEMS, INC.
220
Airport Blvd.
Watsonville, CA
95076



comments

trapatt diodes

Dear HR:

While employed by Boeing Aircraft during the early months of 1970, I was doing research on Trapatt (for TRAPPED Plasma Avalanche Triggered Transit) and Impatt (for IMPACT Avalanche Transit Time) oscillators and amplifiers. Co-workers and I were using diodes developed in the Boeing Silicon Laboratory.

I discovered that most common silicon signal diodes tried would oscillate in the Trapatt mode. In fact, while not performing as well as Boeing diodes, signal diodes did tend to "drop" into the Trapatt mode with less tuning. A fixture was then designed and built which involved very little metal work and cost. A summary of the results obtained with this circuit is given in table 1.

In all cases pulse lengths were $0.5 \mu\text{sec}$ with a pulse frequency of 1 kHz. The pulse frequency probably could have been increased an order of magnitude: pulse lengths much greater than $1.0 \mu\text{sec}$ would probably result in burnout.

The power output and efficiencies are lower than those listed in "A Second Look" for October 1971. The frequencies are higher and, in most cases, located in amateur bands. My feelings at the time were that CW operation in the Trapatt mode with inexpensive diodes would be most difficult if not impossible. I therefore concentrated my efforts to obtain

operation in the 2.3-GHz band and higher — where pulsed operation is allowed. Even with properly designed diodes, the difficulty in achieving good Trapatt results increases rapidly with frequency. This becomes evident when comparing the results obtained with the same FD600 diode at 2.3 GHz and at 3.34 GHz.

The Impatt pumping frequency of the diodes in this circuit was as high as 11.4 GHz in some cases. The circuit may be used with the signal diodes as an Impatt oscillator merely by using a different tuning technique. The circuit did not appear to be as efficient in the Impatt mode as waveguide designs. Outputs were obtainable, however, from S-band to X-band using this circuit.

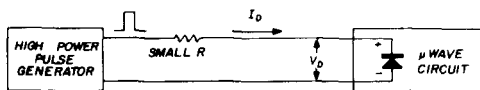


fig. 1. Bias diagram of the Trapatt experimental setup.

Trapatt mode operation is easily identified not only by sudden increase in output power but also by dramatic and exciting increases in diode current and "drop" in diode voltage. A bias diagram will help to describe the phenomenon. The diode is reverse biased.

The pulse amplitude is increased until a certain pulse current is achieved. This varies considerably, but is about 500 mA for most signal diodes. The microwave circuit is then mechanically tuned. When tuning is adjusted such that the diode sees the proper impedances to support the Trapatt mode, the diode voltage V_D will suddenly decrease and the diode current

table 1. Summary of various diode performance in the Trapatt mode.

diode	1N914	1N3064	1N4148	FD333	FD600	FD600
power out (watts)	3	26	8	22	4	1.2
(peak pulse)						
frequency (GHz)	2.25	1.2	1.2	1.7	2.4	3.34
efficiency (percent)	1.1	10.0	8.5	14.5	4.9	1.8
V_B (volts)	120	100	120	200	90	90

suddenly increase. An increase from 200 mA to 1100 mA in diode current was observed with one FD333 diode. More typical values are a voltage decrease and current increase by a factor of two. A sketch of diode voltage, current and rf pulses is shown in fig. 2.

A current and voltage change may occur without a subsequent rf output pulse, a phenomenon peculiar to signal diodes. None of the Boeing avalanche diodes tested displayed this mode. Neither types of diodes oscillated at subharmonic frequencies or at Trapatt efficiencies without the current and voltage change.

It is important that the experimenter include in his data reverse capacitance vs voltage plots for each diode tested. The C vs V curve published by the diode manufacturer may be used but is not as useful since C vs V curves are different from diode to diode. C vs V data should be plotted on log-log paper with capacitance on the dependent axis. The slope characteristics and value should be noted for each diode. Slope is measured on the graph by using a *linear* rule to measure the ratio of rise to run.

An ideal 1- to 3-GHz Trapatt diode

will have a slope value approaching 0.5, the theoretical maximum. Higher breakdown voltages usually signify lower frequency operation. Approximately 100 volts is optimum for 2.0 GHz. A tendency for the slope to decrease suddenly at a reverse voltage 1/3 to 2/3 of V_B is considered desirable; however, the only signal diode found to have this characteristic failed to operate in the Trapatt mode! Many exceptions to these guidelines will be found, but they may serve as a beginning point.

It is my belief that an enterprising amateur, by experimenting with different circuits and inexpensive diodes, could make significant contributions in the field of transit-time microwave devices, even possibly discovering new modes. For example, I am not convinced that all the results obtained in various labs throughout the country qualify to be lumped into one giant Trapatt mode category. It is very likely different labs are calling seemingly similar results operation in the Trapatt mode, when possibly more than one phenomenon is being observed. Why did signal diodes operate with much lower efficiency than Boeing diodes, but tune into the Trapatt mode with greater ease? Why did some 1N4148 diodes with nearly flat C vs V curves operate better than an FD333 with an ideal curve?

I would be most happy to provide assistance to anyone wishing to experiment in this very exciting area. The circuit used in these tests is available to anyone seriously interested in experimentation.

Randall W. Rhea, WA7NLA
920 W. Indian School
Phoenix, Arizona 85013


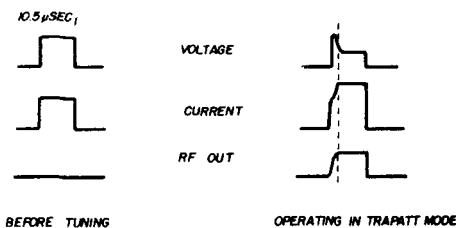


fig. 2. Typical diode voltage, current and rf pulses observed by WA7NLA.

new products

fm adapter for the Communicators

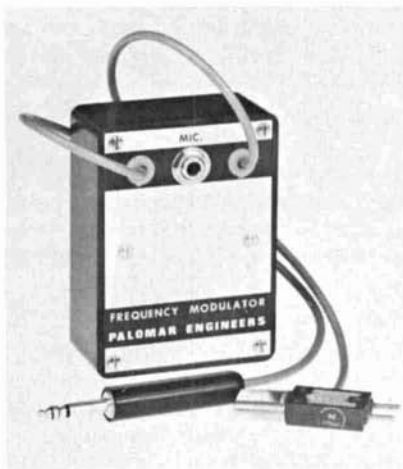

The Gonset Communicators have been among the most popular two-meter transmitter-receivers of all time. But they are a-m rigs and two meters is now heavily fm.

Palomar Engineers' new *frequency modulator* puts the Communicators on fm without any modification or rewiring. The microphone plugs into the *frequency modulator*. One of the cables coming out of the *modulator* plugs into the Communicator's microphone jack and carries the push-to-talk line, but no audio. A second cable has the crystal plug. It plugs into any one of the Communicator crystal sockets and the crystal plugs into it. A variable capacitance diode in the crystal plug frequency modulates the crystal and the

frequency multipliers in the Communicator increase the deviation to about 8.5 kHz at the output frequency.

The *frequency modulator* works with the Communicator I, II, III, IV and GC-105. There are no tuned circuits in the *modulator* so operation is not restricted to the two-meter amateur band alone. Built-in tone burst is available for use with repeaters. The half-second tone burst is keyed by the push-to-talk switch. A carrier frequency adjustment allows the frequency to be set exactly.

Other modulation, such as frequency shift keying, can be applied to the *frequency modulator*. An audio level of 10 mV is required. The frequency response of the *modulator* is 200 to 3500 Hz. Clipping on voice is approximately 7 dB.

The unit is priced at \$34.50 postpaid. Built-in tone burst is \$10. Communicator model and tone-burst frequency must be specified with order. For more information write to Palomar Engineers, Box 455, Escondido, California 92025 or use *check-off* on page 110.

improved signal one

Computer Measurements, having taken over Signal/One, has announced an improved version of the CX7 transceiver. The new radio, designated the CX7A, incorporates a series of modifications found desirable after years of use of the CX7 in the field. The major modifications include power supply protection to eliminate transients and surge problems which have destroyed sensitive solid-state circuitry in the CX7. The audio passband in both transmit and receive has been broadened to enhance the lower-frequency response. Vox turn-on has been changed to cure the syllable-clipping problems old owners have complained about. TVI and spurious outputs have been reduced by changes to the rf driver circuitry. A few minor changes have also been incorporated in the new CX7A.

Signal/One sells the CX7A for \$2195,

the same price as the original CX7. Owners of the older model can have all the factory modifications incorporated in their transceiver for \$69.50. The entire set of modifications, besides improving overall reliability, is said to give the unit a new sound.

For more information on the new CX7A or on modification for A CX7, write to Signal/One, 1645 West 135th Street, Gardena, California 90249.

rf fet design kit

A special rf fet design kit is being offered by Siliconix to help familiarize amateur experimenters and professional designers with the capabilities of rf fets. The kit includes three E300s suitable for fm preamps, two 2N5397s for mobile rigs, two U310s for community antenna television amplifiers, two UT100s for uhf preamps, one 2N5912 for a uhf/vhf mixer, a set of fet design ideas, application notes and data sheets and a copy of the *FET Handbook*.

The regular retail price of the kit would be \$55.15, but it is being offered as a package for \$19.95 from local Siliconix distributors. It is also available by mail for an additional \$1.50 postage and handling fee from Siliconix Incorporated, Attention: Mr. B. Siegal, 2201 Laurelwood Road, Santa Clara, California 95054. More information is available from this address or by using *check-off* on page 110.

worldradio

Wordradio is a new amateur-radio newspaper published every three weeks by Armond Noble, WB6AUH. Completely non-technical and non-political, *Wordradio* covers public service, humanitarian and international aspects of the hobby as well as FCC news. Service nets, ham expeditions, unusual amateurs, amateur connected rescues and mercy missions are all reported in the new newspaper. For a sample copy write to *Worldradio*, 2509 Donner Way, Sacramento, California 95818.

digital clock



Aero-Metric is now offering their new, all solid-state digital clock in both a 12- and a 24-hour version. Time display is in hours and minutes, using bright red neon readout tubes rated at 200,000 hour life (over 22 years). The circuit uses TTL logic and includes 15 integrated circuits, 4 transistors and 7 diodes.

The time base of the logic circuit is taken from the 117-volt power line frequency of 60 Hz so accuracy is based on the United States power grid 60 Hz standard of within 3 seconds per year. The power supply has a built-in, rechargeable battery which holds time in the logic circuit during short interval power line failures up to 5 minutes.

The 24-hour clock has a station-identification feature for amateur operators which consists of a bright red neon light which flashes for 30 seconds every 10 minutes. This serves as a reminder to transmit the station call letters as required by FCC regulations. This station-identification feature can be switched off.

The 12-hour clock is \$93.00, and the 24-hour clock is \$99.00 with standard metal cabinets in a choice of black or gold. A choice of walnut or maple cabinets is available at \$9.00 extra. These clocks are unconditionally guaranteed for one year on all parts and labor, under normal use.


Clocks can be purchased direct from the factory with BankAmericard or Master Charge (include card number), C. O. D. (\$20.00 down), check or money order. All postage is prepaid except C. O. D. For free literature write to Aero-Metric General, Inc., 155 Franklin Street, Dayton, Ohio 45402 or use *check-off* on page 110.

AMATEUR ELECTRONIC SUPPLY

- has -

ROBOT

*In Stock for
Immediate Delivery*

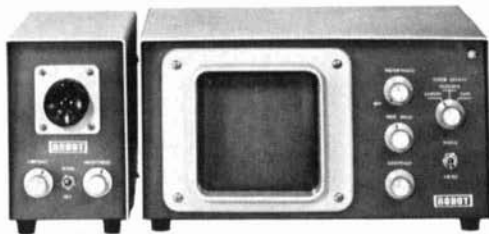

ROBOT MODEL 70 MONITOR... \$495
ROBOT MODEL 80 CAMERA... \$465
25mm, f1.9 lens \$ 30
25mm, f1.4 lens \$ 40
25mm, f1.4 Macro lens \$ 60

AMATEUR ELECTRONIC SUPPLY

4828 West Fond du Lac Ave. Milwaukee, Wis. 53216
Phone (414) 442-4200

HOURS: Mon & Fri 9-9; Tues, Wed & Thurs 9-5:30; Sat 9-3

To: AMATEUR ELECTRONIC SUPPLY
4828 West Fond du Lac Avenue
Milwaukee, Wisconsin 53216

I am interested in the following new equipment:

I have the following to trade: (what's your deal?)

Ship me the following New Equipment.

I enclose \$ _____; I will pay balance (if any)

COD (20% deposit) Revolving Charge Plan

Name _____

Address _____

City _____

State _____ Zip _____

Send Reconditioned Equipment Bulletin

scanning fm transceiver



Regency Electronics is now marketing their Transcan* base and mobile transceivers for the 2-meter fm band. Units are in production and are being distributed throughout the country.

Regency calls Transcan a new reception concept in fm transceivers. The receiver section of the transceiver scans as many as 8 crystal-controlled channels anywhere in the band. Upon reception of a signal, scanning stops, and the receiver monitors the frequency being used. At the end of the transmission the receiver resumes scanning at the rate of 15 channels per second. Each channel can be quickly programmed in or out of service by the push of a button so the receiver will not be locked onto one frequency if the channel is tied up.

All eight transmit channels are also pushbutton selected. When a transmit button is pushed the receiver stops scanning and locks on the receiver channel paired to the selected transmit frequency. Both transceivers — the HR-2S 117-Vac base transceiver and the HR-2MS 13.6-Vdc mobile transceiver — are American made and are fully solid state.

The receiver boasts 0.35 μ V sensitivity for 20-dB quieting, selectivity at 6 dB down of ± 16 kHz, 45-dB image rejection and 60-dB spurious rejection. Modulation acceptance is ± 15 kHz and audio output is 5 watts into a built-in front panel speaker.

The transmitter runs 15 watts output across the entire 144- to 148-MHz band and has adjustable deviation zero to 15 kHz. Spurious and harmonic emissions are measured at 55 dB or more below the

*Transcan is a trademark of Regency Electronics, Inc.

"What do you think of SSTV?"



"Doc" Taylor, WØFEE answers

We recently called Doc, one of the most active amateur radio operators in the country, who we knew owned a Robot SSTV Camera and Monitor, and asked him, "What do you think of SSTV?" Here are some of his comments:

"I've been an active ham since 1946 and SSTV is the greatest thing that's ever happened to amateur radio... I love the friendliness of SSTV because we can be so personal, sending pictures of ourselves and our families to one another... I spend practically all my spare time operating SSTV... there are many, many people on SSTV now, new Robot stations are popping up every day... I've worked Australia, New Zealand, Laos, South America, Africa, Italy, Hawaii, Alaska. Establishing contacts is no problem... As far as the Robot equipment is concerned,

it's excellent equipment, the Cadillac of the industry. And I've gotten excellent service. I'm really pleased with the Robot gear."

ROBOT MODEL 70 SSTV MONITOR...\$495
ROBOT MODEL 80 SSTV CAMERA...\$465

For complete information on Slow Scan TV, the Robot SSTV Camera and Monitor, and a copy of our SSTV operator directory, write:

ROBOT

ROBOT RESEARCH INC.

7591 CONVOY COURT, SAN DIEGO, CA 92111
(714) 279-9430

See the complete line of Robot SSTV equipment at your nearest dealer.

Birmingham, Ala. 35233, James W. Clary Company, 1713 Second Avenue South, (205) 322-2486 • **Anaheim, Calif. 92804**, Henry Radio Company, 931 North Euclid, (714) 772-9200 • **Los Angeles, Calif. 90064**, Henry Radio Company, 11240 West Olympic Boulevard, (213) 272-0861 • **Oakland, Calif. 94607**, Amrad Supply, 1025 Harrison Street, (415) 451-7755 • **Denver, Colo. 80202**, CW Electronic Systems, 1401 Blake Street, (303) 244-5523 • **Miami, Fla. 33137**, Amateur Radio Center, Inc., 2805 NE Second Avenue, (305) 374-4101 • **Honolulu, Hawaii 96803**, Honolulu Electronics, 819 Keeaumoku Street, (808) 949-5564 • **Baltimore, Md. 21211**, Amateur Radio Center, 1117-19 W. 36th Street, (301) 889-5214 • **Wheaton, Md. 20902**, Electronics International Service Corp., 11305 Elkin Street, (301) 946-1088 • **Reading, Mass. 01867**, Graham Radio Company, 505 Main Street, (617) 944-4000 • **Muskegon, Mich. 49441**, Electronic Distributors, Inc., 1960 Peck Street, (616) 726-3196 • **Butler, Mo.**, Henry Radio (816) 679-3127 • **St. Louis, Mo. 63132**, Ham Radio Center, 8342 Olive Boulevard, (314) 993-6060 • **Las Cruces, New Mexico 88001**, Mannies Electronic and Photo Supplies, 802 So. Solano, (505) 524-3646 • **New York, N.Y. 10012**, Barry Electronics, 512 Broadway, (212) 925-7000 • **Ashville, North Carolina 28801**, Freck Radio Supply, 38 Biltmore Avenue, (704) 254-9551 • **Cincinnati, Ohio 45231**, Queen City Electronics, 1583 McMakin Ave., (513) 931-1577 • **Cleveland, Ohio 44112**, Amateur Electronic Supply, 17929 Euclid Ave., (216) 486-7330 • **Dayton, Ohio 45404**, SREPCO, 314 Leo St., (513) 224-0871 • **Portland, Oregon 97205**, Portland Radio Supply, 1234 S. W. Stark St., (503) 228-8647 • **Pittsburgh, Pa. 15222**, Cameradio Co., 2801 Liberty Ave., (412) 391-7400 • **Treose, Pa. 19047**, Hamtronics, 4033 Brownsville Rd., (215) 357-1400 • **Fort Worth, Texas 76110**, Ed Juge Electronics, 3850 So. Freeway, (817) 926-5221 • **Houston, Texas 77002**, Madison Electronics Supply, 1508 McKinney Ave., (713) 224-2668 • **Spokane, Wash. 99206**, HCJ Electronics, E. 8214 Sprague, (509) 924-2343 • **Milwaukee, Wisc. 53216**, Amateur Electronic Supply, 4828 W. Fond du Lac Avenue, (414) 442-4200 • **CANADA: Fredericton, N.B.**, Audio Lectronics Ltd., 79 Prospect Street, (506) 454-3380 • **Toronto, Ontario**, VE Amateur Radio, 3768 Bathurst Street, (Downsview), (416) 636-3636 • **Montreal, Quebec**, Payette Radio Company, 730 St. Jacques, (514) 866-6681.

ONE COMPLETE SOURCE
SPECIALIZING

DALE
ELECTRONICS

**2 METER
FM RIGS**

TOP BRANDS

AVAILABLE FOR

IMMEDIATE SHIPMENT

- SONAR RADIO
- STANDARD COMMUNICATIONS
- DYCOMM
- GAM ANTENNAS
- HYGAIN
- DRAKE
- CUSH CRAFT
- ANTENNA SPECIALTIES
- INTERNATIONAL CRYSTAL
- GALAXY
- BOMAR
- CRYSTEX
- LARSEN ANTENNAS
- SHURE COMM MIKES

We stock crystals
and parts for all sets we sell

— Write for free literature —

DALE ELECTRONICS CORP.

244 West 14th St., New York, N.Y. 10011
Free Parking 212-255-3660

carrier.

The mobile HR-2MS sells for \$319, and the base HR-2S sells for \$349 including a ceramic push-to-talk microphone and crystals for 146.94 MHz Simplex.

For more information write to Regency Electronics, Inc., 7900 Pendleton Pike, Indianapolis, Indiana 46226 or use *check-off* on page 110.

parts kits



Assortments of the most widely used Centralab electronic components are offered in eight new service kits designed to provide hams, experimenters, service dealers and designers with a well-balanced supply of their component requirements. Briefly described, the new kits are: Kit-10F, Fastatch II controls; -20W, miniature wire-wound controls; -30T, miniature trimmer controls; -50A, axial lead electrolytics; -55P, pc lead electrolytics; -60D, general purpose capacitors; -70H, high voltage capacitors and -100P, packaged electronic circuits.

Each kit is housed in a rugged steel frame cabinet with 15 plastic drawers. Cabinet size is 10 x 8 x 6¼ inches, and the cabinets are portable with convenient handles. The cabinets may be stacked in groups or wall mounted. All kits are supplied completely ready to use with components functionally arranged in drawers by value, type and size. Each drawer is pre-labeled clearly showing contents. The latest edition of H. W. Sams "Replacement Control Guide" is included in the 3 control units (Kit-10F, -20W, -30T).

HAMFEST


WESTERN N. Y.
HAMFEST and
VHF CONFERENCE

MAY 13, 1972

Monroe County
Fairgrounds
Rt. 15A
Rochester, N. Y.
(Near Thruway Exit 46)

- Huge Flea Market
- Top Programs
- Award Presentations
- Banquet
- Friday Night Cocktails

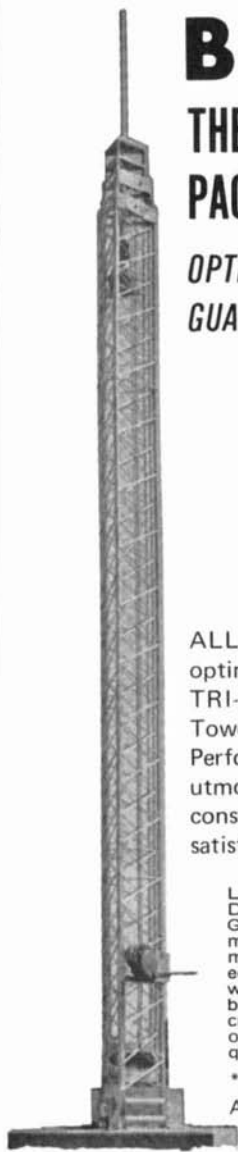WRITE:
WNY HAMFEST
BOX 1388
ROCHESTER, N. Y.
14603



W51 SHOWN

BONUS THE BEST ANTENNA PACKAGES YET!

*OPTIMUM PERFORMANCE
GUARANTEED SAVINGS*



ALL NEW, engineered for optimum performance with TRI-EX's Certified* Antenna Towers & HY-GAIN's TOP Performance Antennas. The utmost in craftsmanship and construction for your satisfaction. . . .

Local Bank Financing - 15% Down or Trade-In Down - Good Reconditioned Equipment. Nearly all makes and models. Our reconditioned equipment carries a 30 day warranty and may be traded back within 90 days for full credit toward the purchase of NEW equipment. Inquiries invited.

* Certified Welders & Approved by L.A. City

LAE MW35 "STANDARD" Package
(Free Standing Crank-Up Tower
9.5 Sq. Ft. - 50 MPH) (35 Ft.)
CDR AR-22R Rotator*
100 ft. RG-58/U Coax & Control Cable
Substitute 50 ft. free standing, add \$100
*Complete with one of the following
antennas:*

- | | |
|---------------------------|-------|
| HY-GAIN TH2MK3 | \$259 |
| HY-GAIN TH3JR | \$259 |
| HY-GAIN DB10-15A | \$265 |
| HY-GAIN HY QUAD | \$280 |
| HY-GAIN TH3MK3 | \$290 |
| *TR-44 rotor w/cable add: | \$ 30 |
| HAM-M rotor w/cable add: | \$ 60 |

LAE W51 "DELUXE" Package (51 Ft.)
(Free Standing, 9 Sq. Ft. - 50 MPH)
CDR TR-44 rotor*
100 ft. RG58/U Coax & Control Cable
Substitute 67 ft. free standing, add \$400
*Complete with one of the following
antennas:*


- | | |
|------------------|-------|
| HY-GAIN DB10-15A | \$575 |
| HY-GAIN HY QUAD | \$590 |
| HY-GAIN 204BA | \$610 |
| HY-GAIN TH3MK3 | \$610 |
| HY-GAIN TH6DXX | \$635 |

Free stdg. base incld. NO/CHARGE
*HAM-M rotor w/RG8/U add: \$ 40
LAE LM354 "SUPER" Package (54 Ft.)
(16 Sq. Ft. - 60 MPH)
CDR HAM-M Rotor
100 ft. RG8/U Coax & Control Cable
Substitute 70 ft. free standing, add \$650
*Complete with one of the following
antennas:*

- | | |
|----------------|-------|
| HY-GAIN TH3MK3 | \$735 |
| HY-GAIN 204BA | \$740 |
| HY-GAIN TH6DXX | \$765 |

Freight PREPAID to your door in the Continental USA west of the Rockies. For shipment east of the Rockies, add \$10.00. Substitutions may be made.... write for prices.

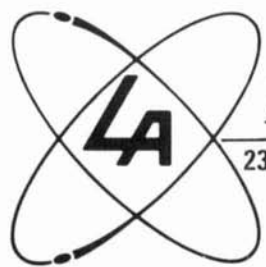"WEST COAST'S FASTEST GROWING AMATEUR RADIO DISTRIBUTOR"
"WE SELL ONLY THE BEST"



Electronix Sales

23044 S. CRENSHAW BLVD., TORRANCE, CALIF. 90505
Phone: (213) 534-4456 or (213) 534-4402
HOME of LA AMATEUR RADIO SALES

YOU ASKED FOR IT!

HERE IT IS! . . . one complete U.S. Callbook and one complete DX Callbook per year and no change in price. In addition you can keep your CALLBOOKS up-to-date through a subscription to the new Service Edition Series published each March 1, June 1 and September 1 — each one covering new licenses and all activity during the preceding quarter. Annual subscription to complete Winter CALLBOOKS plus 3 Service Editions only **\$14.95** postpaid for the U.S. and **\$11.45** postpaid for the DX.



Over 285,000 QTHs
in the U.S. edition
\$8.95

Over 180,000 QTHs
in the DX edition
\$6.95

These valuable EXTRA features included in both editions!

- QSL Managers Around the World!
- Prefixes by Countries!
- Census of Radio Amateurs throughout the world!
- Zips on all QTHs!
- Radio Amateurs' License Class!
- A.R.R.L. Phonetic Alphabet!
- World Prefix Map!
- Where To Buy!
- International Radio
- Great Circle Bearings!
- Amateur Prefixes
- International Postal Information!
- Plus much more!

See your favorite dealer or order direct (add 25¢ for mailing in U.S., Possessions & Canada. Elsewhere add 50¢).

**50 YEARS OF SERVICE
TO RADIO AMATEURS**

GET YOUR NEW ISSUE NOW!

**WRITE FOR
FREE
BROCHURE!**



RADIO AMATEUR **callbook** INC.

Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

Complete information on these eight new service kits is available from Centralab distributors, or by writing directly to Distributor Products, Centralab, the Electronics Division of Globe-Union Inc., 5757 North Green Bay Avenue, Milwaukee, Wisconsin 53201, or using *check-off* on page 110.

wire stripper

Radio Shack is offering a new automatic wire stripper and cutter in their line of Archer tools. The new tool strips number 24 to number 12 gauge wire in a second. To operate the wire stripper you insert the wire, squeeze the insulated handles and release. Insulation is removed cleanly and completely without nicking or breaking the wire. A strip gauge guides the wire to the correct portion of the blade and assures a uniform stripped length every time.

The Archer automatic wire stripper and cutter is priced at \$4.95 and is available exclusively through Radio Shack's more than 1100 stores or by mail from Allied Radio Shack, 2400 West Washington Boulevard, Chicago, Illinois 60680. More information is available through *check-off* on page 110.

light-emitting diodes

The ham and experimenter can now get four different light-emitting diodes in the Motorola HEP line. The new diodes lend themselves to digital displays, burglar alarms, panel lights, digital clocks, frequency counters and other digital read-out circuits in which the low power requirements and long life of the light-emitting diode offer new design possibilities.

The new Motorola LEDs include three visible red diodes (P2000, P2001 and P2003) and one infrared diode (P2002). They are available through any HEP dealer. More information is available from Motorola HEP Semiconductors, Box 20924, Phoenix, Arizona 85001 or use *check-off* on page 110.

THE SCRUBBER

ELIMINATES QRN AND QRM




NEW DESIGN PRINCIPLE GIVES YOU

- **TOTAL ISOLATION**—The SCRUBBER is NOT A FILTER. The SCRUBBER Output tone is completely isolated from the Incoming Signal by use of the new Douglas Randall FRITCH® (Pat. Pend.), a FREQUENCY RESPONSIVE SWITCH. The audio output of any station receiver drives the FRITCH. When the selected audio tone is received, the FRITCH keys a local oscillator by means of an integral reed relay. The OSCILLATOR tone is adjustable for pitch and volume to suit the operator's taste. THIS IS THE ONLY SOUND THE OPERATOR HEARS.
- **EASY OPERATION**—Connect the SCRUBBER to any standard receiver, tune until the meter on the SCRUBBER peaks, and flip the "SCRUB" switch to "IN" for completely noise free reception.
- **A MULTI-PURPOSE ACCESSORY**—Housed in a handsome wood grained cabinet, the SCRUBBER can also be used as a STATION SPEAKER, on the air CW MONITOR, or as a CODE PRACTICE OSCILLATOR.

®Registered trade name of Douglas Randall Frequency Responsive Switch

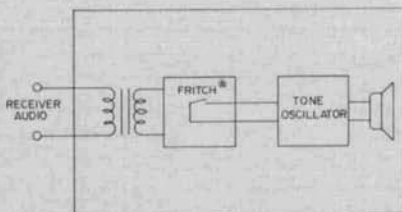DOUGLAS RANDALL DIVISION
WALTER KIDDE & COMPANY INC.
6 PAWCATUCK AVENUE
PAWCATUCK, CONN. 02891



- **REDUCES OPERATOR FATIGUE.**
- **ELIMINATES ADJACENT SIGNALS.**
- **355 SIGNALS BECOME 599.**

DOUGLAS RANDALL SALES DEPT.
6 PAWCATUCK AVENUE
PAWCATUCK, CONN. 02891

Enclosed is Money Order— Personal Check and order for One SCRUBBER @ \$94.50 (Connecticut Residents add 5% Sales Tax). Freight Prepaid in Continental U.S.A.

Name Call

Address

City State ZIP

MEMORY-MATIC 500 KEYS

Today's newest and most advanced keyer. 500 bit/40 character Read-Write memory. Stores any message instantly. Near-Full and overload alarms. Includes all Space-Matic 21 features.

\$198.50



SPACE-MATIC 21 KEYS

Instant self-starting, self-completing dots, dashes, and associated dot, dash, character and word spacing. Adjustable weighting, 3.5-85 wpm. Built-in sidetone and speaker. Iambic. Dot and dash memories. Suitable for use with all standard keys.

\$89.50



FREQUENCY MARKER STANDARD

Markers at 5, 10, 25, 50, 100, 200 and 400 kHz. 400 kHz crystal. No unwanted markers. Latest low power ICs. Buffered osc. and output.

\$32.95 (Less Batteries)



ELECTRONIC FEATHER TOUCH KEY

The solid-state design detects the mere touch of your finger and eliminates such problems as contact bounce, proper adjustments and dirty contacts. Weighted.

\$19.95, \$22.95 SPDT Switch Option



5-year guarantees • PPD USA • Send for brochures

DATA ENGINEERING INCORPORATED

BOX 1245 • SPRINGFIELD, VA. 22151

CRYSTAL BARGAINS

Depend on . . .

We supply crystals from 16 KHz to 100 MHz in many types of holders. Over 6 million crystals in stock. We manufacture crystals for almost all model SCANNERS, MONITORS, 2-WAY RADIO, REPEATERS, ETC. Inquire about special quantity prices. Order direct with check or money order.

For first class mail add 15¢ per crystal...for airmail add 20¢ ea.



DIVISION OF BOB WHAN & SON ELECTRONICS, INC.

2400 Crystal Dr.
Fort Myers
Florida 33901
(813) 936-2397

Send 10¢ for new catalog with oscillator circuits and lists of thousands of frequencies in stock.

SPECIALS! CRYSTALS FOR:

Frequency Standards	
100 KHz (HC13/U)	\$4.50
1000 KHz (HC6/U)	4.50
Almost All CB Sets, Trans. or Rec. (CB Synthesizer Crystal on request)	2.50
Any Amateur Band in FT-243 (Except 80 meters)	1.50
80 Meter Range in FT-243	4 for 5.00
80 Meter Range in FT-243	2.50
Color TV 3579.545 KHz (wire leads)	1.60
	4 for 5.00

ALL SOLID-STATE SSB TRANSCEIVER



**SSB-3
\$195.50**

- Complete single-band SSB transceiver 4 to 5 watts PEP output 15, 20, 40 or 75 meters.
- VFO tuning 3750 to 4000 on 75, full coverage on 40, 20 and 15 meter amateur bands.
- Suitable for dry battery operation.
- Light weight, small size, makes excellent portable — boat, aircraft, field or mobile.
- Contains 15 transistors, 1 mosfet, 2 Darling-ton amps, 1 i.c. and 17 diodes. Four-pole filter.
- Available accessories, AC power supply, MIC, headsets, lightweight dipole and 40 watt PEP linear amplifier.
- Xtal controlled emergency and net transceiver available. Write for full information on transceivers and accessories.

JUSTIN INC.

2663 LEE STREET
SOUTH EL MONTE, CALIF. 91733

INTEGRATED CIRCUITS

FACTORY FRESH — NO REJECTS
W/SPEC. SHEETS

FAIRCHILD — PHILCO — RCA
MOTOROLA — NATIONAL

NEW LOW PRICES
RTL or TTL LOGIC

UL 900 Buffer	80¢	10/5.50
UL 914 Gate	80¢	10/5.50
UL 923 JK Flip-flop	\$1.50	10/8.50
MC 790P Dual JK Flip-flop	\$2.00	10/18.95
MC 890P Dual JK Flip-flop	\$2.00	10/18.95
MC 789P Hex Inverter	\$1.00 ea.	10/9.25
MC 724P Quad 2 Input Gate		
MC 799P Dual Buffer		

MC 780P Decade	\$3.00
MC 767P Quad Latch	3.00
MC 9760P Decade	5.00
ONE EACH OF 3 ABOVE \$10.50	

7400 Quad 2 Input NAND Gate	65¢	10/5.95
7404 Hex Inverter	65¢	10/5.95
7441A Decimal Decoder/Driver	\$3.50	10/29.95

NEW!! 7447 7 Segment Decoder/Driver	\$3.10 each	10/\$27.95
7473 Dual JK Flip-flop	\$1.30	10/10.95
7475 Quad Latch	\$2.10	10/19.95
7490 Decade Counter	\$2.40	10/19.95
709 Op Amp	\$1.75	10/16.50
741 Op Amp	\$2.70	10/25.00
CA 3035 Linear Amplifier	\$2.25	10/21.95
LM 309K 5V Regulator	\$3.75	10/\$34.95
14 Pin Dual Inline socket terminals	25¢	10/2.25
16 Pin Dual Inline socket terminals	30¢	10/2.75

NEW NATIONAL Long Life Nixie tubes NL 940S 0-9 with two decimal points	\$4.50 ea.	10/42.95
Japanese Readout will replace 5750 tube	\$2.95 each	10/\$27.50
SOCKET for NL 940S	50¢ each	
100 KC CRYSTAL NEW	\$3.95	

88 MH TOROIDS 10/3.00

TRANSFORMERS	
Pri 115V 60 cyc Sec. 6.3V ct 20 amp	12 lbs \$3.95 each
Pri 117V 60 cyc Sec. 850V ct — 310 MA	6.3V ct — 18 Amp
	6.3V ct — 5.5 Amp
	20V — 2.8 Amp
	23 lbs. \$5.95 each

COOLING FAN BLOWER 4 pole 110V 60 cyc motor with 4 bladed nylon fan. Very quiet, about 50 CFM 2 1/4" W x 3" H x 2 1/4" D. Sh. wt. 3 lbs. \$2.25 each

CAPACITORS	
1000 MFD 15V	25¢ ea 10/\$2.00
50 MFD 15V	20¢ ea 10/\$1.50



R & R ELECTRONICS
311 EAST SOUTH ST.
INDIANAPOLIS, IND.
46225

\$5.00 minimum order.
Please add sufficient postage.

the all "NEW" CRYSTAL CALIBRATOR

FROM



- 100 - 50 - 25 KC MARKERS
- ZERO BEAT TO W W V
- USES NEW 100 KC CRYSTALS (included in all units)
- GLASS EPOXY BOARDS
- VERY COMPACT 2" x 3" x 1/2"
- 3.5 V. OPERATION

\$12⁹⁵ KIT
with
100 KC CRYSTAL



Wired and zeroed to W W V \$15.95

SPECIAL OFFER

10% Off any item on this page if you tell us you saw it in Ham Radio.

Offer expires April 30.

ARN-30 108-135 mc tunable receivers. High frequency version of the famous command receivers. Listen to local airport frequency or convert to 2 meters. Like New with schematic and operating instructions. 12 lbs. \$14.95

Western Union facsimile machines, send and receive pictures and memos. Works on 115 v 60 cycles. Shipped with auto-start, auto-phase pos-to-pos, conversion instructions. 20 lbs. \$19.95

Telfax paper for above facsimile.
2¢ each 1000 for \$12.95

BARRY

PAYS CASH for your unused equipment, tubes, components, semi-conductors, etc. Send your list today for a fast cash offer.
512 BROADWAY NEW YORK, NEW YORK 10012 212-WA-5-7000

HQS for ONE of the LARGEST STOCKS of NEW & UNUSED TUBES and SEMICONDUCTORS

Two Meter 19" Magnetic-mount whip antenna, with 10' of Amphenol coax & PL-259 Connector. @ \$9.95
Net wt. 1 lb.

Drake "Demos": Receivers 2-C @ \$195.00, SPR-4 @ \$370.00, SW4-A @ \$250.00, Transmitters: TR-4 @ \$465.

Dycomm Super Brick Booster; for TR-22. 30 watts out for 1W in @ \$99.95

Dycomm Brick Booster; 1W to 2W in, 20 to 25 watts out @ \$79.95

Dycomm Block Booster; 50 watts out for 10 watts in @ \$99.95

Dycomm "10-0" 100 watts out for 10 watts in typ. @ \$195.00

VHF Specialists 2M FM RF power amps. FM-3-30, 3 watts in 30 watts out typ. @ \$79.95, FM-10-50, 10 watts in 50 watts out typ. @ \$99.95.

2M Pre-amp, 13db gain, 3.5db NF. @ \$12.95.

IC-20 2M FM TCVR; 12 channels, 12 volt operation. With mike, mounting bracket and 3 channels supplied. 10 watts output @ \$289.00

Rechargeable Battery Pac. @ \$49.00.

IC-3P Discriminator meter/power supply, 110 AC operation of IC-20. @ \$75.00

IC-21 2M FM TCVR with 24 channel operation, AC-DC power supply, Deviation meter, 3 Ch., SWR & RF power meter and R.I.T., 10 watts output. @ \$389.00

Drake TR-22 2M FM Portable, complete with mike and ni-cads. New. @ \$199.95

Hallcrafters HT-44 80-10 meter SSB-CW-AM Transmitter with PS-150-120 pwr sup. @ \$250.00

Swan 250 6 Meter SSB Transceiver, 117XC power supply & speaker. @ \$325.00

Clegg "Venus" 6 Meter Transceiver with National AC power supply. @ \$275.00

Swan "Cygnet" Transceiver with built-in 12-vdc/220AC power supply. New, write.

Jennings UCSXF-2300 @ 10KV. Vacuum Variable Capacitor, 50 to 2300pf. Unused, Orig. box @ \$195. 64,000 ufd/30 vdc/40 surge, computer grade capacitors. New @ \$4.95.

8000 ufd/55 vdc, New @ \$2.50

Gonset G-76 80 thru 6 meter transceiver with AC supply. @ \$130.00, DC supply @ \$55.00

Ten-Tec; RX-10 @ \$59.95, S-30 @ \$49.95, PM-3A @ \$79.95, PM-2B @ \$65.95

Robot SSTV Camera @ \$465.00, Monitor @ \$495.00, F 1.9, 25mm Lens @ \$30.00

Pearce-Simpson 25 watt 2M FM TCVR, 6 channels independent transmit and receive, 2 ch. supplied. 12 volt DC operation @ \$249.95.

With AC supply @ \$299.95

Polarad Microwave Signal Generator Model SG-400 A/U, 4.2 to 11.0 KMC with direct read-out on frequency. Iuv to 200mv output, internal and external modulation and all cables, accessories and spare tubes. New @ \$795.00

Call or write for information on the CX7A Transceiver and the New SBE Digital Transceiver.

Also Alpha/Sevento Linear Amplifiers. Barry Electronics is also an Export company and can handle orders from all over the world. Prices FOB N.Y., N.Y. 10012.

BARRY 512 Broadway NY, NY 10012 212-WA-5-7000 ELECTRONICS

AT LAST -- A SPEECH COMPRESSOR THAT REALLY WORKS!



RPC-3M MODULE
(ONLY \$22.50)

- LOW DISTORTION CIRCUIT
- FULLY WIRED & TESTED NOT A KIT
- WORKS WITH PHONE PATCH
- INTERNAL UNITS & MODULES WORK MOBILE
- FULL WARRANTY — ONE YEAR
- INTRODUCTORY LOW PRICES (Illinois residents add 5% Sales Tax)

Write for specifications and information sheets (free)

Demonstration Tape (cassette) available (\$2.00 deposit)



RPC-3C CABINET MODEL
(\$34.95)



RPC-3,3U INTERNAL UNIT
(\$24.95)

Rp Electronics

BOX 1201H
CHAMPAIGN, ILL.
61820

PHONE ORDERS

NOW ACCEPTED FOR

1 DAY C.O.D. SHIPMENT

ON ALL OUR

PRE-AMPS

AND SOME OF OUR

CONVERTERS

If you need a low noise pre-amp in a hurry for communications or instrumentation, we can fill your order custom tuned to any frequency from 5 MHz. to 475 MHz. within 24 hours by air mail or special delivery. All you pay is our regular low price plus C.O.D. shipping charges. This rush service is also available on some of our stock converters. See Oct., Nov. and Dec. 1971 issues of 73 Magazine for our 2 page condensed catalog. Call us between 9AM and 4PM, Monday thru Friday except holidays (no collect calls please). If line is busy keep trying.

PHONE: 212-468-2720

VANGUARD LABS


196-23 JAMAICA AVE.
HOLLIS, N.Y. 11423

for the most advanced antennas under the sun!



HY-GAIN 204BA MONOBANDER

...a
tiger
on
20 meters

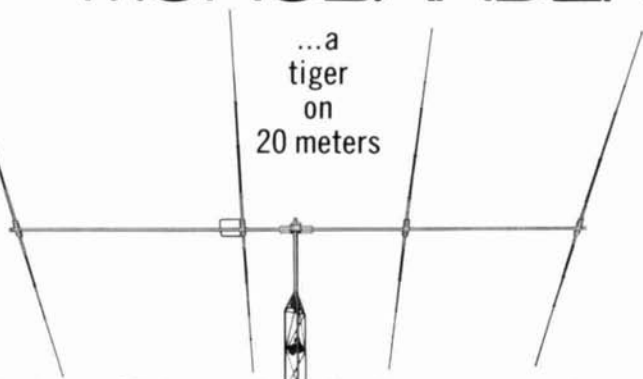

The best antenna of its type on the market. Four wide spaced elements (the longest 36'6") on a 26' boom along with Hy-Gain's exclusive Beta Match produce a high performance DX beam for phone or CW across the entire 20 meter band.

- 10 db forward gain
- 28 db F/B ratio
- Less than 1.05:1 SWR at resonance
- Feeds with 52 ohm coax
- Maximum power input 1 kw AM; 4 kw PEP
- Wind load 99.8 lbs. at 80 MPH
- Surface area 3.9 sq. ft.

The 204BA Monobander is ruggedly built to insure mechanical as well as electrical reliability, yet light enough to mount on a lightweight tower. (Recommended rotator: Hy-Gain's new Roto-Brake 400.) Construction features include taper swaged slotted tubing with full circumference clamps; tiltable cast aluminum boom-to-mast clamp; heavy gauge machine formed element-to-boom brackets; boom 2" OD; mast diameters from 1½" to 2½"; wind survival up to 100 MPH. Shipping weight 51 pounds.

See the best distributor under the sun...the one who handles the Hy-Gain 204BA Monobander.

Model 204BA (4-element, 20 meters).....	\$149.95
Model 203BA (3-element, 20 meters).....	\$139.95
Model 153BA (3-element, 15 meters).....	\$ 69.95
Model 103BA (3-element, 10 meters).....	\$ 54.95




FERRITE BALUN MODEL BN-86

Improves transfer of energy to the antenna; eliminates stray RF; improves pattern and F/B ratio. **\$14.95**

HY-GAIN ELECTRONICS CORPORATION

P. O. Box 5407-WD, Lincoln, Nebraska 68505

ELECTRONIC SURPLUS BARGAINS

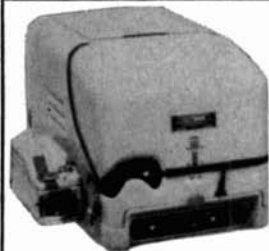

KLEINSCHMIDT TELETYPWRITERS

Model TT-100. Capable of sending 60-100 WPM., 115 v, 60 cyc. Self contained pwr. supply. Shipping wt. 70 lbs. **\$59.50 ea.**

Model TT-843 - Same as above.
UNUSED **\$150.00 ea.**




REPERFORATOR-TRANSMITTER


Model TT-179/FG Mfg by Kleinschmidt
Tape printing & punching, also transmitter-distributor. 115 volts, 60 cyc, shpg. wt. 90 lbs. Used, excellent cond., (gov't. cost \$2,000). **\$59.50**

TELETYPWRITER TABLES

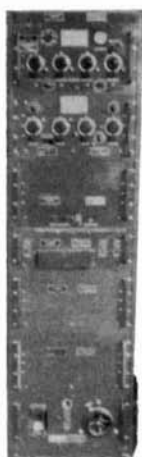Heavy duty construction, shpg. wt. 20 lbs. for page printer, 22" x 18" x 27" ht. **\$15.95**



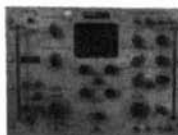2-METER-VHF BC-640 X'MITTER
50 watt - CW and AM.
Freq. range 100-156 MC crystal controlled
Pwr. rgmt. 100/125 60 cyc. Crated wt. 600 lbs. 6' x 22" wide. **\$49.50**



AN/USM-50 OSCILLOSCOPE **\$79.00**

A wide-range, high gain, portable test unit for observation of pulses, short-period electrical disturbances, sine waves, Band width 3 cyc.-15 mc. 105/125 VAC. 50-1000 cyc.

TEST SCOPE

TDMS Transmitter used in testing of teletype equipment, contains 1-3RP1, 1-5687, 1-6N030, 2-12AX7 & 13-12 AU7. No pwr. sply. Shpg wt. 20 lbs. **\$15.00**



ANDY ELECTRONICS — DIV. OF ANDY INTERNATIONAL

6427 Springer

Houston, Texas 77017

713-645-7057

FM RINGO

3.75 db GAIN
AR-2 — \$12.50

WORLD'S BEST VHF FM ANTENNA, IN STOCK AT YOUR LOCAL DISTRIBUTOR.



FM YOUR GONSET COMMUNICATOR

- New! Plug-in modulator puts the Communicator transmitter on FM.
- No modification or rewiring on your Communicator. Just plug into mike jack and crystal socket.
- Compact self-contained modulator measures 4" x 3" x 1 1/2".
- Works with Communicator I, II, III, IV and GC-105.
- FM at a tenth the cost of a new rig.
- Frequency adjust for netting built in.
- Built-in tone burst available. Keyed by push-to-talk switch.
- \$34.50 postpaid U.S.A. Built-in tone burst \$10.00. Specify Communicator model and tone-burst frequency. California residents add 5% sales tax. (HC-6/U crystal and 9 volt transistor battery not supplied.)
- Send for free descriptive brochure.



PALOMAR ENGINEERS



BOX 455, ESCONDIDO, CA 92025

Cush
Craft
CORPORATION


621 HAYWARD STREET
MANCHESTER, N. H. 03103

MAGNUM SIX

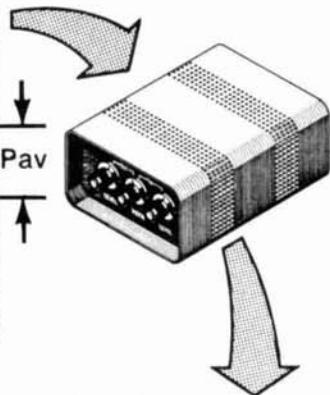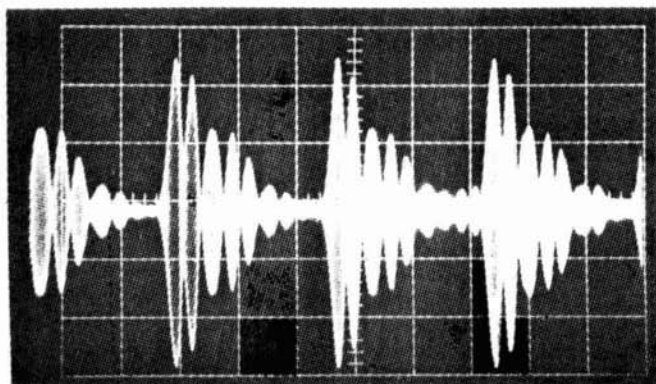RF SPEECH PROCESSOR FOR
COLLINS 'S' LINE & HEATH 'SB'/'HW'* SERIES



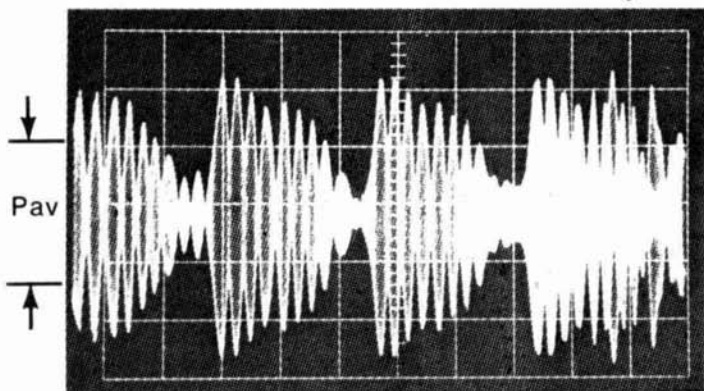↑
KWM-2 SB100
32S-1 SB101
32S-3 SB102
SB400
SB401
*HW100
*HW101



**INTRODUCTORY
OFFER—HURRY
LIMITED TIME ONLY**
\$129.95 Postpaid U.S.
(Add 5% in Washington)

- TRUE RF SPEECH CLIPPING
- > 6db UNDISTORTED AVERAGE POWER GAIN
- DUPLICATE O.E.M. CRYSTAL (HEATH) OR MECHANICAL (COLLINS) FILTER
- HIGHEST QUALITY SOLID STATE COMPONENTS
- REGULATED FAIL-SAFE POWER SUPPLY

Send for FREE Brochure
Communication Technology Group
"A Division of Bitcil Systems, Inc."
31218 Pacific Highway South
Federal Way, Washington 98002



Communication Technology Group
A Division of Bitcil Systems Inc.

the Magnificent **CX7A** by  **signal/one**

Features:

1. All modes 10 through 160 meters in full 1 MHz ranges.
2. Broad band tuning. Instant band changes without tuning.
3. True break-in CW with T/R switching.
4. IF shift — a real QRM slicer.
5. Pre IF noise blanker that really works.
6. RF envelope clipping sounds like a KW.
7. Transceiver — Plus — Receiver built-in two VFO's.



Phone or write

DON PAYNE K4ID

for a brochure and
a big trade-in on
your gear

PAYNE RADIO

Box 525

Springfield, Tenn. 37172

Days Nites - Sundays
(615) 384-5573 (615) 384-5643

8. Calibration within 100HZ on frequency meter nixie digital counter.
9. 300 watt p.e.p. continuous duty cycle.
10. Built-in: FSK shift, spotter level, watt meter, SWR meter, transmit offset, CW electronic Keyer.
11. Quality-Plus. American-made. Hand-picked instrument grade components.
12. New unequalled reliability. "Ham" tested by hams.
13. Perfection **\$2195.00**

EK-404 DELUXE KEYS \$124.95

ALL THE FEATURES YOU'VE ASKED FOR


- 115VAC AND 12Vdc
- READ JAN. 1972 CQ AND MAR. 1972 QST FOR REVIEW OF SIMILAR EK-402 PROGRAMMABLE KEYS

WRITE FOR BROCHURES

GURTS

ELECTRO DEVICES

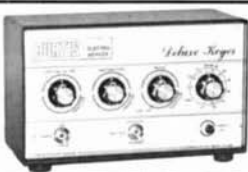BOX 4380 • MOUNTAIN VIEW, CALIFORNIA 94040 • TEL. (415) 964-2126



VARACTORS and VVC'S

for Amateur Radio Service in Voltage Controlled Oscillators, AFC, remote tuning, variable filters . . . try the NEW WAY TO TUNE.

write for data sheets

EASTRON CORP.

25 Locust St., Haverhill, MA 01831



KOJO AUDIO FILTERS FOR SSB AND CW

The KOJO audio filters can greatly improve reception on all receivers, even the most sophisticated receivers. Large amounts of high-frequency hiss, background noise and sideband buckshot can be removed.

The SSB filter is of a low pass configuration, designed with a sharp cutoff to provide a rejection of better than 30 decibels at all ham band frequencies above approximately 3500 Hz. The filter is specifically designed to be placed in a low-impedance line for earphones or speaker.



The CW filter has a spot frequency of 780 Hz and a passband of 1100 Hz with a reference level, 40 decibels below the signal level at the design frequency. The peak of the passband is 100 Hz wide at the -3 decibel reference points. The CW filter is specifically designed for low-impedance input and high-impedance output. High-impedance crystal earphones are recommended. However, with low impedance earphones a small auxiliary amplifier or impedance matching transformer may be used.

KOJO filters are made up of top grade coils and components and are available in easy to assemble kit form with simplified instructions, or in a deluxe model. The deluxe model is completely built up and ready for use and is enclosed in a Gray cabinet[®] with convenient IN-OUT switch.

Try a KOJO and see what you can hear now and could not clearly hear before.

*Slight cabinet layout changes subject to take place without notice.

CW Filter Kit \$ 8.95 Deluxe CW Filter \$16.95
SSB Filter Kit \$12.95 Deluxe SSB Filter \$21.95

All filters shipped postpaid. Arizona residents add 4% sales tax.

THE J. LYNCH CO.

P. O. Box 7774, Phoenix, Arizona 85011

New
3 Digit Counter



• The model fm-36 3-digit frequency meter has the same features that has made the 2 digit model so popular with Hams — low price, small size (smaller than a QSL card), 35 Mhz top frequency, simple connection to your transmitter, +0 -0.1 Khz readout — PLUS the added convenience of a third digit to provide a 6 digit capability. Kit or Assembled.

Example: 28,649,800 Hz reads 28.6 MHz or 49.8 Khz. (Add the 10 Hz module to read 9.80.)


FM-36 KIT \$134.50

NEW

300 MHz PRESCALER only \$45.00
with fm-36 order

Micro-Z Co.

Box 2426 Rolling Hills, Calif. 90274

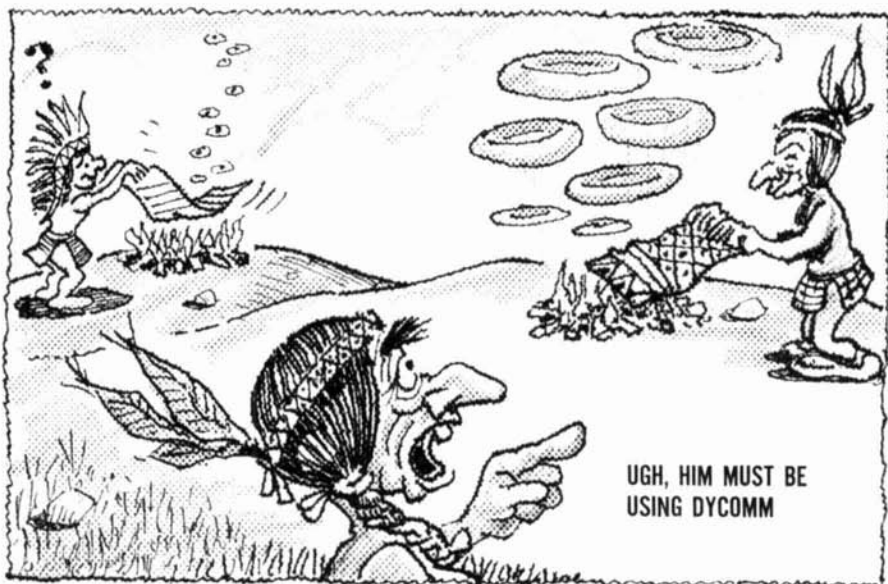

ADD A LINEAR* TO MY 2M FM RIG? WHY NOT?
 YOU DID IT ON 80-40-20-15-& 10!
 And you did it for a good reason!

You wanted to put out a signal that others could hear — without noise, fade, fatigue, or interference.

A **DYCOMM BOOSTER*** can do for you what it has for over 3,000 amateurs:

- Provide up to 50 times increase in power.
- Reduce the cost over a higher power rig.
- Is fully transistorized — no tubes to ever replace.
- Provide mobile rig with more variety — car-car, car-base plus more repeaters you can work through.
- Is fully guaranteed to perform with an outstanding warranty program.

A model for virtually EVERY 2M rig!

Model Line Up:

10-0	10 W input	100 W output	\$195.00
D	10 W input	40 W output	99.95
ES	1 W input	40 W output	99.95

Write for a brochure or call your nearest amateur dealer — you hear!

*A common term for add-on amplifiers.

DYNAMIC COMMUNICATIONS, INC.

948 AVENUE E, P. O. BOX 10116
 RIVIERA BEACH, FLORIDA 33404
 305-844-1323

Master Mobile

COILS GIVE YOU ULTRA-HI "Q"



FOR 80 - 40 - 20 & 15 METERS

You get coil performance for any band based on years of testing and proof in use. Power ratings of 500 and 1000 watts A.M. Use with 36" base section, 60" whip. 2 3/4" diam. Low as \$7.25.


ORDER TODAY FROM

Master Mobile Mounts

Div. of CRYSTEK

1000 Crystal Drive, Fort Myers, Florida 33902

NEW CT-1

From 
Will allow you
to Dynamically test all
types of capacitors.



The Model CT-1 features a built-in electronic power supply providing BOTH AC and DC Test Voltages in a special circuit with highly sensitive NEON type leakage indicator.

Only \$16.95 postpaid

LEE ELECTRONIC LABS, INC.

88 Evans St., Watertown, MA 02172

Dealer Inquiries Invited.

BONUS SALE! NEW LOW, LOW PRICES!

free 810 operational amplifier (dual) DIP w/data for all prepaid orders of \$10. or more.\$1.25 value
FREE 810 op-amp and one LM309K 5 volt 1 amp. power supply module (TO-3) with prepaid orders
of \$25. or more.\$3.75 value
With prepaid orders for \$50. or more you get the \$25. bonus plus ten percent discount on all items
purchased.

TRANSISTORS

Popular numbers. Guaranteed minimum of 40 pieces of TO-5 and TO-18 mixed. Untested, but sampling indicates over 85% good. Approximately 1-ounce—40+ transistors. for only \$1.89

DIGITAL SPECIAL

Ten brand new (on carriers) dual-in-line JK flip-flops—LU321 with data sheet and two pages of application notes describing hookups for—divide by three through ten, and twelve. Also self correcting ring counter hookups, etc. 10 LU321 W/data \$5.00

TTL dual-in-line

7400, 7401, 7402, 7404, 7405, 7410, 7420, 7430, 7440, 7450, 7451, 7453 ea. .30. 7441 BCD decoder driver 1.40. 7442 BCD decoder 1.40. 7473 dual JK flip-flop .65. 7474 dual type D FF .50. 7475 quad latch 1.40. 7476 dual JK FF .65. 7480 gated full adder .80. 7483 4 bit full adder 1.60. 7489 64 bit RAM 4.00. 7490 decade counter 1.40. 7492 divide by 12 counter 1.40. 7493 4 bit binary counter 1.40. 74192 up/down decade counter 2.25. 74193 up/down binary counter 2.00. 74195 unv. 4 bit SR 1.40. 8242 4 bit comparator .90. 8280 preset decade counter 1.40. 8281 preset binary counter 1.40. 8520 25 MC divide by "N" 2 to 15 2.00. 7495 4 bit SHIFT REGISTER 1.40. 8590 8 bit shift register 2.00. 8270 4 bit shift register 2.00.

LINEAR SPECIAL

Ten (10) Teledyne TO-5 741 operational amplifiers with a two-page sheet of application notes covering the basic circuits using op-amps .75 each. Op-amp package 10-741's, data sheet and application notes only \$7.00.

DIGITAL COUNTER MODULE 30MC

Unit includes board, SN7490, SN7475 quad latch SN7447 7-segment driver and RCA "numitron" display tube W/

decimal. 1" x 4.5" module will mount on 1" centers. kit \$12— wired and tested \$15
LED Red Emitting Lamp60

LINEAR IC's (dual-in-line)

709 operational amplifier .50. 710 voltage comparator .75. LM309K 5V-1A power supply module 2.50. LM100 positive voltage reg. .80. 747 dual 741 op amp DIP 1.25. LM302 voltage follower op-amp 1.25.

All IC's are new and fully tested — leads are plated with gold or solder. Orders for \$5 or more will be shipped prepaid. Add 35¢ handling and postage for smaller orders. California residents add sales tax. IC orders are shipped within two workdays of receipt of order — kits are shipped within ten days of receipt of order. Money back guarantee on all goods sold.

BABYLON ELECTRONICS

SEND FOR FREE FLYER

P. O. Box 85
CARMICHAEL, CA 95608
(916) 966-2111

The most powerful signals under the sun!



Hy-gain

Redesigned

HAMCAT



Out-hustles them all!

The famous HAMCAT...now redesigned for greater performance...*equals* or *exceeds* the performance of any other Amateur Mobile antenna. *We guarantee it!* And you need buy only one mast...whether you mount it on fender, deck or bumper. There's just one set of coils and tip rods...and they all stand up to maximum legal power. That's performance, that's value...*THAT'S HY-GAIN!*

Original Hy-Q "quick changer" coils wound on tough fiberglass coil forms for greater heat resistance, less RF absorption / Fiberglass shielded coils can't burn up, impervious to weather / Shake-proof, rattle-proof, positive lock hinge now even stronger...eliminates radio noise / All stainless steel tip rods won't bend or break / Full 5' mast gives you 10% more radiating area than the competition / Rugged swivel-lock stainless steel base for quick band changes, easy garaging.

Get the Hamcat...from Hy-Gain

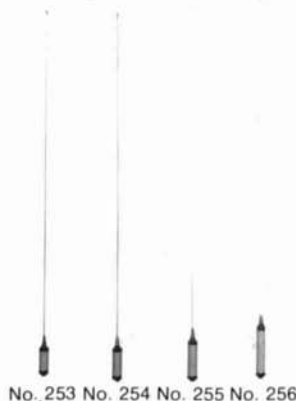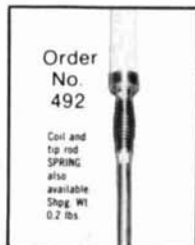- Order No. 257 All new design 5' long heavy duty mast of high strength heavy wall tubing **\$16.95**
- Order No. 252 75 meter mobile coil **\$19.95**
- Order No. 256 40 meter mobile coil **\$17.95**
- Order No. 255 20 meter mobile coil **\$15.95**
- Order No. 254 15 meter mobile coil **\$12.95**
- Order No. 253 10 meter mobile coil **\$10.95**
- Order No. 499 Flush body mount **\$ 6.50**



HY-GAIN ELECTRONICS CORPORATION

P. O. Box 5407-WD Lincoln, Nebraska 68505

DTL LOGIC CARDS

5+1 CARDS! 5 USEABLE CIRCUITS **\$1.25**
SEE HAM RADIO FEB., 72 ISSUE FOR PPD US&CAN
CONTEST DETAILS. 1st WINNERS IN MAY HR!!!

RF TOROIDS TOROID ASSORTMENT FOR THE SERIES BUILDER — 70 CORES — Only \$1.50 PPD. \$3.50

XTAL OSC. 30KC 12VDC 9VP-P Out! \$1.25 PPD

MC301G — 5 Input Or/Nor Gate
MC302G — RS Flip Flop (Buffered Outputs)
MC306G — 3 Input Or/Nor Gate
MC307G — 3 Input Or/Nor Gate
MC310G — Dual 2 Input Nor Gate
MC311G — Dual 2 Input Nor Gate

COPPER CLAD LAMINATES

G10 EPOXY GLASS
1 oz. Copper 1 Side

Pkg. Quant.	3/64"	1/16"	3/32"	1/8"
1 9x12"	\$1.50	\$2.50	\$3.50	\$5.00
2 6x9"	"	"	"	"
4 4 1/2 x 6"	"	"	"	"
6 3x4 1/2"	"	"	"	"

This item postage prepaid.

Every order unconditionally guaranteed.

TRI O

Electronics

2614 Lake Shore Dr. LaCrosse, 2, Wis. 54601

Wisconsin Residents add 4% Sales Tax.

HAM RADIO CENTER Announces!



NOW: Call your order in, and we'll pick up the tab for the phone call. (Minimum order \$10.00)

HOW: Place station to station call. When phone bill is received, forward copy along with our invoice covering order phoned in, we'll send refund check. **DO NOT CALL COLLECT.**

PLUS: We will ship your order PREPAID if destination is in our UPS surface shipping area. (Limit-108" width & girth combined and 50 lbs. max. wt.)

**COMPLETE STOCKS ALL NATIONAL BRANDS
WE BUY-SELL-TRADE USED EQUIPMENT**

Write for List

HAM RADIO CENTER

8342 Olive Bl., St. Louis Mo. 63132
Phone (314) 993-6060

NEW — 6T-HR-2

ADD MORE TRANSMIT FREQUENCIES
TO YOUR HR-2



Will let you add six more transmitter frequencies to your HR-2 or HR-2A, also may be used on Transcan.

6T-HR-2 Kit \$ 9.50
6T-HR-2 Wired \$13.50

Shipping \$.60
Complete with all mounting hardware.

Large stock of crystals for HR-2's and TMR scanners.

HR-2 Xmit. xtals \$5.75
HR-2 Receive xtals \$3.99
TMR Receive xtals \$3.99
Shipping \$.60

Entire Regency amateur line in stock. We ship pre-paid in Continental U.S.A.

TFME 2 METER PRE-AMPS



New!

Improved HF-144U pre-amp. Silver plated epoxy glass circuit board. Filter kit and B+ kit. All mount on new circuit board which is slightly smaller than original. This new board replaces all former except Motrac. Comes with mounting hardware and feet. Designed to work with the new solid state transceivers and older tube equipment. Kit-\$11.50 wired-\$16.50. Ship-.60¢

TOPEKA FM ENGINEERING

1313 East 18th Terrace
Topeka, Kansas 66607



RF SPEECH PROCESSOR



Price
\$79.50* ea

- INCREASE TALK POWER TYPICALLY 5 db
- UNIQUE PLUG-IN UNIT — NO MODIFICATIONS NECESSARY TO THE RIG
- SPECIFICALLY DESIGNED FOR THE 32S-1, 32S-3, KWM-2
- S-LINE QUALITY
- PRE-ALIGNED — NO ADJUSTMENTS
- IN-OUT SWITCH
- SMALL SIZE — BY USE OF PIEZOELECTRIC DRIVE MECHANICAL FILTER & SOLID STATE COMPONENTS

*California Residents add 5% Sales Tax

DX ENGINEERING

2455 Chico Ave., So. El Monte, CA 91733
213/442-7952

for the EXPERIMENTER!

INTERNATIONAL EX CRYSTAL & EX KITS
 OSCILLATOR • RF MIXER • RF AMPLIFIER • POWER AMPLIFIER



1. MXX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 3 to 170 MHz range. Harmonics of the OX oscillator are used for injection in the 60 to 170 MHz range. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering).....\$3.50



2. SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive MXX-1 mixer. Single tuned input and link output. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering).....\$3.50



3. PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX oscillator. Outputs up to 200 mw, depending on the frequency and voltage. Amplifier can be amplitude modulated. Frequency 3,000 to 30,000 KHz.....\$3.75



4. BAX-1 BROADBAND AMP

General purpose unit which may be used as a tuned or untuned amplifier in RF and audio applications 20 Hz to 150 MHz. Provides 6 to 30 db gain. Ideal for SWL, Experimenter or Amateur.....\$3.75



5. OX OSCILLATOR

Crystal controlled transistor type. Lo Kit 3,000 to 19,999 KHz, Hi Kit 20,000 to 60,000 KHz. (Specify when ordering).....\$2.95



6. TYPE EX CRYSTAL

Available from 3,000 to 60,000 KHz. Supplied only in HC 6/U holder. Calibration is $\pm .02\%$ when operated in International OX circuit or its equivalent. (Specify frequency).....\$3.95

for the COMMERCIAL user...

**INTERNATIONAL
PRECISION RADIO CRYSTALS**

International Crystals are available from 70 KHz to 160 MHz in a wide variety of holders. Crystals for use in military equipment can be supplied to meet specifications MIL-C-3098E.

CRYSTAL TYPES: (GP) for "General Purpose" applications
 (CS) for "Commercial Standard"
 (HA) for "High Accuracy" close temperature tolerance requirements.



**write for
CATALOG**



CRYSTAL MFG. CO., INC.
 10 NO. LEE • OKLA. CITY, OKLA. 73102

FM

145 AND 220 MHz
REGENCY, CLEGG, TEMPO
AND STANDARD

VHF ANTENNAS
FIXED AND MOBILE
CUSHCRAFT, HY-GAIN, ANTENNA
SPECIALISTS AND NEW-TRONICS

Ready for shipping
anywhere in the U.S.A. from:

COMMUNICATIONS WORLD, INC.
4788 STATE ROAD
CLEVELAND, OHIO 44109
(216) 398-6363

(From the Midwests Newest
Complete Communications Center.)

FM Schematic Digest

A COLLECTION OF
MOTOROLA SCHEMATICS

Alignment, Crystal, and Technical Notes
covering 1947-1960
136 pages 11½" x 17" ppd \$6.50

S. Wolf
P. O. Box 535

Lexington, Massachusetts 02173

CIRCUIT BOARDS in 10 Minutes

with just a pair
of scissors



Pressure Sensitive Copper Foil
Tape and Sheet

- No Chemicals — No Mess
- No Layout Restrictions
- Full Instructions
- Simple Circuit Changes
- Flexible — Conforms to any surface shape
- Use for Crossovers — Either insulate with Teflon or Mylar or use other side of board.

5 feet 1/16" or 1/8" wide \$6.00
100 feet 1/16" or 1/8" wide \$9.95

Sheets 6" x 12" — \$2.50 each
or 5 for \$9.95

Order Now
Cir-kit

Division of PHASE CORPORATION
315A Boston Avenue
Medford, Mass. 02155

KW BALUN KIT STILL ONLY \$5!

The AMIDON Toroid Balun Kit makes a modern, compact antenna transformer that can be wired for either 4:1 or 1:1 impedance ratio. The balun is ideal for use between a coaxial feedline and a balanced antenna. It reduces coax radiation and properly balances the energy for application to the antenna's feedpoint. The balun also acts as an isolation device and removes the capacity of the coax from the antenna which extends the low SWR frequency range of the array. Baluns made from this kit can be used to advantage on these antenna types: Dipole, Quad, Beam, Inverted Vee, Windom and Folded Dipole.

SEND FOR
FREE FLYER!

AMIDON
Associates



Pack & Post: 50c

12033 OTSEGO STREET • NORTH HOLLYWOOD, CALIF. 91607

Collins

Service!

Signal/One

HIGHEST QUALITY, GUARANTEED SERVICE FOR ALL
TYPES OF AMATEUR AND COMMERCIAL GEAR, ABLY
PERFORMED BY FCC LICENSED, FACTORY TRAINED
PERSONNEL, AT

Swan

BRISTOL RADIO

420 HOPE STREET, BRISTOL, R. I. 02809
401-253-7105

Clegg Inoue

Galaxy

Drake

and others

CW or RTTY, whichever way you go,
**HAL HAS TOP QUALITY
 YOU CAN AFFORD!**



TOP QUALITY RTTY... WITH THE HAL MAINLINE ST-6 TU. Only 7 HAL circuit boards (drilled G10 glass) for all features, plug-in IC sockets, and custom Thordarson transformer for both supplies, 115/230 V, 50-60 Hz. Kit without cabinet, only \$135.00; screened, punched cabinet with pre-drilled connector rails, \$35.00; boards and complete manual, \$19.50; wired and tested units, only \$280.00 (with AK-1, \$320.00).*



TOP QUALITY... WITH THE HAL 1550 ELECTRONIC KEYSER. Designed for easy operation; perfectly timed CW with optional automatic ID for sending call letters, great for DX and RTTY; TTL circuitry, transistor switching for grid block, cathode keying. Handsome rugged crackle cabinet with brushed aluminum panel. With ID, only \$90.00; without ID, \$65.00.*

OTHER HAL PRODUCTS INCLUDE:

ID-1 Repeater Identifier (wired circuit board) . . .	\$ 75.00*
ID-1 (completely assembled in 1 1/2" rack cabinet) . . .	\$115.00*
HAL ARRL FM Transmitter Kit . . .	\$ 50.00*
W3FFG SSTV Converter Kit . . .	\$ 55.00*
Mainline ST-5 TU Kit . . .	\$ 50.00*
Mainline AK-1 AFSK Kit . . .	\$ 27.50*
HAL RT-1 TU/AFSK Kit . . .	\$ 51.50*



TOP QUALITY... WITH THE HAL MKB-1 MORSE KEYBOARD.

As easy as typing a letter—you get automatic CW with variable speed and weight, internal audio oscillator with volume and tone controls, internal speaker, and audio output jack. Smooth operation; completely solid-state, TTL circuitry using G10 glass boards, regulated power supplies, and high voltage transistor switch. Optional automatic ID available. Assembled MKB-1, \$275.00; in kit form, \$175.00.*



NEW FROM HAL—TOP QUALITY RVD-1002 RTTY VIDEO DISPLAY UNIT. Revolutionary approach to amateur RTTY . . . provides visual display of received RTTY signal from any TU, at four speeds (60, 66, 75, and 100 WPM), using a TV receiver modified for video monitoring. Panasonic solid-state TV receiver/monitor, or monitor only, available. Complete, \$495.00; Panasonic TV receiver/monitor, \$160.00; monitor only, \$140.00.*

TOP QUALITY... WITH THE HAL RKB-1 TTY KEYBOARD. Gives you typewriter-easy operation with automatic letter/number shift at four speeds (60, 66, 75, and 100 WPM). Use with RVD-1002 video display system, or insert in loop of any teleprinter, for fast and easy RTTY. Completely solid state, TTL circuitry using G10 glass boards, regulated power supplies, and transistor loop switch. Optional automatic ID available. RKB-1 assembled, only \$275.00; in kit form, only \$175.00.*



HAL provides a complete line of components, semi-conductors, and IC's to fill practically any construction need. Send 24¢ to cover postage for catalog with info and photos on all HAL products available.

*Above prices do not include shipping costs. Please add 75¢ on parts orders, \$2.00 on larger kits. Shipping via UPS whenever possible; therefore, street address required.

HAL COMMUNICATIONS CORP., Box 365 H, Urbana, Illinois 618

JUGE

SELECTED RECONDITIONED ITEMS — 30-day WARRANTY

AMECO TX 62	\$ 85.00	JOHNSON VALIANT like new	\$199.95
DRAKE 2NT	125.00	NATIONAL 200 and 200AC	289.95
DRAKE TR 3 & AC	449.00	NEW NATIONAL 200AC supply	67.50
DRAKE SC-2/CPS1	69.95	RAYTRACK HOR. VI	495.00
GALAXY GT 550A & AC (demo)	547.40	SWAN 500C/SS 16 factory recond.	425.00
GONSET COMM III	99.95	SWAN 250 & AC	299.95
GONSET C.IV	135.00	UTICA 650/VFO	89.00
HAMMARLUND: HQ 170	189.00	YAESU FTV-650 new 6m transverter	119.95
HQ 170A/VHF	239.00		
HQ 180AC	299.00		

New 4-amp 14 volt DC power supply, perfect for 10-15 watt 2 meter transistor rigs, car stereo, etc. Guaranteed 1 year. \$ 19.95

2-meter FM crystals for Drake TR-22 and ML-2, Regency HR-2, HR-2S, HR-2MS, Tempo, and Swan FM 2X. All frequencies stocked on 30KHz intervals between 146.100 and 146.970, plus most MARS frequencies. One day shipment. 10 days on special order frequencies. \$ 3.95


Our specialty is service! We're open 9 to 5:30, Tuesday through Saturday, but our phone is automatically answered 24 hours per day. Call your order in any time. We accept Master Charge and Bank Americard. Stock all major ham gear and accessories. **We want your business!**

ED JUGE ELECTRONICS, INC.

3850 SOUTH FREEWAY
FORT WORTH, TEXAS 76110
Phone (817) 926-5221

GEM-QUAD FIBRE — GLASS

ANTENNA FOR 10, 15, and 20 METERS.

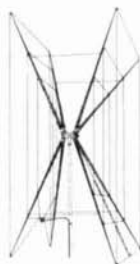

Two Elements \$107.00
Extra Elements \$60.00 ea.

Submit Payment with Order
Shipped Freight collect.

Price includes
Canadian Federal Sales Tax
or U.S. Customs Duty.

KIT COMPLETE WITH

- SPIDER
- ARMS
- WIRE
- BALUN KIT
- BOOM WHERE NEEDED

SEE OUR FULL PAGE IN MAY ISSUE

Buy two elements now — a third and fourth may be added later with little effort.

Enjoy optimum forward gain on DX, with a maximum back to front ratio and excellent side discrimination.

Get a maximum structural strength with low weight, using our "Tridetic" arms.



MANITOBA DESIGN INSTITUTE
AWARD WINNER

Structural Glass
LIMITED

Canadian Patent No. 794506
U.S. Patent No. 3532315

20 Burnett Avenue, Winnipeg 16, Manitoba, Canada

FM'ers!

Plagued by adjacent channel interference? More repeaters inevitably means increased use of 30 kHz channel spacing. You can update your receiver now simply and inexpensively with KVG's new four pole crystal filter type **XM 107S04**. You will see a vast improvement in your receiver's selectivity! The **XM 107S04** comes in an **HCG/U** can, so small that it even can be fitted in walkie talkies! Application data for tube and solid state circuits are provided with each filter.

Technical data: Frequency 10.7 MHz. Bandwidth 14 kHz min. (-6 dB), 42 kHz max. (-40 dB). Ult. attenuation 60 dB min. Insertion loss 3 dB max. Ripple 1 dB max. Input/output 910 Ohms w. 35 pF. Price only **\$15.95**

Also for 10.7 MHz: 8-pole filters for NBFM and WBFM \$35.40 each.

For 9 MHz: **SSB** (5-pole \$23.12, 8-pole \$32.85), **CW** (4-pole \$24.49, 10-pole \$65.64), **AM** (8-pole \$35.40). USB, LSB, BFO, carrier crystals \$2.75 each.

si

SPECTRUM
INTERNATIONAL
BOX 87 TOPSFIELD
MASSACHUSETTS 01983

SAROC

HELD ANNUALLY IN LAS VEGAS, NEVADA



SEE YOUR FAVORITE AMATEUR MAGAZINE FOR FURTHER DETAILS
OR WRITE

SOUTHERN NEVADA AMATEUR RADIO CLUB, INC.
P.O. BOX 73, BOULDER CITY, NEVADA 89005

FM 2 Meter UHF 6 Meter USED

GENERAL ELECTRIC . . . RCA . . . MOTOROLA

GENERAL-ELECTRIC VOICE COMMANDER III


FULL SOLID STATE FM TRANSMITTER-RECEIVER

132 to 172 MHz
Size: 9.5" x 5.3" x 1.7"

1 WATT OUTPUT
1/2 MICRO-VOLT SENSITIVITY

High performance, completely self-contained two-way FM radio. Compact, lightweight, easily operated and hand-carried. Housed in high-impact 2-section case. All external hardware polished stainless steel.

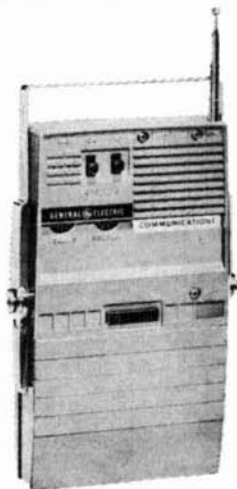Top section has transmitter and receiver modules, built-in mike and speaker, antenna, carrying handle, all switches and controls. Bottom section has battery power supply. Power connections to top section made by plug and jack connection.



Proper chargers available separately.

Each **\$15⁰⁰**

Includes rechargeable nickel cadmium battery pack and charger.

\$148⁰⁰

Lots of 5 less 10% - \$133.20
Lots of 10 less 15% - \$125.80

(Crystals and tuning, add \$50.)

15,000 2-way FM Mobile units in stock!
Send for new 1972 catalog.



GREGORY ELECTRONICS CORP.

The FM Used Equipment People

241 Route 46, Saddle Brook, N. J. 07662

Phone (201) 489-9000

THE FIRST OF ITS KIND!

DIGITAL AUDIO FREQUENCY METER




- * Solid State LED Display
- * LSI Circuitry
- * Crystal Time Base
- * Overload Protected
- * High Input Impedance
- * 10 Hz to 2 MHz

The Model 1200 has all the essential features required for accurate audio and broadcast frequency measurements. Direct reading to 2 MHz, indirect to 3.5 MHz, typ. Special low range allows a resolution of .1 Hz. 5 or 6 digit resolution obtainable by range switching. The input has a 20 mV sensitivity and is protected to 200 V. Crystal oscillator can be recalibrated at any time with an ordinary AM receiver. Unit completely assembled. One year warranty on parts and workmanship.

1200W Audio Frequency Meter

\$180

LR-100 SERIES

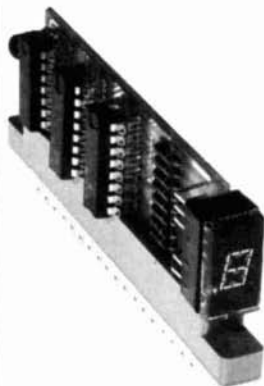

The LR-100 series counter/display modules are an excellent combination of compact size and functional versatility. They are suitable for individual projects, laboratories, prototypes, and production. TTL logic and solid state displays have been incorporated to enhance reliability. The double sided PC boards have a ground plane shield and plated conductors. All control functions are brought out to contact fingers which fit standard 18 pin connectors.

The LR-110, LR-110H, and the LR-110UD have integral latches. The first two count up at 20 and 70 MHz rates, while the latter counts up or down at a 25 MHz rate. The LR-106 contains a divide-by-6 counter for clock applications.

All LR-100 series modules require a single 5 V supply, and each board has its own decoupling. PC boards measure 1.25" x 3.1". Sockets are provided for both IC's and display. Avg. assembly time 20 min. Kits supplied with applications information.

LR-110 Decade Counter Kit	20 MHz . . .	\$16.95
LR-110H Decade Counter Kit	70 MHz . . .	18.95
LR-106 Modulo 6 Counter Kit	20 MHz . . .	14.95
LR-110UD Up/Down Decade Counter Kit	25 MHz . . .	20.95
PCC-18 PC Connector for LR-100 series95



Environmental Products

BOX 406 Lafayette, IN 47902 Ph:317-743-1893

flea market



■ **RATES** Commercial Ads 25¢ per word; non-commercial ads 10¢ per word payable in advance. No cash discounts or agency commissions allowed.

■ **COPY** No special layout or arrangements available. Material should be typewritten or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check out each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue. Deadline is 15th of second preceding month.

■ **SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

QSL'S — BROWNIE W3CJ1 — 3111B Lehigh, Allentown, Pa. 18103. Samples 10¢. Cut catalogue 25¢.

MECHANICAL FILTERS: 455Khz. 2.1Khz \$18.95, 300Hz \$22.95. J. A. Fredricks, 314 South 13th Avenue, Yakima, Washington 98902.

WORKED ALL CALIFORNIA COUNTIES award. Handsome certificate. For further details write Oakland Radio Club, 2111 E. 14th St., Oakland, California 94601.

STOLEN from CLEM MATHIAS W6NPV on January 25, 1972 from his car ONE 2 meter FM STANDARD XMITTER SRC 806M SERIAL NUMBER 102703. W6NPV, 3134 Coronado Ave., Imperial Beach, Ca. 92032.

HAMFEST — WABASH COUNTY ARC fourth annual hamfest, Sunday, May 21. Rain or shine. Admission is still only \$1. Flea-market, food, tech. talks and much more. For information write Bob Mitting, 663 Spring, Wabash, Indiana 46992.

EVANSVILLE, INDIANA HAMFEST 4H Grounds (Highway 41 North 3 miles) Sunday, May 7, 1972; airconditioned, auction, overnight camping, ladies' bingo, reserved flea market booths. Advance Registration. For flyer, contact Morton Silverman, W9GJ, 1121 Bonnie View Drive, Evansville, Ind. 47715.

WANT CLEAN COLLINS 51J4; also Drake C4; with manuals and original shipping containers. No junk! First letter give each serial number, condition, price; also price for both, if have both. Watson, 700 West Willow Street, Long Beach, CA 90806.

TV & RADIO TUBES 36¢. FREE CATALOG. Cornell, 4219 N. University, San Diego, California 92105.

NEW ELECTRONIC PARTS. Buy-Sell. Free Flyer. Large catalog \$1.00 deposit. Bigelow Electronics, Dept. HR, Bluffton, Ohio 45817.

EXCLUSIVELY HAM TELETYPE — 19th year, RTTY Journal, articles, news, DX, VHF, classified ads. Sample 30¢. \$3.00 per year. Box 837, Royal Oak, Michigan 48068.

ON FEBRUARY 3, 1972, YAESU Model FT-101 Transceiver S/N 107036, with CW filter, was stolen from the automobile of WA2YSW while parked in the driveway at his home. Please contact Frank W. Widmann, 328 Farwood Road, Haddonfield, N. J. 08033 or Officer Latham, Police Headquarters, Haddonfield, N. J. 08033, if you can provide information leading to the recovery of the equipment.

QSL'S. Second to none. Same day service. Samples 25¢. Ray, K7HLR, Box 331, Clearfield, Utah 84015.

MOULTRIE AMATEUR RADIO KLUB, 11th annual Hamfest, Wyman Park, Sullivan, Illinois, April 30, 1972, indoor-outdoor market. Ticket donation \$1.00 in advance — \$1.50 at the gate. Open 8:30 a.m. W9BIL-146.94mhz. M.A.R.K. Inc., P. O. Box 327, Mattoon, Illinois 61938.

PC BOARD MAKERS, one square foot, 1/16 G-10 copper clad laminate, \$4.95, and — cut in the size more useful for you, add 25¢ for shipping. E P G, Box 68, Somerville, Mass. 02144.

SWAN 350C wanted, with or without power supply. W6YO, 1416 7th Avenue, Delano, CA 93215.

2-METER FM INOUE IC-20, Brand New, 1 & 10 watts, solid state, 12 channel, w/xtls, w/accessories, \$235.00. Bob Brunkow, 206-747-8421, 15112 S.E. 44th, Bellevue, Washington 98006.

WARREN ARA'S FAMOUS HAMFEST, now family style, Aug. 20, Yankee Lake, Ohio. Gigantic flea market, swimming, picnicking, playground, all free. Camping available. Details: QSL W8VTD.

SELL: Hallicrafters SX-115 Receiver, Johnson 275W Matchbox/SWR, Johnson TR switch, Knight T150, PH Linear LA400c. Bud Johnson, K1HGK, 48 New Seales Road, Nashua, N. H. 03060.

TOROIDS! LOWEST PRICE ANYWHERE. 40/\$10.00 POSTPAID (5/\$2.00). Center tapped, 44 or 88mhz. 32KSR page printer, reconditioned, perfect \$225. MITE UGC41KSR page printer, reconditioned, \$250. Model 28 sprocket to friction kit, \$25. Model 15KSR, \$65. Matching RA87 P.S. unused, \$5. Sync motors, \$7. 14TD 60 speed, \$25. 14DPE tape punch, \$15. HP 200CD audio oscillator, \$75. 11/16" reperfector tape, 40/\$1.00. Model 33ASR complete \$650. Stamp for listing. Van, W2DLT, 302H Passaic, Stirling, N. J. 07980.

HELP! I'm trying to collect a ham auto license plate from each state. Please write Jim Fox, 11 Deepwood Blvd. #5, Mentor Ohio 44060.

TECH MANUALS — \$6.50 each: R-388/URR, R-389/URR, R-220/URR, URM-25D, BC-639A, BC-799B, TS-497B/URR, LM-21, BC348JNQ, SP-600JX, TS-34A/AP, OS-8E/U. W3IHD, 4905 Roanne Drive, Washington, DC 20021.

SELL: 2N2109 \$60, 2N2226 \$25, 2N1016A \$12, 1N4245 or 1N3757 4/\$1. Unused, limited qty. WA7HYW/6, Box 1111, Santa Clara, Calif. 95053.

SURPLUS MILITARY RADIOS, Electronics, Radar Parts, tons of material for the ham, free catalogue available. Sabre Industries, 1370 Sargent Avenue, Winnipeg 21, Manitoba, Canada.

TWO RCA7094 TUBES — Brand new — worth \$91 — both for \$40. KIABE, 130 Bishop Avenue, Rumford, R. I. 02916. Phone 401-438-5426.

TOROIDS, Iron powder "E", 80-10 meters Q. D. .500" eight for \$1.00, Q. D. .940 four for \$1.00. Include 25¢ postage. Fred, WA2BLE, 274 E. Mt. Pleasant Ave., Livingston, N. J. 07039.

SBE SB-36 SSB/CW Transceiver. Robyn SSB Xcvr Digital 500. Sonar FM3601 \$299.95. Regency HR-2 \$229. Galaxy FM-210 \$229.95. Standard SRC-146 \$279. Ross-White 2m FM Xcvr \$319.95. Dycomm 10-10 \$350. Hallicrafters SX-122A \$495. CAI CR-70 General coverage solid state synthesized HF rec. \$4875. Sherwood S7100 stereo rec. \$199.95. Used Galaxy V, HQ-200, GRP-90. Write to Steven Kullmer, Evergreen Inc., Dysart, Iowa 52224.

TELL YOUR FRIENDS about Ham Radio Magazine.

Buy Any 3
Take 10%
Discount!

GIANT SALE ON NEW TTL TEXAS & NATIONAL ICs

100 or more, 25% discount

Factory Guaranteed! Tested! Marked!

Type	Circuit Functions	Sale
SN7400N	Quad 2 input gate	\$0.35
SN7401N	A SN7400N, with open collector	0.35
SN7402N	Quad 2 input NOR gate	0.35
SN7404N	Hex inverter	0.35
SN7405N	Hex inverter, open collector	0.39
SN7410N	Triple 3 input NAND gate	0.35
SN7420N	Dual 4 input NAND gate	0.35
SN7430N	8 input NAND gate	0.35
SN7440N	Dual 4 input NAND buffer	0.35
SN7441N	BCD-to-decimal decoder/driver	1.35
SN7442N	BCD-to-decimal decoder	1.35
SN7446N	BCD-to-7-segment decoder/driver	1.95
SN7447N	BCD-to-7-segment decoder/driver	1.95
SN7448N	BCD-to-7-segment decoder/driver	1.95
SN7472N	J-K Master slave flip flop	0.49
SN7473N	Dual J-K Master slave flip flop	0.62
SN7474N	Dual D triggered flip flop	0.45
SN7476N	SN7473N, with preset & clear	0.62
SN7481N	16 Bit scratch pad MEMORY	1.50
SN7483N	4 Bit binary FULL ADDER	1.55
SN7490N	Decade counter	1.25
SN7491N	8 Bit shift register	1.25
SN7492N	Divide by 12 counter	1.25
SN7493N	4 Bit binary counter	1.25
SN7494N	4 Bit shift register	1.25
SN7495N	4 Bit right shift left shift reg.	1.25
SN7496N	5 Bit shift register	1.25
SN74121	One short monostable	1.00
SN74123	Dual retrig. 1s/multiv. with clear	2.50
SN74181	4 Bit arithmetic logic	7.95
SN74182	Look ahead carry generator	3.45
SN74192	Up/down decade counter	3.45
SN74193	Up/down binary counter	3.45

BRAND NEW! LINEAR IC AMPS

Factory Guaranteed! Factory Marked! Factory Tested

Type	Description	Sale
SN5510L	40Mz. Video Amp	\$3.50 3 for 9.00
702	Hi Gain, DC amp TO-5	.79 3 for 2.00
703	RF-IF, 14 hookups, TO-5	1.19 3 for 3.00
709C	Operational Amp***	.59 2 for 1.00
710C	Differential Amp***	.59 2 for 1.00
711C	Memory, Sense, Amp***	.59 2 for 1.00
723A	Voltage Regulator ***	1.49 3 for 3.75
TVR-2000	Hi-power 723 ***	1.59 3 for 3.95
741C	Freq. Comp. 709***	.95 3 for 2.50
748C	Freq. Adjustable 741***	.95 3 for 2.50
709-709	DIP 709's (DIP)	1.49 3 for 4.00
741-741	Dual 741's (DIP)	2.25 3 for 6.00
739-739	16 Transistor stereo PREAMP (DIP)	2.49 3 for 6.00
749-749	Dual channel audio amp (DIP)	2.49 3 for 6.00

*** State 1st, 2nd choice. Dual In Line, TO-5

INTEGRATED CIRCUIT SOCKETS

Buy Any 3	14-Pin, dual in line	\$.45
Take 10% Discount!	16-Pin, dual in line	.50
	TO-5, 8 or 10 pins	.29

NATIONAL LM-565 PHASE LOCK LOOP IC's

14 Pin In Line TO-5 Case \$4.95

6-AMP FULL WAVE BRIDGES		400	1.50
PIV	SALE	600	1.75
50	\$.88	800	1.95
100	.99	1000	2.25
200	1.25		

"AMATEUR" 400 MC NPN HI-POWER TRANSISTOR

Only \$2.95 Buy 3 — Take 10%

TO-60 case. Similar to 2N3632 .400 mc, 3 amps, 60 hvcb, 100 hfe 23 watts.

'SILICON' TUBES		400	1.50
SU4	600	1.75
SR4	800	1.95
866	1000	2.25

INCANDESCENT

ALPHA-NUMERIC 7-SEGMENT READOUTS 3.95

Buy any 3 — Take 10% Discount

A Poly Pak exclusive! Two different types. Both compatible with SN7446, SN7447, SN7448, SN7475, SN7490 and SN74192 IC's. Both with decimals, 0 to 9 numerals and 10 letters. With specs & hookups.

16-PIN MICRO MINIATURE

Fits into 16 pin dual in line socket. Life: 250,000 hours. Delivers 700-ft. Lamberts brightness with 5 volts 8 mils per segment. Characters .362" H. x .197" W

9-PIN TUBE TYPE

For printed circuit board or socket. Life: 100,000 hours. Delivers 6,000-ft. Lamberts with 5 volts 23 mils per segment. Characters .47" H. x .26" W.

7-SEGMENT ALPHA-NUMERIC \$6.50 LED READOUT 3 for \$18.


0-9 numbers and 9 letters. Compatible with SN7446 and SN7447 7-segment BCD IC drivers. Snaps into dual in line sockets. Only 3/4 x 1/4 x 1/8". Specs: 5V 20-mils.

FAIRCHILD "VISIBLE" LED's

Buy 3 — Take 10% Discount!



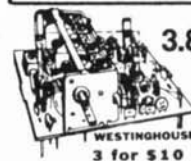79c Color: Red. For readouts, panel lights, etc. TO-18 case.



3.88

SOLID STATE AM-FM TUNER

FM 88-108MHz & AM 550-1600Kcs. Sensitive 2 3/4 x 1 1/2" module. Can be used with 10.7mc & 455Kcs IF strips & any hi-fi amp. P.C., wired. 4-gang variable supply voltage 9V 6mils. Varactor diode for AFC. Schematics.

ALLEN BRADLEY'S 'TRANSISTOR POTS

Any 2 for \$1

Type F. Screwdriver adjust.

Ohms	100	500	2.5K	20K	100K	500K
	200	1.0K	5.0K	25K	200K	1 Meg.
	250	2.0K	10K	50K	250K	2 Meg.

'MICRO-POTS' 2 for \$1

Ohms	100	1.0K	10K	100K	1 Meg.
	250	2.5K	25K	250K	2 Meg.
	500	5.0K	50K	500K	5 Meg.

EPOXY SILICON RECTIFIERS *micromini

PIV	2Amp	2Amp	3Amp
50	\$.06	\$.05	\$.08
100	.06	.06	.12
200	.07	.07	.15
400	.09	.09	.22
600	.12	.12	.28
800	.15	.15	.39
1000	.18	.18	.45

HIGH VOLT PIV 1AMP SALE

2000	1.00
3000	1.35
4000	1.65
5000	2.25
6000	2.96
8000	3.50
10000	3.95

COUNTING SYSTEM

Includes SN7490, decade counter, SN7475 latch, SN7441 BCD decoder driver, 0-to-9 Nixie tube, socket & instructions.

5-Pc. Kit
6.99

3 sets for \$18.

Terms: add postage, cod's 25%. Rated: net 30
Phone Orders: Wakefield, Mass. (617) 245-3829
Retail: 211 Albion St., Wakefield, Mass.
C.O.D.'S MAY BE PHONED IN

P.O. BOX 942H LYNNFIELD, MASS. 01940

POLY PAKS

15¢ CATALOG on Fiber Optics, 'IC's', Semi's, Parts

21st ANNUAL DAYTON HAMVENTION will be held on April 22, 1972 at Wampler's Dayton Hara Arena. Technical sessions, Exhibits, Hidden transmitter hunt, Flea market and special program for the XYL. For information write Dayton Hamvention, Dept. H, Box 44, Dayton, Ohio 45401.

VHF NOISE BLANKER — See Westcom ad in Dec. '70 and Mar. '71 Ham Radio.

WANTED: KWM2A, mint condition, details W3HZ.

TELEPHONE EQUIPMENT: New. Touch and Rotary Dial Telephones, Decoders. Special: STYLELINE Touch Dial handsets w/wall base \$49.95 if color not specified. Send SASE for catalog. Junction Distributors, 164 Cypress Lane, Nashua, N. H. 03060.

INSTANT NOISE LIMITER MODULE — Easy 20-Minute installation for Heathkit, Galaxy, Swan and most other amateur equipment; \$8.95 Postpaid. Welborn Electronics, 133 Linden Street, Henderson, Nevada 89015.

GREATER BALTIMORE HAMBOREE. Sunday, April 9 at 10 a.m. Calvert Hall College, Goucher Blvd. and LaSalle Road, Towson, Maryland 21204 (1 mile south of Exit 28 Beltway-Interstate 695), Food Service, Prizes, Flea Market, \$1.50 Admission, NO TABLE CHARGE OR PERCENTAGE.

AUTOMATIC MORSE CODE Copying Machine. Featured in Ham Radio Magazine November 1971. Copy up to 120 wpm without knowing Morse code. Simply hook to your receiver's audio and read printout. Send \$14.95 for detailed construction plans. VMG Electronics, 2138H West Sunnyside, Phoenix, Arizona 85029.

SELL: ANTIQUES! Amplifex Loop, Murdock variometer, rheostat, variable and condenser. Amplion horn speaker. Baldwin phonograph reproducer and speaker driver. All new in original cartons. W6RXW, 341 La Mesa Drive, Menlo Park, Calif. 94025.


THE "BIRMINGHAMFEST" this year will be on Sunday, May 7 at the Exhibition Hall at the Alabama State Fairgrounds near Five Points, West in Birmingham. For entertainment, prizes, contests, net meetings, eyeball QSO's and fun for the entire family, plan to attend. For further information contact the Birmingham Amateur Radio Club—W4CUE, P. O. Box 603, Birmingham, Ala. 35201.

NEW YORK STATE QSO PARTY open to all amateurs and SWL's 1700 - April 29 thru April 30 GMT 0500, 1200 - April 30 thru April 30 GMT 2359. Stations may be worked once on fone and once on CW on each band. NY stations may work other NY stations. Exchange QSO number, RS(T), QTH — Out of state stations use ARRL sections; NY stations use counties. Suggested frequencies: CW - 1810, 3560, 7060, 14060, 21060, 28060 khz. FONE - 3975, 7275, 14285, 21375, 28875 khz. NOVICE - 3725, 7175, 2114 khz. 6 and 2 meter activity encouraged. Fone activity: Try even GMT hours. Score one point per contact on 80 - 10; two (2) points for each 160, 6, or 2 meter contact; times number of NY counties or ARRL sections. LOGS must contain date and time, band, mode station worked, QSO number, QTH's. First new contact for each multiplier numbered. Stations making over 50 contacts include a check list. Multi-op stations note calls of all participating operators. Logs, comments, photos, etc. should be sent before June 1 to: LERA ARC Contest Committee, Jeff Ronner, WB2AEQ, 35 Gottlieb Dr., Pearl River, N. Y. 10965. For results sheet be sure to include a #10 size envelope (SASE).


WORLD QSL BUREAU — See ad page 107.

DIGITONE TONE CONTROL DEVICES—New improved product line of reliable, reasonably priced, compact, solid-state, plug-in modules. Decoders, logic processors, auto-patch control, 12-button "pads", other associated devices. 12 or 24-VDC operation. Application Notes/Catalog. Write Digitone, Box 73, Bellbrook, Ohio 45305.

COLOR-CODING YOUR COMPONENTS? SEE p. 58 February issue Ham Radio; \$1.00 PPD for 12 bottles of colors and thinner. Send self-addressed envelope for free specifications of twenty (house-number) IBM transistors. Cortland Electronics, Inc., 16 Hudson St., NYC 10013.



DIODES



PIV	TOP-HAT		STUD. MOUNT	
	1.5 AMP	EPOXY 1.5 AMP	EPOXY 3 AMP	6 AMP
50	.04	.06	.12	.15
100	.06	.08	.16	.20
200	.08	.10	.20	.25
400	.12	.14	.28	.50
600	.14	.16	.32	.58
800		.20	.40	.65
1000		.24	.48	.75

CAPACITORS

ALL NEW FULL AXIAL LEADS

1 Mfd @	25 Volts	5 for \$1.00
3 Mfd @	6 Volts	5 for \$1.00
5 Mfd @	15 Volts	5 for \$1.00
10 Mfd @	6 Volts	5 for \$1.00
25 Mfd @	50 Volts	5 for \$1.00
30 Mfd @	15 Volts	5 for \$1.00
80 Mfd @	2.5 Volts	5 for \$1.00
100 Mfd @	15 Volts	5 for \$1.00
250 Mfd @	30 Volts	3 for \$1.00
500 Mfd @	25 Volts	3 for \$1.00
500 Mfd @	50 Volts	40¢ ea.
800 Mfd @	20 Volts	3 for \$1.00
1000 Mfd @	12 Volts	3 for \$1.00



NEW - Panelmount Fuseholder. High Quality American Made for 3AG Fuses. All Hardware Included. 3 for \$1.00 ppd.

115 VOLT TRANSFORMER
Secondary 32-0-32 Volts at 1 Amp
Also low current 6.3 Volts Secondary for Pilot lights
\$2.50 each ppd.




1 1/2" SQUARE SPEAKER
8 Ohm V.C. Heavy Magnet. Made for Stereo Headsets. 50¢ Each ppd.



MOLDED 1/2 AMP BRIDGE RECTIFIER
1200 Volts PIV Per Leg. Ideal for P.C. Board Use. Size Approximately 1/2" Square x 3/16" Thick. \$1.00 each or 3 for \$2.50 ppd.

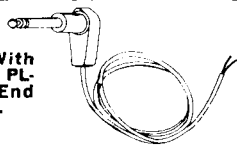HIGH QUALITY PATCH CORD
6 Foot Gray Shielded Cord With Molded Right Angle PL-55 Plug. Other End Stripped And Tinned. 75¢ Each 3 For \$2.00 ppd.



ITT 1N4002	12¢ Each ppd.
ITT 1N4004	18¢ Each ppd.
ITT 1N4007	28¢ Each ppd.
ERIE 1N270	5 For \$1.00 ppd.
GI 1N914	16 For \$1.00 ppd.
RCA - 2N3055	\$1.50 Each or 3 For \$4.00 ppd.

SEND STAMP FOR BARGAIN LIST
Pa. Residents add 6% State sales tax
ALL ITEMS PPD. USA



m. weinschenker
K 3DPJ BOX 353 · IRWIN, PA. 15642

IMPOSSIBLE? BARGAINS IN SURPLUS ELECTRONICS AND OPTICS

SANKEN HYBRID AUDIO AMPLIFIERS AND SUPPLY KIT



We have made a fortunate purchase of Sanken Audio Amplifier Hybrid Modules. With these you can build your own audio amplifiers at less than the price of discrete components. Just add a power supply, and a chassis to act as a heat sink. Brand new units, in original boxes, guaranteed by B and F, Sanken and the Sanken U.S. distributor. Available in three

sizes: 10 watts RMS (20 watts music power), 25 watts RMS (50 watts M.P.) and 50 watts RMS (100 watts M.P.) per channel. 20 page manufacturers instruction book included. Sanken amplifiers have proved so simple and reliable, that they are being used for industrial applications, such as servo amplifiers and wide band laboratory amplifiers.

- 10 Watt RMS Amplifier \$ 4.75
- 25 Watt RMS Amplifier \$14.75
- 50 Watt RMS Amplifier \$22.50
- Complete kit for 100 watt rms stereo amplifier (200 watt music) including two 50 watt Sanken hybrids, all parts, instructions, and nice 1/16" thick black anodized and punched chassis \$88.00
- Same for 50 watt rms stereo amplifier includes two 25 watt Sankens, etc. \$58.00
- Same for 20 watt rms stereo, includes two 10 watt Sankens, etc. \$30.00

SUBMINIATURE TOGGLE SWITCHES




These are nice, American made switches, of a size compatible with subminiature equipment and digital control panels. Available in two electrical configurations, conventional on-off SPDT, or on-off-on momentary SPDT. Specify which type. All brand new, at 1/3 catalog price.

- Subminiature Switches (specify on-off or momentary)
 - \$1.00 each
 - 10 for \$ 8.50
 - 100 for \$75.00

THIS MONTH'S SUPER SPECIAL!

JENSEN HIGH COMPLIANCE SPEAKER SYSTEMS

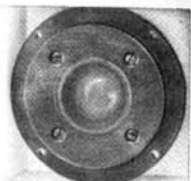

A local manufacturer went out of the speaker enclosure business, and we were lucky enough to buy his inventory of Jensen high-compliance (acoustic suspension) speaker systems. These systems consist of a 12" extended range woofer, a hemispheric dome tweeter, plus crossover. The dome tweeter response extends into the supersonic.

The dome shape provides an ideal polar pattern response. The system is ideal for use with our Sanken Amplifier Systems, or any system capable of putting out at least 20 watts rms per channel. Full instructions for cabinet construction are included.

- Single System (One Woofer, Tweeter and Crossover) . . . \$29.00
- Shipping weight 10 lbs.
- Stereo System (Two of Above) \$55.00
- Hi Compliance Woofer Only (8 lbs.) \$22.00
- Dome Tweeter only (3 lbs.) \$5.75

FEATURE ITEM!



Texas Instruments TMS-1802 "Calculator on a Chip". This is tomorrow's technology today, and at a fraction of list price. This calculator logic unit consists of a 3,520 bit read-only program memory, a 182 bit random memory, a decimal arithmetic logic unit, plus timing control, and output decoders. The


This successor of device portays the evolution of micro-computer units necessary for implementation of an 8 digit calculator in 1969 the effort required dozens of bipolar devices. By 1970 the same calculator could be produced using only four MOS LSI devices, and now it has been implemented on a single MOS LSI chip.

features are: eight digits • four operations • floating or fixed point decimal • constant or chain operations • automatic roundoff • leading zero suppression • internal keyboard encoding and debouncing • decoded display outputs • single phase clock operations • 28 pin DIP package • internal power on clear.

Every TM-1802 is a brand new Texas Instruments factory packaged, fully guaranteed unit. The only devices required to build a calculator are a battery, clock generator, keyboard, display drivers, and eight digits of display, all available from B & F. Full schematics, specifications and instructions from T.I. are included.

- Texas Instrument TMS 1802 Calculator Chip \$29.00
- Texas Instruments keyboard \$19.00
- T.I. SN25391, SN26392 Drivers, 4 required . . . 1 for \$ 3.00
- All parts for clock generator \$ 4.75
- Readouts, eight required 1 for \$ 3.50
- Complete package, except battery \$88.00

DIGITAL CLOCK KIT WITH NIXIE DISPLAY

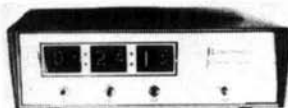

We have well over 20,000 surplus nixies in stock, and because of this bargain purchase we can sell a complete digital clock kit for less than the usual cost of the display tubes only. We provide

a complete etched and thru-plated circuit board, all integrated circuits, complete power supply, display tubes, I.C. sockets and a nice front panel with polaroid visor. We have never seen anyone offer this kit for less than \$100.00 before. Includes BCD outputs for use as with timer option. May be wired for 12 or 24 hour display. Indicates hours, minutes, seconds.

- Clock Kit, complete less outside cover \$57.50
- Aluminum blue or black anodized cover (specify) . . . \$ 4.50

To our customers:

B and F is moving to a new location: 119 Foster Street, Peabody Mass. 01960 (same address, but different building). Our apology to any customers who experienced delays in shipments during the move. Our new expanded shipping and storage areas will allow us to service your order faster than ever before. Retail customers are now welcome at all working hours (Monday through Friday, 9:55; Saturday, 9 - 3). Special few of a kind items are being cleared out, so come and visit our new location with twenty five thousand square feet of surplus bargains.

ALL ITEMS (WHERE WEIGHT IS NOT SPECIFIED)
POSTAGE PAID IN THE U. S. A.

CHARGES WELCOME!

Phone in charges to 617 531-5774 or 617 532-232: BankAmericard - Mastercharge. \$10.00 minimum. No C.O.D. please.

B. & F. ENTERPRISES

Phone (617) 532-2323

P.O. Box 44, Hathorne, Massachusetts 01937

FOR SALE: BC-610-I Transmitter. Good condx. with 6 tuning units and 6 coils. Extra tubes: 250th 1, 4-125 3, 3B28 2, 100th 3. William Lee, Rt. 2, Paxton, Illinois 60957.

"DON AND BOB" GUARANTEED BUYS. Motorola HEP170 epoxy diode 2.5A/1000PIV 39¢; MOT MC-1709CG OPAMP(709) 50¢; capacitors: Sangamo DCM600MFD/450V 4.95; computer grade 10000MFD/15V 1.95; vacuum 50PF/7.5KV 1.95; 6.3VCT/600MA transformer 1.95; Ham-M 99.00; TR44 59.95; Mosley CL33 114.00; CL36 134.00; Hy-Gain hqquad 99.00; Tri-Ex MW50 tower 229.00; Gladding 25, AC 255.00; Airdux 2408T coil 5.00; KY65 code identifier 5.95; Aluminum boomless quad mount, HDW 10.95; guaranteed used gear: 75A4 (clean) 395.00; 51J4 350.00; SX115 250.00; Tempo Kenwood dealer. Prices collect. Write quote note. Mastercharge, BAC. Warranty guaranteed. Madison Electronics, 1508 McKinney, Houston, Tx. 77002. 713/224-2668.

ASK HARRY FIRST. Good trades accepted. S.A.S.E. Name literature wanted. Harry's Amateur Radio Supply, 3528 Gaskin Rd. (Belgium) Baldwinville, NY 13027. 10AM-9PM. Closed Sunday. 315-635-7452.

FREQUENCY LISTS. We stock every callbook and frequency list published. Long wave to UHF. World Radio TV Handbook \$6.95. ITU, FBIS and EBU publications. Special receiving antennas and preselectors. Gilfer Associates, Box 249, Park Ridge, NJ 07656.

R1051/URR synthesized, digital, solid-state, triple conversion AM/CW/LSB/USB/ISB/FSK Z-30MHz. Best offer over \$500. P. O. Box 1190, Berkeley, California 94701.

EXHIBITORS — Reserve space now for ARRL Hudson Division Convention, Oct. 21-22, Tarrytown, N. Y. Contact Hank Frankel, WB2DQP, Box 535, Bellmore, N. Y. 11711. Phone 212 394-5257.

BOONTON 260A Q METER, manual, good condition \$325.00. Dumont 303A, 5in, 10MHz scope, manual \$100.00 OK. Ray Harland, Rte 1, Box 745A, Escondido, Ca. 92025.

NEW, NAME BRAND 50 OHM potentiometers linear taper, screwdriver adjustment 2 watt, .75 each; Elapsed time meters 110V 50 cycle \$5.00 each; PL 259 coax connectors 7 for \$2.00; Removed from new equipment UTC-A24 audio transformers 15K split Pri. 20/150/200/250/500/600 sec. \$5.00 each. All plus postage. Bill Hayward, WOPEM, 1307, N.E. 57th Terrace, Gladstone, Mo. 64118.

TONE ENCODERS AND DECODERS — New line of solid state encoders and decoders compatible with any sub-audible continuous tone system. Small in size, usable from 67-250 Hz, \$8.95 to \$14.95. Send for literature. Communications Specialists, Box 153, Brea, Calif. 92621.

SAVE MONEY on parts and transmitting-receiving tubes. Foreign-Domestic. Send 25¢ for giant catalog. Refunded first order. United Radio Company, 56-HR Ferry Street, Newark, N.J. 07105.

AUDIO FILTERS: Knock down that background noise. KOJO SSB, AM and CW filters do the job. Write for free brochure and see how serious DX boys hear them. KOJO, Box 7774, 741 E. Highland Ave., Phoenix, Arizona 85011.

ATTENTION "H" SERIES HANDY TALKY USERS. Solid state conversion for Motorola H Series Tube Type Receivers. Three assembled and tested circuit boards for plug-in conversion. Improved receiver sensitivity and reliability. Complete kit with instructions \$21.95. Creative Enterprises, Box 13253, Reno, Nevada 89507.

TRADE FOR SSB GEAR or antenna R391 receiver, CMC201B counter, NLS V35 digital voltmeter, EM regulated power supply 208B, HP425 DC micro-voltmeter, CV89 RTTY converter. W4OPR, Winter Park, Florida 32789.

DRAKE R4, T4, AC4, MS4. Just factory aligned and retubed \$445.00. Also Drake TC6, SC6, CPS1, \$225.00. Gordon D. Scallion, 1420 Hebron Ave., Glastonbury, Conn. 06033.

YOUR AD belongs here too. Commercial ads 25¢ per word. Non-commercial ads 10¢ per word. Commercial advertisers write for special discounts for standing ads not changed each month.

RADIATION SURVEY INSTRUMENT

Victoreen Model 710B



Measures Gamma radiation from 0.1-50 roentgens/hr. This surplus Civil Defense meter is new, guaranteed and comes with a complete manual of instructions, theory of operation, circuitry and detailed list of parts.

The 20-ua meter is calibrated in roentgens per hour, indicating the presence of gamma radiation. Three multiplier scales (Victoreen 100,000meg; 10,000meg; 1,000meg decade) matched within plus or minus 2%.

Imagine the many other uses this instrument, or its components can be put to. Wt. 3 lbs; Size 5"x4"x8 1/2" long. Includes shoulder strap.

Price \$9.95

\$10.95 With batteries

BURROUGHS NIXIE

B-7971

from discontinued read-out equipment. A fifteen segment, neon tube — all alpha and digital characters, 2 1/2" high; overall 4 1/2". Nixies carefully retested and sold on a money-back 30 day warrantee.



Price \$1.95

Socket 50¢



REED SWITCHES

SPST-no15¢
SPDT29¢



KNOB, Raytheon Spinner, 1/4"75¢

CRYSTAL, 1.000 MHz (Hoffman) 1.00

COLOR-CODING Kit, 12 bottles RETMA Colors & thinner (see Pg 58, Feb. HAM RADIO mag.)1.00



Timer, ONE HOUR, 15 Amp. Switch; big current-carrying capacity; Adjustable to 60 minutes. Size 2 x 1 3/4 x 2 3/4" long; 1/4" Shaft, w/flat; 3/4" long.1.45



Power XFMR; 240 volt, multi-tapped Regulated with 660 VAC capacitor; size 4 x 4 x 5 1/2" high; 75 W. 2.60

TWENTY CONSTRUCTION PROJECTS

If you have an electronic hobbyist among your younger friends, we have twenty simple, but interesting, do-it-yourself kits. Priced from 69¢ to \$1.95 each, with complete step-by-step, illustrated, instructions — everything included (even the solder) but no batteries or line cords. **Total cost \$20.00;** Keeps the youngsters busy and interested. Write for complete information — circuits, layouts, perf. boards, components, etc.; a post-card will do.

CORTLANDT ELECTRONICS INC.

16 HUDSON ST.

NEW YORK, N. Y. 10013

See you at the
World's Largest
Hamvention!

22 APRIL 1972

21st
ANNUAL

DAYTON HAMVENTION

WAMPLER'S HARA ARENA

Dept. H — Box 44

Dayton, Ohio 45401

TECHNICAL SESSIONS • EXHIBITS
LADIES PROGRAM • AWARDS
FLEA MARKET • TRANSMITTER HUNT
BANQUETS

A complete combined index of every article published in Ham Radio right from the first issue through December 1971.

Infinitely increases the usefulness of your Ham Radio library.

Now you can find all those great ideas we've been passing along to you each month — quickly — easily.

You asked for it!

ham radio

cumulative index

of all issues

published through

December 1971

ONLY \$1.00 POSTPAID

HAM RADIO MAGAZINE

GREENVILLE, N. H. 03048

GATEWAY ELECTRONICS

8123 PAGE AVENUE

ST. LOUIS, MISSOURI 63130

314-427-6116

DESK TELEPHONE - Modern Dial Type. Ship.
Wt. 7 lb. \$ 7.50

WALL TELEPHONE - Modern Dial Type. Ship.
Wt. 7 lb. 7.50

VARIABLE CONDENSER - 1000 pf @ 4000 v.
.125 air gap, 16" x 5 1/2" x 5 1/2". Ship. Wt.
5 lb. 10.95

DUAL VARIABLE CONDENSER - 1000 pf @
2500 v. 14 1/2" x 4 x 4. Ship. Wt. 6 lb. 10.95

TRANSFORMER 12 VOLT CENTER TAPPED @
3/4 Amp. Ship. Wt. 1 lb. 1.25

TRANSFORMER 30 VOLT CENTER TAPPED @
2 1/2 Amp. Ship. Wt. 1 1/2 lb. 2.00

TRANSFORMER 6 VOLT @ 15 Amp. 3 x 3 x 5.
Ship. Wt. 5 lb. 3.50

TRANSFORMER 12.6 VOLT CENTER TAPPED @
20 Amp. 6 1/2 x 5 x 7. Ship. Wt. 20 lb. 10.00

Minimum order \$5.00. Stop in and see us
when you're in St. Louis.

CONNECTICUT HAMS

Visit Roger Miner's Surplus Electronics, 246 Naugatuck Ave., Milford, Conn. Ph. 877-0555. Nights 7 pm to 10 pm and all day Saturday. DRAKE TR-3 W/PS-\$350. Collins 75S1 W/NBR-\$300. HEATHKIT SB-200-\$165. SB-620-\$65. OP-1 Scope-\$90. H.P. 460b Wideband amp-\$25. 210a Sq. W. Gen.-\$15. 522b-\$120. AMPEX FR-1100 Stereo tape rec.-\$350. 4-1000A Filament Trans 7.5 vac @ 42 amps, will run a pair-\$30. Amp filament chokes 3-30mcs 30 amps \$9.50. Johnson 15 amp rotary ind. 27uh-\$25. HIGH POWER HEAD-QUARTERS IN THE NORTHEAST. COME IN AND SEE US — K1DQV.

The Roger S. Miner

SURPLUS ELECTRONICS COMPANY

246 NAUGATUCK AVENUE • MILFORD, CONNECTICUT 06460

WE PAY **HIGHEST**
PRICES FOR ELECTRON
TUBES AND SEMICONDUCTORS

H & L ASSOCIATES

ELIZABETHPORT INDUSTRIAL PARK

ELIZABETH, NEW JERSEY 07206

(201) 351-4200

Semiconductor Supermart

• MOTOROLA • RCA • FAIRCHILD • NATIONAL • HEP • PLESSEY •



Actual Size

DIGITAL READOUT

At a price everyone can afford **\$3.40**

- Operates from 5 VDC
- Same as TTL and DTL
- Will last 250,000 hours.

The MINITRON readout is a miniature direct viewed incandescent filament (7-Segment) display in a 16-pin DIP with a hermetically sealed front lens. Size, and appearance are very similar to LED readouts. The big difference is in the price. Any color filter can be used.

SPECIAL OFFER

- Digital readout
- BCD to 7 — Segment Decoder/driver
- 7490 Decade Counter
- 7475 Latch

Only **\$8.40**

PLESSEY SL403D

3.5 W AUDIO AMP IC
HI-FI QUALITY

\$3.95

with 12 pages of construction data

NATIONAL DEVICES

LM370 AGC/Squelch amp	\$4.85
LM373 AM/FM/SSB IF strip/Det	\$4.85
LM309K 5V 1A regulator. If you are using TTL you need this one.	\$3.50

POPULAR IC's

MC1550 Motorola RF amp	\$1.80
CA3020 RCA 1/2 W audio	\$3.07
CA3020A RCA 1 audio	\$3.92
CA3028A RCA RF amp	\$1.77
CA3001 RCA	\$6.66
MC1306P Motorola 1/2 W audio	\$1.10
MC1350P High gain RF amp/IF amp	\$1.15
MC1357P FM IF amp Quadrature det	\$2.25
MC1496 Hard to find Bal. Mod.	\$3.25
MFC9020 Motorola 2-Watt audio	\$2.50
MFC4010 Multi-purpose wide-band amp	\$1.25
MFC8040 Low noise preamp	\$1.50
MC1303P Dual Stereo preamp	\$2.75
MC1304P FM multiplexer stereo demod	\$4.95

FETs

MPF102 JFET	\$6.00
MPF105/2N5459 JFET96
MPF107/2N5486 JFET VHF/UHF	\$1.26
MPF121 Low-cost dual gate VHF RF85
MFE3007 Dual-gate	\$1.98
40673	\$1.75
3N140 Dual-gate	\$1.95
3N141 Dual-gate	\$1.86

PLESSEY INTEGRATED CIRCUITS GREAT FOR SSB RCVRs AND XMTRS

SL610 low noise 150 MHz RF good AGC	\$5.65
SL612 low distortion IF good AGC	\$5.65
SL621 AGC generator for SSB rcvrs	\$8.30
SL620 AGC gen. SL630 Audio	\$8.30
SL630 multipurpose audio amp	\$5.35
SL640 top performing balanced mixer	\$10.88
SL641 low-noise rcvr mixer	\$10.88

SIGNETICS PHASE LOCKED LOOP

NE561B Phase Lock Loop	\$9.50
NE562B Phase Lock Loop	\$9.50
NE566V Function Generator	\$9.50
NE567V Tone Decoder	\$9.50
N5111A FM/IF Demodulator	\$2.65

PREMIUM QUALITY TEXAS INSTRUMENTS TTL IC's

7447 7-seg. decoder/driver for the digital readout.	\$2.25
7400 gates35
7441 NIXIE driver	\$1.95
7490 decade counter	\$1.40
7475 quad latch	\$1.40
7495 shift Reg.	\$2.00
7493 divide by 16	\$1.90
74121 monostable	\$1.80
7473 dual flip-flop85

MOTOROLA DIGITAL

MC724 Quad 2-input RTL Gate	\$1.00
MC788P Dual Buffer RTL	\$1.00
MC789P Hex Inverter RTL	\$1.00
MC790P Dual J-K Flip-flop	\$2.00
MC799P Dual Buffer RTL	\$1.00
MC1013P 85 MHz Flip-flop MECL	\$3.25
MC1027P 120 MHz Flip-flop MECL	\$4.50
MC1023 MECL Clock driver	\$2.50
MC4024 Dual VCO	\$3.00
MC4044 Freq. Phase Det	\$3.00

TRANSISTORS & DIODES

MPS657160
MPS A12 NPN Darlington gain 20K90
2N706 packet of 4	\$1.00
2N2218 packet of 2	\$1.00
1N4001 packet of 6	\$1.00
1N4002 packet of 6	\$1.00
1N4004 packet of 6	\$1.00

Please add 35¢ for shipping

CIRCUIT SPECIALISTS CO.

Box 3047, Scottsdale, AZ 85257

FACTORY AUTHORIZED
HEP-CIRCUIT-STIK
DISTRIBUTOR



**Radio Amateurs
Reference Library
of Maps and Atlas**

WORLD PREFIX MAP — Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables postpaid \$1.25

RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles. postpaid \$1.25

RADIO AMATEURS MAP OF NORTH AMERICA! Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus informative information on each of the 50 United States and other Countries. postpaid \$1.25

WORLD ATLAS — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages, size 8 3/4" x 12" postpaid \$2.00

Complete reference library of maps — set of 4 as listed above postpaid \$3.50
See your favorite dealer or order direct.

WRITE FOR FREE BROCHURE! RADIO AMATEUR **callbook** INC.
Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

Many thousands of you have become very familiar with the various Radio Society of Great Britain books and handbooks, but very few of you are familiar with their excellent magazine, **Radio Communication**.

It includes numerous technical and construction articles in addition to a complete rundown on the month's events in amateur radio. Surely a most interesting addition to your amateur radio activities.

We can now offer this fine magazine to you along with the other advantages of membership in the RSGB (such as use of their outgoing QSL Bureau) for \$9.95 a year.

comtec

Greenville, New Hampshire 03048

2 METER PREAMP

More Gain, Less Noise For The Money!

20 DB GAIN

NOISE FIGURE 2.5

12 VDC OPERATION

Small Size: 1 1/4 x 2 1/4 x 1/2 - Only \$12.50

Kit \$9.50

Option for 150-250 VDC Operation - \$1.00



DATA ENGINEERING INC.
Box 1245 Springfield, Va. 22151

NEW 2M PREAMPLIFIER

12 vdc powered

27 db gain (approximately)

noise figure 2.5

will bring most receivers

to .1 μV sensitivity

without appreciable noise.

Metal case. ONLY \$17.95 ppd.

CRAWFORD ELECTRONICS

302 West Main, Genoa, IL 60135

AMERICAN CRYSTAL CO.

1623 Central Ave., Kansas City KS 66102, 913-342-5493
Mfg. Crystals for most communication Equip.

Small Orders Accepted

For use in:	Crystal prices @ .002%
TWO WAY	FUNDAMENTALS
SCANNERS	2 to 14.9Mhz \$5.25
MONITORS	15 to 19.9Mhz 6.10
TRANSMITTERS	THIRD MODE
C.B. SYNTHESIZERS	10 to 44.9Mhz 5.35
REPEATERS	45 to 55.9Mhz 6.10
SCANNERS (oper. 152.50 to 163.50 Mhz .002%)	\$5.00
ELEMENT CRYSTALS .0005%	
(channel freq. changed in customer's element)	15.00
C.B. (Class D Single channel)	2.75
AMATEUR NOVICE, (HC6/U, ±1 kc, 32 mmF, Fund.	
3.5-8.9 Mhz	3.00
Extras: Oven use \$1.50, Subminiature 25¢, .093 pins 10¢	
Postage 1-2 crystals 2 oz. each additional 1-2 crystals 1 oz.	
Write for quantity discount	



FACTORY FRESH SEMICONDUCTOR BARGAINS
SN7400N DIP SERIES TTL: 7400, 7401, 7402, 7403, 7404, 7410, 7420, 7430, 7440, 7451 & 7454 gates 30¢;
7441A Nixi Driver \$1.60; 7442 BCD-Decimal \$1.50;
7447 7 Segment Driver \$1.79; 7472 F-F 50¢; 7473 Dual F-F 60¢; 7474 Dual F-F 60¢; 7475 Quad Latch \$1.25;
7476 Dual F-F 65¢; 7490 Decade Counter \$1.25; 7492 Twelve Counter \$1.25; 7493 4 Bit Counter \$1.25; 7495 Shift Reg. \$1.50; 74107 Dual F-F 65¢; 74121 Monostable 75¢.

LINEAR IC'S:
709C DIP or TO-5 50¢, 10 for \$4.50
741C DIP or TO-5 62¢, 10 for \$5.75
723C Voltage Regulator TO-5 \$1.35
NE565A Signetics PLL DIP \$6.00
TRANSISTORS (General Purpose)
2N5134 Silicon NPN 15¢, 8 for \$1.00
2N5138 Silicon PNP 15¢, 8 for \$1.00
RECTIFIERS (Silicon Epoxy)
1N4001 1 AMP 50 PIV, 1N4002 1 AMP 100 PIV, 1N4004 1 AMP 400 PIV: 10 for \$1.00, 100 for \$7.50
Discounts offered on large orders. Many other parts are available. Free catalog. Orders less than \$10.00 add 25¢ handling. Over \$10.00 postpaid.

DIGI-KEY

P.O. BOX 126, THIEF RIVER FALLS, MN 56701



FIRE & BURGLAR ALARMS

1971 Handbook & Catalog

Save
Hundreds
of
Dollars

Professional equipment from famous manufacturers. Easy step by step illustrated instructions, no special tools required. Save up to 75%. This handbook is a must for every homeowner and businessman. Just \$1 cash, check or M.O.

Write W1JFT

ALARM COMPONENT DISTRIBUTORS

33 NEW HAVEN AVE., DEPT. HR
MILFORD, CONN. 06460

BROADBAND AMPLIFIERS at a price you can afford



The BBA-1 series offer high gain over the HF to UHF region with Noise Figures as low as 3dB max. BBA-1PB covers 30 to 400 MHz with 17dB. ± 1 dB gain and 3.2dB maximum Noise Figure. The BBA-1P covers 3 to 500 MHz with gain between 15 and 30dB, and maximum Noise Figure of 3.0 dB. For less critical use order

the BBA-1 which has the same coverage as the BBA-1P but with slightly reduced UHF gain and higher Noise Figure. They are all a bargain! BBA-1PB, BBA-1P - \$45.00, BBA-1 - \$30.00 FOB Baltimore

RADIATION DEVICES CO.

P.O. Box 8450, Baltimore, Md. 21234

WORLD QSL BUREAU

THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next country, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 5¢ each.

5200 Panama Ave., Richmond, CA USA 94804

SPACE-AGE TV CAMERA KITS & PLANS



BE A PIONEER IN HOME TELECASTING! Build your own TV CAMERA. Model XT-1A Series D, \$116.95 pp. Solid-State. Step-by-step construction manual. High quality. Connects to any TV without modification. Ideal for hobby, experimenters, education, industry, etc.

PHONE or WRITE for CATALOG.

DIAL 402-987-3771

Many other kits, parts and plans available including starter kits, focus/dell. coils, vidicon tubes, const. plans, etc.

1301 BROADWAY, NW. **ATV Research** DAKOTA CITY, NEBR. 68731

FREE CATALOG

HARD-TO-FIND PRECISION TOOLS

Lists more than 1700 items—pliers, tweezers, wire strippers, vacuum systems, relay tools, optical equipment, tool kits and cases. Also includes four pages of useful "Tool Tips" to aid in tool selection.



JENSEN TOOLS AND ALLOYS

4117 N. 44th Street, Phoenix, Arizona 85018

NEW GLADDING 25

FM TRANSCIVER, 25 WATTS OUTPUT, 6 channels complete with xtals for 146.34/146.76 and 146.94/146.94, low power position, completely separate xmit-rec tctal switching. (Amateur net \$249.95) OUR LOW INTRODUCTORY PRICE \$212.50. With matching AC supply (reg. \$299.95) \$255.00. Write for literature. Ham-M's \$99.00.

AMATEUR-WHOLESALE ELECTRONICS
8817 S.W., 129 Terrace, Miami, FL 33156, 305-233-3631

KW

ELECTRONICS
LIMITED

The KW2000B
the transceiver
with 160Meters

\$699 with spkr
and AC pwr supply



NOW in the USA

KW Electronics

DIVISION OF SYSTEMS Inc

10 Peru St., Plattsburg, N.Y. 12901

USED TEST EQUIPMENT

All checked and operating unless otherwise noted, FOB Monroe. Money back (less shipping) if not satisfied.

Gen. Microwave 550 - WWV rcvr-comparator	105
Gertsch FM-7-Freq.-mtr.20-1000MHz .0001%	650
GR1100AP - Freq. Standard, includes 1101A osc., 1102A multivib., 1103A Synchronometer and PS complete	350
HP160B(USM105)-14MHz dual trace scope	525
HP175A - 50MHz scope w/dual trace, delayed sweep plug-ins	975
HP185B-DC-1gHz sampling scope	186B
HP524D-Freq. counter 10Hz-10MHz	495
HP525A-10-100MHz plug-in for above	65
HP540B-Trans.Osc.for counter-to 12gHz	410
HP2590B-Precision Trans. osc-synchronizer	950
Kintel 301-DC standard-null voltmeter	235
Meas. 80 - Standard Sig. Gen. 2-400mHz	225
Meas 82-Stand sig.gen. 20Hz-50mHz	275
NE 14-20C-Freq.counter (sim. HP524C)	209
NE 14-21C-10-100MHz plug-in for above	65
NE 14-22C-100-220MHz plug-in for above	80
NLS M-24-Digital Volt-ratio-ohmmeter	585
NLS V-35 - Digital Voltmeter complete	385
Polarad R-microwave rcvr (plug-ins avail)	275
Polarad TSA-spectrum analyzer 10MHz-44gHz (plug-ins available)	325
Polarad SA84W-spectrum analyzer, band switching 10MHz-41gHz	1260
Rollin 30-Stand.sig.gen.40-400MHz-hi-pwr.	585
ME26D/U-(HP410B) VTVM-to 700mHz	85
TS-403A-Sig. Gen. (HP616) 1.8-4gHz	385
URM26-Stand. Sig.Gen. 3-410mHz	225
USM-16-Stand. Sig.Gen.10-440mHz AM-CW-FM-Pulse-Sweep, Phase-locked osc.	675
Tek RM15-DC-15mHz GP scope	465
Tek B-scope plug-in-hi-gain, 30mHz	40

(Send SASE for complete list)

GRAY Electronics

P. O. Box 941 Monroe, MI 48161

Specializing in used test equipment

BRAND NEW FREQ-SHIFT TTY MONITOR
 NAVY OCT-3: FM Receiver type, freq. range 1 to 26 MHz
 in 4 bands, cont. tuning. Crystal calib. Reads up to 1500 Hz
 deviation on built-in VTVM. Cost \$110.00 each! In
 original box, with instruct. book & cord, fob Mariposa, Cal.
 Shpg. wt. 110 lbs. 49.50

HIGH-SENSITIVITY WIDE-BAND RECEIVER
 COMMUNICATIONS • BUG DETECTION
 SPECTRUM STUDIES

38-1000 MHz AN/ALR-5: Consists of brand new tuner/
 converter CV-253/ALR in original factory pack and an exc.
 used, checked OK & grtd main receiver R-444 modified for
 120 v, 50/60 Hz. The tuner covers the range in 4 bands:
 each band has its own Type N Ant. input. Packed with each
 tuner is the factory inspector's checkout sheet. The one we
 opened showed SENSITIVITY: 1.1 uv at 38.4 mhz, 0.9 at
 133 mhz, 5 at 538 mhz, 4 1/2 at 778 mhz, 7 at 1 ghz. The
 receiver is actually a 30 mhz IF ampl. with all that follows,
 including a diode meter for relative signal strengths: an
 atten. calibrated in 6 db steps to -74 db, followed by an
 AVC position; Pan., Video & AF outputs; switch select pass
 of ± 200 kHz or ± 2 mhz; and SELECT AM or FM! With
 Handbook & pwr. input plug, all only 375.00

We have SP-600-JX, R390, WRR-2 Receivers. Ask!

REG. PWR. SPLY FOR COMMAND, LM, ETC.

PP-106/U: Metered. Knob-adjustable 90-270 v up to 80 ma
 dc; also select an AC of 6.3 v 5A, or 12.6 v 2 1/2 A or 28 v
 2 1/2 A. With mating output plug & all tech. cata. Shpg. wt.
 50 lbs. 19.50

BARGAINS WHICH THE ABOVE WILL POWER:

LM-(1/2) Freq. Meter: 125-20 MHz, .01%, CW or AM, with
 serial-matched calib. book, tech. data, mating plug. Shipping
 wt. 16 lbs. 57.50
 TS-323 Freq. Meter: 20-480 MHz, .001% 169.50
 R22A/ARC5 Command Q-5er 190-550 kHz, exc. cond. 16.95
 A.R.C. R22 Command rcvr 540-1600 KHz, exc. cond. 17.95
 A.R.C. R15(MIL R-509)Command. 108-135 MHz, new 27.50

NEMS-CLARKE #1670 FM Rcvr 55-260 MHz 475.00
 like new 250.00
 WWV Rcvr/Comparator 2 1/2 - 20 MHz, solid state 250.00
 Empire Devices NF-114 RF1 meter is a red-hot receiver
 from 150 KHz to 80 MHz 295.00
 Spectrum Analyzer Give-Away: Polarad TSA with STU-1
 head: 10-1000 MHz. Looks good, sold as-is 350.00
 Overhauled & Certified 495.00

Attention Buyers, Engineers, Advanced Technicians: We have
 the best test-equipment & oscilloscope inventory in the
 country so ask for your needs . . . don't ask for an overall
 catalog . . . we also buy, so tell us what you have.

R. E. GOODHEART CO. INC.
 Box 1220-HR, Beverly Hills, Calif. 90213
 Phone: Area Code 213, Office 272-5707

signal/one CX-7A

160 - 10 meters • 300 watts • trans-
 ceiver or split freq. w/two built in VFO's •
 CW keyer built in • notch filter • I-F noise
 blanker • digital nixie frequency readout •
 superb computer grade construction by Com-
 puter Meas., Inc. • \$2195 • THE incomparable
 prestige transceiver • Write for brochure
 and THE BEST DEAL ANYWHERE •

AMATEUR-WHOLESALE ELECTRONICS
 8817 S.W., 129 Terrace, Miami, FL 33156, 305-233-3631

A New Magazine?

Not really. New in the U.S.A. perhaps,
 but very well known in Great Britain and
 now being offered to you here.

RADIO CONSTRUCTOR is almost exclu-
 sively construction material. Clearly writ-
 ten, concise articles give you full details
 on:

- Audio Construction Projects
 - Receiver Construction Projects
 - Transmitter Construction Projects
 - Test Equipment Projects
 - Radio Control Projects
- ... and much more

Try a subscription to this interesting
 magazine, we are sure that you will not
 be disappointed.

ONE YEAR SUBSCRIPTION — \$7.00

Write
RADIO CONSTRUCTOR
 Greenville, N. H. 03048

Central New York Specialty Headquarters
FM by STANDARD COMMUNICATIONS
 High Power by EHRHORN
 Quality-Selected Used Ham Gear

Write for listing, updated twice monthly

CFP ENTERPRISES
 10 Graham Road West
 Ithaca, New York 14850
 607-257-1575

TOROIDS — TELETYPE

Lowest Prices Anywhere!

44 or 68 mhz
 TOROIDS \$10 FOR 40

MODEL 15-19
 60 W.P.M. GEAR SET
 (74912-74913) \$3.50

FRESH RIBBONS
 FIT ALL MODELS 14-15
 19-20-32-33 \$3.50 BOX OF 12

MANY OTHER BARGAINS—SEND FOR CATALOG



Van's W2DLT Electronics
 302 Passaic Avenue
 Stirling, N. J. 07980
 CALL 201-647-3325

QSOs
 EN
 ESPANOL

Special
 Any Course on 5" reel
 \$9
 (check)
 Spanish
 German
 Japanese

QSOs
 AUF
 DEUTSCH

Courses in Spanish, German, and Japanese designed
 for amateurs. Enables hams to exchange greeting
 and signal reports and to chat with foreign hams.
 Each course has many typical QSO's, technical terms,
 and slang. Narrated by native speakers.

Spanish course: 75 minutes Spanish dialogue with
 English-Spanish manual taped on 7" reel 3 1/4 IPS for
 \$11.95, on C-90 Cassette \$10.95. For German course
 running 90 mins. add \$2 to above prices. Japanese
 course 30 mins. same prices as Spanish course. Dual
 language manuals alone \$2.50. Mailed 3rd class in
 U.S. PPD. Send checks to:

Foreign Language QSOs, Box 53, Acton, Mass. 01720




220 MHz

Join the action on 220MHz with the JANEL deluxe receiving converters and preamps. Extremely sensitive with freedom from spurious responses.

220CA Converter, 28-32 MHz i-f, \$69.95 ppd
220PA Preamp, 2.5 dB NF, \$19.95 ppd
Write for full details. Other models available for 50, 144, and 432 MHz.

P. O. BOX 112
SUCCASUNNA, N. J.
07876
(201) 584-6521

JANEL LABORATORIES

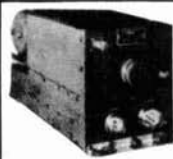

ARC R-19 (R-508) Receiver 118-148 MHz tunable, 9 tube Superheterodyne AM Receiver. If 15 MHz checked out with schematic, \$14.95. Blower 115 VAC 60 CPS 1PH. 20 CFM 3400 RPM, \$4.95. Teletype Tape 3/8 canary, 10 rolls \$1.25. New catalogue now available 10¢

FRANK ELECTRONICS
407 Ritter Road, Harrisburg, Pa. 17109

SPACE ELECTRONICS division of MILITARY ELECTRONICS CORP. WANTS TO BUY

All types of military electronic equipment and parts. Call collect for cash offer.

76 Brookside Drive, Upper Saddle River
New Jersey 07458 • (201) 327-7640

COMPUTER BOARDS, CORE MEMORY MATS, IC'S and HOME EXPERIMENTER'S ELECTRONIC COMPONENTS ALL AT TRUE BARGAIN PRICES. SEND 10c FOR LATEST CATALOG. **TRI-TEK**, P.O. BOX 14206, PHOENIX, AZ. 85031

NEW-HEAVY DUTY ANTENNA BALUN.

1:1 or 1:4 ratio, 2KW power input, 3-30MHZ. silver plated 2KV teflon insulated wire for lower loss and higher voltage capability, makes "tuned line" operation possible. Encapsulated, replaces center insulator, with coax connector input.

Specify Desired Ratio \$8.95 PPD, USA
Gregory Kordes — Box 1279, Tustin, Calif. 92680

FREE ALARM CATALOG

64 PAGES FILLED WITH 350 BURGLAR AND FIRE ALARM PRODUCTS FOR INSTALLERS AND ELECTRONIC TECHNICIANS. INCLUDES RADAR, INFRARED, CONTROLS, HARD-TO-FIND PARTS, AND 6 PAGES OF APPLICATION NOTES.




mountain west alarm
4215 n. 16th st., phoenix, az. 85016



TELEGRAPHERS WANTED - For membership in Morse Telegraph Club, Inc.

Non-profit - Historical - Fraternal
Includes subscription to dots & Dashes
Dues \$2 per annum

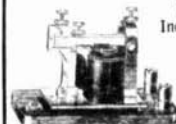Write: James E. Smith, GS&T
P.O. Box 70
LaMirada, Ca 90638



TYMETER

Time At A Glance
DIGITAL CLOCKS



24 HOUR CLOCK

CALL-IDENT 10-MINUTE STATION CALL REMINDER

#124

23⁵⁰

Made in U.S.A.



10-minute repeating timer buzzes warning to sign in your call letters. Walnut or ebony plastic case. 4" H, 7 3/4" W, 4" D. 110V, 60 cy. One Year Guarantee. Made in U.S.A.

At Your Dealer, or DIRECT FROM


PENNWOOD NUMECHRON CO.

TYMETER ELECTRONICS

7249 FRANKSTOWN AVE


PITTSBURGH PA 15208

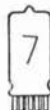AMPEREX
READOUT
TUBE
Brand new
\$3.00 ea.
10/\$25.00



COUNTING
PACKAGE
Amperex Tube
SN 7490
SN 74141
All above \$6.75

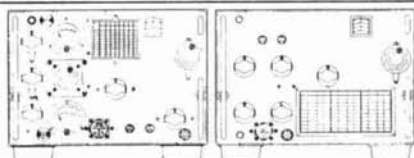Giant Alpha-Numeric Neon Readout. Complete alphabet plus all digits, 15 segments, 2 1/2" high. \$3.00 each, 10 for \$25.00. Sockets available at 50¢ each.



TCS — Collins Design: 1.5 thru 12 mcs. 4 channel crystal or tuneable, voice or CW. Receiver is fine for general short wave listening. Transmitter is excellent for the Ham, Novice, CD, etc. First class condition, with schematic and power supply info. \$40.00 each unit or \$75.00 the pair.

3 WATT LASER DIODE TA-2628 \$5.00
PANADAPTER BC 1031 Used \$45, unused w/spares \$75
56K MEMORY CORE STACK \$100
LASER DISCHARGE CAP 40 uf 3 KV 180 JOULES \$10
COMPUTER GRADE CAPS 1000 uf 450V \$1.50 ea. 10/\$12

Please add postage for above items.
Send 25¢ for Surplus Catalog . . .

JOHN MESHNA JR. ELECTRONICS
P.O. Box 62 E. Lynn, Mass. 01904

Advertisers check-off

... for literature, in a hurry —
we'll rush your name to the companies
whose names you "check-off"

INDEX

- ATV
- Aerometric
- Alarm
- Allied
- Amateur Wholesale
- American Crystal
- Amidon
- Andy
- B & F
- Babylon
- B & W
- Barry
- Bitcil
- Bristol
- CFP
- Centralab
- Cir-Kit
- Circuit Specialists
- Communications World
- Cortland
- Crystek
- Crawford
- Curtis
- Cushcraft
- DX
- Dale
- Data
- Dayton Hamvention
- Digi-Key
- Drake
- Dycomm
- Eastron
- Eimac
- Environmental
- Foreign Language
- Frank
- Gateway
- Gray
- Gregory
- H & L
- HAL
- Hallicrafters
- Ham Radio Center
- Henry
- Hy-Gain
- International Crystal
- Jan
- Janel
- Jensen
- Juge
- Justin
- KW
- Kordes
- L A
- Lee
- Linear
- Lynch
- Meshna
- Micro-Z
- Mini-Products
- Morse
- Motorola
- Mountain West
- Palomar
- Payne
- Pennwood
- Poly Paks
- R P
- R & R
- Radiation
- Callbook
- Radio Constructor
- Randall
- Regency
- Robot
- Rochester
- SAROC
- Savoy
- Signal/One
- Siliconix
- Space Military
- Spectronics
- Spectrum
- Standard
- Structural Glass
- Surplus
- Swan
- Ten-Tec
- Topeka
- Tri-Rio
- Tri-Tek
- Van
- Vanguard
- Weinschenker
- Wolf
- World
- Worldradio

April 1972

Please use before May 31, 1972

Tear off and mail to
HAM RADIO MAGAZINE — "check-off"
Greenville, N. H. 03048

NAME.....
CALL.....
STREET.....
CITY.....
STATE..... ZIP.....

Advertisers iNdex

ATV Research	107
Alarm Component Distributors	107
Amateur Electronics Supply	5, 27, 76
Amateur Wholesale Electronics	107, 108
American Crystal Co.	106
Amidon Associates	94
Andy Electronics	86
B & F Electronics	102
Babylon Electronics	78
Barker & Williamson	112
Barry Electronics	84
Bitcil Systems, Inc.	87
Bristol Radio	94
CFP Enterprises	108
Cir-Kit	94
Circuit Specialists	105
Communications World	94
Cortland Electronics, Inc.	103
Crystek	90
Crawford Electronics	106
Curtis Electro Devices	88
Cushcraft Corp.	86
DX Engineering	92
Dale Electronics Corp.	90
Data Engineering	82, 106
Dayton Hamvention	104
Digi-Key	106
Drake Co., R. L.	2
Dynamic Communications, Inc.	89
Eastron Corp.	88
Eimac Division of Varian	Cover IV
Environmental Products	98
Foreign Language QSO's	108
Frank Electronics	109
Gateway Electronics Corporation	104
Goodheart Co., Inc. R. E.	108
Gray Electronics	107
Gregory Electronics	97
H & L Associates	104
HAL Communications Corp.	95
Hallicrafters Co., The	Cover II
Ham Radio Center	92
Henry Radio	Cover III
Hy-Gain Electronics Corp.	23, 67, 85, 91
International Crystal Manufacturing Co.	93
Jan Crystals	82
Janel Labs	109
Jensen Tools & Alloys	107
Juge Electronics, Inc.	96
Justin, Inc.	82
KW Electronics	107
Kordes, Gregory	109
LA Electronic Sales	79, 111
Lee Electronic Labs Co.	90
Linear Systems, Inc.	71
Lynch Co., J.	88
Meshna, John, Jr.	109
Micro-Z Co.	88
Mini-Products, Inc.	15
Morse Telegraphers	109
Mountain West Alarm	109
Palomar Engineers	86
Payne Radio	88
Pennwood Numechron Co.	109
Poly Paks	100
RP Electronics	84
R & R Electronics	83
Radiation Devices	107
Radio Amateur Callbook, Inc.	80, 106
Radio Constructor	108
Randall, Douglas, Division	81
Robot Research	77
Rochester Hamfest	90
SAROC	96
Savoy Electronics, Inc.	31
Signal/One	56, 57
Space-Military Electronics	109
Spectronics	63
Spectrum International	96
Standard Communications Corp.	1
Structural Glass Ltd.	96
Surplus Electronics	104
Swan Electronics	35
Ten-Tec, Inc.	51
Topeka FM Engineering	92
Tri-Rio Electronics	92
Tri-Tek, Inc.	109
Van	108
Vanguard Labs	84
Weinschenker, M.	101
Wolf, S.	94
World QSL	107

A "broadband" isn't an all girl orchestra.

ITS A BALUN FROM LA-TRONIX

SPECIFICATIONS

Bandwidth 3 through 30 MHz Continuous
VSWR 1:1 (when terminated with a
balanced 52 ohm load)
Power Rating 1 kw DC
Impedance Ratio 1:1 at 52 ohms
Input Connector SO-239



Mod. LA-BN330

IMPROVE YOUR ANTENNA PATTERN
AND REDUCE TVI.....FOR ONLY



\$11.77

WANTED! CLEAN DRAKE GEAR

REWARD:

* MUST BE CLEAN, IN GOOD OPERATING CONDITION WITH MANUALS

\$ 195.00	→	FOR YOUR 2B ON A NEW R4B	@	\$ 475.00
\$ 220.00	→	FOR YOUR R4 ON A NEW R4B	@	\$ 475.00
\$ 275.00	→	FOR YOUR R4A ON A NEW R4B	@	\$ 475.00
\$ 285.00	→	FOR YOUR T4X ON A NEW T4XB	@	\$ 495.00
\$ 400.00	→	FOR YOUR TR4 ON A NEW TR4	@	\$ 599.00

**COLLECT YOUR
REWARD FROM**



Electronix Sales

23044 S. CRENSHAW BLVD., TORRANCE, CALIF. 90505
Phone: (213) 534-4456 or (213) 534-4402

B&W**BARKER & WILLIAMSON, INC.**

CANAL STREET, BRISTOL, PENNA. 19007



Dummy Load/Wattmeter
Model 334A
Freq. range: 0-230 MHz
Load Impedance: 52 ohms
4 Calibrated Scales:
0-10w 0-300w
0-100w 0-1000w
Price—\$149.95



Hybrid Phone
Patch Model 3002W
with built in
compression amp.
Price—\$99.95



Automatic Keyer Model 361
provides automatic timing
& spacing of speeds from
5-50 wpm
Price—\$69.95




Clipream Model 372
A preamplifier/clipper to
increase your talk power
without exceeding FCC
legal limits or transmitter
design.
Price—\$19.95

MINIDUCTORS—COILS**SPECIFICATION**

Model	Coil Diam.	Turns per Inch	Length	Inductance (Approx.)	Consumer Net Prices
3001	1/2"	4	2"	.40	1.20
3002	1/2"	8	2"	.96	1.26
3003	1/2"	16	2"	3.2	1.38
3004	1/2"	32	2"	13.7	1.43
3005	3/8"	4	2"	.56	1.20
3006	3/8"	8	2"	1.4	1.26
3007	3/8"	16	2"	4.9	1.38
3008	3/8"	32	2"	19.2	1.43
3009	3/8"	4	3"	.94	1.31
3010	3/8"	8	3"	2.9	1.50
3011	3/8"	16	3"	10.9	1.56
3012	3/8"	32	3"	42.5	1.76
3013	1"	4	3"	1.9	1.34
3014	1"	8	3"	4.8	1.46
3015	1"	16	3"	19.9	1.59
3016	1"	32	3"	73.0	1.71
3017	1 1/4"	4	4"	2.56	1.38

**SPECIFICATION**

Model	Coil Diam.	Turns per Inch	Length	Inductance (Approx.)	Consumer Net Prices
3018	1 1/4"	8	4"	9.4	1.64
3019	1 1/4"	16	4"	37.5	1.95
3020	1 1/4"	32	4"	145	2.07
3021	1 3/8"	4	4"	4.5	1.64
3022	1 3/8"	8	4"	17.2	1.70
3023	1 3/8"	16	4"	72.0	2.00
3024	1 3/8"	32	4"	280	2.13
3025	2"	6	10"	33	3.53
3026	2"	8	10"	60	3.42
3027	2"	10	10"	92	3.38
3029	2 1/2"	6	10"	52	4.05
3030	2 1/2"	8	10"	92	3.86
3031	2 1/2"	10	10"	142	3.60
3033	3"	6	10"	74	4.91
3034	3"	8	10"	135	4.71
3035	3"	10	10"	200	4.67

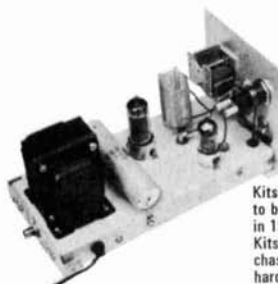ARRL PROJECT KITS

Kits include all components to build projects described in 1971 ARRL Handbook. Kits do not include metal, chassis, batteries or hardware.

Other Models Available

Other Models Available	B&W Kit No.	Price
ARRL "Novice Special Transmitter"	A111	\$59.95
"10 Watt One Tube Transmitter"	A112	69.95
"R.F. Actuated C.W. Monitor"	A113	19.95
"A 75-120 Watt C.W. Transmitter"	A114	85.00
"Matching Indicator For Low Power"	A115	17.95
"Q.R.P. Rig For 3.5 and 7 MHz"	A116	29.50
"Front End Overload Protection"	A117	8.25
"Transistorized VOX"	A118	39.95
"An FM Pip Squeak For 2 Meters"	A119	56.00
"All Band Electronic T.R. Switch"	A120	27.50
"Low Noise Converter For 50 MHz"	A121	43.50
"Low Noise Converter 144 MHz"	A122	48.50
"Trap Antenna"	A124	21.50
"Two Broad Band Toroidal Balun"	A125	10.95
"Wide Range Transmission Line Coupler"	A126	89.65



Filament Choke—FC15,
15 amp, 80-10 meters
Price—\$19.95
FC30, 30 amp, 80-10
meters
Price—\$23.95



R. F. & Antenna Coax
Switches Model 550A
SP—5 Pos.
Price—\$10.95
Coax Switch Model 550A-2
SP—2 Pos.
Price—\$7.43



TVI Filter Model 424,
100w, 80-10 meters
Price—\$10.88
Model 425 1000W—
80-10 meters
Price—\$24.95



Weatherproof dipole
center connector
Model CC-50
Price—\$4.95

TEMPO...a quality name...a growing family



TEMPO "2000" LINEAR AMPLIFIER

The Tempo "2000" Amplifier makes an ideal supplement to the Tempo "ONE" Transceiver. It is the smallest self-contained, full-legal-limit kilowatt amplifier in its price range. It has an entirely self-contained, solid-state power supply that makes it fully operational within three seconds from turn-on.

Price: \$395.00.

TEMPO "ONE"

SSB TRANSCEIVER

.....represents the culminating achievement of many years of experience in the amateur radio field. Modern design, superb performance, high styling, sturdy construction, outstanding reliability, exceptional value.



Tempo "ONE" Transceiver \$319.00

AC/ONE Power Supply (117/230 Volt 50/60 cycle) \$99.00

DC/1-A Power supply (12 volts DC) \$110.00

TEMPO DKT ELECTRONIC KEYS



The Tempo DKT keyer is the latest in electronic keyer design. Using integrated circuit techniques it provides the unique features of dot memory and single dot injection which, with a specially designed twin lever key assembly, affords effortless sending and perfect character formation regardless of speed.

Price: \$89.00.



TEMPO FMP

Truly mobile, the Tempo fmp-3 watt portable gives amateurs 3 watts, or a battery saving 1/2 watt, FM talk power anyplace at anytime. With a leather carrying case included, this little transceiver will operate in the field, in a car, or at home with an accessory AC power supply. The battery pack is of course included. Price: \$225.00.

TEMPO LW 1500 DUMMY LOAD WATTMETER



The Tempo LW1500 load-wattmeter offers typical Tempo price-performance value. Designed for amateur or commercial use, the LW1500 is completely portable. An internal "D" cell battery powers the overheating warning light so no AC connections are necessary. The built-in handle and light weight make the load convenient for desk, bench, auto or field testing.

Price: \$119.00.

Other Tempo products:

FMA (25 watt - 2 meter FM transceiver)
RBF-1 Wattmeter & SWR Bridge
VHF & UHF Amplifiers

Henry Radio

11240 W. Olympic Blvd., Los Angeles,
Calif. 90064
931 N. Euclid, Anaheim, Calif. 92801
Butler, Missouri 64730

213/477-6701
714/772-9200
816/679-3127



EIMAC
conduction
cooled
8873s

keep Henry Radio's new Ultra Linear amplifier ultra quiet.

Henry Radio beat the blower noise problem by eliminating it. In their quiet, compact, rugged and reliable 2K Ultra Linear Amplifier, anode heat is silently conducted to an efficient heat sink. No more blower. No more blower noise. No more annoying problem.

Two EIMAC conduction cooled, high-mu 8873 power triodes are used in this very linear, state-of-the-art amplifier to provide 2 kW PEP input over the 3.5 to 30.0 MHz range.

Operating in cathode driven service, these tubes typically provide high power gain (greater than 13 decibels) in combination with low, low intermodulation distortion (3d order products better than -35 decibels below one tone of a two-tone test signal). These excellent characteristics of the 8873 may be utilized up to 500 MHz.

With Henry Radio, you know quality counts. And they know you can't do better than EIMAC. For full specifications on the 8873 and its sturdy companions, the 8874 and 8875, write to EIMAC Division of Varian, 301 Industrial Way, San Carlos, California 94070.

