

\$1.50

ham radio

magazine

hr 

AUGUST 1977

- Yagi antenna design 22
- Touch-Tone encoder 41
- IC frequency standard 44
- microwave spectrum analyzer 54
- speech processor 48
- and much more . . .

**direct output
two-meter
synthesizer**



TEMPO

VHF/ONE PLUS



MORE POWER / 25 OR 5* WATTS OUTPUT SELECTABLE

REMOTE TUNING / ON MICROPHONE

NEW LOWER PRICE / NOW ONLY \$399.00

SIDEBAND OPERATION WITH SSB/ONE ADAPTER / MARS OPERATION CAPABILITY / 5 KHz NUMERICAL LED

The Tempo VHF/One Plus is a VHF/FM transceiver for dependable communication on the 2 meter amateur band • Full 2 meter coverage, 144 to 148 MHz for both transmit and receive • Full phase lock synthesized (PLL) • Automatic repeater split—selectable up or down • Two built-in programmable channels • All solid state • 800 selectable receive frequencies with simplex and +600 KHz transmit frequencies for each receive channel. *Adjustable internally 3 to 15 watts



TEMPO FMH-2, FMH-5 & FMH-42 (UHF)

6 channel capability • selectable 1 or 2 - 1 or 5 Watts output • Solid-state • Battery level meter • Earphone jack • Built-in charging terminals and separate charging jack for Ni-cad batteries • Flex antenna • Carrying case standard • Excellent frequency stability allows use with booster amplifier for high power output over 100 Watts • 8 AA batteries or 10 AA Ni-cads.*

*Not furnished.
FCC Type accepted models available.

TEMPO VHF & UHF AMPLIFIERS

VHF (135 to 175 MHz)

Drive Power	Output	Model No.	Price
2W	130W	130A02	\$199
10W	130W	130A10	\$179
30W	130W	130A30	\$189
2W	80W	80A02	\$169
10W	80W	80A10	\$149
30W	80W	80A30	\$159

UHF (400 to 512 MHz)

Drive Power	Output	Model No.	Price
2W	70W	70D02	\$270
10W	70W	70D10	\$250
30W	70W	70D30	\$210
2W	40W	40D02	\$180
10W	40W	40D10	\$145
2W	10W	10D02	\$125

FCC Type accepted models available.

TEMPO POCKET RECEIVERS

MS-2, 4 channel scanning receiver for VHF high band, smallest unit on the market. MR-2 same size as MS-2 but has manual selection of 12 channels. VHF high band. MR-3, miniature 2-channel VHF high band monitor or paging receiver. MR-3U, single channel on the 400 to 512 UHF band. All are low priced and dependable.



Sold at Tempo dealers throughout the U.S. and abroad. Please call or write for further information.

Prices subject to change without notice

11240 W. Olympic Blvd., Los Angeles, Calif. 90064
931 N. Euclid, Anaheim, Calif. 92801
Butler, Missouri 64730

213/477-6701
714/772-9200
816/679-3127

Henry Radio

The Century/21 started with a clean sheet of paper...



OBJECTIVE: To design a no-compromise HF transceiver for the beginning Ham or Old Timer and at an economical, affordable price.

CRITERIA: Cw transmit, cw and ssb receive. Full break-in. 70 watts input. Full band coverage 80-15 meters, 1 MHz on 10. All solid state. Instant,


no-tune band change. Built-in regulated power supply. Overload protection. Linear crystal mixed VFO. Direct frequency readout. Offset receiver tuning, defeatable. Built-in speaker. Sensitive receiver section. High selectivity — three position. Sidetone with adjustable level. Full line of matching accessories.

THE RESULT . . . TEN TEC *Century/21*

The Century/21 was designed and tooled from scratch for high performance cw. A unique Double Direct Conversion receiver performs as well as the conventional superhet. Broadband transmitter with instant break-in is a highly desired luxury. Accessory keyer and crystal calibrator available now, with additional accessories to follow. And . . .

THE AFFORDABLE PRICE:

Century/21, Model 570	\$289.00
Century Keyer, Model 670	29.00
Century Calibrator, Model 276	29.00

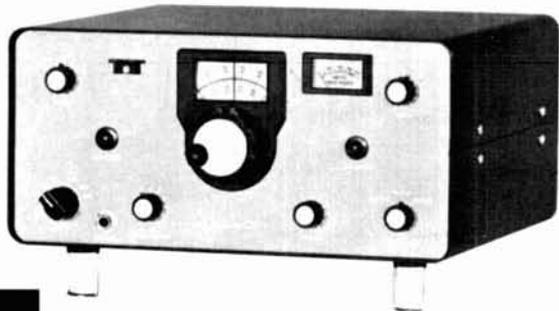

For further information, write:

TEN-TEC, INC.
SEVIERVILLE, TENNESSEE 37862
EXPORT: 5715 LINCOLN AVE., CHICAGO, ILL. 60646

This NEW MFJ Deluxe Keyer at \$69.95 . . .

gives you more features per dollar than any other keyer available.



Based on the Curtis 8043 IC keyer on-a-chip, the new MFJ Deluxe Keyer gives you more features per dollar than any other keyer available.

Sends iambic, automatic, semi-automatic, manual. Use squeeze, single lever or straight key.

Iambic squeeze key operation with dot and dash insertion lets you form characters with minimal wrist movement for comfortable, fatigue-free sending.

Semi-automatic "bug" operation provides automatic dots and manual dashes. Use a manual straight key to safely key your transmitter or to improve your fist.

Dot memory, self-completing dots and dashes, jam-proof spacing and instant start for accurate and precise CW.

Totally RF proof. No problems, whatever.

Ultra-reliable solid-state keying. Keys virtually any transmitter: grid block, -300V max., 10 ma, max.; cathode and solid state transmitters +300V max., 200 ma, max.

All controls are on the front panel: speed, weight, tone, volume, function switch. Smooth linear speed control. 8 to 50 WPM.

Weight control lets you adjust dot dash space ratio; makes your signal distinctive to penetrate thru heavy QRM for solid DX contacts.

Tone control. Room filling volume. Built-in speaker. Ideal for classroom teaching.

Function switch selects off, on, semi-automatic/manual, tune. Tune keys xmtr for tuning.

Completely portable. Take it anywhere. Operates up to a year on 4 C-cells. Miniature phone jack for external power (3 to 15 VDC).

Beautiful Ten Tec enclosure. Eggshell white, walnut sides. Compact 6x6x2 inches.

Three conductor quarter-inch phone jack for key, phono jacks for keying outputs.

Optional squeeze key. Dot and dash paddles have fully adjustable tension and spacing for the exact "feel" you like. Heavy base with non-slip rubber feet

eliminates "walking". \$29.95 plus \$2.00 for shipping and handling.

Try it—no obligation. If not delighted, return it within 30 days for a refund (less shipping). This keyer is unconditionally guaranteed for one year.

To order, simply call us toll-free 800-647-8660 and charge it on your BankAmericard or Master Charge or mail us an order with a check or money order for \$69.95 plus \$2.00 shipping/handling for the MFJ-8043 keyer and/or \$29.95 plus \$2.00 shipping/handling for the squeeze key.

Don't wait any longer to enjoy the pleasures of the new MFJ Deluxe Keyer. Order today.

**CALL TOLL FREE
800-647-8660**

Write in today for free catalog of our complete line.

This NEW MFJ Super Antenna Tuner . . .

matches everything from 160 thru 10 Meters: dipoles, inverted vees, random wires, verticals, mobile whips, beams, balance lines, coax lines.

Up to 200 watts RF OUTPUT. Built-in balun, too!



\$ 69⁹⁵

With the NEW MFJ Super Antenna Tuner you can run your full transceiver power output — up to 200 watts RF power output — and match your transmitter to any feedline from 160 thru 10 Meters whether you have coax cable, balance line, or random wire.

You can tune out the SWR on your dipole, inverted vee, random wire, vertical, mobile whip, beam, quad, or whatever you have.

You can even operate all bands with just one existing antenna. No need to put up separate antennas for each band.

Increase the usable bandwidth of your mobile whip by tuning out the SWR from inside your car. Works great with all solid state rigs (like the Atlas) and with all tube type rigs.

It travels well, too. Its ultra compact size 5x2x6 inches fits easily in a small corner of your suitcase.

The secret of this tiny, powerful tuner is a wide range 12 position variable inductor made from two stacked toroid cores and high quality capacitors manufactured especially for MFJ. For balanced lines a 1:4 (unbalanced to balanced) balun is built in. Made in U.S.A. by MFJ Enterprises.

This beautiful little tuner is housed in a deluxe eggshell white Ten-Tec enclosure with walnut grain sides.

SO-239 coax connectors are provided for transmitter input and coax fed antennas. Quality five way binding posts are used for the balance line inputs (2), random wire input (1), and ground (1).

Try it — no obligation. If not delighted, return

it within 30 days for a refund (less shipping). This tuner is unconditionally guaranteed for one year.

To order, simply call us toll-free 800-647-8660 and charge it on your BankAmericard or Master Charge or mail us an order with a check or money order for \$69.95 plus \$2.00 shipping/handling for the MFJ-16010ST Super Antenna Tuner.

Don't wait any longer to tune out that SWR and enjoy solid OSO's. Order today.

MFJ ENTERPRISES

P. O. BOX 494

MISSISSIPPI STATE, MS. 39762

CALL TOLL FREE . 800-647-8660

ham radio

magazine

AUGUST 1977

volume 10, number 8

T. H. Tenney, Jr., W1NLB
publisher

James R. Fisk, W1HR
editor-in-chief

editorial staff

Charles J. Carroll, K1XX
Alfred Wilson, W6NIF
assistant editors

James H. Gray, W2EUQ
Patricia A. Hawes, WA1WPM
Thomas F. McMullen, Jr., W1SL
Joseph J. Schroeder, W9JUV
associate editors

Wayne T. Pierce, K3SUK
cover

publishing staff

Harold P. Kent, WA1WPP
assistant publisher

Fred D. Moller, Jr., WA1USO
advertising manager

Cynthia M. Schlosser
assistant advertising manager

Theresa R. Bourgault
circulation manager

ham radio magazine
is published monthly by
Communications Technology, Inc
Greenville, New Hampshire 03048
Telephone: 603-878-1441

subscription rates

U.S. and Canada: one year, \$10.00
three years, \$20.00
Worldwide: one year, \$15.00
three years, \$35.00

foreign subscription agents

Ham Radio Canada
Box 114, Goderich
Ontario, Canada, N7A 3Y5

Ham Radio Europe
Box 444
S-194 04 Upplands Vasby
Sweden

Ham Radio UK
P. O. Box 63, Harrow
Middlesex HA3 6HS
England

Holland Radio, 143 Greenway
Greenside, Johannesburg
Republic of South Africa

Additional foreign subscription agents
are listed on page 108

Copyright 1977 by
Communications Technology, Inc
Title registered at U.S. Patent Office

Microfilm copies
are available from
University Microfilms, International
Ann Arbor, Michigan 48103

Second class postage
paid at Greenville, N.H. 03048
and at additional mailing offices
Publication number 23340



contents

**10 direct-output
two-meter synthesizer**
Gerald Pulice, WB2CPA

22 designing yagi antennas
Joseph H. Reisert, W1JR

**32 the future of the
amateur satellite service**
Martin Davidoff, K2UBC

41 Touch-Tone encoder
Howard M. Berlin, W3HB

44 CMOS frequency standard
Frederick M. Griffee, W4IYB

48 logarithmic speech processor
Frank C. Getz, K3PDW


54 microwave spectrum analyzer
H. Paul Shuch, WA6UAM

**67 Baudot and ASCII converter
for 8-level teleprinters**
Eric Kirchner, VE3CTP

**76 admittance and impedance
circuit analysis**
Leonard H. Anderson

4 a second look
126 advertisers index
101 flea market
116 ham mart

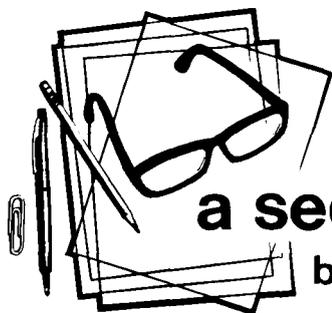86 new products
6 presstop
126 reader service



a second look

by Jim Fisk

As more and more amateurs switch to factory-made gear, and as industry uses more ICs and disposable plug-in modules, the life of the dyed-in-the-wool ham homebrewer gets tougher and tougher. If you've recently tried any of the construction articles in the amateur magazines, you are already well acquainted with the hassle involved in obtaining a few needed components.

At one time you could drop in at your local corner radio store with a list of parts and the man behind the counter would fill your order. But that was when the vacuum tubes, resistors, and capacitors in your ham gear were the same as those in the family radio. It's not the same anymore — now the transistors and ICs in the radios and television sets are designed specifically for that purpose and have operating characteristics that are of little use elsewhere. There are exceptions, but they are few and far between.

Another problem that faces the serious home builder is the tremendous variety of transistors and ICs available from different manufacturers. Although some types of devices are made by more than one company, in most cases the semiconductor manufacturers crank out devices that are completely different from those of their competitors. And to add insult to injury, the same device may carry a dozen different part numbers: a 2N number, a replacement number, plus special numbers for units sold in large quantities to equipment manufacturers.

There is only one way to combat this lunacy: arm yourself with a good semiconductor cross-reference guide and a wide selection of electronic parts catalogs. Tops on the list of replacement guides is Howard Sams' *Transistor Substitution Handbook* available from *Ham Radio's* Communications Bookstore. This handy little paper back, which is updated every year, covers practically every transistor ever made, from 2N34 to 2N6500, with recommended substitutes. It also covers devices from Japan and Europe, as well as replacement types manufactured by Delco, General Electric, International Rectifier, Motorola, RCA, Semitronics, Sylvania, and Workman. Most of these manufacturers also publish replacement guides, available for the asking from their authorized distributors.

If you live in a large metropolitan area, chances are that there is an industrial electronics supply house that can fill your parts needs. Many of these firms don't advertise because they are not particularly interested in small quantity sales, but if you show up at their office, they will sell you the parts. If you want to find them, pick up your telephone directory and check the *Yellow Pages*: look under "Electronic Equipment and Supplies."

If you live out in the sticks, the problem is more difficult, unless you can get into the city. If you can't, you must purchase your components through the mail. Allied Electronics is the best bet in this case and you can get a catalog from any Radio Shack store. Be sure to get their industrial catalog though — the more common entertainment catalog is devoted primarily to CB and hi-fi and lists few electronic parts for amateur communications equipment.

Jim Fisk, W1HR
editor-in-chief



That's all, Folks!

All you need for All Mode Mobile, that is.

All Mode Mobile is now yours in a superior ICOM radio that is a generation ahead of all others. The new, fully synthesized **IC-245/SSB** puts you into FM, SSB and CW operation with a very compact dash-mounted transceiver like none you've ever seen.

- **Variable offset:** Any offset from 10 KHz through 4 MHz in multiples of 10 KHz can be programmed with the LSI Synthesizer.
- **Remote programing:** The **IC-245/SSB** LSI chip provides for the input of programming digits from a remote key pad which can be combined with Touch Tone* circuitry to provide simultaneous remote program and tone. Computer control from a PIA interface is also possible.

* a registered trademark of AT&T.

- **FM stability on SSB and CW:** The **IC-245/SSB** synthesis of 100 Hz steps make mobile SSB as stable as FM. This extended range of operation is attracting many FM'ers who have been operating on the direct channels and have discovered SSB.

The **IC-245/SSB** is the very best and most versatile mobile radio made: that's all. For more information and your own hands-on demonstration see your ICOM dealer. When you mount your **IC-245/SSB** you'll have all you need for All Mode Mobile.

SPECIFICATIONS

FREQUENCY COVERAGE MODES
SUPPLY VOLTAGE
SIZE (mm)
WEIGHT
TRANSMITTER TX OUTPUT
CARRIER SUPPRESSION

*144.00 to 148.00MHz FM (F3)
**SSB (A3); CW (A1)
DC 13.8V ± 15%
90° ± 150W ± 20%
2.7
F3 10W
*A33 10W (PEP); A1 10W
40 dB OR BETTER

SPURIOUS RADIATION
MAXIMUM FREQUENCY DEVIATION
MICROPHONE IMPEDANCE
RECEIVER SENSITIVITY

-60 dB BELOW CARRIER
1.5kHz
600 OHMS
*A3: A1 @ 5 MICROVOLT INPUT GIVES 10 dB S+N
F3 @ 5 MICROVOLT OR LESS FOR 20 dB QUIETING
S+N = 0 IN AT 1 MICROVOLT INPUT: 30 dB

SQUELCH THRESHOLD
SPURIOUS RESPONSE
SYNTHESIZER
FREQUENCY RANGE
STEP SIZE
STABILITY

-8 dB OR LESS (F3)
40 dB OR BETTER
144 MHz to 148 MHz
5 KHz to FM
*100 Hz or 5 KHz for SSB
PER C IN THE RANGE CF -10
TO +40C: ±0.00014%

*VALID WITH SSB UNIT ONLY

VHF/UHF AMATEUR AND MARINE COMMUNICATION EQUIPMENT

Distributed by:



ICOM

ICOM WEST, INC.
Suite 3
13256 Northrup Way
Bellevue, Wash. 98005
(206) 747-9020

ICOM EAST, INC.
Suite 307
3331 Towerwood Drive
Dallas, Texas 75234
(214) 620-2780

ICOM CANADA
7087 Victoria Drive
Vancouver B.C. V5P 3Y9
Canada
(604) 321-1833



IMMINENT COMMUNICATOR LICENSE action is being rumored by several industry sources. Departing Chairman Dick Wiley's support of the Communicator concept and his reported desire to see it realized before he steps down is one very strong argument; its probable impact on the Personal Radio Division's budget, which will be reviewed shortly along with next year's proposed budget, is another.

It Appears Very Likely that the Communicator license will see some sort of official review within the next few weeks or so. What will come out of that review is another question.

EXISTING AMATEUR TRANSMITTERS WERE "GRANDFATHERED" June 2nd by an FCC modification to the first Report and Order on Docket 20777 that had become effective April 15. Under the modification all Amateur transmitters and transceivers (but not amplifiers) manufactured before April 15 are permanently exempted from the Report and Order's harmonic and spurious specifications. All Amateur equipment made after April 15 must meet the new specs, of course, but existing new equipment made before that date can be marketed until January 1, 1978. Individual Amateurs, however, are still responsible for meeting the 40-dB harmonic and spurious specifications of the FCC's first Report and Order on Docket 20777 in the operation of their own stations, even though the equipment itself has been grandfathered. The FCC's June 2nd relaxation applied only to the sale of non-complying equipment, and users are still expected to use it in such a way (with appropriate filters or an antenna tuner) that their stations meet the tighter requirement. Officially, the relaxation became effective July 18th.

UNRETURNED NOVICE EXAMS are still a big problem with the FCC in Gettysburg despite the dropping of multiple-exam mailings. Volunteer examiners have a major responsibility to see that a Novice exam, whether or not the applicant actually takes it, is returned to Gettysburg on time. Failure to do so can jeopardize the volunteer examiner's own license, and continuation of the present "unacceptable" number of unreturned exams could trigger drastic changes in Novice licensing!

GETTYSBURG RECEIVED A REPRIEVE when a radical personnel cut scheduled for June 10th didn't come off. Best news of all is that the previous "temporary" positions the people leaving had held are to be made permanent, and those people who have been filling the slots so well, will be staying in their jobs and working into permanent status.

The Reprieve Doesn't solve all of Gettysburg's problems, however. The Amateur workload continues to increase, and an estimated 10-20 additional people are going to be needed if the facility is to keep working smoothly.

"GUILTY ON TWO COUNTS" was the verdict the jury handed down June 6th in the trial of FCC Special Licensing Chief Richard Ziegler (July Presstop). One of the original four counts of bribery for the issuance of special Amateur call signs was dropped and the jury failed to reach a decision on the second during the two-day trial.

18-YEAR-OLD GENERAL CLASS, or higher, Amateur license holders were permitted to administer Novice exams, effective June 13th. The amendment to Section 97.28(b) of the rules came about as a result of a Petition for Rule Making filed by WB4EKC.

A NEWLY-UPDATED EDITION of the FCC's Amateur Radio Rules, including all Part 97 changes through March 7, is now available from the Superintendent of Documents, U.S. Government Printing Office, Washington D.C. 20402. It's stock number 004-000-00338-1 and postpaid price is \$1.30.

EXTENSIVE ELECTRONIC CONTROLS used in 1977 autos are causing RFI problems — a recent Illinois Bell notice warned that the "cruise control" in 1977 Cadillacs (and presumably other GM cars) is sensitive to strong RF fields, which could cause sudden speed up or slow down. Some electronic skid control braking systems have locked up from RFI, and complete engine failure in fuel-injected engines has been reported by two-meter users.

A BOOKLET PROMOTING CANADIAN Amateur Radio has been published by the Radio Society of Ontario, Inc. The very attractive publication is available free to Canadian clubs or groups wishing to use it — an SASE to RSO, Box 334, Station U, Toronto, Ontario M8Z 5P7 will bring a sample and ordering information.

COMPUTER VOICE GENERATOR shown at the Dayton Hamvention is being used on 6 meters by WB4IVG in Dalton, Georgia. K1ZZ was "its" first contact.

DenTron amateur radio products have always been strikingly individual. This is the result, not of a compulsion to be different, but of a dedication to excellence in American craftsmanship. This dedication now extends to one of the worlds finest high performance Military amateur amplifiers.

Luxury styling, however, would not be fully appreciated without an exceptional power source. The heart of the MLA-2500 is a heavy duty, self-contained power supply.

Compare the MLA-2500. It has the lowest profile of any high performance amplifier in the world. It's modular construction makes it unique, and at \$799.50 it is an unprecedented value.

Very few things in life are absolutely uncompromising. We are proud to count the DenTron MLA-2500 among them. And so will you.

MLA-2500 FEATURES

- 160 thru 10 meters
- 2000+ watts PEP input on SSB
- 1000 watts DC input on CW, RTTY, or SSTV
- Variable forced air cooling system
- Self contained continuous duty power supply
- Two EIMAC 8875 external-anode ceramic/metal triodes operating in grounded grid.
- Covers MARS frequencies without modifications
- 50 ohm input and output impedance
- Built in RF watt meter
- 117 V or 234 V AC 50-60 hz
- Size: 5½" H x 14" W x 14" D.

All DenTron products are made in the U.S.A.

Introducing the new MLA-2500

The linear amplifier beyond compromise.



Amplifier in actual operation.

DenTron
Radio Co., Inc.

2100 Enterprise Parkway
Twinsburg, Ohio 44087
(216) 425-3173



WHO ELSE BUT KENWOOD

WHO ELSE BUT KENWOOD CARES ENOUGH TO OFFER FINE AMATEUR RADIO GEAR IN ALL THREE SEGMENTS OF THE RF SPECTRUM... HF, VHF, AND NOW UHF. EQUIPMENT FOR THE NOVICE JUST COMING UP FROM CB TO THE EXTRA CLASS "OLD TIMER", PORTABLE, MOBILE OR BASE STATION, 2 METER OR 6 METER OR EVEN THE SPECIAL INTEREST OPERATOR WHO WANTS A "KENWOOD" QUALITY 450 MHz RIG LIKE THE TR-8300. A DEDICATION TO DESIGNING AND BUILDING THE VERY FINEST EQUIPMENT POSSIBLE... A DEDICATION TO INNOVATIVE ENGINEERING BACKED BY A SOLID SERVICE POLICY... A DEDICATION TO GIVING YOU MORE SATISFACTION FOR EVERY DOLLAR YOU SPEND... WHO ELSE BUT KENWOOD *****THE



WHO PACESETTER IN AMATEUR RADIO.

*THE TR-8300 IS KENWOOD'S NEWEST OFFERING... A 450 MHz MOBILE/BASE STATION RUNNING 10 WATTS WITH 22 CHANNEL CAPABILITY.



THE PEOPLE WHO SELL KENWOOD

ALTHOUGH EVERY KENWOOD PRODUCT LINE IS CAREFULLY MANUFACTURED, FACTORY TESTED AND TESTED AGAIN UPON ARRIVAL IN OUR CALIFORNIA FACILITY, A UNIT MAY NEED SERVICE AT SOME FUTURE DATE. IN ORDER TO GUARANTEE THE BEST LOCAL SERVICE NATIONWIDE, KENWOOD HAS CAREFULLY SCREENED AND CHOSEN A SELECT GROUP OF DEALERS WHOSE SALES AND SERVICE PERSONNEL ARE THOROUGHLY FAMILIAR WITH KENWOOD PRODUCTS, WHO STOCK THE CORRECT PARTS, WHO ARE KEPT UP TO DATE ON SERVICING TECHNIQUES AND WHO, OF COURSE, HAVE THE SOLID BACKING OF KENWOOD'S FACTORY TRAINED STAFF.

WHEN YOU BUY YOUR KENWOOD PRODUCT FROM AN *AUTHORIZED KENWOOD DEALER* YOU CAN BUY WITH CONFIDENCE.

FOLLOWING IS A LIST OF AUTHORIZED DEALERS.

(As of May 31, 1977)

ARIZONA

Power Communications*
6012 North 27th Ave.
Phoenix, AZ 85017

ALABAMA

Long's Electronics
3521 10th Ave. North
Birmingham, AL 35234

CALIFORNIA

Gary Radio
8199 Clairemont Mesa Blvd
San Diego, CA 92112

Ham Radio Outlet

999 Howard Ave.
Burlingame, CA 94010

Ham Radio Outlet

13754 Victory Blvd.
Van Nuys, CA 91401

Henry Radio, Inc.

11240 West Olympic Blvd.
Los Angeles, CA 90064

Henry Radio, Inc.

931 North Euclid
Anaheim, CA 92801

Webster Radio

2602 East Ashlan
Fresno, CA 93726

COLORADO

CW Electronics
1401 Blake St.
Denver, CO 80202

FLORIDA

Amateur Electronic Supply
621 Commonwealth
Orlando, FL 32803

Amateur Radio Center

2805 N.E. Second Ave.
Miami, FL 33137

Grice Electronics

320 East Gregory St.
Pensacola, FL 32501

HAWAII

Lafayette Radio Company
1111 Mc Cully St.
Honolulu, HI 96814

ILLINOIS

Erickson Communications
5935 North Milwaukee Ave.
Chicago, IL 60646

Klaus Radio, Inc.

8400 North Pioneer Parkway
Peoria, IL 61614

INDIANA

Graham Electronics
133 South Pennsylvania
Indianapolis, IN 46240

Hoosier Electronics

43 B Meadows Shopping Center
Terre Haute, IN 47802

IOWA

Hi, Inc.
1601 Avenue "D"
Council Bluffs, IA 51501

KANSAS

Associated Radio Comm.
8012 Conser
Overland Park, KS 66204

MAINE

Craig Radio Company
Route 1 By-Pass South
Kittery, ME 03904

MARYLAND

Electronic International Service
11305 Elkin St.
Wheaton, MD 20902

Professional Electronics

1710 Joan St.
Baltimore, MD 21204

MICHIGAN

Electronic Distributors
1960 Peck St.
Muskegon, MI 49441

Radio Supply & Engineering

1207 W. 14 Mile Rd.
Clawson, MI 48017

MINNESOTA

Electronic Center
127 Third Ave. North
Minneapolis, MN 55401

MISSOURI

Ham Radio Center
8342 Olive Blvd.
St. Louis, MO 63132

Henry Radio Company

211 North Main St.
Butler, MS 64730

Midcom Electronics, Inc.

2506 South Brentwood Blvd.
St. Louis, MO 63144

MONTANA

Conley Radio Supply
318 North 16th St.
Billings, MT 59101

NEW MEXICO

Electronic Module
601 North Turner
Hobbs, NM 88240

NEW YORK

Adirondack Radio Supply
185 West Main St.
Amsterdam, NY 12012

Harrison Radio Corporation

20 Smith St.
Farmingdale, L.I., NY 11735

NORTH CAROLINA

Freck Radio Supply
252 Patton Ave.
Asheville, NC 28801

Vickers Electronics

500 East Main St.
Durham, NC 27702

OHIO

Amateur Electronic Supply

17929 Euclid Ave.
Cleveland, OH 44112

Srepcu Electronics

314 Leo St.
Dayton, OH 45404

OKLAHOMA

Derrick Electronics
714 West Kenosha
Broken Arrow, OK 74012

Radio Inc.

1000 South Main
Tulsa, OK 74119

OREGON

Portland Radio Supply

1234 S.W. Stark St.
Portland, OR 97205

PENNSYLVANIA

Electronic Exchange
136 Main St.
Souderton, PA 18964

Hamtronics

4033 Brownsville Rd.
Trevose, PA 19047

JRS Distributors

646 West Market St.
York, PA 17404

SOUTH CAROLINA

Accutek, Inc.
420 Laurens Rd.
Greenville, SC 29607

SOUTH DAKOTA

Burghardt Amateur Center
124 First Ave. N.W.
Watertown, SD 57201

TENNESSEE

Sere-Rose & Spencer Elec.
1465 Wells Station Rd.
Memphis, TN 38108

TEXAS

AGL Electronics*
3068 Forest Lane #309
Dallas, TX 75234

Douglas Electronics

1118 South Staples
Corpus Christi, TX 78404

Electronics Center

2929 North Haskell
Dallas, TX 75204

Madison Electronics

1508 McKinney Ave.
Houston, TX 77002

UTAH

Manwill Supply Company

2780 South Main St.
Salt Lake City, UT 84115

WASHINGTON

ABC Communications

17541 15th Ave. N.E.
Seattle, WA 98155

Amateur Radio Supply Company

6213 — 13th Ave. South
Seattle, WA 98108

WISCONSIN

Amateur Electronic Supply

4828 West Fond Du Lac Ave.
Milwaukee, WI 53216

*Pending

direct output

two-meter synthesizer

New techniques permit the construction of a synthesized vhf transmitter which does not require frequency multiplication

This article will describe a unique, to amateur radio, method of building a two-meter synthesizer. Rather than function as a replacement for a crystal, *direct synthesis* generates the desired frequency without multiplication. Using ECL, TTL, and CMOS integrated circuits, the completed transmitter will produce 800 individual frequencies spaced every 5 kHz between 144 and 147.995 MHz. In addition, a local oscillator output, 10.7 MHz above the transmitter, can be used for receiver injection. With a phase-locked loop (PLL) ultimately controlling the vco (voltage-controlled-oscillator), the frequency accuracy is determined by a single crystal.

Contrary to some synthesizer designs, the receive and transmit frequencies in this unit are totally independent. This eliminates problems when odd frequency splits are encountered. Also, the two frequencies are available as BCD data for further processing or for a convenient readout rather than the thumbwheel switches. Again, another step into the realm of microprocessor-controlled equipment! The

total cost for this 15-milliwatt exciter and local oscillator is approximately 100 dollars.

frequency generation

The two-meter fm frequencies are all multiples of 5 kilohertz; therefore, with an accurately generated 5-kHz reference frequency, each channel can be produced through multiplication by using the proper integer (**fig. 1**). However, there are inherent problems in this scheme, primarily because no easily programmed frequency *multipliers* are available. On the other hand, programmable *dividers* do exist. By inserting the correct number of dividers (counters) into a feedback loop as shown in **fig. 2**, we have effectively created a frequency multiplier; this is the beginning of our PLL. Unfortunately, this method has several problems. For the output to be exactly on frequency, the difference detector must be driven to zero. Therefore, the detector must not have any offset; in addition, the error amplifier should have infinite gain. To overcome these problems, a PLL uses the phase of the vco as the controlling factor rather than its frequency. The phase detector will be discussed in more detail later.

There are two special problems in PLL frequency synthesis. Extreme care must be taken in the design to prevent the radiation of excessive sidebands and spurious outputs. The reference sidebands are caused by the vco being modulated at the sampling rate of the phase-detector. The more difficult (to control) spurious outputs are caused by close physical proximity to the digital logic. Also, the spurs can cause birdies in a companion receiver. Proper mechanical design, however, has reduced the levels to -55 dB and -90 dB, respectively.

programmable divider and prescaler

Unfortunately, since we are working with a closed loop system, any problems in one area are reflected in other portions of the circuit. Consider the final output signal; there should be a minimum of buzz or hum associated with the signal. Also, the transient response (time to settle after a channel change) should be small. These problems can be reduced by

By Jerry Pulice, WB2CPA, 143 Gibson Avenue, Staten Island, New York 10308

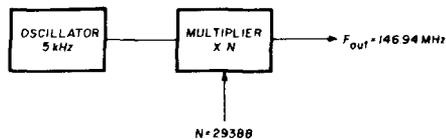


fig. 1. Block diagram of a basic frequency synthesizer that uses integer multipliers to generate the output frequency.

using a high performance loop to control the vco. As an example consider the PLL shown in fig. 3. With the vco prescaled by a factor of 20, the output frequency is determined by

$$F_{OUT} = 20(N)(0.005 \text{ MHz}) \quad (1)$$

Therefore, the minimum channel spacing will be 100 kHz instead of 5 kHz. To regain the original channel spacing, it would be necessary to divide the reference by a factor of 20. With a low reference frequency (250 Hz), the vco must have exceptional stability

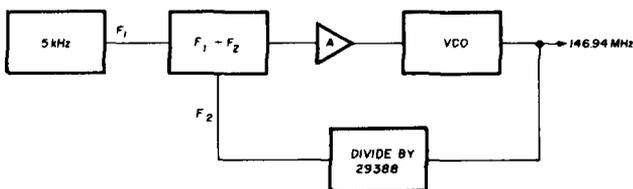


fig. 2. This system eliminates the multipliers and uses more commonly available dividers to generate the required integer.

since it can only be corrected 250 times per second. From these facts it can be seen that for best loop performance the digital logic should operate at the highest possible frequency.

TTL logic cannot operate directly at 144 MHz, and prescaling by at least 10 is required for any two-meter synthesizer. Conventional designs call for a programmable divider that can be preset to some number other than zero to modify the count length. Regardless of the counters toggle speed, this method will limit the upper frequency to approximately 15 MHz because not enough time elapses during one clock cycle to guarantee presetting the counters. It would appear that these problems would require the reference frequency to be lowered regardless of the loop considerations. However, return to eq. 1, which is one step beyond the basic form

$$F_{OUT} = (N)(M)(0.005 \text{ MHz}) \quad (2)$$

where N = integer number

M = prescale factor

Rearranging eq. 2 yields

$$N = \frac{F_{OUT}}{(M)(0.005 \text{ MHz})} \quad (3)$$

Where N is now the number of divisions required by the prescaler and reference frequency. With a pre-

scaler that divides by 20, N would be 1440 divisions at 144 MHz.

Now, consider a prescaler that can divide by not only M , but $M + 1$. To maintain the same output frequency, eq. 2 must be rewritten to account for M and $M + 1$:

$$F_{OUT} = [M(N - A) + (M + 1)(A)](0.005 \text{ MHz}) \quad (4)$$

where N = total number of divisions (integer number)

M = prescale factor

A = number of divisions at $M + 1$

$$\text{or } 144 \text{ MHz} = [20(1440 - 0) + 21(0)](0.005 \text{ MHz})$$

Reducing eq. 4 to real components shows that a relatively slow counter (divider) can be used to control a fast two-mode (modulus) prescaler. In other words, the slow counter tells the prescaler to divide by twenty 1440 times and by 21 zero times. This technique is called pulse swallowing.


If one division though is by 21 instead of 20, eq. 4 produces

$$[20(1440 - 1) + 21(1)](0.005 \text{ MHz}) = 144.005 \text{ MHz}$$


Therefore, for each division by 21, the vco frequency is raised 5 kHz. This relationship will continue each time the integer number is changed, producing channels that are separated by 5 kHz. The use of pulse-swallowing techniques overcomes the problems of vco and reference frequency, permitting the design of a vhf synthesizer with a channel spacing equal to the reference frequency.

divider details

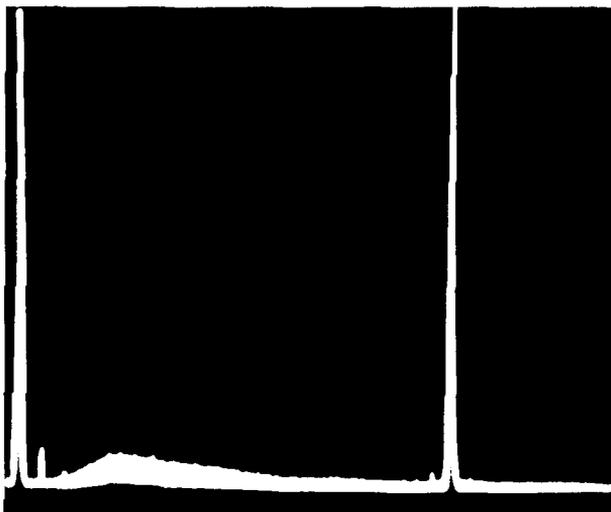As shown in fig. 4, the programmable divider is



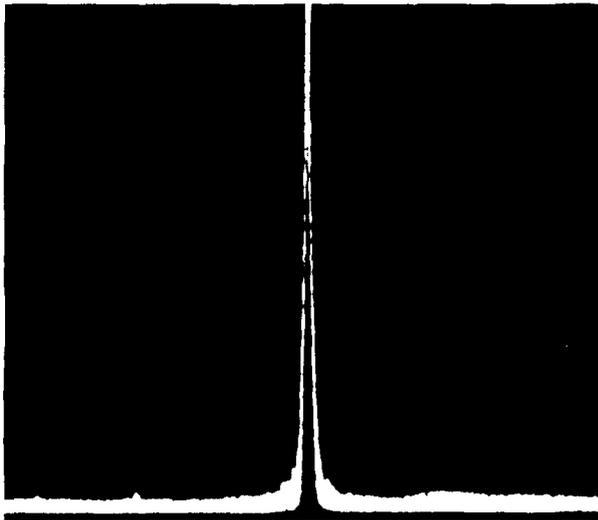As shown on this spectrum analyzer photograph, the output is very clean from 0 to 200 MHz. The signal frequency is 146 MHz. The low-frequency noise is being generated by the rf amplifier on the rf board.



Spectrum analyzer presentation of the final output. The signal is centered at 146 MHz. The left and right edges represent 143.5 and 148.5 MHz, respectively. The base line is approximately 80 dB down from the full output.

split into a two modulus prescaler and a low-speed main counter. In conjunction with the 7474 flip-flop, the prescaler will divide by either 20 or 21, depending upon the level on the 95H90s SWALLOW ENABLE line. If this line is held high, one output will occur for each 21 input pulses. If the line is low, the output will be 1 pulse for each 20 input pulses. This output from the prescaler section then drives three synchronous-binary 4-bit counters arranged as a 12-bit binary divider. In transmit the counters are reset by U15 at 1479_2 and in receive at 1586_2 by U14. The initial input frequency is converted by the 7483s into data that presets the binary counters between 0 and 39. Assuming a transmit condition, the 1479_2 count is shortened by the amount of preset, 0 to 39. The output of the counter will then occur at 1479_2 to 1440_2 representing 147.9XX to 144.0XX (eq. 2). It's now possible to generate any multiple of 100 kHz between the two frequency extremes.

Bit 1024_2 (pin 12 U13) goes high once per count cycle and is used as the 5-kHz output to feed the phase detector. This pulse is much wider than the 5-kHz pulse at pin 9 of the binary counters and will

provide a more reliable trigger for the CD4046 phase detector.

Unfortunately, the 100-kHz multiples have not fulfilled the requirement of 5-kHz channel spacing. Between 100-kHz increments there are nineteen desired channels spaced every 5 kHz. As determined by eq. 4, each time the prescaler divides by $M + 1$ the vco frequency will increase by 5 kHz. Using 144.035 MHz as an example, the prescaler would have to divide by $M + 1$ seven times and by M , 1433 times. To generate the required number of $M + 1$ divisions, 10 and 5 kHz data, a rate multiplier is used. This device, comprised of a series of gates and counters, will produce a specific number of pulses on command. Controlled by frequency data (144.035 MHz) from thumbwheel switches, the rate multiplier will, each time it's enabled, generate seven pulses. The 1024_2 bit from the binary counters is used to enable the multiplier. After 64 clock pulses EN OUT goes low, stopping the multiplier at 1088_2 . The rate pulses from U4 are temporarily held in a D-type flip-flop, U2. When released, these pulses are synced with the next clock pulse and also stretched into a full clock period for the SWALLOW ENABLE line. U2 is only enabled between counts 1024_2 and 1088_2 , the same as the rate multiplier. The RS flip-flop (U3) controls U2. A timing diagram is shown in fig. 5. The use of hard-wired BCD data from the thumbwheel switches prevents the rate multiplier from generating more than 19 pulses for the prescaler.

voltage controlled oscillator

One of the main criteria for vco design is that it be stable by itself. This synthesizer uses the Motorola MC1648 ECL logic oscillator (fig. 6). Of its many features, most important is its use of an external LC network as the frequency determining element. This type oscillator has less phase jitter than the RC switching oscillators (NE566 or MC4024).

The tank circuit consists of a Motorola MV109/209 varactor diode and a tuned line made from 3 inches (7.6mm) of miniature Teflon coax (RG-17U). This combination is extremely effective in combating the microphonics that plague other configurations. You

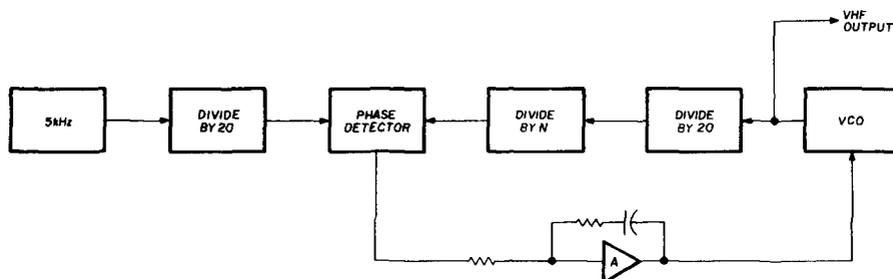


fig. 3. Block diagram of the basic phase locked loop system. With a vco that runs greater than about 50 MHz, a prescaler is required for the loop.

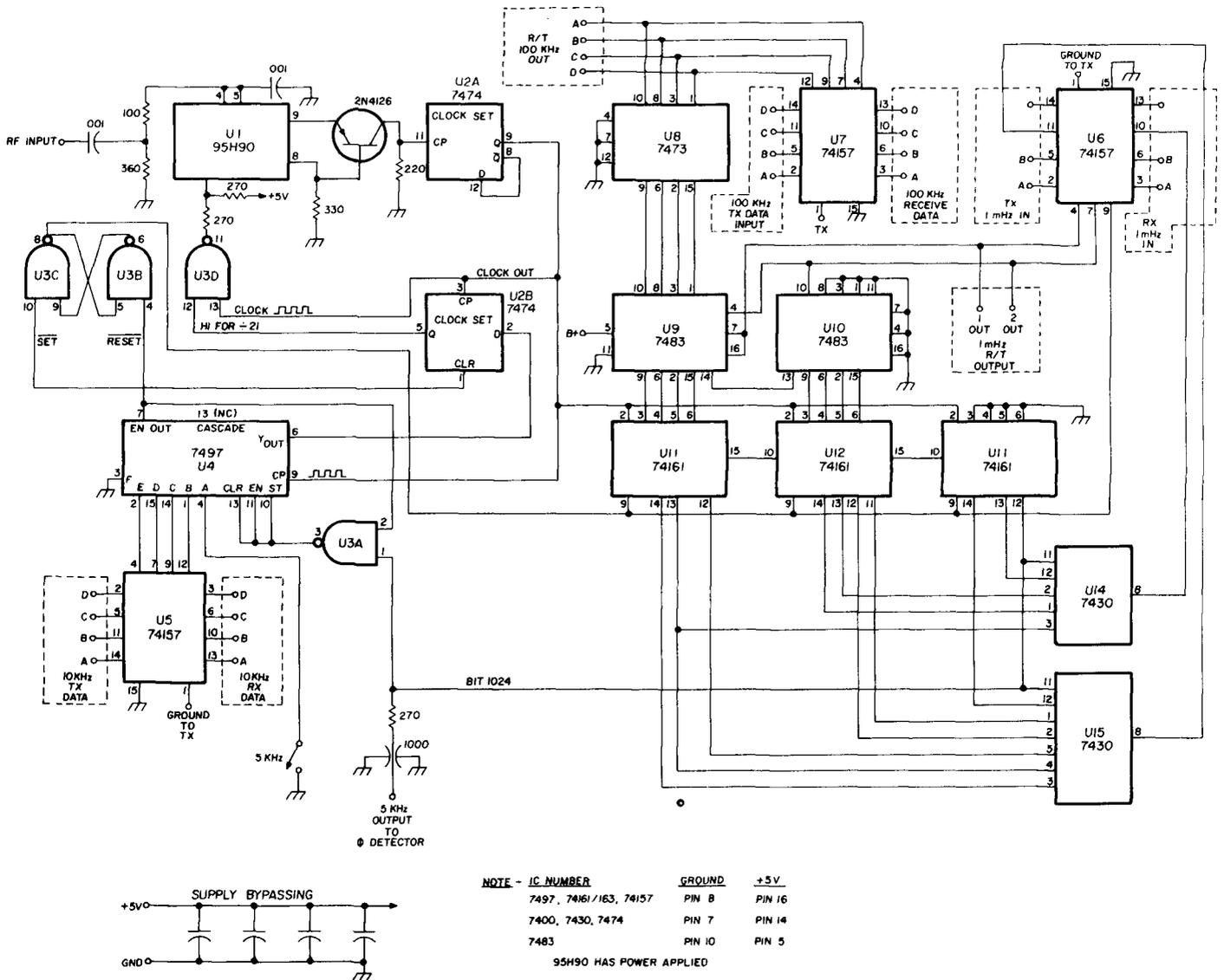


fig. 4. Schematic diagram of the digital board. The prescaler section contains the 95H90 and the dual-D flip-flop. Pin 2, SWALLOW ENABLE, controls whether the prescaler is in the divide by 20 or 21 mode. The 0.001 μ F capacitor connected to pin 5 of U1 should be mounted close to the IC. The V_{CC} line requires bypassing with several values of capacitors to eliminate any switching transients from appearing on the line. Low-power Schottky ICs have been tested, and are recommended for replacement of the 74161/163, 7483, 74157, 7430, and 7474. When transmitting, the line marked TX should be grounded.

can substitute any combination which will tune from 144 to 159 MHz with a tuning voltage of not less than 2.5 volts nor more than 10.5 volts.

The MC1648 drives three rf amplifiers in parallel. Each stage is untuned and delivers at least 20 milliwatts into a 50-ohm load. Even though hand-wound transmission line transformers are used, the lack of tuning makes the boards less prone to parasitics. One output drives the digital logic, another is used for the receiver local oscillator, and the last drives the transmitter. In this case, the "transmitter" is nothing more than additional power amplifiers.

A CMOS CD4046 is used as a frequency/phase

detector. During a channel change, it departs from true phase lock and forces the vco to slew back to the correct frequency. When this point has been reached, the CD4046's output becomes a series of pulses with a duty cycle that is proportional to the phase difference. As soon as the phase difference also reaches zero, the output from the CD4046 enters a third state that effectively disconnects it from the loop amplifier. When correction is needed, the detector switches into the appropriate state.

The advantages of the CD4046 over a simple phase detector are many. Among these are the faster response to large channel changes and also lower


reference frequency sidebands in the rf output. A simple digital phase detector has a square-wave output with a 50 per cent duty cycle when locked. This represents no dc output so no further frequency change is required. However, there is a large ac output at the reference frequency which can be difficult to remove. In the design presented here, a locked condition is signalled by an open circuit from the detector which considerably simplifies the loop amplifier design. In practice the phase detector cannot operate at a zero phase difference and it has been set to produce an output pulse of approximately 5 per cent duty cycle.

The CD4046 drives a loop amplifier consisting of a MC1458V dual-operational amplifier. Despite what some articles on PLL would lead you to believe, more than just a lowpass filter is needed for optimum results. The first op amp could be classed as an integrator, but it also provides three time constants which insure stability of the loop. The second op amp is a simple 12 dB/octave lowpass filter which reduces the 5-kHz ripple on the tuning voltage. The simpler approach of using a lowpass filter versus a notch filter is justified since the performance improvement is very small.

The 5-kHz reference frequency is generated by the CMOS CD4060. This IC contains a 14-stage binary divider and three inverters for use as a crystal oscillator. The only other parts required are a parallel-resonant crystal and a few resistors and capacitors. The trimmer adjusts the crystal exactly to frequency and sets the final output accuracy.

audio

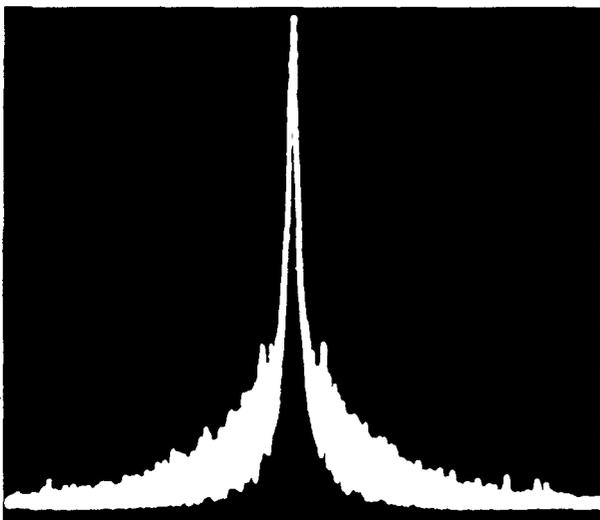To produce direct fm, the audio is summed with



This spectrum analyzer photograph shows the output within 50 kHz of the center frequency. The 5-kHz sidebands can be seen to be 54 dB down from full output.

the tuning voltage after the op amps. The following requirements should be adhered to:

1. Audio compression and/or limiting should be used to hold constant deviation level.
2. Employ rapid rolloff past 3500 Hz to keep the radiated bandwidth narrow.

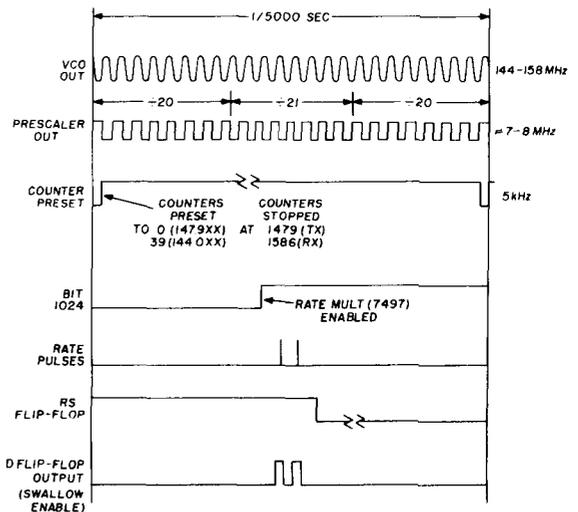


fig. 5. Programmable divider timing diagram. This diagram represents a frequency of 14X.X10 MHz.

3. Use standard 75 μsec pre-emphasis (fig. 7). This is direct fm and the audio will sound muffled if pre-emphasis is not included. The pre-emphasis should be applied after the clipping and filtering. There should be 1 volt p-p available after preconditioning the audio. As a warning, the vco has a sensitivity of 5 MHz/volt. Therefore, it only takes 1 mV of noise in the system to make this synthesizer useless in a narrowband fm system. Ground noise, loops, and proximity to other systems can also cause problems. The vco assembly *must* be housed in a completely sealed metal box. Diecast aluminum boxes are the best. Attempts at ultimate miniaturization will only produce 5 kHz whine, and possibly 60 Hz hum on the signal.

circuit board checkout

Digital card. The initial testing of the digital board can be done at a frequency that will allow the pulses to be seen without relying on a high performance oscilloscope. An approximately 0.8 V p-p, 10-MHz signal should be injected into pin 1 of the 95H90. With power applied, the prescaler will run warm and total current drain will be about 600 mA for standard TTL. The complementary output pins, eight and nine, of the 95H90 should show an ECL level square-wave (3.3V to 4.1 V). The waveform will alternate be-

tween one tenth and one eleventh of the input frequency, which will cause blurring of the oscilloscope display. With the rest of the prescaler section working properly, the binary counters (U11-U13) will have a clock input on pin 2 that alternates between 1/20 and 1/21 of the input signal. If multiples of 100 kHz are selected, the input to the binary counters will be 1/20 of the input frequency; otherwise blurring will occur.

When it has been confirmed that the prescaler is functioning properly, the divide by $M + 1$ function can be disabled by applying 5 volts to pin 3 of the 95H90. If gates U14 and U15 are operating correctly, a narrow negative-going pulse will appear on pin 9 of

the binary counters. This pulse is used to load the binary counters after each cycle has been completed, 1479₂ for transmit and 1586₂ for receive. The ratio of the pulses at pins 2 and 9 of U11-U13 will correspond to the channel selected, 1440 to 1479. If the transmit line is high, 107 will be added to the ratios. This process can be extended to the entire programmable counter. With the 95H90 input as B and the pulses at pin 9 of the counters A, the ratios will be:

144.00 MHz Transmit	B / A - 28800
144.005 MHz Transmit	B / A - 28801
146.940 MHz Transmit	B / A - 29388
146.940 MHz Receive	B / A - 31528
147.995 MHz Receive	B / A - 31739

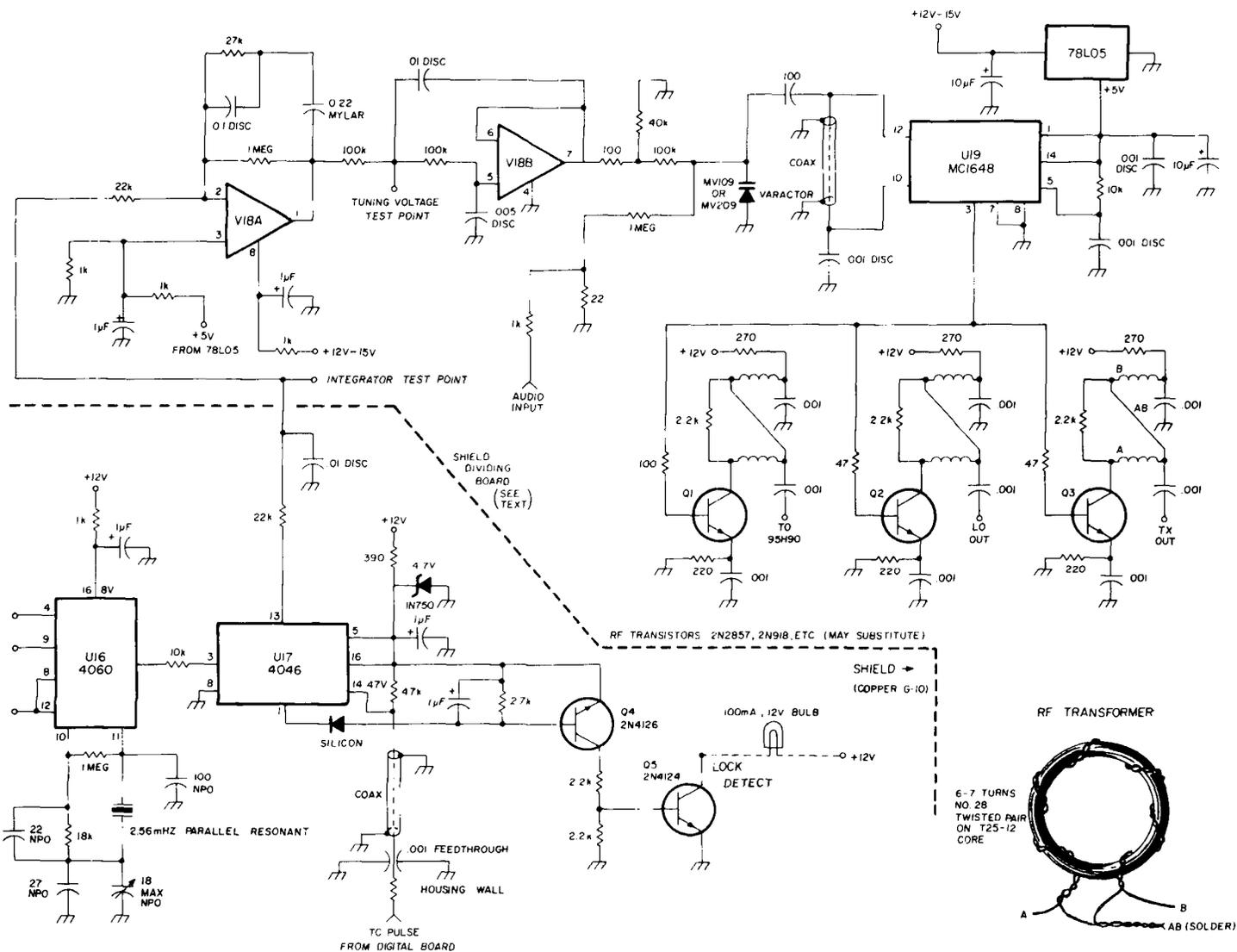


fig. 6. Schematic diagram of the rf circuitry for the synthesizer. All resistors are 1/4 watt; the electrolytics are dipped radial lead tantalums. The coax line can be replaced with 3 turns of number 22 AWG (0.6mm) wire. It should initially be wound to be 1/4-inch (0.6mm) in diameter. The final configuration will be dictated by the required tuning voltage vs tuning range. The rf transformers are 6 to 7 turns of number 28 AWG (0.3mm) twisted pair wound on a T25-12 core. The 2.2k resistors across the transformers are soldered on the back of the printed circuit board.

Rf Board. With power applied to the board from a 12-15 volt supply, the current drawn should be 60-75 mA. Check for the desired voltages on U16-U19 as shown on **fig. 6**. Testing of the vco and associated amplifiers will start at the vco and work back to the crystal oscillator. I recommend the Motorola MV109/209 varactor diode because of its wide ΔC range. This allows the vco to tune from 144 to 159 MHz with an input voltage of 2.5 to 10.5 volts. For test purposes only, the voltage can be supplied by a small adjustable supply connected to the test point just prior to the second op amp. Since the op amp has unity gain, correct operation of the vco can be determined from this point.

The integrator, first half of the MC1458, can be tested by grounding its inverting input. The vco should swing to at least 159 MHz when the junction of the two 22k resistors (integrator test point) is grounded. Conversely, it should move to below 144 MHz when 5 volts is applied to the same point.

At pin 4 of U16 there should be a 40-kHz square wave that can be used to set the crystal on frequency. By using the 125th harmonic of the 40-kHz signal, the crystal can be zero beat against the 5-MHz WWV frequency standard. The phase detector requires a 5-kHz input that is TTL compatible.

To test the phase detector, connect an NE555, or similar, oscillator to the 5-kHz pulse input on the rf board. With a pulse frequency less than 5 kHz, the vco should be driven to its lower frequency limit. If the pulse frequency is decreased below 5 kHz, the vco should swing to its upper limit. At this point the boards can be connected together forming an almost complete synthesizer.

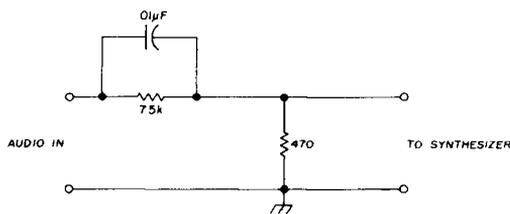


fig. 7. Schematic diagram of a standard 75 μ sec pre-emphasis network.

Switches. Due to the method of generating the correct presets for the binary counters and inputs to the rate multiplier, two forms of input data were used, BCD and \overline{BCD} . The information for the 10-kHz frequencies is in the normal BCD form, while that for the 100 kHz and MHz is \overline{BCD} . Using the basic premise that an open on a line is equivalent to a digital 1 (high) the appropriate switches can be selected. It should be remembered that a \overline{BCD} switch, not a BCD switch, produces four open circuits for a BCD zero. Regardless of the switch type you select, to use the switch in its true form connect

the common terminal to ground and pull the four outputs to 5 volts through 4 to 10-kilohm resistors. To complement the switch, connect the common lead to 5 volts and pull each output to ground through 270-ohm resistors. **Table 1** shows the correct BCD input information. To add 5 kHz to the output frequency, the 5-kHz line should be taken high (1).

The complete synthesizer can now be tested. The appropriate inputs and outputs on the two boards can be connected with lengths of either miniature coax or twisted-pair cable. A small 12-volt lamp can

table 1. Synthesizer truth table

1 MHz	B A	100 kHz	D C B A	10 kHz	D C B A
144	0 0	0.0	1 1 1 1	0.0	0 0 0 0
145	0 1	0.1	1 1 1 0	0.1	0 0 0 1
146	1 0	0.2	1 1 0 1	0.2	0 0 1 0
147	1 1	0.3	1 1 0 0	0.3	0 0 1 1
		0.4	1 0 1 1	0.4	0 1 0 0
		0.5	1 0 1 0	0.5	0 1 0 1
		0.6	1 0 0 1	0.6	0 1 1 0
		0.7	1 0 0 0	0.7	0 1 1 1
		0.8	0 1 1 1	0.8	1 0 0 0
		0.9	0 1 1 0	0.9	1 0 0 1

be attached to the LOCK DETECT terminals. Since this is only a test, the output will not be very clean and the signal should not be put on the air. Connect one rf output to a frequency counter and terminate the third in 50 ohms. When power is applied to both boards the lamp should flash once and the synthesizer *should* be on the correct frequency. If the synthesizer does not lock at all, the lamp will remain lit.

troubleshooting

If there are problems, a return to the circuit board checkout phase might be appropriate. Remember that this is a feedback system and trouble in one section can cause apparent difficulty in another. A good way to troubleshoot the unit is to clamp the tuning voltage at some fixed value from an external power supply. If the vco will not tune within the desired range, lock cannot be achieved.

A more subtle problem is a locked synthesizer but with the output on the wrong frequency. The cause of this problem will be found on the digital board, assuming the initial 5-kHz signal is correct. Make sure that the components are soldered on each side of the printed-circuit board. Unless plated-through holes are used, it may be difficult to solder sockets on both sides of the board. One solution is to use Molex pins, another is to mount the sockets over spacers. If the synthesizer is still off frequency, observe the pattern of the errors.

1. No channel spacing less than 100 kHz. This means that the divide by 21 function of the prescaler is not being enabled. Start at pin 2 of the 95H90 and work back to pin 6 of the rate multiplier (U4).

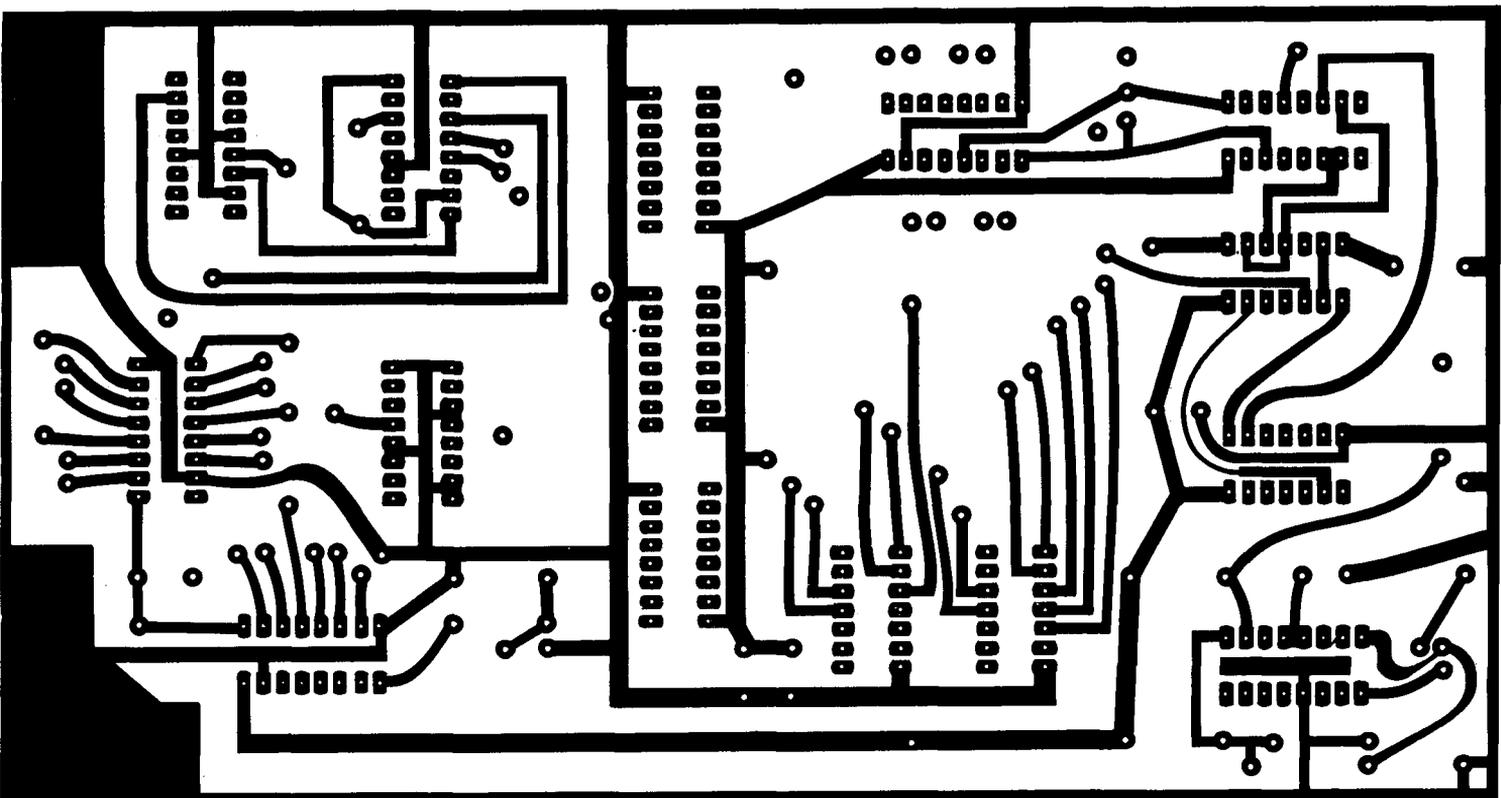
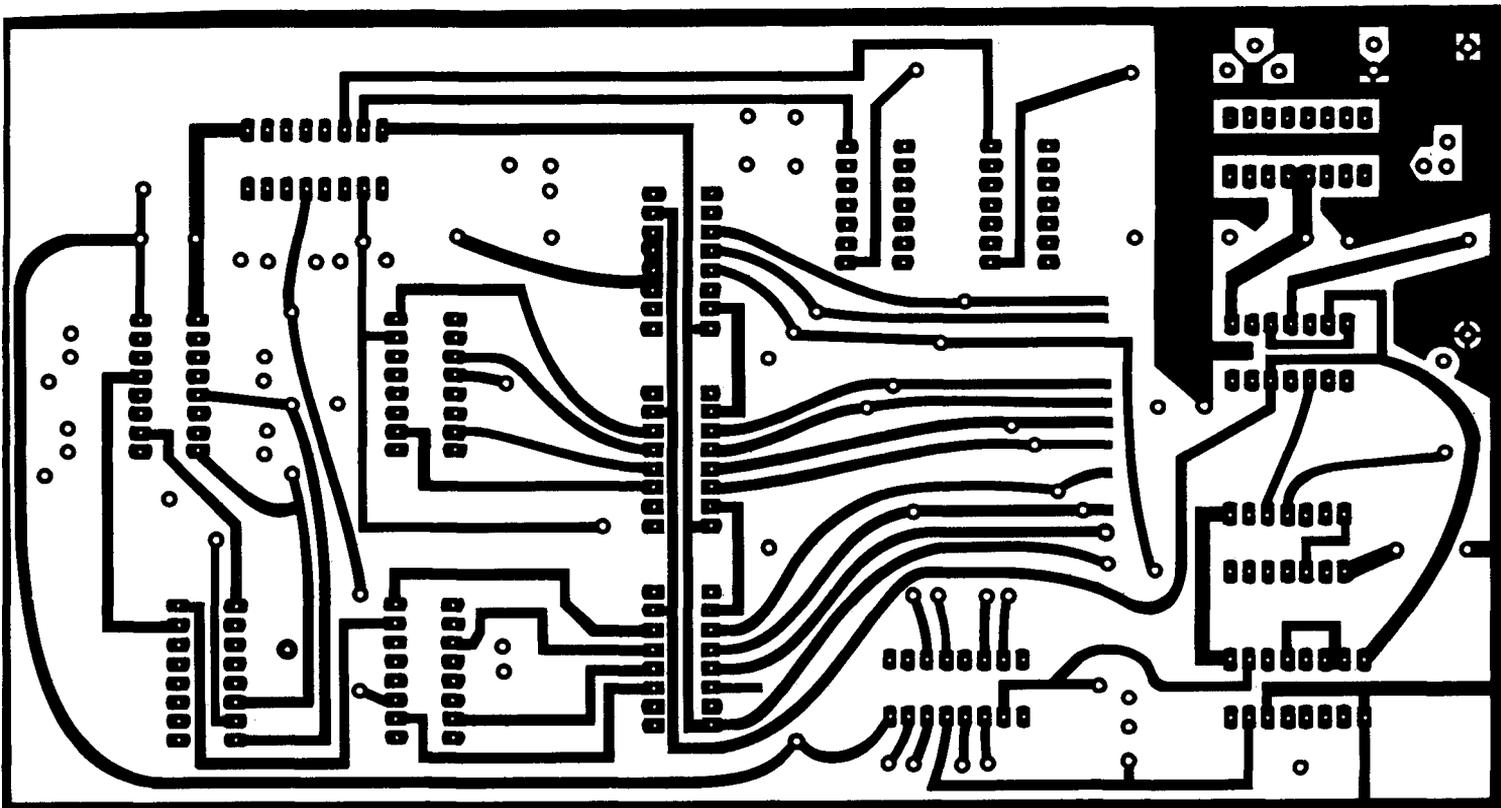


fig. 8. Circuit-board layout for the digital board. The top diagram shows the foil pattern for the top of the board, while the other side of the board is shown at the bottom.

2. Constantly high frequencies. The divide by 21 feature is being enabled too long.
3. Constant error in hundreds of kHz could mean that a 7483 full adder is faulty. They convert the BCD data into a binary code.
4. An output that is correct only on alternating binary increments means that a bit has been dropped between the 7483s and the preset inputs of the counters. For example, 144.000 to 144.200 is correct, 144.200 to 144.400 is wrong, and 144.400 to 144.600 is correct, etc.
5. If one of the 7430s (U14 or U15) is bad, either *all* the transmit or *all* the receive channels will be off.

Substitution is the best method of checking the ICs. You can save enormous amounts of time by mounting them in sockets, except the MC1648 and 95H90. If you don't have adequate test equipment, use a signal generator at a lower frequency to test the digital board.

synthesizer related problems

With the techniques used to generate this type of synthesized equipment, there can be many problems

that are system oriented. Some areas may require a look at the overall performance before the basic problem can be solved.

1. Sidebands at the TTL clock rate are caused by insufficient isolation between the circuit boards. If these sidebands are radiated by your transmitter, they are illegal; they will appear at the output frequency divided by 20, $144.00 \pm 7.2 \text{ MHz}$, $\pm 14.4 \text{ MHz} \pm 21.6 \text{ MHz}$, etc. The general cure for this type of problem is to put the rf board into a sealed metal box (leads that enter the box should go through $0.001 \mu\text{F}$ feedthrough capacitors).

2. This synthesizer delivers 10 kHz p-p deviation with less than 0.2 volt input so it will be prone to over-modulation. The deviation can be set quite easily if you make use of the synthesized local-oscillator output. With this output connected to a receiver, modulate the synthesizer until the audio level is the same as a local repeater. It doesn't matter to the discriminator whether it's the actual incoming signal that is being modulated or the local oscillator. For normal operation though, use a relay contact to short out the audio line during receive periods. Otherwise, audio feedback will occur.

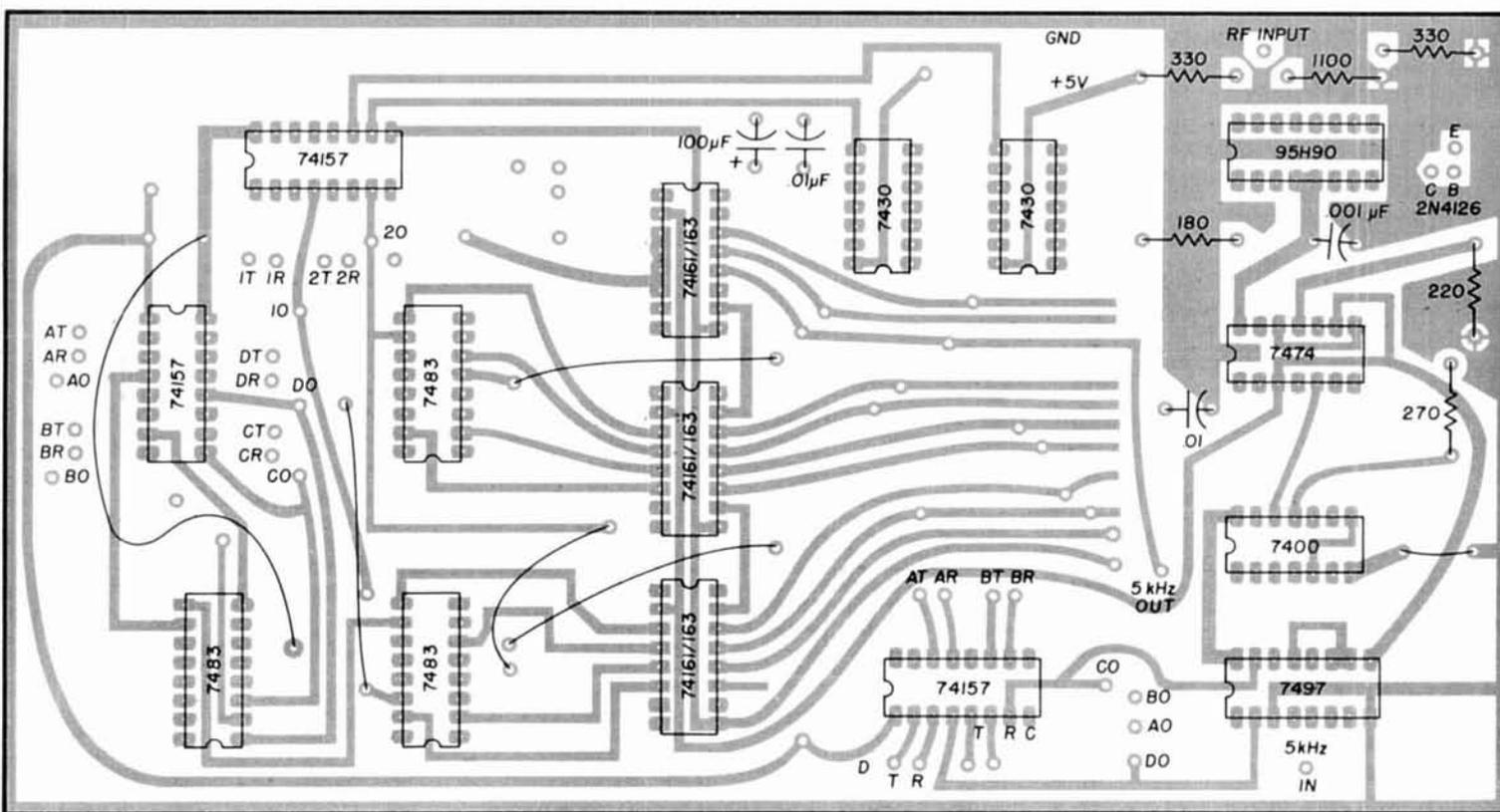


fig. 9. Component placement for the digital board.

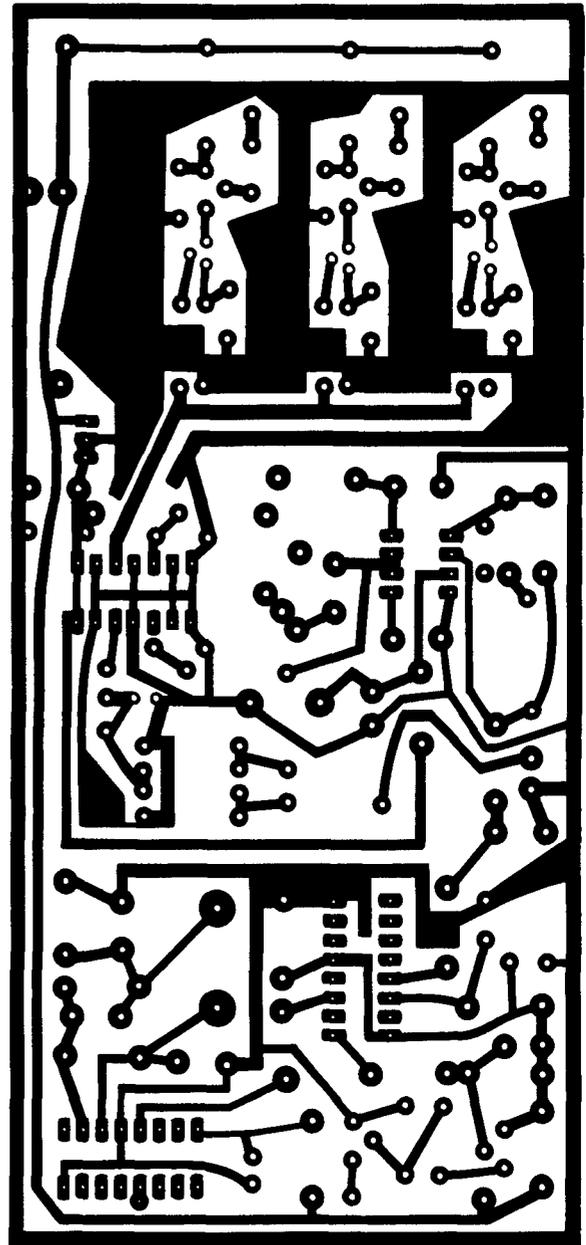
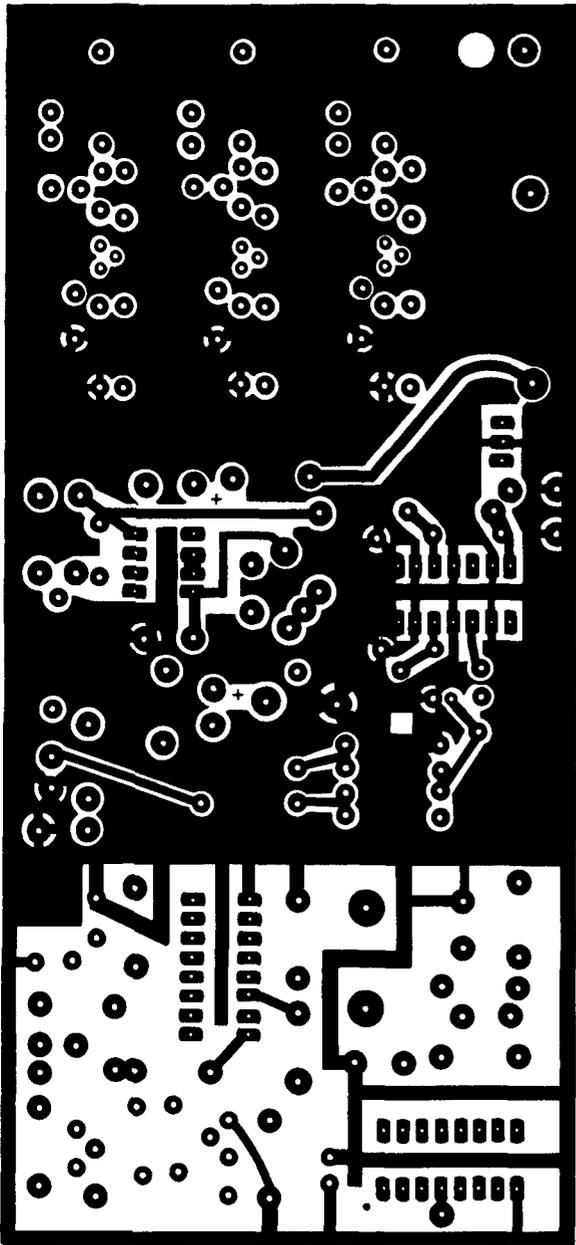


fig. 10. Circuit-board layout for the rf board. The top of the board is shown at the left and the bottom at the right.

3. Sidebands at 5 kHz cause annoying whine in your receiver and will be transmitted as well. Any sidebands experienced are caused by the physical placement of the rf board. Also, the shield between the portions of the board must be in place. This can be made from a piece of double-sided printed-circuit board. The output of the digital board must enter the enclosure through the resistor and capacitor combinations shown on the schematic diagram (fig. 4).

4. Receiver birdies are possible if the programmable divider is not shielded. Microphonics are not a problem and the enclosure does not have to be some type of sealed box. To avoid the problem of many feed-through capacitors for the digital switches, I suggest

that you mount the switches inside this box.

If you follow the previous suggestions, a clean transmitter should be no problem. I use four amplifier stages to directly increase the output to 40 watts. The LOCK DETECT output should be used to prevent keying the transmitter if the synthesizer is running wild.

receiver interfacing

To be entirely free of birdies, on-channel spurious radiations must be on the order of 100 dB below the local-oscillator level. Achieving this requires constant attention to small details such as shielding, removal of ground loops, and maintaining isolation. Certain receiver designs can give you perhaps 20 dB margin against such birdies (this assumes the birdies are

the MC1648 do not fall off quite as fast as those of a well designed discrete vco. The difference is slight and transmitter performance is unaffected. Residual audio fm measures less than 100 cps in this design. However, adjacent channel rejection in the receiver will be degraded. In normal operation, crystal-controlled equipment would be able to maintain DX communications within 10 kHz of a repeater channel. This design will require a spacing of about 15 kHz from the active channel. The difference is not noticeable unless your receiver has a good quality i-f filter and the shielding necessary to make full use of it. Also, you'd have to check closely to notice the difference. It is worth mentioning that Heathkit chose the same vco for their down-converting multiple-crystal synthesizer; they were able to attain a 30-kHz selectivity of 60 dB minimum.

convenience options

Because the synthesizer has the BCD frequency data available at all times, some other type of display can be connected. It would be much easier to see a seven-segment display in the dark than the thumb-

wheel switches. In fact, you do not need switches at all. The channel information could be generated by a circuit that would scan a frequency range until a signal is detected. The combinations are almost endless. Remember though, both BCD and $\overline{\text{BCD}}$ data is required.

conclusions

I hope that this article has removed some of the air of black magic that seems to have been associated with frequency synthesizers in the past. Unlike other articles, this one was concerned with how to get the radio to work, what you can expect to go wrong with it, and what you can do about it. Most of the literature on synthesizers has been an endless tirade about Laplace transforms and loop stability. These are important, but a critically damped response and the associated theoretical model by themselves only make a good BSEE senior term paper. This unit has been on the air for a year at WB2CPA, and successful duplication should not pose a problem to a reasonably competent amateur.

ham radio

TS-1 MICROMINIATURE ENCODER-DECODER

- Available in all EIA standard tones 67.0Hz-203.5Hz
- Microminiature in size, 1.25x2.0x.65" high
- Hi-pass tone rejection filter on board
- Powered by 6-16vdc, unregulated, at 3-9ma.
- Decode sensitivity better than 10mvRMS, bandwidth, ± 2 Hz max., limited
- Low distortion adjustable sinewave output
- Frequency accuracy, ± 25 Hz, frequency stability ± 1 Hz
- Encodes continuously and simultaneously during decode, independent of mike hang-up
- Totally immune to RF

Wired and tested, complete with K-1 element


\$59.95

K-1 field replaceable, plug-in, frequency determining elements

\$3.00 each

COMMUNICATIONS SPECIALISTS

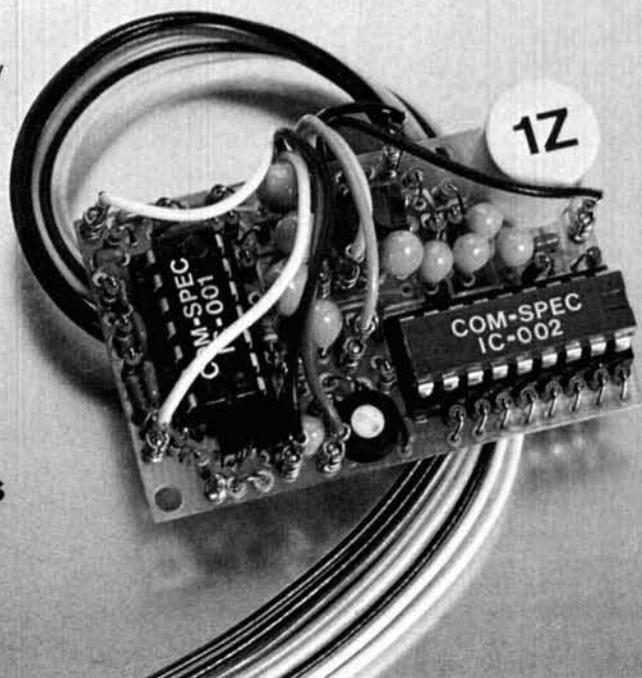P.O. BOX 153
BREA, CALIFORNIA 92621
(714) 998-3021



how to design Yagi antennas

Discussion of a new
Yagi design method,
developed at the
National Bureau of Standards,
which allows you
to design Yagis
for your own
operating requirements
with optimized,
reproducible gain characteristics

Have you ever wondered how to design a really good Yagi for your own requirements rather than just guessing, or using an existing design? If so, this article should be just what you are looking for. By using the information presented here you can design your own optimum Yagi for any frequency, from hf through uhf, with booms up to 4.2 wavelengths long.

Up until now, there has been little design information for Yagi antennas in the amateur literature. Kmosko and Johnson¹ designed a 13-element Yagi at 144 MHz but gave information only on that specific model. Greenblum² provided ranges of design values but was not specific as to exact sizes. The tables from Greenblum's article have appeared in recent *ARRL VHF Handbooks* and *Antenna Handbooks*, and several amateurs have reported good correlation using the mean values specified. Recent articles in the professional journals (such as the *IEEE Professional Group on Antennas and Propagation*, and others) have published computer-aided designs, but specific *cook-book* information is not available.

Now, for the first time, a straightforward approach to Yagi designs of various sizes and gains is available.³ It is the result of an exhaustive study by the National Bureau of Standards in the early 1950s to explore all the major antenna types (Yagis, corner reflectors, rhombics, etc.) suitable for use on vhf

By Joseph H. Reisert, Jr., W1JR, 17 Mansfield Drive, Chelmsford, Massachusetts 01824

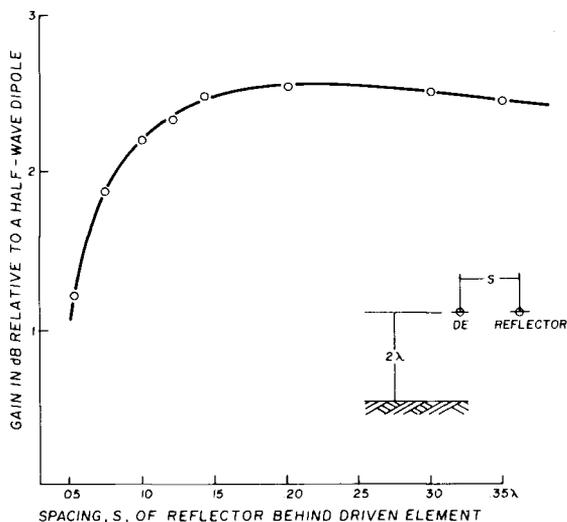


fig. 1. Gain in dB of a driven element and reflector for different spacings between elements.

ionospheric scatter. The NBS report tabulates all the design information necessary to construct six different boomlength Yagis (this portion of the project took nine man years to complete). The only known amateur use of these data are the W0EYE 432-MHz Yagi⁴ and several unpublished Yagi designs by W0PW (ex W0EYE) and W1JR.

This NBS report shows the interrelationship between director and reflector diameters, lengths, and spacings, as well as the effects of a metal supporting boom. Optimum designs and gains for various boomlengths from 0.4 to 4.2 wavelengths are shown along with nomographs for designing a Yagi for your own operating requirements. Those readers who are interested in all the specifics will find the NBS publication invaluable. This article will highlight the results and present all the information necessary to design such Yagis; several working design examples will also be discussed.

reflectors

During the NBS investigation into optimum Yagi design, various reflector lengths and spacings were tried on a two-element Yagi. As can be seen from fig. 1, maximum gain is 2.6 dBd, peaking broadly at 0.2λ behind the driven element. Hence, all the Yagi designs presented here are optimized using this reflector spacing.

The NBS engineers tried various other reflector configurations in order to realize any possible increase in gain. The trigonal configuration shown in fig. 2 yielded the maximum increase, 0.75 dB over a single reflector, when tested on a Yagi 4.2λ long. It should be applicable to the other designs and may be desirable if high front-to-back ratios are desired.

The heart of any Yagi design is the director. Extensive tests have shown that the diameter, length, and spacings are all interrelated. Also, it should be pointed out that these parameters become increasingly critical as the number of directors (and hence the boomlength) increase.

NBS tested various director lengths using spacings of 0.01 to 0.40λ on booms to 10λ long. Plots of these combinations show that there are optimum spacings for maximum gain. As the boomlength is increased, the optimum director spacing also increases. In addition, the gain of the antenna can be further increased if the length of each director is carefully chosen. It is noted that the diameter of the element affects its length, thicker directors being shorter than thinner ones. A comparison of maximum gain versus boomlength for uniform and optimized length directors is shown in fig. 3. Those readers desiring further information are referred to *NBS Technical Note 688*.³

A set of optimum director and reflector lengths normalized to 0.0085λ diameter elements is

table 1. Optimized lengths of parasitic elements for Yagi antennas of six different lengths (reflector spaced 0.2λ behind driven element, element diameter 0.0085λ).

Length of Reflector, λ	Length of Yagi in Wavelengths					
	0.4	0.8	1.20	2.2	3.2	4.2
1st	0.442	0.428	0.428	0.432	0.428	0.424
2nd		0.424	0.420	0.415	0.420	0.424
3rd		0.428	0.420	0.407	0.407	0.420
4th			0.428	0.398	0.398	0.407
5th				0.390	0.394	0.403
6th				0.390	0.390	0.398
7th				0.390	0.386	0.394
8th				0.390	0.386	0.390
9th				0.398	0.386	0.390
10th				0.407	0.386	0.390
11th					0.386	0.390
12th					0.386	0.390
13th					0.386	0.390
14th					0.386	
15th					0.386	
Spacing between directors, in λ	0.20	0.20	0.25	0.20	0.20	0.308
Gain relative to half-wave dipole, dB	7.1	9.2	10.2	12.25	13.4	14.2
Design curve (see fig. 4)	(A)	(C)	(C)	(B)	(C)	(D)

presented in table 1. These data, with respective gains noted, yield optimum performance for the six boomlengths which are shown. If a different element diameter is desired (isn't that always the case?), the elements can be scaled by using the nomograph in fig. 4. Element diameters from 0.001 to 0.04λ can be easily scaled as will be discussed later.

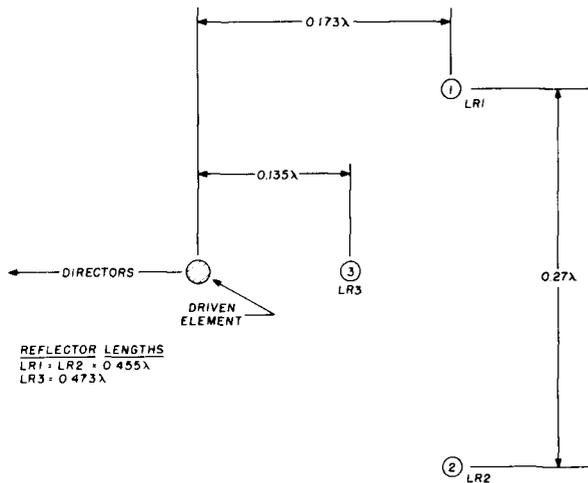


fig. 2. Trigrinal reflector arrangement (three reflector elements), when used with 4.2λ Yagi, provides 0.75 dB increase in gain (lengths not corrected for boom thickness).

The element data presented in the NBS report is based on an *air* boom which, in the original tests, was simulated by a triangular plexiglass structure. After optimization was completed, various booms and materials were tested to check the effects of the test boom. All measurements verified that the designs tested on plexiglass were optimum in an air dielectric. However, attempts to repeat these results using wooden booms were dismal. According to Peter Viezbickie, the author of the NBS report, changes in moisture and directivity due to the wooden booms made repeatability almost impossible despite various coatings applied to the wood.

Metal-boom Yagis were entirely repeatable if the elements were lengthened to compensate for the boom structure. At first glance, it may seem that a constant factor could apply. However, tests conducted by NBS showed that small diameter booms (with respect to wavelength) had less effect on element lengths than larger booms. These data are plotted on fig. 5 for boom diameters up to 0.04λ. Tests also showed that, for correction purposes, the effect of square and round booms were identical.

feed systems

Detailed feed systems are not discussed in the report. On most tests, a folded dipole using a 4:1 half-wavelength coaxial balun was followed by a stub tuner. However, any of the usual feed systems can be used.⁵ Reference 6 describes how to test these matching systems.

patterns

Finally, the NBS report shows radiation patterns for the *E* and *H* planes. For the sake of brevity, only the patterns for the 1.2λ and 4.2λ Yagis are presented in this article (see figs. 6 and 7). You will note the symmetrical pattern, the low side lobes, and the high

front-to-back ratio, all characteristics of a well-designed Yagi antenna.

Tests made by W6FZJ and W0EYE on a 15-element, 4.2λ Yagi for 432 MHz, designed with the method described in this article, showed that the antenna had about 1% vswr and 1-dB gain bandwidth, slewed to the low-frequency side of the center design frequency; performance above the center frequency fell off quite rapidly. It is estimated that the gain and vswr bandwidth for the 1.2λ Yagi is about 2%. It should be pointed out that the bandwidth of a Yagi is quite often limited by the matching and feed system, not by the basic Yagi design. In this respect most amateur beams use narrowband feed systems compared with Yagis designed for use in commercial service.

designing a yagi antenna

We will now proceed to design a 1.2λ Yagi for 50.1 MHz, a 2.2λ Yagi for 205 MHz, and a 4.2λ Yagi for

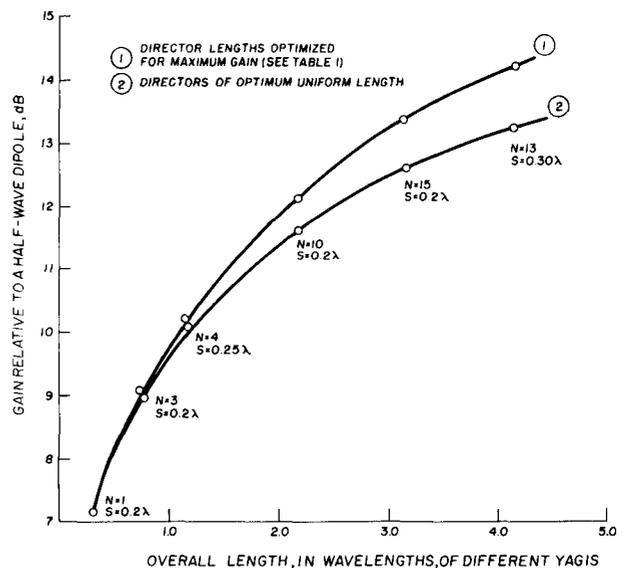


fig. 3. Gain comparison of different length Yagis, showing the relationship between directors optimized in length to yield maximum gain, and directors of optimum uniform length. *N* is the number of directors; *S* is the spacing between directors (reflector spaced 0.2λ on all antennas).

432 MHz to demonstrate how the NBS design material can be used. I actually built and tested each of these designs to verify the validity of the design data. In all cases the performance of the finished antennas matched the results reported by NBS.

The first step in any design is to choose the desired gain, compare it with the designs in table 1, and see if the stated boom length is within the desired range. Next, the element diameter should be chosen to fall within the specified ranges (0.001 to 0.04λ) on the design nomograph, fig. 4. Finally, the boom or supporting structure should be chosen.

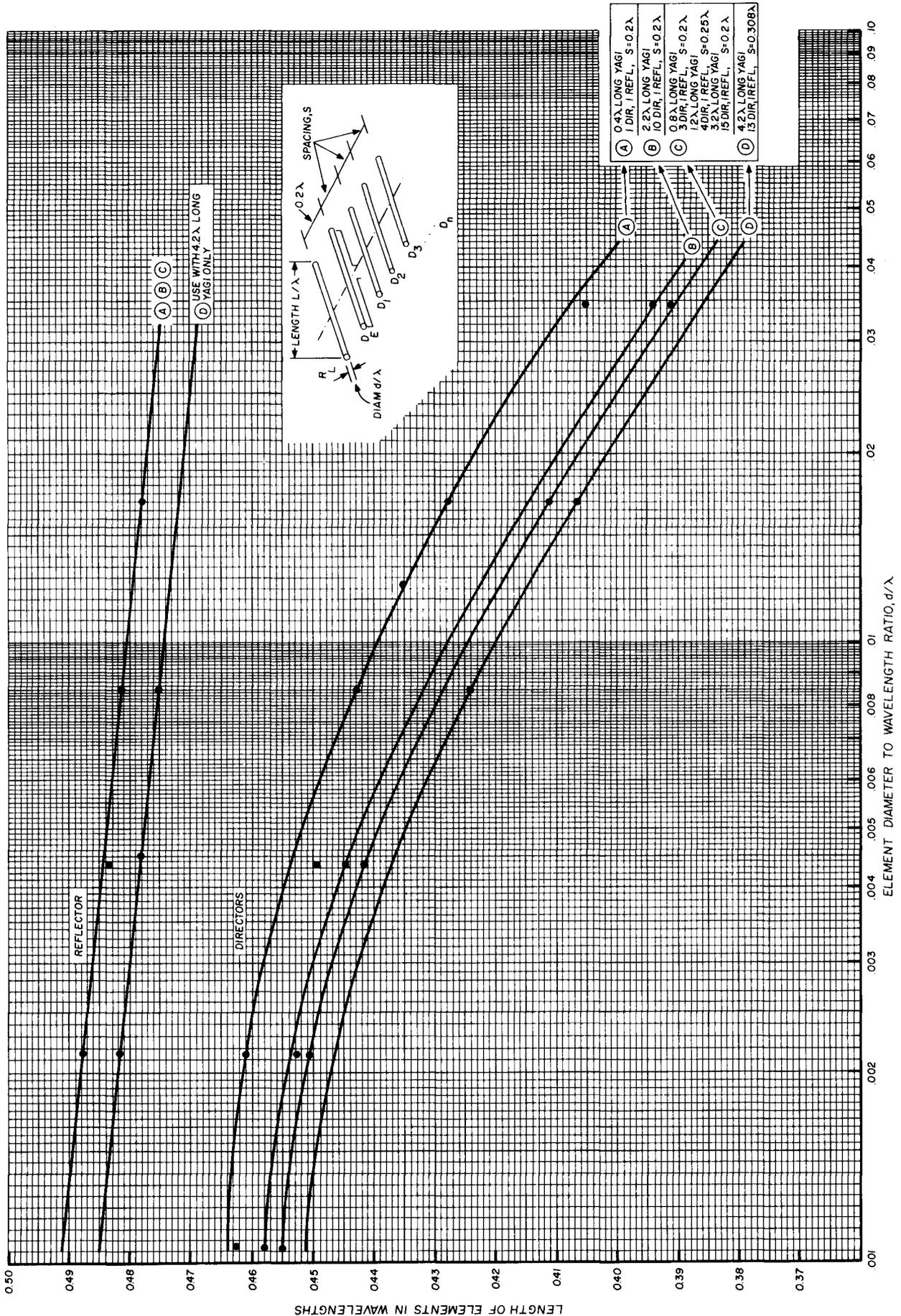


fig. 4. Yagi antenna design nomograph showing the relationship between element diameter to wavelength ratio (d/λ), and element length for different antennas. Detailed procedure for using this chart is presented in the text.

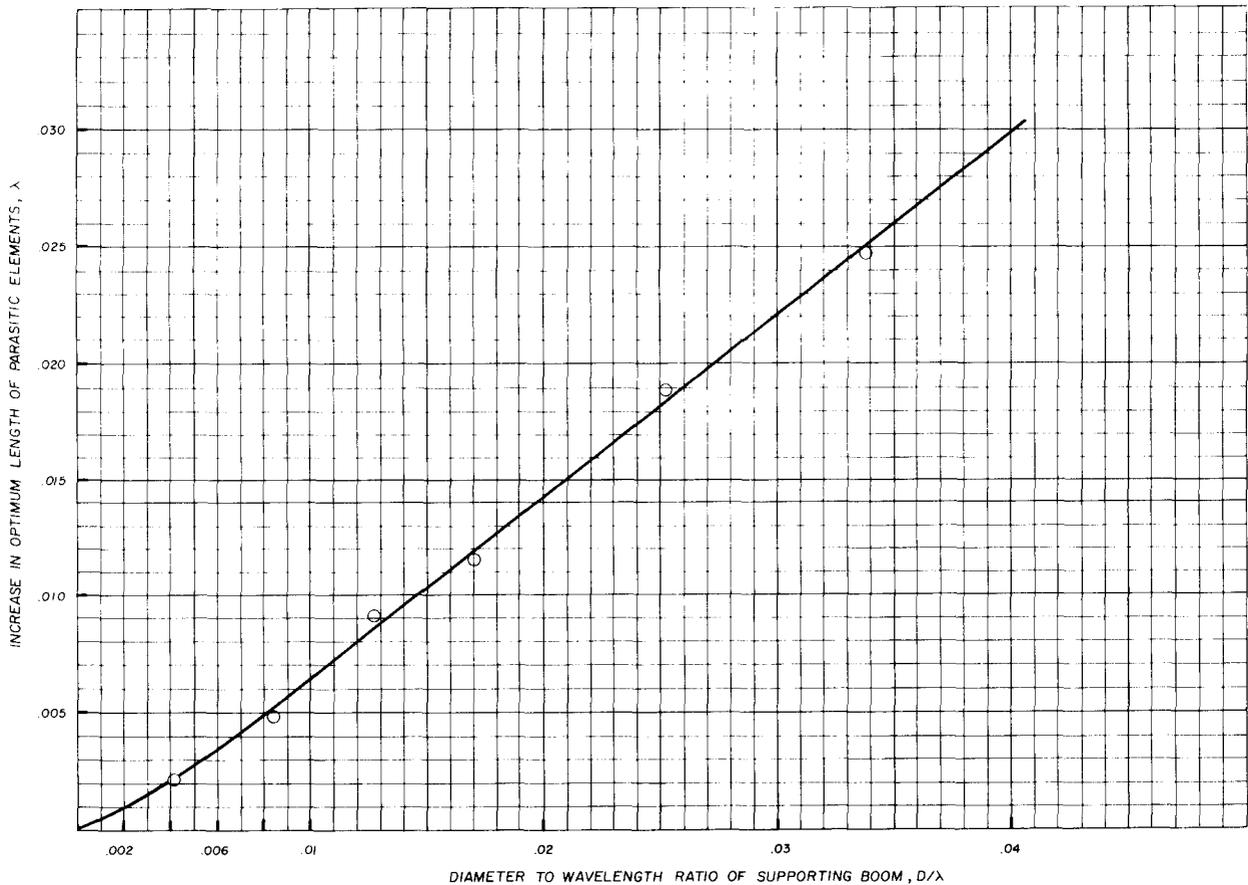


fig. 5. Graph showing the effect of a supporting metal boom on the length of the parasitic elements.

Example 1. It is desired to build a 6-meter Yagi with 10.2 dBd gain, using 0.5 inch (13mm) diameter elements mounted on insulating blocks above a 1.5 inch (38mm) diameter boom. This is the 1.2λ design in table 1.

The formula for wavelength is

$$L = \frac{11803}{F} \text{ (inches)} \quad (1)$$

$$L = \frac{29980}{F} \text{ (cm)} \quad (2)$$

where L = length
 F = frequency in MHz

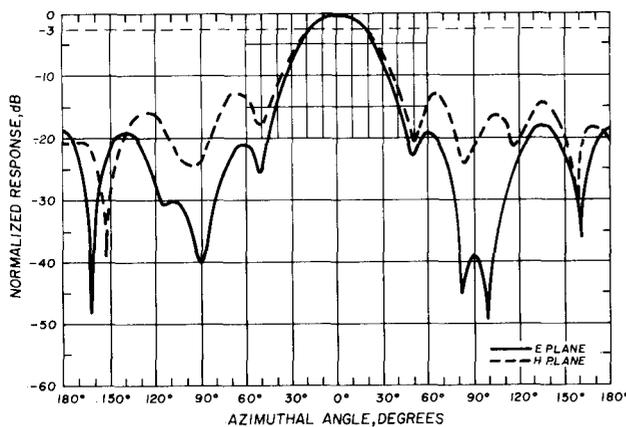


fig. 6. Radiation patterns of a 6-element, 1.2λ long Yagi, built with the dimensions shown in table 1. Beamwidth of the E plane is 40 degrees; H plane beamwidth is 42 degrees.

Frequency	50.1 MHz
Wavelength	235.6 inches (5.98 meters)
Element diameter (d/λ)	0.0021 λ
Reflector spacing	47 inches or 120 cm (0.2 λ)
Director spacings	59 inches or 150 cm (0.25 λ)
Boom diameter	not important, discussed later
Overall length	283 inches (approximately 24 feet) or 7.2 meters (1.2λ)

1. Plot the lengths of the parasitic elements for the 1.2λ design from table 1 on the design nomograph

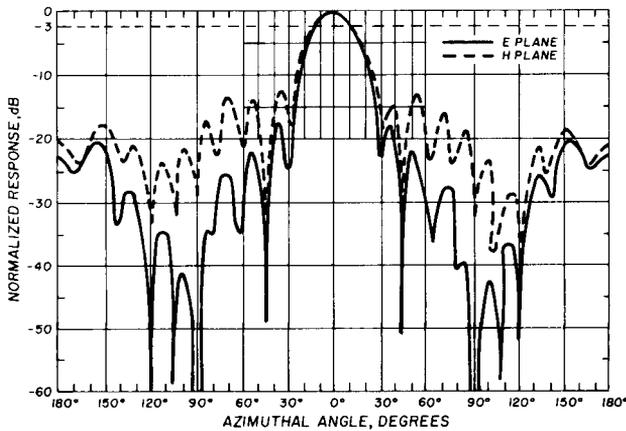


fig. 7. Radiation patterns of a 15-element, 4.2λ long Yagi. Beamwidth of the E plane is 26 degrees; H plane beamwidth is 29 degrees.

(see fig. 8) for parasitic elements with a diameter, $d/\lambda = 0.0085\lambda$.

$$L_R = 0.482\lambda$$

$$L_{D1} = L_{D4} = 0.428\lambda$$

$$L_{D2} = L_{D3} = 0.420\lambda$$

2. However, our element diameters are 0.0021λ so the element lengths must be adjusted. Draw a vertical line from 0.0021λ on the horizontal axis on the nomograph. This intersects the compensated lengths for the reflector and directors 1 and 4:

$$L_{R'} = 0.488\lambda$$

$$L_{D1'} = L_{D4'} = 0.451\lambda$$

3. Using a pair of dividers (or a compass), measure the distance between director 1 (D1) and director 2 (D2) determined in step 1. Transpose this distance from the point established in step 2 to the left along the 1.2λ Yagi curve to 0.0021λ to determine the compensated length for directors 2 and 3:

$$L_{D2'} = L_{D3'} = 0.446\lambda$$

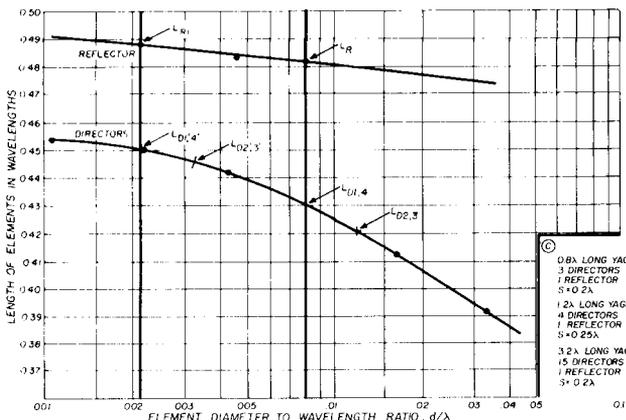


fig. 8. Use of the Yagi design curves (fig. 4) to determine the element lengths for a 6-element, 50.1-MHz Yagi on a boom 1.2λ long (see example 1 in text).

When I built this antenna I decided to use large element insulating blocks which I purchased from Swan Antennas (now KLM). Therefore, it wasn't necessary to put the elements through the boom. Since the wavelength is long with respect to the chosen boom diameter, I didn't feel that any boom correction was necessary. This was verified by subsequent tests. When the boom diameter represents a substantial portion of the operating wavelength, however, a correction for the boom diameter is required; this will be discussed in example 3.

The reflector and director lengths for the 50.1-MHz Yagi are as follows:

Reflector	$0.488\lambda = 115$ inches (2.92m)
Director 1	$0.451\lambda = 106.25$ inches (2.70m)
Director 2	$0.446\lambda = 105.06$ inches (2.67m)
Director 3	$0.446\lambda = 105.06$ inches (2.67m)
Director 4	$0.451\lambda = 106.25$ inches (2.70m)

The approximate length of the driven element can be calculated from

$$L = \frac{5500}{F} \text{ (inches)} \quad (3)$$

$$L = \frac{13970}{F} \text{ (cm)} \quad (4)$$

where L = length

F = frequency in MHz

Therefore, at 50.1 MHz, the length of the driven element is 109.75 inches or 2.79 meters. For simplicity I decided to use a gamma match and to attach the driven element to the boom with a U bolt. During the matching adjustments the driven element was short-

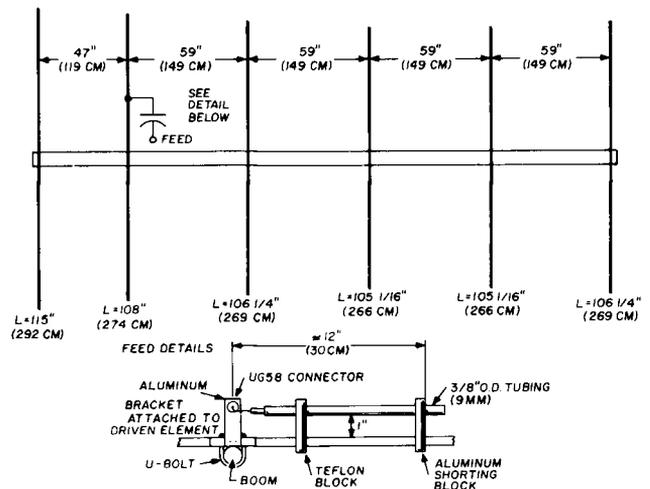


fig. 9. Layout of a 6-element Yagi for 50.1 MHz on a 1.2λ boom. All elements are $\frac{1}{2}$ inch (13mm) OD aluminum tubing, mounted on insulating blocks attached to a $\frac{1}{2}$ inch (38mm) OD aluminum boom. The gamma capacitor is approximately 12 inches (30cm) of RG-8/U coaxial cable with the outer jacket and shield removed, then inserted in a $\frac{3}{8}$ -inch (10mm) diameter tube.

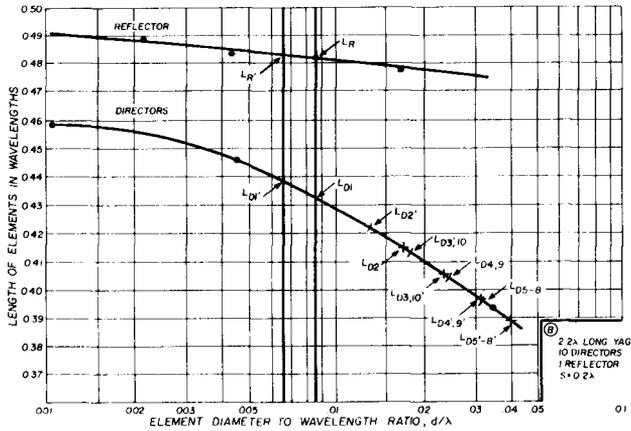


fig. 10. Use of the Yagi design curves (fig. 4) to determine the parasitic element lengths for a 12-element 205.25-MHz Yagi on a boom 2.2λ long (example 2).

ened to 108 inches (2.74m) for optimum vswr (the length of the driven element is not critical for maximum gain, as will be discussed later).

The completed 6-meter Yagi is shown in fig. 9. On-the-air receiving tests at W1JR have shown the 3 dB beamwidth to be between 40-45 degrees, while all sidelobes were at least 15 dB down; the front-to-back ratio was 18 dB. This agrees closely with the published NBS data.

Example 2. During the summer of 1973, when I was W6FZJ, transpacific tests to Hawaii were conducted on 220 and 432 MHz. Television video carriers seemed like a good propagation indicator so I designed a converter for Channel 12 on Mt. Haleakela on Maui. Since I had no good designs for a moderate gain Yagi

with low sidelobes (to discriminate against Channel 12 TV stations in California), I chose the NBS 2.2λ Yagi design using $3/8$ inch (1cm) diameter elements.

Frequency	205.25 MHz
Wavelength	57.5 inches (1.46 meters)
Element diameter (d/λ)	0.0065 λ
Reflector spacings	11.5 inches or 29.2 cm (0.2 λ)
Director spacings	11.5 inches or 29.2cm (0.2 λ)
Boom diameter	not important, discussed later
Overall length	126.5 inches or 3.21 meters (2.2λ)

1. Plot the director element lengths for the 2.2λ Yagi design from table 1 on the design nomograph (see fig. 10) for $d/\lambda = 0.0085$.

- $L_R = 0.482\lambda$
- $L_{D1} = 0.432\lambda$
- $L_{D2} = 0.415\lambda$
- $L_{D3} = L_{D10} = 0.407\lambda$
- $L_{D4} = L_{D9} = 0.398\lambda$
- L_{D5} through $L_{D8} = 0.390\lambda$

2. Since the chosen element diameters are 0.0065λ , draw a vertical line from 0.0065λ on the horizontal on the nomograph. This intersects the compensated length for the reflector and the first detector:

- $L_{R'} = 0.483\lambda$
- $L_{D'} = 0.4375\lambda$

3. Using a pair of dividers, measure the distance be-

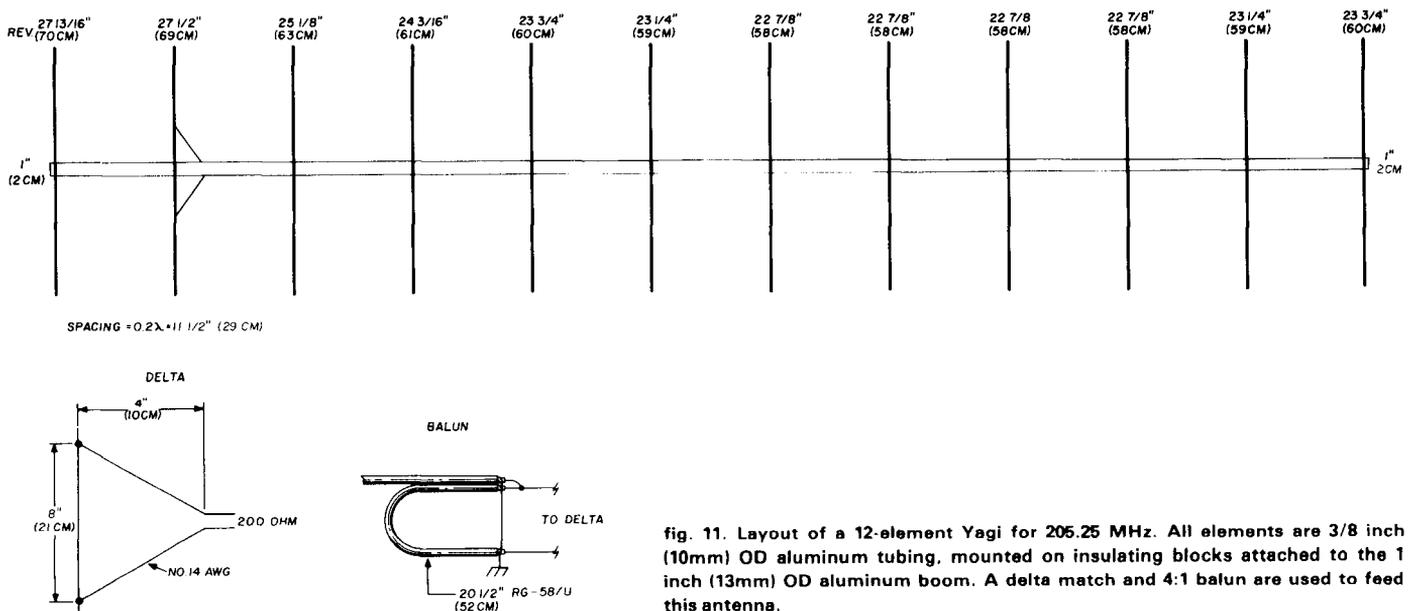


fig. 11. Layout of a 12-element Yagi for 205.25 MHz. All elements are $3/8$ inch (10mm) OD aluminum tubing, mounted on insulating blocks attached to the 1 inch (13mm) OD aluminum boom. A delta match and 4:1 balun are used to feed this antenna.

tween director 1 (D1) and director 2 (D2) determined in **step 2**. Transpose this distance from the point established in **step 2** to the left along the 2.2λ curve to determine the compensated length of director 2 ($L_{D2}' = 0.421\lambda$). Now span the distance between directors 1 and 3 (D1 and D3) with the dividers, and move this dimension along the curve, making sure to reference D1' (at the 0.0065 line). Follow this same procedure until all directors have been scaled. The remaining director lengths are as follows:

$$\begin{aligned} L_{D3}' &= L_{D10}' = 0.414\lambda \\ L_{D4}' &= L_{D9}' = 0.405\lambda \\ L_{D5}' \text{ through } L_{D8}' &= 0.398\lambda \end{aligned}$$

As in the case of the 6-meter Yagi, I decided to use element insulators which I purchased from KLM Electronics. Since the elements are mounted well above the boom, an element correction factor was not applied. The reflector and director lengths for the 205.25 MHz Yagi are as follows:

Reflector	$0.483 = 27\text{-}13/16$ inches (70.6cm)
Director 1	$0.4375\lambda = 25\text{-}1/8$ inches (63.9cm)
Director 2	$0.421\lambda = 24\text{-}3/16$ inches (61.5 cm)
Directors 3 and 10	$0.414\lambda = 23\text{-}3/4$ inches (60.5cm)
Directors 4 and 9	$0.405\lambda = 23\text{-}1/4$ inches (59.2cm)
Directors 5 - 8	$0.398\lambda = 22\text{-}7/8$ inches (58.1cm)

You will note that these lengths have been slightly rounded off. The NBS report states that tolerances of 0.003λ should be maintained (0.173 inch or 4.4mm at 205.25 MHz). Furthermore, tests made by WØEYE

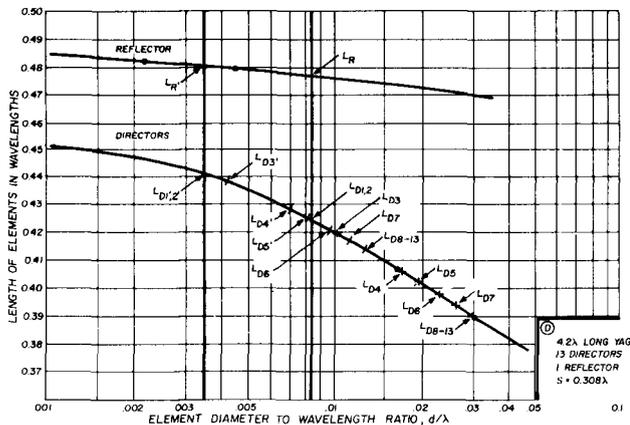


fig. 12. Use of the Yagi design curves (fig. 4) to determine the parasitic element lengths for a 15-element Yagi for 432 MHz; boom is 4.2λ long (example 3).

and W6FZJ in 1973 clearly showed that the gain and radiation pattern of a Yagi antenna degrades quite rapidly on the high side of the design frequency, but much more slowly on the low side. Therefore, if you must round off to a standard dimension, it is better to

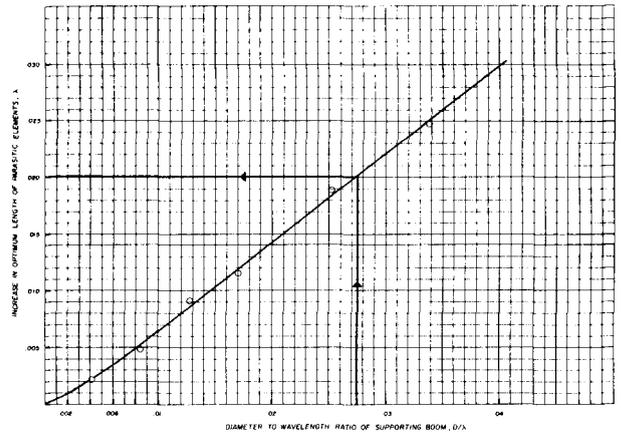


fig. 13. Supporting boom correction factor for the 15-element 432-MHz Yagi. Boom diameter is 0.0275λ (3/4 inch or 1.9cm at 432 MHz); length of each parasitic element must be increased to 0.2λ .

cut the director elements slightly shorter — not longer. Reflector length, on the other hand, should be rounded off on the long side. The element lengths for the Channel 12 Yagi were shortened to the nearest 1/16 inch, or only about 0.001λ .

For simplicity I decided to use a delta matching system and a 4:1 balun on this antenna. The driven element length was calculated using eq. 3. During final tests using the procedures outlined in reference 6 the driven element was extended slightly to obtain a 1:1 vswr. The length of the driven element is not a critical factor as long as the driven element is always shorter than the reflector.

The final design for the 205.25-MHz Yagi is shown in fig. 11. The desired discrimination to other Channel 12 television stations was achieved. This antenna is now in use at W1JR for indicating tropo, meteor shower, and aurora openings.

Example 3. The transpacific tropo tests mentioned in the previous example required an easily transportable antenna for the 432-MHz system to be installed at KH6BZF's station in Hawaii. I decided to use four 4.2λ Yagis similar to the WØEYE type⁴ and stack them accordingly. The humidity and salt air are high in Hawaii so the elements were mounted through the boom using knurled 3/32-inch (2.4mm) diameter brass rods; this is similar to the method used on the W6FZJ extended, expanded collinear array described in QST.⁷

For the sake of brevity, **steps 1, 2, and 3** will not be repeated here. However, the marked up nomograph for the 4.2λ 432-MHz Yagi is shown in fig. 13;

Since I decided to mount the elements through a metal boom, the elements must be lengthened to

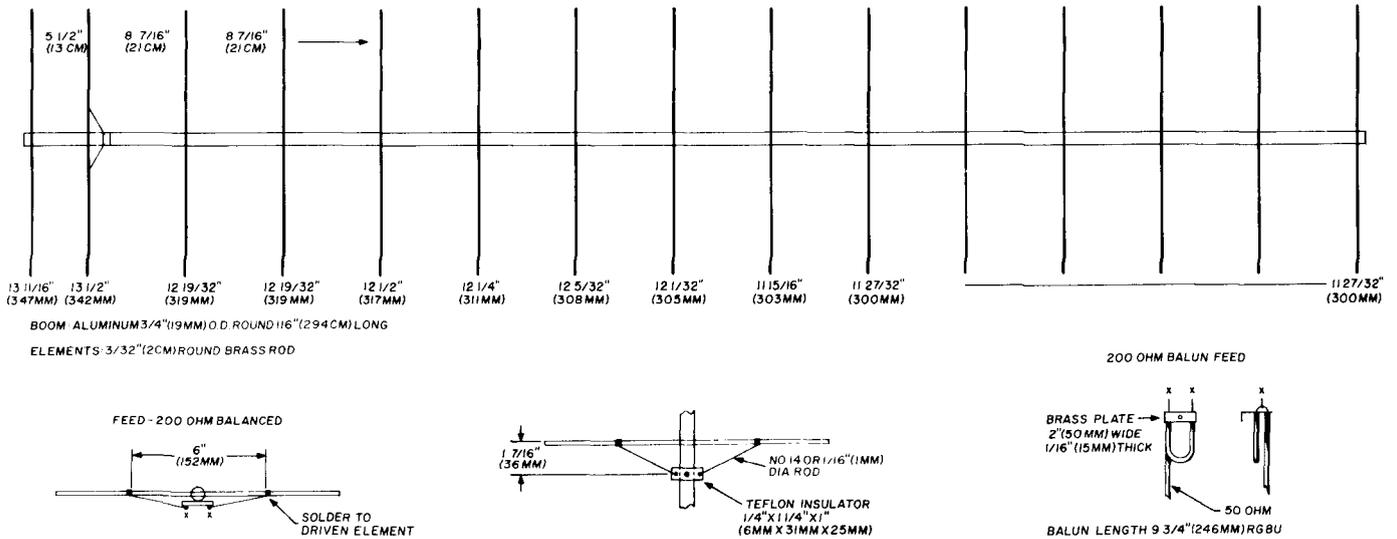


fig. 14. Layout of the 15-element 432-MHz Yagi on a 4.2λ boom. All elements are 3/32 inch (2.4mm) OD brass rod; elements are knurled and tapped into under-size holes in the 3/4 inch (1.9mm) aluminum boom. Element spacing of all directors is 8-7/16 inches (21.4cm); reflector is 5 1/2 inches (14cm) behind the driven element. Details of the delta matching system and 4:1 balun are also shown.

compensate for the shortening effect of the boom.

Frequency	432 MHz
Wavelength	27.32 inches (69.40 cm)
Element diameter (d/λ)	0.00343λ
Reflector spacing	5-1/2 inches or 13.9cm (0.2λ)
Director spacing	8-7/16 inches or 21.4 cm (0.308λ)
Boom diameter	3/4 inch or 1.9 cm (0.0275λ)
Overall length	115 inches or 2.915 meters (4.2λ)

- $L_{R'} = 0.480\lambda$
- $L_{D1'} = L_{D2'} = 0.441\lambda$
- $L_{D3'} = 0.438\lambda$
- $L_{D4'} = 0.428\lambda$
- $L_{D5'} = 0.425\lambda$
- $L_{D6'} = 0.421\lambda$
- $L_{D7'} = 0.417\lambda$
- $L_{D8'} \text{ through } L_{D13'} = 0.414\lambda$

To determine the corrected element length, first convert the boom diameter (3/4 inch or 1.9cm in this case) to wavelength (d/λ) or approximately 0.0275λ . Draw a vertical line from 0.0275λ on the boom correction nomograph (see fig. 13) to the DATA line. Move to left-hand axis and read the correction factor; 0.02λ for this antenna. Add this length correction factor to all elements as shown below.

Note that all the director lengths have been rounded off to the *short* side, as in example 2. The driven element length was calculated with eq. 3, but a better match was obtained when it was extended to 13 1/2 inches (34.3cm); a delta match with a 4:1 balun was used. The final design for the 432-MHz Yagi is shown in fig. 14.

This antenna stacks well at 1.6λ in the *H* plane, and 1.8λ in *E* plane. As tested at NBS, this quad Yagi array yielded 19.6 dBd. A one-way 432-MHz contact was attained between KH6BZF and W6FZJ in July, 1973 (don't ask me why it wasn't two-way because I'll cry loudly). During October, 1973, using only 200

Reflector	$0.480 + 0.02 = 0.500$	13-11/16 inches	(34.7cm)
Directors 1 and 2	$0.441 + 0.02 = 0.461$	12-19/32 inches	(32.0cm)
Director 3	$0.438 + 0.02 = 0.458$	12-1/2 inches	(31.8cm)
Director 4	$0.428 + 0.02 = 0.448$	12-1/4 inches	(31.1cm)
Director 5	$0.425 + 0.02 = 0.445$	12-5/32 inches	(30.9cm)
Director 6	$0.421 + 0.02 = 0.441$	12-1/32 inches	(30.6cm)
Director 7	$0.417 + 0.02 = 0.437$	11-15/16 inches	(30.3cm)
Directors 8 - 13	$0.414 + 0.02 = 0.434$	11-27/32 inches	(30.1cm)

watts and this array, EME signals from KH6BZF were copied and identified at W6FZJ. KH6BZF now uses this setup on Oscar 7, Mode B.

This article has presented a new and relatively precise way to consistently design and build Yagi antennas with optimum, reproducible gain characteristics — selecting a boomlength to suit your own requirements. Three design examples have shown Yagi antennas with demonstrated performance. If construction tolerances are held to 0.003λ maximum (0.001λ preferred), you should be able to design your own Yagis with the same excellent results. As pointed out earlier, director elements should be slightly shortened, while reflectors should be lengthened when rounding off the calculated dimensions.

Before actually starting to build a given design, double check your mathematics and scaling; it will pay off a 100-fold in time saved (and frustration). In those cases where the numbers in **table 1** do not agree exactly for the first director, reference at $0.0085 (d/\lambda)$ on the chart. The feed methods are not critical, and attention to the details outlined in references 5 and 6 should fill any voids in this article.

In closing, I would especially like to thank Don Hilliard, W0PW (ex W0EYE), who first introduced me to this information, and to Peter Viezbickie who, after much prodding by Don and myself, finally published this wealth of information. Now you, too, can be an expert in designing your own Yagi antennas.

references

1. J. Kmosko, W2NLY, and H. Johnson, W6QKI, "Long, Long Yagis," *QST*, January, 1956, page 19.
2. C. Greenblum, "Notes on the Development of Yagi Arrays — Multielement Beams," *QST*, August, 1956, page 11.
3. P. Viezbickie, "Yagi Antenna Design," *NBS Technical Note 688*, December, 1976, (available from Superintendent of Documents, U.S. Government Printing Office, Washington, DC 20420, SD Catalog no. C13.46:688, \$.65 per copy).
4. "15-element Yagi by W0EYE," *QST*, (World Above 50 Mc), January, 1972, page 96 (also see revision, page 101, March, 1972, *QST*).
5. J. Reiser, W1JAA, "Feeding and Matching Techniques for VHF/UHF Antennas," *ham radio*, May, 1976, page 54.
6. J. Reiser, W1JAA, "Matching Techniques for VHF/UHF Antennas," *ham radio*, July, 1976, page 50.
7. J. Reiser, W6FZJ, "VHF Antenna Arrays for High Performance," *QST*, December, 1974, page 38.

ham radio



Calling All Hams...

...All Hams Call Us!

It's Toll Free... So Dial Away!

1-800-325-3636

FOR NEW OR USED AMATEUR RADIO GEAR ... we're specialists and carry <i>in stock</i> most of the famous-brand lines. Or, we will talk trade.	FOR FAST, DOOR-STEP DELIVERY ... give us a call. You'll be amazed; for we guarantee we'll ship your equipment the same day. Plus, most shipments are PRE-PAID .	TO SAVE MONEY ... join thousands of our satisfied customers who buy from us as easily as from their local supplier. So, remember your call is Toll Free .
---	---	---

We welcome your Master Charge or Bank Americard

HAM RADIO CENTER, INC.

8340-42 Olive Blvd. P.O. Box 28271 St. Louis, MO 63132



the future of the amateur satellite service

During Phase III of the amateur satellite program AMSAT will place advanced communications satellites in high-altitude orbits which will allow long-range communications for up to 15 hours per day. This article discusses the capabilities of those satellites, and the financial support required from the amateur community

Amateur radio stands on the threshold of the most exciting and comprehensive change in its history, a change more revolutionary than that from spark to CW, or a-m to ssb, or the advent of vhf-fm repeaters. The Phase III Amateur Satellite Program, about which you'll be reading a great deal in the coming months, sounds more like science fiction than fact. However, in the past few years the *facts* have become increasingly clear: amateurs are already in command of the technology needed to produce a cost-effective satellite system — a *system*, not just a single satellite, capable of greatly enhancing the reliability of long-distance communications while simultaneously reducing the cost of the average amateur radio station.

One day, probably in late 1979, the first amateur Phase III satellite will be launched, and a new era in amateur communications will begin. It's possible that within ten years from today the majority of long-distance communications (over 50 miles or 80 km) by amateurs interested in DX, contests, traffic handling, and casual rag chewing will be by satellite. As a result, crowding of the high-frequency bands may be significantly reduced, even with a rapidly increasing amateur population.

Using satellite relays for global radio communications was first proposed by Arthur C. Clarke in the British journal *Wireless World* in 1945. Approximately 20 years later (March 9, 1965) the first active communications satellite, OSCAR 3, was launched. It may be hard to believe, but radio amateurs were communicating through OSCAR 3 months before the first commercial communications satellite, *Early Bird* (Intelsat I), was placed into orbit. Yet today, 12 years later, while satellites are carrying approximately two-thirds of all commercial transoceanic communications,¹ amateurs are still relying almost entirely on erratic high-frequency circuits for distant contacts.

Long-distance propagation on the high-frequency bands depends on signals being reflected by the ionosphere. A much more reliable communications system results when a satellite is substituted for the somewhat erratic ionosphere, and vhf or uhf bands are used for the radio links. You don't need to know much about the workings of the ionosphere to use the high-frequency bands; surprisingly, you don't need to know much about satellites to enjoy the advantages of this new mode of communications.

The satellite subsystem of primary interest to radio amateurs is the transponder, the electronic package which receives signals from stations on the ground and then retransmits them, on a different frequency with great amplification, back to earth. Although transponders are somewhat similar to 2-meter fm repeaters, there are significant differences: the linear transponders used on AMSAT satellites work equally well with ssb and CW signals, and they can simultaneously handle a large number of users.

To appreciate the communications capabilities which high-altitude spacecraft will provide we can

**By Martin Davidoff, Ph.D., K2UBC, 13803
Manor Glen Road, Baldwin, Maryland 21013**

compare communications links involving Phase III (high-altitude) satellites, Phase II (low-altitude) satellites such as OSCAR 6 and OSCAR 7 which are currently in orbit, and the 20-meter band. The comparison will consider a number of characteristics of specific interest to radio amateurs using these systems.

1. **Daily access time.** How many hours each day does the user have access to the satellite?
2. **Maximum communications range.** What is the maximum terrestrial distance over which two stations can communicate?
3. **Communications performance.** How strong and intelligible are received signals? Can openings over specific paths be predicted reliably?
4. **Communications capacity.** How many stations can use the satellite at the same time?
5. **Frequencies.** What frequency bands will Phase III satellites use?
6. **Tracking techniques and operating schedules.** Will the paper work involved in tracking and checking operating schedules be complicated and laborious?
7. **Ground-station equipment.** How much transmitter power and how large an antenna will be needed? Will commercial or surplus equipment be available for a moderate cost ground station?
8. **Antenna aiming.** Will the direction in which the antenna is pointed have to be continually adjusted while operating?
9. **Miscellaneous.** How will factors such as satellite lifetime, signal time delay, lack of skip zone, Doppler shift, and crowding affect users?
10. **Financing the Phase III program.** Can amateurs afford the Phase III program?

daily access time

The average amount of time that a satellite will be

This article focuses on the potential impact of the amateur satellite program on amateur radio over the next ten years. The author, Dr. Martin Davidoff, K2UBC, is an assistant professor of mathematics at a community college in Maryland where he directs a National Science Foundation project involving satellites and college level science instruction. In conjunction with the NSF project, he recently authored a textbook featuring the AMSAT-OSCAR series of satellites, *Using Satellites in the Classroom: A Guide for Science Educators*. K2UBC obtained his doctorate in Physics from Syracuse University in 1974 and has held an amateur license since 1956. **Editor.**

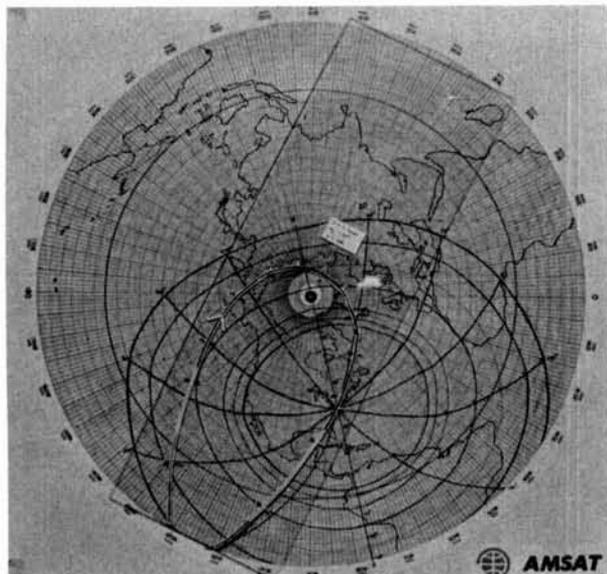


fig. 1. Photograph of *Satellable* style tracking nomograph for elliptical orbit of the type used by the Phase III-A spacecraft.

within range of a specific ground station each day (daily access time) is determined solely by the ground station's latitude. The first Phase III satellite will be injected into an orbit that initially places it within range of ground stations at mid-northern latitudes (this includes most of the United States) for about 15 hours each day, and within range of ground stations at mid-southern latitudes for about 5 hours each day. The first Phase III satellite will therefore provide northern hemisphere amateurs with as much access time as ten optimally spaced OSCAR 7 satellites! Can you recall the last time that 20 meters was open 15 hours per day on a regular basis?

As the years pass, ground stations will find that their average daily access time will change. By 1985 the first Phase III satellite will only be within range of northern hemisphere stations about 5 hours each day while southern hemisphere stations will have about 15 hours of access time each day. But don't despair, AMSAT is capable of producing two additional Phase III spacecraft before 1985. If these spacecraft are inserted into orbits similar to that of the first Phase III spacecraft, ground stations anywhere on earth will have access to at least one Phase III satellite for about 20 hours each day.

maximum communications range

Phase II satellites provide a maximum communications range of about 5000 miles (8000km). While this is adequate for Worked All States and DXCC, it's not very satisfactory by high-frequency standards. Phase III satellites will enable amateurs to communicate over a much greater distance — up to about 11200 miles or 18000 km — leaving only a very

small region at the opposite side of the earth out of range. The 20-meter band will continue to reward its followers with somewhat unpredictable openings to all parts of the globe.

If you've had the opportunity of listening to ssb stations using the 432/146-MHz transponder on OSCAR 7, you know that satellites are capable of providing *telephone quality* links. The 20-meter band can provide similar performance, albeit in a some-

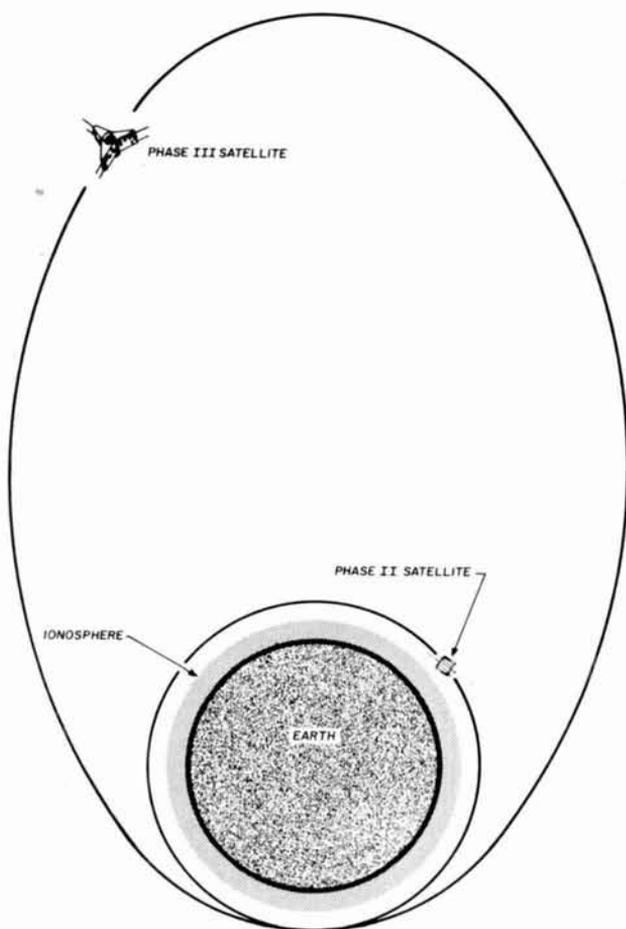


fig. 2. Relative altitudes of Phase II satellites, Phase III satellites, and the ionosphere — shown approximately to scale. Drawing does not take inclination of orbits into account.

what erratic manner. As an example, assume it's August, 1977, and you're interested in the Denver-Frankfurt path during January, 1978. The best prediction high frequency propagation experts can offer is that 20 meters will probably be open over the path of interest sometime between 1600 and 1800 UTC on about 15 days during January. If the first Phase III satellite was in orbit at this time, you could predict with better than 99% certainty, that the Denver-Frankfurt circuit would be open for several hours every day in January during time slots specified almost to the minute.

The advantages of a Phase III satellite for pre-arranged point-to-point schedules are even more im-

pressive when you consider a three-way contact between, for example, New York, London and Tokyo. Satellites will make such contacts possible daily with clocklike regularity. What are the odds of being able to accomplish this on 20-meters?

The received signal strengths observed by stations communicating through a high-altitude satellite will be largely independent of the distance between the stations. This results from the fact that the earth-satellite-earth distance and path loss are, for all practical purposes, constant regardless of how far apart the two ground stations might be. Since distance doesn't count, a station across town and one nearly halfway around the globe will produce similar signals if they are using similar equipment. In fact, listening to your own signal being returned from the transponder will indicate quite accurately how you sound to any station within range of the satellite.

communications capacity

The first Phase III satellite will provide a band of frequencies, nominally 150 kHz wide, capable of handling hundreds of simultaneous conversations. All users will be sharing the 50-watt satellite transmitter. Therefore, ssb and CW will be the preferred modes because they efficiently use the available satellite power. The satellite transponders will also be able to handle slow-scan TV, RTTY, and fm. But these modes should only be used in emergencies, or for special experiments coordinated with AMSAT, because they use a disproportionate amount of satellite transmitter power and, in the case of fm, excessive bandwidth.

A recent cost-effectiveness study suggests that crowding will not become a serious problem with the first Phase III spacecraft until 30,000 users are equipped to transmit on the uplink frequency.² To prevent crowding problems AMSAT plans an ongoing Phase III construction program which is designed to keep pace with a rapidly increasing user population. Placing an additional satellite in orbit every 24 months appears to be a realistic goal.

frequencies

The first Phase III satellite will include two transponders. Therefore, even if one transponder fails, the satellite will still be available for communication on a full-time basis. If possible, the two transponders on the first Phase III spacecraft will use reciprocal frequency combinations: one transponder will receive on 435 MHz and transmit on 146 MHz, the other will receive on 146 MHz and transmit on 435 MHz. Users will be able to compare the performance of both transponders and express their preferences for scheduling and for future satellites.

The amateur satellite program will continue to rely heavily on the 146-MHz and 435-MHz bands

throughout the 1980s. In the mid or late 1980s Phase III satellites are likely to include links at even higher frequencies such as the 920 MHz (32cm) and 2.3 GHz (13cm) bands; specific plans must await the outcome of the 1979 World Administrative Radio Conference.

Low-altitude (Phase II) satellites may continue to use 10 meter downlinks, a band which is not suitable for Phase III. Readers interested in the factors involved in selecting frequencies for amateur satellite systems are referred to the excellent paper by Ray Soifer, W2RS.³

tracking techniques and operating schedules

You may be pleasantly surprised to learn that you won't need to know anything about tracking to use a Phase III satellite. After the first Phase III spacecraft is in orbit, you'll be able to turn on your receiver (with an omni-directional antenna connected) and check to see whether or not the band is open (satellite within range) by simply tuning for signals. About 65% of the time stations in mid-northern latitudes (most of the United States) will find that they're in luck — signals will be present. If a second Phase III spacecraft is launched into a similar orbit, the probability of finding the band open will be about 90%. When the band is open, you'll switch to a beam antenna and home in on the satellite by peaking your S-meter on a beacon signal. The same antenna setting will work for all stations received via the satellite. Peaking the antenna every 15 minutes should be more than sufficient.

While the casual user can get away without any knowledge of tracking, some tracking skill (like a little insight into 20-meter propagation) will pay big dividends by enabling you to predict specific openings, to rare countries.

Many radio amateurs think that satellite tracking is very difficult and requires a strong mathematical aptitude. This just isn't true. Tracking is a simple, mechanical skill that takes only a few minutes to learn, and the only math needed is basic arithmetic. The ability to predict 20-meter propagation stands in sharp contrast; it's an impressive skill which requires a great deal of knowledge and experience.

Most tracking methods use some sort of nomograph which usually consists of a map and transparent overlay. Until recently everyone had to build their own tracking nomograph from scratch — a straightforward but tedious job which is no longer necessary since excellent commercial tracking aids are now available.⁴ With minor modifications the basic tracking techniques and nomographs used with OSCAR 6 and 7 will also work for the radically different orbits which early Phase III spacecraft will introduce. In fact, these same nomographs were ac-

tually used to evaluate the communications capabilities provided by the various orbits considered for Phase III. Construction details for Phase III tracking nomographs will be published in the near future.

In the past, OSCAR 6 and 7 users have sometimes complained about the bookkeeping involved in determining which OSCAR 6 orbits are available for general use and which OSCAR 7 transponder is scheduled to operate. The latest W6PAJ orbit calendar⁵ eliminates most of the bookkeeping drudgery by clearly listing the times and operating status for every OSCAR 6 and OSCAR 7 orbit during 1977. AMSAT will have a great deal of flexibility in scheduling future Phase III satellites because they will be controlled by onboard microcomputers that can be programmed by suitably equipped ground stations. User convenience will be the primary consideration when satellite schedules are chosen so bookkeeping requirements should be minimal. Tracking nomographs and orbit calendars will be made available for Phase III satellites soon after they're in orbit.

ground station equipment

Receiving. Ground stations working with Phase III satellites will need a good ssb/CW receiver capable of tuning a few hundred kHz around 146 MHz and/or 435 MHz.

Transmitting. A CW or ssb transmitter with about 50 watts output at 146 or 435 MHz will be required for the uplink.

Antennas. Ground station communication via the Phase III satellite will usually require moderate gain (10-15 dBi) beam antennas for receiving and transmitting. A typical antenna array may consist of two or more Yagis mounted on a common mast using a single set of azimuth and elevation rotators. The entire structure can be smaller and lighter than the average three-element beam used on 20 meters.

The selected antenna site should place the antenna clear of surrounding objects and relatively close to the operating position since feedline losses are an important consideration at 146 and 435 MHz. As a result, a chimney mount will often be as effective as a large tower. Neighbors (and zoning committees) will probably be unable to distinguish between a roof-mounted Yagi array for satellite work and a large television antenna!

Although beam antennas will usually be required for reliable communications, simple omnidirectional antennas will also be useful at times. For example, an omnidirectional receiving antenna can be used during the entire orbit to determine whether the satellite is within range. In addition, omnidirectional transmitting and receiving antennas will sometimes be convenient for communication when the satellite altitude is relatively low (less than 15% of each orbit).

General. The satellite ground station that you put together will no doubt depend on the size of your pocketbook, the equipment you already own, the amount of time you have to devote to the project, and the transponder frequency.

Here are some options that you may want to consider. If you presently own a good high-frequency receiver, a top-line vhf or uhf converter will provide you with a state-of-the-art receiving setup. For transmitting, the 10-watt multimode or ssb/CW transceivers currently available for 2 meters and 70 cm look like a good choice. A linear amplifier with 6-10 dB of gain will keep the transmitting antenna requirements within modest limits.

Numerous pieces of commercial equipment suitable for satellite work (converters, transmitters, antennas) are currently available off the shelf; I'm not speculating as to what the future may offer. If you have some time and a little technical knowhow, you'll be able to put together a relatively inexpensive station using a surplus fm strip as a CW transmitter and homebrew helix antennas. In any event, if you're currently thinking of investing in a vhf or uhf fm transceiver or amplifier, consider paying a little extra to obtain a rig with ssb/CW capabilities and purchasing an amplifier that can be run in the linear mode for ssb.

Let's look at the equipment procurement problem from a different perspective by putting ourselves in the shoes of a newcomer to amateur radio five years from now (1982). If the newcomer intends to stick with the hobby for quite a few years and wants to set up a first-class station for local and DX work with new, off-the-shelf equipment what are the options?

Option A

Synthesized 2-meter fm transceiver
Separate transmitter and receiver for high-frequency bands
Kilowatt high-frequency amplifier
50-foot (80m) tower and triband Yagi

Option B

10-watt multimode 2-meter transceiver
10-watt multimode 70-cm transceiver
50-watt, 2-meter and 70-cm linear amplifiers
Modest roof-mounted antenna array

While each of these options will provide roughly equivalent capabilities, **Option B**, which depends on satellites for long-distance work, costs approximately half as much as **Option A**. Since prices for vhf and uhf ssb/CW gear are likely to decrease when a big new market opens up, the financial advantage of **Option B** is likely to increase.

The first Phase III satellite will be a moving target. The question that concerns radio amateurs is: How difficult will it be to track this satellite with a moderate gain beam? In other words, how frequently will the ground station operator be required to adjust the azimuth and elevation controls? The answer depends on a number of factors including: satellite orbit characteristics, location of the ground station with respect to the satellite, and the beamwidth of the antenna.

An analysis of the problem, taking these factors into account, shows that a ground station using a moderate gain beam will, on the average, need to adjust azimuth and elevation controls about once every 15 minutes during most of the orbit. However, there will be times while the satellite is near the low point on its orbit (perigee) when almost continual adjustment of beam elevation and azimuth will be required. Since signals will be very strong near perigee, ground stations will find it convenient to switch from beams to simple fixed omnidirectional antennas during this relatively short period of time.

Let's compare the dynamic antenna aiming requirements for Phase III, as just outlined, to requirements for Phase II satellites and the 20-meter band. Radio amateurs who have been using low or moderate gain beams to access OSCAR 6 and OSCAR 7 will find that they'll be able to pay far less attention to azimuth and elevation controls when they communicate via a Phase III satellite. Operators familiar with 20 meters will probably also be pleased to observe how a single antenna setting will work for all stations using the satellite; there's no need to repeatedly adjust the antenna for each weak DX signal.

AMSAT hopes that some future Phase III satellites may be placed in geostationary (or nearly geostationary) orbits.⁶ A satellite in a geostationary orbit will appear to remain fixed directly above a spot on the earth's equator; a satellite in a nearly geostationary orbit will appear to drift slowly in longitude while remaining directly above the equator. Ground stations using these satellites will only need to adjust azimuth and elevation controls when switching from one satellite to another or when turning on the ground station after it's been off for a day or longer.

miscellaneous

Lifetime. Satellite lifetime concerns radio amateurs for several reasons. First, lifetime affects the yearly cost of the satellite. This subject will be covered in detail in the next section. Second, lifetime affects the long-term reliability of a satellite communications system. If a system depends on a single satellite, satellite failure shuts down the system. Potential

users of a system based on a single satellite are naturally hesitant about investing time, energy, and money in a ground station that might suddenly have no function. Although the long lifetimes of OSCAR 6 and OSCAR 7 have alleviated this concern to some extent, the real solution is to produce a multiple satellite system so that the failure of a single satellite causes users only minor inconvenience. The term Phase III connotes just such a system. For this reason amateurs building ground stations for Phase III need not worry about their station suddenly becoming useless.

Let's look briefly at some of the plans for implementing the Phase III system. Experience with Phase II has shown that it's reasonable to expect operational lifetimes of five years for Phase III satellites. During the five year period following the launch of the first Phase III satellite, additional spacecraft will be placed into orbit; a new satellite every two years is a realistic goal for the 1977-1985 time frame. By 1984 the system should average three or more Phase III spacecraft in orbit and operating at any given time.

In the past amateurs thought that a satellite's useful life ended when it ceased to function. In the future AMSAT might decide to retire an old operating spacecraft from service in order to replace it with a new, more powerful model before total failure occurs


Time delay. Time delays from 10 to 300 milliseconds on the earth-satellite-earth path will make continuous monitoring of your own downlink distracting — to say the least. This is just one illustration of the many subtle differences between terrestrial and satellite communications systems which amateurs will encounter in the future.

Each time amateurs have introduced new communications systems (ssb in the 1950s, for example, or fm repeaters in the 1960s), they've had to develop new operating procedures. Satellite systems will also require such innovations. One way to compensate for the time delays encountered while using high-altitude satellites might be to set the hang time on the vox or CW break-in system to 300 milliseconds and pause periodically for a second or two to enable the other party to break in.

No skip zone. Satellite communication systems do not exhibit skip zones. Consequently, it's easy to tell if a frequency is being used and a lot of unintentional interference can be avoided. In addition, round-table and net operation will be greatly facilitated since all users will hear each other. No problems to cure here — just a big bonus for satellite operators.

Doppler shift. Anyone who has listened to signals from a low-altitude satellite such as OSCAR 6 or 7 has

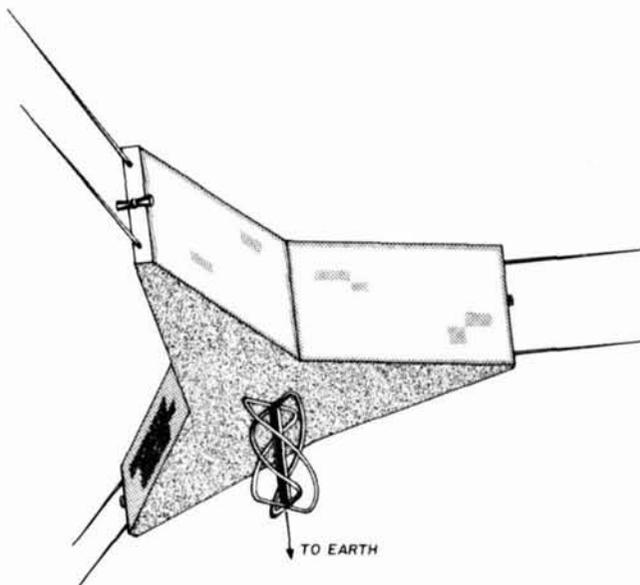probably noticed the pronounced downward shift in frequency that signals exhibit during nearby passes. A similar downward shift in frequency can be observed when a train passes with its whistle blowing. In both cases the frequency shift (called Doppler shift) is observed even though the source frequency is constant. The magnitude of the Doppler shift which amateurs encounter during satellite com-



Sketch of AMSAT-Phase III-A spacecraft.

munications depends on the relative velocity between satellite and ground station and the frequency being used — higher relative velocities and higher frequencies produce greater shifts.

Single-sideband communication is especially sensitive to Doppler shift since frequency changes of a few hundred cycles can make an ssb signal unintelligible. The largest Doppler shift that amateur radio operators have so far encountered during two-way communications occurs when OSCAR 7 passes directly overhead with the 432/146 MHz transponder in use. Under these conditions the Doppler shift is annoying, but ssb stations are able to compensate by frequent receiver tuning.

The first Phase III satellite will be moving slowly (relative to the surface of the earth) most of the time. During this portion of the orbit, Doppler shift will be smaller than observed with Phase II spacecraft which use the same transponder frequency combinations. However, there will be a small segment of each orbit, amounting to less than 10% of the period, when Doppler shift may be annoying, although ssb communications should still be possible.

Later Phase III satellites may be placed in geostationary orbits. Since these satellites will appear to re-

main fixed in space (no relative motion between satellite and ground station), no Doppler shift will be observed. In sum, Doppler shift will be of minor concern only with early Phase III satellites and of no concern with geostationary Phase III satellites.

Crowding. It has been estimated that the first Phase III satellite can accommodate 30,000 users equipped to transmit on the uplink bands. The estimate is based on ssb stations using 100 kHz and CW stations using 50 kHz of the transponder. If crowding becomes a problem before the follow-on Phase III spacecraft is launched, users have several options. Many may shift from ssb to CW to accommodate more stations in a given bandwidth. However, the opposite strategy, switching from CW to ssb, may actually be more effective in reducing crowding problems because a station can pass a given amount of information in a much shorter time period with ssb than with CW, while using less total spacecraft energy. This strategy would work only if amateurs limit themselves to essential information — a questionable objective.

Crowding effects can also be minimized by increasing the amount of roundtable and net operation. Phase III satellites are especially suitable for such use since there will not be any skip zone, and Doppler shift will be minimal. In any event, it should be evident that a number of viable options exist in response to any crowding problems that may temporarily occur. I have no doubt that amateurs who were raised on the 40- and 80-meter Novice bands will be able to devise satisfactory solutions.

financing

Phase III will become a reality only if the international amateur community is willing and able to financially support the program. While large donations from individuals, corporations, and foundations are needed to produce the first Phase III spacecraft, a long-term Phase III program depends on small donations from a very wide base of support in the amateur community.

An educated guess places the procurement cost for a commercially built Phase III satellite in excess of five million dollars. An early AMSAT estimate pegs the cost of the first Phase III satellite at two-hundred thousand dollars, a considerably smaller but still imposing figure. A much more meaningful number is the cost per year of service. Experience has shown that it's reasonable to expect an operational lifetime of five years for a Phase III spacecraft, so the cost per year of service for the first Phase III satellite is expected to be less than \$45,000.

Let's look at this figure more closely. When the number of amateur radio operators equipped for the

uplink reaches 15,000 (half the estimated spacecraft capacity), the yearly cost per user will be less than three dollars! This means that when AMSAT membership reaches 50% of user capacity, the current \$10 AMSAT membership fee* should be able to support an expanding program of satellite construction and provide for membership services, educational programs, and the *AMSAT Newsletter*. However, AMSAT satellites will always be free access and available to anyone licensed to operate on the uplink frequencies. Readers interested in cost breakdowns for the first Phase III satellite should read the current series in *QST* by Jan King, spacecraft project manager.

general comments

Phase III satellites have been compared to Phase II satellites and 20 meters throughout this article. The points of comparison were chosen to illustrate Phase III satellite capabilities in familiar terms. As a result many of the unique and desirable characteristics of Phase II satellites and 20 meters have been ignored. I will now briefly discuss some of these features.

The 20-meter band will certainly remain a favorite of amateurs for a number of reasons. It's probabilistic nature is actually a very appealing characteristic — a skilled, knowledgeable, patient operator with a simple low-power 20-meter station will eventually be rewarded with exciting openings to the entire world. In addition, RTTY and sstv buffs can use 20 meters for hour after hour without ever worrying about using an unfair amount of satellite power.

Low-altitude satellites can be used by very simple ground stations. Contacts through Phase II satellites have been made with as little as 100 milliwatts, and numerous amateurs have had contacts using less than 1 watt of transmitter power; it is therefore possible to communicate through low-altitude satellites using small hand-held portable units. Low-altitude satellites can also be used in a broadcast mode, for example, to carry a single bulletin to the entire United States via 2-meter fm. Because of these features AMSAT will launch another Phase II satellite in late 1977 and continue the Phase II program through the 1980s. If you haven't already done so, try your hand at using the low-altitude satellites currently in orbit; they can provide a great deal of fun and excitement.

I think it's clear that Phase III will add a new dimension to amateur radio by augmenting the existing long-distance communication modes, not by replacing them.

*Regular AMSAT membership is \$10 per year; life membership is \$100. Write to AMSAT, Post Office Box 27, Washington, DC, 20044.

With the uncertain outcome of amateur frequency allocations at the World Administrative Radio Conference in 1979, and the rapidly increasing amateur population in the United States and abroad, the question is no longer "Can we afford to go ahead with the Phase III project?" The question is, "Can we afford not to go ahead with the Phase III project?"

The European Space Agency has selected the first AMSAT Phase III satellite for a late 1979 launch. The selection was a significant honor for the AMSAT team, but satellite construction can proceed on schedule only if AMSAT can obtain adequate funds. The money needed can be raised if amateurs are willing to demonstrate their commitment to the Phase III satellite program by joining AMSAT now, before the first Phase III satellite is launched.

Individuals who would like to make a more substantial contribution are encouraged to do so by donating money — contributions are tax deductible under section 170 of the IRS codes and/or donating time — volunteers are needed for a myriad of Phase III related activities (and you don't have to live in the greater Washington, D.C. area to participate).

Ten years from today amateurs will probably look back at the years 1977-1981, bracketing the launch of the first Phase III satellite, as one of the most exciting periods in the history of amateur radio. Take part in making history and enjoy it as it happens; *invest yourself in the future of amateur radio.*

acknowledgements

Much of the information presented in this article was derived from conversations with Jan King and Perry Klein of AMSAT. Their comments on pre-publication drafts of this article were extremely useful. I am also grateful to Linda Davidoff. Her editorial assistance considerably improved the clarity of the manuscript.

references

1. B. I. Edelson, "Global Satellite Communications," *Scientific American*, February, 1977, page 58.
2. M. Davidoff, K2UBC, "Cost-Performance Criteria for Evaluating Phase III Satellites," *AMSAT Newsletter*, March, 1977.
3. R. Soifer, "Frequency Planning for AMSAT Satellites," *Proceedings of the ARRL Technical Symposium on Space Communications*, Reston, Virginia, September, 1973, ARRL, Newington, Connecticut 06111, page 101.
4. *Satellable*, available from Ham Radio, Greenville, New Hampshire 03048 (\$7.95).
5. *Orbit Calendar*, Skip Reymann, W6PAJ, P.O. Box 374, San Dimas, California 91773. Cost: AMSAT Life Members, free; AMSAT regular members, \$3.00; others, \$5.00.
6. SYNCART (SYNChronous Amateur Radio Transponder) Project. AMSAT proposal to NASA, July 24, 1971.

ham radio



DON'T GET BENT OUT OF SHAPE OVER REPEATER CRYSTALS.

**Amateur crystals 143.99-148.01
only \$4.50 postpaid.**

Florida residents add 4% sales tax. Send frequencies, make and model when ordering. Our price includes most gear on our free Parts List. For special equipment not listed, we'll provide prices on request. Master Charge and BankAmericard telephone orders accepted. No COD's.



Savoy Electronics Inc.

Manufacturers of Quality Quartz Crystals Since 1937
P.O. Box 5727, Fort Lauderdale, Florida 33310
305/563-1333

MAKE IT THE HEART OF YOUR ULTIMATE SSB/CW SYSTEM!

THE NEW HEATHKIT SB-104A TRANSCEIVER

The world-famous SB-104 improved. The SB-104A now offers improved receiver sensitivity and a fully-assembled and tested receiver front end circuit board for greatly reduced assembly time. And it's still at the same low price!

Totally broadbanded, completely solid-state, the SB-104A operates USB, LSB, or CW. Go from CW on the low end of 80 to USB on the high end of 10 in seconds while maintaining 0.5 μ V receiver sensitivity and a full 100 watts transmitter output. Just choose the band and select the mode; no more preselector, loading or tuning controls. Just flick a switch for instant 1-watt QRP output. The SB-104A offers true digital frequency readout and specs and performance that are incredible. Harmonic and spurious radiation are extremely low with third order distortion down 30 dB

or better! Alignment requires only a dummy load, mike and VTVM.

Complete SB-104A SPECIFICATIONS

Frequency Coverage: 3.5 MHz through 29.7 MHz amateur bands, 15 MHz WWV receive only. Frequency Stability: Less than 100 Hz/hr drift after 30-min. warmup; less than 100 Hz drift for $\pm 10\%$ change in primary voltage. Readout Accuracy: Within ± 200 Hz ± 1 count. Dial Backlash: 50 Hz max. Phone Patch Impedance: 4 ohm output to speaker; high impedance to transmitter. TRANSMITTER — RF Power Output: High Power: (50-ohm non-reactive load) SSB: 100 watts PEP ± 1 dB; CW: 100 watts ± 1 dB. Low Power SSB: 1 watt PEP (minimum); CW: 1 watt (min.). Output Impedance: 50 ohms, less than 2:1 SWR. Carrier Suppression and Unwanted Sideband Suppression: —50 dB down from 100 watt single-tone output at 1000 Hz reference. Harmonic Radiation: —40 dB below 100 watt output. Spurious Radiation: —40 dB within ± 4 MHz of carrier; —60 dB farther than ± 4 MHz. Microphone Input: High impedance, —45 to —55 dB; approx. 22k ohms. RECEIVER — Sensitivity: 0.5 μ V for 10 dB S+N/N for SSB. Selectivity: 2.1 kHz minimum at —6 dB, 5 kHz max. at —60 dB. (2:1 nominal shape factor). CW Selectivity: (with accessory CW filter) 400 Hz at —6 dB, 2 kHz max. at —60 dB. Audio Output: 2.5 watts into 4 ohms, 1.25 watts into 8 ohms, less than 10% THD. 4-8 ohm headphones. AGC: Less than 1 millisecond attack time; switch selectable 100 msec and 1 sec. release, and OFF. IM Distortion: —65 dB min.; —57 dB typ. with noise blanker. Image Rejection: —60 dB min. Dimensions: 5 $\frac{3}{4}$ " H x 14 $\frac{1}{2}$ " W x 13 $\frac{1}{2}$ " D.

...AND STILL ONLY
\$669⁹⁵!



HEATH
Schlumberger

Heath Company, Dept. 122-320
Benton Harbor, Michigan 49022

Please send me my FREE Heathkit Catalog.
I am not on your mailing list.

Name _____

Address _____

City _____

State _____ Zip _____

AM-351A



Read all about the SB-104A
and it's exciting station
accessories in the new
Heathkit Catalog!

FREE!

THE BIG NEW HEATHKIT CATALOG

Send for your copy today!

*There's more for the
ham at Heath*

Heath Company, Dept. 122-320
Benton Harbor, Michigan 49022

homebrew Touch-Tone encoder

Details for building
a simple encoder
designed around
the 555 timer IC

For those who like to make their own *Touch-Tone*† encoders, a cursory review of the amateur radio literature shows several reliable circuits. Several are built around the Western Electric Model 35 pad.¹⁻⁴ Another encoder used a pair of 565 IC voltage-controlled oscillators,⁴ while others have used the recently developed MC14410 cmos encoder.^{5,6} However, to my knowledge, no encoder has been built or described using the type 555 IC timer.

This article is the result of the challenge to design and build a simple *Touch-Tone* encoder with automatic PTT control using the 555 timer.

design

For a 12-button pad, *Touch-Tone* information is encoded in pairs using two of seven possible frequency tones. As shown in **table 1**, these seven

†*Touch-Tone* is the registered trademark of the American Telephone and Telegraph Company.

tones are divided into a "low" group (rows) of 697, 770, 852, and 941 Hz; and the "high" group (columns) of 1209, 1336, and 1477 Hz.

To generate the required *Touch-Tone* codes, two 555 timers are required, each connected as an astable multivibrator with an output frequency given by

$$f(\text{Hz}) = \frac{1}{0.693(R_A + 2R_B)C}$$

R_A is the resistance between the timer discharge output and $+V_{CC}$, and R_B is the resistance between the threshold input and discharge output. As shown in **fig. 1**, R_A is replaced by a resistive divider string for both the low- and high-tone oscillators.

table 1. Frequencies used in the Touch-Tone signaling system.

low-tone group	high-tone group		
	1209 Hz	1336 Hz	1477 Hz
697 Hz	1	2	3
770 Hz	4	5	6
852 Hz	7	8	9
941 Hz	*	0	#

For the low tone oscillator, U1, letting $R_A = R1 = 4.3\text{k ohms}$, $C = 0.047 \mu\text{F}$, and $f = 941 \text{ Hz}$, solving for R_B yields 14,164 ohms. To generate the next lower tone (852 Hz), R_A is now equal to $R1 + R2$, so that $R2 = 3.3\text{k ohms}$. For the 770-Hz tone, R_A now equals $R1 + R2 + R3$, giving $R3 = 3.9\text{k ohms}$. In a like manner, $R4 = 4.3\text{k ohms}$.

The high-tone oscillator U2, is designed in a similar manner. Starting with the 1477-Hz tone, letting $R5 = R_A = 3.9\text{k ohms}$ and $C = 0.047 \mu\text{F}$, $R6 = 2.2\text{k ohms}$ and $R7 = 2.4\text{k ohms}$.

For both oscillators the outputs are taken from the

By Howard M. Berlin, W3HB, 2 Colony Boulevard, Apartment 123, Wilmington, Delaware 19802

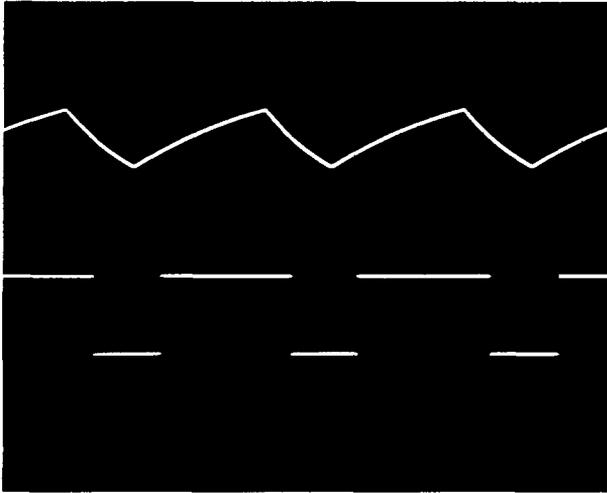


fig. 2. Type 555 timer output waveforms. When connected as an astable multivibrator upper trace is obtained from pins 2 and 6; lower trace from pin 3.

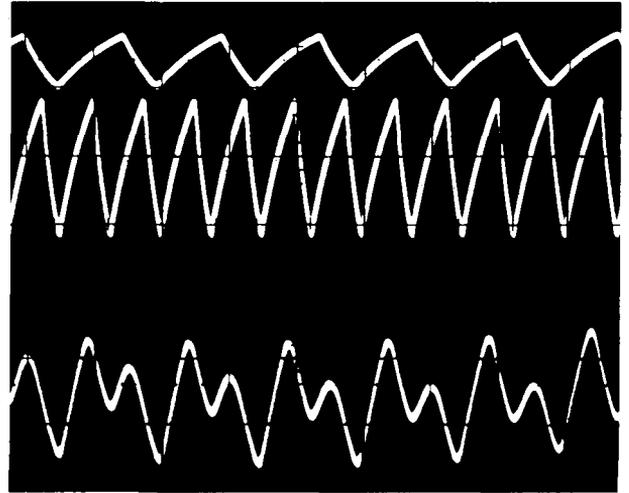


fig. 3. Addition to the low-tone oscillator (top trace) and the high-tone oscillator (center trace) to give a two-tone output signal when the digit 2 is pressed.

timer discharge junction and trigger pins (pins 2 and 6), which produce a pseudo-triangular waveform between $1/3$ and $2/3 V_{CC}$ (fig. 2). A 741C op-amp, U3, adds the output of both oscillators, shown in fig. 3, and is coupled to a 10-k ohm pot, which is an output-level control.

The automatic PTT control consists of another 555 timer, U4, connected as a 1-second one-shot and relay K1.

components

For good thermal stability the 0.047- μ F capacitors should be either tantalum or mylar, and resistors

R1-R9 should be 1%. Several manufacturers currently advertise a 4X3 pad similar to the Chomerics type ER-21623. R10 and R11 are 10-turn pots. If desired, a type 556 dual timer can replace U1 and U2. Fig. 4 compares the pin connections to of the 555 and 556 timers.

adjustment

Start by pressing the * key and adjust R10 so that the low-group oscillator reads 941 Hz at pin 3 of U1. Consequently, frequencies of 852, 770, and 697 Hz should be obtained to within 2% when the numbers 7, 4, and 1 are respectively pressed. For the high tone

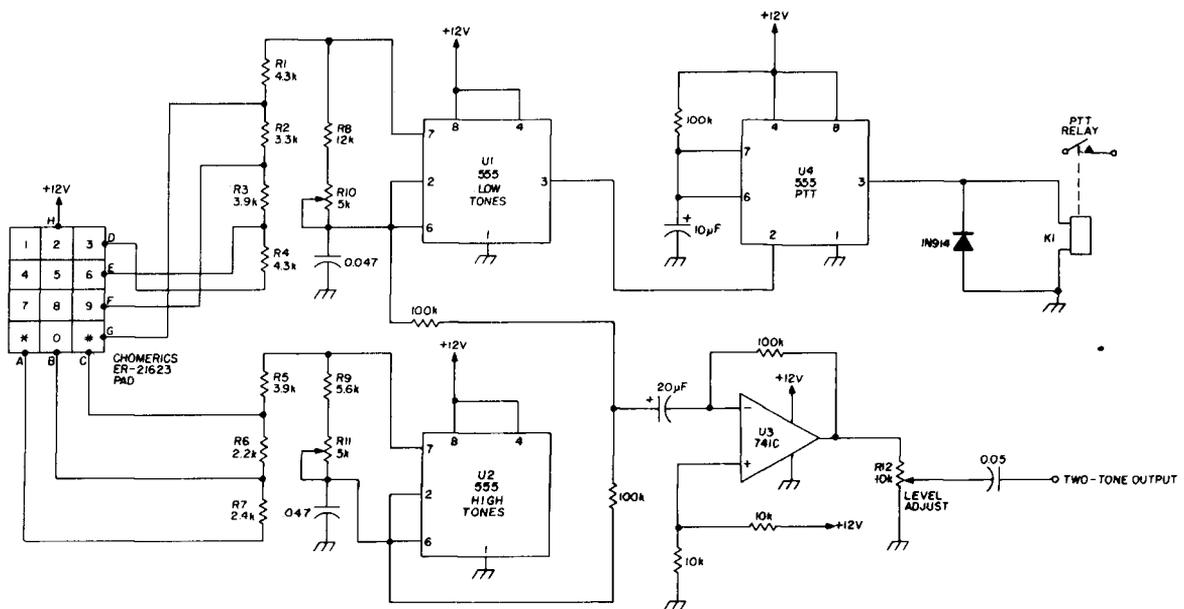


fig. 1. Touch-Tone encoder schematic using the type 555 IC timer with high and low tones. Automatic PTT control is also included.

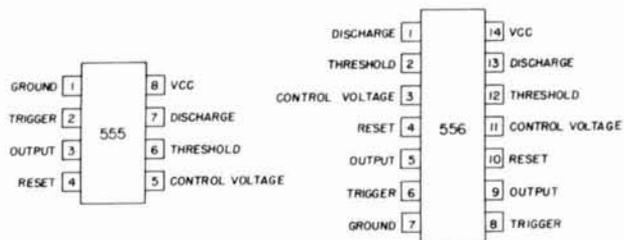


fig. 4. Pin-connection comparison for the type 555 and 556 timers.

group, press the # key and adjust R11 so that the oscillator reads 1477 Hz at pin 3 of U2. Consequently, frequencies of 1336 and 1209 Hz should be obtained to within 2% when the 0 and * keys are pressed.

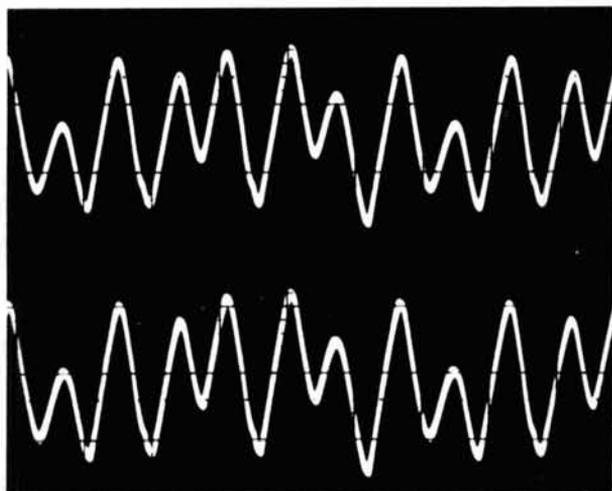


fig. 5. Comparison of two-tone output obtained from the 555 timer encoder (upper trace) with Western Electric Model 35 pad (lower trace) for the digit 1.

A comparison of the digit 1 generated by a Model 35 pad and the 555 encoder is shown in fig. 5.

For proper operation output-level control R12 should be set against a deviation meter; otherwise on-the-air testing will be required to set the output level.

references

1. William P. Lambing, W0LPO, "Mobile Operation with the Touch-Tone Pad," *ham radio*, August, 1972, page 58.
2. Roy C. Hejhall, K7QWR, "Solid-State Mobile Touch-Tone Circuit," *ham radio*, March, 1973, page 50.
3. Larry McDavid, W6FUB, "Universal Tone Encoder for vhf fm," *ham radio*, July, 1975, page 16.
4. *FM and Repeaters for the Radio Amateur*, ARRL, page 117.
5. Jon DeLaune, W7FBB, "Digital Touch-Tone Encoder for vhf fm," *ham radio*, April, 1975, page 28.
6. Al Lowenstein, K7AYM, "Hand-Held Touch-Tone," *ham radio*, September, 1975, page 44.

ham radio

THE COMPUTER ROOM

SMALL COMPUTER SYSTEMS • SOFTWARE • AMATEUR RADIO EQUIPMENT

1455-B So. 1100 E. Salt Lake City, Utah 84105 Phone: 801-466-7911

"WE TAKE THE
MYSTERY OUT OF THE MICRO"



One Of The Nations Largest
Full-Service Computer Stores

Over 1600 Square Feet Of Sales
And Service Facilities.

WHEN YOU WRITE FOR OUR CATALOG AND ENCLOSE \$1 TO HELP DEFRAY THE COST OF HANDLING AND MAILING, HERE'S WHAT YOU GET:

1. A CERTIFICATE GOOD FOR \$2 ON YOUR NEXT PURCHASE
2. THE **COMPUTER ROOM** EASY TO UNDERSTAND CATALOG COVERING

IMSAI
THE DIGITAL GROUP
POLYMORPHIC SYSTEMS
SOUTHWEST TECHNICAL PRODUCTS CORPORATION
TECHNICAL DESIGN LABS
ETC.

3. THE **COMPUTER ROOM** "EASY GUIDE" TO HELP YOU PICK THE RIGHT SYSTEM, PERIPHERALS, COMPONENTS, AND SOFTWARE FOR

THE BEGINNER
THE ADVANCED
THE EXPERT
THE SMALL BUSINESS

4. A CURRENT LISTING OF PRESENTLY AVAILABLE
- SOFTWARE
PUBLICATIONS
PERIPHERALS

5. INFORMATION ON REPAIR SERVICE, LOW COST CUSTOM PROGRAMMING AND OTHER SPECIAL SERVICES.

AT THE **COMPUTER ROOM** YOUR WRITTEN QUESTIONS ARE HAPPILY RECEIVED AND PROMPTLY ANSWERED

WE ALSO STOCK A COMPLETE
LINE OF AMATEUR RADIO EQUIPMENT

BANKAMERICARD MASTERCHARGE

frequency-marker standard using CMOS logic

Low power consumption
and fast
switching speeds
through the hf bands
are featured
in this circuit

A few frequency-marker standards have appeared in the amateur literature, but most use linear ICs or TTL logic. The frequency standard described here uses CMOS CD4000-series logic elements, which result in reduced power consumption but switch fast enough to allow sufficient switching speed and harmonic energy throughout the hf bands for good response.

circuit description

The divider arrangement is shown in **fig. 1**, in which a 400-kHz crystal-reference frequency is used. A 1-MHz reference would be better; however, the 400-kHz frequency was chosen because of available parts.

The oscillator is somewhat different than others using logic elements,¹ such as that using TTL ICs.² Resistor R1 keeps the input of the first NOR gate, U1A, stable; otherwise the oscillator refuses to oscillate at the crystal frequency. Resistor R2 is not critical and can be any value between 1 and 20

megohms. It should be close to 10 megohms if temperature extremes are experienced.¹ Resistor R3 provides load isolation between Y1 and the NOR-gate output. RC network C2, R3, R2, C1 forms a feedback arrangement similar to that recommended by reference 1, wherein C2 can be adjusted to vary crystal frequency to zero-beat with WWV or CHU. Capacitor C1 is used for crystal loading and centering of the crystal-frequency range.

Buffer NOR gate U1B isolates the crystal oscillator from the following divider chain, U2-U6. U2A-U3B are a divide-by-4 circuit in which the logic elements are JK flip-flops connected as D flip-flops (D flip-flops could be used here).

Calibration markers were desired at 200, 100, 50, 25, 10 and 5 kHz. This means that some additional dividing was necessary along with the following flip-flops to allow the desired symmetrical waveshape, since any feed back-type counter-divider produces an unsymmetrical waveform output. Therefore, U4 was chosen as a divide-by-N counter IC, and the latch arrangement of U5 was used to reset the selected divide-by-5 logic.

The 100-kHz output was first divided by 5, which was then divided by 2 to provide the symmetrical 10-kHz output; this output was then divided by 2 to provide 5-kHz. A switch, S1, and a final buffer, U1C, were used between selected output and the output coupling point. (A small 100-pF capacitor can be used for output coupling.)

construction

The photo shows component layout. I used perf board with straight pin-to-pin wiring. If you wish to use a PC board, one could be easily designed. Nothing is critical about parts layout; however, short leads should be used in the oscillator circuit to preclude problems with stray capacitance.

**By Fred M. Griffee, W4IYB, 8809 Stark Road,
Annandale, Virginia 22003**

CHOOSE TOP NOTCH RIG PERFORMANCE FROM THIS SHOWCASE OF SWAN METERS.

Swan precision meters are designed and built to help you make sure you're putting out all the watts your rig can deliver.


And Swan meters are priced so low they'll probably pay for themselves in improved rig performance and signal power.



Measure power coming and going. Measure SWR and get maximum power to your antenna. Then get your antenna pattern right by measuring relative radiated power. A one-two power punch at a knockout price. **FS-2 SWR and Field Strength Meter . . . \$15.95**



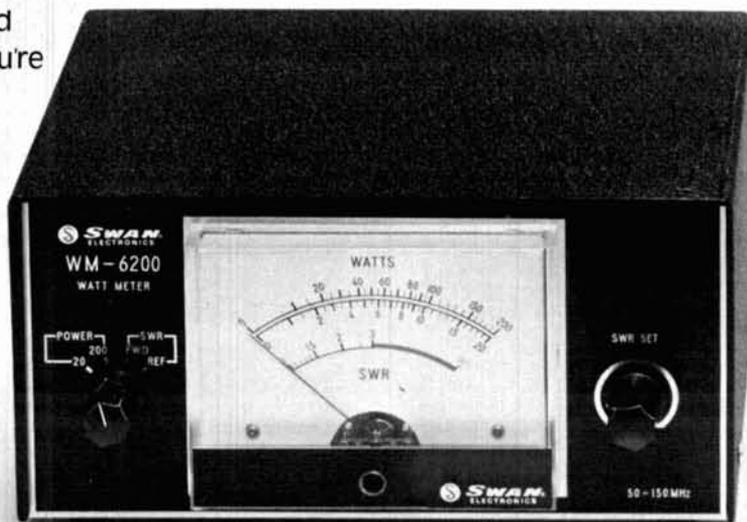Easy-on-the-pocket pocket SWR. Mighty mite SWR meter with high accuracy, SWR-3 Indicates 1:1 to 3:1 SWR at 50 ohms on frequencies from 1.7 to 55 MHz. Precision PC board directional coupler makes it a solid value at a rock-bottom price. **SWR-3 Pocket SWR Meter . . . \$12.95**




At last. A precision wattmeter for the 2-meter man. The upper-band man needs accurate output measurements, too. Now our WM6200 gives them to him with $\pm 7\%$ accuracy output power at 50 to 150 MHz. Two scales to 200 watts. Reads SWR on expanded range scale.

WM6200 In-Line Wattmeter . . . \$59.95



SWR bridge bridges the price barrier. This little jewel gives you relative forward power and SWR on two 100 microampere meters at a remarkably low price. Rear mounted coax connectors for easy, neat installation. Capable of handling 1000-watt signals on frequencies from 3.5 to 150 MHz. With low insertion loss, it's great for mobile operations, too. **SWR-1A Relative Power Meter and SWR Bridge . . . \$25.95**

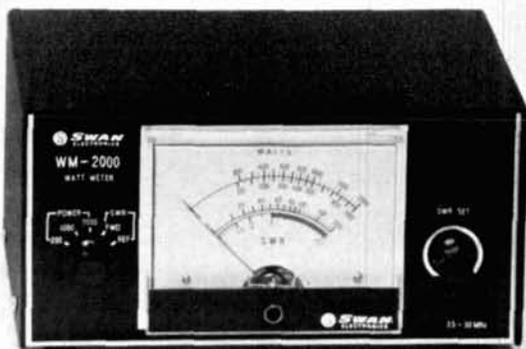

All-the-law-allows in-line wattmeter. With three scales to 2000 watts, new flat-frequency-response directional coupler for maximum accuracy and a price anybody can afford, this meter has become an amateur radio standard. 3.5 to 30 MHz with expanded range SWR scale.
WM2000 In-Line Wattmeter . . \$59.95




This wattmeter tells the truth about SSB. True peak envelope power of your voice modulated signal is what you want to know most about your SSB transmission, and that's where our WM3000 shines. Flat response forward or reflected power from 3.5 to 30 MHz on scales to 2000 watts in RMS or PEAK at the flip of a switch. **WM3000 Peak/RMS Wattmeter \$79.95**



Sniffs out radiated power wherever it is. This little unit is so compact it could measure relative radiated power in your pocket. Telescoping antenna and a frequency range of 1.5 MHz all the way to 200 MHz.
FS-1 Field Strength Meter \$10.95



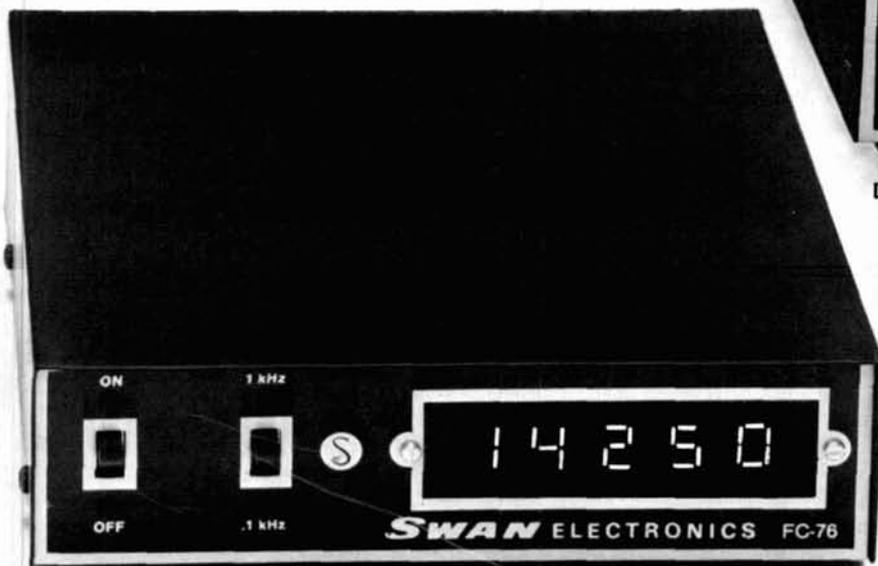
Double-duty in-line wattmeter. Use this meter for output power measurement and troubleshooting, too. Better than 10% full scale accuracy from 2 to 30 MHz, and you can go to 50 MHz with only slightly reduced accuracy. Four scales to 1500 watts and selector for forward or reflected power.
WM1500 In-Line Wattmeter . . \$74.95



Put your frequency up in lights. Perfect tuning and matching don't mean a thing if you're not on frequency. This counter tells the story on big, bright 5-digit LED display. Reads to ± 100 Hz or ± 1 kHz between 5 KHz and 40 MHz. Signal levels to 50 millivolts so you can use as a test meter, too. **FC-76 Frequency Counter \$169.95**

Use your Swan credit card for any Swan meter Applications at your dealer or write:

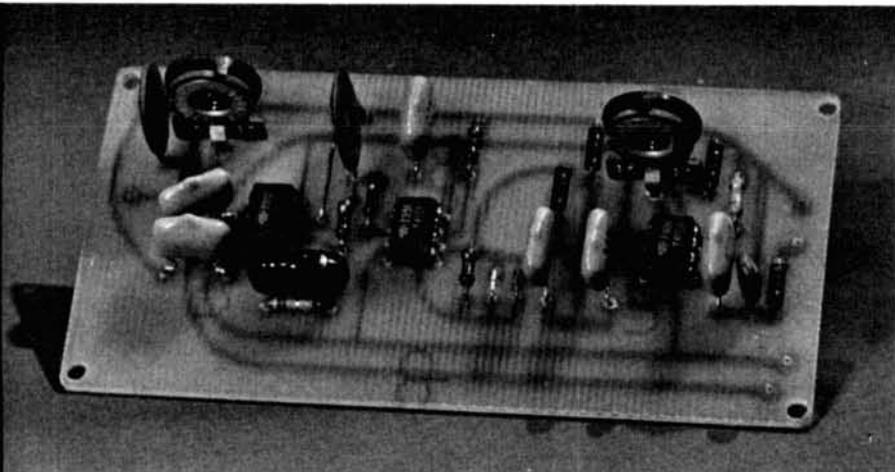SWAN ELECTRONICS®
 A subsidiary of Cubic Corporation
 305 Airport Road • Oceanside, CA 92054 (714) 757-7525



audio-frequency speech processor

Design and
construction of a
logarithmic limiting type
speech processor
featuring $\mu A741$ ICs

An easy way to improve ssb-transmitter performance is to use a well-designed speech processor between microphone and transmitter. Such a processor, if properly adjusted, will make a noticeable improvement in your transmitter speech readability. Contrary to current rumors, poor audio quality and increased bandwidth are not inherent in a good design.

Audio-signal conditioning requires no transmitter modifications with the exception of a cooling fan to protect components because of the increase in average power input to the final amplifier. Such a fan may be mounted externally if needed.

The speech processor described here is of the

logarithmic type¹ and is easy to adjust and use. When used with my SB-401, this speech processor resulted in a signal-strength increase at the receiving end of at least two S-units. I've yet to get a report of poor audio quality or splatter, even from operators using monitor scopes. As a result, I use the processor at all times.

response

Much has appeared in the amateur literature regarding the ideal response of speech processors. For example, reference 2 states that, "The only way to accurately evaluate the actual improvement of-

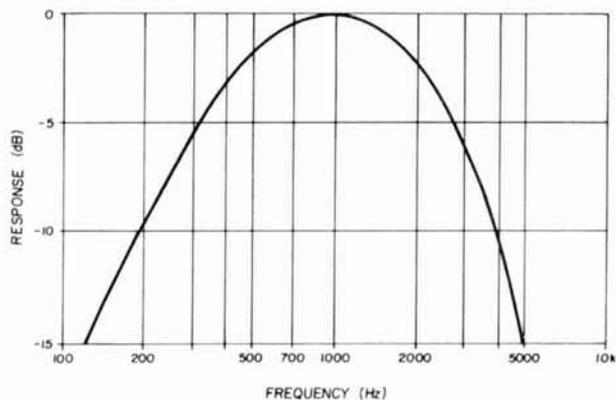


fig. 1. Speech-processor response below clipping level. $V_{in} = 0.054$ volt p-p; $V_{out} = 0.230$ volt p-p at 0 dB; Generator $Z_{out} = 50$ ohms; $Z_{load} = 1$ megohm.

By Frank C. Getz, K3PDW, 685 Farnum Road, Media, Pennsylvania 19063

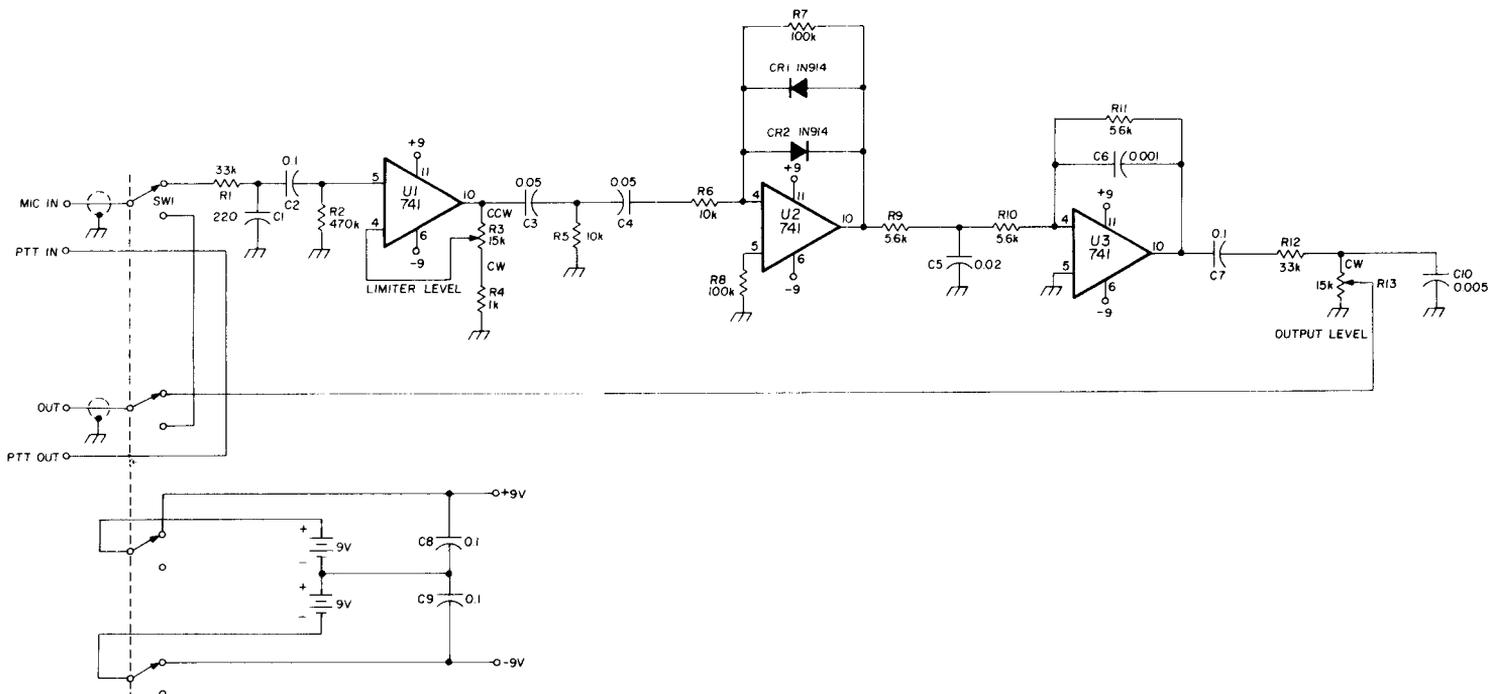


fig. 3. Speech-processor schematic. Numbering for 14-pin DIPs is shown.

- U1, U2, U3 μ A741 operational amplifier (use mini-dip for PC board)
- SW1 4 pdt rotary switch
- C1 220 pF, 50 WVdc disc ceramic
- C2, C7, C8, C9 0.1 μ f, 50 WVdc mylar
- C3, C4 0.05 μ f, 50 WVdc, 5% mylar
- C5 0.02 μ f, 50 WVdc, 5% mylar
- C6 0.001 μ f, 50 WVdc, 5% mylar
- C10 0.005 μ f, 50 WVdc mylar
- CR1, CR2 1N914 diodes
- R3, R4 15k or 10k linear pot, composition type
- All other resistors 1/4 watt, 5%
- SW1 4 pole, 2 position

ferred by a speech processor is to measure the Intelligibility Threshold Improvement (ITI).” After much experimentation, I found the frequency response of **fig. 1** to be a good compromise between maximum readability and good audio quality. The audio bandwidth is sufficiently limited without impairing voice quality.

circuit description

Fig. 2 shows the block diagram for the processor. The schematic is shown in **fig. 3**. R1C1 forms an rf filter to prevent rf on the microphone cable from getting into the processor. C2R2 gives some highpass filtering action. R2 provides bias to the noninverting input of U1, and combined with the input impedance of U1, will provide sufficient load to a crystal or ceramic microphone to attenuate low-frequency components and reduce harmonic distortion produced by very-low-frequency energy entering the microphone.

U1 is an adjustable gain-preamplifier, which overcomes losses in the highpass filter (C3, C4, and R5) and sets the input level to U2, the limiting amplifier.

U2 limits because the nonlinear resistance characteristics of CR1 and CR2 supply increasingly heavier negative feedback as U2 output amplitude increases, which provides a logarithmic response. Limiting is soft and is similar to that of a compressor followed by a hard limiter. R8 eliminates any dc offset in U2 output due to input bias current. R9, R10, R11, and C5, C6, and U3 form a lowpass active filter, which attenuates frequencies above 2.8 kHz that may be generated in the clipping process. R13 provides output level adjustment, so that the transmitter drive-

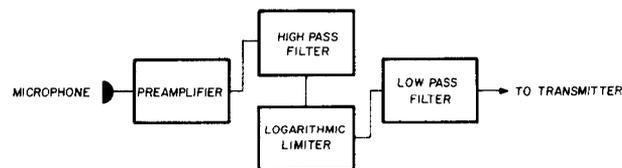


fig. 2. Block diagram of the logarithmic speech processor.

level control doesn't have to be changed when the processor is switched in or out.

construction

Wiring and component values with the possible exception of the resistors and capacitors that comprise the high- and lowpass filters are not particularly critical. The usual precautions applicable to audio circuitry should be observed.

The original version was wired on a small PC board intended for breadboarding DIP integrated circuits. It was then mounted along with two standard alkaline transistor radio batteries, in a 3 x 4 x 5-inch (77x102x 128mm) aluminum box with plenty of room to spare.

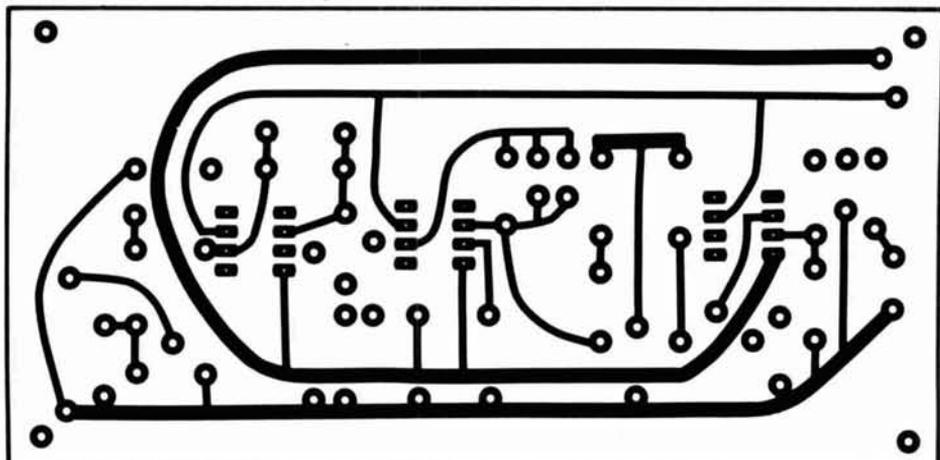


fig. 4. PC board layout, foil side.

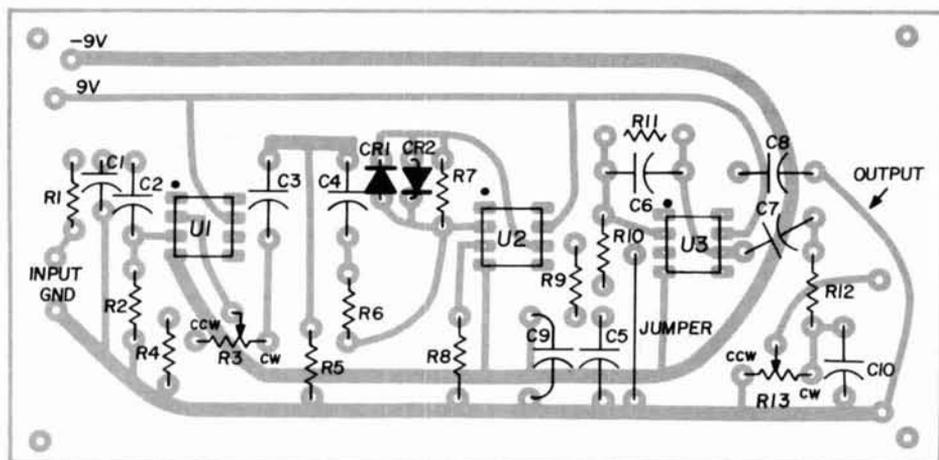


fig. 5. Component side of the PC board showing parts placement.

A PC board layout is shown in **figs. 4 and 5**.* I used IC sockets in my original unit, but these are not absolutely necessary.

The alkaline batteries should be good for about a year of normal operation, but an ac power supply could be substituted if precautions are taken to minimize ac hum, which would be particularly troublesome if introduced at this level.

I mounted two double-pin audio connectors of the same type used for the transmitter microphone connector on the rear of my processor. These are the input and output connectors and permit easy insertion and removal of the processor. The cable between processor and transmitter is of the same type as used on the microphone and is terminated at each end with a connector identical to that used on the microphone. (Don't forget to carry any PTT lines directly through the unit.)

*A printed-circuit board is available from the author for \$4.95 and a self-addressed stamped envelope.

Although holders are available for 9-volt batteries, I found that the heavy flat plastic wire ties used by electricians to bundle conductors make a very secure mounting. Make sure to use the type with a mounting hole molded in one end. Standard battery clips were used for the electrical connections.

operation

Operation is simple. Once the settings of R3 and R13 have been established, the on-off switch is the only control used. I used screwdriver-adjust pots in my unit.


The transmitter should be tuned in the normal fashion with the processor switched out. The transmitter microphone gain control should be set at the proper level, using a monitor scope or the transmitter's ALC indicator according to the instruction manual. Turn limiting control R3 about one-half turn clockwise, switch in the processor, and adjust output control R13 for the same ALC indication or peak-monitor-scope deflection that was obtained

without the processor. On-the-air reports can then be used to determine the optimum setting of R3.

After adjusting R3, always recheck the setting of R13. Use discretion in adjusting R3. Extreme limiting should be avoided if the best combination of signal strength and audio quality is to be attained.

A too-high setting of R3 will also cause normal background noise to become objectionable as the audio gain for low-level signals is increased. Consequently, the processor can be used most effectively in a quiet, echo-free environment.

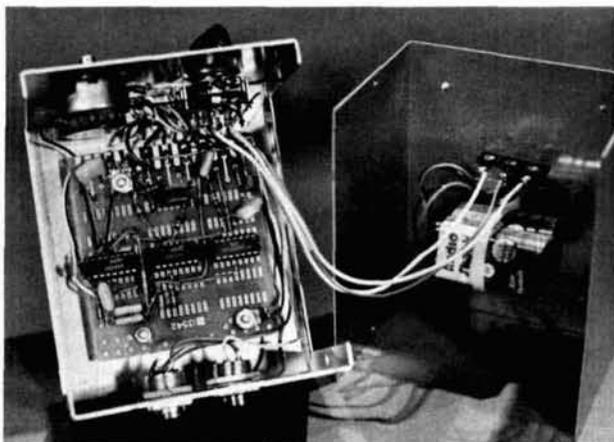The use of this speech processor will increase the average power input to the final amplifier and cause some increase in final-amplifier -tube dissipation. To



Breakaway section showing wiring and underchassis layout.

extend tube life, I added a small cooling fan. The fan I used is of the axial type. It is rectangular, about 5 inches (128mm) on a side and about 1 1/2 inches (38.25mm) thick, with mounting holes in each corner. I fastened four small rubber feet at the mounting holes and placed the fan on top of the perforated lid of the transmitter, directly above the final tubes, so that the fan draws air from inside the cabinet. I decreased the air flow and noise level of the fan, both of which were excessive, by installing a resistor of about 375 ohms in series with the fan motor, which resulted in a quiet cooling system.

Performance over a 12-month period has been excellent. The increased range and number of solid ssb contacts have more than justified the modest investment in time and material for the speech processor.

references

1. Bob Myers, W1FBY, "A Quasi-Logarithmic Analog Amplitude Limiter With Frequency-Domain Processing," *QST*, August, 1974, page 22.
2. Gene Nurkka, VK9GN, "Integrated-Circuit Single-Sideband Speech Processor," *ham radio*, December, 1971, page 31.

ham radio

SUPER STATION BUYS

HY GAIN 18AVT/WB + 100 feet RG8 coax \$100.00
 HY GAIN 18V vertical \$19.95 Model 214 2m Yagi \$21.50
 VHF SPECIALS: Kenwood TS-700A List... \$599 Call for quote
 KLM: Antennas, Linears, Accessories All In Stock
 JANEL PREAMPS: In Stock. Technical Books (ARRL, Sams, Tab, RCA, T.I., etc.)
 HAM X ROTOR (New Model) Turns 28 sq. ft. of antenna (August delivery) List... \$325 Order Now Your Price \$289
 KLM KR400 ROTOR \$85.00
 CDE Big Talk Rotor \$79.00 CDE HAM-II \$129.00
 BIRD WATTMETERS: In Stock
 SWAN METERS: WM 6200 VHF Wattmeter \$49.95; SWR 1A \$21.95
 TELEX HEADSETS: In Stock CETRON 572B \$24.95 ea.
 CABLE 5/32", 6-strand, soft-drawn guy cable. For mast or light tower, 3¢ foot.
 BELDEN COAX CABLE: 8237 RG8 19¢ ft., 8214 RG8 foam 23¢ ft., 8448 rotor cable 14¢ ft., 8210 72 ohm kw twinlead \$19/100 ft., 8235 300 ohm kw twinlead \$12/100 ft., PL259 49¢; UG175 adapter 19¢; PL258 double female \$1.00.
 NYLON CORD 5000 ft. + per roll \$15.00
 BELDEN 14 gauge copper stranded antenna wire \$5.00/100 ft.
 RG8 foam Xtra-Flex coax 23¢ ft. RG8 foam Superflex coax \$25¢ ft.
 22 gauge plastic covered for long wire, radials \$3.50/1000 ft.

CALL FOR QUOTES ON: ATLAS 350XL, KENWOOD TS520S, TS600A, TR7400A, FT101E, TEMPO 2020 & ETO-ALPHA. ALL IN SEALED CARTONS. CALL FOR QUOTES ON ITEMS NOT LISTED.

CALL FOR FAST QUOTE, OR WRITE AND INCLUDE TELEPHONE NUMBER. IF WE HAVE YOUR BARGAIN, WE'LL CALL YOU PREPAID.

TERMS: All prices FOB Houston. Prices subject to change without notice. All Items Guaranteed. Some items subject to prior sale. Send letterhead for Amateur dealers price list. Texas residents add 5% tax. Please add postage estimate, excess refunded.

MADISON ELECTRONICS SUPPLY, INC.
 1508 MCKINNEY HOUSTON, TEXAS 77002
 713/658-0268 Nites 713/497-5683

talk power by **TPL**
 Econo-line



- Quality for an Economy Price
- Solid State Construction
- Linear Switch (FM/SSB)
- Broad Band

Model	Input	Output	Typical	Frequency	Price
702	10W-20W	50W-90W	10W in/70W out	143-149MHz	\$149.00
702B	1W- 5W	60W-80W	1W in/70W out	143-149MHz	\$179.00

Now get TPL COMMUNICATIONS quality and reliability at an economy price. The solid state construction, featuring magnetically coupled transistors and a floating ground, gives you an electronically protected amplifier that should last and last.

The Linear Bias Switch allows you to operate on either FM or SSB. The 702 and 702B are exceptionally well suited for 2-meter SSB. Typical power output levels as high as 100W PEP can be achieved with the proper drive.

The broad band frequency range means that your amplifier is immediately ready to use. No tuning is required for the entire 2-meter band and adjacent MARS channels on TPL's new *Econo-line*.

See these great new additions to the TPL COMMUNICATIONS product line at your favorite radio dealer.

TPL

Call or write for prices and information on TPL's complete line of amateur and commercial amplifiers.

COMMUNICATIONS INC.

1324 W. 135TH ST., GARDENA, CA 90247 • (213) 538-9814

Canada: A.C. Simmonds & Sons Ltd., 285 Yorkland Blvd., Willowdale, Ontario M2J 1S8
 Export: EMEC Inc., 2350 South 30th Avenue, Hollandale, Fla. 33009

SAROC™

HAWAII WEEK

INCLUDING

SAROC'S THIRD HAWAIIAN CONVENTION November 1 to 8, 1977

SPEND 8 FABULOUS DAYS IN EXCITING HAWAII ON SAROC'S HAWAII WEEK



Your holiday includes:

- Attendance at SAROC Hawaiian Convention, Saturday and Sunday, November 5 and 6.
- Seven nights at the fabulous HYATT KUILIMA RESORT HOTEL and COUNTRY CLUB on Oahu's North Shore.
- Roundtrip air transportation, double occupancy in hotel room and SAROC Advance Registration just \$350 per person. Limit 2 pieces of luggage per person. Tax and gratuity included.
- Departs Los Angeles, November 1, 1977 — Returns November 8, 1977. (United Airlines OTC Flight)
- Optional plan: \$360 per person departing from and returning to Las Vegas via United.
- \$100 deposit immediately, full payment by September 15, 1977.
- SAROC Advance Registration \$3.00, with Saturday Banquet \$11 per person.

Write for further details

SAROC™

BOX 945, BOULDER CITY, NEVADA 89005

We've just made the impossible...

a professional 3½ digit DMM Kit for less than \$60.



The Sabtronics Model 2000 is an impossible \$59.95! And that price still includes phenomenal accuracy, range and professional features.

This all-new bench/portable multimeter, reading to ± 1999 , has a basic accuracy of $0.1\% \pm 1$ digit, and has five functions giving 28 ranges, 100% overrange and overload protection. So you know it's no toy!

Besides, what toys are as automatic as the 2000? With automatic overrange indication, automatic polarity, even automatic zeroing!

Yet the 2000 is easy to assemble. We send you all the parts you need, even the high-impact case. We also send you clear, step-by-step assembly instructions.

So you end up with a professional quality 3½ digit DMM for the unheard-of price of less than \$60. From Sabtronics, specialists in digital technology. And manufacturers of the impossible.

Order yours today!



Made in U.S.A.

sabtronics 
INTERNATIONAL INC.

P.O. Box 64683 Dallas, Texas 75206 (214) 369-7310

GUARANTEE:

Our guarantee to you; examine the 2000 DMM kit for 10 days. If you're not satisfied, return it unassembled for a full refund of purchase price.

SPECIFICATIONS:

DC volts in 5 ranges: $100\mu\text{V}$ to 1000V.
AC volts in 5 ranges: $100\mu\text{V}$ to 1000V.
DC current in 6 ranges: 10nA to 2A.
AC current in 6 ranges: 10nA to 2A.
Resistance in 6 ranges: 1Ω to $20\text{M}\Omega$
Input Impedance: $10\text{M}\Omega$
Display: 9mm (.36") LED.
Power requirements: 4.5 VDC to 6.5 VDC
(4 "C" cells - not included).
Size: 8"W x 6.5"D x 3.0"H.
(203W x 165D x 76H mm).

To: Sabtronics International, Inc.
P.O. Box 64683, Dallas, TX 75206

HR

Please send me _____ Sabtronics Model 2000 DMM kit(s) at
\$59.95 each. _____ subtotal

Shipping and Handling, \$5.00 per unit* _____ subtotal

Texas Residents Add Sales Tax _____

TOTAL enclosed _____

Name _____

Street Address _____

City _____

State _____ Zip _____

*USA only. Canada, \$6.50. All Other Countries, \$10.00.

low-cost microwave spectrum analyzer

How to put together
a microwave
spectrum analyzer
from surplus
odds and ends —
the completed unit
covers dc to 2 GHz

My ongoing efforts to develop low-cost modules for the 1296-MHz band have often required the use of a spectrum analyzer for monitoring (and minimizing) harmonic and spurious frequency components. Numerous excursions through the local surplus test equipment emporiums revealed that an acceptable instrument could cost several thousand dollars — well beyond the budget of the most dedicated experimenter. While searching for the unbeatable surplus buy which never materialized, I noticed the ready availability and comparatively low cost of a wide variety of S-band (2-4 GHz) test instruments and components. It occurred to me that a microwave spectrum analyzer could be put together from these available parts at a considerable savings. This article documents the design, construction, operation, and performance limitations of the resulting microwave spectrum analyzer. While I doubt that any reader will want to duplicate my design in its entirety, I hope this article will provide

guidance and encouragement to anyone attempting a similar project.

performance requirements

The operation of any spectrum analyzer can be characterized in terms of its frequency coverage, dispersion, dynamic range, sensitivity, and resolution. To display frequency components well into the microwave region, I designed my spectrum analyzer to cover dc to at least 2 GHz. The same design strategy could be easily applied to other frequency bands. In fact, the upper frequency limit of this analyzer was later extended to 2.5 GHz, as discussed later.

Dispersion describes the ability of a spectrum analyzer to display a broad slice of the frequency spectrum in a single sweep. Many of the low-cost analyzers on the surplus market display only a few MHz at a time. Such narrow-dispersion spectrum analyzers are useful as panadaptors, which display all signals within several hundred kHz of a specified operating frequency, but when tuning a microwave local-oscillator chain, monitoring mixer image response, or measuring transmitter harmonic content, it is often desirable to display a band several hundred (or even thousand) MHz wide. The spectrum analyzer shown here can display the spectrum from dc to 2 GHz in a single sweep. Since it's often desirable to narrow this sweep for a closer look at a particular signal, variable dispersion capabilities are included in the design.

Sensitivity and dynamic range define the minimum and maximum signal amplitudes which an analyzer can display without distortion. In accordance with good engineering practice, I try to suppress all transmitted spurious products by 50 dB or more. To accurately measure this performance, the spectrum analyzer requires at least 50 dB of dynamic range. As

By **H. Paul Shuch, WA6UAM**, Microcomm,
14908 Sandy Lane, San Jose, California 95124

for maximum input level, I often want to display a +10 dBm (10 mW) signal (this is the local-oscillator injection level required of many balanced mixers). Thus, 50 dB dynamic range with a +10 dBm maximum input level yields an ultimate sensitivity require-

with this design, I can resolve frequency components to within about 2 MHz.

As most amateurs know, a general-coverage communications receiver can be used as a rudimentary high-frequency spectrum analyzer. With an input

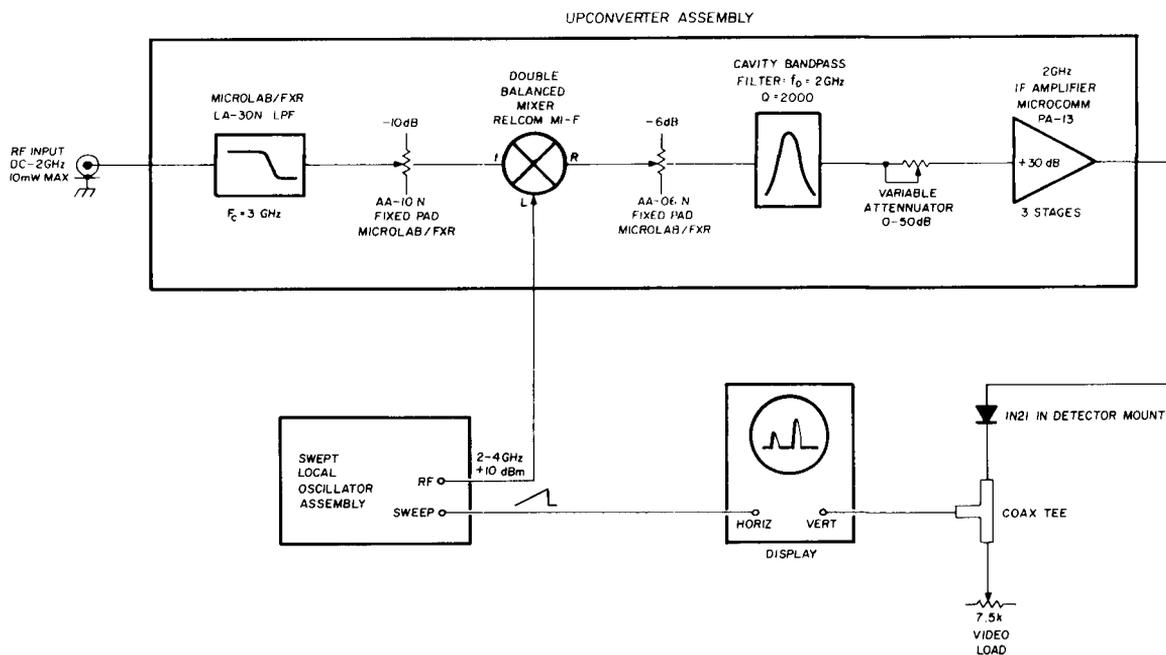


fig. 1. Block diagram of the microwave spectrum analyzer. Most components were purchased on the surplus market. The swept local oscillator, the key to the analyzer, is a surplus 2.4 GHz backward-wave oscillator. The display is an ordinary oscilloscope with dc coupling and provisions for external sweep.

ment of -40 dBm, or 0.1 μ W. Greater sensitivity (a lower minimum discernible signal) could have been obtained, but only at the expense of dynamic range.


The objective of any spectrum analyzer is to display the various components of a complex waveform in the frequency domain. The closer the frequencies of any two components, the more difficult it is to separate them on the spectral display. Resolution relates to the minimum frequency separation between two signals of equal amplitude which will still permit the operator to discern two separate frequency components on the display.

Resolution can be approximated as twice the i-f bandwidth of the analyzer system. Generally, the objectives of wide dispersion and narrow resolution are mutually exclusive. When measuring transmitter audio intermodulation products with a two-tone test, for example, a resolution of a few hundred Hz is required, and dispersion is likely to be several tens of kHz. When viewing harmonics of a 100-MHz oscillator, on the other hand, 2-GHz dispersion may be required, but a resolution of several tens of MHz is acceptable.

Resolution is primarily a function of i-f bandwidth, which for my analyzer is fixed at 1 MHz. Therefore,

signal applied to the antenna terminals, the receiver is manually tuned through its frequency range (dispersion). Frequency components are detected and displayed (perhaps with the receiver's S-meter). Resolution is a function of the i-f bandwidth, which is probably a few kHz. Sensitivity is a function of the receiver's noise floor, and dynamic range is limited by the receiver's agc and overload characteristics. Obviously, wide dispersion measurements require considerable operator intervention, in the form of tuning. Gain variations of the receiver from band to band will limit the accuracy of its amplitude indication. Additionally, any nonlinearity in the receiver's agc circuit may prevent accurate amplitude measurement across the receiver's entire dynamic range. Also, the receiver's image and spurious rejection may be insufficient to eliminate false indications.

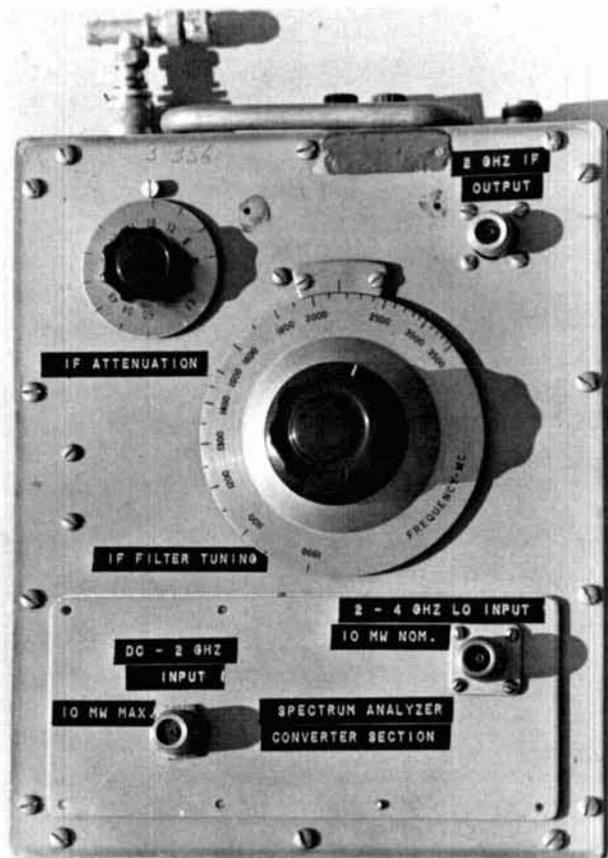Ideally, a workable spectrum analyzer should be a superheterodyne receiver in which these shortcomings are minimized. Frequency tuning should be both automatic and rapid. Instead of an S-meter, amplitude is displayed on an oscilloscope. If the scope's horizontal deflection is slaved to the receiver's tuning mechanism, the result is a display in the frequency domain. Dynamic range must be max-



Front panel of the microwave spectrum analyzer showing the operating controls. The variable i-f attenuator (upper left), although calibrated in 6 dB steps, permits amplitude comparison of signals displayed on the oscilloscope. The i-f bandpass filter (center) sets the frequency coverage of the analyzer, as discussed in the text.

imized, and spurious/image responses eliminated, to the greatest possible extent.

Many of the objectives discussed previously are met in the design shown in **fig. 1**, a wide dynamic range microwave receiver with an electronically tuned local oscillator and ample image rejection. It includes a 2-GHz i-f amplifier with variable gain and fixed bandwidth, and a sensitive detector for driving an oscilloscope. Unlike conventional receivers, this design up-converts the incoming signal to an i-f in the microwave region. Although this approach complicates i-f design, it permits wide dispersion tuning. It also improves separation of the rf and image signals so a simple lowpass filter can be used to eliminate image responses.


The microwave spectrum analyzer is divided into three separate sub-systems: the local oscillator, unity-gain upconverter, and display sections.

local oscillator

Central to the design of this spectrum analyzer was the availability, on the surplus market, of a leveled, swept signal source covering 2 to 4 GHz. I used an

Alfred 622BK sweep oscillator, but any similar generator should work satisfactorily. These sweep generators consist of a voltage-controlled oscillator, typically a backward wave oscillator or BWO (a microwave oscillator built around a device similar to a traveling wave tube), power supplies, a sawtooth generator for developing a constantly varying vco control voltage, and leveling circuitry to maintain constant output across the band. *Start* and *stop* frequency adjustments permit the oscillator to sweep all, or any portion of, the 2 to 4 GHz band. Leveled output power is typically 10 to 30 milliwatts.

Many companies are currently retiring their BWO sweep generators in favor of wideband, solid-state units, so quite a few BWO generators have recently appeared on the surplus market at prices ranging from \$200 to \$400 or so. Since this is the most costly component of the microwave spectrum analyzer, make sure the unit you buy is in good operating condition. Reputable electronics surplus dealers will often let you power up an instrument and make a few measurements prior to purchase. A practical test requires the use of a microwave power meter (bolometer bridge or equivalent) to observe output power in the leveled CW mode as the generator is manually tuned across the band. Although a few dB variation is acceptable, dead spots or severe power drop-off at the high end of the band indicates a failing BWO. A good, used BWO should provide years of reliable life in intermittent amateur service.

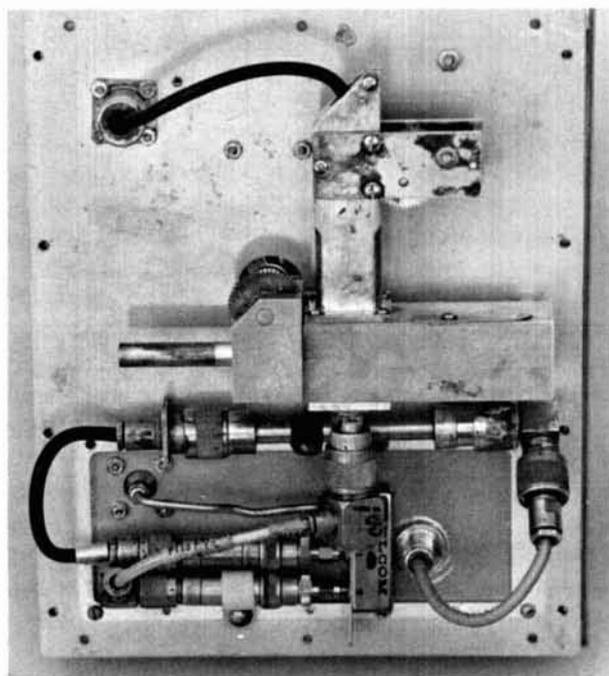

Interior of the spectrum analyzer converter section showing the double-balanced mixer and attenuation pads, input filter, i-f filter, and variable i-f attenuator.

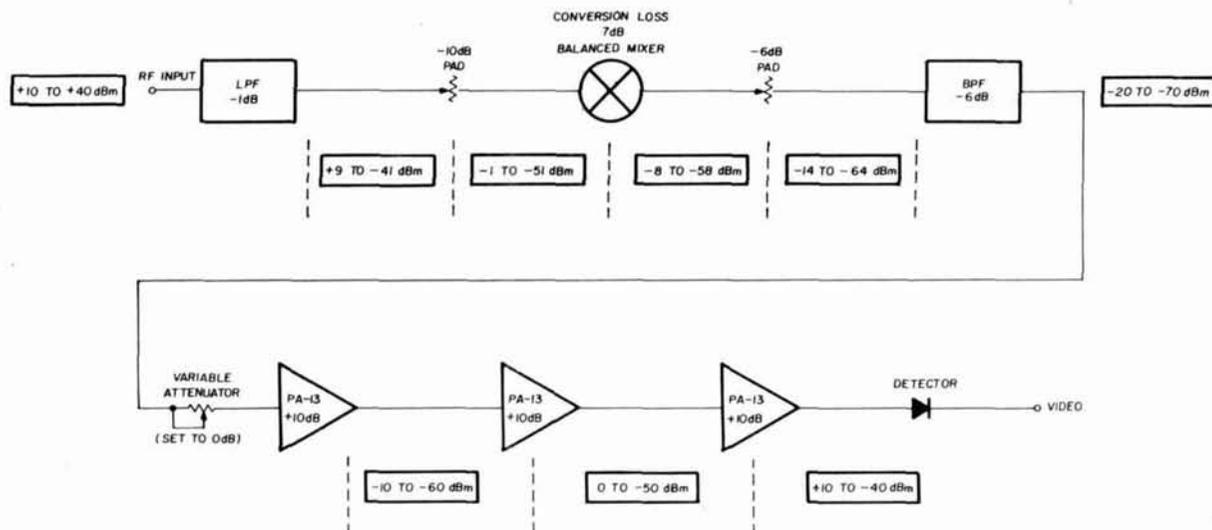


fig. 2. Power levels in the upconverter used with the microwave spectrum analyzer (with the variable attenuator set at 0 dB, which results in unity conversion gain).


As can be seen in the block diagram, **fig. 1**, the spectrum analyzer converter assembly consists of an input lowpass filter, an S-band double-balanced mixer, some attenuator pads, a high-Q i-f filter, a variable i-f attenuator, and sufficient i-f amplification to bring maximum conversion gain to unity. The i-f detector and its video load, though installed in the converter assembly, are discussed later with the display.

The characteristics of the balanced mixer, more than any other component, establish the linearity and dynamic range of the analyzer. I used a Relcom M1F mixer which I found on the surplus market for \$35 (the mixer retails for about \$200). The rated frequency response of this mixer is dc-2 GHz at the i-f port, and 2-4 GHz at the rf and LO ports. Note that the incoming signal is applied to the *i-f* port; the *rf* port drives the i-f system. Thus, all ports are operated within their specified frequency ranges.

With the 10 mW of local-oscillator injection applied to the mixer from the sweep generator, the mixer's conversion efficiency is compressed by 1 dB at an input signal level of 1 mW. Since I wanted to analyze a 10 mW signal on the spectrum analyzer without exceeding 1 dB compression, it was necessary to place a 10 dB attenuation pad ahead of the mixer's input (i-f port). This pad also assures proper impedance termination for the mixer, as does the 6 dB attenuator at the output (rf port). Fixed attenuators for dc to 2 GHz are available to the surplus bargain hunter for as little as \$5.00, or may be purchased new for \$15 to \$20.

With 2 GHz i-f, and a swept LO covering 2 to 4 GHz, the mixer will respond to signals in the dc-2 GHz region, as well as in the 4-6 GHz image band. Any components in the image band will cause con-


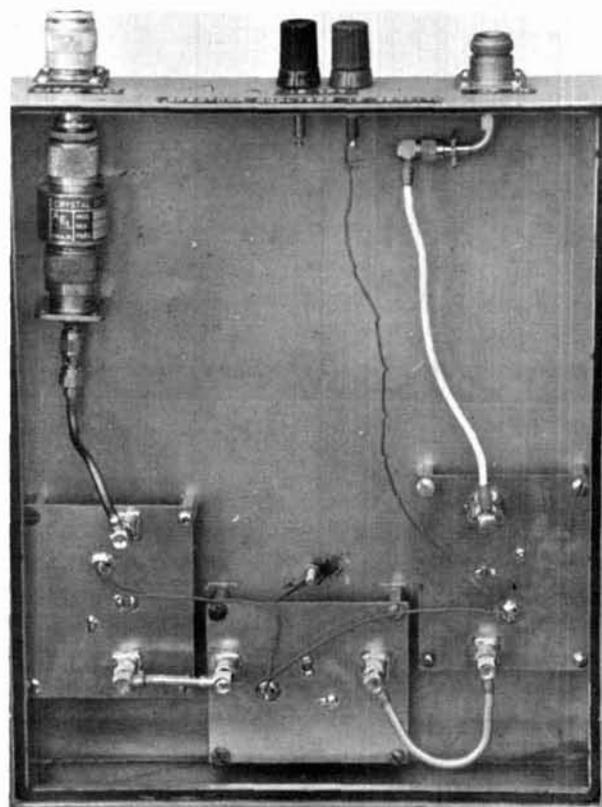
siderable confusion on the display. Thus an input lowpass filter was installed in the system to block all signals above 3 GHz from entering the mixer. I used a Microlab/FXR LA-30N filter which I salvaged from another piece of equipment. Although the filter originally cost \$40, similar devices are available through surplus outlets for \$5 to \$10.



Spectrum analyzer i-f section. The three 2-GHz amplifiers are at the bottom. Diode detector is at upper left.

The i-f bandwidth of this analyzer is established by a high-Q tunable coaxial or cavity filter which is tuned to 2 GHz. I used the filter from a surplus TS-406 noise generator, but any cavity with a Q of 1000 or greater should be acceptable. It's also possible to use

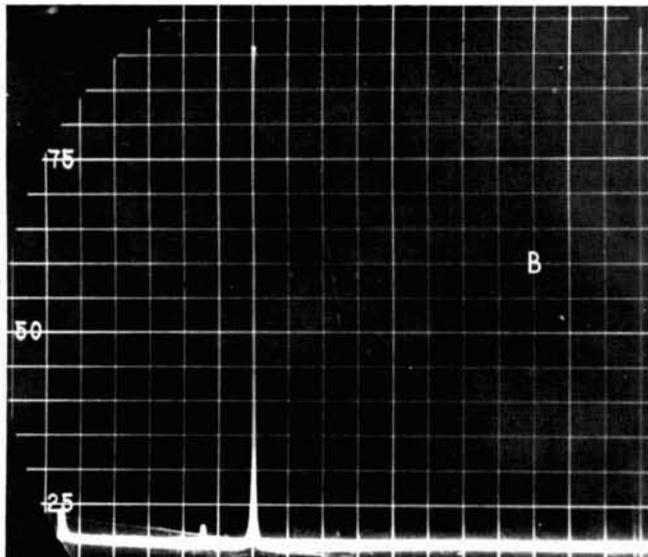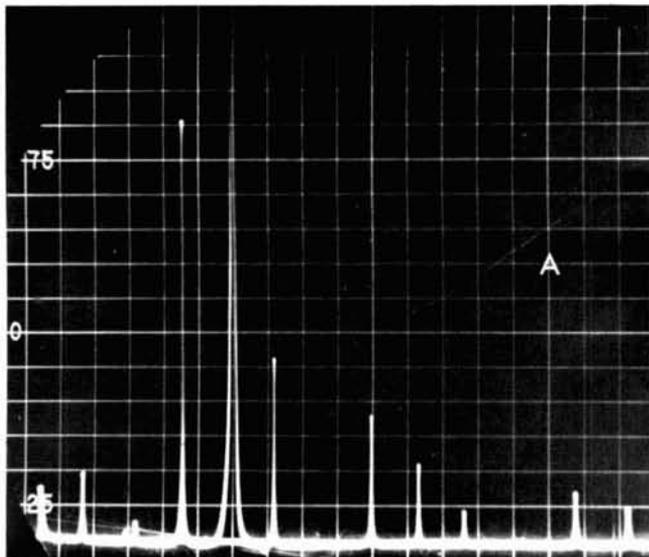filter to vary i-f gain. The attenuator I used was also salvaged from the TS-406 noise generator, but any continuously variable or step attenuator rated to 2 GHz is acceptable — 10 dB steps will allow coarse system gain control; if 1 dB resolution is included,



Example of spectral impurity, as displayed on the microwave spectrum analyzer. Presence of harmonic, subharmonic, and spurious signals shown in A is the result of an overdriven uhf amplifier. The same amplifier, with drive reduced to the rated level, is shown at B; the one spurious component is down by more than 20 dB. Display is from dc to 2 GHz.

a *transmission-mode* cavity wavemeter as an i-f filter. These widely available devices have a loaded Q of several thousand, and exhibit only a few dB of insertion loss at resonance. Note that an absorption-type wavemeter is *not acceptable* because the filter must pass maximum signal to the i-f amplifiers at resonance.


A 50 dB variable attenuator was installed after the

the attenuator can also be used for accurate signal level comparison. This is accomplished by viewing one signal component, setting a convenient reference level on the display, varying the attenuator for a like indication on the other signal component, and noting the change in attenuator settings.

Considerable i-f gain is required to achieve the desired sensitivity. I cascaded three stages of the Microcomm PA-13 buffer amplifier.* These microstripline amplifier modules offer 10 dB of gain per stage across the 2.0-2.3 GHz band, and are biased for 30 mW output at 1 dB gain compression. Since i-f noise figure is not a limiting factor so far as system sensitivity is concerned, any available wide dynamic range amplifier for 2 GHz may be used.


display

The local-oscillator signal for the spectrum analyzer is swept by a sawtooth waveform; therefore, displaying a signal in the frequency domain is simply a matter of detecting the output signal from the i-f amplifiers, applying the recovered video to the vertical deflection amplifier of an oscilloscope, and applying the sawtooth output voltage from the sweep generator to the oscilloscope's horizontal axis. Since a relatively slow sweep rate is used, the

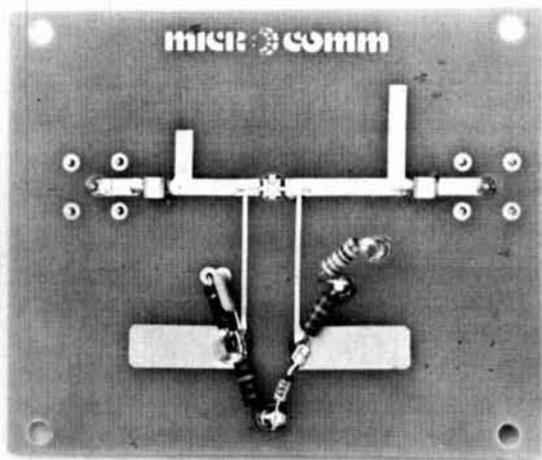

Microstripline side of the 2-GHz amplifier (Microcomm PA-13). Three of these units provide 30 dB gain at 2 GHz.

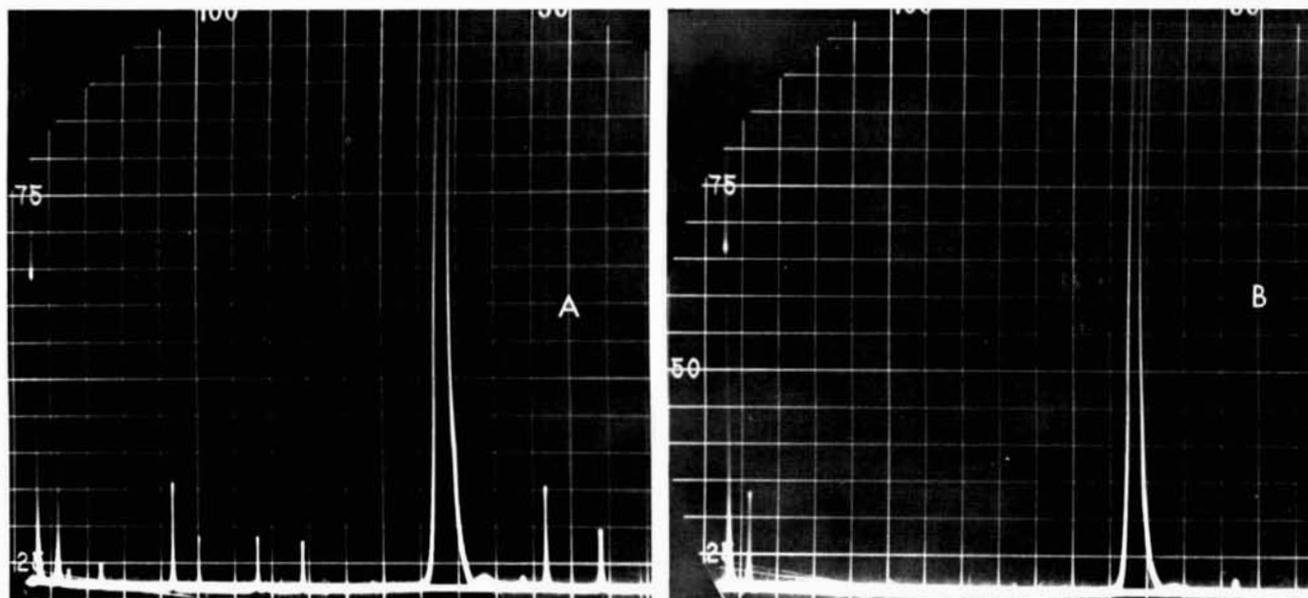* Available for \$64.95 per stage (plus postage and handling) from Microcomm, 14908 Sandy Lane, San Jose, California 95124.



Output of a local-oscillator chain for a 1296-MHz converter. At *A* the i-f gain of the spectrum analyzer has been increased to show the spurious signals, which are 30 dB below the desired signal. The display at *B* shows the output of the same local oscillator after it has passed through a 3-pole bandpass filter. Although the filter has attenuated the desired signal by 1 dB, all spurious signals are down more than 50 dB.

frequency response of the oscilloscope is unimportant. Virtually any scope with dc coupling and provisions for external sweep may be used.

The dynamic range of the detector which follows the i-f amplifiers is of major concern. **Fig. 2** shows the nominal gain or loss of each element of the analyzer upconverter, as well as maximum and minimum signal levels present at each stage with zero i-f attenuation (maximum sensitivity). Since the upconverter is operated at unity gain, the power available to the detector will vary from +10 to -40 dBm. Thus the diode's tangential sensitivity must be considerably below -40 dBm, and the diode's saturation point above +10 dBm, for a usable display. Although I know of no diode whose transfer characteristics are uniform over so wide a range, the 1N21 family of point-contact diodes are acceptable within certain limitations (discussed later).

Diode dynamic range is enhanced by the optimum terminating impedance, which may vary between 1000 ohms and 10 kilohms or so. The input impedance of an oscilloscope's vertical deflection amplifier is typically 1 megohm; thus, to assure proper termination for the diode, a loading resistor is required, as shown in **fig. 1**. Since terminating the diode's video port degrades the amplitude of the recovered video, increased oscilloscope vertical sensitivity is required. On my analyzer, a 7.5k ohm video load, in conjunction with a vertical sensitivity of 10 mV/cm, provides an acceptable display.

Note that the vertical display of the spectrum analyzer is approximately linear, not logarithmic. Therefore, it is possible to view only about 25 dB of

amplitude range at once, and only with extremely limited amplitude resolution. However, by using the i-f attenuator to establish reference levels as described previously, the entire 50 dB of usable

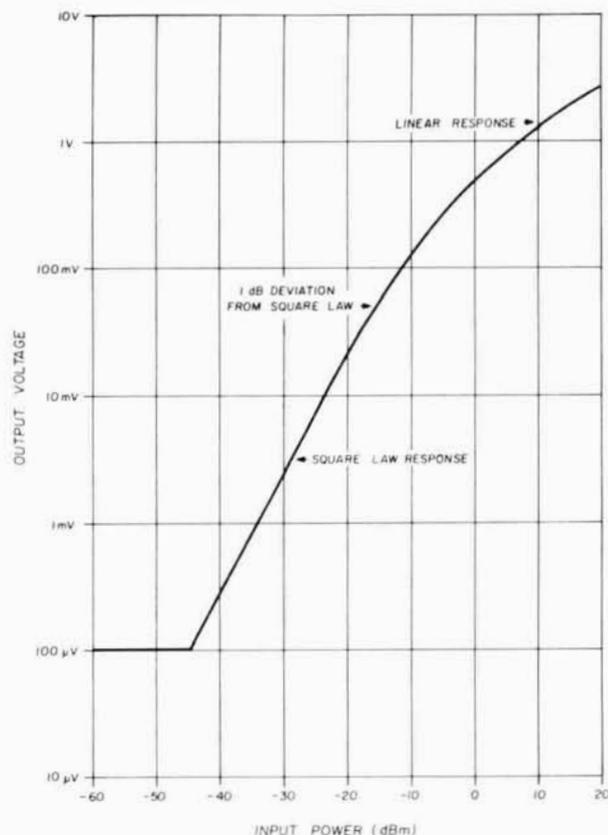


fig. 3. Transfer characteristics of a typical microwave diode detector using a point-contact diode.


dynamic range can be put to use. Future plans include capability for a logarithmic display, as outlined toward the end of this article.

I built the entire upconverter module in the case of a surplus noise generator (the filter and attenuator of which formed key i-f elements in my system). As can be seen in the photographs, the i-f amplifiers are mounted on standoffs inside the main chassis, and connected with UT-141 semi-rigid coaxial cable. If

converter image response, and transmitter inter-modulation products.


improving sensitivity

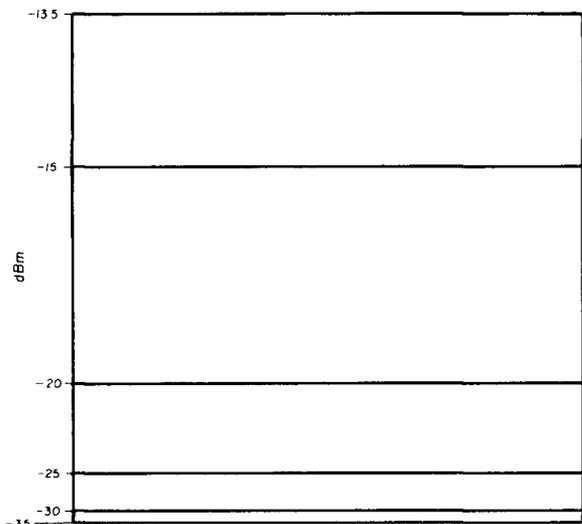One of my primary design objectives was the ability of the analyzer to handle relatively large (+10 dBm) input signals without overloading. The input pad shown in **fig. 1**, although it prevents mixer overload at these signal levels, obviously limits the



VERTICAL SENSITIVITY = 10 mv/cm
IF ATTENUATION = 0 dB

A

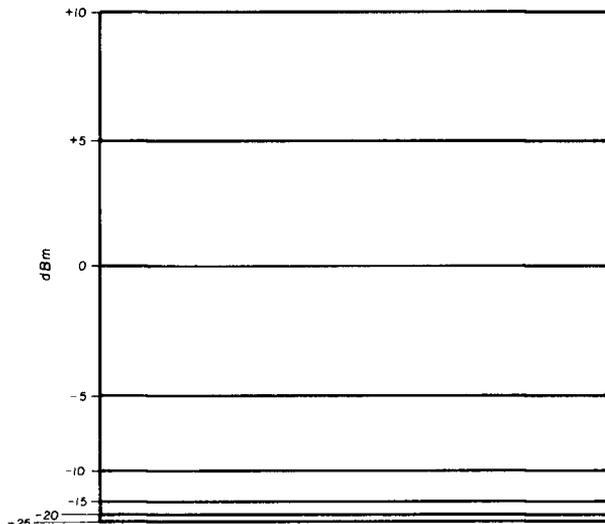

VERTICAL SENSITIVITY = 200 mv/cm
IF ATTENUATION = 0 dB

B

fig. 4. Approximate vertical scale calibration of the analyzer display (no video processing). Note the excellent linearity at high power levels, and the compressed display when the detector diode is operated in the square-law region.

flexible coax is used, I recommend RG-142B/U. This ¼-inch (6.5mm) cable is double-shielded, silver plated, has a Teflon dielectric, and accepts clamp-type SMA plugs of the low-cost E. F. Johnson JCM series.

If desired, the i-f amplifiers may be mounted in Pomona 3601 die-cast aluminum boxes. These boxes present a neat appearance and afford somewhat better shielding than the standoff approach I used.

The various components of the upconverter assembly sport a variety of connectors; between-series adapters are required to interface types N, SMA, and TNC receptacles.

operation and applications


A recent article discussed a variety of spectrum analyzer applications of interest to amateurs.¹ For additional information, Hewlett-Packard has published two application notes which discuss both the procedures and the theory of spectrum analysis.^{2,3}

The accompanying photographs show the displays obtained with this analyzer when measuring LO harmonic content, balanced mixer carrier rejection ,

ultimate sensitivity of the system. Additional i-f amplification would enhance the ability of the analyzer to display very small signals — but then the detector diode would saturate at high input signals.

Where both increased sensitivity and large-signal handling capability are required, it's necessary to replace the 10 dB input pad with an appropriate step attenuator (and possibly adding additional i-f stages). One candidate for the input attenuator is the Kay 520 which offers 10 dB steps to 70 dB and is flat to 2 GHz. This unit is priced under \$100 , but like everything else in my spectrum analyzer, units are often available through surplus sources at considerable savings.

Note that no variation in input attenuation or i-f gain can increase the dynamic range of this analyzer beyond 50 dB or so. Therefore, it is essential that the operator select input attenuation which is appropriate for the anticipated signal level. In short, input attenuation should be such that the signal applied to the mixer does not exceed 1 mW, and that to the detector remains below 30 mW. A simple operating check involves increasing the input at-

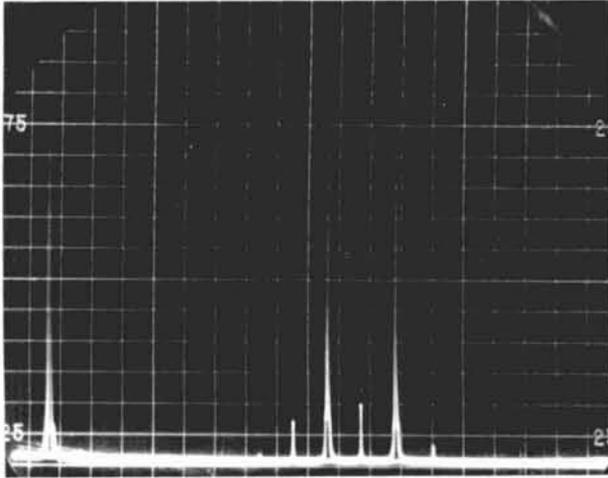

As a transmitting mixer's i-f port is overdriven, intermodulation products at $LO \pm 2i-f$ become more pronounced, and the amplitude of signals at $LO \pm 3i-f$ begins to increase. This display also shows the second harmonic of the i-f injection signal (at the left).

tenuation by 10 dB while decreasing i-f attenuation by the same amount. An increase in the apparent amplitude of the displayed signal indicates that the mixer was being over-driven.

expanding frequency coverage

Recently I became involved in designing amplifier, mixer and LO modules for 2304 MHz, and wanted to extend the upper frequency limit of this spectrum analyzer. This could be accomplished by varying either the swept LO frequency or the i-f frequency, or both. Since the LO frequency range is limited by the coverage of the available sweep generator, I chose to change the i-f frequency.

With a 2 to 4 GHz swept LO, frequency coverage from 500 MHz to 2.5 GHz could be obtained by modifying the analyzer's i-f to 1.5 GHz. However, this exceeds the rated frequency range of the mixer's rf and i-f ports. Fortunately, the frequency response of the i-f port of the mixer I used exceeded the specified 2 GHz. At 2.5 GHz input, vswr is degraded somewhat, but the use of the 10 dB input pad effectively masks this mismatch. As for the frequency response of the mixer's rf port (used to develop i-f output), reducing the i-f frequency to 1.5 GHz degrades conversion efficiency by several dB. The i-f is fixed, however, so this degradation applies equally to all input signals, and no system linearity is sacrificed.

I originally planned to switch in a separate i-f system for high band (0.5-2.5 GHz) coverage, but I discovered that the PA-13 i-f amplifiers were sufficiently broadband that they have usable gain at 1.5 GHz. Since the cavity filter used to establish i-f bandwidth is tunable, setting the spectrum analyzer up for high-band coverage is simply a matter of retuning the i-f filter to 1.5 GHz. In this mode, overall analyzer


sensitivity is degraded by about 10 dB, but it is still adequate for many applications.

With a 1.5 GHz i-f, the input signal range extends from 500 MHz to 2.5 GHz, and the image band from 3.5 to 5.5 GHz; therefore, the existing 3-GHz lowpass filter provides ample image rejection without degrading input frequency coverage.

detector limitations

In normal operation (**fig. 2**) the diode detector sees a power level from -40 to $+10$ dBm. **Fig. 3** shows the transfer characteristics of a typical microwave detector diode over this range. It can be seen that the diode is being driven from its square-law region into its linear region. Thus, at high signal levels, 10 dB of signal change results in approximately a 10 dB change in recovered video amplitude; at lower power levels a 10 dB input signal variation may change video amplitude by up to 20 dB. Obviously, the linearity of the display is marginal, at best, and usable dynamic range is restricted to about 25 dB unless the operator varies i-f gain, or vertical sensitivity or both.

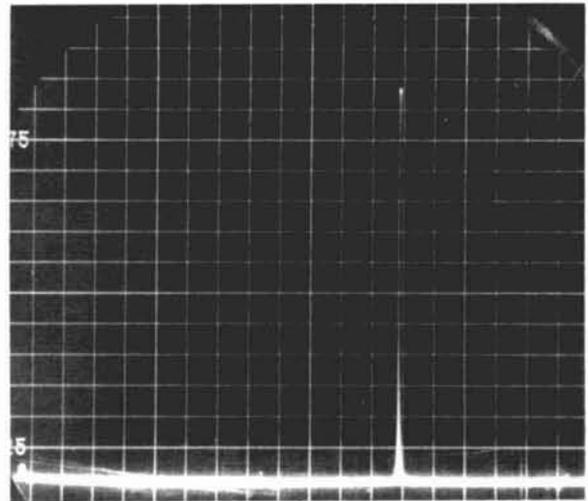Hewlett-Packard introduced a series of oscilloscope overlays for interpreting non-linear



Properly driven 1296-MHz transmit mixer, at the output of a 3-pole bandpass filter. The image, i-f, and LO signals are all 40 dB down; intermodulation products are more than 50 dB down. The small pip at the left side of the trace is the bandedge marker and represents zero frequency; it is produced when the LO sweeps through the i-f filter.

(more properly, non-logarithmic) swept displays.⁴ A similar set of overlays, which I have derived for my spectrum analyzer, is shown in **fig. 4**. Although this calibration data is valid only for my analyzer, a similar vertical axis can be derived for any spectrum display. All you have to do is apply an input signal of known amplitude through an accurate step attenuator. By varying the attenuation and noting the

displayed amplitude, calibration lines can be grease-penciled directly on to the face of the CRT.

The utility of this spectrum analyzer would be greatly enhanced if it were possible to display simultaneously all signals between -40 and $+10$ dBm. If you want to view the entire 50 dB dynamic range without adjusting reference levels with the i-f attenuator or varying vertical sensitivity, it will be necessary to apply the output of the detector into a compression video amplifier.

There are several integrated circuits available which provide logarithmic video amplification; with a logarithmic amplifier a display such as that shown in **fig. 5** can be obtained. Note that below about -10 dBm, the display approaches a uniform 5 dB per centimeter deflection. However, the transition from square-law to linear detection results in severe scale compression at higher power levels.

An ideal spectrum analyzer display should have vertical response similar to that shown in **fig. 6**. Although I have not yet been able to achieve this performance, it should be possible by developing a logarithmic video amplifier which makes its transition to linear response above a selected input level.

An approach used successfully by Pacific Measurements in their logarithmic power meters involves an operational amplifier in which the feedback resistance is a nonlinear element (a semiconductor junction). As the junction potential of this feedback path is exceeded, the gain curve of the op amp changes. The result is an amplifier which makes its

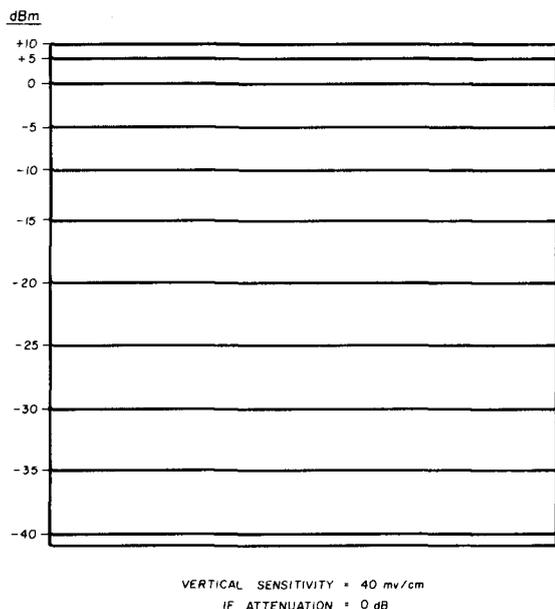


fig. 5. Typical vertical scale calibration of a spectrum analyzer with a logarithmic video amplifier. In this case display linearity is good at lower input signal levels, but compresses rapidly as the detector diode enters the linear region.

transition from logarithmic to linear response at selected power level. Perhaps some reader will be able to contribute a similar circuit for appropriately shaping the video output of the spectrum analyzer's diode detector. What is needed is a display whose

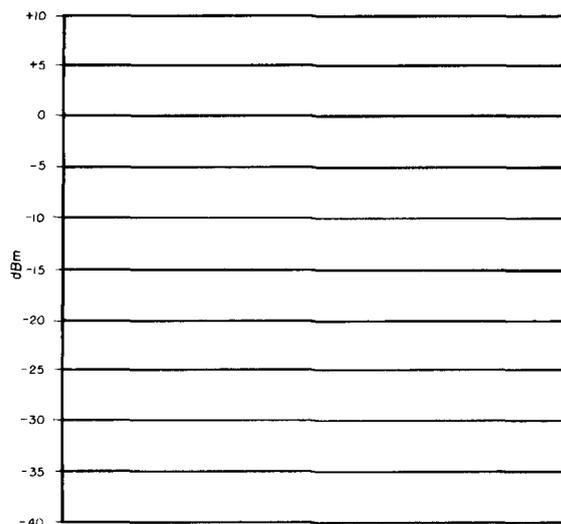


fig. 6. Ideal vertical response for a spectrum analyzer. This response requires a video amplifier with a logarithmic compression curve below an input of 200 mV, and linear response above 400 mV.

amplitude is graduated at 5 dB per centimeter, over the entire dynamic range of the system. This modification would significantly enhance both measurement accuracy and ease of operation.

acknowledgements

Thanks are in order to Nick Marshall, W6OLO, for first encouraging me to try to build my own spectrum analyzer, and to Richard Chatelain, WB6JPY, who took the photographs. I must also acknowledge the eager support of my wife, WA6PLF. She reasoned that, if I built my own analyzer rather than spending funds I didn't have to buy one I couldn't afford, we would make good use of the money we saved. Although I'm not sure I understand the economics, I'm enjoying both the homebrew spectrum analyzer and our new car.

references

1. Courtney Hall, WA5SNZ, "Understanding Spectrum Analyzers," *ham radio*, June, 1974, page 50.
2. *Spectrum Analysis*, Application Note 63, Hewlett-Packard, 1501 Page Mill Road, Palo Alto, California, May, 1965.
3. *More On Spectrum Analysis*, Application Note 63A, Hewlett-Packard, Palo Alto, California, November, 1965.
4. *Swept Frequency Techniques*, Application Note 65, Hewlett-Packard, Palo Alto, California, August, 1965.

ham radio

TR-7500



There are a number of good 2 meter FM transceivers on the market. You may already own one. But, even if you do, we suggest that you put your radio to this test. And, if you're thinking of buying one, this test should be a helpful guide.

	NO	YES
Is it PLL synthesized?	<input type="checkbox"/>	<input type="checkbox"/>
Does it have 100 channels (88 pre-programmed)?	<input type="checkbox"/>	<input type="checkbox"/>
Does it have 12 extra diode programmable channels?	<input type="checkbox"/>	<input type="checkbox"/>
Does it have single knob channel selection?	<input type="checkbox"/>	<input type="checkbox"/>
Does it have a LED digital frequency display?	<input type="checkbox"/>	<input type="checkbox"/>
Does it have a powered tone pad connection?	<input type="checkbox"/>	<input type="checkbox"/>
Does the receiver have helical resonators?	<input type="checkbox"/>	<input type="checkbox"/>

If your answer is NO to any of these, the TR-7500 is the radio that you should own. And, in addition to these important features, you get proven Kenwood quality, value and service.



Specifications

Semiconductors: Transistors	41
FETs	8
ICs	7
Diodes	35
Frequency Range:	146.01 to 147.99 MHz
Mode:	FM
No. of Channels:	100
Operating Temperature:	-20 to +50 degrees C
Power Voltage:	11.5 to 16.0V DC (13.8V DC nominal)

Grounding Polarity: Negative ground
Antenna Impedance: 50 Ohms

Current drain: Less than 0.5A in receive with no input signal
Less than 3A in transmit (HI) Less than 1.5A in transmit (LOW) (at 13.8V DC)

Dimensions: 172 mm (6-3/4") wide
250 mm (9-7/8") deep
75 mm (2-15/16") high

Weight: Approximately 2.2 kg (4.8 lbs.)

TRANSMIT SECTION
RF Output Power: High: 10 Watts
Low: 1 Watt (approximately)

Modulation: Variable reactance frequency shift
Frequency Deviation: ±5 KHz
Spurious Radiation: Better than -60dB

Tone Pad Input Impedance: 600 Ohms
Microphone: Dynamic microphone with PTT switch, 500 Ohms

RECEIVE SECTION
Receive System: Double conversion superheterodyne

Intermediate Frequency: 1st IF: 10.7 MHz
2nd IF: 455 kHz

Sensitivity: Better than 0.4 uV for 20dB quieting Better than 1 uV for 30dB S/N

Squelch Sensitivity: Better than 0.25 uV
Selectivity: 12kHz at -6dB down
40 kHz at -70dB down

Image Rejection: Better than -70dB
Spurious Interference: Better than -60dB

Audio Output: More than 1.5 watts across 8 Ohms load 10% distortion
Intermodulation: Better than 66dB

KENWOOD'S NEW TS-520S AND DG-5 DIGITAL FREQUENCY DISPLAY

A NEW STANDARD IN ECONOMY TRANSCEIVERS

The NEW TS-520S combines all of the fine, field-proven characteristics of the original TS-520 together with many of the ideas, comments, and suggestions for improvement from amateurs worldwide. Kenwood's ultimate objectives . . . to make quality equipment available at reasonable prices.

FULL COVERAGE TRANSCEIVER

The new TS-520S provides full coverage on all amateur bands from 1.8 to 29.7 MHz. Kenwood gives you 160 meter capability, WWV on 15.000 MHz., and an auxiliary band position for maximum flexibility. And with the addition of the TV-502 and TV-506 transverters, your TS-520S can cover 160 meters to 2 meters on SSB and CW.

DIGITAL DISPLAY DG-5 (option)

The new Kenwood DG-5 provides easy, accurate readout of your operating frequency while transmitting and receiving.

OUTSTANDING RECEIVER SENSITIVITY AND MINIMUM CROSS MODULATION

The new TS-520S incorporates a 3SK-35 dual gate MOSFET for outstanding cross modulation and spurious response characteristics. The 3SK35 has a low noise figure (3.5 dB typ.) and high gain (18 dB typ.) for excellent sensitivity.

NEW IMPROVED SPEECH PROCESSOR

A new audio compression amplifier gives you extra punch in the pile ups and when the going gets rough.

VERNIER TUNING FOR FINAL PLATE CONTROL

A new vernier tuning mechanism allows

easy and accurate adjustment of the plate control during tune-up.

FINAL AMPLIFIER

The new TS-520S is completely solid state except for the driver (12BY7A) and the final tubes. Rather than substitute TV sweep tubes as final amplifier tubes in a state of the art amateur transceiver, Kenwood has employed two husky S-2001A (equivalent to 6146B) tubes. These rugged, time-proven tubes are known for their long life and superb linearity.

HIGHLY EFFECTIVE NOISE BLANKER

An effective noise blanking circuit developed by Kenwood that virtually eliminates ignition noise is built-in to the TS-520S.

RF ATTENUATOR

The new TS-520S has a built-in 20 dB attenuator that can be activated by a push button switch conveniently located on the front panel.

VFO-520 — NEW REMOTE VFO

The VFO-520 remote VFO has been designed to match the styling of the TS-520S and provide maximum operating flexibility on the band selected on your TS-520S.

AC POWER SUPPLY

The TS-520S is completely self-contained with a rugged AC power supply built-in. The addition of the DS-1A DC-DC converter (option) allows for mobile operation of the TS-520S.

EASY CONNECTION PHONE PATCH

The TS-520S has 2 convenient RCA phono jacks on the rear panel for PHONE PATCH IN and PHONE PATCH OUT.

CW-520 — CW FILTER (OPTION)

The CW-520 500 Hz filter can be easily installed and will provide improved operation on CW.

AMPLIFIED TYPE AGC CIRCUIT

The AGC circuit has 3 positions (OFF, FAST, SLOW) to enable the TS-520S to be operated in the optimum condition at all times whether operating CW or SSB.

The TS-520S retains all of the features of the original TS-520 that made it tops in its class: RIT control • 8-pole crystal filter • Built-in 25 KHz calibrator • Front panel carrier level control • Semi-break-in CW with sidetone • VOX/PTT/MOX • TUNE position for low power tune up • Built-in speaker • Built-in Cooling Fan • Provisions for 4 fixed frequency channels • Heater switch.



Specifications

Amateur Bands: 160-10 meters
plus WWV (receive only)
Modes: USB, LSB, CW
Antenna Impedance: 50-75 Ohms
Frequency Stability: Within ± 1

kHz during one hour after one
minute of warm-up, and within
100 Hz during any 30 minute
period thereafter

Tubes & Semiconductors:

Tubes 3
(5Z0D1A x 2, 12BY7A)
Transistors 52
FETs 19
Diodes 101

Power Requirements: 120/220 V
AC, 50/60 Hz, 13.8 V DC
(with optional DS-1A)

Power Consumption: Transmit:
280 Watts Receive: 26 Watts
(with heater off)

Dimension: 333(13 $\frac{1}{4}$) W x 153 (6-0)
H x 335(13- (13-3/16) D mm(inch)

Weight: 16.0 kg(35.2 lbs)

TRANSMITTER

RF Input Power: SSB: 200 Watts
PEP CW: 160 Watts DC

Carrier Suppression: Better than
-40 dB

Sideband Suppression: Better
than -50 dB

Spurious Radiation: Better than
-40 dB

Microphone Impedance: 50k Ohms
AF Response: 400 to 2,600 Hz

RECEIVER

Sensitivity: 0.25 μ V for 10 dB
(S+N)/N

Selectivity: SSB: 2.4 kHz/-6 dB,
4.4 kHz/-60 dB

Selectivity: CW: 0.5 kHz/-6 dB,
1.5 kHz/-60 dB (with optional
CW-520 filter)

Image Ratio: Better than 50 dB

IF Rejection: Better than 50 dB

AF Output Power: 1.0 Watt (8

Ohm load, with less than 10%
distortion)

AF Output Impedance: 4 to 16
Ohms

DG-5

SPECIFICATIONS

Measuring Range: 100 Hz to
40 MHz

Input Impedance: 5 k Ohms
Gate Time: 0.1 Sec.

Input Sensitivity: 100 Hz to 40
MHz... 200 mV rms or over, 10
kHz to 10 MHz... 50 mV or over

Measuring Accuracy: Internal time
base accuracy ± 0.1 count

Time Base: 10 MHz

Operating Temperature: -10° to
50° C/14° to 122° F

Power Requirement: Supplied
from TS-520S or 12 to 16 VDC
(nominal 13.8 VDC)

Dimensions: 167(6-9/16) W x
43(1-11/16) H x 268(10-9/16) D
mm(inch)


Weight: 1.3 kg(2.9 lbs)

DG-5 (optional)



The luxury of digital readout is available on the TS-520S by connecting the new DG-5 readout (option). More than just the average readout circuit, this counter mixes the carrier, VFO, and heterodyne frequencies to give you your exact frequency. This handsomely-styled accessory can be set almost anywhere in your shack for easy to read operation... or set it on the dashboard during mobile operation for safety and convenience. Six bold digits display your operating frequency while you transmit and receive. Complete with DH (display hold) switch for frequency memory and 2 position intensity selector. The DG-5 can also be used as a normal frequency counter up to 40 MHz at the touch of a switch. (Input cable provided.)

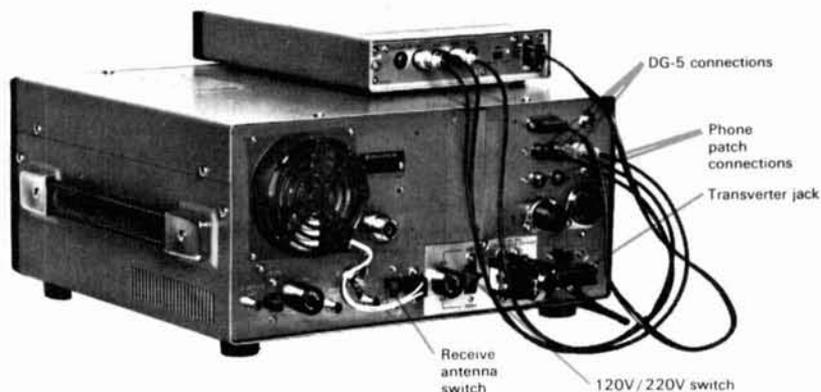NOTE: TS-520 owners can use the DG-5 with a DK-520 adapter kit.



TS-820S



We told you that the TS-820 would be the best. In little more than a year our promise has become a fact. Now, in response to hundreds of requests from amateurs, Kenwood offers the TS-820S... the same superb transceiver, but with the digital readout factory installed. The worldwide demand for the TS-820 far exceeded our initial production plans. However, production capacity has been substantially increased and our objective is to make the TS-820S more readily available to you. As an owner of this beautiful rig, you will have at your fingertips the combination of controls and features that even under the toughest operating conditions make the TS-820S the Pacesetter that it is.

Features

Following are a few of the TS-820S' many exciting features.

SPEECH PROCESSOR • An RF circuit provides quick time constant

compression using a true RF compressor as opposed to an AF clipper. Amount of compression is adjustable to the desired level by a convenient front panel control.

IF SHIFT • The IF SHIFT control varies the IF passband without changing the receive frequency. Enables the operator to eliminate unwanted signals by moving them out of the passband of the receiver. This feature alone makes the TS-820S a pacesetter.



TV-506

TV-502

VFO-820

TS-820S

SP-520

PLL • The TS-820S employs the latest phase lock loop circuitry. The single conversion receiver section performance offers superb protection against unwanted cross-modulation. And now, PLL allows the frequency to remain the same when switching sidebands (USB, LSB, CW) and eliminates having to recalibrate each time.

DIGITAL READOUT • The digital counter display is employed as an integral part of the VFO readout system. Counter mixes the carrier, VFO, and first heterodyne frequencies to give exact frequency. Figures the frequency down to 10 Hz and digital display reads out to

100 Hz. Both receive and transmit frequencies are displayed in easy to read, Kenwood Blue digits.

Specifications

FREQUENCY RANGE: 1.8-29.7 MHz (160 - 10 meters)
Modes: USB, LSB, CW, FSK
INPUT POWER: 200W PEP on SSB
 160 W DC on CW
 100 W DC on FSK
ANTENNA IMPEDANCE: 50-75 ohms, unbalanced
CARRIER SUPPRESSION: Better than -40 dB
SIDE BAND SUPPRESSION: Better than -50 dB
SPURIOUS RADIATION: Greater than -60 dB (Harmonics more than -40 dB)
RECEIVER SENSITIVITY: Better than 0.25uV

RECEIVER SELECTIVITY:
 SSB 2.4 kHz (-6 dB)
 4.4 kHz (-60 dB)
 CW* 0.5 kHz (-6 dB)
 1.8 kHz (-60 dB)
 *(with optional CW filter installed)
IMAGE RATIO: 160-15 meters: Better than 60 dB
 10 meters: Better than 50 dB
IF REJECTION: Better than 80 dB
POWER REQUIREMENTS: 120/220 VAC, 50/60 Hz, 13.8 VDC (with optional DS-1A DC-DC converter)
POWER CONSUMPTION: Transmit: 280 Watts
 Receive: 26 Watts (heaters off)
DIMENSIONS: 13-1/8" W x 6" H x 13-3/16" D
WEIGHT: 35.2 lbs (16 kg)

VFO-820
 Function switch provides any combination of transmit/receive/transceiver with the TS-820S. Both are equipped with VFO indicators showing which VFO is in use.

SP-520
 Although the TS-820S has a built-in speaker, the addition of the SP-520 provides improved tonal quality. A perfect match in both design and performance.

TV-502
 The TV-502 transverter puts you on 2-meters the easy way. Operates in the 144.0-145.7 MHz frequency range with a 145.0-146.0 MHz option. Completely compatible with the TS-820S, the TS-520S and most any HF transceiver.

TV-506
 Similar to the TV-502 except that it opens up the 6-meter band (50.0-54.0 MHz) to your HF rig.
 *The TS-820 and DG-1 are still available separately.

serial converter

for 8-level teleprinters

This converter translates Baudot to ASCII and ASCII to Baudot using readily available ICs — recommended for the experienced amateur only

At the outset I'd like to stress that this is a project for the experienced amateur with the technical know-how to connect the converter described to appropriate points in his demodulator or fsk circuit.

The heart of the converter is the universal asynchronous receiver/transmitter (UAR/T), a 40-pin IC that contains both an independent, 8-bit asynchronous, digital-data receiver, and an 8-bit asynchronous, digital-data transmitter. The UAR/T has been described earlier in *ham radio*.^{1,2}

Parts layout and wiring of the converter is quite a task in itself. Sockets are mandatory for the ICs as some are MOS devices, which are sensitive to ungrounded soldering irons. Fairly heavy bus wire is necessary for ground (common) and +5-volt leads. Also, liberal use of 0.01- μ F ceramic disc capacitors (not shown in the schematic) is required to bypass +5, and -12 volt circuits.

All NAND gates used as inverters can be replaced by hex inverters to reduce component count. Type 74121s can be replaced by 74123s except where both A inputs are used.

Those readers interested only in receiving RTTY with an 8-level machine can save much time and money by deleting the connections (except for grounds and clock inputs) to the much more complex ASCII-to-Baudot section, which is shown below the dashed lines of both UAR/Ts in **fig. 1**.

The cost for the complete converter should be well below \$100; possibly around \$50. The 8223 proms can be replaced with 82S23s, which are currently on the market for about \$3 each. The UAR/T ICs can be replaced with the GI AY-5-1013A, which is less expensive, about \$6.50. The 3351 fifo devices can be obtained for about \$14 through W6KS, as mentioned in the *RTTY Journal*. The other chips are standard devices and are available for about 50 cents or so.

Baudot-to-ASCII/ASCII-to-Baudot converters have been described in other publications but were not directly compatible with RTTY, which is a serial system, and didn't take advantage of the UAR/Ts.

circuit description

The converter schematic is shown in **fig. 1**. The serial 5-bit Baudot signal at TTL level enters U1 at pin 20 and appears in parallel form at pins 8 through 12. ICs U2, U3 sense whether letters or figures have been sent and set R/S flip-flop U4 to enable either U5 or U6, which translate the 5-bit Baudot code to 7-bit ASCII code; this translation appears at U6 pins 1 through 7. (The no. 8 bit is a parity bit, which is used with computers, and is unnecessary for amateur RTTY. I have modified my model 35ASR so that the no. 8 bit is always a zero.)

Output from U6 is applied to UAR/T U7 and appears in serial form at pin 25, which is connected through driver Q1 to a 4N33 opto-isolator, U8. Another 4N33, U9, is connected in series with U8, whose output with that of U8 is inserted into the loop of a model 33 or 35 ASR. This circuit keeps modifications of the ASCII machine to a minimum.

The signal originating from either the keyboard or tape reader of the ASCII machine is connected to the input of the second 4N33, U9, and its output serially feeds into U7-20. This data appears in parallel form at U7 pins 12 through 19.

Because there are no *LTRS* or *FIGS* in the ASCII code, these characters must be generated. For this reason the 6th and 7th ASCII bit, which appear at pins 7 and 6 respectively to U7, are sensed by 7474 flip-flop U10. In combination with 7474 flip-flop U11, U10 will disable the 8223 proms U12, U13 temporarily.

By Eric Kirchner, VE3CTP, Ontario Science Center, Don Mills, Ontario, Canada

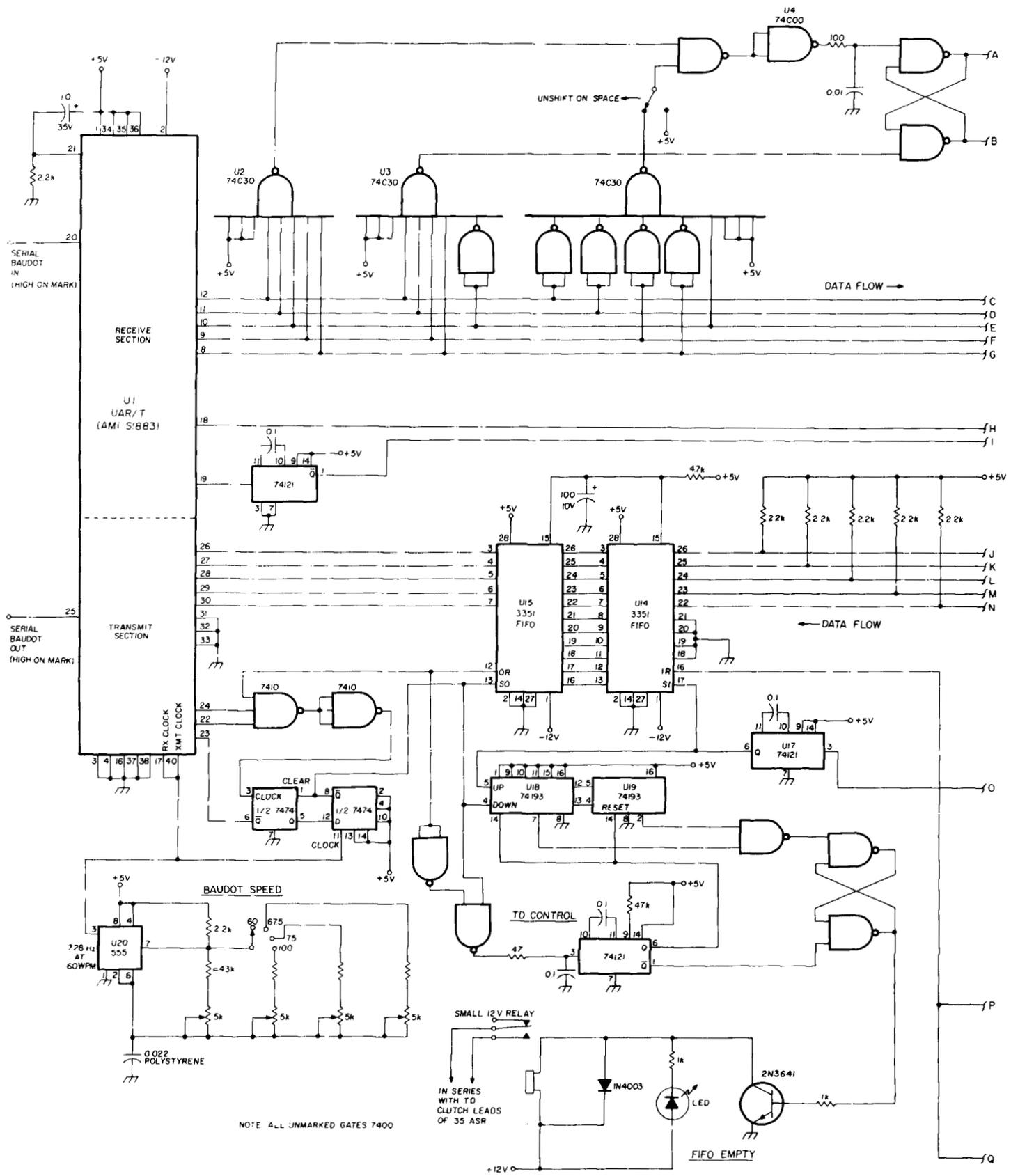


fig. 1. Schematic of the serial Baudot-to-ASCII-to-Baudot converter for model 33 and 35 ASR machines.

table 1. Program for 8223 prom, Baudot-to-ASCII letters (U5).

Word	A 4 3 2 1 0	Symbol	B 0 1 2 3 4 5 6 7
0	0 0 0 0 0	Blank	0 0 0 0 0 0 0 0
1	1 0 0 0 0	T	0 0 1 0 1 0 1 0
2	0 1 0 0 0	CR	1 0 1 1 0 0 0 0
3	1 1 0 0 0	O	1 1 1 1 0 0 0 1 0
4	0 0 1 0 0	Space	0 0 0 0 0 1 0 0
5	1 0 1 0 0	H	0 0 0 1 0 0 0 1 0
6	0 1 1 0 0	N	0 1 1 1 0 0 0 1 0
7	1 1 1 0 0	M	1 0 1 1 0 0 0 1 0
8	0 0 0 1 0	LF	0 1 0 1 0 0 0 0 0
9	1 0 0 1 0	L	0 0 1 1 0 0 0 1 0
10	0 1 0 1 0	R	0 1 0 0 1 0 1 0
11	1 1 0 1 0	G	1 1 1 0 0 0 0 1 0
12	0 0 1 1 0	I	1 0 0 1 0 0 0 1 0
13	1 0 1 1 0	P	0 0 0 0 1 0 1 0
14	0 1 1 1 0	C	1 1 0 0 0 0 1 0
15	1 1 1 1 0	V	0 1 1 0 1 0 1 0
16	0 0 0 0 1	E	1 0 1 0 0 0 0 1 0
17	1 0 0 0 1	Z	0 1 0 1 1 0 1 0
18	0 1 0 0 1	D	0 0 1 0 0 0 0 1 0
19	1 1 0 0 1	B	0 1 0 0 0 0 0 1 0
20	0 0 1 0 1	S	1 1 0 0 1 0 1 0
21	1 0 1 0 1	Y	1 0 0 1 1 0 1 0
22	0 1 1 0 1	F	0 1 1 0 0 0 0 1 0
23	1 1 1 0 1	X	0 0 0 1 1 0 1 0
24	0 0 0 1 1	A	1 0 0 0 0 0 0 1 0
25	1 0 0 1 1	W	1 1 1 0 1 0 1 0
26	0 1 0 1 1	J	0 1 0 1 0 0 0 1 0
27	1 1 0 1 1	FIGS	0 0 0 1 1 0 0 0
28	0 0 1 1 1	U	1 0 1 0 1 0 1 0
29	1 0 1 1 1	Q	1 0 0 0 1 0 1 0
30	0 1 1 1 1	K	1 1 0 1 0 0 0 1 0
31	1 1 1 1 1	LTRS(delete)	1 1 1 1 1 1 1 0

table 2. Program for 8223 prom, Baudot-to-ASCII figures (U6).

Word	A 4 3 2 1 0	Symbol	B 0 1 2 3 4 5 6 7
0	0 0 0 0 0	Blank	0 0 0 0 0 0 0 0
1	1 0 0 0 0	5	1 0 1 0 1 1 0 0
2	0 1 0 0 0	CR	1 0 1 1 0 0 0 0
3	1 1 0 0 0	9	1 0 0 1 1 1 0 0
4	0 0 1 0 0	Space	0 0 0 0 0 1 0 0
5	1 0 1 0 0	#	1 1 0 0 0 1 0 0
6	0 1 1 0 0	.	0 0 1 1 0 1 0 0
7	1 1 1 0 0	.	0 1 1 1 0 1 0 0
8	0 0 0 1 0	LF	0 1 0 1 0 0 0 0
9	1 0 0 1 0)	1 0 0 1 0 1 0 0
10	0 1 0 1 0	4	0 0 1 0 1 1 0 0
11	1 1 0 1 0	&	0 1 1 0 0 1 0 0
12	0 0 1 1 0	8	0 0 0 1 1 1 0 0
13	1 0 1 1 0	0	0 0 0 0 1 1 0 0
14	0 1 1 1 0	:	0 1 0 1 1 0 1 0
15	1 1 1 1 0	;	1 1 0 1 1 1 0 0
16	0 0 0 0 1	3	1 1 0 0 1 1 0 0
17	1 0 0 0 1	"	0 1 0 0 0 1 0 0
18	0 1 0 0 1	\$	0 0 1 0 0 1 0 0
19	1 1 0 0 1	?	1 1 1 1 1 1 0 0
20	0 0 1 0 1	Bell	1 1 1 0 0 0 0 0
21	1 0 1 0 1	6	0 1 1 0 1 1 0 0
22	0 1 1 0 1	!	1 0 0 0 0 1 0 0
23	1 1 1 0 1	/	1 1 1 1 0 1 0 0
24	0 0 0 1 1	-	1 0 1 1 0 1 0 0
25	1 0 0 1 1	2	0 1 0 0 1 1 0 0
26	0 1 0 1 1	1	1 1 1 0 0 1 0 0
27	1 1 0 1 1	FIGS	0 0 0 1 1 0 0 0
28	0 0 1 1 1	7	1 1 1 0 1 1 0 0
29	1 0 1 1 1	!	1 0 0 0 1 1 0 0
30	0 1 1 1 1	(0 0 0 1 0 1 0 0
31	1 1 1 1 1	LTRS	1 1 1 1 1 1 1 0

If a *LTRS* character must be inserted into the text, transistor Q2, a 2N3641, will be nonconducting so that all bits on the left-hand side of proms U12, U13 will be high, signifying the *LTRS* code. If a *FIGS* character must be inserted into text, Q2 will conduct, making the center bit a zero, which signifies the *FIGS* code.

The ASCII bits are applied to the address lines of 8223 proms U12, U13. Here the ASCII code is translated into the corresponding Baudot code; this data is fed into the two 3351 fifos, U14 and U15. A "data available" pulse at U7-19, delayed by the two 74121 one-shots (U16, U17), appears at the "shift-in" pin of U14 (pin 17). The Baudot characters are thus loaded into the fifo memory.

The fifo memories are necessary because the information from the ASCII machine is fed in at 100 wpm, while the Baudot output from UAR/T U1 is at 60 wpm. When typing, the ASCII speed will exceed 60 wpm only occasionally. However, when the ASCII tape reader runs, the memory will eventually become fully loaded. Because the two fifos can store only 80 characters, the tape reader control circuit, consisting of up-down counter U18, U19, will interrupt current to the tape-reader clutch, holding it until the fifo memory is again empty.

The parallel data at fifo U15 output is applied to UAR/T U1 and appears in serial form at TTL level at

U1-25. This signal can be used to key an afsk generator, as described below.

The 555 clocks, U20, U21, will be stable if high-grade components are used. Crystal stability is nice but unnecessary. Precise resistance values have not been given as they may differ from case-to-case, but they can be easily determined with a frequency counter.

Because the equivalent Baudot character for the ASCII space signal is contained in the ASCII-to-Baudot *FIGS* prom, a space signal between words is always preceded and followed by a *LTRS* and *FIGS* signal. This is undesirable because two extra characters will be sent, which are unnecessary. This problem can be resolved by TTL IC U22 which steers U10 (fig. 1).

Note that when using the converter with an afsk demodulator it may be necessary to insert a level changer, inverter, or both between the demodulator and U1-20. The data must enter this point at TTL level. The *Baudot speed* switch (fig. 1) allows you to copy signals at speeds other than the amateur speed of 60 wpm.

Pin numbers for the gates in fig. 1 (type 7400s) have not been given as a new layout will be made for the final version. Except for the proms, the ICs in the Baudot to ASCII section are CMOS devices. These happened to be available, so they were used. The cir-

table 3. Program for 8223 prom, ASCII-to-Baudot letters (U13).

Word	A 4 3 2 1 0	Symbol	B 0 1 2 3 4 5 6 7
0	0 0 0 0 0	Null	0 0 0 0 0 0 0 0
1	0 0 0 0 1	A	1 1 0 0 0 0 0 0
2	0 0 0 1 0	B	1 0 0 1 1 0 0 0
3	0 0 0 1 1	C	0 1 1 1 0 0 0 0
4	0 0 1 0 0	D	1 0 0 1 0 0 0 0
5	0 0 1 0 1	E	1 0 0 0 0 0 0 0
6	0 0 1 1 0	F	1 0 1 1 0 0 0 0
7	0 0 1 1 1	G	0 1 0 1 1 0 0 0
8	0 1 0 0 0	H	0 0 1 0 1 0 0 0
9	0 1 0 0 1	I	0 1 1 0 0 0 0 0
10	0 1 0 1 0	J	1 1 0 1 0 0 0 0
11	0 1 0 1 1	K	1 1 1 1 0 0 0 0
12	0 1 1 0 0	L	0 1 0 0 1 0 0 0
13	0 1 1 0 0	M	0 0 1 1 1 0 0 0
14	0 1 1 1 0	N	0 0 1 1 0 0 0 0
15	0 1 1 1 1	O	0 0 0 1 1 0 0 0
16	1 0 0 0 0	P	0 1 1 0 1 0 0 0
17	1 0 0 0 1	Q	1 1 1 0 1 0 0 0
18	1 0 0 1 0	R	0 1 0 1 0 0 0 0
19	1 0 0 1 1	S	1 0 1 0 0 0 0 0
20	1 0 1 0 0	T	0 0 0 0 1 0 0 0
21	1 0 1 0 1	U	1 1 1 0 0 0 0 0
22	1 0 1 1 0	V	0 1 1 1 1 0 0 0
23	1 0 1 1 1	W	1 1 0 0 1 0 0 0
24	1 1 0 0 0	X	1 0 1 1 1 0 0 0
25	1 1 0 0 1	Y	1 0 1 0 1 0 0 0
26	1 1 0 1 0	Z	1 0 0 0 1 0 0 0
27	1 1 0 1 1	Null	0 0 0 0 0 0 0 0
28	1 1 1 0 0	Null	0 0 0 0 0 0 0 0
29	1 1 1 0 1	CR	0 0 0 1 0 0 0 0
30	1 1 1 1 0	LF	0 1 0 0 0 0 0 0
31	1 1 1 1 1	Null	0 0 0 0 0 0 0 0

table 4. Program for 8223 prom, ASCII-to-Baudot letters (U12).

Word	A 4 3 2 1 0	Symbol	B 0 1 2 3 4 5 6 7
0	0 0 0 0 0	Space	0 0 1 0 0 0 0 0
1	0 0 0 0 1	!	1 0 1 1 0 0 0 0
2	0 0 0 1 0	"	1 0 0 0 1 0 0 0
3	0 0 0 1 1	#	0 0 1 0 1 0 0 0
4	0 0 1 0 0	\$	1 0 0 1 0 0 0 0
5	0 0 1 0 1	Null	0 0 0 0 0 0 0 0
6	0 0 1 1 0	&	0 1 0 1 1 0 0 0
7	0 0 1 1 1	,	1 1 0 1 0 0 0 0
8	0 1 0 0 0	(1 1 1 1 0 0 0 0
9	0 1 0 0 1)	0 1 0 0 1 0 0 0
10	0 1 0 1 0	Null	0 0 0 0 0 0 0 0
11	0 1 0 1 1	Null	0 0 0 0 0 0 0 0
12	0 1 1 0 0	.	0 0 1 1 0 0 0 0
13	0 1 1 0 1	-	1 1 0 0 0 0 0 0
14	0 1 1 1 0	.	0 0 1 1 1 0 0 0
15	0 1 1 1 1	/	1 0 1 1 1 0 0 0
16	1 0 0 0 0	0	0 1 1 0 1 0 0 0
17	1 0 0 0 1	1	1 1 1 0 1 0 0 0
18	1 0 0 1 0	2	1 1 0 0 1 0 0 0
19	1 0 0 1 1	3	1 0 0 0 0 0 0 0
20	1 0 1 0 0	4	0 1 0 1 0 0 0 0
21	1 0 1 0 1	5	0 0 0 0 1 0 0 0
22	1 0 1 1 0	6	1 0 1 0 1 0 0 0
23	1 0 1 1 1	7	1 1 1 0 0 1 0 0
24	1 1 0 0 0	8	0 1 1 0 0 0 0 0
25	1 1 0 0 1	9	0 0 0 1 1 0 0 0
26	1 1 0 1 0	:	0 1 1 1 0 0 0 0
27	1 1 0 1 1	;	0 1 1 1 1 0 0 0
28	1 1 1 0 0	Null	0 0 0 0 0 0 0 0
29	1 1 1 0 1	Null	0 0 0 0 0 0 0 %
30	1 1 1 1 0	Null	0 0 0 0 0 0 0 0
31	1 1 1 1 1	LTRS	1 0 0 1 1 0 0 0

cuit should work just as well with TTL devices. Fig. 2 shows socket connections for the devices.

The circuit in fig. 3 makes programming a cinch as the burn-out time is automatically determined by the 74121 one-shot, U1. The time is fixed at 150 milliseconds. Programming must be done carefully, while you're wide awake, or mistakes are bound to occur! The +15 and +5-volt leads must be connected to a regulated power supply that provides at least 1 ampere. Proceed as follows:

1. With the power supply shut off, insert the 8223 to be programmed into its socket.
2. Set S2B to *BURN*.
3. Set address switches S3-S7 and output switch S8 according to the program pattern for the first bit.
4. Switch on the power supply and depress S1.
5. Set S3-S7 and S8 to the next bit and depress S1. Continue this procedure, bit-by-bit, until the entire pattern is programmed into the chip. You can test the programming by setting S2 to *TEST*. Go through the entire pattern again, using switches S3-S7 and S8. The LED will illuminate for a 1 and remain dark for a zero. If the test yields the desired pattern your 8223 is ready for use.

Four 8223s are necessary for the Baudot-to-ASCII conversion and vice versa. For more information on

the makeup of the programming pattern, see reference 3. An article describing a memory for automatic CW identification using an 8223 prom can be found in reference 4.

In tables 1-4 you'll find one program for each of the four proms used in the code converter. The A column determines the prom address line switch positions, while the B column determines the switch positions of the prom outputs.

example

To program the letter Y into the prom that translates Baudot to ASCII letters (table 1), proceed as follows:

1. Set switches S2A-B to *TEST* and set the prom output line-selector switch, S8, to *B0*.
2. Look up the letter Y on the program (table 1).
3. Set the address line switches, S3-S7 (fig. 3) according to the information in the table: A4 = high; A3 = low; A2 = high; A1 = low; and A0 = high — i.e., 10101. (Low is ground and high is +5 volts.)
4. Set switches 2A-B to *BURN*.
5. Set the prom output line switch to *B0* (a 1 in this case), then depress switches S1A-B.
6. Advance the output line selector switch to *B3*, picking up another 1.

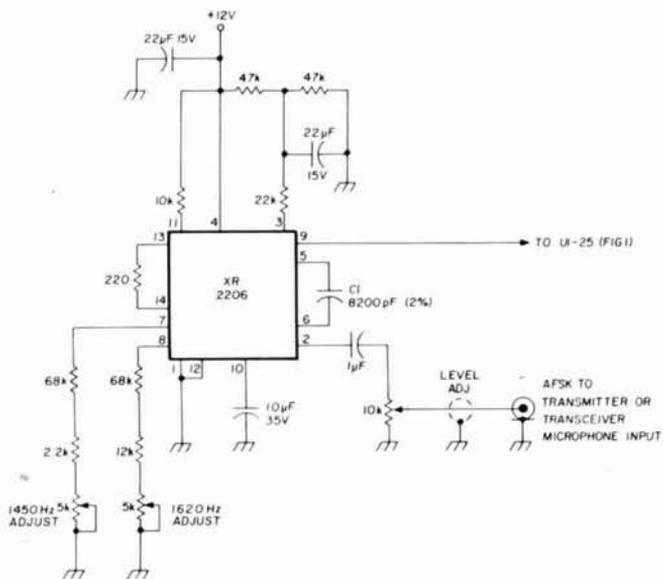


fig. 4. AFSK generator. Phase-continuous frequency shift is featured to prevent out-of-band transients. Sine-wave frequency is determined by C1 and the total resistance connected to either pin 7 or 8 of the XR2206.

The afsk-generator audio frequencies of 1620 and 1450 Hz were chosen to put the second harmonic outside the passband of modern ssb equipment and to eliminate the need for special carrier-frequency crystals in such equipment.

The overall converter system can be tested by feeding data from a Baudot keyboard or tape reader to U1-20 (fig. 1). As the output and input of U7 are a closed loop through the two 4N33 optoisolators, U8 and U9, the data is fed back to U1, and its output at pin 25 can be used to operate the printer magnets of the Baudot machine through a suitable driver. In this case, the Baudot data is converted to ASCII, then back to Baudot. The only character not translated from ASCII to Baudot is the bell signal. With additional gates this could be accomplished, but I felt that the additional complexity was unjustified.

acknowledgement

I'd like to thank my friend, Paul Hudson, VE3CWA, for suggestions in preparing this article.


references

1. J. A. Titus, "The UAR/T and How it Works," *ham radio*, February, 1976, page 58.
2. P. E. Field et al, "Microcomputer Interfacing: a Software UAR/T," *ham radio*, November, 1976, page 60.
3. R. D. Pascoe, "How to Program Read-Only Memories," *Popular Electronics*, July, 1975, page 27.
4. L. Nurse, W6LLO, "CW Memory for RTTY Identification," *ham radio*, January, 1974, page 6.
5. E. Kirchner, VE3CTP, "Continuous-Phase Audio-Shift Keyer for RTTY," *ham radio*, October, 1973, page 10.

ham radio

An Introductory offer **SAVE**

HIRAM PERCY MAXIM

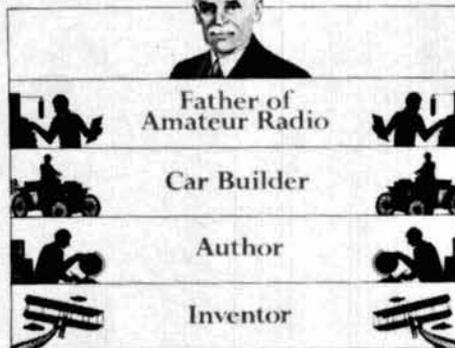

By Alice Clink Schumacher

Revised Second Printing with Full Color Cover



FATHER OF AMATEUR RADIO

Organized, guided, promoted and 3 times saved Amateur Radio from being legislated out of existence.



PIONEER IN THE AUTO INDUSTRY

49 patents many of which are features in today's cars. Drove the first car in Connecticut.



AUTHOR

Three books, movie script and syndicated newspaper column.



INVENTOR

Known to the world as the Inventor of the Maxim Silencer and pioneer in gilders, home movies, air conditioning and space research.

It all adds up to reading excitement — a great book about a great man and a must for every Radio Amateur bookshelf. **Order HR-HPM — SAVE 55¢ — Regularly \$4.50 — NOW JUST \$3.95**

Greenville, NH 03048

ham radio's communications bookstore

Enclosed is check or money order for _____

Please send _____ copies @ \$3.95

Name _____

Address _____

City _____ State _____ Zip _____

FINGER TIP CONTROL

ATLAS 210x / 215x


5 BAND—200-WATT ALL SOLID STATE HF SSB/CW TRANSCEIVER

From its compact size of 9½" x 3½" x 9½" and 7 pounds weight, to its silky smooth tuning dial, the Atlas 210x/215x gives you finger tip control.

Even its mobile mount and AC console are specially designed so you simply slip the 210x or 215x into them, and connections for the antenna jack, mic jack, and AC or DC input are all made automatically.

But don't let its finger tip size fool you. The Atlas 210x/215x transceivers are packed full of the most advanced, state of the art engineering, and provide unequalled performance in both transmit and receive modes.

Model 210x or 215x Transceiver	\$679.
(With noise blanker installed add \$40)	
Plug-in Mobile Kit	\$ 48.
Portable AC Supply 110/220V	\$100.
AC Console 110/220V	\$149.
(With VOX and semi-CW installed add \$46)	
10XB Crystal Osc. less crystals	\$ 59.

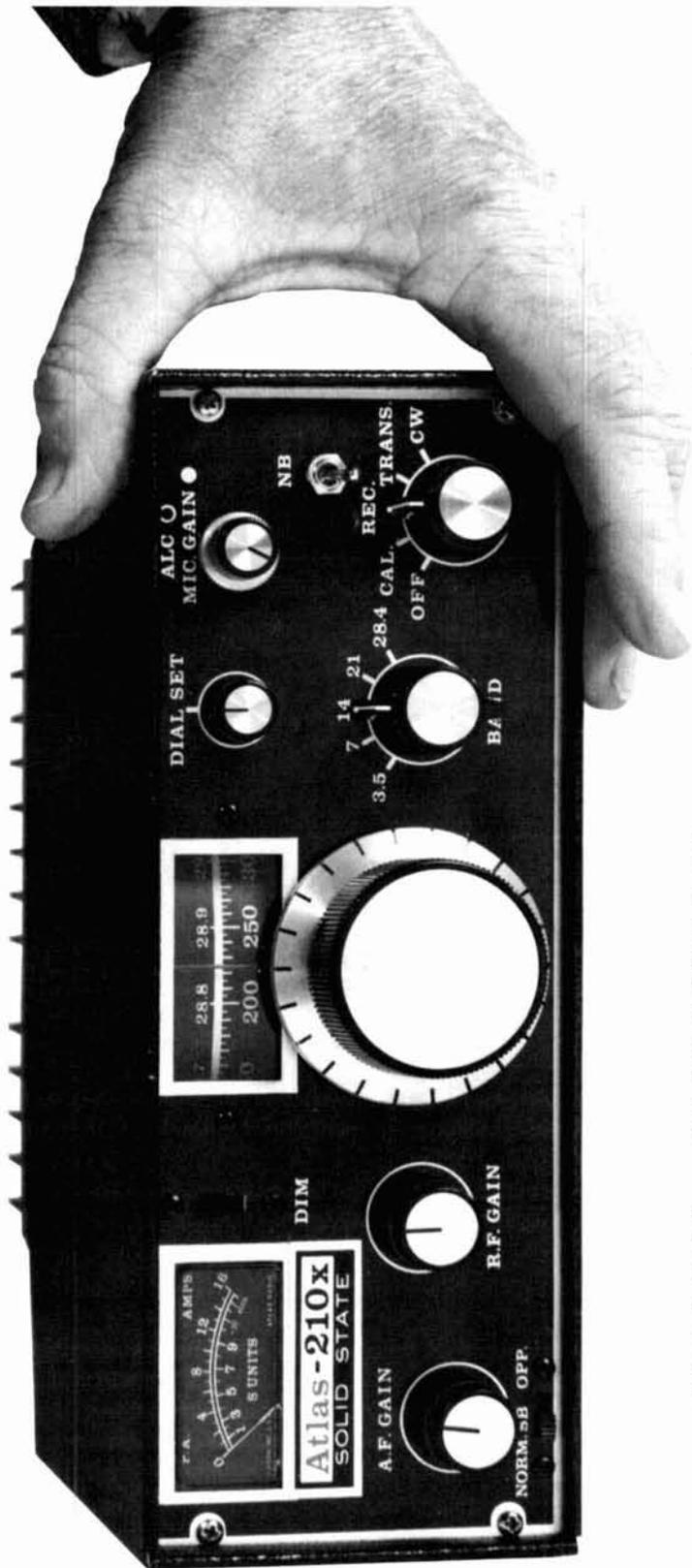


**ATLAS
RADIO INC.**

417 Via Del Monte, Oceanside, CA 92054
Phone (714) 433-1983
Special Customer Service Direct Line
(714) 433-9591

For complete details see your Atlas dealer, or drop us a card and we'll mail you a brochure with dealer list.

ATB-34

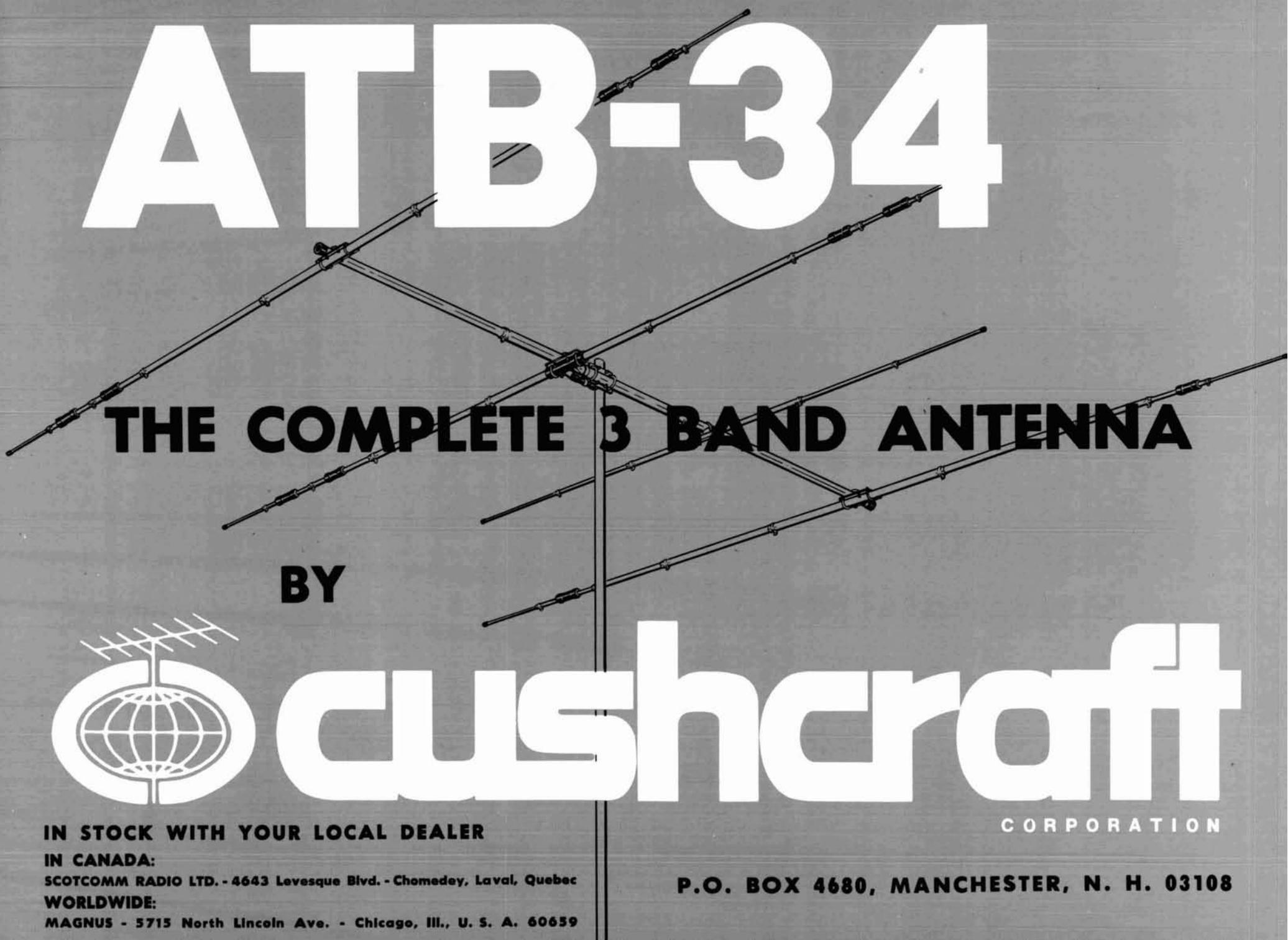

THE COMPLETE 3 BAND ANTENNA

BY



cushcraft

CORPORATION

IN STOCK WITH YOUR LOCAL DEALER

IN CANADA:

SCOTCOMM RADIO LTD. - 4643 Levesque Blvd. - Chomedey, Laval, Quebec

WORLDWIDE:

MAGNUS - 5715 North Lincoln Ave. - Chicago, Ill., U. S. A. 60659

P.O. BOX 4680, MANCHESTER, N. H. 03108

admittance, impedance and circuit analysis

A circuit with impedances seems very complicated to those lacking experience in circuit analysis. Throw in names like *admittance*, *conductance*, or *susceptance*, and circuit analysis seems to take on a certain mystique beyond the average amateur. Many texts present such a bewildering array of symbols and mathematical operators that analysis seems hopeless unless you have a computer. Wrong — all you need is paper, pencil, and a pocket calculator.

Impedance, admittance, and complex numbers are really simple expressions with a few extra rules. Once you know them and how to set up an analysis "model," the rest is just careful number manipulation. Presented here are the basics, how to handle them, and simple circuit modeling for the majority of transmitter and receiver circuits.

If the names and expressions are unfamiliar, just read and study slowly. They will become familiar with a little practice.

the rectangular form

The two forms of expressing impedance or admittance are *rectangular* and *polar*. Fig. 1 shows the rectangular form with the expressions and circuit symbols in columns for impedance, Z , and admittance, Y .

Any L C R (inductance, capacitance, and resistance) combination can be shown as either an impedance or an admittance because each is the inverse of the other. Common use has a series combination given as impedance, a parallel combination as admittance. Opposite expressions are shown later.

If you are unfamiliar with complex number notation, pay attention to the j symbol. The j , also called the *j-operator*, denotes everything to the right of it as *imaginary*. This is in the mathematical sense since $j = \sqrt{-1}$, an imaginary number. A complex number has a *real* part (the resistance, R , or conductance, G) and an *imaginary* part (the reactance, X , or susceptance, B). Ordinary math rules apply only to the real part or the imaginary part. Rules for handling both at the same time are given later.

Values of impedance, resistance, and reactance are given in familiar ohms values. Values of admittance, conductance, and susceptance are given in *mhos*. Some time ago the inverse spelling was ap-

plied because admittance is the inverse of impedance. If $R = 10 \text{ ohms}$, then $G = 0.1 \text{ mho}$.

reactance and susceptance

Both are frequency sensitive; that is, their ohm and mho values vary with frequency. This is shown by

$$\begin{array}{ll} X_L = \omega L & B_L = -1/\omega L \\ X_C = -1/\omega C & B_C = \omega C \end{array}$$

with L in henries, C in farads, and

$$\omega = 2\pi f$$

where f is in hertz (radian frequency). The subscript refers to inductance or capacitance. Total reactance or susceptance is expressed without a subscript as

$$\begin{array}{l} X = \omega L - (1/\omega C) \\ B = \omega C - (1/\omega L) \end{array}$$

Note especially that signs are shown; this *must* be followed in reactance and susceptance calculation. Remember the resonance condition where inductive and capacitive reactance (or susceptance) cancels.

Imaginary parts can be stated in opposite terms:

$$\begin{array}{l} X = -1/(B_C + B_L) = -1/B \\ B = -1/(X_C + X_L) = -1/X \end{array}$$

Note the signs. Reactance and susceptance are related by *negative* inversions while resistance and conductance are related by *positive* inversions. Real and imaginary parts are handled separately and the part relationships are different but admittance is still the inverse of impedance and vice-versa. Y and Z are complex numbers of different rules while R , X , G and B are simple numbers with ordinary rules.*

Most modern hand-held calculators have a pi-constant key and at least one memory register. Storing the radian frequency ($2\pi f$) in memory allows rapid calculation of X or B values. For *rf* circuits, entering scaled values of megahertz, microhenries,

*A good algebra text will show the proof and following rules for those readers desiring more information.

By Leonard H. Anderson, 10048 Lanark Street, Sun Valley, California 91352

or microfarads saves using the exponent key or inputting lots of zeros.

With complex numbers $(a + jb)$ and $(c + jd)$, the rules are:

$$(a + jb) + (c + jd) = (a + c) + j(b + d)$$

$$(a + jb) - (c + jd) = (a - c) + j(b - d)$$

Notice the expression statements on each side. On the left there are two complex numbers indicated by the parenthesis. The right side shows that each part of the complex answer has at least two terms. The j -operator designates the entire b, d term group as imaginary.

The addition rule is useful for expressing a combination LCR circuit as one impedance if all components are in series. Suppose the inductor has winding resistance. The total resistance is the sum of R and winding resistance. The inductive reactance adds to capacitive reactance and each could be in the two impedances or combined in one of them. Any number of combinations, including parallels, can be added to give one real part and one imaginary part. Remember to keep the parts separate, observe signs, use admittance for parallel combinations, and impedance for series combinations.

table 1. Keyboard steps. HP-35 calculator impedance/admittance conversion.

	Stack Registers					
Keyboard	x	y	z	t		Display. (remarks)
Input R	R					
1 STO	R					(hold R in memory)
Input X	X					
2 ENTER	X	X				
3 ENTER	X	X	X			(fill stack with X)
4 X	X ²	X				
5 RCL	R	X ²	X			
6 RCL	R	R	X ²	X		
7 X	R ²	X ²	X			
8 +	Mag ²	X				
9 \sqrt{x}	Mag	X				Z Magnitude
10 1/x	1/M	X				Y Magnitude
11 xy	X	1/M				
12 RCL	R	X	1/M			
13 +	X/R	1/M				
14 arc						
15 tan	pha	1/M				Z phase angle
16 CHS	- pha	1/M				Y phase angle
17 STO						(hold angle in memory)
18 RI	1/M					
19 ENTER	1/M	1/M				
20 ENTER	1/M	1/M	1/M			(fill stack with Y magnitude)
21 RCL	- pha	1/M	1/M	1/M		
22 cos	Cos	1/M	1/M	1/M		
23 X	G	1/M	1/M			conductance
24 x-y	1/M	G	1/M			
25 RCL	- pha	1/M	G	1/M		
26 sin	Sin	1/M	G	1/M		
27 X	B	G	1/M			susceptance

28 1/x	1/B	G				
29 CHS	Xp	G				parallel reactance
30 x-y	G	Xp				
31 1/x	Rp	Xp				parallel resistance

The sign in front of the j -operator can take the sign of the imaginary part. This is strictly a sign and *does not* mean the *parts of one* complex number add or subtract. The subtraction rule will be useful in impedance matching to be discussed later.

why admittance?

There are as many parallel combinations of com-

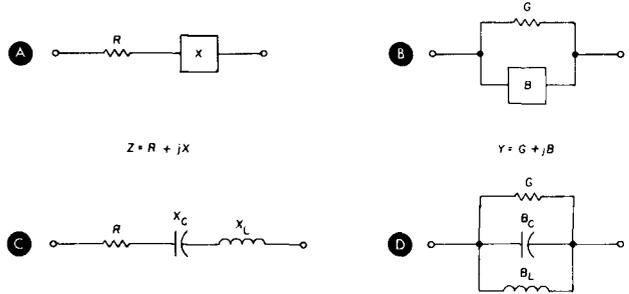


fig. 1. Rectangular form of impedance and admittance.

ponents as there are those in series. Any circuit to be analyzed should be separated into *branches* of component combinations in series or parallel. Each branch is then expressed as an admittance or impedance having only two connections or *nodes*. The easiest form of expressing a parallel combination is admittance since all real parts and all imaginary parts add.

In fact, you have probably been using admittance without realizing it. The familiar parallel resistance formula

$$R_{total} = \frac{R_1 R_2}{R_1 + R_2}$$

was derived from the basic expression

$$R_{total} = \frac{1}{(1/R_1) + (1/R_2) + \dots + (1/R_n)}$$

Invert the basic expression and you will find the sum of conductances $(1/R)$ equals total conductance.

multiplying and dividing complex numbers

These will be used in solving the circuit or converting admittance to impedance and vice-versa. The rules are:

$$(a + jb) \times (c + jd) = (ac - bd) + j(ad + bc)$$

$$\frac{(a + jb)}{(c + jd)} = \left[\frac{(ac + bd)}{(c^2 + d^2)} \right] + j \left[\frac{(bc - ad)}{(c^2 + d^2)} \right]$$

$$(inversion) 1/(a + jb) = [a/(a^2 + b^2)] - j[b/(a^2 + b^2)]$$

These rules are hard to work with, even with a calculator. There is an easier way by using the *polar form equivalents* shown in **fig. 2**. The angle symbol is as important as the j -operator: All terms to the

right of the angle symbol are, appropriately, *angles*; terms to the left are *magnitudes*.

$$(A \angle \phi) \times (B \angle \theta) = (A \times B) \angle (\phi + \theta)$$

$$\frac{(A \angle \phi)}{(B \angle \theta)} = \frac{A}{B} \angle (\phi - \theta)$$

$$(inversion) \quad \frac{1}{A \angle \phi} = \frac{1}{A} \angle -\phi$$

Magnitudes operate algebraically just like the polar expression, but angles add or subtract. Again, the

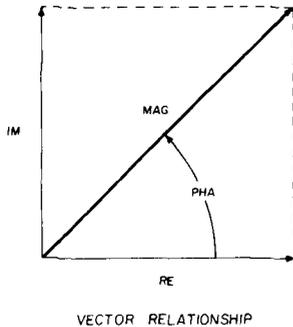


fig. 2. Comparison of the rectangular and polar form.

parts are different from the whole. A calculator with trig functions is preferred; one with built-in polar/rectangular conversion is even better.

polar form

Y and Z can be expressed equally well this way. This has the advantage of showing magnitude and phase angle as shown by the little vector diagram of **fig. 2**. Voltage and current in a complex circuit will also be complex quantities. The ac or rf voltage you measure in a circuit is the magnitude. Phase angle is also measurable although the instruments cost more. Some rf bridges read directly in polar form.

Both forms are needed in circuit analysis. Rectangular form can be used in calculating circuit branch values while the polar form is used for voltage response and as an intermediate step in conversion. Input impedance or admittance can be expressed in either form. The angle is a signed number but the magnitude is always a *positive* number.

form conversion by calculator

All of the expressions and forms necessary for circuit analysis have now been presented. Before going into the analysis setup it is useful to observe conversion of impedance to admittance with the aid of rectangular/polar form changes. The program steps in **table 1** apply to the older HP-35 model or any other *RPN/Stack* machine that does not have polar/rectangular conversion functions.

This form conversion is basic to the ladder network solution to be presented later. Calculators with built-

in functions can use part of this step sequence, either manually or automatically with a programmable version.

Steps 4 through **15** change rectangular impedance to polar impedance. **Step 10** finds the polar admittance magnitude; its location in the sequence is arbitrary and could be placed after **step 18**. **Step 16** finds the polar admittance angle.

Steps 17 to **20** set up the registers for polar to rectangular conversion — the remaining steps perform it. The magnitude inversion and angle sign change has already done conversion of impedance to admittance. Polar/rectangular identities are the same for impedance and admittance.

Steps 28 to **31** are used only to show how parallel resistance and reactance are derived from the main program. There are simpler ways to derive the parallel equivalents from series components. You are invited to try out the simpler way from the formulas given. If you succeed, you have already begun programming.

Steps 1 to **27** will convert admittance to impedance without changing any steps. To prove this to yourself, just change the terms and expressions in the register and remarks columns.

As an example, $Z = 4 + j3$ ohms converts to $Y = 0.16 - j0.12$ mhos. The parallel reactance equivalent is 8.33 ohms, resistance equivalent is 6.25 ohms.

the analysis model

The term *model* simply means the branches connected at nodes. A reduction to this structure is done to simplify overall calculations calculation time and effort. The basic pi structure in **fig. 3** can be used with almost every circuit and is expandable to a ladder structure.

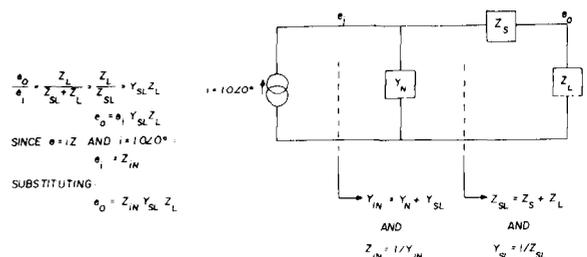


fig. 3. Basic model structure of the familiar pi network.

The model is allowed only one signal source, a current of 1.0 ampere with no phase angle. Any source admittance must be included as part of Y_n . A unity current source allows each output voltage, e_o , to be relative and the solution to be dependent solely on impedances and admittances in the model. This is the simplest method and applies well to calculator solution.

It may seem that a relative e_o solution is unrealistic

but this is only partly true. Networks such as filters are almost always described in relative terms. As an example, an i-f amplifier can be modeled as several individual blocks with individual block model response summed for overall response. The actual e_o can be found by multiplying relative e_o by the actual input current.

Most of us think of an amplifier stage as output vs input. For the model the transistor or tube must be split into the input impedance and the output admittance with a current source that is dependent on input signal. Most data sheets on transistors and tubes are oriented to this form.

Most of us also think of an amplifier output in terms of voltage. Since voltage is easiest to measure, it is easy to neglect current. All transistor collectors and pentode tube plates are really current sources with an output admittance (h_{oe} for common emitter, $1/\tau_p$ for pentodes). Measured output voltage is the product of the current source and the *total* load impedance, including output admittance of the device. The scarcity of ac current measuring instruments has misled a lot of us in understanding actual circuit operation.

The basic pi model can be thought of as the coupling circuit between two amplifiers. The output admittance of the first becomes part of Y_n , and the input impedance of the second becomes part of Z_L . The current flowing into the second state input can be found relative to unity (the model input current) because the output voltage is known.

You can use Ohm's law with complex quantities. The difference from dc is that current and voltage have *both* magnitude and phase angle. The rectangular form also applies, but the polar form is more convenient since an ac voltmeter measures magnitude. An oscilloscope will display voltage phase angle but that is dependent on the scope sweep triggering point; a dual-trace scope shows *relative* voltage phase.

Note the progression of Z and Y looking towards the load in **fig. 3**. This is important to the model extension following.

extending the model for ladder networks

A *ladder* configuration is a shunt-series-shunt sequence — a five-branch model is shown in **fig. 4**. Again, the current source is unity and e_o is relative and solved directly from impedances and admittances. This model is well suited to filter analysis.

Output voltage solution is self-explanatory but note the progression of Y_{12} to Z_{45} .* Y_{12} is the inverted sum of Z_d and Z_L ; Z_{23} is the inverted sum of Y_c and Y_{12} , and so on. Each Y or Z is the total, looking towards the load, of the model Y and Z at each node. Z_{45} is the *total* input impedance; the network input

admittance is found by subtracting source admittance from $Y_{45}(1/Z_{45})$.

So far, circuit analysis seems complicated and a lot of work. Here is where the calculator comes in handy and it is useful to recall the form-conversion calculator steps in **table 1**. Let's assume that all shunt branches have been precalculated for admittance and all series branches in impedance.

Enter Y_L and begin the conversion. Pause when you reach the magnitude and angle of Z_L , and write down the polar values. By **step 27** the rectangular

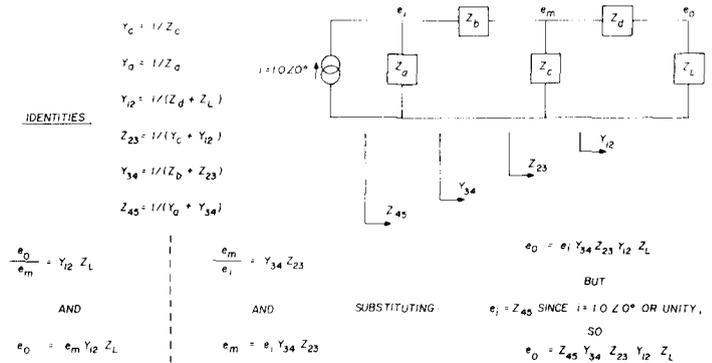


fig. 4. Five-branch ladder network, showing derivation of circuit quantities. A hand-held calculator is very useful in solving problems of this type.

form of Z_L is reached and the real and imaginary parts of Z_d are added. Go back to the beginning and start the conversion for Y_{12} ; the calculator's stack already has the entry so it is just a matter of storing the real part in memory and the imaginary part in the stack. Pause at the polar form of Y_{12} and write down the values. At the end of the second run add the precalculated Y_c parts to parts of Y_{12} and return to the beginning. Continue the repetition, writing down each numbered-subscript polar value, until the input branch has been reached.

Solution of e_o is made by multiplying all tabulated magnitudes and adding all tabulated angles. This is the same as the last e_o expression in **fig. 4** and polar multiplication rules are used. Network input impedance can be found by subtracting source admittance using rectangular form rules and converting.

Six-digit accuracy of precalculation and tabulation is more than sufficient for most purposes; angle tabulation can be rounded to three fractions using degrees, four with radians. If a mistake is made in stepping through the sequence, just begin in mid-

*Amateurs who are not familiar with networks are often confused by the numeric subscripts which are used. The designator Y_{12} , for example, refers to the admittance looking into sections 1 and 2 of the network; likewise, Z_{45} refers to the impedance looking into sections 4 and 5 of the network (see **fig. 4**). In filters, capacitors and inductors are often designated in the same manner — in terms of their relative positions within the filter network.

sequence by clearing registers and entering the last tabulated polar value; just make certain that magnitude and angle are positioned correctly.

The repetitive sequence or iteration is well suited to a programmable calculator. If it has a larger memory, the partial products of e_o can be accumulated automatically.

modifying a model with branches that jump adjacent nodes

Fig. 5 shows this condition and defeats the ladder configuration. Fig. 5 also shows how a model subsection can be transformed by the *delta-to-tee* method, yielding a result that fits the ladder. Transformation must be done with precalculated values.

A delta sub-section that is pure resistance requires transformation only once. Any other condition requires a transform at every solution frequency. The resulting tee values become the new precalculated values for solution iteration.

Similar transformations can be made for tee-to-delta and lattice networks. Most engineering handbooks contain the transform equations, usually given as impedances, but the equations work just as well with admittances. It is worthwhile to study the circuit to be modified and arrange the branches for the least amount of transformation.

Pi networks are good examples and published design data can be used as a starting point. Unfortunately, most designs assume only a resistive load while an actual load such as an antenna will vary considerably. The object of impedance matching is to make the real part of the matched load equal to the source, and reduce the imaginary part to zero.

Let's take the case of matching an antenna over a few frequencies with a pi network. The basic design data is available and the components can be modeled as in fig. 3. The approximate antenna impedance data is known either by measurement or from handbook data. Will the network components do the job?

A way to find out is to solve only for Z_{in} , omitting source admittance and susceptance of the first-branch network component (usually a variable capacitor). The rectangular form of Z_{in} is a bit better for solution.

Tabulate the results at each frequency and antenna impedance expected and examine the imaginary part sign. If the sign does *not* change, the input component can be reactive and the value can be calculated by the *opposite-sign* reactance. The imaginary part must go to zero when the component is included in the model. Value range variation can also be seen; make certain that this can be realized in practice.

An imaginary-part sign change means that another component value must change. The most common

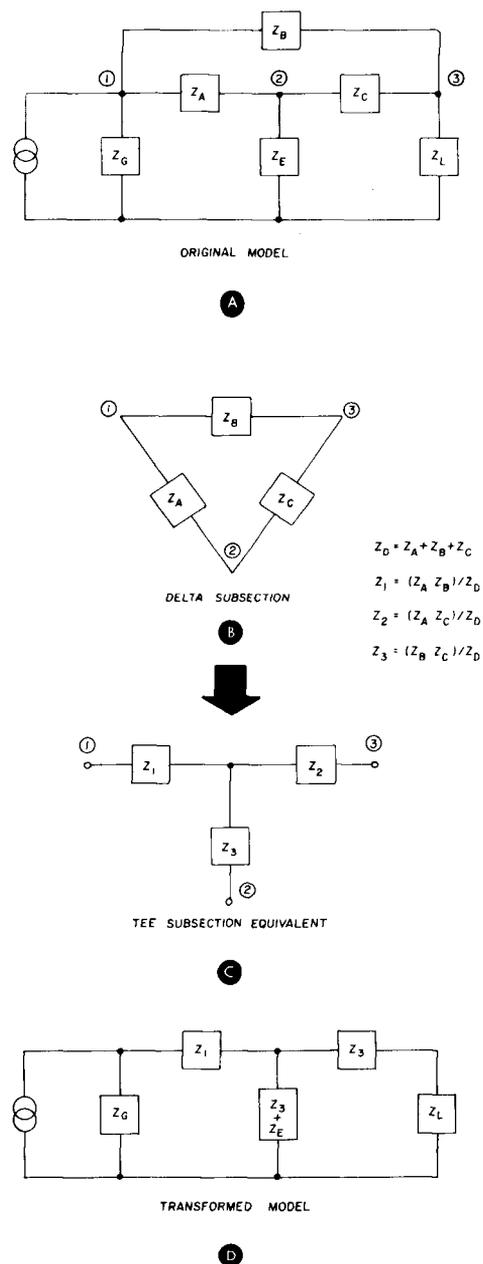


fig. 5. Model transformation. Here the delta subsection (consisting of Z_A , Z_B , and Z_C) is transformed into an equivalent tee section. The tee section is then added to Z_G , Z_L , and Z_0 to yield the transformed model.

pi network uses a variable capacitor at each end with a fixed series inductor. If this is the circuit, try varying the other capacitor, solving again and inspecting the signs.

The real part of Z_{in} should be reasonably close to the required resistive value for best power transfer. The difference depends on the type of source. A 20 to 30 per cent variation is probably good enough in most cases. If this part is not close, another component value must be changed. After a few changes you will be able to tell which way to change and you can zero in on the correct set of values. The best effi-

ciency occurs with source impedance equal to matched load impedance.

Other networks can be designed from the efficiency rule and reducing reactance to zero. Some careful study and algebra will result in a matching formula. Impedance or admittance — as a quantity — obeys algebraic rules. The only difference is that real and imaginary parts must be handled by the rules given.

circuits with more than one load

Suppose you have a circuit model like fig. 4 and there are two Z_d and two Z_L branches in separate paths. Solve Y_{12} for the second path and record it. Solve the first path as before except the second path's Y_{12} is also added to Y_c plus Y_{12} of the first path. Z_{23} is the total impedance of both paths.

The second path e_o is found from Z_{45} , Y_{34} , Z_{23} recorded in solving the first path and Y_{12} and Z_L of the second path. This can be extended to longer paths with different lengths provided that the common-node impedance value is the total impedance of all paths.

bilaterality

All illustrations have shown the source at left, load at right. This conforms to conventional left-to-right flow but doesn't mean the schematic must be interpreted this way. Many schematics are drawn differently, so take care in forming the model — properly locate the source and load.

Q equivalents

Every coil and capacitor is lossy. To properly analyze a filter this loss must be modeled as resistance or conductance in the proper branches. General values are X/Q for impedance and a series resistance, B/Q for admittance and a parallel conductance. Add losses in LC branches.

Some simplification is possible. Q is fairly constant over an octave of frequency. A fixed R or G value can be used for resonant circuits and filters. The fixed value would be obtained at the center frequency or cutoff frequency for highpass and lowpass filters.

other analysis methods

Most circuit theory texts have them. The inexperienced should be cautious since the math is high level, usually involved with matrices or transfer functions. A matrix is best solved on a computer. The other methods are more versatile, but not more accurate. The ladder form given here will fit a manual or programmable pocket calculator better. It will not solve all circuits, but most of them. Programs for the HP-25 will be given in a future article.

ham radio

the famous HAM KEYS

The keys that are easy
to put your fingers on!



JUST DIAL
1-800-325-3636
TOLL FREE



Model HK-1

- Dual-lever squeeze paddle
- Use with HK-5 or any electronic keyer
- Heavy base with non-slip rubber feet
- Paddles reversible for wide- or close-finger spacing

\$29⁹⁵



Model HK-2

- Same as HK-1, less base for incorporation in own keyer

\$19⁹⁵



Model HK-3

- Deluxe straight key
- Heavy base — no need to attach to desk
- Velvet smooth action


\$16⁹⁵

Model HK-3A

- Same as above less base

\$9.95

Navy type knob, only \$2.75

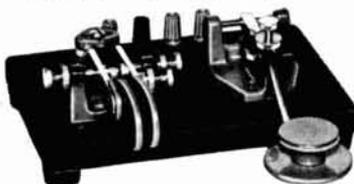

Model HK-4

- Combination of HK-1 and HK-3 on same base

\$44⁹⁵

- Base only with rubber feet

\$12.00

Terminals, red or black, \$.75 each



Model HK-5 Electronic Keyer

- Iambic Circuit for squeeze keying
- Self-completing dots and dashes
- Dot memory
- Battery operated with provision for external power

\$69⁹⁵

- Built-in side-tone monitor
- Speed, volume, tone and weight controls
- Grid block or direct keying
- For use with external paddle, such as HK-1

Same day shipment . . . PREPAID

We welcome the use of your



HAM RADIO CENTER, INC.

8340-42 Olive Blvd • P.O. Box 28271 • St. Louis, MO 63132

NOTICE: 73 MAGAZINE printed an untrue report in the June, 1977, issue regarding the KDK FM144. They are now printing a retraction regarding this untrue report. The FM144 does not need tuning to cover the full 5 MHz range.



NEW! FM144-10SXRII

All Solid State-PLL digital synthesized — No Crystals to buy! 5KHz steps — 144-149 MHz-LED digital readout PLUS MARS-CAP.*

- 5MHz Band Coverage — 1000 Channels (instead of the usual 2MHz to 4MHz — 400 to 800 Channels)
- Priority Channel
- Audio Output 4 Watts
- 15 Watts Output
- Unequaled Receiver Sensitivity and Selectivity — 15 POLE FILTER, MONOLITHIC CRYSTAL FILTER AND AUTOMATIC TUNED RECEIVER FRONT END — COMPARE!!
- Superb Engineering and Superior Commercial Avionics Grade Quality and Construction Second to None at ANY PRICE.

- **FREQUENCY RANGE:** Receive: 144.00 to 148.995 MHz, 5 KHz steps (1000 channels). Transmit 144.00 to 148.995 MHz, 5 KHz steps (1000 channels) + MARSCAP.*
- **FULL DIGITAL READOUT:** Six easy to read LED digits provide direct frequency readout assuring accurate and simple selection of operating frequency.
- **AIRCRAFT TYPE FREQUENCY SELECTOR:** Large and small coaxially mounted knobs select 100KHz and 10KHz steps respectively. Switches click-stopped with a home position facilitate frequency changing without need to view LED'S while driving and provides the sightless amateur with full Braille dial as standard equipment.
- **FULL AUTOMATIC TUNING OF RECEIVER FRONT END:** DC output of PLL fed to varactor diodes in all front end R-F tuned circuits provides full sensitivity and optimum intermodulation rejection over the entire band. **No other amateur unit at any price** has this feature which is found in only the most sophisticated and expensive aircraft and commercial transceivers.
- **TRUE FM:** Not phase modulation — for superb emphasized hi-fi audio quality second to none.
- **FULLY REGULATED INTEGRAL POWER SUPPLIES:** Operating volgate for all circuits, i.e., 12v, 9v and 5v have independently regulated supplies. 12v regulator effective in keeping engine alternator noises out and protects final transistor from overload.

- **MONITOR LAMPS:** 2 LED'S on front panel indicate (1) incoming signal-channel busy, and (2) un-lock condition of phase locked loop.
- **DUPLEX FREQUENCY OFFSET:** 600KHz plus or minus, 5KHz steps. Plus simplex, any frequency.
- **MODULAR COMMERCIAL GRADE CONSTRUCTION:** 6 unitized modules eliminate stray coupling and facilitate ease of maintenance.
- **ACCESSORY SOCKET:** Fully wired for touch-tone, phone patch, and other accessories.
- **RECEIVE:** .25 uv sensitivity. **15 pole filter** as well as monolithic crystal filter and **automatic tuned LC** circuits provide superior skirt selectivity.
- **AUDIO OUTPUT: 4 WATTS.** Built in speaker.
- **HIGH/LOW POWER OUTPUT:** 15 watts and 1 watt, switch selected. Low power may be adjusted anywhere between 1 watt and 15 watts, fully protected—short or open SWR.
- **PRIORITY CHANNEL:** Instant selection by front panel switch. Diode matrix may be owner re-programmed to any frequency (146.52 provided).
- **DUAL METER:** Provides "S" reading on receive and power out on transmit.
- **OTHER FEATURES:** Dynamic microphone, mobile mount, external speaker jack, and much, much more. Size: 2 1/8 x 6 1/2 x 7 1/2. All cords, plugs, fuses, mobile mount, microphone hanger, etc., included. Weight 5 lbs.



NEW! 6 METER FM50-10SXRII

Same specifications as above except transmit/receive: 51.00-53.995 MHz. 600 channels
Introductory Price \$389.00



SUMMER SPECIAL
FM144-10SXRII
\$389.00
VALUE \$599.00
Regulated AC/PS
Model FMPS-4R ... \$49.00

NEW!
TONE
ENCODER/
DECODER
SC 12A 12 CHANNELS DUAL TONE
Introductory Price \$119.00

Touch-Tone
Pad
MODEL FMTP-1
... \$59.00

Manufactured by one of the world's most distinguished Avionics manufacturers, Kyokuto Denshi Kaisha, Ltd.

First in the world with an all solid state 2 meter FM transceiver.

AMATEUR-WHOLESALE ELECTRONICS

8817 S.W. 129th Terrace, Miami, Florida 33176
Telephone (305) 233-3631 • Telex: 51-5628
U.S. DISTRIBUTOR

PLEASE ORDER FROM YOUR LOCAL
DEALER OR DIRECT IF UNAVAILABLE.

Regional Sales & Service Centers:
Northeast: Buzzards Bay Electronics
Buzzards Bay, Mass.
East: Sanford Communications, Inc.
Colonia, N.J.
West: Consumer Communications, Inc.
Seattle, Wash.





NEW SIGMA XR-3000 LINEAR AMPLIFIER

INTRODUCTORY PRICE **\$789**



2 DAY AIR SHIPMENT ANYWHERE IN U.S. \$35. ALASKA AND HAWAII SLIGHTLY HIGHER

- FULL BAND COVERAGE 160-10 METERS INCLUDING MARS.
- 2000 WATTS P.E.P. SSB INPUT. 1000 WATTS INPUT CONTINUOUS DUTY, CW, RTTY & SSTV.
- TWO EIMAC 3-500Z CONSERVATIVELY RATED FINALS
- ALL MAJOR HV AND OTHER CIRCUIT COMPONENTS MOUNTED ON SINGLE G-10 GLASS PLUG IN BOARD. HAVE A SERVICE PROBLEM? (VERY UNLIKELY) JUST UNPLUG BOARD AND SEND TO US.
- HEAVY DUTY COMMERCIAL GRADE QUALITY AND CONSTRUCTION SECOND TO NO OTHER UNIT AT ANY PRICE!
- WEIGHT: 90 lbs. SIZE: 9 1/2" (h) x 16" (w) x 15 1/4" (d).

FEATURES

CUSTOM COMPUTER GRADE COMMERCIAL COMPONENTS, CAPACITORS, AND TUBE SOCKETS MANUFACTURED ESPECIALLY FOR HIGH POWER USE—HEAVY DUTY 10KW SILVER PLATED CERAMIC BAND SWITCHES • SILVER PLATED COPPER TUBING TANK COIL • HUGH 4" EASY TO READ METERS—MEASURE PLATE CURRENT, HIGH VOLTAGE, GRID CURRENT, AND RELATIVE RF OUTPUT • CONTINUOUS DUTY POWER SUPPLY BUILT IN • STATE OF THE ART ZENER DIODE STANDBY AND OPERATING BIAS PROVIDES REDUCED IDLING CURRENT AND GREATER OUTPUT EFFICIENCY • BUILT IN HUM FREE DC HEAVY DUTY ANTENNA CHANGE-OVER RELAYS • AC INPUT 110V OR 220V AC, 50-60Hz • TUNED INPUT CIRCUITS • ALC-REAR PANEL CONNECTIONS FOR ALC OUTPUT TO EXCITER AND FOR RELAY CONTROL • DOUBLE INTERNAL SHIELDING OF ALL RF ENCLOSURES • HEAVY DUTY CHASSIS AND CABINET CONSTRUCTION AND MUCH, MUCH MORE.



SIGMA RF-2000 SWR & POWER METER
Introductory Price **\$29** Cal PWR Scales 200W-2000W
Freq Range 3.5 - 150 MHz Please do not confuse the RF2000 with similar appearing lower priced units - RF2000 is an individually calibrated professional quality instrument - Unequaled at many times the price Size 7" (w) x 2 1/2" (h) x 2 1/3" (d).



NEW AM/FM ANALYZER SIGMA AF-250L

INTRODUCTORY PRICE **\$199**
Deviation/Modulation Meter - FM: 0-20 KHz, AM: 0-100%. Size: 5 1/2" (h) x 10 1/4" (w) x 7 1/4" (d)
Weight 7 lbs. Frequency: 1.8MHz-520MHz



ALSO MODEL AF-251LW WITH BUILT IN 125 WATT CALIBRATED WATT METER & DUMMY LOAD PRICE **\$289**. PLEASE WRITE FOR COMPLETE INFORMATION.

NEW—CDR HAM ROTATORS—Reg. **\$159.95** **\$125**.

STANDARD NEW 2 METER FM TRANSCEIVERS Model SRC 146A SPECIAL SALE



SRC 146A \$314
4 Xtals: 34/94 and 94/94 NC
USA 2 Deluxe Base Charger \$40
PT3644 Leather Case \$10
AT 19 Rubber Ant and Whip \$6
NI Cads \$30
Reg \$400
Our Price **\$279**

NEW!!! Touch Tone pad completely wired and ready to plug in \$69.00



NEW! FMSC-2 SCANNER FOR KDK FM-144

14 CHANNEL PROGRAMMABLE INTRODUCTORY PRICE **\$109**



NEW! 7400 SCANNER

FOR KENWOOD TR-7400A
14 CHANNEL PROGRAMMABLE INTRODUCTORY PRICE **\$109**



FMSC-1 - **\$169**

TWO NEW SCANNERS!

FMSC-1 Scanner for KDK FM 144 and 7400 Scanner II for Trio-Kenwood TR-7400A

- Full scan 146 and 147 MHz consecutively or 1 MHz, or any MHz range • Scan rate: 1 MHz/2 seconds adjustable
- Controls: Scan/Hold, Latch/Delay, 600 KHz offset (off, up, down), program 1 MHz • Simple installation.



7400 Scanner II-**\$189**



ACCESSORIES FOR KDK FM 144

FMPS 4R	Regulated AC/PS	\$49
FMTP 1	Touch Tone Pad	\$59
FMTP 2	Touch Tone Pad with 10 Number Programmable Memory	\$99
FMCC 1	Microphone with Built in Touch Tone Pad	\$59
FMTD 1	Private Call Decoder for use with and Programmed by Any Touch Tone Pad	\$129
SC 12A	Audible Tone Encoder Decoder	\$119
FMSC 1	Scanner - Random Any Range	\$169
FMSC 2	Scanner - Programmable 14 Channels	\$109
MARS CAP	Option Kit - Any Frequency, Any Split	\$12
FMOF-1	Offset Option Kit - 2 Extra Positions, Crystals Required	\$19
FMOF 2	- 1 MHz Offset Option Kit (No Crystals To Buy)	\$19
FMTIE 1	Sub Audible Tone (100 Hz - Adjustable 67 203 Hz)	\$29
FMAT 1	1/2 Wave Portable Antenna for Hotel, Motel or Apartment	\$7.95
	Extra DC Cord & Plug	\$3.50
	ACC Socket 5 Pin Din Plug	\$1.50
	Owners Manual (Extra)	\$5.00
	Service Manual	\$2.00
	Mounting Bracket (Extra)	\$6.00



NEW - TEMPO 2020

A brilliant new SSB transceiver providing advanced engineering and unique operating features. Please write for information



YAESU FT 101E TRANSCEIVER'S

write for special deal.



NEW! AMCOMM

S 2 25 Two Meter Synthesized VHF-FM Transceiver. 25 watts output. 600 kHz and 1 MHz offsets built in. Please write for complete information and SPECIAL INTRODUCTORY PACKAGE PRICE.

ATLAS 210X-215X and 350-XL

Please write for special bonus and package offers.



The indispensable BIRD 43 THURLINE WATTMETER Authorized Bird Distributor Please write for special deal

ATLAS, COLLINS, DEN-TRON, CUSHCRAFT, BIRD, STANDARD, KLM, HYGAIN, KENWOOD, TEMPO, MINI-PRODUCTS, MIDLAND, ICOM, MARINE, EIMAC, VHF, AMCOMM, etc. Please write for quote.

Amateur-Wholesale Electronics

8817 S.W. 129th Terrace, Miami, Florida 33176

Please Note: We will be closed for annual vacation August 12-21. Prices subject to change without notice.

COURTEOUS PERSONAL SERVICE—SAME DAY SHIPMENT • TELEPHONE: (305) 233-3631 • TELEX 51-5628 • STORE HOURS: 10-5 MON.-FRI.

OUR CREW: S.I. GREGORY WA4KGU J.R. MAGGIO Mgr. S.E. GLICKMAN
Owner/Gen. Mgr. WB8CXL WB4HFJ



2 METER FM

and HF too ...
Summer Specials On
HAND HELDS



Standard
Wilson
Plus Antennas
All Other Accessories
In Stock!
Call or Write for
Erickson's Deal

- Ameco • ASP • Atlas
- Belden • Bird • CDE
- CES • Collins • Cushcraft
- Dentron • Drake • HAL
- Hy-Gain • Icom • KLM
- Kenwood • Larsen • MFJ
- Midland • Mosley • NPC
- Newtronics • Nye
- Regency • Shure • Swan
- Standard • TPL • Tempo
- Ten-Tec • Wilson • Yaesu



An Excellent Selection of Fine
Used Equipment Always in Stock

Hours: 9:30-9 Mon. & Thurs,
9:30-5:30 Tues, Wed. & Fri. 9-3 Sat.

E ERICKSON
COMMUNICATIONS
5935 N. Milwaukee Ave.
Chicago, IL 60646
(312) 631-5181

This is easy-
anyone can solder-
WITH
KESTER SOLDER

KESTER
SOLDER



Handymen! Hobbyists!
DO-IT-YOURSELFERS!

Let Kester Solder aid you in your home repairs or hobbies. For that household item that needs repairing — a radio, TV, model train, jewelry, appliances, minor electrical repairs, plumbing, etc. — Save money — repair it yourself. Soldering with Kester is a simple, inexpensive way to permanently join two metals.

When you Solder go "First Class" — use Kester Solder.

For valuable soldering information send self-addressed stamped envelope to Kester for a FREE Copy of "Soldering Simplified".



KESTER SOLDER
Litton 4201 WRIGHTWOOD AVENUE/CHICAGO, ILLINOIS 60639

ALUMA TOWERS

40 Ft.
Crank-Up
Ham Model T-140

60 Ft.
Ham Crank-Up
Model T-60-H

HIGHEST QUALITY

MADE IN ALUMINUM

- ★ TELESCOPING
(CRANK UP)
- ★ GUYED
- ★ TILT OVER MODELS

QUALITY MADE

Excellent for


**HAM
COMMUNICATIONS**

MANY MODELS MFG.

Towers to 100 feet. Specials
designed & made. See dealer
or send for free catalog.

ALUMA TOWER CO.
BOX 2806HR
VERO BEACH, FLA. 32960
PHONE (305) 567-3423

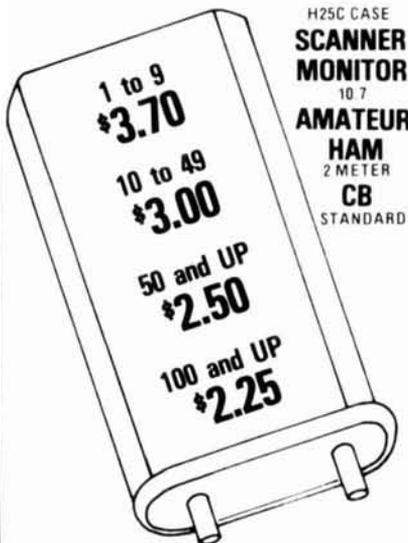**10's OF THOUSANDS
OF CRYSTALS
IN STOCK!**



H25C CASE
**SCANNER
MONITOR**
10 7
**AMATEUR
HAM**
2 METER
CB
STANDARD

Immediate delivery on most frequencies!
OTHERS ARE SPECIAL ORDER

CRYSTAL BANKING SERVICE
P.O. BOX 683
LYNNFIELD, MASSACHUSETTS
01940

NEW FROM HY-GAIN 2-METER BEAMS THAT LAST LONGER. WORK HARDER. AND COST LESS.

Introducing a whole new generation of Hy-Gain 2-Meter beams.


Completely redesigned for greater strength and corrosion resistance. So they last longer.

Newly engineered for greater performance and maximum efficiency. So they work harder, your transceiver works better.

And built better. So you pay less for the performance you want.

Our new 2-Meter beams give you the kind of performance you expect from the world's largest manufacturer of quality antennas. Yet, thanks to Hy-Gain technology, they weigh less, have lower wind loading and are UPS shippable.

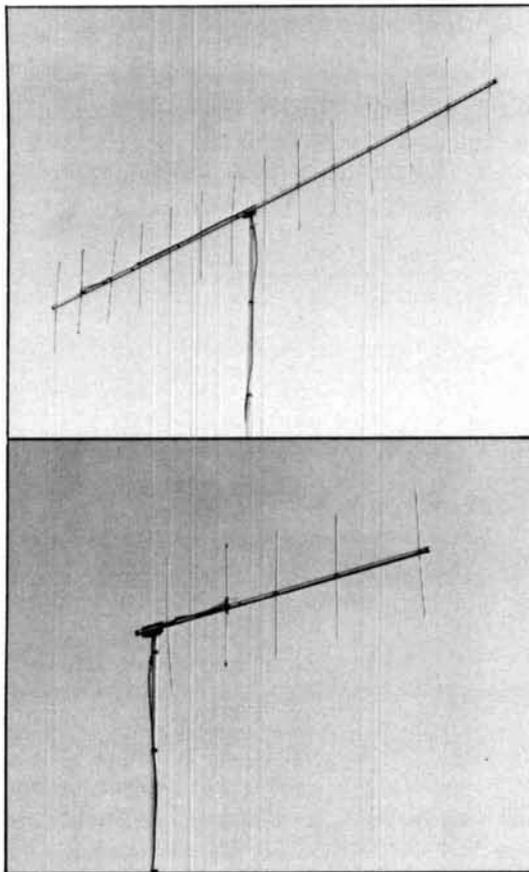They use an exclusive new element to boom mounting system that's mechanically stronger and electrically more efficient. All can be



vertically or horizontally polarized. And all are constructed of the finest aluminum and ZMI hardware.

Hy-Gain 214 14-element close spaced beam with extremely high forward gain and narrow beam width. **\$26.95**

Also available with 8-element optimum spacing, **Hy-Gain 208. \$19.95**

Hy-Gain 205 5-element optimum spaced end mount beam with high forward gain and broad frequency response. **\$16.95**

Also available with 3 elements, **Hy-Gain 203. \$12.95**

See the new generation of Hy-Gain 2-Meter beams at your amateur radio dealer. Or write Hy-Gain; 8601 Northeast Highway Six; Lincoln, NE 68505.

hy-gain

WE KEEP PEOPLE TALKING.

Hy-Gain reserves the right to change prices, designs and/or specifications at any time without notice.


SPECIFICATIONS	214	208	205	203
Mechanical				
Boom length	186"	148 3/4"	75"	43 1/2"
Longest element	39 1/2"	40 1/4"	39 5/8"	40 1/4"
Turning radius	95"	75 1/8"	73"	43 1/2"
Wind survival	80 mph	80 mph	80 mph	80 mph
Mast diameter	1 1/4"-1 5/8" O.D.			
Boom diameter	1 1/4" O.D.	1 1/4" O.D.	1 1/4" O.D.	1 1/4" O.D.
Wind load area	1.65 ft ² max.	1.26 ft ² max.	.740 ft ² max.	.496 ft ² max.
Net weight	5.5 lbs	4.1 lbs	2.9 lbs	2.2 lbs
Electrical				
Forward gain	13.0 dBd*	11.8 dBd*	9.1 dBd*	6.1 dBd*
Front-to-back ratio	20 dB	20 dB	20 dB	20 dB
Maximum SWR	2:1	2:1	2:1	2:1
Band width	2 MHz	2 MHz	4 MHz	4 MHz
Maximum power	250/500 PEP	250/500 PEP	250/500 PEP	250/500 PEP
Impedance w/balun	52 ohms	52 ohms	52 ohms	52 ohms
1/2 power beam width	35° vertical	43° vertical	60° vertical	95° vertical
	35° horizontal	36° horizontal	45° horizontal	60° horizontal
Stacking distance	82" min.	82" min.	82" min.	82" min.

*Hy-Gain antennas are gain rated against a standard dipole antenna (dBd) instead of a theoretical isotropic source (dBi). This is a more honest and realistic means of comparing forward gain.

ME-3 microminiature tone encoder

Compatible with all sub-audible tone systems such as: Private Line, Channel Guard, Quiet Channel, etc.

- Powered by 6-16vdc, unregulated
- Microminiature in size to fit inside all mobile units and most portable units
- Field replaceable, plug-in, frequency determining elements
- Excellent frequency accuracy and temperature stability
- Output level adjustment potentiometer
- Low distortion sinewave output
- Available in all EIA tone frequencies, 67.0 Hz-203.5 Hz
- Complete immunity to RF
- Reverse polarity protection built-in

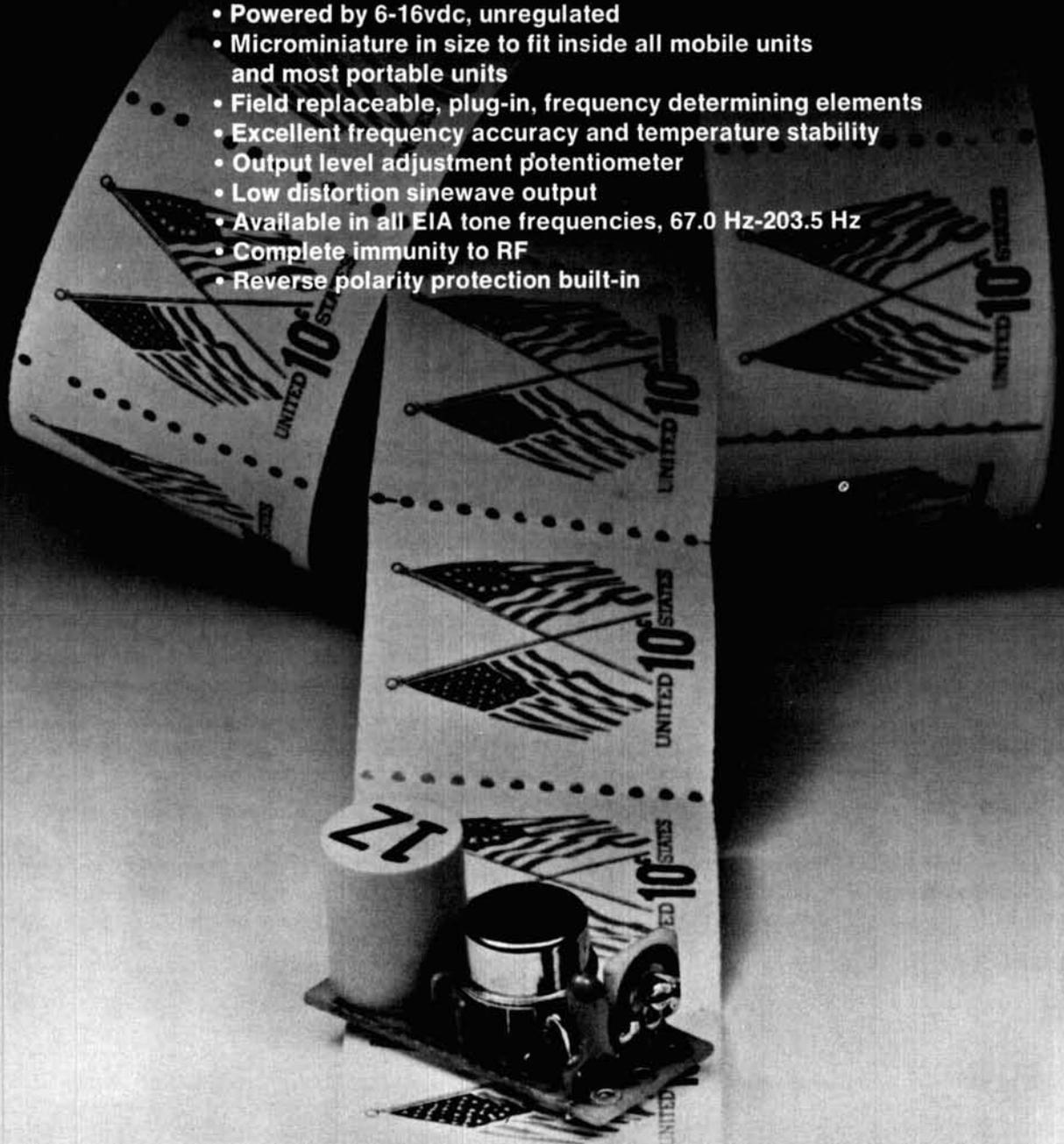

\$29.95 each

Wired and tested, complete with K-1 element

communications specialists

P. O. BOX 153
BREA, CALIFORNIA 92621
(714) 998-3021




K-1 FIELD REPLACEABLE,
PLUG-IN, FREQUENCY
DETERMINING ELEMENTS

\$3.00 each

for the experimenter!

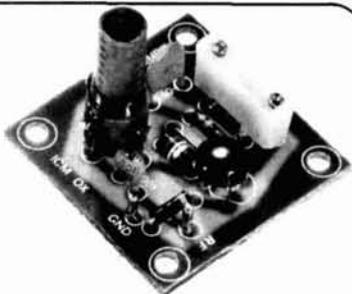INTERNATIONAL CRYSTALS & KITS
OSCILLATORS • RF MIXER • RF AMPLIFIER • POWER AMPLIFIER



OX OSCILLATOR

Crystal controlled transistor type. 3 to 20 MHz, OX-Lo, Cat. No. 035100. 20 to 60 MHz, OX-Hi, Cat. No. 035101
Specify when ordering.

\$3.95 ea.



MXX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 30 to 170 MHz range. Harmonics of the OX or OF-1 oscillator are used for injection in the 60 to 179 MHz range. 3 to 20 MHz, Lo Kit, Cat. No. 035105. 20 to 170 MHz, Hi Kit, Cat. No. 035106
Specify when ordering.


\$4.50 ea.



PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX or OF-1 oscillator. Outputs up to 200 mw, depending on frequency and voltage. Amplifier can be amplitude modulated. 3 to 30 MHz, Cat. No. 035104
Specify when ordering.


\$4.75 ea.

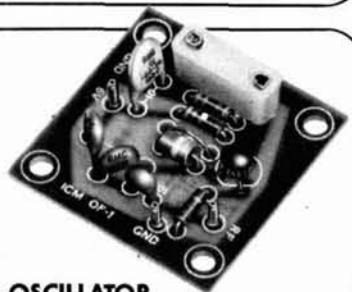

OF-1 OSCILLATOR

Resistor/capacitor circuit provides osc over a range of freq with the desired crystal. 2 to 22 MHz, OF-1 LO, Cat. No. 035108. 18 to 60 MHz, OF-1 HI, Cat. No. 035109
Specify when ordering.

\$3.25 ea.

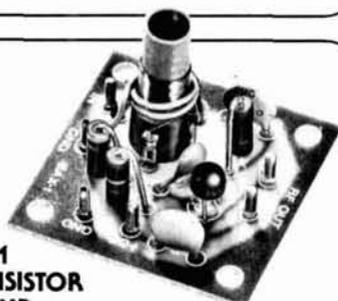

SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive the MXX-1 Mixer. Single tuned input and link output. 3 to 20 MHz, Lo Kit, Cat. No. 035102. 20 to 170 MHz, Hi Kit, Cat. No. 035103.
Specify when ordering.

\$4.50 ea.



DAX-1 BROADBAND AMP

General purpose amplifier which may be used as a tuned or untuned unit in RF and audic applications. 20 Hz to 150 MHz with 6 to 30 db gain. Cat No. 035107
Specify when ordering

\$4.75 ea.



.02% Calibration Tolerance
EXPERIMENTER CRYSTALS
(HC 6/U Holder)

Cat. No.	Specifications	
031080	3 to 20 MHz — for use in OX OSC Lo	\$4.95 ea.
	<i>Specify when ordering</i>	
031081	20 to 60 MHz — For use in OX OSC Hi	\$4.95 ea.
	<i>Specify when ordering</i>	
031300	3 to 20 MHz — For use in OF-1L OSC	\$4.25 ea.
	<i>Specify when ordering</i>	
031310	20 to 60 MHz — For use in OF-1H OSC	\$4.25 ea.
	<i>Specify when ordering.</i>	

Shipping and postage (inside U.S., Canada and Mexico only) will be prepaid by International. Prices quoted for U.S., Canada and Mexico orders only. Orders for shipment to other countries will be quoted on request. Address orders to:
M/S Dept., P.O. Box 32497,
Oklahoma City, Oklahoma 73132.




International Crystal Mfg. Co., Inc.
10 North Lee
Oklahoma City, Oklahoma 73102



NEW products

parabolic dish reflector kit

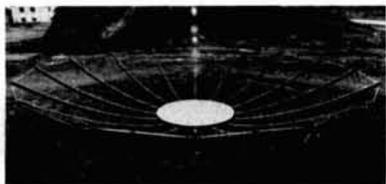

Moonbouncers, radio astronomers, TV DXers, and others who have needed a parabolic dish antenna at a reasonable price will like the *Paraframe* — a rigid, accurate, parabolic antenna framework kit which one person can easily assemble with ordinary hand tools. The *Paraframe* design permits the reflector to be fine-focused for peak performance, yet the weight is low, while strength is high.

Prestressed *Paraframes* are made of wood, and the ribs are furnished with two coats of premium-quality latex exterior sealer-primer, followed by two coats of premium quality latex exterior paint in a neutral gray. Other colors are available upon request.

The *Paraframe's* price is such that you can build a parabolic reflector for less than one-third the cost of a similar antenna of equivalent aperture. For example, the SD12 is a 12-foot (3.66-meter) design with a focal length/diameter (f/d) ratio of 0.5. Sixteen prestressed ribs provide sufficient rigidity for useful work at 2300 MHz in a 40-mph (65-kmh) wind. The ribs will accept 7/16 inch (11mm) staples for attaching the aluminum window-screen reflector material. Model SD16 has a sixteen foot (4.88 meter) diameter and 20 ribs; model SD20 has a twenty-foot (6.1 meter) diameter and 24 ribs.


A complete selection of expanded

and perforated aluminum covering material, together with low-loss coaxial cable suitable for uhf purposes, is available from the *Paraframe* kit supplier.

The model SD12 is priced at \$690 (shipping weight is 140 pounds or 64 kg); model SD16 is \$1120 (shipping weight is 230 pounds or 104 kg); and model SD20 is priced at \$1680 (shipping weight 400 pounds or 181 kg). Shipping cost will be approximately \$25 per cwt (45kg), maximum, anywhere in the continental United States. Terms are 50% of the purchase price with the order, the balance COD. Illinois residents are asked to include 5% sales tax.

For a complete description and illustrated brochure, write to James K. Vines, 611 Farmview Road, Park Forest South, Illinois 60466, or call (312) 534-0889 after 7 PM CDT.

rf hybrid amplifiers

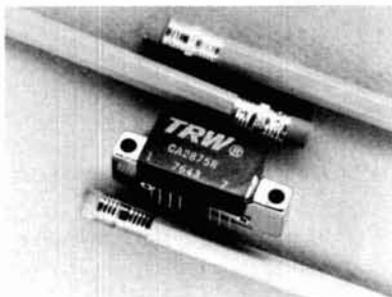

TRW RF Semiconductors has introduced an rf-hybrid gain block which will meet or exceed the most demanding requirements of i-f amplification in advanced microwave radio relay system applications.

The amplifier, designated CA2875/2875R, has a noise figure of

typically 4 dB and a third-order intercept of +42 dBm. Requiring a 15 to 24 volt power supply, the CA2875 is suitable for positive power supply polarity while the CA2875R will accommodate a negative supply polarity.

Other parameters of the hybrid amplifier include a return loss of greater than 30 dB at both the input and output ports, phase linearity from 30 to 110 MHz and wide dynamic range. These i-f gain/blocks have a center frequency of 70 MHz as well as a nominal gain of 17.5 dB and an operating temperature range of -40°C to $+100^{\circ}\text{C}$.

In quantities of 100 pieces, the CA2875/2875R is priced at \$31.50. For more information contact Warren Gould at (213) 679-4561 or TRW RF Semiconductors, 14520 Aviation Boulevard, Lawndale, California.

equipment directory


Have you ever searched through a pile of magazines, a loose-leaf collection of product releases, or a collection of dog-eared catalogs looking for a particular antenna, the specs on a new transceiver, or the nearest distributor-dealer for a certain brand of amateur equipment, only to give up in frustration?

Well, you don't have to repeat that futile exercise this year. The new 1977 *Amateur Radio Equipment Directory*, published by Kengore Corporation, got it all together just for you. Here is a comprehensive catalog of amateur equipment, complete with the names and addresses of manufacturers and distributors, together with product photographs, specifications, and prices, conveniently and

attractively bound between soft covers for your reference library.

Not every last item made by every manufacturer is listed, nor do the prices reflect recent price increases, but the catalog lists telephone numbers where you can get the latest, correct information. In spite of these minor (and expected) shortcomings, you'll have to look a long time before finding anything nearly as useful or informative. For your copy, send \$2.95 to Kengore Corporation, 9 James Avenue, Kendall Park, New Jersey 08824.

70-watt two-meter amplifier

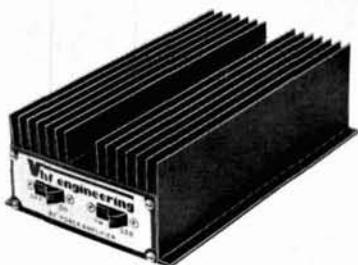

A new 70-watt, four-mode, two-meter amplifier has been introduced by VHF Engineering. This new amplifier, the Blue Line BLC 10/70, is designed to be used with the popular 10-watt fm transceivers and multi-mode transceivers in the 5-15 watt class; it will deliver 70 watts output in both the class C or linear mode. An additional model, the Blue Line BLC 2/70, offers the same features as the BLC 10/70 but will operate with transceivers or transmitters in the 1 or 2 watt class.

The VHF Engineering Blue Line series of amplifiers have been designed for reliability and long life and feature unique broadband, strip-line designs which require no tuning or adjustment during their lifetime. Automatic sensing and relay switching are provided to automatically switch the amplifier into the circuit when drive is applied in the class C (fm) or linear (ssb) modes. The amplifiers offer high efficiency and introduce a receive insertion loss of less than 1 dB. They are designed for

Rugged Giants Tri-Ex Sky Needle Towers Give your antennas a big lift!

Regular and
heavy duty
towers

This advanced state-of-the-art "Sky Needle" is fast earning its own special place of honor in the ham-communications field. Tri-Ex takes great pride in being the developer and first to build this crank-up, freestanding tubular tower for the amateur. Uniquely eye-pleasing, the slim and graceful "Sky Needle" is a symbol of pride to its owner as well as proof positive that he has the very best in towers. Tri-Ex offers immediate delivery. Act now! Write for your free brochure, today.

* Three Hy-Gain 10, 15, 20M long Johns.

** Log-periodic antenna for MARS use 13 to 30 MHz.

MODEL	HEIGHT	
	EXTENDED	NESTED
TM-240	40'	22'
TM-358	58'	22½'
TM-370/370HD	70'	27'
TM-490	90'	28'
TM-5100R	100'	29'



Tri-Ex TOWER CORPORATION

7182 RASMUSSEN AVE., VISALIA, CALIF. 93277

the word's out your ears tell you there's a difference with Kūlrod®



Just listen on VHF or UHF. Before long you'll discover that the guy with the full quieting signal, the readable signal, the one that gets through best usually says: "... and I'm using a Larsen Kūlrod Antenna."

This is the antenna designed, built and ruggedly tested in the commercial two-way field. It's the fastest growing make in this toughest of proving grounds. Now available for all Amateur frequencies in 5 different easy-on permanent mounts and all popular temporary types.

Make your antenna a Larsen Kūlrod and you'll have that signal difference too. Also good looks, rugged dependability and lowest SWR for additional pluses.

FREE: Complete details on all Kūlrod Amateur Antennas. We'll send this catalog along with names of nearest stocking dealers so you can get the full quieting "difference" signal.

* Kūlrod is a registered trademark of Larsen Electronics



Larsen Antennas

11611 N.E. 50th Ave. • P.O. Box 1686 • Vancouver, WA 98663 • Phone: 206/573-2722
In Canada write to: Canadian Larsen Electronics, Ltd.
1340 Clark Drive • Vancouver, B.C. V5L 3K9 • Phone: 604/254-4936

12-14 Vdc operation in base station or mobile service.

The BLC 10/70 sells for \$139.95 and the BLC 2/70 sells for \$159.95. These new four-mode amplifiers are available from dealers nationwide or from VHF Engineering, 320 Water Street, Binghamton, New York 13902, as wired and tested units.

new antennas from cubic corporation



A series of new amateur radio antennas, including four beam, two mobile, and one trap vertical model, are available now from Swan Electronics, a subsidiary of Cubic Corporation. The fixed antennas include the TB-4HA, a triband beam for \$259.95, featuring four working elements on 10, 15, and 20 meters; the 24-foot boom permits optimum spacing for maximum forward gain and front-to-back ratio.

Also available are the TB-3HA, a triband beam for \$199.95 which features three working elements on 10, 15, and 20 meters with a 16-foot boom; and the TB-2A, a triband beam for \$129.95 which features two working elements on 10, 15, and 20 meters. The MB-40H, a new heavy-duty two-element, 40-meter beam is priced at \$199.95, and features two working elements on a 15.75-foot steel boom. All Swan beam antennas are rated for 2000 watts PEP and are designed for a vswr of 1.5:1 or better at resonance.

The deluxe mobile models include a five-band mobile 45 antenna which features all band manual switching

for 10, 15, 20, 40 and 75 meters, a *High-Q* tapped coil, eight positive stop manual positions with gold-plated contacts, featuring a base section, mobile coil and 6-foot whip top section. It is power rated at 2000 watts PEP; cost is \$119.95.

The new Swan 742 tri-band antenna, priced at \$109.95, which, once adjusted to desired operating frequency for 20, 40, and 75 meters, requires no further adjustment. It is power rated at 500 watts PEP.

The Golden Swan Trap Vertical antenna, Model 1040V, an omnidirectional, low radiation angle unit designed for 52 ohm coaxial feedline is priced at \$122.95. Power rated at 2000 watts PEP, it measures 21 feet high and covers 20, 15, 20, and 40 meters. A 75-meter add-on kit is available for \$39.95.

Accessories include a *Kwik-on* connector for easy installation and removal of the mobile antenna for \$7.95; an MMBX mobile impedance in-line, low loss match box, \$23.95; and WM 3000 in-line peak reading wattmeter for \$79.95.

For further information about products and prices, contact Swan Electronics, 305 Airport Road, Oceanside, California 92054.

10-500 kHz vlf converter



Palomar Engineers has introduced a new vlf converter which converts signals in the 10-500 kHz vlf band to the amateur 80-meter band so they can be heard on an ordinary short-wave receiver. The converter provides reception of the 1750-meter band at 160-190 kHz where transmitters of one-watt power can be operated without FCC license. It also covers the navigation radio-beacon

INTRODUCES THE VERSATILE NEW

HR-312

- More Channels...at the flip of a switch**
 Unlock the unique mode switch and 12 channels become 144
- More Sensitivity, Less Interference.**
 .25 μ V Sensitivity plus 75 db adjacent channel selectivity and 70 db image rejection
- More Power Out**
 35 watts nominal with a minimum of 30 watts across the band

... for a lot less

\$269⁰⁰

Amateur Net

© 1976 **Regency ELECTRONICS, INC.** 7707 Records Street
Indianapolis, Indiana 46226

THE FM LEADER

2 METER	220 MHz
6 METER	440 MHz

ALL MODE VHF amplifier

130 WATTS ☆ 143-149 MHz
**Designed for Base Station
and Repeater Operation**



- ☆ AM - FM - CW - SSB
- ☆ Continuous Duty
- ☆ + 13V Accessory Socket
- ☆ 115/230V Operation
- ☆ T/R Switch
- ☆ Metered
- ☆ Fully Protected

1W input, 70W output, Model V71 - \$329
15W input, 70W output, Model V70 - \$298
25W input, 130W output, Model V130 - \$389



RF POWER LABS, INC.

11013-118th Place N.E. • Kirkland, Washington 98033
Telephone: (206) 822-1251 • TELEX No. 32-1042

band, standard frequency broadcasts, ship-to-shore communications, long-range navy transmitters, and the European low-frequency broadcast band.

The Palomar converter is simple to use and has no tuning adjustments. Tuning of vlf signals is done by the associated receiver which picks up 10-kHz signals at 3510 kHz, 100-kHz signals at 3600 kHz, and 500-kHz signals at 4000 kHz. The converter features crystal control for accurate frequency conversion, a low noise rf amplifier for high sensitivity, and a multi-pole filter to reject broadcast and shortwave interference. Price is \$55.00 postpaid in the United States and Canada. For more information write to Palomar Engineers, Post Office Box 455, Escondido, California 92025.

co-resident 8080 editor/assembler

Tychon has announced its co-resident editor/assembler (TEA) for 8080 systems. Requiring only 5k of memory (R/W or PROM) it is completely I/O independent and relies upon its own I/O software or the I/O routines already available in a user's system. The Tychon Editor/Assembler accepts both octal and hexadecimal values throughout the program and the program listings may be in either octal or hexadecimal form. The switch between octal and hex is made at any time using keyboard commands. The TEA package is the only editor/assembler available which allows the user to easily change the numbering system used. The editor/assembler is relocatable using a special relocater within the program which will place TEA anywhere in the 8080's memory space. The program is available in 1702A or 2708 PROMs and on paper tape. Listings are also available. Prices start at \$35 for a paper tape version plus the User's Manual. For further information contact Tychon, Inc., Blacksburg, Virginia 24060.

PARAFRAME

PARABOLIC ANTENNA FRAMEWORKS

FOR ...

- EME TV DXing
- Radio Astronomy
- Experimenting
- Student projects

Apertures available —
12', 16', 20' TBA: 24'

With PARAFRAME you can build a complete 20' parabolic antenna for \$1300. With interchangeable feeds you can have several antennas for the price of one.

JAMES K. VINES

611 Farmview Rd.
Park Forest South, IL
60466
(312) 534-0889
after 7 PM CDT

test for resonant resistance with an omega-t antenna noise bridge



The Omega-t Noise Bridge is an inexpensive and flexible testing device that can effectively measure antenna resonant frequency and impedance. This unique piece of test equipment does the work of more expensive devices by using an existing receiver for a bridge detector. There is no longer a need for power loss because of impedance mismatch. Get more details or order now!

Model TE7-01 for 1-100 MHz Range \$29.95
Model TE7-02 for 1-300 MHz Range \$39.95

ELECTROSPACE SYSTEMS, INC.

320 TERRACE VILLAGE
RICHARDSON, TEXAS 75080
TELEPHONE (214) 231-9303

Sold at Amateur Radio Dealers
or Direct from Electrospace Systems, Inc.

GET TO THE TOP FAST!



NOW YOU CAN CHANGE, ADJUST OR JUST PLAIN WORK ON YOUR ANTENNA AND NEVER LEAVE THE GROUND!

Rohn manufactures towers that are designed and engineered to do specific jobs and that is why we have the FOLD-OVER TOWER... designed for the amateur. When you need to "get at" your antenna just turn the handle and there it is. Rohn "fold-over" towers offer unbeatable safety. These towers let you work completely on the ground for antenna and rotator installation and servicing. This eliminates the hazard of climbing the tower and trying to work at heights that could mean serious injury in a fall. So use the tower that reduces the risks of physical danger to an absolute minimum... the Rohn "fold-over"!


Like other Rohn big communication towers, they're hot dip galvanized after fabrication to provide a maintenance free, long lived and attractive installation. Rohn towers are known and used throughout the world... for almost a quarter century... in most every type of operation. You'll be in good company. Why not check with your distributor today?

Do not attempt to raise antenna or antenna support near power lines— You can be KILLED.

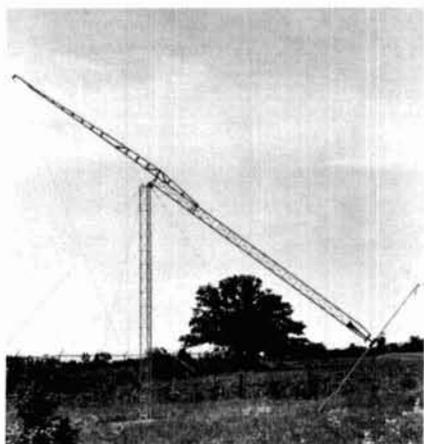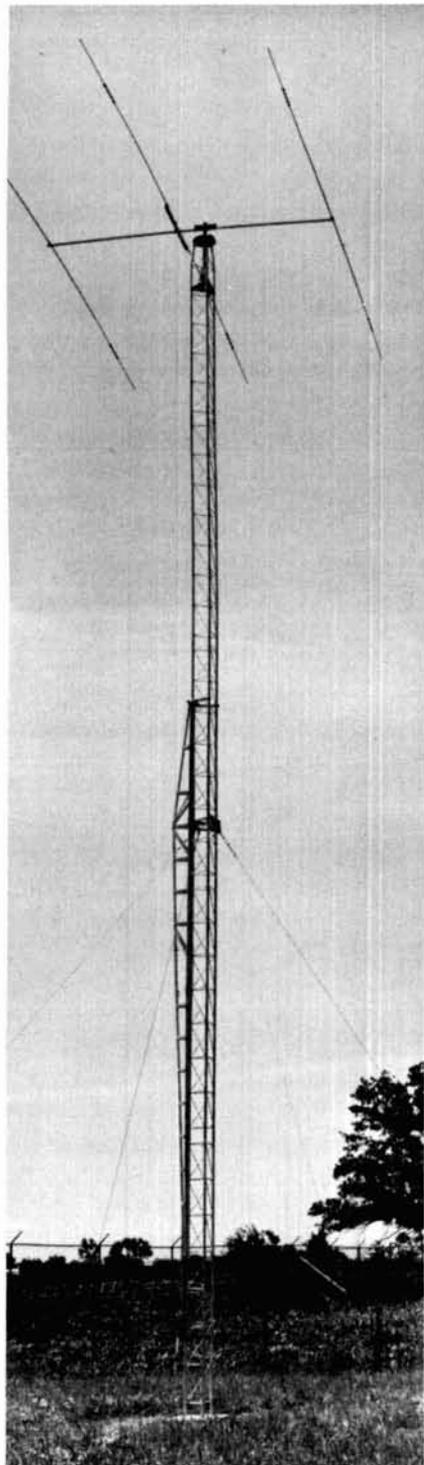Unarco-Rohn
Division of Unarco Industries, Inc.
P.O. Box 2000, Peoria, Illinois 61601



ADVA

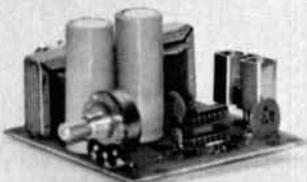

KIT \$11⁹⁵

ASSEMBLED \$17.95
ADD \$1.25 FOR
POSTAGE/HANDLING

FREE

IC or FET's WITH
\$5 & \$10 ORDERS.
DATA SHEETS
WITH MANY ITEMS.

VARIABLE POWER SUPPLY

- Continuously Variable from 2V to over 15V
- Short-Circuit Proof
- Typical Regulation of 0.1%
- Electronic Current Limiting at 300mA
- Very Low Output Ripple
- Fiberglass PC Board Mounts All Components
- Assemble in about One Hour
- Makes a Great Bench or Lab Power Supply
- Includes All Components except Case and Meters

OTHER ADVA KITS:

LOGIC PROBE KIT—Use with CMOS, TTL, DTL, RTL, HTL, HNIL and most MOS IC's. Built in protection against polarity reversal and overvoltage. Draws only a few mA from circuit under test. Dual LED readout. Complete kit includes case and clip leads. **ONLY \$7.95**

FIXED REGULATED POWER SUPPLY KITS—Short-circuit proof, with thermal current limiting. Compact size and typical regulation of 0.5% make these ideal for most electronic projects. Available for 5V @ 500mA, 6V @ 500mA, 9V @ 500mA, 12V @ 400mA, 15V @ 300mA. Specify voltage when ordering. **\$9.95 ea.**

These easy-to-assemble kits include all components, complete detailed instructions and plated fiberglass PC boards. Power supply kits do not include case or meters. Add \$1.25 per kit for postage and handling.

MAIL NOW! FREE DATA SHEETS supplied with many items from this ad. **FREE ON REQUEST**—741 Op Amp with every order of \$5 or more—749 Dual Op Amp or two 100 FET's with every order of \$10 or more, postmarked prior to 3/31/77. One free item per order. **ORDER TODAY!** All items subject to prior sale and prices subject to change without notice. All items are new surplus parts—100% functionally tested.

WRITE FOR FREE CATALOG #76 offering over 350 semiconductors carried in stock. Send 13¢ stamp.

TERMS: Send check or money order (U.S. funds) with order. We pay 1st Class postage to U.S., Canada and Mexico (except on kits). \$1.00 handling charge on orders under \$10. Calif. residents add 6% sales tax. Foreign orders add postage. COD orders—add \$1.00 service charge.

MORE SPECIALS:

RC41950N -15V @ 50mA VOLTAGE REGULATOR IC. Very easy to use. Makes a neat Highly Regulated -15V Supply for Op AMP's, etc. Requires only unregulated DC (18-30V) and 2 bypass capacitors. With Data Sheet and Schematics. 8-pin mDIP. **\$1.25**

LM741 FREE COMPENSATED OP AMP. μ A741, MC1741, etc. mDIP 5/S1

MC1458 DUAL 741 OP AMP mDIP 3/S1

RC4558 DUAL 741 OP AMP mDIP 3/S1

2N3904 NPN TRANSISTOR AMPLIFIER/SWITCH to 50 mA β 100 6/S1

ZENERS—Specify Voltage 3.3, 3.9, 4.3, 5.1, 6.8, 8.2, 9.1, 10, 12, 15, 16, 18, 20, 22, 24, 27, or 33V (+10%) 1 Watt 3/S1/100

- MONEY-BACK GUARANTEE
- ALL TESTED AND GUARANTEED

ADVA

ELECTRONICS
BOX 4181 O, WOODSIDE, CA 94062
Tel. (415) 851-0455

DIODES & RECTIFIERS	TRANSISTORS	TRANSISTORS	TRANSISTORS	LINEAR IC's
1N456 to 6/S1	2N706 80 24	2N4001 3/S1	2N6138 2/S1	LM3008 5 1/15
1N458 6/S1	2N718 24	2N4002 50 75	2N6460 2/S1	LM3007 1 1/75
1N459 6/S1	2N720 48	2N4003 3/S1	CP643 54 00	LM3001 6 1/75
1N460 6/S1	2N722 30	2N4004 3/S1	CP650* 56 00	LM3001 12 1/75
1N461 6/S1	2N723 24	2N4005 3/S1	CP651 56 00	LM3001 24 1/75
1N462 6/S1	2N724 24	2N4006 3/S1	1E100 4/S1	LM3001 24 1/75
1N463 6/S1	2N725 24	2N4007 3/S1	1E101 3/S1	LM3278* .55
1N464 6/S1	2N726 24	2N4008 3/S1	1E102 3/S1	LM3279 2.50
1N465 6/S1	2N727 24	2N4009 3/S1	1E103 3/S1	LM3280 1.20
1N466 6/S1	2N728 24	2N4010 3/S1	1E104 3/S1	NE555V* 2/S1
1N467 6/S1	2N729 24	2N4011 3/S1	MPF102 100 100	NE556A 50.90
1N468 6/S1	2N730 24	2N4012 3/S1	MPF112 3/S1	LM3008 29
1N469 6/S1	2N731 24	2N4013 3/S1	MPF109 3/S1	LM3009 29
1N470 6/S1	2N732 24	2N4014 3/S1	SE1001 4/S1	LM723H 2/S1
1N471 6/S1	2N733 24	2N4015 3/S1	SE1002 4/S1	LM722N* 3/S1
1N472 6/S1	2N734 24	2N4016 3/S1	SE1003 4/S1	LM733H 3/S1
1N473 6/S1	2N735 24	2N4017 3/S1	SE1004 4/S1	LM741CN 3/S1
1N474 6/S1	2N736 24	2N4018 3/S1	SE1005 4/S1	LM741CN14 34
1N475 6/S1	2N737 24	2N4019 3/S1	SE1006 4/S1	LM741CN 34
1N476 6/S1	2N738 24	2N4020 3/S1	SE1007 4/S1	78C5 DIP 35
1N477 6/S1	2N739 24	2N4021 3/S1	SE1008 4/S1	78C5 DIP 1.00
1N478 6/S1	2N740 24	2N4022 3/S1	SE1009 4/S1	844CP mDIP .90
1N479 6/S1	2N741 24	2N4023 3/S1	SE1010 4/S1	LM338 1.15
1N480 6/S1	2N742 24	2N4024 3/S1	SE1011 4/S1	LM1458N* 3/S1
1N481 6/S1	2N743 24	2N4025 3/S1	SE1012 4/S1	LM2111N \$1.40
1N482 6/S1	2N744 24	2N4026 3/S1	SE1013 4/S1	XC2556CP 1.55
1N483 6/S1	2N745 24	2N4027 3/S1	SE1014 4/S1	27400E 1.85
1N484 6/S1	2N746 24	2N4028 3/S1	SE1015 4/S1	CA3028A 1.75
1N485 6/S1	2N747 24	2N4029 3/S1	SE1016 4/S1	CA3046 .84
1N486 6/S1	2N748 24	2N4030 3/S1	SE1017 4/S1	LM3075M 1.45
1N487 6/S1	2N749 24	2N4031 3/S1	SE1018 4/S1	CA3086* .55
1N488 6/S1	2N750 24	2N4032 3/S1	SE1019 4/S1	LM3900N .55
1N489 6/S1	2N751 24	2N4033 3/S1	SE1020 4/S1	RC4194D 1.50
1N490 6/S1	2N752 24	2N4034 3/S1	SE1021 4/S1	RC4194E* 2.50
1N491 6/S1	2N753 24	2N4035 3/S1	SE1022 4/S1	RC41950N* 1.25
1N492 6/S1	2N754 24	2N4036 3/S1	SE1023 4/S1	RC4195T* 2.25
1N493 6/S1	2N755 24	2N4037 3/S1	SE1024 4/S1	LM2420CN 2.00
1N494 6/S1	2N756 24	2N4038 3/S1	SE1025 4/S1	RC4558DN .55
1N495 6/S1	2N757 24	2N4039 3/S1	SE1026 4/S1	LM3090 2.85
1N496 6/S1	2N758 24	2N4040 3/S1	SE1027 4/S1	LM3090 2.85
1N497 6/S1	2N759 24	2N4041 3/S1	SE1028 4/S1	LM3090 2.85
1N582 6/S1	2N844 24	2N4126 3/S1	SE1113 4/S1	LM3090 2.85

Proposed bands for tomorrow?

13950-14400 kHz

160-190 kHz

20700-21200 kHz

6950-7300 kHz

1750-1900 kHz



Drake FS-4 Solid State Synthesizer shown with Drake R-4C, MS-4 and T-4XC

Drake is ready for 1979 TODAY!

- **NEW and EXPANDED** amateur bands will be proposed at the 1979 World Administrative Radio Conference!
- If you have the Drake 4-Line, you are ready NOW for any of these hf frequencies by using either the Drake FS-4 solid state general coverage synthesizer or Drake selectable range crystals.
- Drake 4-Line equipment is designed for you to use — without fear of obsolescence — year after year after year.

Drake 4-Line gear is already designed to give you coverage of any of the proposed new amateur band expansions in the hf range.

You can have them *all*, and everything in between, with the Drake FS-4 solid state synthesizer. It's ready to go with the R-4 series/T-4X series without modification. You can transceive as is or run split frequency with the Drake 1524 adapter.

You can adapt the Drake SPR-4 solid state receiver to use with the FS-4 by ordering interface kit 1523. The SPR-4 receiver will even cover the proposed new 1600 meter band at 160 kHz. If you do not wish to use the FS-4, you may select any of the specific new ranges with front panel selectable range crystals. There are 15 extra ranges on the R-4C, and four on the T-4XC.

Also consider the Drake L-4B linear amplifier — full power 2 kW PEP, ssb and 1000 W-dc cw, full rated for RTTY, offering full operator convenience with front panel by-pass switch and built-in precision high power wattmeter.

R. L. DRAKE COMPANY



Will your gear still score in 1979?

540 Richard Street, Miamisburg, Ohio 45342 • Phone (513) 866-2421 • Telex 288-017

Western Sales and Service Center, 2020 Western Street, Las Vegas, Nevada 89102 • 702/382-9470

a NEW antenna principle

PROVEN IN EXACTING TESTS AND MANY YEARS ON THE AIR AT W0MBH — K0AST — K8VRM



THE *Little* GIANT BEAM ANTENNA

A COMPLETELY NEW ANTENNA

only 27 inches high
by 22 inches wide

Here is an ultra compact beam antenna which can be tuned to any frequency between 7.0 and 14.5 MHz. Weighing only 18 lbs. this antenna may not outperform a full sized beam but it sure will give you your share of DX and stateside contacts. Will handle 1 KW over a 100 kHz bandwidth.

- Fully weather proof
- Mounts easily on TV masting
- Figure 8 pattern
- Hi-Q, attenuates harmonics
- Comes assembled & tested

LITTLE GIANT MODEL 100X1000-40

Other models available for 10, 15 & 20 meters

KITS 10-40 \$94.50

\$149.50


Add \$3 trans.

Little Giant Antenna Labs, Box 245, Vaughnsville, Ohio 45893

Subsidiary "Apollo Products" Village-Twig Co.

419-646-3495

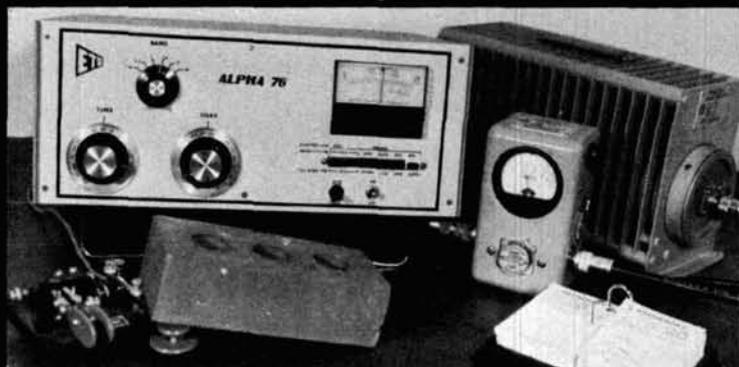We Don't Claim That Your ALPHA Linear Will Run A Kilowatt Key-Down FOREVER . . .



But We Don't Put A Time Limit On It, Either.

YOU'LL PROBABLY NEVER SET A BRICK ON YOUR KEY FOR 26,000 MINUTES. BUT WE DID IT TO ILLUSTRATE WHAT ETO'S NO TIME LIMIT [NTL] CONTINUOUS DUTY RATINGS REALLY MEAN TO EVERY ALPHA AMPLIFIER OWNER.

April 7th: A standard ALPHA 76 was taken from production, loaded up to a full 1000 watts key-down dc input, and left operating with a brick on the key.

April 25th: The '76 was still operating completely normally, delivering about 675 watts of continuous rf carrier output into a very hot dummy load — after 18 days — 435 hours — some 26,000 consecutive minutes key-down at a full kilowatt. You may have seen the same unit running key-down all day long the following week-end at the Dayton Hamvention. It's still as good as new — a fact which will surprise no one who knows how all ALPHA's are built. You'd expect no less.

The point is, every ALPHA linear amplifier — including the power- and value-packed ALPHA 76 and the exclusive NO-TUNE-UP ALPHA 374 — is meticulously engineered and built to handle continuous operation IN ANY MODE AT MAXIMUM LEGAL POWER [NTL]. . . No Time Limit. And ETO's warranty on every ALPHA amplifier protects you FOR EIGHTEEN MONTHS — FIVE TIMES LONGER than most amateur equipment warranties!

ALPHA: SURE YOU CAN BUY A CHEAPER LINEAR. . . BUT IS THAT REALLY WHAT YOU WANT?

A LINEAR AMPLIFIER IS A BIG INVESTMENT. . . MAKE IT WISELY. For an enlightening glimpse at what goes into the design of every ALPHA by ETO's power professionals, or to aid you in comparing one linear with another, call or write for our brief guide entitled, "EVERYTHING YOU ALWAYS WANTED TO KNOW ABOUT (COMPARING) LINEARS. . . BUT DIDN'T KNOW WHOM TO ASK." We'll also send you fully detailed and illustrated literature describing the entire ETO line of superb ALPHA power amplifiers and ALPHA/VOMAX — the new split-band speech processor that's your key to rf clipper type "talk power" combined with easy mike-line installation and low-distortion, practically foolproof operation.



EHRHORN TECHNOLOGICAL OPERATIONS, INC.
P.O. BOX 708 — INDUSTRIAL PARK
CANON CITY, CO. 81212 PHONE (303) 275-1613

GROTH-Type

COUNTS & DISPLAYS YOUR TURNS

- 99.99 Turns
- One Hole Panel Mount
- Handy Logging Area
- Spinner Handle Available

Case: 2x4"; shaft 1/4"x3"

Model	POST PAID
TC 2	\$8.00
TC 3	\$8.75
Spinner (S)	\$1.00

Add \$0.75 for Air or UPS

Model TC2: Skirt 2-1/8"; Knob 1-5/8"
Model TC3: Skirt 3"; Knob 2-3/8"

R. H. BAUMAN SALES
P.O. Box 122, Itasca, Ill. 60143

TEXAS INSTRUMENTS INCORPORATED

Electronic Calculators



TI-30-SP	\$18.95
TI-1750	21.95
TI-5015	69.95
TI-5050M	84.95
TI-5040	99.95
TI-5100	45.95
Bus. Anal.	29.95
SR-40	27.95
SR-51-II	49.95
SR-57	69.95
SR-58	109.95
SR-59	259.95
PC-100A	149.95
Software	29.95



Texas Instruments Microelectronic Digital Watches from \$9.95 (TI-503)

Hewlett-Packard Calculators
10% discount from list.

Add \$2 per unit for shipping. CA shipments add 6% sales tax. Send cashiers check or money order for immediate delivery (personal checks must clear). Most items shipped from stock within 48 hours.

The Calculator Shop

1160 Marsh Street
San Luis Obispo, CA 93401
(805) 544-1432

SPECSCAN-S Programmable Scanner

... The ONLY Digital Scanner made for the IC-22S. It adds a whole new dimension to 2M FM. If any other accessory can make your IC-22S as versatile as the SPECSCAN-S does, Buy It!

- Scans the entire 146-147 MHz Band in 15 kHz steps, automatically, or manually
- Exclusive VARI-SCAN™ control allows full control of scan rate in either direction!
- Full compatibility with the duplex mode.
- Uses state of the art CMOS logic.
- Low power consumption. Less than 500 Ma.
- RF Immune. Unaffected by nearby equipment and in high RF areas.
- Large LED display lets you see every channel at a glance.
- Manual mode feature lets you scan past any portion of the band and manually select a desired channel.
- Can be used as a remote unit with the radio hidden under the seat, etc.
- Easy installation. Uses only one matrix position leaving the other 21 useable for manual programming.
- Automatically reads out your other 21 channels when they are used.
- Plugs into 9 pin accessory socket.
- Adjustable scan delay feature.




ONLY **149⁹⁵** Amateur Net

SPECIAL PACKAGE PRICE
BRAND NEW IC-22S AND
SPECSCAN DIGITAL SCANNER
Both for only **\$398⁰⁰**

DIGITRAN KEYBOARD

12 Key
\$8.00

16 Key
\$10.00

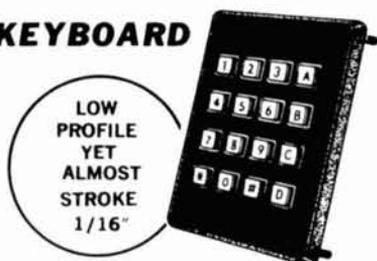

LOW
PROFILE
YET
ALMOST
STROKE
1/16"

This very popular item at the 1976 Dayton Hamvention is NOW OFFERED TO YOU at these low prices. Incorporates the ideal "tactile feel" leaving no doubt that contact has been made. These NEW keyboards, manufactured by THE DIGITRAN COMPANY, are furnished with instructions for combining with a MOSTEK or MOTOROLA chip and a crystal (plus several small components) to become a Tone Encoder.

12 Key (2 of 7 Matrix) 2" x 2.7" x 5/16" \$8.00 plus shipping
16 Key (2 of 8 Matrix) 2.5" x 2.7" x 5/16" \$10.00 plus shipping

QUALI-COMP SWR/FS METERS

Model 120

\$19.95



Model 110

\$24.95



Model 110 SWR/Power/Field Strength Meter. Shows SWR from 1:1 to 3:1, RF power from 0-10 watts and 0-100 watts. Accuracy: SWR, 5%; Power, 10%. Frequency range: 1.5 to 144 MHz. Impedance: 52 ohms. Has 100 microamp DC meter, 5" bar antenna, SO-239 connector \$24.95 plus shipping

Model 120 SWR/Field Strength Meter. Indicates SWR from 1:1 to 3:1 with 5% accuracy. Has 300 microamp DC meter, 5" bar antenna, 52-ohm impedance \$19.95 plus shipping

IT'S NOT TOO LATE TO SEND FOR YOUR 1977 BUYER'S GUIDE. 44 PAGES OF AMATEUR GOODIES.

SEE US AT HAMFESTERS HAMFEST . . .
SANTA FE PARK, IL — AUGUST 14; DES
MOINES HAMFEST . . . DES MOINES, IA —
AUGUST 21.



BIRD

... If you have been having difficulty locating the Wattmeter or element just right for you. . . . You may have been looking in the wrong places. Our large inventory of most common elements lets you get what you want when you need it. Give us a call first for your BIRD needs.



SPECTRONICS, INC.

1009 GARFIELD
OAK PARK, IL. 60304
312-848-6777
TELEX 72:8310

HOURS


STORE HOURS:

Mon-Thurs 9:30-6:00, Fri. 9:30-8:00
Sat. 9:30-3:00, Closed Sun. & Holidays.



Barry

presents

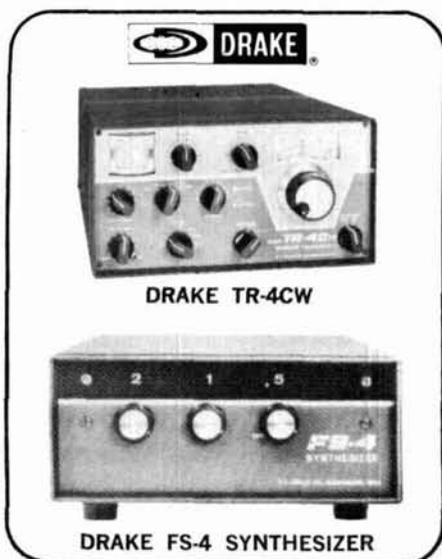

NEW! Drake ENCODER MIKE NOW IN STOCK.

WE CARRY A FULL LINE OF ANTENNAS, ROTATORS AND TOWERS. ARRL PUBLICATIONS AND CODE PRACTICE TAPES. HY-GAIN MARINE VHF TRANSCEIVER IN STOCK.

Qualified service and repair facilities on premises. Call for info.

TUBES AVAILABLE

COMPLETE YAESU, KLM, KENWOOD, DRAKE, ICOM, TEMPO, SHURE, TURNER ASTATIC, HYGAIN, LARSEN, KDK, WILSON, ATLAS, SWAN, BIRD, MINIPRODUCTS, COLLINS, STANDARD, ETC. IN STOCK.

OPEN DAILY 9-5; SATURDAY 10-3

MAIL ALL ORDERS TO: BARRY ELECTRONICS CORPORATION
512 BROADWAY, NEW YORK CITY, NEW YORK 10012
BARRY INTERNATIONAL TELEX 12-7670
212-925-7000

AVAILABLE AT

Barry Electronics

THE NAME THAT'S KNOWN AROUND THE WORLD

60* CHANNELS
DIRECT READOUT / PREPROGRAMMED
WITH YOUR IC-22S

Single knob Selected

15 kHz Option

*120 channels with 15 kHz Split Option

You Get These 56 Frequencies Pre-Programmed in the Conversion:

146.01	146.34	146.82	147.15	147.69
146.04	146.37	146.85	147.18	147.72
146.07	146.40	146.88	147.21	147.75
146.10	146.43	146.91	147.24	147.78
146.13	146.46	146.94	147.27	147.81
146.16	146.49	146.97	147.30	147.84
146.19	146.52	147.00	147.33	147.87
146.22	146.55	147.03	147.36	147.90
146.25	146.58	147.06	147.39	147.93
146.28	146.61	147.09	147.42	147.96
146.31	146.64	147.12	147.45	147.99

Install the VIP-60 switch in place of the original 22 channel switch in your IC-22S and you'll have the 56 pre-programmed frequencies listed plus any four additional frequencies you wish to program for yourself. Add 15 kHz splits with split option.

Fast, simple and clean conversion makes a fine transceiver even better
Valley Instrument Products
P.O. BOX 339 - BARTLETT, ILLINOIS 60103 (312) 741-8820

YOU'VE SEEN THE MAGAZINE ARTICLES

Here's what you can expect from the **DX ENGINEERING RF Speech Processor**

- 6 db INCREASE IN AVERAGE POWER
- MAINTAINS VOICE QUALITY
- IMPROVES INTELLIGIBILITY
- NO CABLES OR BENCH SPACE REQUIRED
- EXCELLENT FOR PHONE PATCH
- NO ADDITIONAL ADJUSTMENTS — MIKE GAIN ADJUSTS CLIPPING LEVEL
- UNIQUE PLUG-IN UNIT — NO MODIFICATIONS REQUIRED



This is RF Envelope Clipping—the feature being used in new transmitter designs for amateur and military use.

Models Now Available
Collins 32S, KWM-2 \$ 98.50 ea.
Drake TR-3, TR-4, TR-6, TR-4C, T-4, T-4X, T-4XB, T-4XC \$128.50 ea.
Postpaid — Calif. Residents add 6% Tax

Watch for other models later!

DX Engineering

1050 East Walnut, Pasadena, Calif. 91106

Valley Instrument Products
P.O. Box 339, Bartlett, IL 60103



Ship _____ VIP-60 conversion kit(s) at \$25.00 each plus

\$1.00 packing and shipping. Include _____ 15 kHz options(s) at \$3.00 each. No C.O.D.'s, PLEASE.
Illinois residents add 5% sales tax.

Name _____ Call _____
Address _____
City _____
State _____ Zip _____
 Check or money order for \$ _____ enclosed
 Charge my VISA/BankAmericard # _____
Card expires _____ Signature _____

ADVANCED MICROCOMPUTER PRODUCTS

MOTOROLA EXORCISER & MEK D1 & MEK D2 COMPATIBLE MODULES

MEK6800D2 - 6800 KIT ONLY	\$235.00	9626K 8K Static RAM Kit	275.00
		9650 B Port Duplex Asyn Serial I/O	395.00
All assembled & tested net Kits			
PLUS MOTOROLA TV MONITORS - PRIME			
		Model M3000 100 12" display	\$219.95
		Model M2000 155 9" display	\$199.95
Add \$10.00 for shipping			

IC MARKET PLACE

MICROPROCESSORS	PROM'S	RAM'S
8008A	\$ 16.95 6330	7 236
8008 B	8.95 6331	2.95 7429A 99
8212	4.25 6300	7429B 70 74251 1.69
8216	8.95 6301	7429C 97 74279 1.10
8224	4.95 6340	7429D 95 74269 1.99
8226	4.95 6306-1	7429E 95 74365 .79
8228	8.75 6306-1	7429F 65 74368 .79
8251	14.95 6352	7429G 45 74369 .79
9501	14.95 6353	7429H 45 74370 .79
9505	14.95 6354	7429I 45 74371 .79
6800P	24.50 1702A	7429J 45 74372 .79
6810A	6.25 1702A-6	7429K 45 74373 .79
6802P	8.95 6834	7429L 45 74374 .79
6834-1	16.95 6834	7429M 45 74375 .79
6834	21.95 6834	7429N 45 74376 .79
6850	9.95 6850	7429O 45 74377 .79
6852	11.95 6850	7429P 45 74378 .79
6860	15.95 7400TTL	7429Q 45 74379 .79
6871A	19.95 7400N	7429R 45 74380 .79
Prog. Man	15.00 7401N	7429S 45 74381 .79
Hard Man	15.00 7402N	7429T 45 74382 .79
Tiny Basic P/T	20.00 7403N	7429U 45 74383 .79
Tiny Basic EPROM	125.00 7404N	7429V 45 74384 .79
6831 MACRO	30.00 7405N	7429W 45 74385 .79
2909	29.95 7406N	7429X 45 74386 .79
2902	29.95 7407N	7429Y 45 74387 .79
2905	9.95 7408N	7429Z 45 74388 .79
2906	9.95 7409N	7429AA 45 74389 .79
2907	10.75 7410N	7429AB 45 74390 .79
2911	21.95 7411N	7429AC 45 74391 .79
2909	21.95 7412N	7429AD 45 74392 .79
2927	7.95 7413N	7429AE 45 74393 .79
2909	7.95 7414N	7429AF 45 74394 .79
Z80	37.95 7415N	7429AG 45 74395 .79
Z80P/U	14.95 7420N	7429AH 45 74396 .79
Z80CTC	14.95 7421N	7429AI 45 74397 .79
6602	24.95 7422N	7429AJ 45 74398 .79
CP1600	48.95 7425N	7429AK 45 74399 .79
RAM'S		7429AL 45 74400 .79
21L02(450ns)	1.75 7427N	7429AM 45 74401 .79
21L02(250ns)	2.25 7428N	7429AN 45 74402 .79
1102(450ns)	1.69 7430N	7429AO 45 74403 .79
2102(650ns)	1.59 7432N	7429AP 45 74404 .79
2102(100ns)	1.40 7437N	7429AQ 45 74405 .79
2111	3.95 7438N	7429AR 45 74406 .79
2111	4.25 7441N	7429AS 45 74407 .79
2112	2.95 7442N	7429AT 45 74408 .79
2101	2.95 7443N	7429AU 45 74409 .79
2110	2.95 7444N	7429AV 45 74410 .79
74C83	4.95 7445N	7429AW 45 74411 .79
74489	2.95 7446N	7429AX 45 74412 .79
74489	2.95 7447N	7429AY 45 74413 .79
74489	2.95 7448N	7429AZ 45 74414 .79
74489	2.95 7449N	7429BA 45 74415 .79
74489	2.95 7450N	7429BB 45 74416 .79
74489	2.95 7451N	7429BC 45 74417 .79
74489	2.95 7452N	7429BD 45 74418 .79
74489	2.95 7453N	7429BE 45 74419 .79
74489	2.95 7454N	7429BF 45 74420 .79
74489	2.95 7455N	7429BG 45 74421 .79
74489	2.95 7456N	7429BH 45 74422 .79
74489	2.95 7457N	7429BI 45 74423 .79
74489	2.95 7458N	7429BJ 45 74424 .79
74489	2.95 7459N	7429BK 45 74425 .79
74489	2.95 7460N	7429BL 45 74426 .79
74489	2.95 7461N	7429BM 45 74427 .79
74489	2.95 7462N	7429BN 45 74428 .79
74489	2.95 7463N	7429BO 45 74429 .79
74489	2.95 7464N	7429BP 45 74430 .79
74489	2.95 7465N	7429BQ 45 74431 .79
74489	2.95 7466N	7429BR 45 74432 .79
74489	2.95 7467N	7429BS 45 74433 .79
74489	2.95 7468N	7429BT 45 74434 .79
74489	2.95 7469N	7429BU 45 74435 .79
74489	2.95 7470N	7429BV 45 74436 .79
74489	2.95 7471N	7429BW 45 74437 .79
74489	2.95 7472N	7429BX 45 74438 .79
74489	2.95 7473N	7429BY 45 74439 .79
74489	2.95 7474N	7429BZ 45 74440 .79
74489	2.95 7475N	7429CA 45 74441 .79
74489	2.95 7476N	7429CB 45 74442 .79
74489	2.95 7477N	7429CC 45 74443 .79
74489	2.95 7478N	7429CD 45 74444 .79
74489	2.95 7479N	7429CE 45 74445 .79
74489	2.95 7480N	7429CF 45 74446 .79
74489	2.95 7481N	7429CG 45 74447 .79
74489	2.95 7482N	7429CH 45 74448 .79
74489	2.95 7483N	7429CI 45 74449 .79
74489	2.95 7484N	7429CJ 45 74450 .79
74489	2.95 7485N	7429CK 45 74451 .79
74489	2.95 7486N	7429CL 45 74452 .79
74489	2.95 7487N	7429CM 45 74453 .79
74489	2.95 7488N	7429CN 45 74454 .79
74489	2.95 7489N	7429CO 45 74455 .79
74489	2.95 7490N	7429CP 45 74456 .79
74489	2.95 7491N	7429CQ 45 74457 .79
74489	2.95 7492N	7429CR 45 74458 .79
74489	2.95 7493N	7429CS 45 74459 .79
74489	2.95 7494N	7429CT 45 74460 .79
74489	2.95 7495N	7429CU 45 74461 .79
74489	2.95 7496N	7429CV 45 74462 .79
74489	2.95 7497N	7429CW 45 74463 .79
74489	2.95 7498N	7429CX 45 74464 .79
74489	2.95 7499N	7429CY 45 74465 .79
74489	2.95 7500N	7429CZ 45 74466 .79

7450	7450A 99	74200 5.95	L3378 1.29
7451	7450B 70	74201 1.69	811995 1.10
7452	7450C 97	74202 1.10	811996 1.10
7453	7450D 95	74203 1.99	811997 1.10
7454	7450E 95	74204 1.99	811998 1.10
7455	7450F 65	74205 1.99	811999 1.10
7456	7450G 45	74206 1.99	812000 1.10
7457	7450H 45	74207 1.99	812001 1.10
7458	7450I 45	74208 1.99	812002 1.10
7459	7450J 45	74209 1.99	812003 1.10
7460	7450K 45	74210 1.99	812004 1.10
7461	7450L 45	74211 1.99	812005 1.10
7462	7450M 45	74212 1.99	812006 1.10
7463	7450N 45	74213 1.99	812007 1.10
7464	7450O 45	74214 1.99	812008 1.10
7465	7450P 45	74215 1.99	812009 1.10
7466	7450Q 45	74216 1.99	812010 1.10
7467	7450R 45	74217 1.99	812011 1.10
7468	7450S 45	74218 1.99	812012 1.10
7469	7450T 45	74219 1.99	812013 1.10
7470	7450U 45	74220 1.99	812014 1.10
7471	7450V 45	74221 1.99	812015 1.10
7472	7450W 45	74222 1.99	812016 1.10
7473	7450X 45	74223 1.99	812017 1.10
7474	7450Y 45	74224 1.99	812018 1.10
7475	7450Z 45	74225 1.99	812019 1.10
7476	7451A 45	74226 1.99	812020 1.10
7477	7451B 45	74227 1.99	812021 1.10
7478	7451C 45	74228 1.99	812022 1.10
7479	7451D 45	74229 1.99	812023 1.10
7480	7451E 45	74230 1.99	812024 1.10
7481	7451F 45	74231 1.99	812025 1.10
7482	7451G 45	74232 1.99	812026 1.10
7483	7451H 45	74233 1.99	812027 1.10
7484	7451I 45	74234 1.99	812028 1.10
7485	7451J 45	74235 1.99	812029 1.10
7486	7451K 45	74236 1.99	812030 1.10
7487	7451L 45	74237 1.99	812031 1.10
7488	7451M 45	74238 1.99	812032 1.10
7489	7451N 45	74239 1.99	812033 1.10
7490	7451O 45	74240 1.99	812034 1.10
7491	7451P 45	74241 1.99	812035 1.10
7492	7451Q 45	74242 1.99	812036 1.10
7493	7451R 45	74243 1.99	812037 1.10
7494	7451S 45	74244 1.99	812038 1.10
7495	7451T 45	74245 1.99	812039 1.10
7496	7451U 45	74246 1.99	812040 1.10
7497	7451V 45	74247 1.99	812041 1.10
7498	7451W 45	74248 1.99	812042 1.10
7499	7451X 45	74249 1.99	812043 1.10
7500	7451Y 45	74250 1.99	812044 1.10
7501	7451Z 45	74251 1.99	812045 1.10
7502	7452A 45	74252 1.99	812046 1.10
7503	7452B 45	74253 1.99	812047 1.10
7504	7452C 45	74254 1.99	812048 1.10
7505	7452D 45	74255 1.99	812049 1.10
7506	7452E 45	74256 1.99	812050 1.10
7507	7452F 45	74257 1.99	812051 1.10
7508	7452G 45	74258 1.99	812052 1.10
7509	7452H 45	74259 1.99	812053 1.10
7510	7452I 45	74260 1.99	812054 1.10
7511	7452J 45	74261 1.99	812055 1.10
7512	7452K 45	74262 1.99	812056 1.10
7513	7452L 45	74263 1.99	812057 1.10
7514	7452M 45	74264 1.99	812058 1.10
7515	7452N 45	74265 1.99	812059 1.10
7516	7452O 45	74266 1.99	812060 1.10
7517	7452P 45	74267 1.99	812061 1.10
7518	7452Q 45	74268 1.99	812062 1.10
7519	7452R 45	74269 1.99	812063 1.10
7520	7452S 45	74270 1.99	812064 1.10
7521	7452T 45	74271 1.99	812065 1.10
7522	7452U 45	74272 1.99	812066 1.10
7523	7452V 45	74273 1.99	812067 1.10
7524	7452W 45	74274 1.99	812068 1.10
7525	7452X 45	74275 1.99	812069 1.10
7526	7452Y 45	74276 1.99	812070 1.10
7527	7452Z 45	74277 1.99	812071 1.10
7528	7453A 45	74278 1.99	812072 1.10
7529	7453B 45	74279 1.99	812073 1.10
7530	7453C 45	74280 1.99	812074 1.10
7531	7453D 45	74281 1.99	812075 1.10
7532	7453E 45	74282 1.99	812076 1.10
7533	7453F 45	74283 1.99	812077 1.10
7534	7453G 45	74284 1.99	812078 1.10
7535	7453H 45	74285 1.99	812079 1.10
7536	7453I 45	74286 1.99	812080 1.10
7537	7453J 45	74287 1.99	812081 1.10
7538	7453K 45	74288 1.99	812082 1.10
7539	7453L 45	74289 1.99	812083 1.10
7540	7453M 45	74290 1.99	812084 1.10
7541	7453N 45	74291 1.99	812085 1.10
7542	7453O 45	74292 1.99	812086 1.10
7543	7453P 45	74293 1.99	812087 1.10
7544	7453Q 45	74294 1.99	812088 1.10
7545	7453R 45	74295 1.99	812089 1.10
7546	7453S 45	74296 1.99	812090 1.10
7547	7453T 45	74297 1.99	812091 1.10
7548	7453U 45	74298 1.99	812092 1.10
7549	7453V 45	74299 1.99	812093 1.10
7550	7453W 45	74300 1.99	812094 1.10
7551	7453X 45	74301 1.99	812095 1.10
7552	7453Y 45	74302 1.99	812096 1.10
7553	7453Z 45	74303 1.99	812097 1.10
7554	7454A 45	74304 1.99	812098 1.10
7555	7454B 45	74305 1.99	812099 1.10
7556	7454C 45	74306 1.99	812100 1.10
7557	7454D 45	74307 1.99	812101 1.10
7558	7454E 45	74308 1.99	812102 1.10
75			

Barrel Bustin' Blast-off

Avg. Ship.
Wt. 6-ozs.

Buy from the
BARRELS
n'SAVE!

EXCLUSIVE AT
POLY PAKS


Buy
10
BARREL KITS
AND CHOOSE THE
11TH
KIT
Free

Test 'em
yourself and save!

Kits include 100% material, too!

Each kit carries a money-back guarantee!

BARREL KIT #239 SHIELDED CABLE 50-ft. \$1.98 For mikes, stereos, 1-cond. plus shield, 22 ga. vinyl jacket. Wt. 1 lb. BH3877	BARREL KIT #230 HALF INCH READOUTS \$1.98 15 for \$1.98 For mikes, stereos, 1-cond. includes Fairchild FND-500 & 507's. Cat. No. BH3629	BARREL KIT #225 SOUND TRIGGERS 3 for \$1.98 "Hand clap" sensitizes crystal mike amplifier, triggers SCR. Cat. No. BH3625	BARREL KIT #221 IC SOCKETS 8 for \$1.98 Mir. 100% good. Four 14-pin, four 18-pin. Solder tail, 9-profile. No. BH3621	BARREL KIT #205 MINI BLOCK CAPACITORS 50 for \$1.98 Unbelievable! Worth \$50. High precision at ridiculous prices for all applications. Wt. 3 ozs. Cat. BH1829	BARREL KIT #203 CALCULATOR KEYBOARDS 10 for \$1.98 It's true! 20-key, 4 function keyboard at ridiculous give-aways! Wt. 12 ozs. Cat. No. BH3524	BARREL KIT #210 GLOWIN' PANELS 3 for \$1.98 4" x 1" panels that glow blue-green with 110VAC. Use for nite lites, indicators, etc. Cat. No. BH3550
100 for \$1.98 KIT #202 PLUGS, SOCKETS Distributor unload! Includes AC, DC, RF, audio 4-0 pin, all kinds. Wt. 1 lb. Cat. No. BH3527	BARREL KIT #201 6V INDICATORS 15 for \$1.98 Test lamp manufacturer dumps inventory! Worth \$24 ea. Like train-owned. Cat. No. BH3526	BARREL KIT #200 9 DIGIT READOUT MODULES 5 for \$1.98 With calculator driver chips, beneath epoxy. Cat. No. BH3515	BARREL KIT #198 400 Parts \$1.98 Includes resistors, caps, transformers, rectifiers, diodes, etc. for p.c. work. Performed, dumped into lots by factory. 100% good. Cat. No. BH1401	BARREL KIT #184 1/4-WATT METAL FILM 150 for \$1.98 100% metal film resistors. Long leads. BH3413	BARREL KIT #182 JUMBO RED LEDS 15 for \$1.98 100% material, user cancellation from factory dumps, 4V @ 90 mls. For 100's of projects, red lens. Cat. No. BH3369	BARREL KIT #163 MINI TRIM POTS 30 for \$1.98 Asst. values 100 to 100k. What a buy. Single turn. 1/4 W. Wt. 6 oz. BH3348
BARREL KIT #160 V. REGULATORS 10 for \$1.98 No. BH3330 LM309K TO-3 V.R.'s barreled. Bot. by the pound.	BARREL KIT #159 MODULAR SWITCHES 25 for \$1.98 We gathered an assortment of switch lab, TV-mikeers, excess. Dadd. Gndr. et Brand new. Cat. No. BH3150	BARREL KIT #154 CLOCK CHIPS 20 for \$1.98 We gathered an assortment of clock chip, alarm, calendar, beepers, who knows, all mixed. Cat. No. BH3308	BARREL KIT #145 MINI TRANSFORMER 15 for \$1.98 1,000,000 RCA phono plugs for this one. You hi-fiers know what we are. 100% material. BH3293	BARREL KIT #144 RCA PHONO PLUGS 40 for \$1.98 1,000,000 RCA phono plugs for this one. You hi-fiers know what we are. 100% material. BH3293	BARREL KIT #138 PANEL SWITCHES 30 for \$1.98 Did you hear of OAK? Another opti maker barreled all types of rotary electric, slugs, etc. BH3268	BARREL KIT #135 MICRO MINI LAMPS 20 for \$1.98 Imagined Micro size (1/4 x 1/4) with wire leads. 1 to 5 VDC. 40 mps. BH3259
BARREL KIT #128 MINI DIP IC'S 100 for \$1.98 Large mfg dumped 100's of into barrels. Includes 741s, LM-390-3, 793, 567, 555, 558—but who knows? Wt. 1 lb. BH3245 hobby	BARREL KIT #127 AXIAL ELECTROS 40 for \$1.98 Asst. capacities and voltages. Cat. No. BH3227	BARREL KIT #126 UPRIGHT ELECTROS 40 for \$1.98 1mf to 300mf in mixture of voltages. 100% marked 'a' good. BH3226	BARREL KIT #115 MOLEX SOCKETS 200 for \$1.98 Calculator maker dump! We got a zillion of 'em. Cat. No. BH3144	BARREL KIT #112 RCA MINI LEDS 40 for \$1.98 All the tiny leds, axial, up-right of Monsanto. Little variety of colors. Yield 60% or better. BH3139	BARREL KIT #108 TERMINAL STRIPS 100 for \$1.98 Wide asst. of terminal strip connectors, from 1 contact up. Strip manufacturers barrel dump is your gain. Wt. 1 lb. Cat. No. BH3136	BARREL KIT #104 SLIDE VOLUME CONTROLS 10 for \$1.98 From a Litronics dump of all kinds of mixed discrete LEDs. BH2859
BARREL KIT #101 RESISTOR SPECIAL 200 for \$1.98 Includes: 1/8, 1/4, 1/2, 1, 2-watt, carbon. 100% good. BH3054	BARREL KIT #99 PHOTO ELECTRIC CELLS 10 for \$1.98 Asst. GE types, CDS types. Mixed by factory. Big job for us to separate. 100% good. Cat. No. BH3052	BARREL KIT #93 HALF WATTS 200 for \$1.98 Resistor factory tried to fool us by mixing 100% color-coded resistors in barrel. But value is there. 4 oz. BH3046 Untested	BARREL #91 SILVER MICAS 100 for \$1.98 Axial, red case, variety of physical sizes & values. Cat. No. BH3018	BARREL KIT #88 LITRONICS LED READOUTS 10 for \$1.98 From Hobby singles, tri-plex, etc. 3 to 0.1. Not from factory. All excellent. Have fun! No. BH2861	BARREL KIT #87 NATIONAL IC BONANZA 100 for \$1.98 Types 8000, 7400 series, DTLs, ROMs, registers, clock & rate clocks, linears, etc. Cat. No. BH2860 Untested.	BARREL KIT #86 HOBBY LEDS 40 for \$1.98 From a Litronics dump of all kinds of mixed discrete LEDs. BH2859
BARREL KIT #83 LM-340T VOLT REG 15 for \$1.98 Factory rejected them for length of leads. May include 6, 8, 12, 15, 18, 24 volts. Power tab. Cat. BH2635	BARREL KIT #81 MINI RESISTORS 200 for \$1.98 PC, up right type, color coded. 1/2 watt. Ass. values. Came in us in a barrel. Cat. No. BH2746 100% good	BARREL KIT #78 1-WATT ZENERS 100 for \$1.98 Factory same as 400-mw's. Never-to-see-again offer, 6, 8, 10, 12, 15V. under glass. Double plug. Cat. No. BH2741 Untested	BARREL #73 TRANSISTOR ELECTROS 50 for \$1.98 We don't wish to separate wide asst voltages & values up to 300 mf. Cat. No. BH2747	BARREL KIT #72 CAPACITOR SPECIAL 100 pcs. \$1.98 micas, molded, plastics, ceramics, discs, etc. Nifty 100% good. Cat. No. BH2738	BARREL KIT #68 2 WATTS 100 for \$1.98 100% good. Suppliers throw 'em in the barrel. It's a 1/4 gold mine. All marked. Cat. No. BH2735	BARREL KIT #65 MIXED READOUTS 10 for \$1.98 Factory returns—such numbers as MAN-4's, MAN-7's, MAN-3's, 11 barrels & no time to separate. Hobby Cat. No. BH2733 Untested.
BARREL KIT #61 POLYSTYRENE CAPS 100 for \$1.98 Finest caps made. As a gamble we bought 10 barrels from factory, mixed values. All good. Cat. No. BH2729	BARREL KIT #58 SLIDE SWITCHES 30 for \$1.98 All shapes, sizes, spst, apst, momentaries, etc. Tremendous shop pick for 100's of switching projects. Cat. No. BH2726 100% good	BARREL KIT #54 DIGIT READOUTS 10 for \$1.98 Bargain of a lifetime! All we got was 1 barrel—the "bicolor digit" types. Multi-plexed. Cat. No. BH2722	BARREL KIT #53 NEON LAMPS 30 for \$1.98 100% good. Famous NE-2's. All prime, but factory made millions and barreled 'em. Your advantage. Cat. No. BH2613	BARREL KIT #52 PREFORMED DISCS 150 for \$1.98 Hi-Fi mfr's shelf inventory but be dumped em in barrels. Performed, for PC use. Mixed values too! 2605	BARREL KIT #49 PNP HIGH-POWER TRANSISTORS 20 for \$1.98 Popular germanium TO-3 case BH2618 100% good	BARREL KIT #48 GERMANIUM DIODES 200 for \$1.98 Famous maker, popular item. Never grows old. Cat. No. BH2614

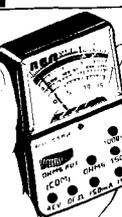

RCO VOM

Specifications
Ranges—DC Voltage: 0 to 15, 150, and 1000 V; AC Voltage: 0 to 15, 150, and 1000 V; Direct Current: 0 to 150 mA; Resistance: R x 1K (measures 100 Ω to 100 K Ω); Sensitivity—AC/DC: 1000 ohms-per-volt.
Battery, for ohms function (not supplied)—one 1.5 V penlite (GCA V5034A or equiv). Direct Current and Weight—Dimensions: 3 1/2 in. (9 cm), 2 1/2 in. (6 cm); 1 1/2 in. (3.8 cm); Weight: 5 oz. (142g). Cat. No. BH3921

\$995

1000 ohms per V.

J.C. Penney's

CB-HAM NOISE CANCELLING COMMUNICATIONS MIC

• UNIVERSAL! Fit virtually all rigs... everywhere.
• Dynamic cartridge.

The answer to the biggest mobile communication problem... automatic noise-cancelling. Works more effectively than power mikes. A must for 2 meter hams, Dodge's "trip" repeaters. Low impedance, frequency response 300-5000 Hz, sensitivity—65db, 6 foot coiled cord, case made of hi-impact black plastic. With wiring instructions for 100's of CB's.

\$995

Cuts out noise of machinery, highway for clear transmission. Spt. wt. 2 lbs. BH3902



8 TRACK TAPE TRANSPORT

• Shielded preamp
• 115VAC fan cooled motor
• Slides easily into modular cabinet

Special purchase from a famous USA maker of quality Hi-Fi systems for J.C. Penney's. Same unit as found in the most expensive home players. Plugs into any stereo amplifier! Excellent replacement unit or design your own high quality stereo tape system that inserts an own high quality stereo tape and turns on automatically! Enjoy up to 80 minutes of non-stop music. Remove cartridge and player shuts off automatically! Built in program indicator lights, automatic and manual track selection. Ready to go, requires only external power supply! With output cables for amplifier, and input cables for power supply. With instructions. Wt. 4 lbs. Size: 9 x 6 x 3 1/2". Cat. No. BH3010

\$995

5 IN 1 PROJECT-ALL SLIDE PROJECTORS \$1250

• Worth many times our asking price.
• Great for Light Shows, Strobes, Light Displays, Slide Projector!
• Wide angle focusing lens!

U.S. maker. Originally designed as a slide projector. Some may be modified for projecting a bar of lite. High quality 3 lens condensing system. Requires standard 100 watt projection bulb. 35mm slides can be inserted and removed manually. Heavy duty bakelite case, grey and hammer-tone finish. Design your own low cost light show. Use a Xenon flash tube and make a strobe light. Many other uses too numerous to mention. Size: 11 x 8 1/2 x 4 1/2". Wt. 5 lbs. Cat. No. BH3870

BARREL KIT #35 NEON LAMPS 30 for \$1.98 100% good. Famous NE-2's. All prime, but factory made millions and barreled 'em. Your advantage. Cat. No. BH2613	BARREL KIT #31 METALLIC RESISTORS 100 for \$1.98 Made mostly by Corning. The finest resistor made. Mostly 1/2 watters. 1% to 5% tol, & a barrel of values. Cat. No. BH2605	BARREL KIT #29 DIPPED MYLARS 60 for \$1.98 Finest capacitors made, shiny finish. Imagine factory dumping 'em in barrels. Cat. No. BH2597 100% good	BARREL KIT #28 PLASTIC TRANSISTORS 100 for \$1.98 Hobby Untested. Type TO-92 (TO-18), all manufacturers, variety of 2N's. Cat. No. BH2604	BARREL KIT #27 PREFORMED DISCS 150 for \$1.98 Hi-Fi mfr's shelf inventory but be dumped em in barrels. Performed, for PC use. Mixed values too! 2605	BARREL KIT #26 MIXED READOUTS 10 for \$1.98 Factory returns—such numbers as MAN-4's, MAN-7's, MAN-3's, 11 barrels & no time to separate. Hobby Cat. No. BH2733 Untested.
BARREL KIT #25 LONG LEAD DISCS 100 for \$1.98 "Auction sale". Prime, marked only. Long leads. Cat. No. BH2598 100% good	BARREL KIT #24 PRECISION RESISTORS 200 for \$1.98 Marked and unmarked 1/4, 1/2, 2 watts. No. BH2428	BARREL KIT #23 SUBMINIATURE IF TRANSFORMERS 75 for \$1.98 Amazing, includes 455kcs, osc. antenna, who knows? Cat. No. BH2422 100% good	BARREL KIT #22 "4000" RECTIFIERS 100 for \$1.98 Untested. 1N4000 series. May include 2N, 50, 100, 200, 400, 600, 800, and 1000 volters. BH2417	BARREL KIT #21 LINEAR OP AMPS, DIPS 75 for \$1.98 Untested. May include 709's, 741's, 703's, 560 series, 555 includes. BH2416 hobby	BARREL KIT #20 RCA MINI LEDS 40 for \$1.98 All the tiny leds, axial, up-right of Monsanto. Little variety of colors. Yield 60% or better. BH3139

Phone: Add postage Rated: net 30
Terms: Wakefield, Mass. (617) 245-3829
Retail: 16-18 Del Carmine St., Wakefield.

POLY PAKS

P.O. BOX 942H LYNNFIELD, MA. 01940

SALE! Send for FREE SUMMER CATALOG

C.O.D.'S MAY BE PHONED

flea market



RATES Non-commercial ads 10¢ per word; commercial ads 60¢ per word both payable in advance. No cash discounts or agency commissions allowed.

HAMFESTS Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing). Repeat insertions of hamfest ads pay the non-commercial rate.

COPY No special layout or arrangements available. Material should be typewritten or clearly printed (not all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. Ham Radio cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue

DEADLINE 15th of second preceding month.

SEND MATERIAL TO: Flea Market, Ham Radio, Greenville, N.H. 03048.

YAESU FTdx 560 Transceiver: 80-10M, 550 Watts SSB/CW with matching speaker, CW filter, new and spare finals, manual. Mint condition. Ship in original carton. \$415 F.O.B. Jordan, 1012 Olmo, San Jose, CA 95129.

HAM RADIO HORIZONS, a super new magazine for the Beginner, the Novice and anyone interested in Amateur Radio... What it's all about. How to get started. The fun of ham radio. It's all here and just \$10.00 per year. HURRY! HURRY! Ham Radio HORIZONS, Greenville, NH 03048.

WANTED: Preamps (Janel) 144PB. 432PA. W6R9Z, 1330 Curtis, Berkeley, CA 94702.

QSL CARDS, \$10/500, postage paid. Includes all pertinent data. Bowman Printing Service, 743 Harvard, St. Louis, Mo. 63130.

QRP TRANSMATCH with Preamp for HW7 Ten-Tec. Send stamp for details to Peter Meacham Associates, 19 Lorreta Road, Waltham Mass. 02154.

VARIABLE AND TRIMMER CAPACITORS — RF chokes — Miniinductors; stocked for immediate shipment. First class stamp for flyer. D & V Radio Parts, RI#2, 12805 W. Sarie, Freeland, Michigan 48823.

CANADIANS 1,000,000 surplus parts. Bargains galore. Free catalog. Etco-HR. Box 741, Montreal, H3c 2v2.

PRESALER BOARD for 650 MHz 11C90. Includes instructions and parts source, 3.00. Also CSJ counter boards 15.00 (see 76 ads). RTC Electronics, P.O. Box 2514, Lincoln, Nebr. 68502.

DISCOUNTS — KLM. Larsen, Brimstone, Stereo Systems, Police Monitors, etc. Catalog available. BankAmericard & Mastercharge. 201-962-4695 Narwid Electronics, 61 Bellot Road, Ringwood, N.J. 07456.

TRANSMITTING TUBES, HV and filament xmtrs, rotary inductors, transmitting capacitors. Send stamp for flyer. T.S. Marinich Electronics, 102 Bell St., Weirton, W. Va. 26062.

ALL TYPES ELECTRONICS supplies and kits, just released, 8 digit, 500 MHz counter kit, all parts, case 169.95, specials include TO-3 heatsinks 1.50 555V, 723N 3/1.25 FND-359 75¢, all new parts, you'll appreciate our service, write for flyer, Chemlab-MMC, Box 41472H, Chicago, Il. 60641.

PORTAPAK the accessory that makes your mobile really portable. \$67.50 and \$88.00. Dealer inquires invited. P.O. Box 67, Somers, Wisc. 53171.

SELL GREENLEE CHASSIS PUNCH'S, a few used one to five times rest are new. 1/2, 9/16, 5/8, 11/16, 3/4, 13/16, 7/8, 15/16, 1, 1-1/16, 1-1/8, 1-3/16, 1-1/2, 1-5/8, 2-1/2, 2-3/4, 2-25/32. Sold as one lot at \$45.00. Local buy \$40.00 T.G. North, 2016 N. Adams St., Arlington, Virginia 22201.

RADIO MUSEUM now open. Free Admission. 15,000 pieces of equipment from 1850 telegraph instruments to amateur and commercial transmitters of the 1920's. Amateur station W2AN. Write for information. Antique Wireless Assn., Main St., Holcomb, N. Y. 14469.

47 MFD 4500 VDC OIL CAPACITOR. Ideal for linears or laser discharge cap. NEW. \$30 — 2/\$55.00. 30 lbs. Transmitter Air Variable Capacitor. 55 to 500 MMF. Spacing .219. NEW. \$8.95. 14 lbs. Please include shipping charge. R. W. Electronics, Inc., 3203 N. Western Avenue, Chicago. IL. 60618. 312-248-2480.

QSL — BROWNIE W3CJ1 — 3035B Lehigh, Allentown, Pa. 18103. Samples with cut catalog 50¢.

MOVING: Six meter, teletype, test gear. Miscellaneous meters, tubes. Too much to list. SASE. W1JTL, P.O. Box 297, Leominster, Mass. 01453.

NEW 4-Varactor, 3-transistor UHF TV tuner. Tunes thru 440 MHz for ATV or repeater applications. \$7.95 ppd. Workshop, Box 393H, Bethpage, NY 11714.

TRAVEL PAK QSL KIT — Send call and 25¢; receive your call sample kit in return. Samco, Box 203, Wynantskill, N.Y. 12198.

STOP LOOKING For a good deal on amateur radio equipment — you've found it here — at your amateur radio headquarters in the heart of the Midwest. We are factory-authorized dealers for Kenwood, Drake, Collins, ICOM, Ten-Tec, Atlas, Regency, Tempo, Swan, Midland, Alpha, Standard, Dentron, Hy-Gain, Mosley, Cushman, and CDE, plus accessories. Thousands of thrifty hams from coast to coast already know us and we invite you to join them by writing or calling us today for our low quote and trying our personal and friendly Hoosier service. HOOSIER ELECTRONICS, P. O. Box 2001, Terre Haute, Indiana 47802. (812)-238-1456.

BUY — SELL — TRADE — write for free mailer. Give name address and call letters. Complete stock of major brands new and reconditioned equipment. Call for best deals. We buy Collins-Drake-Swan Etc. SSB & FM. Associated Radio, 8012 Conser, Overland Park, Ks. 66204. 913-381-5901.

MOTOROLA HT220, HT200, and Pageboy service and modifications performed at reasonable rates. WA4FRV (804) 320-4439, evenings.

RF GENERATOR B&K 2050, one month old, warranty card. \$80 General Radio precision variable, 1000 pf, cast housing, 50:1 gear drive, superb dial, \$45. Stephen Johnson, 2011 Ferry Ave., Apt. 1-#2, Camden, NJ 08104.

WANTED: Collins 455 Kc mechanical filters. Stephen Johnson, 2011 Ferry Ave., Apt. 1-#2, Camden, NJ 08104.

RECONDITIONED TEST EQUIPMENT for sale. Catalog \$50. Walter, 2697 Nickel, San Pablo, Ca. 94806.

THE BEST HANDBOOK in Amateur Radio. The Radio Communication Handbook from the RSGB in 2 volumes \$31.90 from ham radio's Communications Bookstore, Greenville, NH 03048.


HT1000 Motorola wanted. Also pre 1935 QST's. Al Blank W1BL, 272 Pine St., Bristol, Ct. 06010.

TRANSMITTER TECHNICIANS — Voice of America has opportunities for qualified technicians at VOA stations in California, North Carolina, and Ohio. Duties include operations/maintenance of high power shortwave transmitters and related facilities on shift basis. Minimum qualifications: 3-years broadcast chief engineer 5 to 50 KW, or 3-years supervisor of operations/maintenance high power military transmitting plant, or equivalent. U.S. citizenship required. Salary \$15-19,000. Submit standard government application form, SF-171 to: VOA Personnel Office, Code 05-77, 330 Independence Avenue, S.W., Washington, D.C. 20547. AN EQUAL OPPORTUNITY EMPLOYER.


RIDER'S RADIO volumes 4 to 22; fair to new condition. Sams Photofacts, 200 duplicate sets. Will swap for RADEX magazines, WRTHS, Broadcasting Yearbooks, EKKO stamp material and other radio literature. Also have thousands duplicate magazines to swap for my needs. Donald Erickson, 6059-H Essex Street, Riverside, California 92504 714-687-5910.

POWER SUPPLIES — Brand New 2.5 amp. Less regulator circuit. You add. With circuit plans. \$13 PP. Telstar Ent., E. 16109 Longfellow, Spokane, WA 99216.

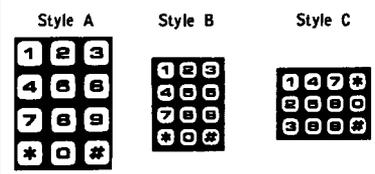NEW NEW NEW Exciting Products DATA SIGNAL AND DIGITRAN KEYBOARDS



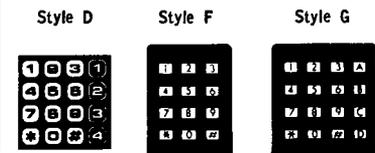2 1/4" x 3" 1 1/8" x 2 1/8" 2 1/2" x 1 1/8"



2 1/2" x 2 1/8" 2" x 2 11/16" 2 1/2" x 2 11/16"

SUB-MINIATURE TOUCH TONE ENCODERS

MODEL SME — Smallest available Touch Tone Encoder. Thin, only .05" thick, keyboard mounts directly to front of hand-held portable, while sub-miniature tone module fits inside. This keyboard allows use of battery chargers. Price \$34.50, with your choice of keyboards.

MODEL DTM — Completely self-contained miniature encoder for hand-held portables. Only 5/16" thick. Three wire connection. Automatic PTT keying optional. With your choice of keyboards. Price: **DTM - \$49.50, DTM/PTT - \$59.50.**

TOUCH TONE ENCODER WITH AUTOMATIC DIALER

MODEL 204 — Completely self-contained 12-digit Touch Tone Encoder, with one automatic telephone number. Only 5/16" thick, for use on hand-held portables. Price **\$89.50** with your choice of keyboard.

MODEL 205 — 16-digit keyboard allows for 12-digit manual encoding with automatic pushbutton keying of up to four telephone numbers. For hand-held portable operation. Price **\$109.50**, Styles D and G keyboards only.

DO-IT-YOURSELF KITS

Or, if you prefer, all components necessary to build your own encoder may be purchased "ala carte".

Your choice of any keyboard\$8.50
Digital T.T. Encoder IC 14410\$9.50
1 MHz ULTRA SMALL Crystal\$5.95
P. C. Board 0.8" x 1.2" and all resistors and capacitors\$3.50



DATA SIGNAL, INC.
2403 Commerce Lane
Albany, GA 31707
912-883-4703

NEW! IC KEYSER

The World's Greatest
Sending Device



Adjustable to Any
Desired Speed

Now available from Palomar Engineers — the new Electronic IC KEYSER. Highly prized by professional operators because it is EASIER, QUICKER, and MORE ACCURATE.

It transmits with amazing ease CLEAR, CLEAN-CUT signals at any desired speed. Saves the arm. Prevents cramp, and enables anyone to send with the skill of an expert.

SPECIAL
RADIO MODEL

Equipped with large specially constructed contact points. Keys any amateur transmitter with ease. Sends Manual, Semi-Automatic, Full Automatic, Dot Memory, Squeeze, and Iambic — MORE FEATURES than any other keyer. Has built-in sidetone, speaker, speed and volume controls, BATTERY OPERATED, heavy shielded die-cast metal case. FULLY ADJUSTABLE contact spacing and paddle tension. The perfect paddle touch will AMAZE you.

Every amateur and licensed operator should know how to send with the IC KEYSER. EASY TO LEARN. Sent anywhere on receipt of price. Free brochure sent on request.

Send check or money order. IC KEYSER \$97.50 postpaid in U.S. and Canada. IC KEYSER LESS PADDLE and non-skid base \$67.50. Add 6% sales tax in California.

Italy write i2VTT, P.O. Box 37, 22063 Cantu.

Fully guaranteed by the world's oldest manufacturer of electronic keys. ORDER YOURS NOW!

PALOMAR ENGINEERS
BOX 455, ESCONDIDO, CA 92025
Phone: (714) 747-3343

flea market

MOBILE IGNITION SHIELDING provides more range with no noise. Available most engines. Many other suppression accessories. Literature, Estes Engineering, 930 Marine Dr., Port Angeles, WA 93862.

TRANSISTORS, IC's, Communications — CB "Buy Dependability" at Low Costs. Send for your dealer confidential price list. B&D Enterprises, Box 32, Dept. 2 Mt. Jewett, PA 16740.

TELETYPE EQUIPMENT for beginners and experienced operators. RTTY machines, parts, supplies. Beginner's special: Model 15 Printer and demodulator \$139.00. Dozen black ribbons \$6.50; case 40 rolls 11/16 perf. tape \$17.50 FOB. Atlantic Surplus Sales, 3730 Nautilus Ave., Brooklyn, N. Y. 11224. Tel: (212) 372-0349.

SWTP AC30 cassette interface, excellent in performance and appearance, with manual, \$60 postpaid. Model 19/14 TELETYPE with printer, keyboard, tape distributor, typing reperfator, power supply, table, manuals — all working, many pieces nearly new. \$100, will deliver within 150 miles. Robert Boyd, Woodlawn Avenue, Kennebunkport, Maine 04046.

MOBILE BONDING STRAPS under 50¢ each. Literature, Estes Engineering, 930 Marine Drive, Port Angeles, Wash. 98362.

CASH for any Collins unit, 618T, 490T, modules, parts, accessories. Air Ground Electronics, P. O. Box 416, Kearny, N. J. 07032.

ELECTRONIC COMPONENTS, Kits, Transistors, IC's. Send stamp for catalog. Electronics Hobbies, 3421 S.E. Hawthorne Rd., Gainesville, Fla. 32601.

FERRITE BEADS: w/specification and application sheet - 10/\$1.00. Assorted PC pots - 5/\$1.00. Miniature mica trimmers, 3-40 pf. - 5/\$1.00. Postpaid. Includes latest catalog. Stamp for catalog alone. CPO Surplus, Box 189, Braintree, MA 02184.

THE "CADILLAC" of QSL's! New! Samples: \$1.00 (Refundable) — MAC'S SHACK; Box #1171-D; Garland, Texas 75040.

FREE Catalog. Solar Cells, Nicads, Kits, Calculators, Digital Watch Modules, Ultrasonics, Strobes, LEDs, Transistors, IC's, Unique Components. Chaney's, Box 27038, Denver Colo. 80227.

MODERN CODE PRACTICE. 0-22wpm on four 60 min. cassettes, \$10. Royal, P. O. Box 2174, Sandusky, Ohio 44870.

TECH MANUALS for Govt. surplus gear — \$6.50 each: SP-600JX, URM-25D, OS-8A/U, TS-173/UR. Thousands more available. Send 50¢ (coin) for 22-page list. W3IHD, 7218 Roanne Drive, Washington, DC 20021.

EXCLUSIVELY HAM TELETYPE 23rd year, RTTY Journal, articles, news, DX, VHF, classified ads. Sample 35¢. \$3.50 per year. 1155 Arden Drive, Encinitas, Calif. 92024.

FIGHT TVI with the RSO Low Pass Filter. For brochure write: Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada. MIS 3B4.

RUBBER STAMP, name/call/QTH \$2.50 p.p.d. (CA residents add tax). LWM Press, Box 22161, San Diego, CA 92122.

TELETYPEWRITER PARTS, gears, manuals, supplies, tape, toroids, SASE list. Typetronics, Box 8873, Ft. Lauderdale, FL 33310. Buy parts, late machines.

WHAT'S GNU WITH LaRue? Factory-authorized dealer for: ICOM, Regency, Standard, Cushcraft and CES Tough-Tone pads. Also stock Antenna Specialists 2-meter 5/8 wave mobile antennas and Bomar 2-meter crystals for the above radios. Mastercharge and BankAmericard accepted. For the greatest deal call or write LaRue Electronics, 1112 Grandview St., Scranton, Pennsylvania 18509. (717) 343-2124.

VERY in-ter-est-ing! Next 4 issues \$1 "Ham Trader Yellow Sheets," Sycamore, IL 60178.

Coming Events

FLINT, MICHIGAN. Greater Genesee Valley A.R.C. swap & shop Sunday September 11, 1977, 8 to 4 pm at Southwestern High School in Flint, Michigan. Tickets are \$1.00 in advance, \$1.50 at the door. Large tables at reasonable price for sellers. No Trunk Sales. Talk-in on 31/91 and 52 Simplex. For advances tickets, table reservation, and additional information, contact Jack Walters WA8UXN, 1315 Butcher Road, Fenton, Michigan 48430.

ALDELCO SEMI-CONDUCTOR SUPERMARKET

RF DEVICES			
2N3375 3W 400 MHz	5.50	2N6080 4W 175 MHz	5.40
2N3866 1W 400 MHz	.99	2N6081 15W 175 MHz	8.45
2N589 3W 175 MHz	4.75	2N6082 25W 175 MHz	10.95
2N5590 10W 175 MHz	7.80	2N6083 30W 175 MHz	12.30
2N5591 25W 175 MHz	10.95	2N6084 40W 175 MHz	16.30
2SC517	3.95	2SC1307	5.25
2SC1276	1.25	2N4427	1.35
2SC1306	4.30	2N5109	2.05

NOW NEW IMPROVED DIGITAL ALARM CLOCK KIT Hours + Minutes + Seconds displayed on six BIG 0.5 Inch 7 Segment Display LEDs. 12 hour alarm with snooze feature, plus elapsed time indicator and freeze feature. Eight pages of pictorial and instructions. NEW on board power transformer and circuitry for optional time base with simulated wood grain cabinet \$23.95
12/24 Hour Clock Kit Six big 5 LEDs freeze feature with simulated wood cabinet. \$23.95

6-digit, 40 MHz FREQUENCY COUNTER KIT with memory. 9 1/2 volt DC, .0001 accuracy. Kit complete with 110V AC plug-in and 2" x 4 1/2" x 6" cabinet. **ONLY \$99.95**
Assembled Unit Complete \$149.95

VARIABLE POWER SUPPLY KITS — 600 Ma, 5-15 VDC **\$6.95**
12-28 VDC **\$6.95** (75 cents per unit shipping)

ZENERS			
1N746 to 1N759 400 Mw ea.	.25	1N4728 to 1N4764 1 w.	.28
2N2876 RCA RF	\$10.95	CA 3028A Di. Amp.	\$1.50
MPSA14	.90	8080A	\$19.95
2N3055	.99	LM309K Volt. Reg.	1.10
MPF 102 FET	.55	2N5401	.95
2N3904 or 2N3906	10/99	21L02 1	8 for \$17.50
MJ3055	2.20	2N6103	.89
MJE 340 (2N5055)	\$1.10	2 Amp 1000 Volt Reg.	10/\$1.00
40673 RCA FET	\$15.55	2N6103 16 Amp to 220	.90
741 or 709 Pin DIP	.25	LM709 or LM741 Min. Dip.	.45
555 Timer	.75	LM741C or TO5 OP Amp.	.45
VHF Ferrite Beads	15/\$1.00	14 or 16 Pin IC Sockets	.30
200 Volt 25 Amp Bridge	\$1.50	MPSA 13 (SP55700)	.80
1N914 1N4148	15/1.00		
1N34 1N60 1N64	10 for 99		

We have 7400 series ICs send stamp for catalog.

Add 5% for shipping. Min. order \$10.00. Out of USA send Certified Check or Money Order. Include postage.

ALDELCO

2281H Babylon Tnpk., Merrick, NY 11566
(516) 378-4555

BE ON TARGET

with
JAN QUARTZ CRYSTALS
for

- CB Synthesized • CB Standard
- General Communications
- Industry • Two-Meter
- Monitor • Scanners
- Marine VHF • Amateur Bands

Dependable USA Mfg. for

- Frequency Control
- Frequency Stability
- High Performance

Write or phone for more details Send 10¢ for our latest catalog

**2400 Crystal Drive
Ft. Myers, Florida 33901
all Phones (813) 936-2397**



K9TRG

A Message from Art ... About AGL



AGL Electronics

LARRY ESSARY
President

ART HOUSHOLDER
Vice President

GORDON FOGG
Secretary-Treasurer

A.G.L. is a comparatively new company with an old-fashioned philosophy about giving our customers the best service we can deliver at the most competitive price.

Everyone at A.G.L. is a licensed ham operator with a strong electronics background, and although A.G.L. is new, we've probably met and talked with most of you at hamfests for the past many years. (We would rather not discuss how many).

We think we have accumulated one of the most complete inventories of electronics in the southwest. We've combined that with our own skills and backgrounds and created a business that we hope you will like doing business with.

By the way, if you like to "barter trade" on equipment, you are more than welcome. In fact, we encourage it.

Stop in and see for yourself, you are going to like A.G.L.

73,

Art Housholder

Art Housholder, K9TRG
Vice President

8008 Forest Lane, Suite 309 • Dallas, Texas 75234 • 214/241-6414



CALL US TODAY TOLL FREE AT 1-800-527-7418

CALL 214-241-6414 (in Texas)

LARRY WA5WWH

GORDON N5AU

MIKE WA5UOB

MIKE WB5ACM

TOM K5TM

BOB W5XC




AGL Electronics



3068 FOREST LANE, SUITE 309 • DALLAS, TEXAS 75234

RF TRANSFORMER

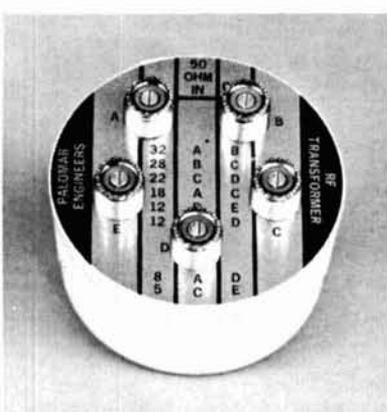

- **New! Broadband antenna matching.**
- **For all verticals and mobile whip antennas.**
- **Smaller size and higher efficiency. Only 3 1/2" diameter for full 5-Kw PEP capability.**

Here is the answer to the matching problem for vertical antennas and mobile whips. A broadband transformer that matches your 50 ohm transmitter to 32, 28, 22, 18, 12, 8, or 5 ohms. Plenty of taps to match any vertical or whip.

And with no tuning or other adjustment. The RF Transformer is completely broadband 1-30 MHz (1-10 MHz on three lowest taps). So when you change frequency within a band you need only re-tune the antenna to resonance; not fiddle with a matching network.

Also, more power goes to your antenna. The RF Transformer is more efficient than a matching network or tuner—less than 0.1 db loss.

As always, when you buy Palomar Engineers you get the best: large ferrite toroid core, teflon insulated wire, sealed epoxy-encapsulated weatherproof construction, stainless steel mounting hardware, full 2000 watt CW (5-Kw PEP) capability.

Send for free brochure.

Improve your station. Simplify your tuneup. Get better results with the new Palomar Engineers RF Transformer.

Order direct. \$42.50 postpaid U.S. and Canada. California residents add sales tax.

PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025
Phone: (714) 747-3343

flea market

MEMPHIS IS BEAUTIFUL IN OCTOBER! The Memphis ARRL-sponsored Hamfest, bigger and better than the 4,500 who attended last year, will be held at State Technical Institute, Interstate 40 at Macon Road, on Saturday and Sunday October 1 and 2. Demonstrations, displays, MARS meetings, flea market, ladies flea market, too! Hospitality room, informal dinners, XYL entertainment, many outstanding prizes. Dealers and Distributors welcome. Contact Harry Simpson W4SCF, PO Box 27015, Memphis, TN 38127 for further information.

BETTER THAN EVER — 1977 EDITION Golden Spread Hamfest and Flea Market—Holiday Inn West Amarillo, Texas Aug. 12, 13 & 14. Six big tech sessions. Commercial exhibits. Family recreation. Two Hospitality Hours. Big pre-registration prize and super Grand Prize, others. \$3.00 advance, \$4.00 at door. For info, pre-registration packet, P.O. Box 10221, Amarillo, Texas 79106.

THE LaPORTE COUNTY Summer Electronic Swapfest will be on Sunday, August 28th at the County Fairgrounds in LaPorte, Indiana, 50 miles Southeast of Chicago. Paved Midway and Indoor booths available at no charge. Good food and cold drink available. Talk-in on 37-97, 01-61, or 52 simplex. Tickets \$2.00 at the gate. Information from P.O. Box 30, LaPorte, IN 46350.

MELBOURNE, FLORIDA, SEPTEMBER 10-11. The 12th Annual Melbourne Hamfest will be held Saturday and Sunday, from 9 a.m. to 5 p.m. each day in the air-conditioned Melbourne Civic Auditorium located on Hibiscus Boulevard. Donation is \$2.50 per person. Full program includes forums, meetings, auction, swap tables, commercial exhibits, awards, prizes, etc. Contact K4HPT, 2749 Herford Road, Melbourne, FL 32935 for swap table reservations. FCC exams on Saturday, donation not needed for exams. Form 610 must be filed with FCC, Room 919, 51 S.W. First Avenue, Miami, FL 33130, not later than August 31, 1977. Hamfest talk-in on 25/85 and 52/52. Sponsored by Platinum Coast Amateur Radio Society. For more info write P.O. Box 1004, Melbourne, FL 32901.

MONTREAL HAMFEST '77. August 6 & 7, 9 AM to 6 PM. St. Lambert Arena.

BARC International Field Day, Burlington, VT. August 13-14 at the Old Lantern (same location as last year). Starts at 7AM Saturday and closes 5PM Sunday. This year's hamfest is dedicated to the memory of K1URQ. Camping at site, flea market both days, early bird registration \$3.00 (\$3.50 at door). Talk-in on 01-61. Write Burlington Amateur Radio Club, P.O. Box 312, Burlington, VT 05401 for information and advance tickets.

FLORIDA: The BOLD CITY HAMFEST sponsored by the Jacksonville Range Association will be held at the Jacksonville Beach Auditorium AUGUST 6-7. Vacation at our Hamfest — 'FLORIDA'S FRIENDLIEST'... Visit our special 'SOLAR' and 'QRPP' forums. Send request for information and tables to HAMFEST COORDINATOR, Jacksonville Range Association, P.O. BOX 10623, Jacksonville, FL 32207. For Motel reservations call RAMADA INN toll free 1-800-228-2828.

MICROCOMPUTER INTERFACING Workshop, September 15, 16, 17, 1977. A three-day workshop based on the popular 8080 microprocessor. Over 20 operating 8080 computers are available for participant use. This session will be held at the VPI & SU Extension Center in Reston, VA (Dulles Airport). For more information contact Dr. Norris Bell, V.P.I. and S.U., Blacksburg, Virginia 24061, (703) 951-6328.


DIGITAL ELECTRONICS for Automation Workshop, September 13, 14, 1977. A two-day workshop based on the small scale and medium scale TTL integrated circuits. Many hours of laboratory time with indepth lectures. This session will be held at the VPI & SU Extension Center in Reston, Va. (Dulles Airport). For more information contact Dr. Norris Bell, V.P.I. and S.U., Blacksburg, Virginia 24061, (703) 951-6328.

HAMFESTERS 43rd Annual Picnic and Hamfest, Sunday August 14, 1977, Santa Fe Park, 91st and Wolf Road, Willow Springs, Illinois, Southwest of Chicago. Exhibits for OM's and XYL's, Famous Swappers Row. Tickets at gate \$2.00, advance \$1.50. For advance tickets send check or money order to Bob Hayes W9KXW, 18931 Cedar Ave., Country Club Hills, Ill. 60477.

SARA HAMFEST Desoto, Illinois, August 22, 1977. Prizes, food, auction, no charge for flea merchants write: Nick Koenigstein, 2009 Gray Dr., Carbondale, Ill. 62901.

SOUTH DAKOTA, Signal Hill A.R.C. of the Northern Black Hills area Ham Flea Market 10:00 AM to 6:00 PM August 20, 1977 at the South Sturgis Church of Christ, Sturgis, South Dakota. Talk-in on 52/52. For further information contact: Dennis Painter WB0FYG, Box 759, Sturgis, South Dakota 57785. Phone 605-347-3087.

ROTOR PROTECTION WITH AUTOBRÄK DELAY

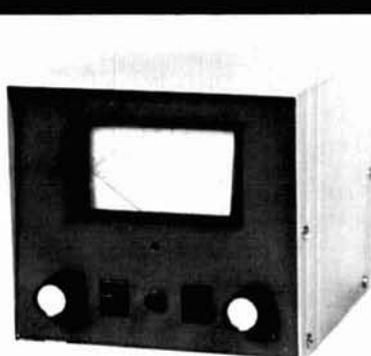

Have you had rotorator damage? Removed the rotorator? Been off the air? Waited for parts? No more! AUTOBRÄK is a complete conversion kit, including punched and finished cabinet for all HAM-M series 1, 2, and 3, rotorator control units.

AUTOBRÄK reduces the inherent problem of damaged rotorator components due to instant brake engagement. AUTOBRÄK allows the antenna array to come to a coasting stop before brake engagement, thereby reducing stress on rotorator components.

Other features include Zener regulated meter circuitry, adjustable brake delay, and handsome up-to-date styling compatible to most Ham gear. Cabinet measures 6" X 7 1/2" X 7 1/4" and is finished in two-tone gray.

Price \$39.95 Shipping and handling \$1.75 in U.S. Illinois residents add 5% sales tax.

Kampp Electronics Inc.
Box 43, Wheaton, IL 60187
312-665-3556

TEST EQUIPMENT

All equipment listed is operational and unconditionally guaranteed. Money back if not satisfied — equipment being returned must be shipped prepaid. Include check or money order with order. Prices include UPS or motor freight charges.

BOONTON 190A Q mtr 30 200mHz	...	\$425
BOONTON 202E AM FM sig gen		
54-216mHz	425
DEI TDU 430mHz video display	55
GR1001A LF sig gen 5kHz 50mHz	385
HP100ER Freq stand .05 parts/mil		
Outputs 10, 100Hz; 1, 100, 100kHz	155
HP160B (USM105) 15mHz scope with		
reg horiz, dual trace vert plugs	375
HP166B (Mil) Delay sweep for above	130
HP170A (USM140) 30mHz scope with		
reg horiz, dual trace vert plugs	475
HP175A 50mHz scope with reg		
horiz, dual trace vert plugs	565
HP185A Sampling scope to 1 GHz		
186B xstr rise time plug	585
HP202B LF Osc .5Hz 50kHz 10v out	75
HP205AG Lab audio gen .02 20kHz	195
HP212A Pulse gen .06 5kHz PRR	65
HP524D Freq counter basic range		
10Hz-10mHz extends w/plug-ins	195
HP540B Trans osc to 12.4GHz for		
use w/HP524 tyoe counters	145
HP616 Sig gen 1.8 4GHz FM CW	365
HP686 Sweep gen 8.2-12.4GHz sweep		
range 4.4mHz-4.4GHz	495
HP803A VHF Ant bridge 50-500mHz	135
SOLITRON 200A SCR tester — all		
functions w/scope output	135
Tek181 Time mark scope calib.	55
Tek190 Sig gen(const ampli) 50mHz	125
Tek536 11mHz X-Y scope — uses		
two letter series plug ins	295
Tek565 Dual beam 10mHz scope		
less plug ins (3 series)	625
TS505 Std VTVM (rf 500mHz)	65

For complete list of all test equipment send stamped, self addressed envelope

GRAY Electronics

P.O. Box 941, Monroe, Mich. 48161
Specializing in used test equipment.

7400N TTL

SN7400N	16	SN7400N	25	SN74154N	1.00
SN7401N	16	SN7401N	25	SN74155N	99
SN7402N	21	SN7402N	37	SN74156N	99
SN7403N	16	SN7403N	37	SN74157N	99
SN7404N	18	SN7404N	32	SN74158N	1.25
SN7405N	24	SN7405N	50	SN74159N	5.50
SN7406N	20	SN7406N	32	SN74160N	99
SN7407N	29	SN7407N	32	SN74161N	1.10
SN7408N	25	SN7408N	5.00	SN74162N	1.10
SN7409N	25	SN7409N	50	SN74163N	1.10
SN7410N	18	SN7410N	98	SN74164N	1.10
SN7411N	30	SN7411N	32	SN74165N	1.25
SN7412N	33	SN7412N	89	SN74166N	2.10
SN7413N	45	SN7413N	39	SN74167N	8.95
SN7414N	40	SN7414N	3.50	SN74168N	1.25
SN7415N	35	SN7415N	2.49	SN74169N	1.25
SN7417N	45	SN7417N	45	SN74170N	2.10
SN7420N	21	SN7420N	75	SN74171N	90
SN7421N	43	SN7421N	49	SN74172N	90
SN7422N	49	SN7422N	49	SN74173N	90
SN7423N	37	SN7423N	78	SN74174N	2.48
SN7424N	29	SN7424N	95	SN74175N	95
SN7425N	29	SN7425N	89	SN74176N	1.95
SN7426N	37	SN7426N	40	SN74177N	2.20
SN7427N	26	SN7427N	3.00	SN74178N	2.20
SN7428N	27	SN7428N	60	SN74179N	6.00
SN7429N	31	SN7429N	39	SN74180N	3.95
SN7430N	27	SN7430N	50	SN74181N	1.19
SN7431N	27	SN7431N	39	SN74182N	1.25
SN7432N	25	SN7432N	60	SN74183N	99
SN7433N	31	SN7433N	39	SN74184N	6.00
SN7434N	37	SN7434N	39	SN74185N	3.95
SN7435N	27	SN7435N	50	SN74186N	1.19
SN7436N	27	SN7436N	60	SN74187N	1.25
SN7437N	27	SN7437N	60	SN74188N	1.25
SN7438N	27	SN7438N	60	SN74189N	1.25
SN7439N	27	SN7439N	60	SN74190N	1.25
SN7440N	27	SN7440N	60	SN74191N	1.25
SN7441N	89	SN7441N	1.09	SN74192N	99
SN7442N	59	SN7442N	1.09	SN74193N	99
SN7443N	75	SN7443N	4.50	SN74194N	1.25
SN7444N	75	SN7444N	4.50	SN74195N	75
SN7445N	75	SN7445N	4.50	SN74196N	75
SN7446N	89	SN7446N	1.15	SN74197N	1.75
SN7447N	69	SN7447N	1.15	SN74198N	5.99
SN7448N	75	SN7448N	4.50	SN74199N	99
SN7449N	26	SN7449N	2.00	SN74200N	6.00
SN7450N	26	SN7450N	2.00	SN74201N	6.00
SN7451N	27	SN7451N	79	SN74202N	6.00
SN7452N	27	SN7452N	79	SN74203N	6.00
SN7453N	27	SN7453N	79	SN74204N	6.00
SN7454N	27	SN7454N	79	SN74205N	6.00

MANY OTHERS AVAILABLE ON REQUEST
20% Discount for 100 Combined 7400's

CMOS

CD4000	25	CD4000	65	74C04N	4.00
CD4001	25	CD4001	65	74C10N	65
CD4002	25	CD4002	65	74C20N	65
CD4003	2.50	CD4003	2.45	74C30N	65
CD4007	25	CD4007	1.90	74C43N	2.15
CD4009	59	CD4009	4.50	74C73N	1.50
CD4010	59	CD4010	2.51	74C74	1.15
CD4011	25	CD4011	2.75	74C90N	3.00
CD4012	25	CD4012	79	74C95N	2.00
CD4013	47	CD4013	79	74C107N	1.25
CD4016	56	CD4016	2.95	74C151	2.90
CD4017	1.35	CD4017	2.95	74C154	4.00
CD4019	55	CD4019	2.25	74C157	2.15
CD4020	1.49	CD4020	1.75	74C160	3.25
CD4022	1.25	CD4022	4.75	74C161	3.25
CD4023	1.25	CD4023	4.75	74C163	3.00
CD4024	1.25	CD4024	4.75	74C164	2.90
CD4025	25	CD4025	3.50	74C173	2.75
CD4026	53.99	CD4026	3.50	74C193	2.75
CD4027	69	MC14566	7.00	74C195	2.75
CD4028	1.65	CD4028	3.99	MC14544	4.90
CD4029	2.90	74C02N	55	MC14016	56

LINEAR

LM309H	80	LM309H	1.60	LM3500N	1.95
LM3010N	35	LM3010N	1.15	LM3500N	1.95
LM3015N	35	LM3015N	1.15	LM3500N	1.95
LM3020N	35	LM3020N	1.15	LM3500N	1.95
LM3500N	35	LM3500N	1.15	LM3500N	1.95

74LS00 TTL

74LS00	29	74LS00	1.99	74LS129	8.55
74LS01	29	74LS01	1.99	74LS130	1.99
74LS02	29	74LS02	1.99	74LS131	1.99
74LS03	29	74LS03	1.99	74LS132	1.99
74LS04	29	74LS04	1.99	74LS133	1.99
74LS05	29	74LS05	1.99	74LS134	1.99
74LS06	29	74LS06	1.99	74LS135	1.99
74LS07	29	74LS07	1.99	74LS136	1.99
74LS08	29	74LS08	1.99	74LS137	1.99
74LS09	29	74LS09	1.99	74LS138	1.99
74LS10	29	74LS10	1.99	74LS139	1.99
74LS11	29	74LS11	1.99	74LS140	1.99
74LS12	29	74LS12	1.99	74LS141	1.99
74LS13	29	74LS13	1.99	74LS142	1.99
74LS14	29	74LS14	1.99	74LS143	1.99
74LS15	29	74LS15	1.99	74LS144	1.99
74LS16	29	74LS16	1.99	74LS145	1.99
74LS17	29	74LS17	1.99	74LS146	1.99
74LS18	29	74LS18</			

TOROID CORES



- ✓ All the popular sizes and mixes.
- ✓ Fast Service. Same day shipment via first class mail or air.
- ✓ No minimum order.

IRON POWDER TOROIDS:

CORE SIZE	MIX 2 5-30 MHz u=10	MIX 6 10-90 MHz u=8.5	MIX 12 60-200 MHz u=4	SIZE OD (in.)	PRICE USA \$
T-200	120			2.00	3.25
T-106	135			1.06	1.50
T-80	55	45		.80	.80
T-68	57	47	21	.68	.65
T-50	51	40	18	.50	.55
T-25	34	27	12	.25	.40

RF FERRITE TOROIDS:

CORE SIZE	MIX Q1 u=125 1-70 MHz	MIX Q2 u=40 10-150 MHz	SIZE OD (in.)	PRICE USA \$
F-240	1300	400	2.40	6.00
F-125	900	300	1.25	3.00
F-87	600	190	.87	2.05
F-50	500	190	.50	1.25
F-37	400	140	.37	1.25
F-23	190	60	.23	1.10

Chart shows uH per 100 turns.

FERRITE BEADS:



\$2.00 DOZEN

WIDE BAND CHOKES



95¢ EACH

TO ORDER: Specify both core size and mix for toroids. Packing and shipping 50 cents per order USA and Canada. Californians add 6% sales tax.

Fast service. Free brochure and winding chart on request.

PALOMAR ENGINEERS
BOX 455, ESCONDIDO, CA 92025
Phone: (714) 747-3343

flea market

NEW ORLEANS HAMFEST/COMPUTERFEST at the Hilton Inn in Kenner, LA. September 24 & 25. Information on tickets, room reservations and etc. will be furnished upon request by contacting the New Orleans Hamfest/Computerfest; PO Box 10111, Jefferson, LA 70181.

ALL SAINTS AMATEUR RADIO GROUP invites you to Hamfest '77 in Saint Andrews-By-The-Sea at the Algonquin Hotel, September 2, 3, & 4. St. Andrews, New Brunswick is a very popular resort area on the border between Maine and New Brunswick with many attractions for the whole family. We have been fortunate to obtain the famous Algonquin Hotel for our Hamfest headquarters. Full info from Barb Sheppard, secretary, RR 325-8, Rothesay NB Canada E0G 2W0.

WARREN, OHIO, HAMFEST — August 21, 1977. Moved again! Trumbull K.S.U. Branch Campus on Route 45 at Warren Outerbelt. Best site in our 20 years. Bigger flea market; all close-in parking; parks & lakes nearby. Displays; talk-in; \$2 door prize registration. Arrowsigns lead from I-80; I-90; Ohio 5; 11; 45. Details? QSL: Hamfest, Box 809, Warren, Ohio 44483.

LAFAYETTE, INDIANA HAMFEST. Sunday, August 21, 1977 at Tippecanoe County Fairgrounds located at 18th St. & Teal Rd., (Indiana Highway) in Lafayette. 55 miles northwest of Indianapolis off I65. Send check or money order with SASE to WA98ZDI, Bill Bayley, 1021 Beck La., Lafayette, IN 47905 for tickets by mail.

"GREATER LOUISVILLE HAMFEST is Sunday Sept. 25, 1977 at Kentucky State Fairgrounds with exits off either I-65 or I-264. Indoor exhibitors area and Flea Market air conditioned. Also an outdoor flea market. Ladies Bingo, Meetings and Forums, refreshments available. Admission is \$2.00 adults, 12 and under free. Flea market vendors pay admission price plus \$2.00 per space indoor or \$1.00 per space outdoor. For more info or motel/camping contact Denny Schnurr, K4GOU 2415 Concord Dr., Louisville, Ky. 40217 (502-634-0619)."

35TH ANNUAL FINDLAY HAMFEST, Riverside Park, Findlay, Ohio September 11. Advance tickets are \$1.50 and \$1.00 at the gate. For tickets and additional information send S.A.S.E. to Clark Foltz, WBUN, 122 W. Hobart, Findlay, Ohio 45840.

THE OLD PUEBLO RADIO CLUB (W7GV) of Tucson, Arizona will conduct a world-wide contest over Labor Day weekend 1977. Permission has been granted for the club to operate from the South Rim of the Grand Canyon on September 2, 3, and 4, 1977. The 80, 40, 20, and 15-meter bands — SSB and CW — will be used. For additional information, contact Ian W. Thomson, W7BQN, P.O. Box 6497, Tucson, AZ 85733.

HAMFEST Zero-Beaters ARC Sunday, August 7, 1977. Washington, MO City Park — 10 AM. Write Box 24, Dut-zow, MO 63342. Flea Market, Army Mars Meeting, Prizes, Bingo, Cake Walk, Candy Scramble, fun for whole family.

L'ANSE CREUSE ARC Swap and Shop, Sunday September 18, 1977, 9 am to 3 pm, at the L'Anse Creuse High School, Mt. Clemens, Michigan. Tickets \$1.00 in advance, \$1.50 at the door. Talk-in 146.52, 146.94. Tickets and information from Harold Price, WB8QFR, 32111 Harper St., Clair Shores, Mich. 48082.

SANGAMON VALLEY Radio Club Second Annual Hamfest on Sunday, September 25th, at the Sangamon County Fairgrounds, New Berlin, Illinois, 16 miles west of Springfield. Indoor display area and covered pavilion. Exhibits, food and ladies activities. Overnight camping! Tickets: \$1 advance, \$1.50 at gate. First Prize — Wilson HT. Talk-in: 146.28/88 and 52 MHz. Information: WB9-QWR, Carole Churchill, 622 Magnolia, Rochester, IL, 62626.

CINCINNATI HAMFEST: 41st Annual — Sunday September 18, 1977 at the improved Stricker's Grove on State Route 128, one mile west of Ross (Venice) Ohio. Flea Market, Contests, Model Aircraft Flying, Food and Beverages all day. Advance Ticket Sales \$7.50 — Tickets at the Gate \$8.00 — covers everything. For further information: Lillian Abbott K8CKI, 1424 Main Street, Cincinnati Ohio 45210.

THE GRAND RAPIDS Amateur Radio Club will hold its annual Swap-N-Shop Saturday, September 17 from 8 a.m. to 4 p.m. at the Hudsonville Fairgrounds in Hudsonville, Michigan, 12 miles southwest of Grand Rapids on M-21. Talk-in on 146.52 and 16/76. \$2 donation at the gate with plenty of refreshments and free tables available.

MT. BEACON Amateur Radio Club 4th Annual Hamfest Saturday, August 6th, 9 AM to 5 PM at Stewart Field, Newburgh, N. Y., inside Hanger. Flea Market & Auction. Talk-in on 37/97 and 16/76. Rain or shine. Plenty of free parking. Admission, \$1; Tailgating, \$1; under 12 free.

Armchair Copy



Barlow XCR-30

Shortwave Listening

Our ONLY occupation is supplying everything you need to tune the mediumwave and shortwave bands—and identify what you hear. Our NEW mini-catalog details Barlow Wadley, Drake and Yaesu receivers, WORLD RADIO TV HANDBOOK, logs, receiving antennas & tuners, calibrators, FM or TV guides, AM pattern maps, QSL albums, ITU publications, RTTY displays, CONFIDENTIAL FREQUENCY LIST, clocks and all SWL books.

GILFER ASSOCIATES, INC

P.O. Box 239, Park Ridge, NJ 07656

See our **HAM MART** listings to find the **Amateur Radio** dealers nearest you.

GREENE center insulator BALUN
"Why not the very best for you!"
Price \$16 ppd USA brochure save
GREENE INSULATOR
44 Ministerial Branch, Bedford,
N. H. 03102

— PCB — PCB — PCB — PCB — PCB — PCB —
PCB — PCB — PCB — PCB — PCB — PCB — Printed Circuit Board —
ETCH-IT-YOURSELF
Printed Circuit
Kit
\$19.95
ppd.
NOW YOU CAN design and produce your own printed circuit boards.
IT'S EASY. Photo positive method. No darkroom required.
LESS THAN 2 HOURS to produce a p.c. board direct from magazine article.
KIT INCLUDES materials to make 4 p.c. boards direct from magazine article.
Add \$1 for COD. S.A.S.E. for details.
EXCEL CIRCUITS co.
4412 Fernlee 313-549-0440
Royal Oak, MI 48073




NEW LSI TECHNOLOGY FREQUENCY COUNTER


TAKE ADVANTAGE OF THIS NEW STATE-OF-THE-ART COUNTER FEATURING THE MANY BENEFITS OF CUSTOM LSI CIRCUITRY. THIS NEW TECHNOLOGY APPROACH TO INSTRUMENTATION YIELDS ENHANCED PERFORMANCE, SMALLER PHYSICAL SIZE, DRASTICALLY REDUCED POWER CONSUMPTION [PORTABLE BATTERY OPERATION IS NOW PRACTICAL], DEPENDABILITY, EASY ASSEMBLY AND REVOLUTIONARY LOWER PRICING!

SIZE:
3" High
6" Wide
5 1/2" Deep

1 3/4 LBS.
COLOR:
BLACK

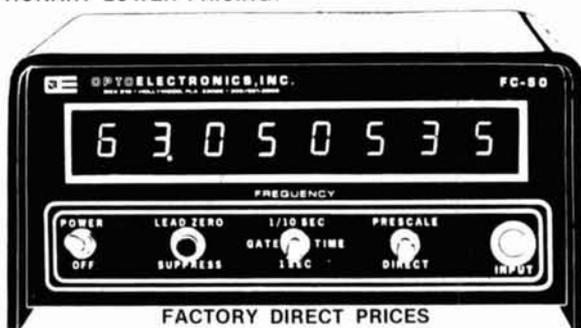

4" DIGITS!

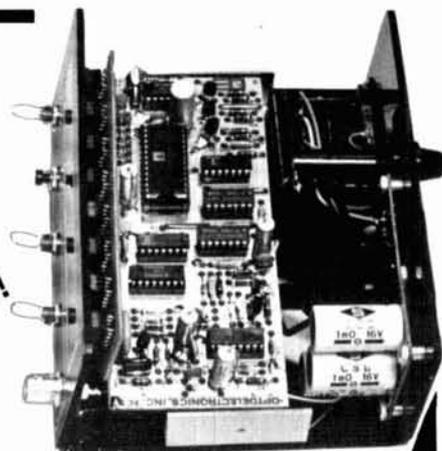

FEATURES AND SPECIFICATIONS:

DISPLAY: 8 RED LED DIGITS .4" CHARACTER HEIGHT
GATE TIMES: 1 SECOND AND 1/10 SECOND
[AUTO DEC. PT. PLACEMENT]
RESOLUTION: 1 HZ AT 1 SECOND, 10 HZ AT 1/10 SECOND.
FREQUENCY RANGE: 10 HZ TO 60 MHZ. [65 MHZ TYPICAL].
SENSITIVITY: 10 MV RMS TO 50 MHZ, 20 MV RMS TO 60 MHZ TYP.
INPUT IMPEDANCE: 1 MEGOHM AND 20 PF.
[DIODE PROTECTED INPUT FOR OVER VOLTAGE PROTECTION.]
ACCURACY: ± 1 PPM $\pm .0001\%$; AFTER CALIBRATION TYPICAL.
STABILITY: WITHIN 1 PPM PER HOUR AFTER WARM UP [0.01% XTAL]
IC PACKAGE COUNT: 8 [ALL SOCKETED]
INTERNAL POWER SUPPLY: 5.2 V DC AT 800 MA. REGULATED.
INPUT POWER REQUIRED: 8-12 VDC OR 115 VAC AT 50/60 HZ.
POWER CONSUMPTION: 4 WATTS
INPUT CONNECTOR: BNC TYPE

FACTORY DIRECT PRICES

KIT #FC-50C	60 MHZ COUNTER WITH CABINET & P.S.	\$99.85
KIT #PSL-350	350 MHZ PRESCALER [NOT SHOWN]	23.95
KIT #PSL-650	650 MHZ PRESCALER [NOT SHOWN]	29.95
MODEL #FC-50WT	60 MHZ COUNTER WIRED, TESTED & CAL.	165.95
MODEL #FC-50/600WT	600 MHZ COUNTER WIRED, TESTED & CAL.	199.95

KIT #FC-50C IS COMPLETE WITH PREDRILLED CHASSIS ALL HARDWARE AND STEP-BY-STEP INSTRUCTIONS. WIRED & TESTED UNITS ARE CALIBRATED AND GUARANTEED. PRESCALERS WILL FIT INSIDE COUNTER CABINET.

PLEXIGLAS CABINETS

Great for Clocks or any LED Digital project. Clear-Red Chassis serves as Bezel to increase contrast of digital displays.

CABINET I

3"H, 6"W, 5 1/2"D Black, White or Clear Cover

CABINET II


2 1/2"H, 5"W, 4"D \$6.50 ea.

RED OR GREY PLEXIGLAS FOR DIGITAL BEZELS
3"x6"x1/8" 95¢ ea 4/23

SEE THE WORKS Clock Kit Clear Plexiglas Stand

- 6 Big 4" digits
- 12 or 24 hr. time
- 3 set switches
- Plug transformer
- all parts included

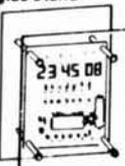Plexiglas is Pre-cut & drilled
Kit #850-4CP
Size: 6"H, 4 1/2"W, 3"D



A SUPER CLOCK!

\$23.50 ea. 2/45.

60 HZ.

XTAL TIME BASE
Will enable Digital Clock Kits or Clock-Calendar Kits to operate from 12V DC.
1"x2" PC Board
Power Req. 5-15V (2.5 MA. TYP.)
Easy 3 wire hookup
Accuracy: ± 2 PPM
#TB-1 (Adjustable)
Complete Kit \$4.95
Wir & Cal \$9.95

SPECIAL PRICING!

PRIME - HIGH SPEED RAM
21L02-3 400 NS

LOW POWER - FACTORY FRESH
1-24 \$1.95 ea 100-199 \$1.60 ea
25-99 1.75 ea 200-499 1.45 ea
OVER 500 PCS. \$1.39 ea.

5-DIGIT LED CLOCK CALENDAR KIT DATE-TIME-SNOOZE ALARM & MORE... KIT 7001

FOR THE BUILDER THAT WANTS THE BEST. FEATURING 12 OR 24 HOUR TIME - 29-30-31 DAY CALENDAR, ALARM, SNOOZE AND AUX. TIMER CIRCUITS

Will alternate time (8 seconds) and date (2 seconds) or may be wired for time or date display only, with other functions on demand. Has built-in oscillator for battery back-up. A loud 24 hour alarm with a repeatable 10 minute snooze alarm, alarm set & timer set indicators. Includes 110 VAC/60Hz power pack with cord and top quality components through-out.

KIT - 7001B WITH 6 - 5" DIGITS	\$39.95
KIT - 7001C WITH 4 - 6" DIGITS & 2 - 3" DIGITS FOR SECONDS	\$42.95
KIT - 7001X WITH 6 - 6" DIGITS	\$45.95



KITS ARE COMPLETE (LESS CABINET)

ALL 7001 KITS FIT CABINET I AND ACCEPT QUARTZ CRYSTAL TIME BASE KIT # TB-1

PRINTED CIRCUIT BOARDS for CT-7001 Kits sold separately with assembly info. PC Boards are drilled Fiberglass, solder plated and screened with component layout.

Specify for 7001

B, Cor X - \$7.95

AUTO BURGLAR ALARM KIT

AN EASY TO ASSEMBLE AND EASY TO INSTALL ALARM PROVIDING MANY FEATURES NOT NORMALLY FOUND. REMOTE ALARM HAS PROVISION FOR POS & GROUNDING SWITCHES OR SENSORS. WILL PULSE HORN RELAY AT 1/2 RATE OR DRIVE SIREN. KIT PROVIDES PROGRAMMABLE TIME DELAYS FOR EXIT, ENTRY & ALARM PERIOD. UNIT MOUNTS UNDER DASH - REMOTE SWITCH CAN BE MOUNTED WHERE DESIRED. CMOS RELIABILITY RESISTS FALSE ALARMS & PROVIDES FOR ULTRA DEPENDABLE ALARM. DO NOT BE FOOLED BY LOW PRICES! THIS IS A TOP QUALITY COMPLETE KIT WITH ALL PARTS INCLUDING DETAILED DRAWINGS AND INSTRUCTIONS OR AVAILABLE WIRED AND TESTED.



KIT #ALR-1 \$9.95
#ALR-1WT WIRED & TESTED \$19.95

VARIABLE REGULATED 1 AMP POWER SUPPLY KIT

- VARIABLE FROM 4 TO 14V
- SHORT CIRCUIT PROOF
- 723 IC REGULATOR
- 2N3055 PASS TRANSISTOR
- CURRENT LIMITING AT 1 Amp

KIT IS COMPLETE INCLUDING DRILLED & SOLDER PLATED FIBERGLASS PC BOARD AND ALL PARTS (LESS TRANSFORMER) KIT #PS-01 \$8.95

TRANSFORMER 24V CT will provide 300MA at 12V and 1 Amp at 5V. \$3.50

MOBILE LED CLOCK

12/24 HR 4" DIGITS!

MODEL 12 VOLT AC or DC POWERED #2001

- 6 JUMBO 4" RED LED'S BEHIND RED FILTER LENS WITH CHROME RIM
- SET TIME FROM FRONT VIA HIDDEN SWITCHES • 12/24-Hr. TIME FORMAT
- STYLISH CHARCOAL GRAY CASE OF MOLDED HIGH TEMP. PLASTIC
- BRIDGE POWER INPUT CIRCUITRY - TWO WIRE NO POLARITY HOOK-UP
- OPTIONAL CONNECTION TO BLANK DISPLAY [Use When Key Off in Car, Etc.]
- TOP QUALITY PC BOARDS & COMPONENTS - INSTRUCTIONS.
- MOUNTING BRACKET INCLUDED

KIT #2001
COMPLETE KIT \$29.95 3 OR MORE \$27.95 115 VAC \$250
[LESS 9V. BATTERY] EA. MORE EA. #AC-1 Power Pack EA.

ASSEMBLED UNITS WIRED & TESTED
ORDER #2001 WT [LESS 9V. BATTERY] \$39.95 1 OR MORE \$37.95 EA. MORE EA.

Wired for 12-Hr. Op. if not otherwise specified.



OPTOELECTRONICS, INC.

BOX 219 • HOLLYWOOD, FLA. 33022 • (305) 921-2056
STORE: 823 S. 21 AVE.

master charge

AMERICAN

ORDER BY PHONE OR MAIL
COD ORDERS WELCOME

Orders Under \$15 Add \$1.00 Handling
Fla. Res. Please Add 4% Sales Tax.

WE PAY ALL SHIPPING IN CONTINENTAL USA - OTHERS ADD 5% [10% FOR AIRMAIL]



BOOKS BY PHONE CALL TOLL FREE 800-258-5353

Almost all popular
Amateur Radio Books
available for immediate
shipment.

HAM RADIO
GREENVILLE, NH 03048

Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Ham Radio Holland
MRL Electronics
Postbus 88
NL 2204 Delft
Holland

Ham Radio Belgium
Sterehouse
Brusselssteenweg 416
B-9218 Gent
Belgium

Ham Radio Italy
S.T.E. Via Maniaco 15
I-20134 Milano
Italy

Ham Radio Canada
Box 114, Goderich
Ontario, Canada N7A 3Y5

Ham Radio Switzerland
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Ham Radio Europe
Box 444
S-194 04 Upplands Vasby
Sweden


Ham Radio France
Christiane Michel
F-89117 Parly
France

Ham Radio UK
P.O. Box 63, Harrow
Middlesex HA3 6HS,
England

Ham Radio Germany
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Holland Radio
143 Greenway
Greenside, Johannesburg
Republic of South Africa

More Economical RTTY

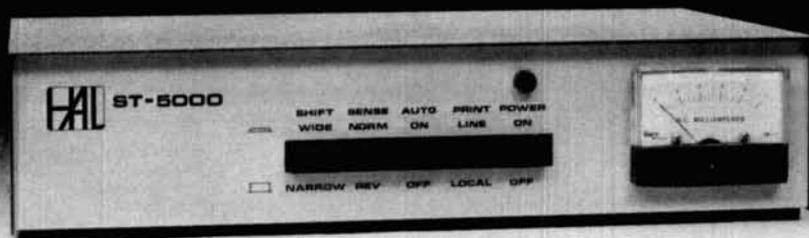

The ST-5000 from HAL

The HAL ST-5000 sets the pace for an economical demodulator/keyer for radio-teletype (RTTY). All the features you need for reception and transmission of HF and VHF RTTY are here.

The demodulator features a hard-limiting front end, active filter discriminator, and active detector circuitry for wide dynamic range. Autostart and motor control circuitry make for easy VHF and HF autostart operation.

Convenient front panel switches are provided for 850 and 170 Hz shift, normal or reverse sense, autostart on/off, print - line or local, and power on/off. 425 Hz press transmissions may also be copied with the ST-5000. High voltage 60 ma. loop output as well as low level RS-232 compatible output are provided by the demodulator.

The audio keyer section of the ST-5000 generates stable, phase-coherent audio tones. Transmission is a simple matter of applying these tones to your HF SSB or VHF FM transmitter.

The ST-5000 is housed in an attractive blue and beige cabinet and is backed by the HAL Communications one year warranty.

For complete specs on the HAL ST-5000, write or call HAL today.

\$275.00



HAL Communications Corp., Box 365, 807 E. Green St.
Urbana, Illinois 61801 • Telephone (217) 367-7373

ICOM — Simply The Best!



*** PACKAGE DEALS ***

- #1. Buy an IC-245 at the regular price **F** and get the **TOUCH TONE HANDSET SET FREE.**
E IC-245 Ready to Go \$499.00
- #2. **HANDSET ONLY** \$79.00
Requires wiring accessory socket on IC-245 & IC-22S.
- #3. **TOUCH TONE HANDSET** with IC-22S \$299.00
Handset 30.00
You pay only **\$329.00**
Ready to go.

Immediate Delivery From Stock.


Write or call for special prices on ICOM Gear without Touch Tone Handsets.

Add \$5.00 for Base Recepticle

801-533-0101

24-hour Message Recorder
801-486-7784

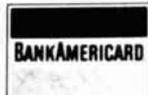UTAH FM SALES, INC.
1588 MAJOR STREET
SUITE #202
SALT LAKE CITY, UTAH 84115




COMPACT POWER!

KLM ANTENNAS

HF Excellent mechanical designs feature multiple driven elements and optimized spacing for wide band operation with low VSWR, clean patterns, maximum power gains.

VHF

UHF

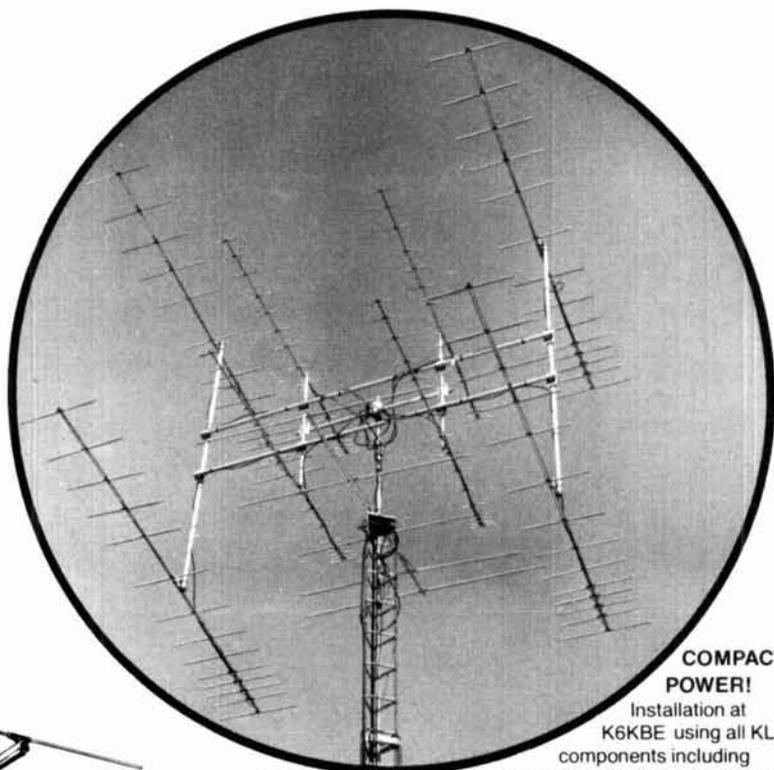


COMPACT POWER!

Installation at K6KBE using all KLM components including 6 meter beam, 144 and 432 MHz arrays, KR-400 and KR-500 rotators.

144 MHz.

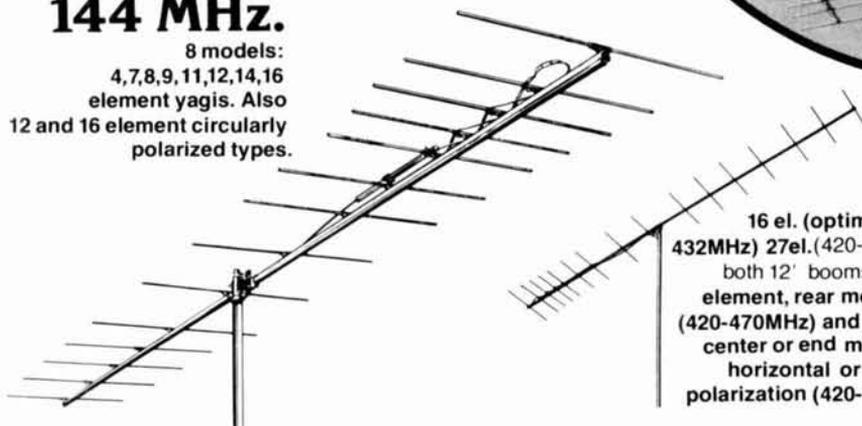8 models: 4,7,8,9,11,12,14,16 element yagis. Also 12 and 16 element circularly polarized types.



70 CM 4 models:

16 el. (optimized for 432MHz) 27el. (420-450MHz) both 12' booms. Also 6 element, rear mountable (420-470MHz) and 14 el. for center or end mounting, horizontal or vertical polarization (420-470MHz)

One of the most versatile series available. Included are rear mount types that can be arranged for either horizontal or vertical polarization. A 16 element long boom type (optimized for 432MHz, ± 2 MHz), really pours out the power! Four or eight are often stacked for EME or DX using efficient KLM couplers.


A broad-band antenna to meet every need; each with contest winning gain and flat VSWR across the entire amateur band. For serious moon bounce (EME) and tropho work, "stack" 'em, using available KLM baluns and couplers. Built tough... with weather resistant 6063-T832 aluminum... stainless steel hardware.

ANTENNA COUPLERS/POWER DIVIDERS

Several broad band models are available for stacking VHF or UHF beams. These replace two, quarter wave matching cables, barrels and "T" needed to interconnect two or four antennas. Phasing and match to 50 ohm line is automatic. Will handle 2KW p.e.p. with ease.

50 MHz. 3 models:

5,8 and 11 elements.

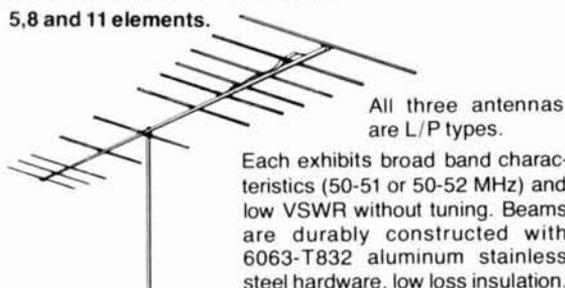

All three antennas are L/P types.

Each exhibits broad band characteristics (50-51 or 50-52 MHz) and low VSWR without tuning. Beams are durably constructed with 6063-T832 aluminum stainless steel hardware, low loss insulation.

STACKING FRAMES.

"H" frames suitable for antenna stacking are available on special order. See top photograph for a typical installation.

ELEVATION ROTATOR KR-500



Provides 180° boom rotation. Heavy duty (used on array illustrated). Rotation, 180°/1 min. Motor disc brake holds to 1750 inch-pounds. Holds booms 1.25 to 1.625"D, masts to 1.5-2.5"D. Weather resistant. Attractive direction indicator. 115VAC.

AZIMUTH ROTATOR KR-400



Medium duty, supports 400 lbs. Ideal for long boomers, HF tri-banders, used in array shown. Motor disc brake holds to 1750 inch-pounds. Has limit switches. Rotation, 360°/1 min. Accommodates 1.5-2.5"D masts. Direction indicator. 115VAC. 50/60 Hz.

HEAVY-DUTY ROTATOR HD-1500



Use for high torque, heavy systems.

Also 3.5, 7, 14, 21, 28 MHz ham antennas and a full line of commercial log-periodic types.

KLM electronics, inc.

At your dealer. Write for catalog.

17025 Laurel Road, Morgan Hill, CA 95037 (408) 779-7363

LUNAR

proudly announces a NEW 2-Meter AMPLIFIER/PREAMPLIFIER the 2M10-80P

The Marriage Between Power Amplifiers and Receiving Preamplifiers is Finally Consummated! Lunar Offers an SCS 2M10-80L Power Amp and an "Anglelinear" 144W Preamp in a Single, Functionally-Designed Package that Combines Two Superior Products Into One!



Features:


- ★ Ten watts input — eighty watts output
- ★ Harmonic reduction exceeds -60 dB to meet FCC R&O 20777 Specifications
- ★ Variable T-R Delay for CW/SSB
- ★ Functionally-Designed Extrusion Includes Mounting Lip
- ★ Preamplifier Selectable Independently of Power Amplifier
- ★ Automatic T-R Switching of Amp & Preamp
- ★ Preamp gain: Nominally 11 dB
- ★ Noise Figure: Nominally 2.5 dB (Including Relay Losses)
- ★ Remote Control Head Available Separately

Introductory Price: Lunar Model 2M10-80P \$189.95

Please add \$3.00 shipping and handling

Also From Lunar:

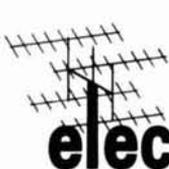- Available Now: Complete Line of Separate Preamplifiers
50-450 MHz
- Coming Soon: Complete Line of 50-450 MHz Amp/Preamp
Combinations
Preamps Through 2.5 GHz
Transverter Systems 50 MHz-2.5 GHz
Converters and Filters 28 MHz-2.5 GHz



P. O. BOX 82183
SAN DIEGO, CA 92138
714-222-9518
Louis N. Anciaux WB6NMT

California residents add 6%. Order today at your dealer or direct from:

STEP UP TO TELREX

WITH A

TELREX "BALUN" FED—"INVERTED-VEE" KIT

THE IDEAL HI-PERFORMANCE

INEXPENSIVE AND PRACTICAL TO INSTALL LOW-FREQUENCY
MONO OR MULTIPLE BAND, 52 OHM ANTENNA SYSTEM



Telrex "Monarch" (Trapped) I.V. Kit
Duo-Band / 4 KWP I.V. Kit \$63.50
Post Paid Continental U.S.

Optimum, full-size doublet performance, independent of ground conditions! "Balanced-Pattern", low radiation angle, high signal to noise, and signal to performance ratio! Minimal support costs, (existing tower, house, tree). A technician can resonate a Telrex "Inverted-Vee" to frequency within the hour! Minimal S/W/R is possible if installed and resonated to frequency as directed! Pattern primarily low-angle, Omni-directional, approx. 6 DB null at ends! Costly, lossy, antenna tuners not required! Complete simplified installation and resonating to frequency instructions supplied with each kit.

For technical data and prices on complete
Telrex line, write for Catalog PL 7 (HRH)



IF WE WERE YOU



MODEL 6154 TERMALINE®

I'D BUY FROM US

YOUR INQUIRY OR ORDER WILL
GET OUR PROMPT ATTENTION

AUTHORIZED

BIRD DISTRIBUTOR

WEBSTER COMMUNICATIONS

115 BELLARMINE

ROCHESTER, MI 48063

313-375-0420



NEW

DIGITAL CLOCK

with
10 MINUTE
TIMER

6 digits - 12/24 hour

Here's the kit everyone has been asking for!
Never fail to identify your station again. And

it's easy to use, just tap timer button to start, 9 minutes later the display will flash on and off to alert you. Reset it by simply touching the timer button or it will reset itself automatically after two minutes! Other features are: jumbo .4" LED readouts, durable extended aluminum case available in 5 colors, plug transformer, Polaroid lens filter, time set buttons, finest quality PC boards and super instructions. You get all parts - no extras are needed, unlike some of the kludges our competitors offer! Colors available: gold, black, silver, bronze, blue (specify). Size: 4.25" x 1.5" x 1.5".

Clock Kit with 10 min. timer, DC-10 \$25.95
Regular 12/24 hr clock kit 22.95
Alarm clock, 12 hr only, DC-8 24.95
Kits are also available fully assembled and tested, just add \$10 to kit price.



FM Wireless Mike Kit \$2.95

Transmit up to 300' to any FM broadcast radio. Sensitive mike input requires crystal ceramic or dynamic mike. Runs on 3 to 9 V.

TONE DECODER KIT

A complete tone decoder on a single PC Board. Features: 400-5000 Hz adjustable frequency range, voltage regulation, 567 IC. Useful for touch-tone decoding, tone burst detection, FSK demod, signaling, and many other uses. Use 7 for 12 button touchtone decoding. Runs on 5 to 12 volts.

Complete Kit, TD-1 \$4.95

LED BLINKY KIT

A great attention getter which alternately flashes 2 Jumbo LEDs. Use for name badges, buttons, or warning type panel lights. Runs on 3 to 9 volts.

Complete Kit \$2.95

SUPER-SNOOP AMPLIFIER

A super-sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as a general purpose test amplifier. Full 2 watts of output, runs on 6 to 12 volts, uses any type of mike. Requires 8-45 ohm speaker.

Complete Kit, BN-9 \$4.95

MUSIC LIGHTS KIT

See music come alive! 3 different lights flicker with music or voice. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable, and drives up to 300 watts. Great for parties, band music, nite clubs and more.

Complete Kit, ML-1 \$7.95

SIREN KIT

Produces upward and downward wail characteristic of police siren. 5 Watts audio output, runs on 3-9 volts, uses 8-45 ohm speaker.

Complete Kit, SM-3 \$2.95

CODE OSCILLATOR KIT

Powerful 1 watt audio oscillator of approx. 1 kHz, good for many uses. Great for warning alarm, battery checker, voltage indicator and code oscillator.

Complete Kit, CPO-1 \$2.50

POWER SUPPLY KIT

Complete triple regulated power supply provides variable ± 15 volts at 200 mA and +5 volts at 1 Amp. 50 mV load regulation good filtering and small size. Kit less transformers. Requires 6-8 V at 1 Amp and 18 to 30 VCT.

Complete Kit, PS-3LT \$6.95

DECADE COUNTER

PARTS KIT

INCLUDES \$3.50

- 7490A decade counter
- 7475 latch
- 7447 LED driver
- LED readout
- Current limit resistors

Complete with instruction and details on how to build an easy, low cost freq. counter.

R8

CAR CLOCK 12/24 HR 6 DIGIT \$25.95

- High accuracy (1 minute/month)
 - Big .4" LED display
 - Special circuit suppress all voltage spikes and transients
 - Same case as illustrated above
 - Display blanks with ignition off
 - Reverse polarity protected
- Complete Kit, DC-7 \$25.95
Assembled and calibrated ... 35.95

CALENDAR ALARM CLOCK 6 Digit LED 12/24 Hour

Has every feature one could ever ask for. Kit includes everything except case, build it into wall, station or even car! **FEATURES:**

- 6 Digits, .5" High LED
- Calendar shows mo./day
- True 24 Hour Alarm
- Battery back up with built in on chip time base
- 12/24 Hour Format
- Snooze button
- 7001 chip does all!

Complete Kit, less case, DC-9 \$34.95

600 MHz PRESCALER \$59.95



Assembled and tested. Extend the range of your counter to 600 MHz. Works with all counters. Available in kit form for \$44.95. Specify $\div 10$ or $\div 100$ with order.

30 WATT 2 Meter Power Amp

The famous RE class C power amp now available mail order! Four Watts in for 30 Watts out, 2 in for 15 out, 1 in for 8 out. Incredible value, complete with all parts, instructions and details on T-R relay. Fully stable, output short proof, infinite VSWR protected! Case not included.

Complete Kit \$22.95

COMING SOON: VIDEO TERMINAL KIT SEND FOR DETAILS \$149.95

TTL	LINEAR	REGULATOR	TRANSISTORS
74500 .35	555 .50	309K .99	NPN 2N3904 type 10/\$1.00
745112 .75	556 .75	309H .99	PNP 2N3906 type 10/\$1.00
7447 .79	567 1.75	340K-12 1.25	NPN Power Tab 40W 3/\$1.00
7473 .35	1458 .50	7805 .99	PNP Power Tab 40W 3/\$1.00
7475 .50	LED DRIVER	7812 .99	FET MPF-102 type 3/\$2.00
7490A .55	75491 .50	7815 .99	UJT 2N2646 type 3/\$2.00
74143 3.50	75492 .50	7818 .99	2N3055 NPN Power .75

DIODES: 1KV,2.5A 5/\$1.00 100V,1A 10/\$1.00 1N914A type 50/\$2.00

LED DISPLAYS	741 OP-AMP SPECIAL Factory prime mini dip with both Xerox and 741 part numbers 10 for \$2.00	SOCKETS 14 PIN 5/\$1.00 16 PIN 5/\$1.00 24 PIN 2/\$1.00 40 PIN 3/\$2.00	FERRITE BEADS with info and specs 15/\$1.00 6 hole Balun Beads 5/\$1.00	SOCKET KIT Assortment of 12 most used IC sockets. Good to have around the shop. \$1.95
--------------	--	---	---	---

FND 3594" C.C.75	8080A \$18.95 Factory Prime - includes FREE socket!	60 Hz XTAL TIME BASE ● Runs on 5-15 VDC ● Low current (2.5 ma) ● Operate clocks in car, boat, plane ● 1 minute/month accuracy Kit, TB-7 ... \$5.50 Assembled & Calibrated ... \$9.95
---------------------------------	--	--

CHEAP CLOCK KIT \$9.95 DC-4 Features: ● 6 digit .4" LED ● 12 or 24 format	Does not include board or transformer	PC Board \$2.95 Transformer \$1.49	Dealers Write for our wholesale price list. Hi M-D
--	---------------------------------------	---------------------------------------	--

ramsey electronics
P.O. Box 4072 Rochester NY 14610
(716) 271-6487

TELEPHONE ORDERS WELCOME

Satisfaction guaranteed or money refunded. COD, add \$1.00. Orders under \$10.00 add \$.75. NY residents add 7% tax.

Master Charge
BankAmericard

TRANSFORMERS

American made, 115V Primaries:

6.3V, 1 Amp, Shielded	\$1.80 ea.
12V, 250 mils, for P. C. Board.	\$1.66 ea.
12 volt 1/2 amp.	\$2.05
12V 1.2 Amp	\$2.84
12V, 3 Amp	\$4.48
36V CT, 1A; 14V CT, 400 Ma	\$4.20 ea.
44V CT — 1A; 6.3V, 1/4 amp tap	\$3.47 ea.
48V CT — 1A; 6.3V, 1/4 amp tap	\$3.46 ea.

NEW ITEM

Thordarson DC to DC converter power supply transformer — for 12 Volt DC service. (Instruc. & schematic incl.)
TR 91 — output 450V, 120W, 270MA DC. \$9.88 ea.

TR-98 — output 1500V, 12MA DC. \$8.15 ea.

9-PIN "TO" IC Socket, gold pit. 6/\$1.08

3000 MFD @ 20V Capacitors. Same size as above. 80¢ ea. or 3/\$2.00

SEND STAMP FOR BARGAIN LIST
PENNSYLVANIA RESIDENTS - ADD 6%
ALL ITEMS PPD. USA

1/2 WATT, 5% Resistors, Full leads, imported. 75, 220, 390, 430, 820, 1.5K, 2K, 10K, 15K, 22K, 39K, 82K, 120K, 220K, 270K. 33/\$1.66

One Value 100/\$4.15
Assorted Values 100/\$4.55

NEW P.C. POTS — 1/4W by Piher. Vert. Mt., 250Ω w/slot drive; Hoz. Mt. 100Ω & 10K, hex slot drive. 20¢ ea. - 6/\$1.00

"S" UNIT METER — Pearce-Simpson #3701-004. Scale 0, 3, 5, 7, 9, +10, +30. 500μA rating. 1 1/2"W x 1 1/4"H x 3/4"D. \$2.95 each

3000 MFD @ 30 Volt Capacitors.
1" Dia. x 3" — 90¢ ea. or 3/\$2.25

UNPOTTED TOROIDS — Center tapped.
88 MHY - 5 oz. - 5/\$2.95; 9 oz. - 5/\$3.49
44 MHY - 5/\$3.95

m. weinschenker
electronic specialties-BOX 353, IRWIN, PA 15642

NO COMPROMISE!



ANTENNA BALUN

- Full 2KW, 3 to 30 MHz, 1:1 or 1:4 ratios.
- Special TEFLON insulated wire windings.
- May be used with tuned matching lines or antenna tuners. Withstands accidental high VSWR, great for antenna experimentation.
- Built-in hang-up and dipole center insulator.
- Totally weatherproofed by encapsulation, silver plated SO-239 coax connector input, and brass terminal output.

Balance your antenna, end radiation from coax, improve beam patterns, and lower receiving noise pick-up.

Free literature upon request.

Available at your dealer
or order direct:

ONLY \$11.45 ppd. (specify ratio)

K. E. ELECTRONICS

2931 Unit F West Central Ave.
Santa Ana, Calif. 92704

QUALITY KENWOOD TRANSCEIVERS ... from KLAUS RADIO

The TS-820 is the rig that is the talk of the Ham Bands. Too many built-in features to list here. What a rig and only \$830.00 ppd. in U.S.A. Many accessories are also available to increase your operating pleasure and station versatility.



TS-820
160-10M TRANSCEIVER

Super 2-meter operating capability is yours with this ultimate design. Operates all modes: SSB (upper & lower), FM, AM and CW. 4 MHz coverage (144 to 148 MHz). The combination of this unit's many exciting features with the quality & reliability that is inherent in Kenwood equipment is yours for only \$599.00 ppd. in U.S.A.



TS-700A
2M TRANSCEIVER

Guess which transceiver has made the Kenwood name near and dear to Amateur operators, probably more than any other piece of equipment? That's right, the TS-520. Reliability is the name of this rig in capital letters. 80 thru 10 meters with many, many built-in features for only \$629.00 ppd. in U.S.A.



TS-520
80-10M TRANSCEIVER

This brand new mobile transceiver (TR-7400A) with the astonishing price tag is causing quite a commotion. Two meters with 25W or 10W output (selectable), digital read-out, 144 through 148 MHz and 800 channels are some of the features that make this such a great buy at \$399.00 ppd. in U.S.A.



TR-7400A
2M MOBILE TRANSCEIVER

Send SASE NOW for detailed info on these systems as well as on many other fine lines. Or, better still, visit our store Monday thru Friday from 8:00 a.m. thru 5:00 p.m. The Amateurs at Klaus Radio are here to assist you in the selection of the optimum unit to fulfill your needs.

KLAUS RADIO Inc.

8400 N. Pioneer Parkway, Peoria, IL 61614
Jim Plack W9NWE — Phone 309-691-4840


TRAGIC WASTE OF RF

could be your fate as precious watts zig-zag round the world to shower just a little — or little or none — on that hoped for DX station. BUT WE HAVE AN ALTERNATIVE — THE JOYSTICK VFA (Variable freq. ant.), which gives low angle, omnidirectional, harmonic free radiation on all bands 160 thru 10 (+ MARS and receive on all BC & SW). Stalwarts W6TYP and G4DJY achieved notable results in contests — just to mention two of the many who have sent glowing reports of the VFA in use, often in poor QTH and/or under QRP. 250W P.E.P. &/or Receiving Only
SYSTEM 'A' \$75.00
SYSTEM 'J' \$99.00
500W P.E.P. &/or Improved Q Factor Receive
Air Mail cost included
(each system 3 sections easily assembled to make unit 7' 6" long. Matching ATU.) Not only will you save space but you will save \$\$\$ at present low exch. rate and by buying direct UK manuf. Rush your order — Mastercharge or check, or ask for brochure.

PARTRIDGE (HR) ELECTRONICS LTD.

BROADSTAIRS, KENT, ENGLAND
G3CED TEL THANET 62535 G3VFA

WANTED FOR CASH

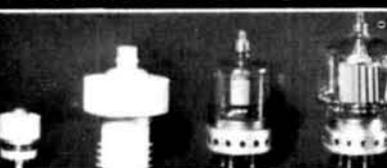

4CX150	4CX1000	4-65	4-250
4CX250	4CX1500	4-125A	4-400
4CX300A	4CX3000		4-1000
4CX350A	4CX5000		304TL
	4CX10,000		
	5CX1500		

Other tubes and Klystrons also wanted.

The Ted Dames Company


308 Hickory St. Arlington, N.J. 07032
(201) 998-4246 Evenings (201) 998-6475

Vhf engineering

BLUE LINE RF Amplifiers

Don't sacrifice maximum power output and high efficiency for linearization. The BLUE LINE offers you the best of both designs. The BLUE LINE amplifiers are engineered using the latest state of the art stripline technology. This design technology means efficient broad band output with a very high degree of mechanical stability.

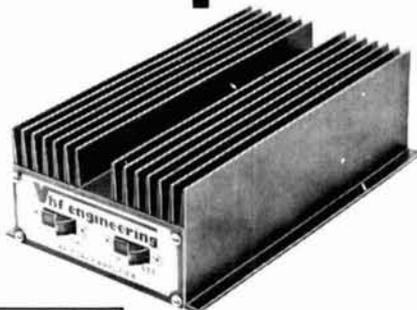Vhf engineering is the only name you have to remember when it comes to VHF or UHF amplifiers, just look at the variety available.



MODEL	BAND	EMISSION	POWER INPUT	POWER OUTPUT	WIRED AND TESTED PRICE
BLC 10/70	144 MHz	CW-FM-SSB/AM	10W	70W	139.95
BLC 2/70	144 MHz	CW-FM-SSB/AM	2W	70W	159.95
BLC 10/150	144 MHz	CW-FM-SSB/AM	10W	150W	259.95
BLC 30/150	144 MHz	CW-FM-SSB/AM	30W	150W	239.95
BLD 2/60	220 MHz	CW-FM-SSB/AM	2W	60W	159.95
BLD 10/60	220 MHz	CW-FM-SSB/AM	10W	60W	139.95
BLD 10/120	220 MHz	CW-FM-SSB/AM	10W	120W	259.95
BLE 10/40	420 MHz	CW-FM-SSB/AM	10W	40W	139.95
BLE 2/40	420 MHz	CW-FM-SSB/AM	2W	40W	159.95
BLE 30/80	420 MHz	CW-FM-SSB/AM	30W	80W	259.95
BLE 10/80	420 MHz	CW-FM-SSB/AM	10W	80W	289.95

FEATURES

- High efficiency means low current drain.
- Broad band design (no tuning).
- Direct 12 volt DC operation.
- Indicator lamps for On/Off and FM/SSB.
- Relay switching (allows you to put amplifier in or out of circuit at the flip of a switch).
- Insertion loss of less than 1 dB.
- One year limited warranty on parts and labor.

Don't forget our popular PA-2501 and PA-4010 at \$74.95 (wired and tested) \$59.95 (Kit)

WANT TO BRING YOUR AMPLIFIER INDOORS?

LOOK AT THESE POWER SUPPLIES!

- Over-voltage protection crowbar.
- Electrostatic shield for added transient surge protection.
- A foldback output limiter operates for loads outside of the operating range.
- Isolation from ground. The circuit is isolated from the case and ground.
- 115/220 volt input — 50/60 cycle.
- Units are factory wired for 115 volt AC, 50/60 cycle power.
- A simple jumper will reconfigure the input for 220 volt AC, 50/60 cycles.
- Temperature range — operating: 0° to +55° C.
- Black anodized aluminum finish.

PS-25M WITH CURRENT METERS



Recommended for:


BLC 10/70 BLD 2/60 BLE 30/80
BLC 2/70 BLD 10/60 BLE 10/80

Voltage Output: adjustable between 10-15V
Load Regulation: 2% from no load to 20 a
Current Output:

25 amps intermittent (50% duty cycle)
Ripple: 50 mV at 20 amps
Weight: 22-1/2 pounds
Size: 12-1/4" x 6-3/4" x 7-1/2"

PS-25M Kit \$149.95
PS-25M Wired & tested . \$169.95

PS-15C LOW COST

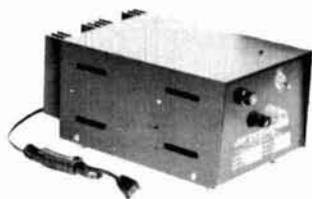

Recommended for:

BLE 10/40 BLE 2/40

Voltage Output: adjustable between 12-14V
Load Regulation: 2% from no load to 10 amps

Current Output:
15 amps intermittent (50% duty cycle)

Ripple: 50 mV at 10 amps
Weight: 13 pounds
Size: 11-1/4" x 5-1/2" x 4-3/4"

PS-15C Kit \$79.95
PS-15C Wired & tested . \$94.95

PS-3012 COMMERCIAL



Recommended for:

BLC 3/150
BLC 30/150
BLD 10/120

Output Voltage: Adjustable, 11-15 VDC
Output Current: 30 amps (50% duty cycle)
Regulation: Better than 2 percent
Output Ripple: 50mV pk-pk maximum
Temperature Range: 0°-60° C operating
Overvoltage Protection: Built in OVP crowbar

Overcurrent Protection: Foldback current limiting at 30 amps

Short Circuit Current: 2 amps maximum
Input Voltage: 105-120 or 208-230 at 50-60Hz


Size: 13-1/4" L x 7-1/8" W x 6-5/8" H
Weight: 25 lbs.
Finish: Black anodized aluminum

PS-3012 Wired & tested . . . \$239.95

Export prices are slightly higher. Prices subject to change.

Vhf engineering
DIVISION OF BROWNIAN ELECTRONICS CORP.

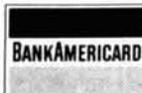BOX H / 320 WATER ST. / BINGHAMTON, N.Y. 13901
Phone 607-723-9574



STEP UP TO TELREX

Professionally Engineered Antenna Systems

Single transmission line "TRI-BAND" ARRAY

**MONARCH
TB5EM/4KWp**

ILLUSTRATION BALUN



ILLUSTRATION TRAP



By the only test that means anything . . . on the air comparison . . . this array continues to outperform all competition . . . and has for two decades. Here's why . . . Telrex uses a unique trap design employing 20 HiQ 7500V ceramic condensers per antenna. Telrex uses 3 optimum-spaced, optimum-tuned reflectors to provide maximum gain and true F/B Tri-band performance.

For technical data and prices on complete Telrex line, write for Catalog PL 7



IAMBIC KEYS



Fully Iambic, both DIT & DAH paddle memories, self completing characters, automatic spacing & weighting, sidetone output, transistorized output that keys grid block or cathode keyed rigs, speed from 5 to 40+ wpm. The Paddles are on a beautiful finished wood base.

Kit \$39.75 with Paddles \$65.00
Assembled \$56.95 with Paddles \$80.00

DAYTRONICS COMPANY **DTR** P. O. BOX 426
12 OAKDALE AVE.
SELDEN, N. Y. 11784

COLLINS & MORE

Collins 51S1 Receiver	\$1450.00
Collins 75S3B, Ham rcvr	\$825.00
Collins 75S3B, late, round	\$950.00
Collins 312B4, Exc. cond.	\$235.00
Collins KWM-2 transcvr. V.G.	\$850.00
Collins CP-1, crystal Pack	\$225.00
Collins 32S3 Ham Xmtr.	\$895.00
Measurements 65B, LF sig. gen.	\$395.00
Henry 4K linear amp., exc.	\$1250.00
Nems-Clark 1302A, 55-260 MHz rcvr.	\$395.00
Yaesu FT401B, orig. box, etc.	\$545.00


We stock good, used equipment from Collins, Drake, Heath and other manufacturers. Hundreds of test items also available. Call for specific requirements, or write for free catalog.

DAMES COMMUNICATION SYSTEMS

201-998-4256

10 SCHUYLER AVENUE
NORTH ARLINGTON, N. J. 07032

PRE-AMP

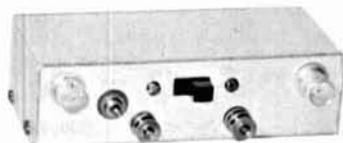

HIGH GAIN • LOW NOISE

35dB power gain, 2.5-3.0 dB N.F. at 150 MHz 2 stage, R.F. protected, dual-gate MOSFETS. Manual gain control and provision for AGC. 4 3/8" x 1 7/8" x 1 3/8" aluminum case with power switch and choice of BNC or RCA phono connectors (be sure to specify). Available factory tuned to the frequency of your choice from 5 MHz to 250 MHz with approximately 3% bandwidth. Up to 10% B.W. available on special order.

N. Y. State residents add sales tax.

Model 201 price: 5-250 MHz \$29.95

Vanguard Labs

196-23 JAMAICA AVE.
HOLLIS, N. Y. 11423

DICK
K4RYR

ORLANDO, FLA.

BOB
W4YYS

**KLM • HY-GAIN • CUSHCRAFT
MINI-PRODUCTS • SHURE
ASTATIC • BEARCAT-210 and More!**

LAFAYETTE RADIO ELECTRONICS

ASSOC.
STORE

1811 HWY 17-92, MAITLAND, FL. 32751



305-831-2271



ONE FEEDLINE FOR TWO ANTENNAS? CHANGE ARRAY DIRECTION REMOTELY?

YES! with INLINE "wireless" controlled weatherproof coaxial relays

A coaxial coupler at the radio controls a weatherproof remote relay on the tower or pole via any length coaxial cable, vertical to horizontal—omni to directional—change bands—a must for satellite work—and more! In world wide use.

Type 103— 20 to 470 MHz—500W PEP— \$41.95

Type 105— 1.5 to 180 MHz—2500W PEP— 51.95

Type 101— .1 to 550 MHz—2000W PEP— 29.95
(Not coax cable controlled)

Special Types—On Order


If not stocked by your dealer order direct

Shipped free via UPS in USA

VISTA—MASTERCHARGE

INLINE INSTRUMENTS, INC.

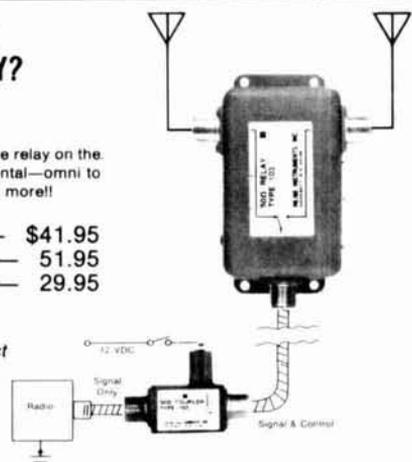Box 473, Hooksett, N. H. 03106 (603) 622-0240



SPECIALS FROM

MHz electronics

Fairchild VHF Prescaler Chips

11C01FC	High Speed Dual 5-4 Input no/nor	15.40
11C05DC	1 GHz Counter Divide by 4	74.35
11C05DM	1 GHz Counter Divide by 4	110.50
11C06DC	UHF Prescaler 750 MHz D Type flip/flop	12.30
11C24DC	Dual TTL VCM same as MC4024P	2.60
11C44DC	Phase Freq. Detector same as MC4044P	2.60
11C58DC	ECL VCM	4.53
11C70DC	600 MHz flip/flop with reset	12.30
11C83DC	1 GHz 248/256 Prescaler	29.20
11C90DC	650 MHz Prescaler Divide by 10/11	16.00
11C90DM	same as above except Mil. version	24.00
11C91DC	605 MHz Prescaler Divide by 5/6	24.00
11C91DM	same as above except Mil. version	24.00
95H90DC	350 MHz Prescaler Divide by 10/11	9.50
95H90DM	same as above except Mil. version	16.50
95H91DC	350 MHz Prescaler Divide by 5/6	9.50
95H91DM	same as above except Mil. version	16.50

Batteries

Gei-Cell 12 volts at 1.5 Amp Hr. #GC-1215 \$19.95

Crystals

1.000000 MHz	4.95	JUST ARRIVED! These radios have just been pulled out of service. Set up for approx. 150 MHz.
5.000000 MHz	4.95	Clean. All tubes included. No accessories. Prices
3579.545 KC	2.95	FOB Phoenix.
10 MHz	\$4.95	Motorola U43 GGT \$49.95
		GE TPL \$99.95
		GE MT-33 \$39.95
		GRC10 Radio Set \$169.95

Motorola MC14410CP CMOS tone Generator uses 1 MHz Crystal to produce standard dual frequency telephone dialing signal. Directly compatible with our 12 key Chomeric pads. Kit includes the following.

- 1 MC14410CP
 - 1 1 MHz Crystal
 - 1 Printed Circuit Board (From Ham Radio Sept. 1975)
- And all other parts for assembly. NOTE: Touch Tone Pad not included! \$15.70

Fairchild 95H90DC Prescaler divide by 10 to 350 MHz. Will take any 35 MHz Counter to 350 MHz. Kit includes the following.

- 1 95H90DC
 - 1 2N5179
 - 2 UG-88/u BNC's
 - 1 Printed Circuit Board
- And all other parts for assembly. \$29.95

Fairchild 11C90DC Prescaler divide by 10 to 650 MHz. Will take any 65 MHz Counter to 650 MHz or with a 82590 it will divide by 10/100 to 650 MHz. This will take a 6.5 MHz counter to 650 MHz. Kit includes the following.

- 1 11C90DC
- 1 2N5179
- 2 UG-88/U
- 1 MC7805CP
- 1 Bridge
- 1 Printed Circuit Board and all other parts for assembly. 82590 add \$5.70 to total. \$59.95

Fairchild 3817 Clock Kit from Ham Radio, Feb. 1976, Pg. 26 — All parts included except transformer and case. 12 hour \$24.95 24 hour \$29.95

I.C.'s

8223B	\$3.00	MuRata 10.7 MHz Ceramic Filters #SFW-10.7MA \$3.95
2102	\$1.99	10.7 Narrow Band Crystal Filters Type 2194F \$7.95 each

Johanson and Johnson

Trimmer Capacitors		Ferrite Beads
1 to 14 pf.	\$1.95	12 for .99 or 120 for 9.99
1 to 20 pf.	\$1.95	

FET'S

2N3070	1.50	2N5460	.90	MFE3002	3.35
2N3436	2.25	2N5465	1.35	MPF102	.45
2N3458	1.30	2N5565	5.45	MPF121	1.50
2N3821	1.60	3N126	3.00	MPF4391	.80
2N3822	1.50	MFE2000	.90	U1282	2.50
2N4351	2.85	MFE2001	1.00	MMF5	5.00
2N4416	1.05	MFE2008	4.20	40673	1.39
2N4875	1.75	MFE2009	4.80	40674	1.49

TUBES

2E26	5.00	5728/T160L	25.00	7377	40.00
3B28	4.00	811A	9.95	8156	3.95
4X150A	15.00	931A	11.95	8908	9.95
4X150G	18.00	5849	32.00	8950	5.50
4CX250B	24.00	6L06	4.50	4-400A	29.95
4CX350A/8321	35.00	6146A	5.25	4-250A	24.95
4CX15000A	150.00	6146B/8298A	6.25	4-125A	20.95
DX415	25.00	6360	7.95	4-65A	15.95
		6907	35.00		

RF TRANSISTORS

2N1561	15.00	2N3927	11.50	2N5641	4.90
2N1562	15.00	2N3948	2.00	2N5643	20.70
2N1692	15.00	2N3950	26.25	2N5764	27.00
2N1693	15.00	2N3961	6.60	2N5841	11.00
2N2631	4.20	2N4072	1.70	2N5842/MM1607	19.50
2N2857	1.80	2N4073	2.00	2N5849/MM1622	19.50
2N2876	12.35	2N4135	2.00	2N5862	50.00
2N2880	25.00	2N4427	1.24	2N5942	49.50
2N2927	7.00	2N4430	20.00	2N5922	10.00
2N2947	17.25	2N4440	8.60	2N6080	5.45
2N2948	15.50	2N4957	6.30	2N6081	8.60
2N2949	3.90	2N5070	13.80	2N6082	11.25
2N2950	5.00	2N5090	6.90	2N6083	12.95
2N3287	4.30	2N5108	3.90	2N6084	14.95
2N3300	1.05	2N5109	1.55	2N6166	36.80
2N3302	1.05	2N5177/MRF5177	20.00	MRF8004	1.90
2N3307	10.50	2N5179	.68	HEPS3014/76	4.95
2N3309	3.90	2N5184		HEPS3002	11.03
2N3375/MM3375	7.00	2N5216	47.50	HEPS3003	29.88
2N3553	1.80	2N5583	5.60	HEPS3005	9.55
2N3571	4.10	2N5589	4.60	HEPS3006	19.90
2N3818	6.00	2N5590	6.30	HEPS3007	24.95
2N3824	3.20	2N5591	10.35	HEPS3008	2.18
2N3866	1.09	2N5635	4.95	HEPS3010	11.34
2N3866 JAN	4.14	2N5636	11.95	RCA TA7994	50.00
2N3866 JAN TX	4.85	2N5637	20.70	RCA 40290	2.48
2N3925	6.00	2N5643	20.70		

We also have the following Wilcox/Sperry circuit boards in stock.

#118788/6118788	#118374/6118374	#117867/6117867
#117198/6117198	#117535/6117535	
#118817/6118817	#117752/6117752	

TRANSFORMERS

F-18X	6.3vct at 6 amps	3.56
F-93X	6.5v to 40v at 750 ma.	3.53
F-92A	6.5v to 40v at 1 amp	4.59
N-51X	Isolation 115vac at 35va.	2.80
Model D-2	6.5v at 3.3 amps	4.95
	6.5v at 3.3 amps	
BE-12433-001	30v at 15 ma.	.49
BGH-9	6.3vct at 10 amps.	6.95
F-107Z	12V @ 4A or 24 V @ 2A	7.80
P6377	12v @ 4a or 24v @ 2a	6.31
P6378	12v @ 8a or 24v @ 4a	10.31
P8196	80vct @ 1.2a	6.28

New Motorola Carbon Microphone Model P-7255A.

This unit is a "noise cancelling" palm type microphone. These mikes come with or without cables. Price without \$19.95 — with \$29.95.

DIODES

1N270 Germanium Diodes	\$7.95/c
HEP170, 2.5A, 1000 PIV	\$4.95/20
Semtech SFMS 20K, 20KV, 10 ma, fast recovery	\$1.26 ea.

H.P. 612A UHF Signal Generator, 450 MHz to 1230 MHz	\$900.00
H.P. 624B Microwave test set, 6565 MHz to 1715 MHz	\$900.00
Beckman "Eput" meter and Heterodyne Plug-in/Freq. meter D.C. to 1 GHz.	\$900.00

FANS

Pamator Fans, Model 4500C 117 VAC, 60 Hz, 19 w. \$7.95

E. F. Johnson Vair. Capacitors

189-1-4	1.2 to 4.2 pf	.99	189-504-4	1.5 to 5 pf	.99
189-4-5	1.5 to 9.1 pf	.99	189-355-5	1.7 to 11 * pf	1.39
189-5-8	1.7 to 11 pf	.99	189-352-5	1.3 to 5.4 * pf	1.39
189-6-8	1.8 to 13 pf	.99		* = Differential	

JUST ARRIVED!

Wilcox/Sperry Circuit Boards:

#118273/6118273 This board has many valuable parts including the following:

1 each crystal	9.700000Mc	1 each 2N5486
	9.800000Mc	5 each 2N5208
	9.900000Mc	4 each 2N4126
	92.734000Mc	4 each 2N3563
	93.134600Mc	2 each 2N4259
	93.535000Mc	3 each #189 - 4 - 51 cap 1.5 to 9.1 pf
	93.935300Mc	and about 100 more capacitors, resistors, coils etc.
	94.335600Mc	Only \$19.95

#118821/6118821 This board has many valuable parts including the following: 4 each 16 pin dip sockets

2	7490	1	7474
2	74123	1	7400
1	MC8300	1	DM8820
1	7405	1	2N4401

and about 35 more capacitors, resistors, crystals, connector Only \$4.95

#118376/6118376 This board has many valuable parts including the following:

4 each	MC1213	3	2N3563
1	MC1234	1	1N4004
4	MC724/824		and about 38 more capacitors, resistors, coils, connectors
5	MC790/890		Only \$8.95

MHz electronics

2543 N. 32nd STREET
PHOENIX, ARIZONA 85008
PH. 602-957-0786



NO C.O.D.

HAM MART

Ham Radio's guide to help you find your local

Alabama

LONG'S ELECTRONICS
3521 TENTH AVE. NORTH
BIRMINGHAM, AL 35234
800-633-3410
Call us Toll Free to place your order

Arizona

MASTERS COMMUNICATIONS
7025 N. 57th DRIVE
GLENDALE, AZ 85301
602-939-8356
Rohn tower distributor, Atlas,
Icom, Tempo, HyGain & service.

POWER COMMUNICATIONS
6012 NORTH 27th AVE.
PHOENIX, AZ 85017
602-242-8990
Arizona's #1 Ham Store.

California

C & A ELECTRONICS
2529 EAST CARSON ST.
P. O. BOX 5232
CARSON, CA 90745
213-834-5868
Not the biggest, but the best —
since 1962.

CARSON ELECTRONICS
12010 EAST CARSON ST.
HAWAIIAN GARDENS, CA 90716
213-421-3786
Dealing exclusively in ICOM
communications equipment.

COMMUNICATIONS CENTER
705 AMADOR STREET
VALLEJO, CA 94590
707-642-7223
Who else has a Spectrum
Analyzer?

HAM RADIO OUTLET
999 HOWARD AVENUE
BURLINGAME, CA 94010
415-342-5757
Visit our stores in Van Nuys
and Anaheim.

QUEMENT ELECTRONICS
1000 SO. BASCOM AVENUE
SAN JOSE, CA 95128
408-998-5900
Serving the world's Radio Amateurs
since 1933.

TOWER ELECTRONICS CORP.
24001 ALICIA PARKWAY
MISSION VIEJO, CA 92675
714-768-8900
Authorized Yaesu Sales & Service.
Mail orders welcome.

Colorado

C W ELECTRONIC SALES CO.
1401 BLAKE ST.
DENVER, CO 80202
303-573-1386
Rocky Mountain area's complete
ham radio distributor.

Florida

CENTRAL EQUIPMENT CO.
18451 W. DIXIE HIGHWAY
NORTH MIAMI BEACH, FL. 33160
305-932-1818
Specializing in Amateur, CB
& Marine Equipment.

RAY'S AMATEUR RADIO
1590 US HIGHWAY 19 SO.
CLEARWATER, FL 33516
813-535-1416
West coast's only dealer:
Drake, Icom, Cushcraft, Hustler.

Illinois

ERICKSON COMMUNICATIONS, INC.
5935 NORTH MILWAUKEE AVE.
CHICAGO, IL 60646
312-631-5181
Hours: 9:30-9 Mon. & Thurs. 9:30-5
Tues., Wed., Fri. 9-3 Sat.

KLAUS RADIO, INC.
8400 NORTH PIONEER PARKWAY
PEORIA, IL 61614
309-691-4840
Let us quote your Amateur needs.

SPECTRONICS, INC.
1009 GARFIELD STREET
OAK PARK, IL 60304
312-848-6777
Chicagoland's Amateur Radio
leader.

Indiana

HOOSIER ELECTRONICS
P. O. BOX 2001
TERRE HAUTE, IN 47802
812-238-1456
Ham Headquarters of the Midwest.
Store in Meadow Shopping Center.

Iowa

BOB SMITH ELECTRONICS
12 SOUTH 21ST STREET
FT. DODGE, IA 50501
515-576-3886
For an EZ deal.

Kansas

ASSOCIATED RADIO
8012 CONSER P.O.B. 4327
OVERLAND PARK, KS 66204
913-381-5901
Amateur Radio's Top Dealer.
Buy — Sell — Trade.

Maryland

COMM CENTER, INC.
9624 FT. MEADE ROAD
LAUREL PLAZA RT. 198
LAUREL, MD 20810
301-792-0600
New & Used Amateur Equipment.
Wilson, Ten-Tec, R. L. Drake

Massachusetts

TUFTS RADIO ELECTRONICS
386 MAIN STREET
MEDFORD, MA 02155
617-395-8280
New England's friendliest
ham store.

Michigan

RADIO SUPPLY & ENGINEERING
1207 WEST 14 MILE ROAD
CLAWSON, MI 48017
313-435-5660
10001 Chalmers, Detroit, MI
48213, 313-371-9050.

Minnesota

ELECTRONIC CENTER, INC.
127 THIRD AVENUE NORTH
MINNEAPOLIS, MN 55401
612-371-5240
ECI is still your best buy.

Missouri

HAM RADIO CENTER, INC.
8340-42 OLIVE BLVD.
ST. LOUIS, MO 63132
800-325-3636
See Our Ads
In This Issue.

Dealers - You should be here too! Contact Ham Radio today for complete details.

Amateur Radio Dealer

MIDCOM ELECTRONICS, INC.
2506 SO. BRENTWOOD BLVD.
ST. LOUIS, MO 63144
314-961-9990
At Midcom you can try before you buy!

Nebraska

COMMUNICATIONS CENTER, INC.
2226 NORTH 48 ST.
LINCOLN, NE 68504
800-228-4097
Yaesu, Drake, Tempo, Swan,
HyGain - call Toll Free

New Hampshire

EVANS RADIO, INC.
BOX 893, RT. 3A BOW JUNCTION
CONCORD, NH 03301
603-224-9961
Icom & Yaesu dealer.
We service what we sell.

New Jersey

ATKINSON & SMITH, INC.
17 LEWIS ST.
EATONTOWN, NJ 07724
201-542-2447
Ham supplies since "55".

New Mexico

ELECTRONIC MODULE
601 N. TURNER
HOBBS, NM 88240
505-397-3012
Yaesu, Kenwood, Swan, Dentrion,
Tempo, Atlas, Wilson, Cushcraft

New York

ADIRONDACK RADIO SUPPLY, INC.
185 W. MAIN STREET
AMSTERDAM, NY 12010
518-842-8350
Yaesu dealer for the Northeast.

CFP COMMUNICATIONS
211 NORTH MAIN STREET
HORSEHEADS, NY 12010
607-739-0187
Jim Beckett, WA2KTJ, Manager
Bryant Hozempa, WB2LVW, Sales

GRAND CENTRAL RADIO
124 EAST 44 STREET
NEW YORK, NY 10017
212-682-3869
Drake, Atlas, Ten-Tec, Midland,
Hy-Gain, Mosley in stock

HARRISON
"HAM HEADQUARTERS, USA"
ROUTE 110 & SMITH STREET
FARMINGDALE, L. I., N. Y. 11735
516-293-7990
Since 1925 . . . Service, Satisfaction,
Savings. Try Us!

RADIO WORLD
ONEIDA COUNTY AIRPORT
TERMINAL BLDG.
ORISKANY, NY 13424
315-337-2622
New & used ham equipment.
See Warren K2IXN or Joe WB2GJR

Ohio

UNIVERSAL SERVICE
114 N. THIRD STREET
COLUMBUS, OH 43215
614-221-2335
Give U.S. a try when ready to buy.

Oklahoma

RADIO STORE, INC.
2102 SOUTHWEST 59th ST.
(AT 59th & S. PENNSYLVANIA)
OKLAHOMA CITY, OK 73119
405-682-2929
New and used equipment —
parts and supply.

Pennsylvania

ELECTRONIC EXCHANGE
136 N. MAIN STREET
SOUDERTON, PA 18964
215-723-1200
New & Used Amateur Radio
sales and service.

"HAM" BUERGER, INC.
68 N. YORK ROAD
WILLOW GROVE, PA 19090
215-659-5900
Communications specialists.
Sales and service.

**HAMTRONICS, DIV. OF
TREVISE ELECT.**
4033 BROWNSVILLE ROAD
TREVISE, PA 19047
215-357-1400
Same location for 25 years.

South Carolina

AMATEUR RADIO ELECTRONICS
100 STATE ST.
WEST COLUMBIA, SC 29169
803-796-7957
Featuring Swan Equipment

Tennessee

J-TRON ELECTRONICS
505 MEMORIAL BLVD.
SPRINGFIELD, TN 37172
615-384-3501
Ten-Tec dealer — call or
write for best trade.

Texas

AGL ELECTRONICS
3068 FOREST LANE, SUITE 309
DALLAS, TX 75234
214-241-6414
Having trouble finding equipment?
Come on in today!

HARDIN ELECTRONICS
5635 E. ROSEDALE
FT. WORTH, TX 76112
817-461-9761
Your Full Line Authorized
Yaesu Dealer.

Virginia

ARCADE ELECTRONICS
7048 COLUMBIA PIKE
ANNANDALE, VA 22003
703-256-4610
Serving Maryland, D.C., and Virginia
area since 1962.

Wisconsin

**AMATEUR
ELECTRONIC SUPPLY, INC.**
4828 WEST FOND du LAC AVENUE
MILWAUKEE, WI 53216
414-442-4200
Open Mon & Fri 9-9, Tues, Wed,
Thurs, 9-5:30, Sat, 9-3.

Washington

AMATEUR RADIO SUPPLY CO.
6213 13TH AVENUE SOUTH
SEATTLE, WA 98108
206-767-3222
First in Ham Radio in Washington
Northwest Bird Distributor

Wyoming

DENCO COMMUNICATIONS CENTER
1728 EAST 2nd STREET
CASPER, WY 82601
307-234-9197
Sales, Service to Wyoming
and the Northern Rockies.

BULLET ELECTRONICS

P.O. BOX 19442
DALLAS, TX. 75219
(214) 823-3240

- POLICIES: No COD'S.
- Send check or Money Order
- Add 5% for Shipping
- Tex. Res. add 5% Sales Tax
- Foreign Orders add 10% (20% for Airmail)
- Order under \$10. add 60c handling
- Accepting phone orders on MC & BAC
- Catalog free with each order.

WE BACK YOU UP!
Bullet will repair any kit we have ever sold for 20% of original purchase price to cover handling. (Warranty void for improper soldering techniques.)

AUTOMATIC TIME-OUT CIRCUIT
or use with the US-01 or any other application. Provides a 17 second entry delay and then energizes your alarm for approx. 10 minutes; re-arms itself. Will source up to 200ma to drive a relay. All components & PC board.
\$3.95

ULTRASONIC SENNER-RECEIVER KIT 19.95

A special buy on a high quality ultrasonic transducer allows us to offer this kit at a super price. Gives you the basics to build INTRUSION ALARMS, MOTION DETECTORS, REMOTE CONTROLS, ECHO RANGING, etc. All components with drilled & plated PC Board. Will cover up to 400 sq. ft. Requires 12-15VDC @ 80 ma (not supplied). Order model US-01.

WARBLE ALARM KIT

Thousands of these are being used in scores of applications. Gives a LOUD two tone scream of 10 watts (pulsed) power. Requires 6-15VDC @ 300ma & 4 or 8 ohm speaker. (spk. not supplied) \$2.50 includes all components & PC Board

FIRE D UP!

Our CDI Kit will give your car that extra spark it needs to burn fuel more efficiently. A special buy allows us to sell the complete kit at a low, low price. \$9.95 Includes: Special toroid transformer, drilled & plated PC board, all components, and complete instructions. (Heatsink and case NOT provided.)

\$9.95

No other clock at any price has all these features:



\$39.95

We offer a beautiful solid hard wood case in either ash or walnut with front ruby filter. Designed and cut specifically for the mini grandfather clock kit. Unfinished Case - \$14.95 Finished Case - \$18.50 Please specify type of wood desired. Case is shipped unassembled.

- Completely Electronic
- 100% Solid State
- All CMOS IC Construction
- 2 Quality Plated PC Boards 6.5" x 4.5"
- New, revised easy to follow instructions
- Large 1/2" LED readout with AM/PM & colon indicators
- Simulated LED swinging pendulum with synchronized tick-tock sound.
- Chimes the hour (ie: 3 times for 3 o'clock)
- Adjustable volume tone and sustain on the chime.
- LOW COST
- Complete with all parts including transformer & speaker.

This quality time piece will catch the eye of everybody who walks into your house! It will be the most unique item on your mantle or bookshelf.

MINI GRANDFATHER CLOCK KIT

\$39.95
(order MG-01)
Case NOT included
\$59.95
(order MG-01/A)
Completely assembled!
(Case NOT included)

THE DOOMSDAY ALARM

Four independently adjustable oscillators are sequentially mixed and disabled by a counter circuit pulsing at a rate that you set. The sound combinations are endless and the effect is amazing. Sounds straight from the Twilight Zone. Complete electronics with plated PC board. Requires 6 to 15 volts DC @ 800ma. 10 watts (pulsed) @ 8 ohms and 12 volts. Order DA-01
\$8.50

AUDIBLE CONTINUITY TESTER KIT

Measures continuity and resistance to 2K. Test LED's, diodes & transistors. Less speaker. Requires 6 to 12 volts, (batteries not included).
\$1.95

THE PS-12 IS THE BEST POWER SUPPLY KIT ON THE MARKET FOR \$49.95

Check these specs:
3 to 16 volts and 15 to 30 volts (2 ranges)
Adjustable fold back current limiting from 4 to 15 amps.
10 amps continuous, 15 amps with fan cooling.
Regulation better than 150 mv from 0 to full load
Ripple less than 200mv @ 10 amps

Look what you get:
11 pound heavy duty transformer

Two 6" 60 watt heatsinks

All resistors, caps, etc.

\$49.95

Large computer grade filter cap.
IC regulator, power transistors and 15A bridge rectifier.

Quality plated and drilled PC board.
*ADD \$3.70 for UPS shipping. Canadian customer add \$10.00 for parcel post shipping and insurance. Price does not include case, meters or jacks.

OVERVOLTAGE PROTECTION KIT

The OVP-1 is an overvoltage protection circuit designed to protect your expensive gear if the series pass regulators short or unauthorized hands tamper with the voltage setting on a variable supply. Set the OVP-1 for 1 or 2 volts over the normal operation voltage and it will instantly go into current limiting; (if the supply has this feature), or blow the fuse. The kit comes complete with PC board, all components including the 25A SCR and complete easy to follow instructions..Designed specifically for the PS-12 Power Supply Kit.
\$6.95

Webster
radio, inc.

has the words
QUALITY, QUANTITY...

EVERYTHING FROM A TO Z IN ELECTRONICS

YAESU



YAESU
HF SSB
FT-101E,
160 thru 10M
\$729.

KENWOOD

KENWOOD
Transceiver
TS-820
160 thru 10M
\$830.



ICOM



ICOM
Transceiver
2M FM
IC 22S
\$299.

CTC - UHF/VHF
POWER TRANSISTORS FOR AMATEUR USE
J101 UNDERWOOD CAPACITORS

Order Direct
3 E-Z Ways:

1. Check or M.O. with order.
2. Bank Americard or Mastercharge.
3. C.O.D. (20% deposit, please).

Write for
FREE brochures
and particulars
on all models.

Webster
radio, inc.

2602 E. Ashlan, Fresno, CA 93726 / Ph. (209)224-5111

SUB-AUDIBLE GENERATOR for FM

- Inexpensive multi tone encoder
- Compatible with PL-CG-QC
- Low distortion sinewave
- Input 8-18 VDC unregulated
- Rugged, plastic encased with leads
- Adjustable frequency (98-250 Hz), Lower available
- Excellent stability



THE CUBE
.5 x .6 x .8 in.

Price \$19.95

Freq. set at
factory
\$5.00 extra

Call. res. add 6%

Send for more info

yle
Products

Dept. hr P.O. Box 2083 Santa Clara, CA. 95051

DIPOLE ANTENNA CONNECTOR

HYE-QUE (HQ-3) dipole connector has coax SO-239 socket molded into glass filled plastic body to accept coax PL-259 plug on feedline. Drip-cap keeps coax fittings dry. Instructions included. Guaranteed. At your dealers or **\$3.95 postpaid**. Companion insulators 2/\$.99.

BUDWIG MFG. Co. PO Box 97H, Ramona, CA 92065

K-ENTERPRISES

Frequency Counters
Prescalers
Marker & Peaking
Generators

Power Supplies
Amplifiers
Frequency
Standards

Write for Free Catalog

Box 410 (N.W. of town) Fairland, OK 74343
Phone: 918-675-3752

Apollo Products-Little Giant Trans Systems Tuner Kit — \$122.50

Designed and engineered after "Apollo" — "Little Giant" 2500X-2, for an "engineered performance" Trans Systems Tuner and Adaptations of the Lew McCoy Transmatch, with power handling at the KW plus level!



Kit includes:

- 1 200 pfd wide-spaced variable with isolantite insulation rated 3,000 volts
- 1 200 pfd dual section parallel condenser isolantited
- 2 finger-grip pointer knobs 2" diam. white indented
- 1 pvc insulated shaft couplings 1/4 to 1/4
- 3 SO-239 coax chassis connectors. Tunes 52 ohm or 52-300-600* or random wires

- 1 heavy inductance for 10-15-20-40-80 meters
- 6 pvc stand-offs, 4 for condensers and 2 for inductance
- 1 HD switch for band catching 10 thru 80 meter coverage
- 1 pkg 12-gauge tinned round wire Cabinet included — Apollo "Shadow Boxes" M Kit includes schematic. Recommend parts layout. INFO NOTE *377 OHM and **600 OHM "Open wire spaced ladder line" air dielectric.
- *53 x wire diam. **84 x wire diam. info only — not supplied.

Apollo Products, Box 245, Vaughnsville, Ohio 45893 419-646-3495
Subsidiary "Little Giant Antenna Labs"

- Booming 25 watts output power @ 14v DC input
- Separate controls for independent transmit and receive frequency selection
- Switch for lock-in of pre-selected frequency pairs allows one-knob operation
- Supersensitive dual-gate MOS FET in receiver head end
- Backlighted for night operation
- Factory-installed, front panel mount 12 digit, alpha-numeric tone encoder



GTX-200T
(incl. 146.94 MHz)
\$249⁹⁵

Features Like These Make Genave The FM Transceiver For You!

The GTX-200T is only one of the superior 2-meter transceivers in Genave's complete line of American-made amateur radios.

All Genave gear is carefully handcrafted under the strictest quality control conditions in a facility inspected and approved by an agency of the federal government for the production of precision aircraft navigation and communication equipment.

And, all Genave amateur FM transceivers are an unprecedented value because you order factory direct eliminating middlemen profits!

Each Genave unit has 10.7 MHz first IF and 455 KHz second IF filters for high selectivity, with RF output stages VSWR protected. In addition, Genave units are unusually lightweight, with fully transistorized integrated circuitry.

Standard features include netting trimmers for each transmit crystal and single circuit board designs which permit easy modifications.

So, take a good look at the GTX-200T and other Genave amateur gear. Then fill out the coupon below—better yet, call collect: 317+546-7959, today!



GTX-2

2 meter FM, 10 channels, 25 watts with pushbutton frequency selector (incl. 146.94 MHz)

\$189⁹⁵



GTX-200

2 meter FM, 100 channel combinations, 25 watts (incl. 146.94 MHz)

\$199⁹⁵



GTX-200T

2 meter FM, 100 channel combinations, factory-installed front panel mount 12 digit alpha-numeric tone encoder.

\$249⁹⁵



GTX-10S

2 meter FM, 10 channels, 10 watts (Xtals not included)

\$149⁹⁵



GTX-1

\$249⁹⁵

GTX-1T

\$299⁹⁵

Hand-held, 2 meter FM, 6 channel, 3.0 watts, GTX-1T with factory installed tone encoder.



4141 Kingman Drive
Indianapolis, IN 46226
Phone-in orders accepted
317/546-1111

Name _____

Address _____ City _____

State & Zip _____ Amateur Call _____

Payment by:

- Certified Check/Money Order Personal Check
 C.O.D. Include 20% down

Note: Orders accompanied by personal checks will require about two weeks to process. 20% down payment enclosed. Charge balance to:

- BankAmericard # _____ Expires _____
 Master Charge # _____ Expires _____
 Interbank # _____ Expires _____

IN residents add 4% sales tax: \$ _____

All orders shipped post-paid within continental U.S.

Add \$4 per radio for Shipping, Handling & Crystal Netting

ACCESSORIES

- Ringo Ranger ARX-2 6 db 2-M Base Antenna \$34.95
- Lambda/4 2-M and 6-M Trunk Antenna \$29.95
- TE-I Tone Encoder Pad \$59.95
- TE-II Tone Encoder Pad \$29.95
- PS-1 Regulated AC Power Supply for use with all makes of transceivers 14 VDC-7 amp \$69.95

and the following **standard crystals**

@ \$4.50 each \$ _____

Non-standard crystals

@ \$6.50 each: \$ _____

ACCESSORIES FOR GTX-1 and GTX-1T

- PSI-18 Optional Nicad battery pack \$29.95
- PS-2 Charger for GTX-1(T) battery pack \$39.95
- GLC-1 Leather carrying case \$12.95
- TE-III Tone Encoder (for use with GTX-1) \$49.95

BI-SYN·FILTER·TONE·TAG

See HR magazine articles on Nov '75 and '76



Model 1100 - 13 IC op amps, 4 transistors, 10 diodes on 4 PC boards. 3 X 6 3/8 X 8 inches deep

TONE-TAG provides you with an excellent method for fighting QRM -- any CW signal tuned to produce a 750 ± 50 Hz beatnote is modulated by a tone that is derived and processed from the signal itself. Signals above and below the TONE-TAG bandwidth remain unmodulated, thus readability is greatly enhanced. At the same time, the BINAURAL SYNTHESIZER channels signals above and below the 750 Hz cross-over frequency to the right and left spacially (stereo headsets or speakers are used). Finally, to make a triple-header, a 4 pole, 150 Hz pre-filter with continuously adjustable skirts is included

THREE TECHNIQUES ARE SELECTING FOR YOU!

... AND NOW -



THE NEW ONE

Model 700 - 7 IC op amps, 6 diodes on 2 PC boards 2 7/8 X 4 X 2 inches deep

Connection to your receiver's headphone or speaker jack (monaural) is all that is required for signal input. Tens to hundreds of millivolts of audio signal is all that is required. Symmetrical limiting takes place on signals above a nominal 1 volt input.

Model 1100 supplies outputs for stereo speakers - 1/2 Watt PEP per channel and a jack at reduced power for stereo headsets. Models 400 and 700 provide outputs that can drive standard stereo headsets directly - or add amplifiers to drive speakers.

PHONE MEN - the stereo system and variable skirt control work well on voice. To borrow a phrase: It has presence!

Model 400 - The original Binaural Synthesizer uses 2 each 9 volt batteries \$29.95 ppd

Model 700 - Binaural Synthesizer with TONE-TAG uses 2 each 9 volt batteries \$44.00 ppd

Model 1100 - Binaural Synthesizer-Filter with TONE-TAG uses 8 economical "D" cells - Less batteries \$86.00 ppd

An economy AC option that uses a wall transformer plus a voltage regulator internal to the Model is available for any of the models listed - add \$10.00

We still supply PC Boards plain or assembled. Write for brochures and list


California residents add state tax

Guarantee? Our self esteem demands your satisfaction - The very best

HILDRETH ENGINEERING
BOX 60003 Sunnyvale CA
94088 (408) 245 3279

FAST SCAN AMATEUR TELEVISION EQUIPMENT

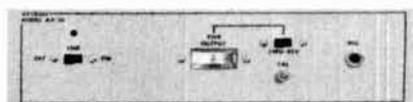- SOLID STATE
- BROADCAST QUALITY PERFORMANCE
- FOR TECHNICAL DATA AND PRICING, WRITE TO:



AX-10 TRANSMITTER



AM-1A RCVR MODEM

APTRON LABORATORIES BOX 323, BLOOMINGTON, IN 47401

DIGITAL TONE ENCODERS

CRYSTAL CONTROLLED DIGITAL INTEGRATED CIRCUIT
DIGITRAN KEYBOARD FOR HI-REL AND GREAT "FEEL"
CONNECTS DIRECTLY TO YOUR BATTERY AND MIKE
WITH NO STANDBY POWER DRAIN

NO NEED TO HUNT FOR TRANSMIT POWER ETC.


HT 220 ENCODER FRONTS

FULLY ASSEMBLED AND TESTED TONE ENCODER FRONTS
JUST ADD YOUR MIKE, SPEAKER, AND HARNESS

NO EXTRA WIRING TO THE RADIO CHASSIS

TONE ENCODER PADS

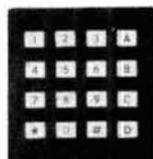THE SAME HIGH QUALITY PAD USED IN OUR HT-220 FRONTS



PRICES

HT-220 FRONTS
450MHZ 5W \$84.50
ALL OTHERS \$74.50

SEND DESCRIPTION OF YOUR RADIO WITH ORDER

TONE ENCODER PADS
ASSEMBLED AND TESTED \$45.00
KIT \$39.50

CAL RES ADD 6% tax

WATCH OUR AD FOR NEW PRODUCT ANNOUNCEMENTS
GROUP DISCOUNTS ARE AVAILABLE

B K PRODUCTS
P.O. BOX 391
HARBOR CITY, CA. 90710

SYNTHESIZERS

We have the worlds largest selection of synthesizers for receivers, transmitters and transceivers. For complete details see our 1/3 page ad in the April 1976 issue of this magazine or call or write for additional information. Phone orders accepted between 9 AM and 4 PM EDT. (212) 468-2720

VANGUARD LABS

196-23 JAMAICA AVENUE
HOLLIS, N. Y. 11423

SST T-1 RANDOM WIRE ANTENNA TUNER



All band operation (160-10 meters) with most any random length wire. 200 watt output power capability. Ideal for portable or home operation. Toroid inductor for small size. 3 x 4-1/4 x 2-3/8. Built-in neon tune-up indicator. SO-239 coax connector. Guaranteed for 1 yr. - 10 day trial. Compact - easy to use. - only \$29.95 postpaid. (Add Sales Tax in Calif.) (213) 376-5887

SST ELECTRONICS, P.O. BOX 1, LAWDALE, CA. 90260

NEW ELECTRONIC PARTS

Resistors Meters LED Displays Fuses
Capacitors Switches Proto Boards IC sockets
Diodes Dozy Boxes Mod U Line Test Clips
Trim pots Transistors Hardware And much more
SASE brings our new parts catalog.

NuData Electronics

104 W. LEMMON ST. MOUNT PROSPECT, ILLINOIS. 60056

CFP ... FOR ALL YOUR AMATEUR NEEDS



TRITON IV DIGITAL

ATLAS
CUSHCRAFT
CIR (ASTRO 200)
DENTRON
DRAKE
TEMPO
TEN TEC
YAESU*

Transmitter sales to licensed amateurs only

REMEMBER, YOUR DEALER IS RESPONSIBLE FOR WARRANTY REPAIRS DURING WARRANTY PERIOD. Mail Orders accepted. N. Y. residents add sales tax. SASE will get our list of used Amateur Equipment.

WANTED: GOOD CLEAN TRADES!

WA2KJT
WB2LVW

CFP COMMUNICATIONS

211 NORTH MAIN STREET
HORSEHEADS, N. Y. 14845
PHONE: 607-739-0187

Store Hours
Tues. to Fri. 10-6 p.m.
Sat. 10-4 p.m.

Fri. & Sat. subject to Hamfest weekends
Closed Sun. & Mon.

DIODES/ZENERS

1N914	100v	10mA	.05
1N4004	400v	1A	.08
1N4005	600v	1A	.08
1N4007	1000v	1A	.15
1N4148	75v	10mA	.03
1N753A	6.2v	z	.25
1N758A	10v	z	.25
1N759A	12v	z	.25
1N4733	5.1v	z	.25
1N5243	13v	z	.25
1N5244B	14v	z	.25
1N5245B	15v	z	.25

SOCKETS/BRIDGES

8-pin	pcb	.25	ww	.45
14-pin	pcb	.25	ww	.40
16-pin	pcb	.25	ww	.40
18-pin	pcb	.25	ww	.75
22-pin	pcb	.45	ww	1.25
24-pin	pcb	.35	ww	1.25
28-pin	pcb	.35	ww	1.45
40-pin	pcb	.50	ww	1.95
Molex pins	.01	To-3 Sockets		.25
2 Amp Bridge		100-prv		1.20
25 Amp Bridge		200-prv		1.95

TRANSISTORS, LEDS, etc.

2N2222	NPN		.15
2N2907	PNP		.15
2N3740	PNP	1A 60v	.25
2N3906	PNP		.10
2N3054	NPN		.35
2N3055	NPN	15A 60v	.50
T1P125	PNP	Darlington	.35
LED Green, Red, Clear			.15
D.L.747	7 seg 5/8" high com-anode		1.95
XAN72	7 seg com-anode		1.50
FND 359	Red 7 seg com-cathode		1.25

C MOS

4000	.15
4001	.20
4002	.20
4004	3.95
4006	1.20
4007	.35
4008	1.20
4009	.30
4010	.45
4011	.20
4012	.20
4013	.40
4014	1.10
4015	.95
4016	.35
4017	1.10
4018	1.10
4019	.70
4020	.85
4021	1.35
4022	.95
4023	.25
4024	.75
4025	.35
4026	1.95
4027	.50
4028	.95
4030	.35
4033	1.95
4034	2.45
4035	1.25
4040	1.35
4041	.69
4042	.95
4043	1.25
4044	.95
4046	1.50
4049	.80
4050	.60
4066	1.35
4069	.40
4071	.35
4082	.45

7400	.15
7401	.15
7402	.20
7403	.20
7404	.15
7405	.25
7406	.35
7407	.55
7408	.25
7409	.15
7410	.10
7411	.25
7412	.30
7413	.45
7414	1.10
7416	.25
7417	.40
7420	.15
7426	.30
7427	.45
7430	.15
7432	.30
7437	.35
7438	.35
7440	.25
7441	1.15
7442	.55
7443	.85
7444	.45
7445	.80
7446	.95
7447	.95
7448	.95
7450	.25
7451	.25
7453	.20
7454	.25
7460	.40
7470	.45
7472	.45

7473	.25
7474	.35
7475	.35
7476	.30
7480	.55
7481	.75
7483	.95
7485	.95
7486	.30
7489	1.35
7490	.55
7491	.95
7492	.95
7493	.40
7494	1.25
7495	.60
7496	.80
74100	1.85
74107	.35
74121	.35
74122	.55
74123	.55
74125	.45
74126	.35
74132	1.35
74141	1.00
74150	1.00
74151	.75
74153	.95
74154	1.05
74156	1.15
74157	.65
74161	.85
74163	.95
74164	.60
74165	1.50
74166	1.35
74175	.80

- T T L -

74176	1.25
74180	.85
74181	2.75
74182	.95
74190	1.75
74191	1.35
74192	1.65
74193	.85
74194	1.25
74195	.95
74196	1.25
74197	1.25
74198	2.35
74221	1.00
74367	.85
75108A	.35
75110	.35
75491	.50
75492	.50
74H00	.25
74H01	.25
74H04	.25
74H05	.25
74H08	.35
74H10	.35
74H11	.25
74H15	.30
74H20	.30
74H21	.25
74H22	.40
74H30	.25
74H40	.25
74H50	.25
74H51	.25
74H52	.15
74H53J	.25
74H55	.25

74H72	.55
74H101	.75
74H103	.75
74H106	.95
74L00	.35
74L02	.35
74L03	.30
74L04	.35
74L10	.35
74L20	.35
74L30	.45
74L47	1.95
74L51	.45
74L55	.65
74L72	.45
74L73	.40
74L74	.45
74L75	.55
74L93	.55
74L123	.55
74S00	.55
74S02	.55
74S03	.40
74S04	.35
74S05	.35
74S08	.35
74S10	.35
74S11	.35
74S20	.35
74S40	.25
74S50	.25
74S51	.45
74S64	.25
74S74	.40
74S112	.90
74S114	1.30

74S133	.45
74S140	.75
74S151	.35
74S153	.35
74S157	.80
74S158	.35
74S194	1.05
74S257(8123)	.25
74LS00	.45
74LS01	.45
74LS02	.45
74LS04	.45
74LS05	.55
74LS08	.45
74LS09	.45
74LS10	.45
74LS11	.45
74LS20	.40
74LS21	.25
74LS22	.25
74LS32	.40
74LS37	.40
74LS40	.55
74LS42	1.75
74LS51	.65
74LS74	.75
74LS86	.75
74LS90	1.30
74LS93	1.00
74LS107	.95
74LS123	1.00
74LS151	.75
74LS153	1.20
74LS157	.85
74LS164	1.90
74LS367	.85
74LS368	.70

9000 SERIES

9301	.85
9309	.35
9322	.85
95H03	.55
9601	.75
9602	.50

LINEARS, REGULATORS, etc.

8266	.35
8836	.95
MCT2	.95
8038	3.95
LM201	.75
LM301	.25
LM308 (Mini)	.75
LM309H	.65
LM309K(340K-5)	.85
LM310	1.15
LM311D(Mini)	.75
LM318 (Mini)	.65

LM320K5 (7905)	1.65
LM320K12	1.65
LM320T12	1.25
LM320T15	1.65
LM339	.95
7805 (340T-5)	.95
LM340T-12	1.00
LM340T-15	1.00
LM340T-18	1.00

LM340T-24	.95
LM340K-12	2.15
LM340K-15	1.25
LM340K-18	1.25
LM340K-24	.95
LM373	2.95
LM380	.95
LM709(8,14 PIN)	.25
LM711	.45

LM723	.50
LM725	1.75
LM739	1.50
LM741 8-14	.20
LM747	1.10
LM1307	1.25
LM1458	.95
LM3900	.50
LM75451	.65
NE555	.50
NE556	.95
NE565	.95
NE566	1.75
NE567	1.35
SN72720	1.35
SN72820	1.35

MEMORY CLOCKS

74S188 (8223)	3.00
1702A	7.95
MM5314	3.00
MM5316	3.50
2102-1	1.75
2102L-1	1.95
TMS6011NC	6.95
8080AD	15.00
8T13	1.50
8T23	1.50
8T24	2.00
2107B-4	4.95

INTEGRATED CIRCUITS UNLIMITED

7889 Clairemont Mesa Blvd. San Diego, CA 92111 (714) 278-4394

All orders shipped prepaid No minimum
Open accounts invited COD orders accepted

Discounts available at OEM Quantities
California Residents add 6% Sales Tax

24 Hour Phone (714) 278-4394

MasterCharge / BankAmericard

TEE/AX PRESENTS; THE FIRST COAX TOGGLE SWITCH

\$39⁹⁵

TEE/AX, INC.

5701 N.W. 31st AVENUE
FT. LAUDERDALE,
FLORIDA 33309

Distributor Inquiries
Invited

Mail Orders Accepted — Add 75¢ for Postage

Patent Pending



Model SW-5000

- 52 ohms
- SPDT, DPDT
- Power 1 KW
- All Brass Construction
- Teflon Insulated
- Captivated Internal Contacts
- Available in UHF, BNC, N, F, all series

ICOM



IC-22S
146 MHz FM 10 W
TRANSCIVER



IC-245
146 MHz FM 10 W
TRANSCIVER

IMMEDIATE DELIVERY
SHIPPING PREPAID IN USA

MASTERS COMMUNICATIONS

7025 N. 57th DR.
GLENDALE, AZ 85301



PHONE
602-939-8356




Attention: CW Operators using Drake!

*These crystal filters
are for you!*

All filters contain specially-treated high-Q crystals.
600 Hz 6-Pole First-IF Filter for Drake R-4C
Improve the early-stage selectivity. Eliminate those high-pitched beat notes from signals that leak around the switchable second-IF filter. Minimize the chance of strong signals overloading the second mixer, causing intermodulation and desensitization. Both the existing filter and our CF-600/6 can be mounted in the receiver and relay switched to retain phone capabilities. CF-600/6 \$75.00 Relay switch kit \$29.00

125 Hz 8-Pole Second-IF Filter for Drake R-4C
Sharpest available! 300 Hz at -60dB! Cuts GRM. Ideal for DX and contest work. Unexcelled under crowded band conditions. Does what no audio filter can do. More selective than audio filters. Puts selectivity in AGC loop. Unlike audio filters, receiver gain not reduced by GRM outside passband. Yet works well with an audio filter to improve receiver performance. Plugs directly into an accessory filter socket of the R-4C. CF-125/8 \$125.00

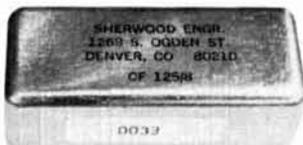

Sherwood Engineering Inc.

Dept. A
1268 South Ogden St.
Denver, Colo. 80210
(303) 722-2257

Money back if not satisfied
Dealer Inquiries Welcome



SCANNER RECEIVERS At Discount Prices

All new factory sealed cartons

Bearcat 101	\$256.82	Regency Whammo 10	\$242.05
Bearcat 210	\$256.82	SBE Optiscan	\$278.41
Tennelec MCP1	\$313.35	Regency Aircraft	\$118.52

Add \$4.00 AMERICAN WHOLESALE
Shipping P.O. Box 3355, Lennox, California 90304


MILITARY SURPLUS WANTED

Space buys more and pays more. Highest prices ever on U.S. Military surplus, especially on Collins equipment or parts. We pay freight. Call collect now for our high offer. 201 440-8787.
SPACE ELECTRONICS CO.
div. of Military Electronics Corp.
35 Ruta Court, S. Hackensack, N.J. 07606

TONE ENCODER PAD

MODEL TTP-03

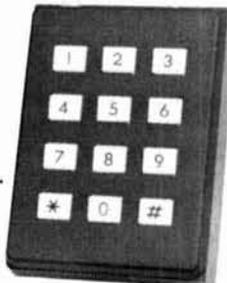- DIGITRAN® Keyboard
- Output Level Set Pot
- Crystal Controlled-Digitally Synthesized Tones
- Strapping for Hi-Low Z Output
- Internal 5 V. Regulator
- Supply Voltage Range 7 to 24 V.
- RFI Suppression
- Velcro and Case Included
- Size 2.80 - 2.00 - 0.60 Inches



\$54.95

POSTPAID
IN U.S.A.

TEXAS RESIDENTS
ADD 5% SALES TAX
CHECK OR M.O.
SEE UP-COMING AD FOR NEW
AUTOMATIC UNIT: ATD-70
2 NUMBERS, FIELD PROGRAM-
MABLE. \$79.95

SATISFACTION
GUARANTEED

CLENG

CLENG ELECTRONICS COMPANY
BOX 12171 DALLAS, TEXAS 75225

RADIO WORLD

CENTRAL NEW YORK'S FASTEST
GROWING HAM DEALER



FT-101E



TRITON IV

Featuring — Yaesu, Atlas, Dentron, Ten-Tec, Swan, Regency, Standard, Tempo, KLM, Hy-Gain, Mosley, and Larsen. We service everything we sell! Write or call for quote. YOU WON'T BE DISAPPOINTED.



We are just a few minutes off the
NYS Thruway (1-90) - Exit 32.

RADIO WORLD

ONEIDA COUNTY AIRPORT
TERMINAL BUILDING
ORISKANY, NY 13424
315-337-2622

Warren
K2IXN

Joe
WB2GJR

GREAT VALUES Ham Radio's Back Issue Collector's Items

March 1968 (first issue)

FEATURING: 5-band SSB exciter, IC-regulated power supply, Remotely-tuned 10-meter beam, Transistor curve tracer, Double-balanced mixers.

May 1969

FEATURING: Potpourri of integrated-circuit applications, FM repeater receiver performance, RTTY converter, IC noise blanker, The ionospheric e-layer.

August 1969

FEATURING: Homebrew Parabolic Reflector, Solid-state Q-5er, Frequency calibrator with mos IC's, New multiband quad antenna, Troubleshooting with a scope.

September 1969

FEATURING: FM techniques and practices, IC power supplies, 1296-MHz varactor tripler, Tunable bandpass filters, Amateur microwave standards.

October 1969

FEATURING: Hot Carrier Diodes, Low-cost linear IC's, Diversity antennas, solid-state 432-MHz exciter, Tropospheric-duct communications.

November 1969

FEATURING: Op Amps . . . theory, selection & application, WWV receiver, Multiband antenna, Electronic key, Six-meter collinear.

June 1970

FEATURING: Communication experiments with light emitting diodes, FM modulation standards, Designing phase-shift networks, Transistor frequency multipliers, RTTY frequency-shift meter.

October 1970

FEATURING: An SWR meter for accurate RF power measurements, Direct-conversion receiver, IC voltage regulators, 432 MHz converter, Introduction to thyristors.

December 1970

FEATURING: SSB generator, RF interference, Antenna bridge, QRP transmitter, AFSK oscillator.

June 1971

FEATURING: A practical approach to 432-MHz SSB, FM carrier-operated relay, Audio agc systems, Practical IC's, Low-noise 1296-MHz preamp.

June 1972

FEATURING: 5 Band solid-state communications receiver, FM repeater control, SSTV synch generator, microwave experimenting.

October 1972

FEATURING: 4 channel spectrum analyzer, HF frequency synthesizer, all-band dipole, 160 meter vertical, multi-function IC's.

February 1973

FEATURING: Communications receiver design, rf speech clipper, fm receiver scanner, Plessey SL600 integrated circuits, solid-state noise blanker.

March 1973

FEATURING: Solid-state 80-meter transceiver, reciprocating detector receiver, AFSK generator, electronic keyers, mobile touch-tone.

HAM RADIO BINDERS

Collectors items deserve the best protection you can give them, and we know of no better than our handsome Ham Radio Binders. Bound in washable buckram and supplied with year labels to identify each volume. Each binder holds 12 issues.

**Large Size Only \$5.95 each
3 for \$15.95**

HAM RADIO BOUND VOLUMES

Here is a handsome addition to your library. Twelve issues (a full year) of Ham Radio bound into a rugged, good looking hard cover book. Certainly the most deluxe way to collect Ham Radio and perhaps the only way to acquire some out of print back issues. Years 1972, 1973, 1974, 1975 and 1976 available.

\$19.95 each or All Five \$85.00

June 1973

FEATURING: Digital RTTY autostart, fm repeater installation, micropower receiver, broadband amplifiers, logic oscillators.

July 1973

FEATURING: SSTV test generator, carrier operated relay, VHF receiver, two-meter frequency synthesizer, antenna matching.

December 1973

FEATURING: Two-meter power amplifier, AFSK generator, VHF cavity filter, Bandpass filter design, High-gain wire antenna.

January 1974

FEATURING: CW memory for RTTY identification, Linear amplifier, IC logic families, FM transceiver, Heatsink design.

April 1974

FEATURING: Communications techniques for Oscar 7, Active filter design, Telefax conversion, FM receivers, Wideband amplifier, Antenna radiation patterns.

May 1974

FEATURING: 5th annual antenna issue, Log periodics, Parabolic antennas, Antennas for satellite communications, Ground systems, Antenna measurements.

August 1974

FEATURING: High-power solid-state linear power amplifier, Wind loading on antenna structures, VHF FM scanners, SSB transceivers, Variable-speed RTTY.

February 1975

FEATURING: 2304-MHz power amplifier, Bandpass filter design, Speech processing RTTY terminal unit, GHz frequency scalars.

April 1975

FEATURING: Integrated-circuit electronic keyer, 1296 MHz preamplifiers, Touch-tone encoder, Capacitance meter, Wideband RF amplifier.

June 1975

FEATURING: A phasing-type single-sideband transmitter, Slim-line touch-tone, UHF prescaler, Crystal oscillators, Noise-figure measurements.

July 1975

FEATURING: UHF double-balanced mixers, Tone encoder, Cubical quad antenna, ATV sync generators, 432 MHz converters, Sweepstakes winners.

August 1975

FEATURING: 500 watt power amplifier for 160 meters, FM alignment techniques, Programmable keyer memory, Solid-state 432 MHz linear amplifier, Adjustable IC voltage regulators.

September 1975

FEATURING: Inductively-tuned six-meter kilowatt, RTTY terminal unit, SSB speech splatter, 432 MHz power amplifier, Hand-held touch-tone, VHF mobile antenna.

October 1975

FEATURING: Special receiver issue, Receiver sensitivity and dynamic range, High dynamic range receiver input stages, High-frequency communications receiver, Pre-amplifier for satellite communications, Crystal discriminator.

November 1975

FEATURING: High-performance VHF FM receiver, RTTY line-end indicator, Tunable audio filter, SSTV preamplifier, Binaural CW reception, Master frequency oscillator.

December 1975

FEATURING: S-line frequency synthesizer, Introduction to microprocessors, 1296-MHz bandpass filters, UHF frequency scaler, Cumulative index.

January 1976

FEATURING: 50-MHz frequency counter, microprocessors, wideband linear amplifier, 432-MHz Yagi, audio power ICs.

June 1976

FEATURING: Survey of FM detectors, audio speech processing techniques, SSB linearity meter, receiver troubleshooting and microprocessors.

July 1976

FEATURING: Frequency synthesizer design, WWV receiver, transistor tester, VHF/UHF antenna matching techniques, carrier operated relay.

September 1976

FEATURING: Digital frequency readout, morse keyboard, UHF dummy load, audio frequency-shift keyer, troubleshooting solid-state.

October 1976

FEATURING: High-frequency receiver design, multiband HF converter, microwave amplifier design, two-channel VHF-FM receiver, four-band VHF converter.

November 1976

FEATURING: Low-frequency receiving converter, RTTY test-message generator, crystal-filter design, servicing power supplies.

December 1976

FEATURING: High-frequency communications receiver, loop antennas, broadband mospower amplifier, ASCII-to-Morse code translator, CUMULATIVE INDEX, first issue thru 1976.

ham radio

GREENVILLE, NH 03048

There's no place like a good collection of HAM RADIO back issues to find answers you're looking for. Go over the list above and find the ones you need.

Enclosed is _____ for the items I have checked.

Name _____

Call _____

Address _____

City _____

State _____ Zip _____


- | | | |
|---|---|---|
| <input type="checkbox"/> March 1968 (first issue) | <input type="checkbox"/> May 1969 | <input type="checkbox"/> May 1974 |
| <input type="checkbox"/> August 1969 | <input type="checkbox"/> August 1974 | <input type="checkbox"/> August 1975 |
| <input type="checkbox"/> September 1969 | <input type="checkbox"/> February 1975 | <input type="checkbox"/> April 1975 |
| <input type="checkbox"/> October 1969 | <input type="checkbox"/> June 1975 | <input type="checkbox"/> June 1975 |
| <input type="checkbox"/> November 1969 | <input type="checkbox"/> July 1975 | <input type="checkbox"/> August 1975 |
| <input type="checkbox"/> June 1970 | <input type="checkbox"/> October 1975 | <input type="checkbox"/> September 1975 |
| <input type="checkbox"/> October 1970 | <input type="checkbox"/> November 1975 | <input type="checkbox"/> December 1975 |
| <input type="checkbox"/> December 1970 | <input type="checkbox"/> December 1975 | <input type="checkbox"/> January 1976 |
| <input type="checkbox"/> June 1971 | <input type="checkbox"/> June 1976 | <input type="checkbox"/> June 1976 |
| <input type="checkbox"/> June 1972 | <input type="checkbox"/> July 1976 | <input type="checkbox"/> September 1976 |
| <input type="checkbox"/> October 1972 | <input type="checkbox"/> July 1976 | <input type="checkbox"/> October 1976 |
| <input type="checkbox"/> February 1973 | <input type="checkbox"/> September 1976 | <input type="checkbox"/> November 1976 |
| <input type="checkbox"/> March 1973 | <input type="checkbox"/> October 1976 | <input type="checkbox"/> December 1976 |
| <input type="checkbox"/> June 1973 | <input type="checkbox"/> November 1976 | <input type="checkbox"/> December 1976 |
| <input type="checkbox"/> July 1973 | <input type="checkbox"/> December 1976 | |
| <input type="checkbox"/> December 1973 | | |
| <input type="checkbox"/> January 1974 | | |
| <input type="checkbox"/> April 1974 | | |

**Just \$1.50 each ppd.
3 for \$3.95**

Binders \$5.95 each 3 for \$15.95

Bound Volumes \$19.95 Specify year(s)

NEW — 2027 DUAL ENCODER

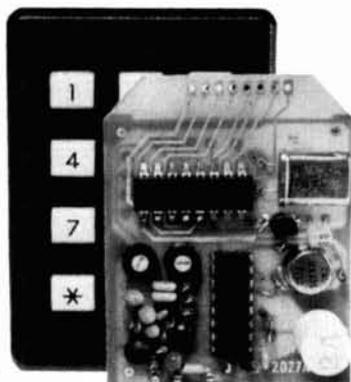

The 2027 dual encoder has both Touch-Tone and Sub-Audible tone on one small board. Simple installation in most radios requires only three connections: ground, plus VDC and tone output. The encoder itself slips over the pins of either a 12-key or 16-key DIGITRAN® keyboard.

The 2027 also offers:


- individual tone level controls
- power by 9-16 VDC, unregulated
- replaceable plug-in tone elements
- EIA tone frequencies from 67.0 Hz to 203.5 Hz. Other EIA frequencies available on special order.
- reverse polarity protected

Priced at:

\$71.96 for 2027A, 12-key keyboard
\$78.95 for 2027B, 16-key keyboard



TG-1A

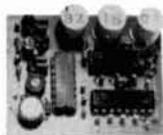

TG-3A

IMPROVED — the TG-1A and TG-3A Both have same features as before, but with improved output and smaller output level control, and, best of all, still the same price.

TG-1A \$24.95 TG-3A \$56.95

Extra tone elements \$3.00 each.

All encoders are wired & tested.

Sizes: TG-1A - 1.0" x 1.2" x 0.6"

TG-3A - 1.6" x 2.0" x 0.6"

COMING SOON —

a CTCSS encoder-decoder

Also, still available, the Trans Com IC-22S Frequency Encoder priced at \$69.95.



ORDER FROM

Trans-Com

P. O. BOX 120
ADDISON, ILL. 60101

Ill. residents add 5% sales tax

UNIVERSAL TOWERS

FREE STANDING
ALUMINUM TOWER

10' to 100'

Prices from
\$128.00 (30')

**MOST
POPULAR**

HAM TOWER

EVER MADE!

REQUEST

NEW CATALOG

OF

TOWERS & ANTENNAS

Communication Specialists

Midwest Ham Headquarters

For Over 38 Years

HAMS! Write For Free Catalog
and Wholesale Prices!

Electronic Distributors, Inc.

1960 Peck Muskegon, MI 49441

Tel: 616-726-3196 TELEX: 22-8411



ALL BAND TRAP ANTENNA!



5 BAND OPERATION - ONLY ONE NEAT SMALL ANTENNA. FOR CONGESTED HOUSING AND APARTMENT DWELLERS!

FOR ALL AMATEUR HF TRANSMITTERS GUARANTEED FOR 1,000 WATTS POWER. LIGHT, NEAT WEATHERPROOF.

Complete as shown total length 102 ft. with 90 ft. of 52 ohm RG58U coax and PL259 connector. Hi-impact molded resonant traps. (wt. 3 oz. 1" x 5" long) You just tune to desired band for excellent report! Excellent for ALL world - wide receivers and amateur transmitters. For NOVICE AND ALL CLASS AMATEURS! NO EXTRA TUNERS OR GADGETS NEEDED! Eliminates 5 separate antennas with excellent performance guaranteed. Can be used as inverted V. NO HAYWIRE HOUSE APPEARANCE! EASY INSTALLATION!

80-40-20-15-10 meter bands. Complete \$34.95
40-20-15-10 meter bands. 54-ft. ant. \$33.95
20-15-10 meter bands. 24-ft. ant. \$32.95
SEND ONLY \$3.00 (cash, ck., mo.) and pay postman balance COD plus postage on arrival or send full price for pp. del. BankAmericard - - - Master Charge - - - Ph 308-236-5333 Free info. available only from. WESTERN ELECTRONICS Dept. AH-8 Kearney, Nebraska, 68847



LOGIC PROBE

from Logic Systems Inc.

Look at This!

- > 2 meg input Z
- Input protection
- Automatic memory
- Use with TTL/DTL/MOS/CMOS
- Detects < 16 nsec pulses
- Assembled and tested

Check or M.O.

L.S.I., Box 7197, Univ. Sta., Provo, Utah 84602

See our HAM MART

listings to find the
Amateur Radio
dealers nearest you.

Bearcat[®] 210 Scanner

\$289.



The Bearcat 210 super synthesized receiver scans and searches 32-50, 146-174 & 416-512 MHz. without expensive crystals. Order now on our 24 hour toll-free credit card order line 800-521-4414. In Michigan and outside the U.S. call 313-994-4441. Add \$5.00 for shipping in U.S. or \$8.00 for air UPS to west coast. Charge cards or money orders only. Foreign orders invited. For additional information, write: Communications Electronics, P.O. Box 1002, Dept. 21, Ann Arbor, Michigan 48106.

COMMUNICATIONS ELECTRONICS
P.O. BOX 1002 DEPT. 24
ANN ARBOR, MICHIGAN 48106



YOUR BEST BUY IN KITS



ANALOG-DIGI-LAB

Features 3 Regulated power Supplies. 3 Output wave forms. 8 digital level switches. 2 no bounce pulser switches. 8 LEDs with drivers. 1 AP Super strip. Easily constructed. Designed by RETS Electronic Schools.

Now only \$139.00

Clock Kit (complete less case) \$12.95
Clock Cabinet \$6.50
or \$4.50 with purchase of clock kit.

Please add \$1.00 Shipping/Handling on any order under \$15.00
Send SASE for flyer. Featuring Electronic components and kits available.

HAL-TRONIX

P. O. Box 1101 • Southgate, Mich. 48195 • (313) 285-1782

FREQUENCY COUNTER

7 Digit 0-300 MHz Freq. Counter \$99.00
7 Digit 0-500 MHz Freq. Counter \$139.00
8 Digit 0-30 MHz Counter with options \$109.00
0-300 MHz Prescaler for 8 Digit Counter \$19.95
0-300 MHz Prescaler with Preamp \$29.95
0-600 MHz Prescaler for 8 Digit Counter \$39.95
Cabinet accessory package available for all of the above \$24.95

Anyone of the above kits available pre-assembled for an additional \$50.00. Allow 3-4 weeks on assembled units.



State
of the art



by
K.V.G.

CRYSTAL FILTERS and DISCRIMINATORS

9.0 MHz FILTERS

XF9-A	2.5 kHz	SSB TX	\$31.95
XF9-B	2.4 kHz	SSB RX/TX	\$45.45
XF9-C	3.75 kHz	AM	\$48.95
XF9-D	5.0 kHz	AM	\$48.95
XF9-E	12.0 kHz	NBFM	\$48.95
XF9-M	0.5 kHz	CW (4 pole)	\$34.25
XF9-NB	0.5 kHz	CW (8 pole)	\$63.95

9.0 MHz CRYSTALS (Hc25/u)

XF900	9000.0 kHz	Carrier	\$4.00
XF901	8998.5 kHz	USB	\$4.00
XF902	9001.5 kHz	LSB	\$4.00
XF903	8999.0 kHz	BFO	\$4.00
F-05	Hc25/u	Socket Chassis	.50
F-06	Hc25/u	Socket P.C. Board	.50

ALSO AVAILABLE FROM KVG

10.7 MHz CRYSTAL FILTERS
OSCILLATOR CRYSTALS 50 kHz TO 150 MHz
Write for Details

VARACTOR TRIPLERS

The low cost, easy way to operate on the 432 MHz and 1296 MHz bands. For OSCAR 7, mode B, drive the MMv432 family varactor tripler with your 2 meter transmitter. The wideband varactor triplers cover the full 2M/432 band without retuning.

NO power supply required for varactor triplers; efficiency approximately 50%.
Three models available at 432, two at 1296.

Model	Max Drive	
MMv432	30 W	\$65.95
MMv432M	50 W	79.95
MMv432H	70 W	115.50
MMv1296	20 W	77.50
MMv1296H	35 W	89.95



shipping: \$2.50

Also available for 144 MHz & 432/440 MHz bands.

Receive Converters: many options. Write for details.

Transverters: Use your 10M rig to get on the VHF bands the easy way. 6M & 2M drive versions available for 432/440 MHz.

Also ch2/ch3 to 438 MHz, fast scan ATV units. At 1296, a full front-end service available. Still the only source with years of experience. Varactor triplers, receive converters and high gain beam.

Send 26¢ (2 stamps) for full line catalogue of KVG crystal products and all your VHF & UHF equipment requirements.

si

Spectrum
International, Inc.
Post Office Box 1084
Concord, Mass. 01742, USA

LINEAR AMPLIFIERS and TRANSVERTERS

by POLAR ELECTRONIC DEVELOPMENTS



EDL144 \$299.95

Drive Power 20 W PEP max
Output Power 100 W PEP max
Rx Pre-Amp Gain 20 dB typ
N.F. 2.5 dB typ
Power Supply 115 V A.C.
Size: 10" x 6" x 7"

The EDL144 amplifier contains a high power transmit linear amplifier (5894 PA) and power supply (115v) together with a low noise receive pre-amplifier (2.5 dB NF). T/R switching is automatic by an internal VOX circuit; no changes are needed to your existing transceiver.

The EDL144 amplifier contains a high power transmit linear amplifier (5894 PA) and power supply (115v) together with a low noise receive pre-amplifier (2.5 dB NF). T/R switching is automatic by an internal VOX circuit; no changes are needed to your existing transceiver.



EDL432P \$299.95

Drive Power 10 W PEP max
Output Power 50 W PEP max
Power Supply 115 V A.C.
Size: 10" x 6" x 11"

The EDL432P amplifier contains a high power triode amplifier (2C39A) with matching power supply (115v). The cabinet also contains the cooling air blower, antenna relays and full metering. The RF section is also available as a complete sub-assembly for use with an existing power supply etc.,

The EDL432P amplifier contains a high power triode amplifier (2C39A) with matching power supply (115v). The cabinet also contains the cooling air blower, antenna relays and full metering. The RF section is also available as a complete sub-assembly for use with an existing power supply etc.,

Model EDL432 \$139.95

Use your 10 meter transceiver with the EDL432P or EDL144-28 transverters to operate on the 6M or 2M bands. These transverters operate in all modes; they have the same style P.A. design as the

EDL144 amplifier. Receiving is with a MMc50 or MMc144 style converter mounted inside the cabinet.

EDT50-28 50-52 MHz
EDT144-28 144-146 MHz
Drive Power, 10M 0.5 W max
Output Power 100 W PEP max
Rx Gain 30 dB typ
N.F. 2.5 dB typ
Size: 10" x 6" x 7"

Price \$299.95
An external power supply is required.



Shipping Via UPS, At Cost.



Model 8XY/2M

\$34.95

Gain 9.5dB in each plane, 50Ω feed.

For OSCAR communications add Circular polarization harness, PMH/2C

\$9.70

Also available for 2 meters:

8 over 8 J-Slot, **Model D8/2M**

\$39.95

8 by 8 vertical J-slot **D8/2M-vert.**

\$48.70

ANTENNAS

144-148 MHz

for
CW AM
FM SSB
OSCAR




420-450 MHz

48 element J-Beam MULTIBEAM

Gain +15.7 dBd. Feed 50Ω coaxial.

Model 70/MBM48 \$47.95

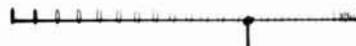

1296 — LY
1296 MHz LOOP-YAGI
GAIN +20dB
FEED 50Ω COAXIAL
\$54.45

1250-1340 MHz

Shipping: Antennas FOB Concord, Mass. via UPS.
Write direct for Polar plots, Gain & VSWR curves.

Plug it in like a key and send perfectly timed Morse code as easily as typing a letter. Sidetone and buffer register make it simple to send at the speed you select.



ATRONICS

BOX 77, ESCONDIDO, CA 92025

(714) 745-1971

Available directly from the factory for only \$225 plus postage & handling. Mastercharge or BankAmericard accepted. Call or write to order or request complete specifications and options.

Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio 234

INDEX	
AGL	558
Adva	265
Advanced Micro	610
Aldelco	347
Aluma Tower	589
Ama. Wholesale Elect.	003
American	554
Apollo	011
Apron	380
Atlas	198
Atronics	382
BK Products	463
Barry	*
Baumán	017
Budwig	233
Bullet	328
CFP	022
Calculator Shop	*
Cleng	465
Comm. Elect.	489
Comm. Spec.	330
Computer Rm	502
Crystal Banking Service	573
Cushcraft	035
DX Engineering	222
Dames Comm.	551
Dames	324
Data Signal	270
Daytronics	612
Dentron	259
Drake	039
E. T. O.	*
Elect. Dist.	044
Electospace	407
Erickson	047
Excel Circuits	535
Genave	168
Gilfer	207
Gray	055
Greene	440
Gregory	201
Hal	057
Hal-Tronix	254
Ham Center	491
Ham Radio	150
Hamtronics	246
Heath	060
Henry	062
Hildreth	283
Hy-Gain	064
Icom	065
Inline Instru.	591
Int. Circuits	518
Int'l Xtal	066
James	333
Jan	067
K-Enterprises	071
KE Electronics	072
KLM	073
Kampp	613
Kenwood	*
Kester Solder	492
Klaus	430
Lafayette	598
Larsen	078
Little Giant	011
Logic Systems	493
Long's	468
Lunar	577
Lyle	373
MFJ	082
MHz	415
Madison	*
Masters	555
NuData	455
Optoelectronics	352
Paraframe	614
Palomar	093
Partridge	439
Pipo	481
Poly Paks	096
Porta Pak	274
RF Power Labs	602
Radio World	592
Ramsey	442
Regency	102
Rohn	410
SST	375
Sabtronics	593
SAROC	*
Savoy	105
Sherwood	435
Space	107
Spectronics	191
Spectrum Int.	108
Swan	111
TPL	240
Tee/Ax	615
Telrex	377
Ten-Tec	*
Trans Com	552
Tri-Ex	116
Utah FM Sales	445
VHF Eng.	121
Valley Instru.	583
Vanguard	*
Varian	043
Webster Comm.	423
Webster Radio	255
Weinschenker	122
Western Elect.	601
Yaesu	127

*Please contact this advertiser directly.

Limit 15 inquiries per request.

August 1977

Please use before September 30, 1977

Tear off and mail to

HAM RADIO MAGAZINE — "check off"
Greenville, N. H. 03048

NAME

CALL


STREET

CITY


STATE ZIP

(213) 834-5868	Long Beach — C&A Electronics
(602) 956-5200	Phoenix — Arden Communications
(602) 939-8356	Glendale — Masters Communications
(213) 843-1647	Burbank — Midnight Radio
(213) 770-3211	Gardena — Advanced Electronics
(209) 224-5111	Fresno — Webster Radio
(408) 998-5900	San Jose — Quement Electronic
(805) 964-5063	Santa Barbara — Pete's Electronics
(805) 643-7789	Ventura — C&C Electronics
(213) 834-5868	Long Beach — C&A Electronics
(415) 763-6262	Oakland — M-Tron
(213) 998-2212	HRO — Van Nuys
(415) 342-5757	HRO — Burlingame
(714) 761-3033	HRO — Anaheim

TROUBLE FREE TOUCH-TONE ENCODER

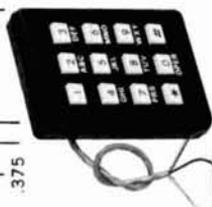

PP-1

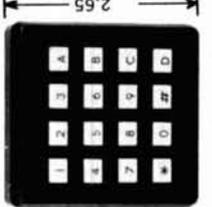

PP-2

POSITIVE TOUCH (KEYS DEPRESS) • MOBILE • HANDHELD DESK MOUNT • NO POTTED PARTS (SERVICEABLE) MIL. SPEC. COMPONENTS • NO RF • SELF CONTAINED XTAL CONTROLLED • LEVEL ADJUSTABLE FROM FRONT Pat. Pend.

NEW Supplied with: Instructions, schematic, template, hardware. Operating Voltage: 4.5 - 60V. PP-1A, designed for Standard Communications Handhelds. (California residents add 6% sales tax.)
NEW PP-1M = \$55.00, PP-2 = \$58.00, PP1A = \$68.00, PP-1M = \$55.00, PP-2M = \$58.00, M series-Mobile
 PP-1K = \$66.00, PP-2K = \$69.00, K-series = Self Contained Delay Relay
 LETTERING OF UNITS OPTIONAL ADD \$1.00

Available at: Ham Radio Center (800) 325-3636
 Denver Colo. CW Electronics (303) 893-5525
 Medford MA, Tufts (617) 395-8280
 Los Angeles, Henry Radio (213) 272-0861
 New York City, Harrison (800) 645-9187

Pipo Communications
 P.O. Box 3435 DEPT. B
 Hollywood, California 90028
 213/852-1515

Advertisers Index

AGL Electronics	103
Adva Electronics	94
Advanced Microcomputer Products	99
Aldelco	102
Aluma Tower Co.	84
Amateur Wholesale Electronics	82, 83
American Wholesale	122
Apollo Products	118
Apron	120
Atlas Radio	74
Atronics	125
BK Products	120
Barry	98
R. H. Bauman	96
Budwig Mfg. Co.	118
Bullet	118
CFP Communications	120
The Calculator Shop	96
Cleng Electronics	122
Communications Electronics	124
Communications Specialists	21, 86
The Computer Room	43
Crystal Banking Service	84
Cushcraft	75
DX Engineering	98
Dames Communications Systems	114
Dames, Ted	112
Data Signal, Inc.	101
Daytronics Company	114
Dentron Radio Co.	7
Drake Co., R. L.	95
Ehrhorn Technological Operations	96
Electronic Distributors	124
Electospace	93
Erickson Communications	84
Excel Circuits	106
General Aviation	119
Gilfer Associates	106
Gray Electronics	104
Greene Insulator	106
Gregory Electronics	94
Hal Communications Corp.	108
Hal-Tronix	124
Ham Radio Center	31, 81
Ham Radio Magazine	73
Hamtronics, Inc.	127
Heath Company	40
Henry Radio Stores	Cover II
Hildreth Engineering	120
Hy-Gain Electronics Corp.	85
Icom	5
Inline Instruments, Inc.	114
Integrated Circuits Unlimited	121
International Crystal	87
James Electronics	104
Jan Crystals	102
K-Enterprises	118
KE Electronics	112
KLM Electronics Inc.	109
Kampp Electronics, Inc.	104
Trio-Kenwood Communications, Inc.	8, 9, 63, 64, 65, 66
Kester Solder	84
Klaus Radio	112
Lafayette Radio Electronics	114
Larsen Antennas	90
Little Giant	96
Logic Systems, Inc.	124
Long's Electronics	128
Lunar Electronics	110
Lyle Products	118
MFJ Enterprises	2
MHz Electronics	115
Madison Electronic Supply	51
Masters Communications	122
NuData Electronics	120
Optoelectronics	107
Paraframe	93
Palomar Engineers	102, 104, 106
Partridge (HR) Electronics	112
Pipo Communications	126
Poly Paks	100
Porta Pak	94
RF Power Labs	92
Radio World	122
Ramsey Electronics	111
Regency Electronics	91
Rohn	93
SST Electronics	120
Sabtronics International, Inc.	53
SAROC	52
Savoy Electronics	39
Sherwood Engineering	122
Space Electronics	122
Spectronics	97
Spectrum International	125
Swan Electronics	46, 47
TPL Communications	51
Tee/Ax, Inc.	122
Telrex Labs	110, 114
Ten-Tec	1
Trans Com	124
Tri-Ex Tower Corp.	89
Utah FM Sales	108
VHF Engineering, Div. of Brownian Valley Instrument Products	113
Vanguard Labs	114, 120
Varian, Eimac Division	Cover IV
Webster Communications	110
Webster Radio	118
Weinschenker	112
Western Electronics	124
Yaesu Electronics Corp.	Cover III

EVER WISH YOUR RECEIVER COULD HEAR THE WEAK ONES?

Almost every amateur and commercial VHF/UHF receiver can be more sensitive with these popular preamps. Over 7000 in use throughout the world!

P8 KIT \$7.95 **P16 W/T 16.95**


Recommended for mounting inside transceivers — only 1/2 x 2-3/8 inches



MODEL	RANGE
P8-30	20-83MHz
P8-150	83-190 MHz
P8-220	220-230 MHz
P16 (W/T)	Give exact freq.

P9 KIT \$9.95 **P14 W/T \$19.95**

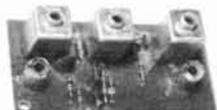Premium model where space permits — 1-1/2 x 3 inches. Ideal for OSCAR!



MODEL	RANGE
P9-30	26-88 MHz
P9-150	88-172 MHz
P9-220	172-230 MHz
P14 (W/T)	Give exact freq.

P15 KIT \$15.95
P35 W/T \$34.95

- Available for any band 380-520 MHz
- 20 dB gain



VHF AND UHF CONVERTERS

- Low noise FET front end
- All common i-f's
- Great for OSCAR!
- Low power drain
- Crystals available for any desired freq scheme



MODEL C25 VHF CONVERTER KIT (shown) \$25.95

- Models for 2M, 6M, 10M, 220 MHz, aircraft, com'l, etc.
- Stable cascode rf stage
- 0.3-0.5 uV sensitivity
- 10-20 dB gain
- Compact 2-1/2 x 4-1/2" pcb
- Any i-f 10-50 MHz
- Featured in HR mag article

MODEL U20-450 UHF CONVERTER \$19.95

- For 432-435 MHz ssb, atv, OSCAR, 450 MHz fm, aircraft, com'l, etc.
- Economy converter
- Use with P15 Preamp for optimum performance
- Any i-f 10-160 MHz

XTAL (either of above) \$5.50

FM/CW TRANSMITTER KITS



200 MW EXCITER MODULE KITS

T40-11 Eleven Channel Exciter for 2M, 6M, or 220 MHz..... \$39.95
T40-1 One Channel Exciter..... 34.95

T20 Tripler/Driver Module Kit, 150 mW 2M input, 200 mW 450 MHz output \$19.95



RF POWER AMPLIFIER MODULES

- NO TUNING
- VSWR PROTECTED
- 150 MW DRIVE
- COMPLETELY STABLE

T80-150, 140-175 MHz, 20-25W output, wired and tested, simply connect your cables..... \$79.95
T80-450, 430-470 MHz, 13-15W 79.95

TEST PROBE KITS



ONLY \$7.95/ea.

- TE-3 RF Detector Probe for VTVM, good from 100 kHz to over 500 MHz
- TE-4 Direct Probe for ac/ohms, etc.
- TE-5 DC Probe w/res for 11 meg input VTVM
- TE-6 Blocking Capacitor Probe for counter, signal generator, etc.
- TE-7 Wideband Detector Probe for scopes
- TE-8 High Z/ Low Capacitance scope probe



Larsen Antennas

We have a large stock of these popular whips. Pick the mount and whip which are right for you! All whips and mounts are interchangeable. Request catalog for more information.

LM-150 5/8 wave 2meter whip..... \$23.85
LM-220 5/8 wave 220 MHz whip... 23.85
LM-440 Colinear 450 MHz whip.... 23.85
Q 1/4 wave whip 144-450 MHz 2.65

MM-LM-K Magnet Mount..... \$14.60
LM-K 3/4" Blind Hole Mount.. 6.35
GC-LM-K Gutter Clip Mount..... 14.60
TLM-LM-K Trunk Lip Mount..... 14.05
AMB-K Trunk Gutter Mount..... 9.10



We have large stock of popular antennas. Call or write for quote or more information.

VHF/UHF FM RCVR KITS



VHF MODELS FOR ANY BAND 28-240 MHz

R60-(), 0.5-1 uV sens, incl VHF Converter and IF/Audio Boards..... \$64.95
R69-(), 0.2-0.4 uV sens, incl P9 Preamp, VHF Converter, and IF/Audio ... \$69.95
Crystals (We stock common freq and will gladly order specials)..... \$5.50



UHF MODELS FOR ANY BAND 380-520 MHz

R60-450, 5-10 uV economy rcvr, incl UHF Conv & IF/Audio Boards only.... \$59.95
R80-450, 2-5 uV sens monitor rcvr, incl UHF Conv, VHF Conv, and IF/Audio . \$84.95
R95-450, 0.4-1 uV sens rcvr, incl P15 Pre-amp, UHF Conv, VHF Conv, and IF-Audio Boards..... \$94.95

FAMOUS ANTENNAS **hy-gain** STOCKED IN DEPTH

REQUEST CATALOG FOR MORE DETAILS

14AVQ	10-40M Vertical	\$67.00
18AVT	10-80M Vertical	97.00
18HT	10-80M Hy-Tower Vert	279.95
TH3-MK3	Tribander	199.95
TH3-JR	Tribander	144.50
TH6-DXX	Tribander, 6 element	249.95
2BDQ	80-40M Trap Dipole	49.95
5BDQ	80-10M Trap Dipole	79.95
263	2M 5/8 wave Trunk Lip	28.95
265	2M 5/8 wave Mag Mt	29.95
214	14 el 2M Beam	26.95



SUPERIOR QUALITY ~ Yet only \$189.95

IF YOU'VE HEARD THE NEW HY-GAIN 2M HT, YOU ALREADY KNOW IT'S FANTASTIC! WE HAVE THEM IN STOCK COMPLETE WITH CRYSTALS AND ACCY'S

Inexpensive DC POWER SUPPLIES

Model	Price	Intermittent	Cont
12CB4	\$29.95	2.5A	1.5A
103R	39.95	4A	2.5A
104R	49.95	6A	4A
108RA	79.95	12A	8A
108RM*	99.95	12A	8A
109R*	149.95	25A	10A

*Indicates model which has panel meter(s)


hamtronics, inc.

182H BELMONT RD., ROCHESTER, NY 14612

- CALL OR WRITE NOW FOR FREE CATALOG OR TO PLACE YOUR ORDER!
- PHONE 716-663-9254, 9AM-9PM EST DAILY.
- Use your credit card or C.O.D.
- Specify operating freq • Add \$1 shipping and handling.

Call 1-800-633-3410 for Dentron*

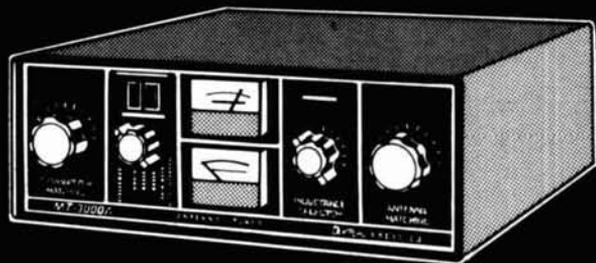*KENWOOD, YAESU, ICOM, CDE, HYGAIN, CUSHCRAFT, NPC, TPL, TRISTAO, NEWTRONICS, REGENCY, ROHN, WILSON, TEN-TEC, B&W, DRAKE, & MFJ.



DENTRON MLA-2500 linear amplifier

- Continuous duty power supply • 160 thru 10 meter coverage • 2000 + watts PEP input on SSB • 1000 watts DC input on CW, RTTY, SSTV • Two external-anode ceramic/metal triodes operating in grounded grid • Covers MARS w/o modifications • 50 ohm input/output impedance • Built-in RF watt meter.

799.50 is list price. Call Toll-Free for quote.

DENTRON MT-3000A antenna tuner

- 160 thru 10 meter coverage • Handles a full 3KW PEP • Continuous tuning 1.8 - 30 mc • Built-in dual watt meters • Built-in 50 ohm dummy load for proper exciter adjustment • Antenna selector switch enables you to by-pass the tuner direct or select the dummy load or 5 other antenna systems.

349.50 is list price. Call Toll-Free for quote.



YAESU FT-101E transceiver

- Solid-state construction • 160 thru 10 meter coverage • Built-in AC & DC power supplies • Built-in RF speech processor • 260 watts PEP, SSB, 180 watts CW & 80 watts AM • Solid-state VFO • Built-in VOX • Auto break-in CW w/sidetone • Built-in WWV/JJY reception • High-Q, permeability tuned, RF stages.

729.00 is list price. Call for quote.




**OVER
50%
OFF!**

ELECTRO-VOICE 719 push-to-talk mike

The 719 has 2 talk switch positions (push-to-talk & grip-to-talk) • Frequency response: 80 to 7000 Hz • Generating element: ceramic • Output impedance: High Z • Polar pattern: omnidirectional.

19.00 List price is 45.00.

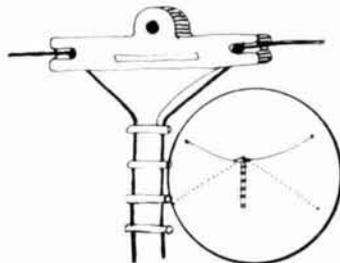

DENTRON all band doublet antenna

This all band doublet or inverted antenna covers 160 thru 10 meters. Has total length of 130 ft. of 14 ga. stranded copper wire. The doublet is tuned & center fed thru 100 ft. of 470 ohm PVC covered transmission line. Assembly is complete.

24.50 is Long's low price.

Remember, you can call TOLL-FREE: **1-800-633-3410** in U.S.A. or call: **1-800-292-8668** in Alabama for our low price quote. Hours: 9:00 a.m. til 5:30 p.m., Monday thru Friday.

AN ENERGY CONSERVATION SUGGESTION FROM YAESU



FT-301S
Analog Dial-20 Watts PEP

OR



FT-301SD
Digital Dial-20 Watts PEP



FL-110 Broadbanded Solid State Linear
200 Watts Output-Power When You Need It

CUT YOUR ELECTRICITY BILL!

Do your part in Uncle Sam's energy conservation program. Obey FCC rules that tell you not to run more power than is needed. But when the going gets tough, switch in the linear!

Yaesu's Deluxe Accessories Complete Your Station



Shown above: Deluxe Power Supply/Speaker/Digital Clock and Programmable CW Identifier
• FT-301SD Transceiver • External VFO • Monitorscope

For a copy of our latest catalog, send your name, address, zip code and ham call sign.

YAESU
The radio.



888

YAESU ELECTRONICS CORP., 15954 Downey Ave., Paramount, CA 90723 (213) 633-4007
YAESU ELECTRONICS CORP., Eastern Service Ctr., 613 Redna Ter., Cincinnati, OH 45215

You've never seen a four tube, 2 megawatt amplifier.



Until Now.

Look at this new generation Continental Electronics 323C medium wave broadcast transmitter. You'll see two EIMAC X-2159 tetrodes are used in each amplifier section, one as a carrier tube and the other as a peak tube. The two Doherty-type screen impedance modulated (SIM) amplifier sections are combined to provide a 2 megawatt carrier, 100 percent modulated.

This is the first of 12 amplifier sections built for three Saudi Arabia locations. They will be used as building blocks for 1 or 2 megawatt transmitters in the

broadcast service. Similar approaches are planned for other locations in Saudi Arabia.

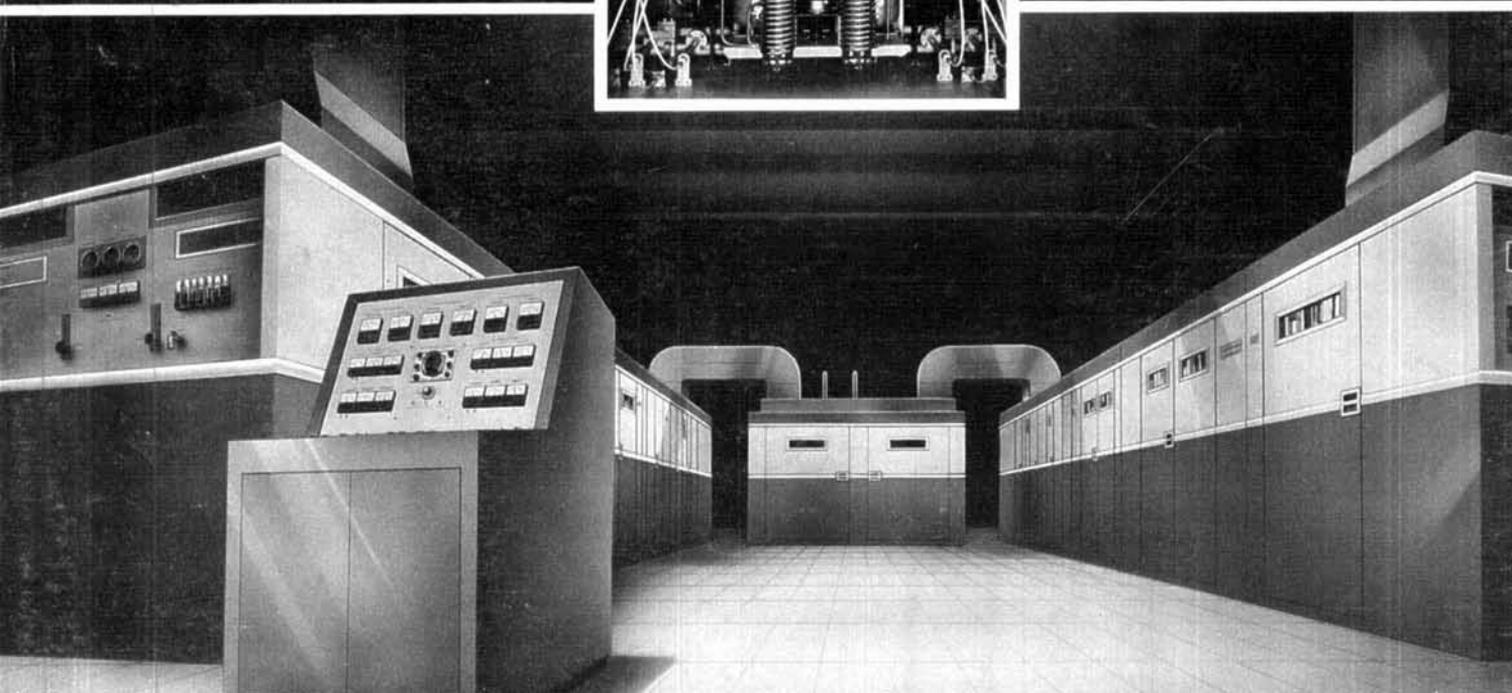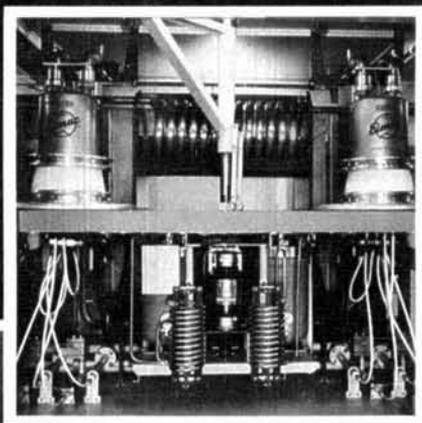For information about power tubes for your transmitter, contact Varian, EIMAC Division, 301 Industrial Way, San Carlos, California 94070. Telephone (415) 592-1221. Or call any of the more than 30 Varian Electron Device Group Sales Offices throughout the world.



Send for your copy of the world's largest catalog of quality kit-form electronic products.



Take your pick of nearly 400 fun-to-build and practical money-saving kits — all backed by Heath — world leader in better electronic kits since 1947.

FREE! mail card now ▶

FREE!

FILL IN THIS
CARD AND
MAIL TODAY

Yes! Please rush me my personal copy of the **NEW Heathkit Catalog.**

I am not on your mailing list.

Name _____

Address _____

City _____

State _____

Zip _____

Dept. 122-32
Ham Radio

PC-124

Get your very own copy of the latest

HEATHKIT

MAIL-ORDER KIT CATALOG

FREE!

Kits for almost everything in electronics; auto and marine accessories, TV, stereo hi-fi, home products and much more. All are easy to build with crystal-clear, step-by-step Heathkit assembly manuals.



SEND FOR IT TODAY!

**PUT STAMP
HERE**

The Post Office
will not deliver
mail without postage

HEATH COMPANY
BENTON HARBOR MI 49022