

Index

3

3cm, getting started on 11.12

A

Abrasives 25.9

ABS 25.5

Absorption wavemeter. 24.13, 24.15

Acetal Copolymer 25.5

Acrylics 25.5

Adhesives 18.25, 25.6

Admittance 14.7

AGC 6.15

Alternating current 1.11

Measurements 24.4

Aluminium 18.25, 25.1

Amateur Television, 10GHz 11.39

Amplifier

435MHz mobile booster. 5.13

Audio 3.21, 5.22

Buffer 4.14

Combining 7.16

DC. 5.22

Feedback in 5.11

FET and MOSFET 5.7, 5.11,

. 6.36

Integrated circuit. 5.9

Intermediate frequency (IF). 5.7, 5.9,

. 6.35

Linear (see Linear amplifier)

Matching. 7.15

MMIC. 5.11

Neutralising 3.30

Operational (op-amps) 3.20, 5.22

Power. 5.9, 5.13

Power for HF 7.11

Power for microwaves. 11.27

Power for VHF/UHF. 9.28

Preamplifiers for LF (see Low Frequencies)

Preamplifiers, microwave 11.21

Preamplifiers, VHF/UHF 5.7, 9.12

. 9.22

Protection 7.15

Radio frequency (RF). 5.9, 6.28

Radio frequency (RF), VHF/UHF 9.13

Solid state versus valve 7.13

Stability. 6.37

Transistor (see Transistor)

Valve. 3.29, 5.16, 7.13

Video. 5.9

Amplitude modulation (see Modulation)

AMTOR 20.7

Analogue to digital

Conversion 1.28

Converter 3.23

Interface 5.40

Antenna bandwidth. 13.4

Antenna cables, routing into house 13.16

Antenna directivity 13.2

Antenna feeders (see Feeders)

Antenna fields, near and far. 13.1

Antenna gain. 1.23, 13.2

Antenna height and propagation 12.10

Antenna insulators 13.13

Antenna masts 13.17

Commercial. 13.18

Counter-weighted fold-over. 13.18

G2XK lightweight fold-over 13.17

Portable 18.13

Wooden 13.20

Antenna matching and tuning 15.12

Balanced ATUs 15.20

Matching a mobile antenna 15.44

Remote controlled 15.14

T-network tuner. 15.15

Transmatch. 15.15

Tuning unit (ATU). 15.12

V-beam 15.40

Versatuner, MFJ 15.19

Vertical beam, phased 15.39

VHF/UHF 16.11

Yagi, HF. 15.33

Z-match 15.22

Antenna modelling / simulation 13.6, 21.3

Antenna polarisation 13.4,

Circular, feed and reversing 16.39

Control of 16.39

Switch, mast-head for 145MHz 16.38

Antenna radiation patterns. 13.2

Antenna resonance. 13.1

Antenna supports (see also Antenna masts)

Chimney 13.16

For microwave dish. 11.14

Trees. 13.20

Wall brackets 13.15

Antenna theory. 1.23

Antenna tubing. 13.11

Antenna wind loading. 13.21

Antenna wire. 13.11

Antennas, constructing beams. 13.14

Antennas for portable. 18.5

Antennas for satellite communication 16.34

Crossed-dipoles 16.34

Eggbeater 16.35

Hairpin 16.35

Quadrifilar helix, or Volute 16.36

Turnstile 16.34

Antennas, HF 15.1

Centre-fed 15.3

Commudipole 15.12

Compact beams 15.38

Delta loop. 15.32

Dipole 1.23, 15.3, 15.12

End-fed 15.1, 15.13

Fixed long wire beams 15.40

G3LDO double-D. 15.39

G5RV. 15.9

G6XN 15.38

Ground plane 15.7

Loop antennas 10.28, 15.24

Marconi. 10.23

Mobile. 15.42

Multi-band 15.8

Off-centre-fed dipole. 15.12

Open wire tuned dipole 15.10

Parallel dipoles. 15.8

Portable 18.5

Quad. 15.35

Rhombic 15.41

Rotary beam. 15.33

Skeleton slot. 15.32

Small loop antennas. 15.31

Using HF wire beam on low bands. 15.3

W6RCA multiband doublet 15.10

Wire loops for low HF bands. 15.27

Antennas, LF (see Low frequencies)

Antennas, microwave. 17.1

Dishes 11.13, 17.13

Helical. 17.1, 17.6

Horn. 17.11

Patch antennas. 17.1

Portable 18.11

Slot 17.1, 17.5

Yagi. 17.1, 17.8

Antennas, VHF/UHF 16.1

Arrays of 16.10

Collinear 16.30

Dipole 16.1

Dipole, gain sleeve 16.27

Dipole, skirted 16.27

Dipole, vertical for portable use. 16.19

Discone. 16.28

Ground-plane, quarter-wave 16.21

GW3YDX Super Moxon 16.9

For a more thorough search, use the CD attached to this book and search for the word or phrase that you want in the pdf version of the *Radio Communication Handbook*.

INDEX

Hand-held and portable 16.18
HB9CV mini-beam. 16.19
Helix, axial mode 16.16
Helix, normal mode. 16.18, 16.21
J antenna 16.31
Log periodic 16.15
Mobile. 16.20
Mounting. 16.14
Omni-directional 16.23
Omni-V for 144MHz 16.23
Portable 18.6
Quad 16.7, 16.13
Repeater, 70cm 16.33
Siting and cabling. 9.2
Stacking 16.14
Whip, dual-band for 144/435MHz
. 16.26
Whip, half and five-eighths-wave . 16.22
Whip, quarter-wave 16.21
Whip, seven-eighths-wave 16.22
Yagi 16.2
Yagi, long. 16.6
Yagi, loop 16.8
Yagi, portable 18.6
Yagi, skeleton slot. 16.12
AppCAD software 11.11
Atmosphere, the Earth's. 12.1
Atoms 1.1, 3.1
Attenuators 5.37, 6.30
Audio stages
 In receiver. 5.26, 6.39
 In transmitter 5.26
Automatic gain control (see AGC)
AX25 (see Packet radio)

B
Balanced circuits 1.20
Balun. 14.11
 Choke 14.13
 Transformer. 14.12, 15.16
 VHF and UHF 14.15
Bandwidth 2.13, 5.1
Batteries 1.4, 23.13
 Charging 18.21, 23.14
 Chemistries. 18.18
 For portable operating 18.18
 Primary 23.13
 Reverse protection 23.15
 Secondary. 23.14, 18.20
Beacon network 12.28
 Data on (see Digital Communications)
Beam tetrode (see Valves)
Bending and forming 25.12
Breakthrough (see Electromagnetic
 compatibility)
Bias
 Circuits 3.11
 Classes of 3.11, 3.29
Block diagrams, using. 5.1
Brass. 18.25, 25.4

C
Cabinets (see Enclosures)
Calibrator, receiver 24.21
Capacitance 1.7
 Formulas A.1
 In AC circuits. 1.13
 Measuring with dip oscillator 24.13
Capacitors, fixed
 Ceramic 2.4, 2.18
 Electrolytic. 2.7
 Glass. 2.7
 Gunn 3.7
 In radio equipment 1.7
 In series and parallel 1.7
 Mica. 2.5, 2.7
 Paper 2.7
 Plastic film 2.7
Capacitors, surface mount
 (see Surface mount)
Capacitors, variable 2.8
Carbon fibre 18.24
Cathode ray tubes. 3.31
Ceramic resonator 2.17
 In oscillators (see Oscillators)
Charge. 1.2
Coaxial connectors 14.7, 18.12
 Connecting to microwave PCBs. 11.4
Coaxial feeder (see Transmission lines)
Coils (See Inductors)
Colour codes (see Components)
Compact disk (CD), info on. 21.5
Compander 5.27
Components. 2.1, 3.1
 Colour codes. A.5
 Measuring. 24.8
 Microwave, modern 11.3
 SMD (see Surface mount)
Compression. 5.1
Computer
 Bluetooth 21.10
 Circuit design by 21.2, 25.20
 Connecting to the real world 21.5
 Controlling your radio by 21.7, 21.11
 CPU 21.1
 DSP (see Digital signal processing)
 EMC 22.12
 Ethernet 21.11
 Inside 21.1
 Internet. 21.4
 For Morse (see Morse)
 Operating system 21.1
 Parallel port 21.10
 PCB design (see PCB)
 Serial port. 21.9
 Software 21.1
 Soundcard 21.6
 (see also SDR)
 Universal Serial Bus (USB) 8, 27, 21.10
Conductance. 1.3
Conductors 1.1

Connectors, coaxial (see Coaxial
 connectors)
Constant current generator 3.13
Construction 25.1
 Design thoughts 25.27
 Of circuits 25.17
 Tips. 25.7
Copper 25.4
Corrosion 25.6
Coupled circuits 1.18, 5.27, 7.1
Crystal
 Buying for oscillator 4.10
 Equivalent circuit 4.11
 Filter (see Filters)
 Oscillator (see Oscillators)
 Quartz 1.17, 2.16
 Temperature coefficient 4.10
 Temperature control 4.10
CTCSS signalling. 5.39
Current flow 1.2
Current measurement. 24.1
Cutting 25.13
CW (see Morse)
Cyanoacrylates 25.6

D
Darlington pair 3.13
Data (see Digital communication)
Decibels 1.30, A.1, 6.1
Demodulation (see Receiver)
Digital communications 20.1
 Error correction. 20.6
 File transfer 20.5
 Fuzzy modes. 20.5
 Keyboard to keyboard. 20.4
 Low bandwidth 20.10
 Modulation 20.1
 On beacons 20.13
 Packet radio (see Packet radio)
 Principles 20.1
 Soundcard-based 20.7
 Specialist modes 20.13
 Wideband modes 20.9
Digital signal processing (DSP). 6.8, 8.41,
 8.42, 21.15
 (see also SDR)
Digital to analogue conversion
 (see Analogue to digital)
Digitising speech. 5.41
Diodes. 3.2
 Germanium. 3.6
 Gunn 11.17
 In power supplies 23.3
 Light emitting (LED) 3.7
 PIN 3.5, 5.15
 Schottky barrier 3.6
 Testing 24.9
 Valve. 3.25
 Varactor. 3.5
 Zener. 3.5

- Dip oscillator 24.14
 Direct conversion receiver (see Receivers)
 Dish antenna (see Antennas, microwave)
 Diversity reception 12.13
 Doping 3.2
 D-Star 9.3
 Dummy load 2.2
 For 136kHz (see Low frequencies)
 Dynamic range 9.8
- E**
- Earth / ground
 Artificial 15.2
 Effect of 13.5
 For 136kHz transmitting (see Low frequencies)
 For EMC 22.2
 On microwave PCBs 11.4
 Real 15.2
 RF 15.2
 Safety (PME) 15.2
 EER (see Low frequency, transmitters)
 Effective aperture of antennas 1.23
 Effective radiated power (ERP) (see Power)
 Electrical units 1.2
 Electromagnetic compatibility (EMC) 22.1
 Electromagnetic spectrum 1.21, 12.4
 Electromagnetic wave 13.1
 Electromagnets (see Magnets)
 Electromotive force (EMF) 1.2, 1.3, 6.1
 EME (see Moonbounce)
 Enclosures 25.8
 Energy 1.2
 Epoxides 25.6
 Etching (see Printed circuit boards)
 EZNEC (see Antenna modelling)
- F**
- Fading (see Propagation)
 Faraday screen 2.11
 Feeders, antenna 1.21, 1.23, 18.12
 (see also Transmission lines)
 Field effect transistor (FET)
 (See Transistor)
 Field programmable gate array (FPGA) 8.23
 Field strength 12.2
 Measurement 10.35
 Meter 5.38, 24.29
 Filing 25.12
 Filters 1.18, 5.27
 Active 5.35, A.16
 Audio 6.37
 Bandpass 5.27, 5.30
 Butterworth A.11
 Ceramic 5.35, 6.27, 7.10
 Chebyshev A.4, A.12
 Crystal 5.32, 6.25, 7.9
 CW 5.36
 Design calculations A.8
 Elliptic A.8
- For EMC 22.6
 High Q types 5.32
 Ideal and real 5.28
 IF 9.16
 LC 5.28
 Low pass 5.12, 5.27
 Mechanical 5.32, 6.27, 7.10
 Microstrip 5.30, A.14
 Notch 5.36
 Roofing 6.24
 Switched capacitor 5.37
 VHF and above 5.30, 18.16
- Flutter (see Propagation)
 Frequency and wavelength 1.22, A.1
 Frequency counter 24.21
 Frequency marker 25.17
 Frequency modulation (see Modulation)
 Frequency standards 11.19, 24.22
 Frequency synthesis 4.14
 Analogue 4.14
 Direct digital synthesis (DDS) 4.17
 Huff and puff stabiliser 4.16
 Partial 6.22
 Phase-locked loop (PLL) 4.15
 FSK 20.11
- G**
- Gain 5.1
 Gain compression 9.8
 Galvanic series 25.4
 Gamma match (see Matching)
 Generators, mechanical 1.5
 Germanium diode (see Diodes)
 Glass fibre 18.25
 Ground (see Earth)
 Ground waves 12.3, 12.8, 12.10
 Gunn diode (see Diodes)
- H**
- HAM-DRM (see DRM)
 Harmonics 1.12
 Distortion 5.1
 Headphones 2.15, 18.16
 Heatshrink 18.26
 Heatsinks 25.15
 For power amplifiers 7.16
 Hole making 25.11
- I**
- Impedance 1.14, 5.1, A.2
 Antenna feed 13.2
 Bridge 24.9
 Characteristic 14.1, A.1
 Measurements 24.9
 Transformation in antennas 14.2
 Inductance
 In AC circuits 1.13
 Measuring with dip oscillator 24.14
 Mutual 1.10
 Self 1.10
- Inductors 2.9
 Chokes 2.10
 Energy storage 2.10
 In series and parallel 1.10, A.2
 Pot cored A.3
 Surface mount (see Surface mount)
 Winding A.3
 Infrared communication 11.65
 Insulation 2.1
 Insulators 1.1
 Antenna (see Antenna insulators)
 Materials 2.13
 Integrated circuits
 Digital 3.21
 In receivers 6.24
 Linear 3.19
 RF power (see also Amplifiers) 5.13
 Interference
 (see Electromagnetic compatibility)
 Intermediate frequency (IF)
 Amplifier (see Amplifiers)
 Choice of 6.20, 9.10
 Intermodulation 1.28, 5.1, 6.13, 9.7, 24.36
 Internet 21.4
 (see also the references section at the end of most chapters)
 Access and EMC 22.8, 22.12
 Ionosphere 12.1, 12.15
 Wave propagation in 12.6
 Ionospheric
 Disturbances 12.21
 Ionisation, irregular 12.17
 Layers 12.16
 Predictions 12.25
 Waves 12.3
 Isolation 5.1
 Isotropic radiator 1.23
- J**
- Jason 20.10
 JT65 20.11
 Junction FET (JFET)
 (See Transistors)
- K**
- Key click filter 1.11
 Keys, Morse (see Morse)
- L**
- Laminates 25.4
 Laser DXing (see Optical Comms)
 Light emitting diodes (see diodes)
 Lightning protection for antennas 13.21
 Linear amplifier
 100W HF 5.13
 50MHz 5.13
 Choosing 7.39
 Constructing 7.40
 Grounded-grid, 200W HF 5.19
 Interfacing to exciter 7.44

INDEX

Medium/high power solid state HF 7.39
 Passive grid, 400W HF 5.21
 SWR protection 7.43
 VHF, double-tetrode 5.19
 VHF/UHF power modules 5.13
 Locators 12.24
 Logbook for portable operation 18.16
 Long-tailed pair 3.14
 Low frequencies (below 1MHz) 10.1
 Amateur receivers and transceivers,
 using 10.2
 Antennas for receiving 10.3, 10.29
 Antennas for transmitting . 10.21, 10.23,
 10.28
 Antenna voltage and safety 10.25
 Commercial equipment 10.2
 Converters 10.5
 Digital modes (see Digital comms)
 Drive sources for transmitters 10.19
 Estimating ERP 10.23
 Ground systems 10.25
 Interference reduction 10.28
 Licensing on 500kHz 10.1
 Loading coils 10.27, 15.5
 Matching loop antennas 10.22
 Matching vertical antennas 10.26
 Measurement & instrumentation. 10.35
 Oscillators 10.19
 Receivers (see also SDR) 10.1
 Receiver preamplifier 10.4
 Transmitters 10.6
 Transverter, EER 10.14
 Very low frequencies (3-30kHz) 10.38

M

Magnetic fields, interaction of 1.9
 Magnetic materials 2.9, 2.14
 Magnetism 1.8
 Magnetosphere, the Earth's. 12.15, 12.20
 Magnets
 Electromagnets 1.9
 Permanent 1.8
 Magnification factor (see Q)
 Map projections 12.23
 Matching
 Antennas 14.15
 Gamma match 14.16
 LF antennas (see Low Frequencies)
 Omega match 14.17
 Using LC circuits 5.32
 Materials for portable operating. 18.24
 Maximum power transfer 1.3
 Measurement (see Test and measurement)
 Memory 3.22
 MEMS resonator 2.17
 Metals 18.25, 25.3
 Metalworking 25.2
 Meters
 Analogue 24.1
 Digital 5.42, 24.5

MFSK 20.8
 Microphones 2.15
 Microprocessor 3.23, 21.11
 PIC 5.42, 21.13
 Microstrip (see Filters)
 Microwave amateur allocations 11.2
 Microwave antennas (see Antennas,
 microwave)
 Mixer 5.2
 Balanced 5.2, 7.5
 Diode 5.3
 'H' mode 6.48
 In receivers 6.31
 JFET 5.3, 5.6
 MOSFET 5.5, 9.15
 Practical circuits 5.3
 Products 5.2
 Ring 5.3, 6.48
 Semiconductor 5.4
 VHF/UHF 9.13
 MMIC (see also Amplifiers)
 For microwave use 11.5
 Modulation (see also Receivers) 1.24
 Amplitude (AM) 1.24, 11.54
 Digital 1.26
 Frequency (FM) 1.25, 9.16, 11.57
 Phase modulation (PM) 1.26
 Single sideband (see SSB)
 Techniques 7.5
 Modulators (see Mixers)
 Molecules 1.1
 Moonbounce, equipment for 17.14
 Morse 19.1
 Advantages of 19.1
 Break-in (QSK) 7.21
 Computers and 19.10
 High speed (QRQ) 19.9
 History of 19.1
 Keyer 19.7
 Keys 18.15, 19.5
 Learning 19.3
 Practice 19.4
 QRSS and DFCW 19.9
 Readers 19.4
 Transmission and reception 19.8

MOSFETs (See Transistor)
 MT63 20.9

N

Neutralising (see Amplifiers)
 Nickel silver 25.6
 Noise 5.1, 23.9
 VHF/UHF 9.2, 9.12
 Noise bridge 24.10
 Noise factor/Noise figure 6.10, 9.7,
 24.35
 Noise limiter/blanker 6.38
 Null steerer 6.38
 (see also LF, Interference reduction)
 Nylon 25.5

O

Ohm's Law 1.3, A.2
 Olivia 20.8
 Op-amps (see Amplifiers)
 Optical communication 11.54
 Oscillator 4.1
 Audio 21.13
 Basic requirements 4.1
 Buffer (see Amplifier)
 Building 4.6
 Butler 4.11
 Ceramic resonator 4.11
 Clapp 4.2, 4.4, 4.7
 CMOS 4.10
 Colpitts 4.2, 4.4, 4.7, 4.9
 Components 4.6
 Crystal 4.9
 Effect on receiver performance 4.2
 Evaluation of 4.8
 Franklin 4.4
 Gouriet-Clapp 4.7
 Gunn diode 11.15
 Hartley 4.2, 4.4, 4.5
 'Huff and puff'
 (see Frequency synthesis)
 Local, microwave 11.17
 Low frequency sinewave 24.16
 Multiplier 4.12
 Noise 6.16
 Overtone 4.9
 Pierce 4.9, 4.11
 Practical 4.4
 SDR, for (see SDR)
 Synthesised (see Frequency synthesis)
 Vackar 4.8
 Variable crystal (VXO) 4.11, 6.23
 Variable frequency (VFO) 4.2, 4.7
 VHF 4.13
 Voltage controlled 4.8
 Oscilloscope 24.7
 Measuring with 24.8
 Tubes 3.31
 Overload 5.1, 5.38

P

Packet radio 20.14
 Painting enclosures 25.9
 Passive components (see Components)
 Passive intermodulation products 22.3
 Patch antennas (see Antennas, microwave)
 Path profiles, plotting 12.25
 PCB (see Printed circuit boards)
 Pentode (see Valves)
 Perspex (see Acrylics)
 Phase 1.12
 Phase modulation (see Modulation)
 Phase shift network 7.7
 PIC chip (See Microcomputers)
 Piezo-electric effect 1.17, 2.15
 PIN diodes (see Diodes)

- PIN junction 3.2
 Plastics 25.4
 Polar diagrams (see Antenna radiation)
 Polycarbonate 25.3
 Polyethylene 25.5
 Polypropylene 25.5
 Polystyrene 25.5
 Portable 18.1
 Potential difference (PD) 1.3, 61
 Power 1.2, 1.5, A.2
 Batteries (see Batteries)
 Consumption 5.1
 Effective radiated 1.23, 10.17
 For portable operating 18.18
 Meter 5.23
 Output measurement 24.23
 Solar 18.23, 23.16
 Power amplifiers (see Amplifiers)
 Power supplies 23.1
 Choice of components 23.6
 Constant current 23.10
 Dual voltage 23.7
 For op-amps 5.23
 From mains supply 23.1
 Over-voltage protection 23.10
 Renewable energy 23.15
 Soft starting 23.5
 Switch mode 23.10
 Voltage regulators 3.21, 5.37, 23.7
 Preamplifiers, (see Amplifiers)
 Preferred values 2.3
 Primary cells 1.4
 Principles 1.1
 Printed circuit boards (PCB)
 As structural material 6.43
 Designing 25.20
 Manufacture 25.19
 Materials for microwave use 11.3
 Propagation 12.1
 Books on 12.28
 Effect of height 12.10
 Forecasts 12.28
 Free space 12.4
 Fresnel zones 12.12
 Grey line 12.26
 Internet sites about 12.28
 Modes of 12.3
 Multi-path, flutter & fading 12.9, 12.12
 Via Moon (see Moonbounce)
 Protective Multiple Earthing 15.2, 22.3
 Prototype boards 25.17
 PSK31 20.8
 PSK, decoding 20.2
 PTFE 25.5
 PVC 25.5
- Q**
 Q the magnification factor 1.15, A.2
 QRSS (see Morse)
 Quartz crystals (see Crystals)
- R**
 Radiation, electromagnetic 12.2
 Radiation resistance 1.23, 13.2
 Reactance (see also Impedance)
 A.2, A.6, A.7
 Receiver 6.1
 Active devices for 6.23
 AGC (see AGC)
 Audio stages (see Audio)
 Basic requirements 6.2
 Basic types of 6.2
 Blocking 6.13
 Building 6.42
 Cross modulation 6.13
 Demodulation (detection) 5.25, 6.37
 (see also SDR)
 Design trends 6.6
 Digital techniques 6.7
 Direct conversion 6.3, 6.45, 8.4, 9.37
 DSP (see Digital signal processing)
 Filters (see filters)
 For 136/500kHz (see Low frequencies)
 For FM 9.16
 Frequency stability (see also Oscillator)
 6.18, 6.20
 Gain distribution 6.20
 HF 6.3
 IF (see Intermediate frequency)
 Input circuits 6.28, 6.46, 6.44
 Intermodulation (see Intermodulation)
 Laser 11.54
 Measurement 24.34
 Mixers (see Mixers)
 Modifications to 6.40
 Multiconversion 6.22
 Noise (see Noise factor/figure)
 Performance, microwave 11.9
 Performance, specifying 6.19
 Polyphase, experimental 6.52
 Protection 6.28
 Reciprocal mixing 6.16
 Regenerative 6.2, 6.44
 Selectivity (see Selectivity)
 Sensitivity 6.10
 Software defined (See SDR)
 Specification 6.10
 Spurious responses 6.18
 Strong signal performance 6.13
 Superhet 6.3
 Third method 6.3
 TRF 6.2, 6.43
 Two-phase 6.3
 VHF/UHF, design 9.6, 9.10
 VHF/UHF front end 9.8
 Yearling, the 6.49
 Reciprocal mixing 9.8, 24.36
 Rectifiers 3.4, 23.1
 Relays 2.14
 For microwave antenna 11.12
 Reliability
 Of components 2.1
 Of portable equipment 18.1
 Resistance
 Dynamic 1.16, A.1
 In AC circuit 1.13
 Resistivity of metals 2.1
 Resistors
 Fixed 2.2
 In radio equipment 1.5
 In series and parallel 1.6, A.2
 Non-linear 2.3
 Surface mount (see Surface mount)
 Variable 2.3
 Resonance 1.14, A.2, A.6, A.7
 Antenna (see Antenna resonance)
 RF clipping (see Speech processing)
 RF measurements 24.4, 24.7, 24.32
 (see also Low frequencies)
 RF switching 5.13
 RMS values 1.12
 Ropes 13.14, 18.25
 ROS 20.9
 RTTY 20.7
- S**
 Safe operating area 3.11
 Safety 11.55, 18.2, 23.1, 23.15,
 25.3, 25.30
 Sampling, RF 24.20
 Satellite
 Antennas for (see Antennas)
 Power amplifier for AO-40 11.27
 Schottky diode (see Diodes)
 Scrapyards as source of hardware 13.13
 Screening 1.19
 SDR (Software Defined Radio) 6.5, 8.1
 Alexaires filters 8.14, 8.38
 AM demodulation 8.20
 Atlas backplane 8.12, 8.28
 Bandscope 8.1, 8.8, 8.17
 Budget kit 8.50
 Communicating with the PC 8.25
 Consoles 8.9
 CW demodulation 8.21
 Digital down conversion 8.3, 8.6,
 8.29, 8.31
 Digital up conversion 7.17, 8.37
 DSP (see Digital signal processing)
 For low frequencies 10.3, 10.6
 Hardware 8.8
 High Performance (HPDSR) Project 8.12
 I and Q signals 8.6, 8.19
 Janus board 8.13, 8.25
 Local oscillators for 8.16, 8.52
 Mercury receiver 8.14, 8.31
 Ozymandias 8.13, 8.27
 Penelope exciter 8.14
 Phase and frequency modulation 8.22
 Quadrature switching detector 8.2, 8.6
 Software 8.6, 8.7

INDEX

- SSB demodulation 8.21
- VHF/UHF/Microwave 8.15
 - Without a radio 8.4
- Sealants 18.25
- Secondary cells. 1.4
- Selectivity 1.16
- Self amalgamating tapes 25.6
- Semiconductors. 1.19, 3.1
- Shaft encoder. 5.38
- Shannon limit 1.27
- Signal source, VHF/UHF 24.18
- Silicon 3.1
- Silicone rubber compounds 25.6
- SINAD, definition of. 6.8
- Single sideband (see SSB)
- Skin effect. 1.17
- Slow scan TV (SSTV) (see Amateur television)
- Smith chart 14.4, 14.18
- Smoothing (in PSUs). 23.3
- Software
 - Antenna modelling (see Antenna modelling)
 - Circuit design. 17.1
 - Defined Radio (see SDR)
- Solar effects on propagation 12.13
- Soldering and desoldering 25.13
 - Surface mount components. 25.25
- Soundcard (see Computer)
- Sounders. 2.14
- Source resistance 1.3
- Spectrum analyser 24.22
- Speech processing. 5.27
- Spurious emissions 22.8
- SSB 1.25, 7.6
 - Filter method 7.7
 - Phasing method 7.6
 - Over optical 11.59
- Standing wave ratio (SWR) 14.1, 14.2
 - Meter 24.24
- Standing waves. 13.1
- Static precautions. 11.3
- Steels 18.25, 25.4
- Stepper motors. 5.38
- Sunspots (see Solar effects)
- Surface mount 2.2, 2.17, 3.24
 - Capacitors. 2.18
 - Component markings 2.20
 - Connectors 2.19
 - Construction using 25.25
 - For microwave use 11.4
 - Inductors and ferrites 2.18
 - Resistors 2.16
- T**
- Television, amateur (see Amateur television)
- Television, breakthrough to 22.5
- Test and measurement. 24.1
 - of receivers. 6.42
 - Using a computer 21.3, 24.34
- Tetrode (see Valves)
- Throb. 20.8
- Thyristor 3.18
- Time constant 1.10, A.2
- Tin plate 25.4
- Titanium 18.25
- Tools
 - And instrumentation. 25.1
 - Useful, homemade 25.10
- Transceiver 7.19
 - Choosing a commercial HF. 7.45
 - Evolution of. 7.45
 - QRP HF 7.24, 18.17
 - VHF - for SHF 9.39
- Transformer 1.18, 2.11
 - Auto 1.19, 2.12
 - Ratios A.2
- Transistor 3.8
 - Amplifier 3.9
 - As a switch 3.13
 - Bipolar. 3.8, 6.21
 - Configurations 3.12
 - Field effect (FET). 3.14, 6.23
 - GaAsFETs 3.15, 11.35
 - Junction Field Effect (JFET). 3.14
 - Transistor testing 24.8
 - MOSFET 3.15
 - VMOS 3.17
- Transmission lines 14.1
 - Coaxial cable 11.14, 14.3, A.3
 - Coaxial cable, splicing 14.10
 - Construction 14.3
 - Losses in. 14.2
 - Twin feeders 14.3
- Transmitters
 - Audio upconverter. 7.17
 - Class D 10.7
 - Class E 10.10
 - For 136 & 500kHz (see Low Frequencies)
 - For ATV (see Amateur television)
 - HF. 7.1, 7.21
 - Laser. 11.56
 - Measurements 24.37
 - Microwave. 11.1
 - Software defined (see SDR)
 - VHF/UHF 9.1
- Transverter
 - For HF 7.21
 - For microwaves 11.12, 11.44, 18.17
 - For optical comms 11.59
 - For VHF/UHF. 9.51
 - VHF, driving. 5.39
- Triac (see Thyristor)
- Triode (see Valves)
- Tropospheric
 - Processes 12.21
 - Waves 12.3, 12.7
- Tubes, electronic (see Valves)
- Tuneable toroid. 2.10
- Tuned circuits 2.9
 - VHF/UHF 9.11
- U**
- Unbalanced circuits 1.20
- V**
- Valves 3.24
 - Amplification factor. 3.28
 - Anode tank circuits 7.3
 - Applications 3.29
 - Characteristics 3.28
 - Construction 3.27
 - Diode (see Diode)
 - Disc seal. 3.30
 - Electrode dissipation 3.28
 - Impedance 3.28
 - Mutual conductance. 3.28
 - Pentode 3.26
 - Power amplifier (see Amplifiers)
 - Receiving 6.23
 - Tetrode 3.26
 - Triode 3.25
- Varactor diodes (see diodes)
- Variable frequency oscillator
 - (see Oscillators)
- Variac 2.12
- Variometer. 2.9, 10.28
- Velocity factor 14.1
- VFO (see Oscillators)
- VHF/UHF receivers, transmitters and transceivers 9.1
- VHF/UHF, books and magazines 9.46
- VHF/UHF station, getting the best out of 9.1
- Voice record-playback device 5.27
- Voltage measurement 24.1, 24.8
- Voltage multiplier 23.3
- Voltage regulator (see Power supplies)
- VSWR (see Standing wave ratio)
- W**
- Wadley loop 6.23
- Walking equipment. 18.2
- Wavelength (see Frequency)
- Wideband activity on 10GHz 11.15
- Wind loading (see Antenna wind loading)
- Wire 2.1
 - Gauge A.3
- WOLF. 20.10
- Wood. 25.6
- Workshop practice 25.1
- WSJT. 20.11
- WSPR 20.12
- Y**
- Yagi antenna (see Antennas, VHF/UHF and Antennas, microwave)
- Z**
- Zener diodes (see diodes)

